

EECS150 - Digital Design

Lecture 3 - Field Programmable Gate Arrays (FPGAs)

January 25, 2010


John Wawrzynek

Spring 2011

EECS150 - Lec03-FPGA


Page 1

Project platform: Xilinx ML505-110

 

FPGA Overview

 - Basic idea: two-dimensional array of logic blocks and flip-flops with a means for the user to configure (program):
 1. the interconnection between the logic blocks,
 2. the function of each block.



Simplified version of FPGA internal architecture:

Why are FPGAs Interesting?

- Technical viewpoint:
 - For hardware/system-designers, like ASICs only better! “Tape-out” new design every few minutes/hours.
 - Does the “reconfigurability” or “reprogrammability” offer other advantages over fixed logic?
 - Dynamic reconfiguration? In-field reprogramming? Self-modifying hardware, evolvable hardware?

Why are FPGAs Interesting?


- Staggering logic capacity growth (10000x):

Year Introduced	Device	Logic Cells	“logic gate equivalents”
1985	XC2064	128	1024
2011	XC7V2000T	1,954,560	15,636,480

- FPGAs have tracked Moore’s Law better than any other programmable device.

Why are FPGAs Interesting?

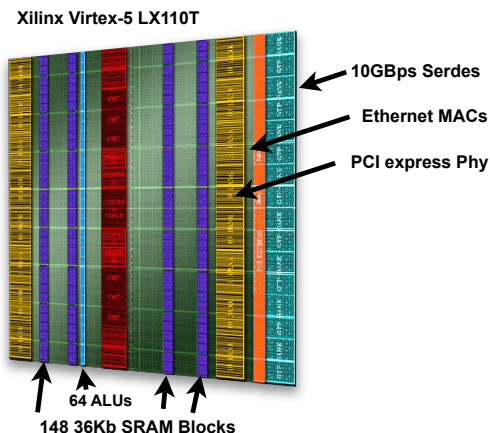
- Logic capacity now only part of the story: on-chip RAM, high-speed I/Os, “hard” function blocks, ...
- Modern FPGAs are “reconfigurable systems”



But, the heterogeneity erodes the “purity” argument. Mapping is more difficult. Introduces uncertainty in efficiency of solution.

Why are FPGAs Interesting?

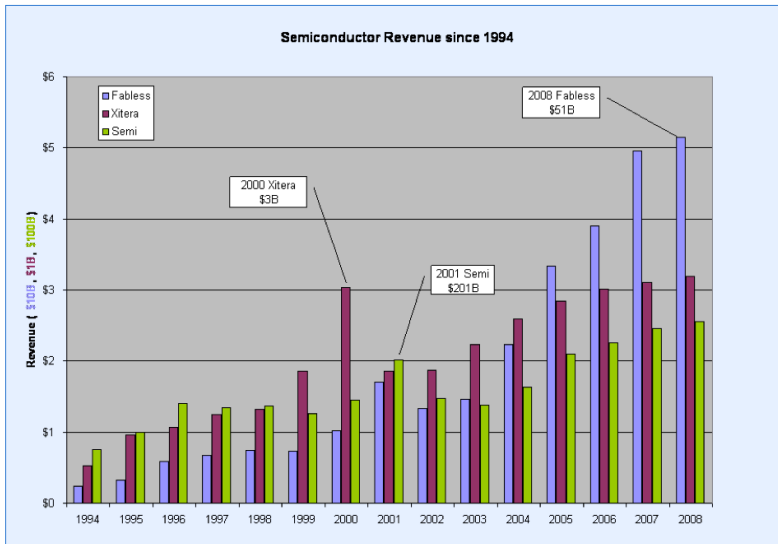- Have been an archetype for the semiconductor industry as a whole:



from: mattrhodes.net

Putting the FPGA Business in Perspective. How large is it compared to others?

	Q3 2009	Q4 2009	Q/Q Growth	Q1 2010 (Guidance)
<i>Broadcom</i>	\$1,194,745	\$1,283,434	7.4%	Up 0 to 5%
<i>Marvell</i>	\$803,098	<TBD>		
<i>Nvidia</i>	\$903,206	\$982,500	8.8%	Flat
<i>Xilinx</i>	\$414,950	\$513,300	23.7%	down 1% to up 3%
<i>Altera</i>	\$286,612	\$365,000	27.3%	up 5 - 10%
<i>TI</i>	\$2,880,000	\$3,005,000	4.3%	down 2% - up 6%
<i>INTEL</i>	\$9,389,000	\$10,600,000	12.9%	down 5-10%
<i>AMD</i>	\$1,396,000	\$1,646,000	17.9%	down "seasonally"
<i>Qualcomm</i>	\$1,699,000	\$1,608,000	-5.4%	Flat
<i>Atheros</i>	\$156,641	\$185,700	18.6%	up 5%
<i>Silicon Labs</i>	\$125,913	\$127,200	1.0%	Flat to down 5%
Average			5.5%	

from: mattrhodes.net

Why are FPGAs Interesting?

- Have attracted an huge amount of investment for new ventures:
 - Most startups have failed. Why?
 - Business dominated by Xilinx and Altera

Worldwide FPGA/PLD vendor revenues and rankings, 2007-2008

Rank 2007	Rank 2008	Company	Revenue (\$M) 2007	Revenue (\$M) 2008	Revenue Change 2007-2008	Market Share 2008
1	1	Xilinx	1,809	1,906	5.4%	51.2%
2	2	Altera	1,216	1,323	8.8%	35.5%
3	3	Lattice Semiconductor	229	222	-3.1%	6.0
4	4	Actel	196	218	11.2%	5.9%
6	5	QuickLogic	28	23	-17.9%	0.6%
5	6	Cypress Semiconductor	32	21	-34.4%	0.6%
7	7	Atmel	14	9	-35.7%	0.2%
8	8	Chengdu Sino Microelectronics System	4	3	-25.0%	0.1%
		Others	0	0	NM	0.0%
		Total Market	3,528	3,725	5.6%	100.0%

Source: Gartner


Why are FPGAs Interesting?

- FPGAs at the leading edge of IC processing:
 - Xilinx V7 out next year with 28nm TSMC processing
 - Foundries like FPGAs - regularity help get process up the “learning curve”
 - High-volume commitment gets interest of foundry
 - (Gives FPGAs a competitive edge over ASICs, which usually are built on an older process.)

Why are FPGAs Interesting?

- FPGAs have been wildly successful even though they are inefficient in silicon area, energy, and performance :
 - “Measuring the Gap Between FPGAs and ASICs”, Ian Kuon and Jonathan Rose, FPGA'06
 - Versus ASICs: area 40X, delay 3-4X, power 12X
- How can this be? Is there something more important than silicon efficiency?

Die Photos: Virtex FPGA vs. Pentium IV

 

- FPGA Vertex chip looks remarkably structured
 - Very dense, very regular structure
- “Full-Custom” Pentium chip somewhat more random in structure
 - Large on-chip memories [caches] are visible



FPGAs are in widespread use

Far more designs are implemented in FPGA than in custom chips.



Fall 2010


CS 294

  


FPGA Variations

- Families of FPGA's differ in:
 - physical means of implementing user programmability,
 - arrangement of interconnection wires, and
 - the basic functionality of the logic blocks.
- Most significant difference is in the method for providing flexible blocks and connections:

- Anti-fuse based (ex: Actel)

 

 - + Non-volatile, relatively small
- fixed (non-reprogrammable)



- Several "floating gate" or eeprom style approaches have been used. One now by Actel.


Fall 2010

CS 294 - Lec01 Intro

Page 14

FPGA Variations

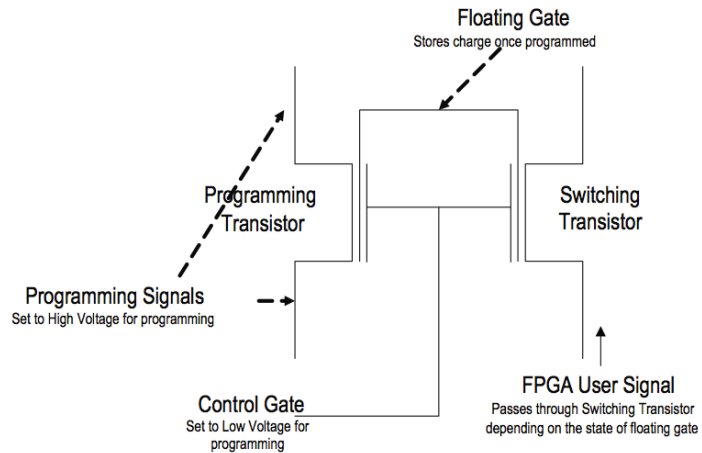
- “Floating-gate” / EPROM / FLASH based (ex: Actel, others)



- + Non-volatile
- + reprogrammable
- larger size than anti-fuse
- requires special process

User Programmability

- Latch-based (Xilinx, Altera, ...)

 


- + reconfigurable
- volatile
- relatively large.

- Latches are used to:
 1. control a switch to make or break cross-point connections in the interconnect
 2. define the function of the logic blocks
 3. set user options:
 - within the logic blocks
 - in the input/output blocks
 - global reset/clock
- “Configuration bit stream” is loaded under user control


Background (review) for upcoming

 - A MUX or multiplexor is a combinational logic circuit that chooses between 2^N inputs under the control of N control signals.




- A latch is a 1-bit memory (similar to a flip-flop).

Idealized FPGA Logic Block

 

- 4-input look up table (LUT)
 - implements combinational logic functions
- Register
 - optionally stores output of LUT

4-LUT Implementation

 

- n-bit LUT is implemented as a $2^n \times 1$ memory:
 - inputs choose one of 2^n memory locations.
 - memory locations (latches) are normally loaded with values from user's configuration bit stream.
 - Inputs to mux control are the CLB inputs.
- Result is a general purpose "logic gate".
- n-LUT can implement any function of n inputs!

LUT as general logic gate

- An n-lut as a direct implementation of a function **truth-table**.
- Each latch location holds the value of the function corresponding to one input combination.

Example: 2-lut

INPUTS	AND	OR
00	0	0
01	0	1
10	0	1
11	1	1

Implements *any* function of 2 inputs.


How many of these are there?

How many functions of n inputs?

Example: 4-lut

INPUTS	
0000	F(0,0,0,0) ← store in 1st latch
0001	F(0,0,0,1) ← store in 2nd latch
0010	F(0,0,1,0) ←
0011	F(0,0,1,1) ←
0011	
0100	•
0101	•
0110	•
0111	
1000	
1001	
1010	
1011	
1100	
1101	
1110	
1111	


FPGA Generic Design Flow

 

- Design Entry:
 - Create your design files using:
 - schematic editor or
 - HDL (hardware description languages: Verilog, VHDL)
- Design Implementation:
 - Logic synthesis (in case of using HDL entry) followed by,
 - Partition, place, and route to create configuration bit-stream file
- Design verification:
 - Optionally use simulator to check function,
 - Load design onto FPGA device (cable connects PC to development board), optional "logic scope" on FPGA
 - check operation at full speed in real environment.


Example Partition, Placement, and Route

- Idealized FPGA structure:

 

- Example Circuit:

- collection of gates and flip-flops

 

Circuit combinational logic must be "covered" by 4-input 1-output LUTs.


Flip-flops from circuit must map to FPGA flip-flops.

(Best to preserve "closeness" to CL to minimize wiring.)

Best placement in general attempts to minimize wiring.

Vdd, GND, clock, and global resets are all "prewired".


Example Partition, Placement, and Route

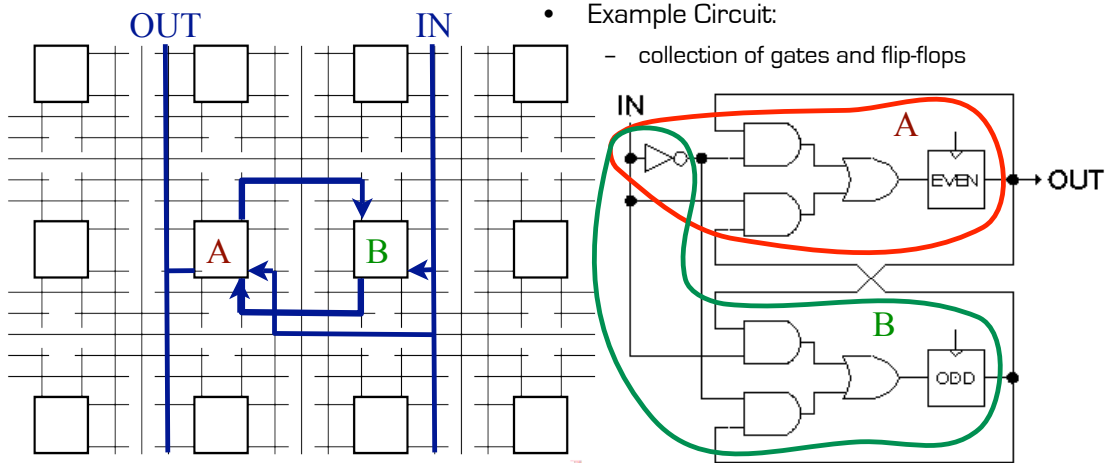


Two partitions. Each has single output, no more than 4 inputs, and no more than 1 flip-flop. In this case, inverter goes in both partitions.

Note: the partition can be arbitrarily large as long as it has not more than 4 inputs and 1 output, and no more than 1 flip-flop.

Xilinx FPGAs (interconnect detail)

 


Project platform: Xilinx ML505-110

 

FPGA: Xilinx Virtex-5 XC5VLX110T





Virtex-5 "die photo"

 


A die is an unpacked part

From die to PC board ...


Ball Grid Array (BGA) Flip-Chip Package

  

Spring 2011

 


50 - Lec03-FPGA

 



Page 27

Banks of I/O placed on chip floor plan

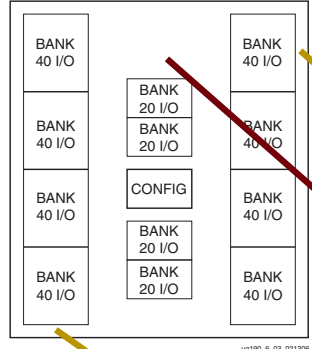

Colors on this package pinout map to banks.


	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16	17	18	19	20	21	22	23	24	25	26
A	16	16	16	16	16	16	16	16	16	16	16	16	16	16	16	16	16	16	16	16	16	16	16	16	16	16
B	16	16	16	16	16	16	16	16	16	16	16	16	16	16	16	16	16	16	16	16	16	16	16	16	16	16
C	16	16	16	16	16	16	16	16	16	16	16	16	16	16	16	16	16	16	16	16	16	16	16	16	16	16
D	16	16	16	16	16	16	16	16	16	16	16	16	16	16	16	16	16	16	16	16	16	16	16	16	16	16
E	14	14	14	12	12	12	3	3	3	3	3	3	3	3	3	3	3	3	3	3	3	3	3	3	3	
F	14	14	14	12	12	12	3	3	3	3	3	3	3	3	3	3	3	3	3	3	3	3	3	3	3	
G	14	14	14	12	12	12	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	
H	14	14	14	12	12	12	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	
J	14	14	14	12	12	12																				
K	14	14	14	12	12	12																				
L	14	14	14	12	12	12																				
M	14	14	14	12	12	12																				
N	14	14	14	12	12	12																				
P	14	14	14	12	12	12																				
R	14	14	14	12	12	12																				
T	14	14	14	12	12	12																				
U	14	14	14	12	12	12																				
V	14	14	14	12	12	12																				
W	14	14	14	12	12	12																				
Y	14	14	14	12	12	12																				
AA	14	14	14	12	12	12	2	2	2	2	2	2	2	2	2	2	2	2	2	2	2	2	2	2	2	
AB	14	14	14	12	12	12	4	4	4	4	4	4	4	4	4	4	4	4	4	4	4	4	4	4	4	
AC	14	14	14	12	12	12	4	4	4	4	4	4	4	4	4	4	4	4	4	4	4	4	4	4	4	
AD	14	14	14	12	12	12	4	4	4	4	4	4	4	4	4	4	4	4	4	4	4	4	4	4	4	
AE	14	14	14	12	12	12	4	4	4	4	4	4	4	4	4	4	4	4	4	4	4	4	4	4	4	
AF	14	14	14	12	12	12	4	4	4	4	4	4	4	4	4	4	4	4	4	4	4	4	4	4	4	

  

Spring 2011

Configurable Logic Blocks (CLBs)

 Slices define regular connections to the switching fabric, and to slices in CLBs above and below it on the die.




The LX110T has 17,280 slices.

X-Y naming convention for slices

X0, X2, ... are lower CLB slices.


X1, X3, ... are upper CLB slices.

Y0, Y1, ... are CLB column positions.

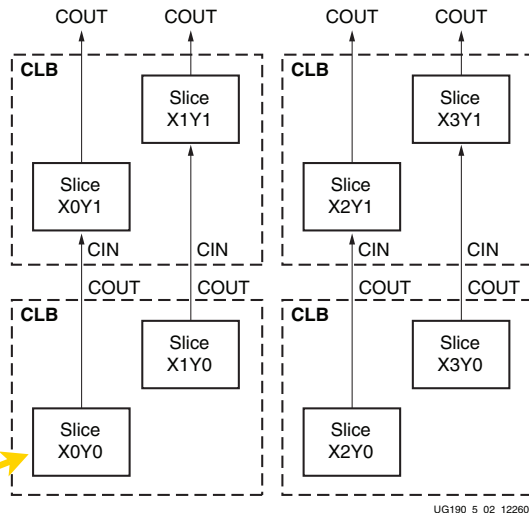

Lower-left corner of the die.

Atoms: 5-input Look Up Tables (LUTs)

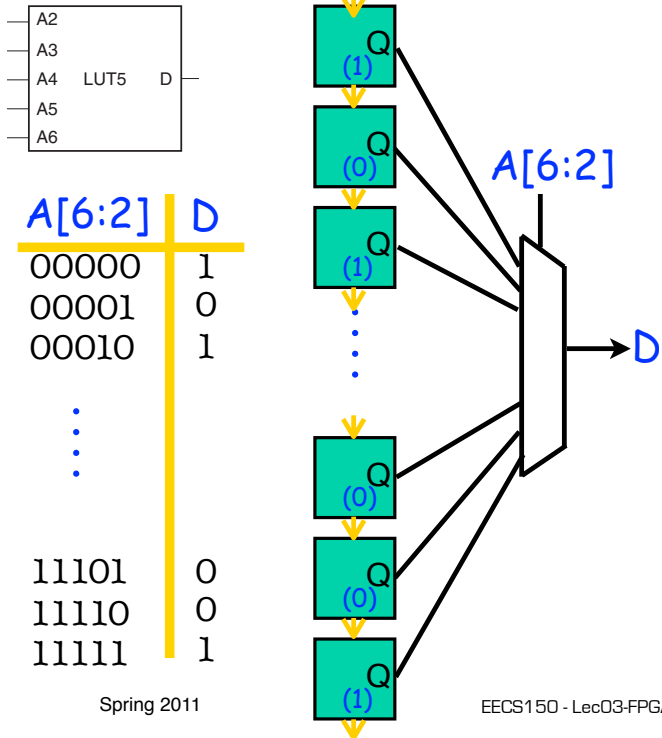

Computes any 5-input logic function.

Timing is independent of function.

Latches set during configuration

Virtex-5 6-LUTs: Composition of 5-LUTs

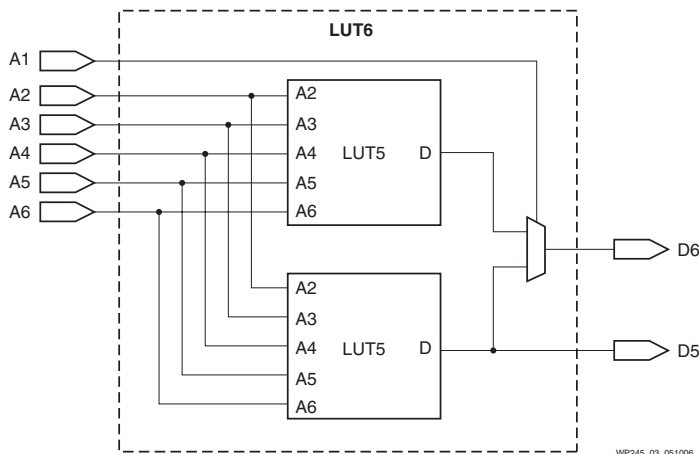


Figure 3: Block Diagram of a Virtex-5 6-Input LUT


May be used as one 6-input LUT (D6 out) ...

... or as two 5-input LUTS (D6 and D5)

Combinational logic (post configuration)

The LX110T has 69,120 6-LUTs
6-LUT delay is 0.9 ns

The simplest view of a slice

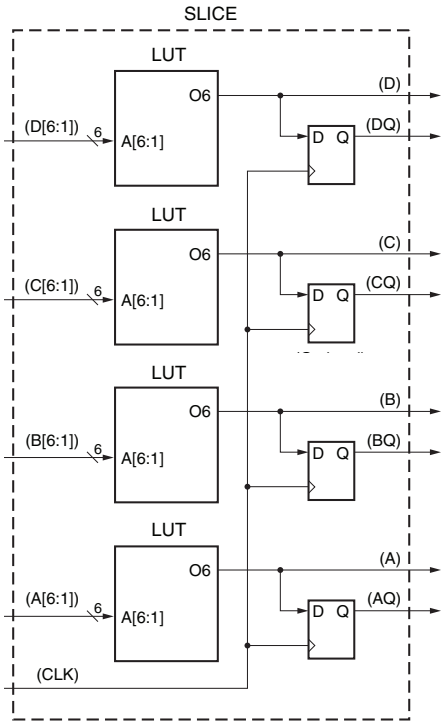

EECS150 - Lec03-FPGA

Page 35


Four 6-LUTs

Four Flip-Flops

Switching fabric may see
combinational and registered
outputs.

An actual Virtex-5 slice adds
many small features to this
simplified diagram. We show
them one by one ...

Two 7-LUTs per slice ...

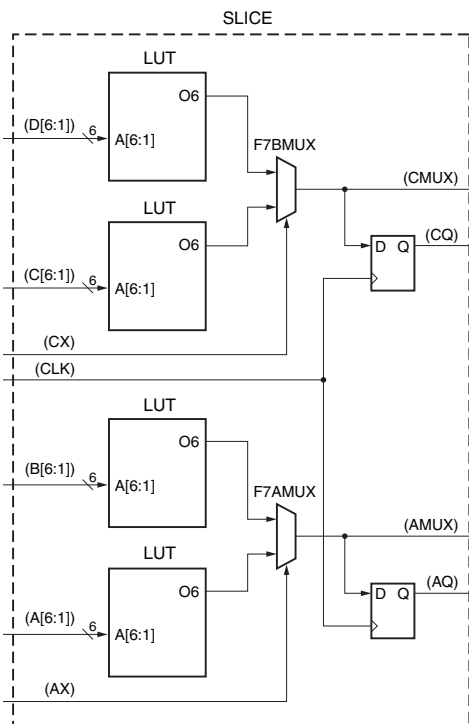


CS150 - Lec03-FPGA

Page 36

Extra multiplexers
(F7AMUX, F7BMUX)

Extra inputs
(AX and CX)

Or one 8-LUTs per slice ...

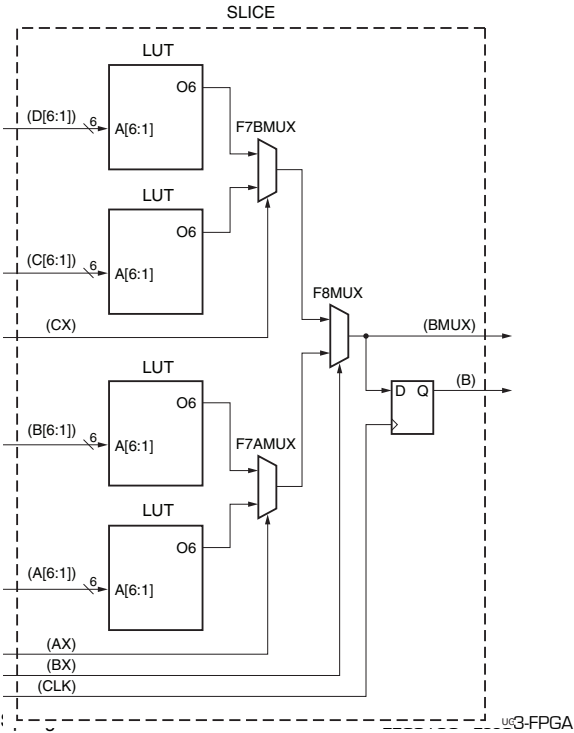


Third multiplexer
(F8MUX)

Third input
(BX)

Configuring the
"n" of an n-LUT ...

Extra muxes to chose LUT option ...

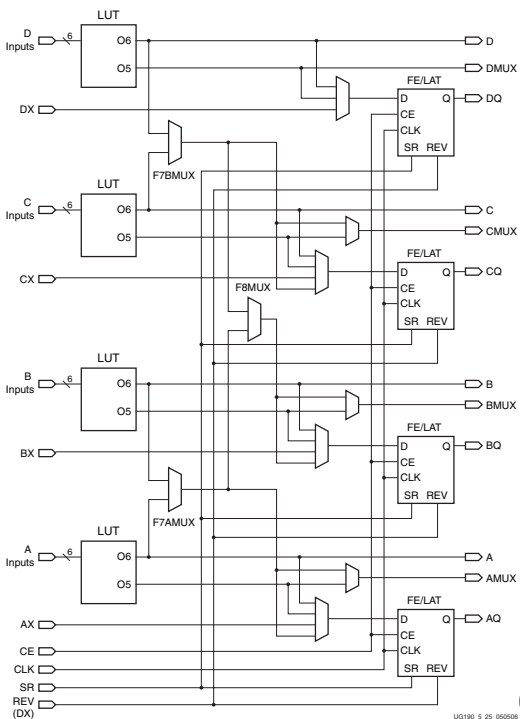


From eight 5-LUTs
... to one 8-LUT.

Combinational
or registered outs.

Flip-flops unused by
LUTs can be used
standalone.

Flip-flops ...

Slice flip-flop properties ...

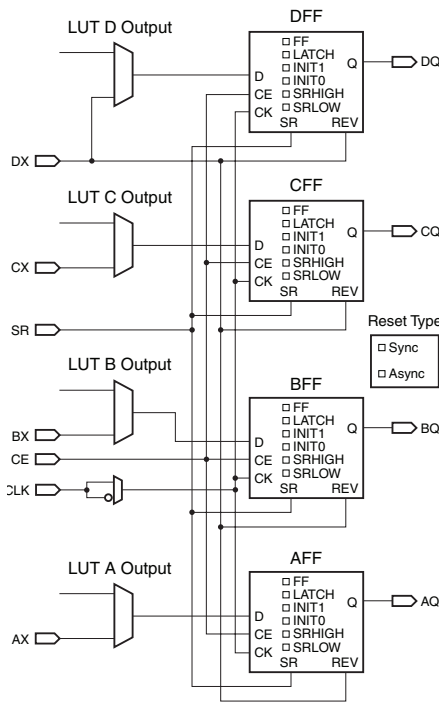


Each state element may be edge-triggered FF or latch.

Clock enable, clock polarity, and set/reset lines in a slice are shared.


Each state element may respond differently to set/reset signal.

Next: The vertical dimension ...

Virtex 5 Verical Logic

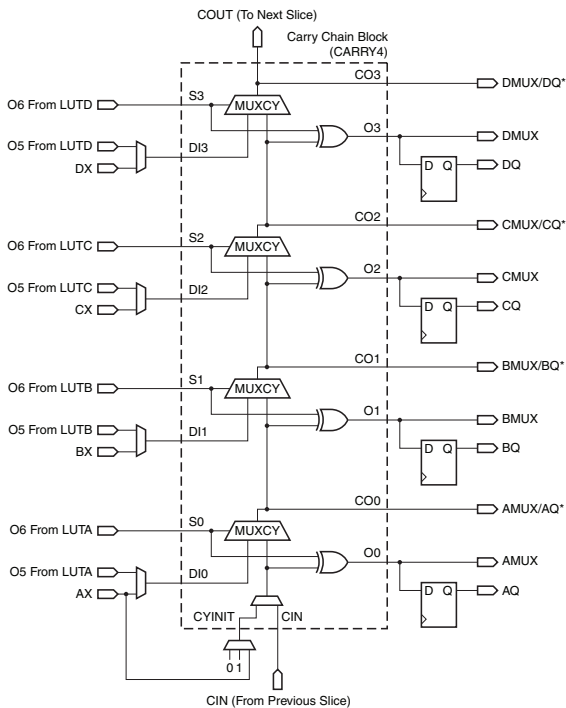


 We can map ripple-carry addition onto carry-chain block.



The carry-chain block also useful for speeding up other adder structures and counters.

Putting it all together ... a SLICEL.

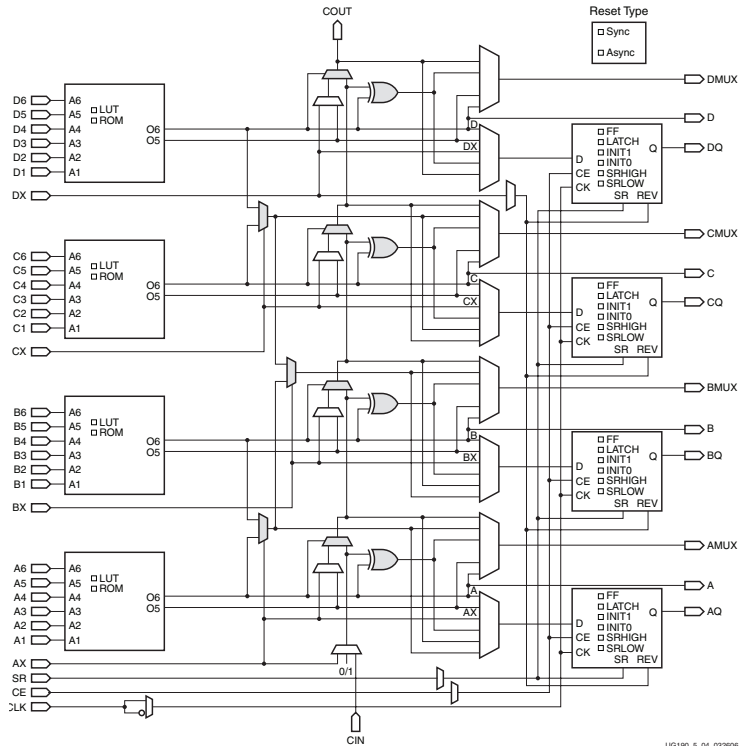


The previous slides explain all SLICEL features.

About 50% of the 17,280 slices in an LX110T are SLICELs.


The other slices are SLICEMs, and have extra features.

Page 41

Recall: 5-LUT architecture ...

 

A[6:2]	D
00000	1
00001	0
00010	1
⋮	⋮
11101	0
11110	0
11111	1

 


- 32 Latches.
- Configured to 1 or 0.

Some parts of a logic design need many state elements.


SLICEMs replace normal 5-LUTs with circuits that can act like 5-LUTs, but can alternatively use the 32 latches as RAM, ROM, shift registers.

A SLICEM 6-LUT ...

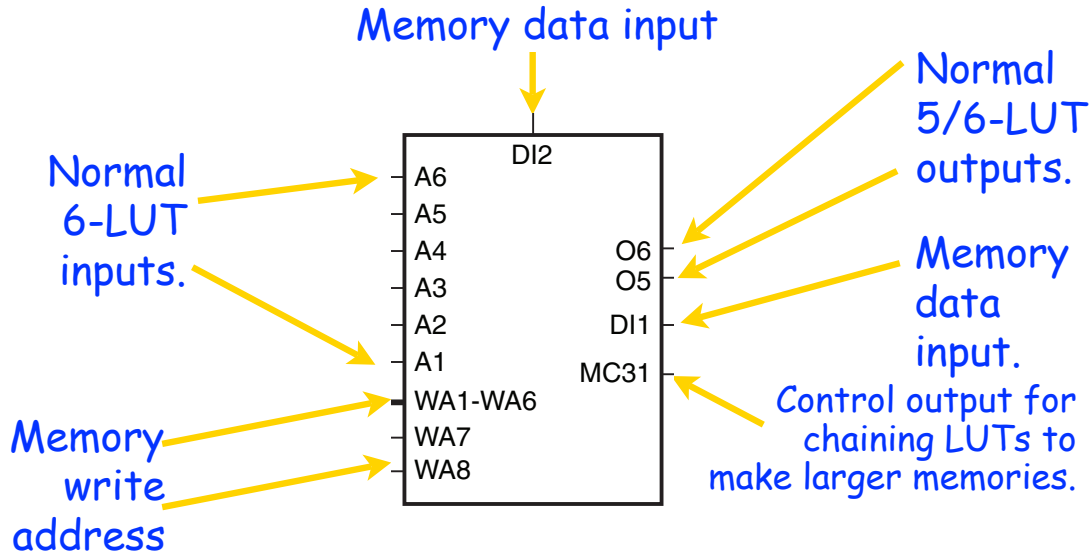

A 1.1 Mb distributed RAM can be made if all SLICEMs of an LX110T are used as RAM.

Many RAM configurations possible ...

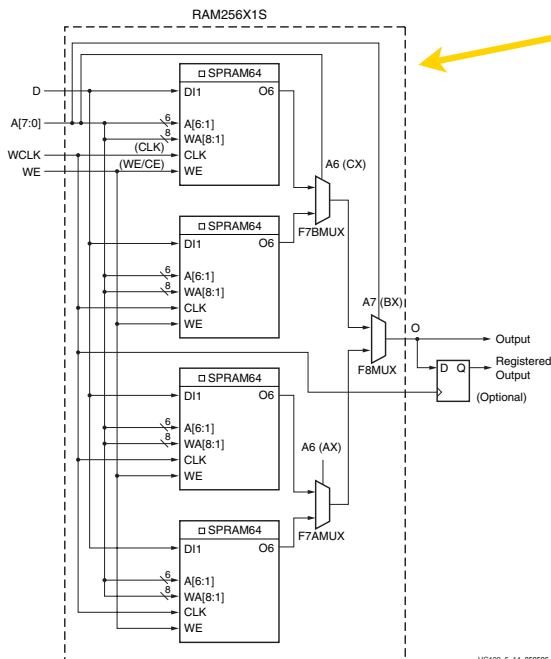


Example configuration:
Single-port 256b x 1,
registered output.

A complete list:

- Single-Port 32 x 1-bit RAM
- Dual-Port 32 x 1-bit RAM
- Quad-Port 32 x 2-bit RAM
- Simple Dual-Port 32 x 6-bit RAM
- Single-Port 64 x 1-bit RAM
- Dual-Port 64 x 1-bit RAM
- Quad-Port 64 x 1-bit RAM
- Simple Dual-Port 64 x 3-bit RAM
- Single-Port 128 x 1-bit RAM
- Dual-Port 128 x 1-bit RAM
- Single-Port 256 x 1-bit RAM

A 128 x 32b LUT RAM
has a 1.1ns access time.


SLICEM shift register (one of many).

 


See Virtex-5 User Guide for an complete list of shift-register types.

SLICEL vs SLICEM ...

SLICEL

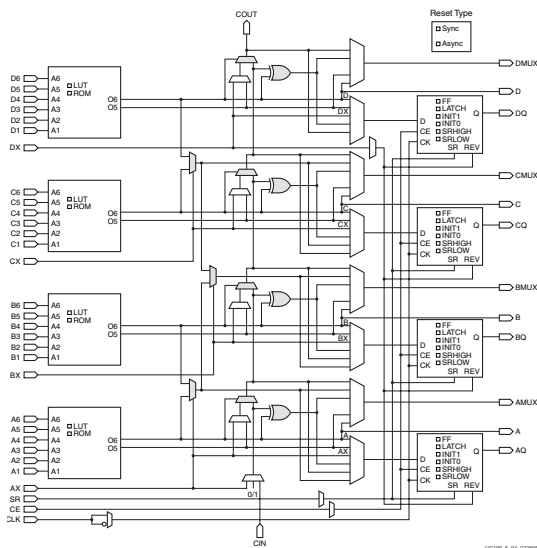


SLICEM

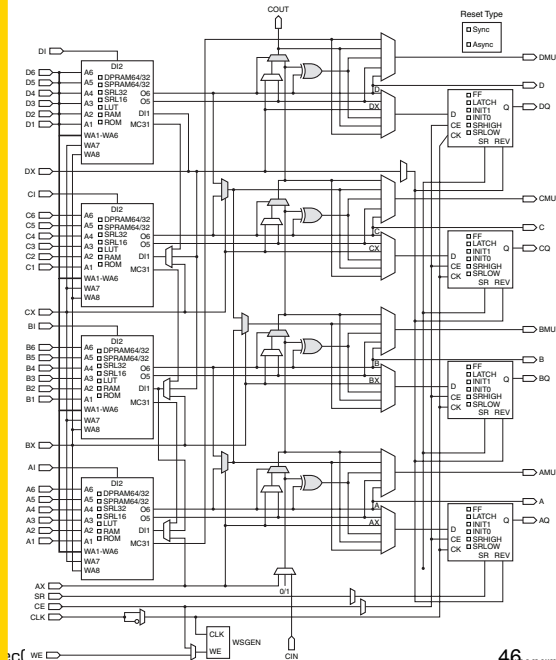

SLICEM adds memory features to LUTs, + muxes.

Virtex-5 DSP48E Slice

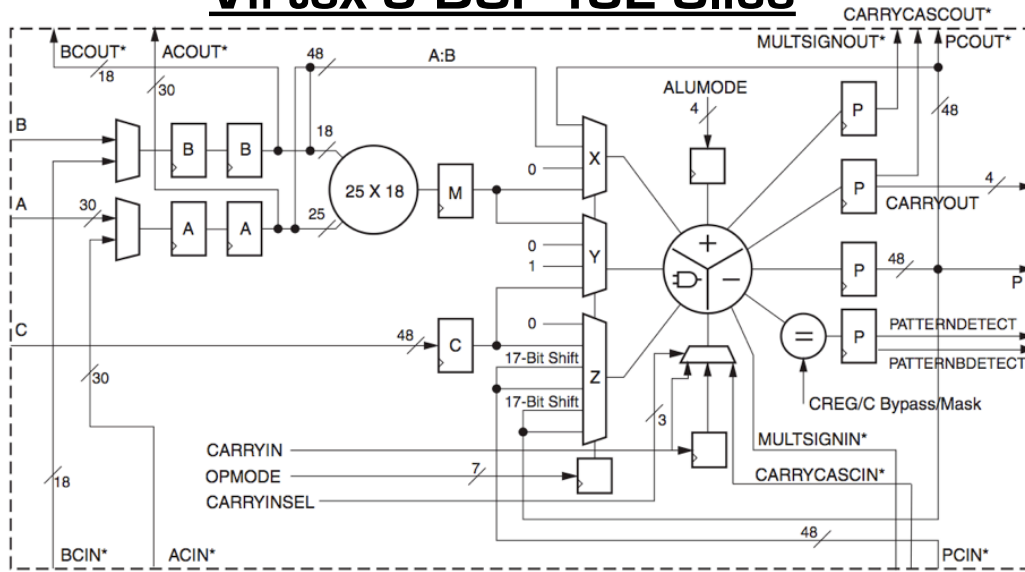

*These signals are dedicated routing paths internal to the DSP48E column. They are not accessible via fabric routing resources.

UG193_c1_01_032806

Efficient implementation of multiply, add, bit-wise logical.

LX110T has 64 in a single column.

Spring 2011

EECS150 - Lec03-FPGA

Page 47

Table 1: Virtex-5 FPGA Family Members

Device	Configurable Logic Blocks (CLBs)			Block RAM Blocks			CMTs ⁽⁴⁾	PowerPC Processor Blocks	Endpoint Blocks for PCI Express	Ethernet MACs ⁽⁵⁾	Max RocketIO Transceivers ⁽⁶⁾		Total I/O Banks ⁽⁸⁾	Max User I/O ⁽⁷⁾	
	Array (Row x Col)	Virtex-5 Slices ⁽¹⁾	Max Distributed RAM (Kb)	DSP48E Slices ⁽²⁾	18 Kb ⁽³⁾	36 Kb					Max (Kb)	GTP			GTX
XC5VLX30	80 x 30	4,800	320	32	64	32	1,152	2	N/A	N/A	N/A	N/A	13	400	
XC5VLX50	120 x 30	7,200	480	48	96	48	1,728	6	N/A	N/A	N/A	N/A	17	560	
XC5VLX85	120 x 54	12,960	840	48	192	96	3,456	6	N/A	N/A	N/A	N/A	17	560	
XC5VLX110	160 x 54	17,280	1,120	64	256	128	4,608	6	N/A	N/A	N/A	N/A	23	800	
XC5VLX155	160 x 76	24,320	1,640	128	384	192	6,912	6	N/A	N/A	N/A	N/A	23	800	
XC5VLX220	160 x 108	34,560	2,280	128	384	192	6,912	6	N/A	N/A	N/A	N/A	23	800	
XC5VLX330	240 x 108	51,840	3,420	192	576	288	10,368	6	N/A	N/A	N/A	N/A	33	1,200	
XC5VLX20T	60 x 26	3,120	210	24	52	26	936	1	N/A	1	2	4	7	172	
XC5VLX30T	80 x 30	4,800	320	32	72	36	1,296	2	N/A	1	4	8	12	360	
XC5VLX50T	120 x 30	7,200	480	48	120	60	2,160	6	N/A	1	4	12	15	480	
XC5VLX85T	120 x 54	12,960	840	48	216	108	3,888	6	N/A	1	4	12	15	480	
XC5VLX110T	160 x 54	17,280	1,120	64	296	148	5,328	6	N/A	1	4	16	20	680	
XC5VLX155T	160 x 76	24,320	1,640	128	424	212	7,632	6	N/A	1	4	16	20	680	
XC5VLX220T	160 x 108	34,560	2,280	128	424	212	7,632	6	N/A	1	4	16	20	680	
XC5VLX330T	240 x 108	51,840	3,420	192	648	324	11,664	6	N/A	1	4	24	27	960	
XC5VSX35T	80 x 34	5,440	520	192	168	84	3,024	2	N/A	1	4	8	12	360	
XC5VSX50T	120 x 34	8,160	780	288	264	132	4,752	6	N/A	1	4	12	15	480	
XC5VSX95T	160 x 46	14,720	1,520	640	488	244	8,784	6	N/A	1	4	16	19	640	
XC5VSX240T	240 x 78	37,440	4,200	1,056	1,032	516	18,576	6	N/A	1	4	24	27	960	
XC5VTX150T	200 x 58	23,200	1,500	80	456	228	8,208	6	N/A	1	4	N/A	40	20	680
XC5VTX240T	240 x 78	37,440	2,400	96	648	324	11,664	6	N/A	1	4	N/A	48	20	680
XC5VFX30T	80 x 38	5,120	380	64	136	68	2,448	2	1	1	4	N/A	8	12	360
XC5VFX70T	160 x 38	11,200	820	128	296	148	5,328	6	1	3	4	N/A	16	19	640
XC5VFX100T	160 x 56	16,000	1,240	256	456	228	8,208	6	2	3	4	N/A	16	20	680
XC5VFX130T	200 x 56	20,480	1,580	320	596	298	10,728	6	2	3	6	N/A	20	24	840
XC5VFX200T	240 x 68	30,720	2,280	384	912	456	16,416	6	2	4	8	N/A	24	27	960

To be continued ...

Throughout the semester, we will look at different Virtex-5 features in-depth.

Switch fabric

Block RAM

DSP48 (ALUs)

Clocking

I/O

Serial I/O + PCI

