

# EECS150 – Digital Design

## Lecture 4 – Synchronous

### Digital Systems Review Part 2

January 27, 2011

John Wawrzynek  
Electrical Engineering and Computer Sciences  
University of California, Berkeley


<http://www-inst.eecs.berkeley.edu/~cs150>

## Outline

- Topics in the review, you have already seen in CS61C, and possibly EE40:
  1. Digital Signals.
  2. General model for synchronous systems.
  3. Combinational logic circuits
  4. Flip-flops, clocking
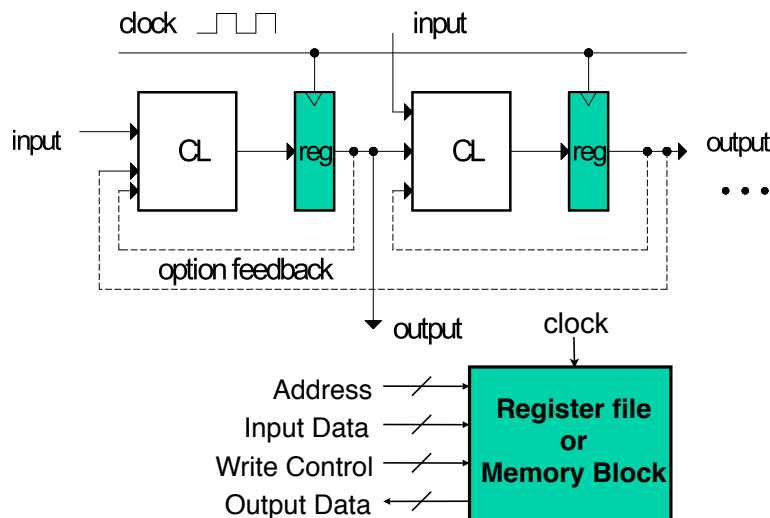
# Only Two Types of Circuits Exist

- Combinational Logic Blocks (CL)
- State Elements (registers)




• State elements are mixed in with CL blocks to control the flow of data.

• Sometimes used in large groups by themselves for "long-term" data storage.

## State Elements: circuits that store info

 
- Examples: registers, memories
- Register: Under the control of the "load" signal, the register captures the input value and stores it indefinitely.



often replace by clock signal (clk)

- The value stored by the register appears on the output (after a small delay).
- Until the next load, changes on the data input are ignored (unlike CL, where input changes change output).
- These get used for short term storage (ex: register file), and to help move data around the processor.


# Register Details...What's inside?

 

- $n$  instances of a "Flip-Flop"
- Flip-flop name because the output flips and flops between 0,1
- $D$  is "data",  $Q$  is "output"
- Also called "d-type Flip-Flop"
 
## Flip-flop Timing

- Edge-triggered d-type flip-flop
  - This one is "positive edge-triggered"
- "On the rising edge of the clock, the input  $d$  is sampled and transferred to the output. At all other times, the input  $d$  is ignored."
- Example waveforms:



# Uses for State Elements

1) As a place to store values for some indeterminate amount of time:


- Register files (like \$1-\$31 on the MIPS)
- Memory (caches, and main memory)

2) Help control the flow of information between combinational logic blocks.

- State elements are used to hold up the movement of information at the inputs to combinational logic blocks and allow for orderly passage.

 
## Accumulator Circuit Example

Assume  $X$  is a vector of  $N$  integers, presented to the input of our accumulator circuit one at a time (one per clock cycle), so that after  $N$  clock cycles,  $S$  hold the sum of all  $N$  numbers.




$S=0$ ; Repeat  $N$  times  
 $S = S + X$ ;

• We need something like this:

 


- But not quite.
- Need to use the clock signal to hold up the feedback to match up with the input signal.

# Accumulator Circuit

 


- Put register, with clock signal controlling its load, in feedback path.
- On each clock cycle the register prevents the new value from reaching the input to the adder prematurely. (The new value just waits at the input of the register).

## Timing:

 


 
# Register Details (again)

- A n-bit wide register is nothing but a set of flip-flops (1-bit wide registers) with a common load/clock signal.




 - A flip-flop captures its input on the edge of the clock (rising edge in this case - positive edge flip-flop). The new input appears at the output after a short delay.



 


# Flip-Flop Timing Details

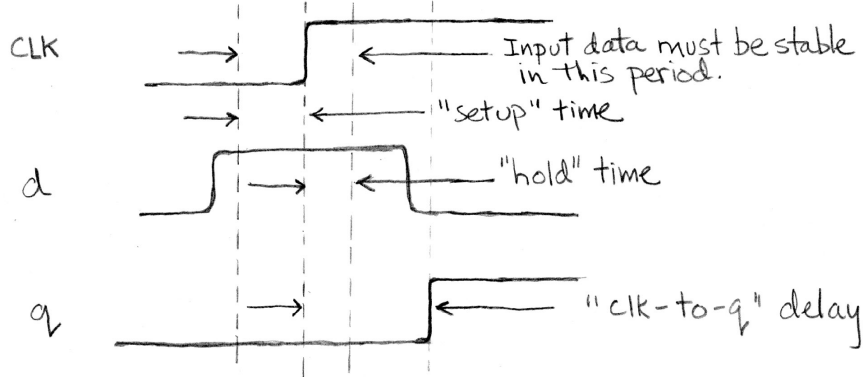


Three important times associated with flip-flops:

- setup time
- hold time
- clock-to-q delay.


# Accumulator Revisited

 

 - Note:
    - Reset signal (synchronous)
    - Timing of X signal is not known without investigating the circuit that supplies X. Here we assume it comes just after  $S_{i-1}$ .
- Observe transient behavior of  $S_i$ .



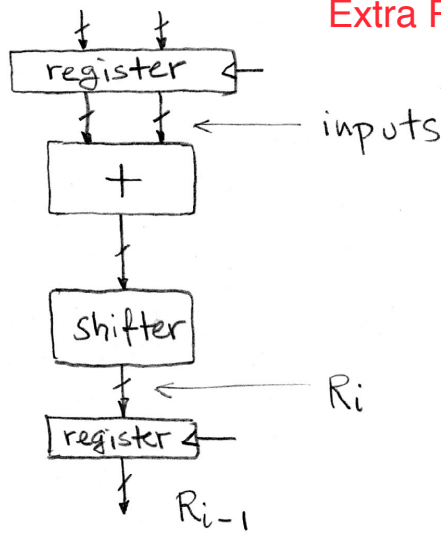
# Pipelining to improve performance (1/2)



Extra Register are often added to help speed up the clock rate.


Timing...

 

Note: delay of 1 clock cycle from input to output.


Clock period limited by propagation delay of adder/shifter.
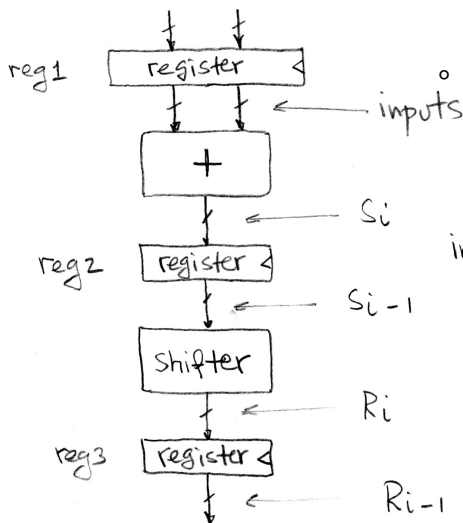
# Pipelining to improve performance (2/2)





◦ Insertion of register allows higher clock frequency.

◦ More outputs per second. Timing...

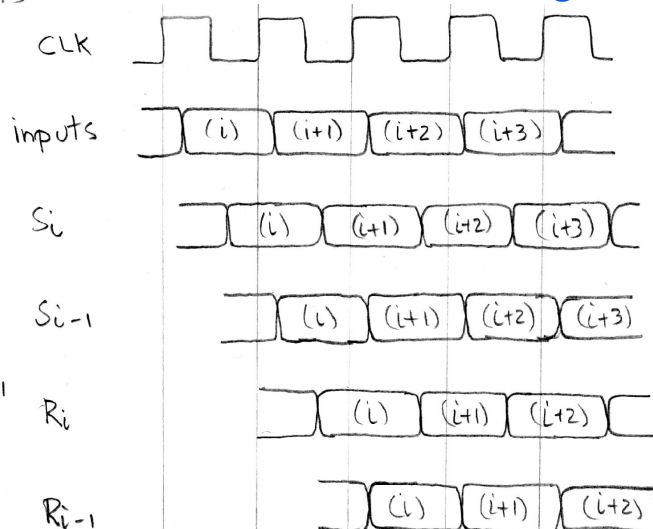


# Level-sensitive Latch

Positive Level-sensitive latch:

  

When CLK is high, latch is transparent, when clk is low, latch retains previous value.

Positive Edge-triggered flip-flop built from two level-sensitive latches:

 

Spring 2011


EECS

Page 15

## Flip-flops on Virtex5 FPGA

SLICEL

SLICEM

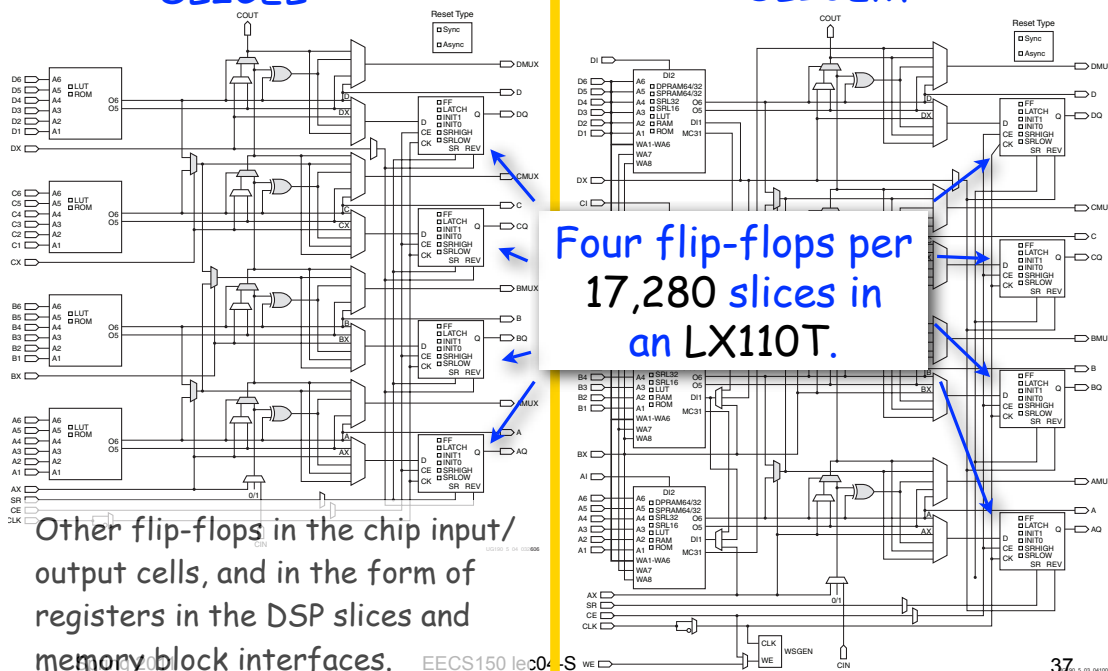


Other flip-flops in the chip input/output cells, and in the form of registers in the DSP slices and memory block interfaces.

EECS150 lec04-S

37



# Virtex5 Slice Flip-flops

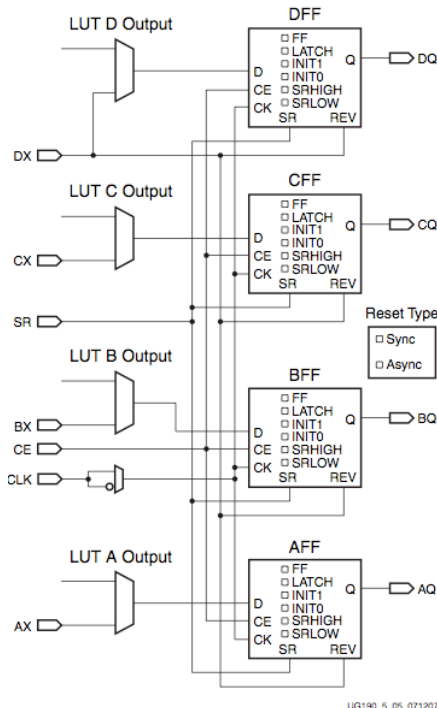

4 flip-flops / slice (corresponding to the 4 6-LUTs)

Each takes input from LUT output or primary slice input.

Edge-triggered FF vs. level-sensitive latch.  
Clock-enable input (can be set to 1 to disable) (shared).

Positive versus negative clock-edge.


Synchronous vs. asynchronous reset.

SRHIGH/SRLOW select reset (SR) set.

REV forces opposite state.

INIT0/INIT1 used for global reset (not shown - usually just after power-on and configuration).


# Virtex5 Flip-flops "Primitives"

 


D Flip-Flop with Synchronous Reset and Set and Clock Enable

Provided by the CAD tools. This maps to single slice flip-flop.


Logic Table						
Inputs						Output
R	S	CE	D	C	Q	
1	-	-	-	↑	0	
0	1	-	-	↑	1	
0	0	0	-	-	No Change	
0	0	1	1	↑	1	
0	0	1	0	↑	0	

 

 Negative-Clock Edge, Synchronous Reset and Set, and Clock Enable



 Negative-Edge Clock, Clock Enable, and Asynchronous Preset and Clear



Clock Enable and Asynchronous Preset and Clear