


EECS150 - Digital Design
Lecture 19 - Combinational Logic
Circuits : A Deep Dive

March 28, 2011
John Wawrzynek

Outline

- Review of three representations for combinational logic:
 - truth tables,
 - graphical (logic gates), and
 - algebraic equations
- Relationship among the three
- Adder example
- Laws of Boolean Algebra
- Canonical Forms
- Boolean Simplification

Combinational Logic (CL) Defined

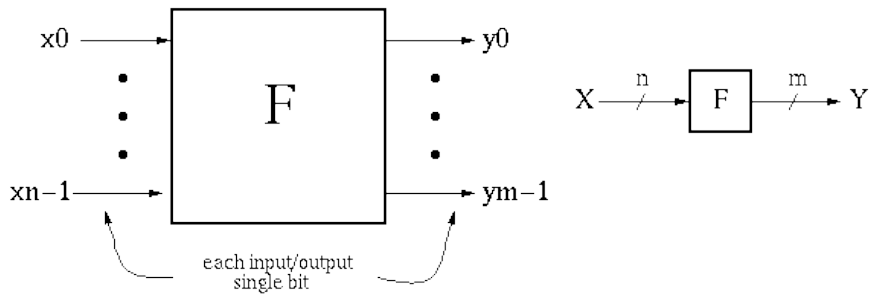


$y_i = f_i(x_0, \dots, x_{n-1})$, where x, y are $\{0,1\}$.

Y is a function of only X .

- If we change X , Y will change immediately (well almost!).
- There is an implementation dependent delay from X to Y .

CL Block Example #1

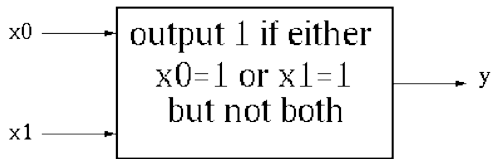

Boolean Equation:


$$y_0 = [x_0 \text{ AND not}\{x_1\}] \\ \text{OR } [\text{not}\{x_0\} \text{ AND } x_1]$$

$$y_0 = x_0x_1' + x_0'x_1$$

Truth Table Description:

x_0	x_1	y
0	0	0
0	1	1
1	0	1
1	1	0

Gate Representation:

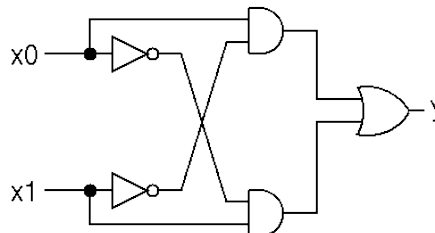

How would we *prove* that all three representations are equivalent?

Boolean Algebra/Logic Circuits

- Why are they called "logic circuits"?
- Logic: The study of the principles of reasoning.
- The 19th Century Mathematician, George Boole, developed a math. system (algebra) involving logic, Boolean Algebra.
- His variables took on TRUE, FALSE
- Later Claude Shannon (father of information theory) showed (in his Master's thesis!) how to map Boolean Algebra to digital circuits:
- Primitive functions of Boolean Algebra:



a	b	AND
0	0	0
0	1	0
1	0	0
1	1	1


a	b	OR
0	0	0
0	1	1
1	0	1
1	1	1

a	NOT
0	1
1	0



Relationship Among Representations

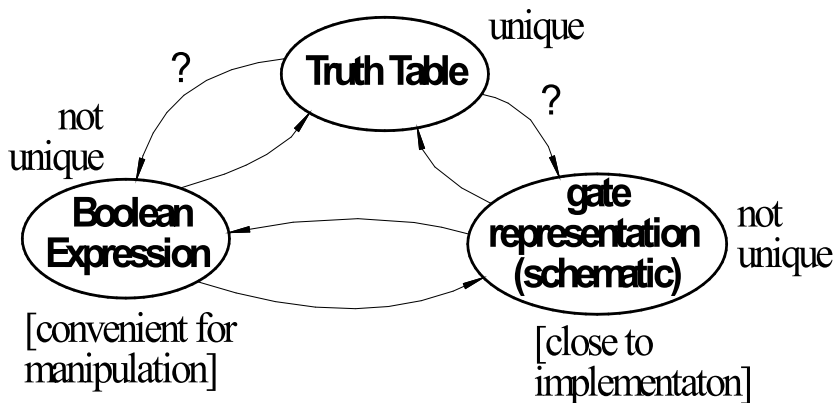
- * Theorem: Any Boolean function that can be expressed as a truth table can be written as an expression in Boolean Algebra using AND, OR, NOT.



How do we convert from one to the other?

CL Block Example #2

- 4-bit adder:

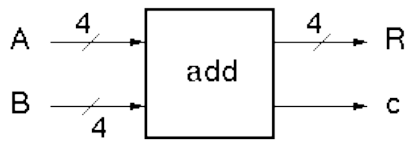

$R = A + B,$
 c is carry out

- Truth Table Representation:

a3	a2	a1	a0	b3	b2	b1	b0	r3	r2	r1	r0	c
0	0	0	0	0	0	0	0	0	0	0	0	0
0	0	0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	0	1	1	0	0	1	1	0
0	0	0	0	0	1	0	0	0	1	0	0	0
⋮												
⋮												
0	0	1	0	0	0	1	0	0	1	0	0	0
0	0	1	0	0	0	1	1	0	1	0	1	0
⋮												
⋮												
0	0	0	1	1	1	1	1	0	0	0	0	1

In general: 2^n rows for n inputs.

256 rows!

Is there a more efficient (compact) way to specify this function?

4-bit Adder Example

- Motivate the adder circuit design by hand addition:

a3	a2	a1	a0	
+	b3	b2	b1	b0
c	r3	r2	r1	r0

a3	a2	a1	a0	
+	b3	b2	b1	b0
c	r3	r2	r1	r0

- Add a_0 and b_0 as follows:

a	b	r	c
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

↖ carry to next stage

$r = a \text{ XOR } b = a \oplus b$
 $c = a \text{ AND } b = ab$

- Add a_1 and b_1 as follows:

c _i	a	b	r	c _o
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1


$r = a \oplus b \oplus c_i$
 $c_o = ab + ac_i + bc_i$

4-bit Adder Example

- In general:


$$r_i = a_i \oplus b_i \oplus c_{in}$$
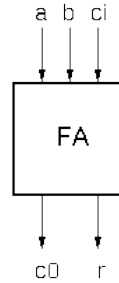
$$c_{out} = a_i c_{in} + a_i b_i + b_i c_{in} = c_{in}(a_i + b_i) + a_i b_i$$



“Full adder cell”

- Now, the 4-bit adder:

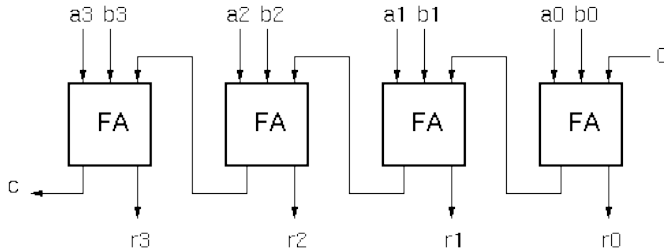

“ripple” adder

4-bit Adder Example

- Graphical Representation of FA-cell




$$r_i = a_i \oplus b_i \oplus c_{in}$$

$$c_{out} = a_i c_{in} + a_i b_i + b_i c_{in}$$

- Alternative Implementation (with 2-input gates):

$$r_i = (a_i \oplus b_i) \oplus c_{in}$$
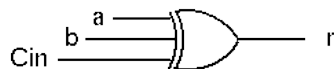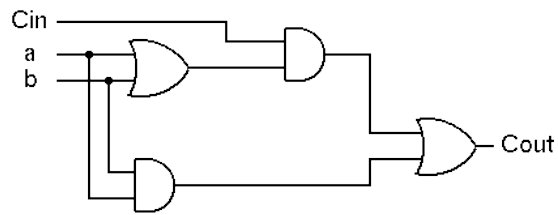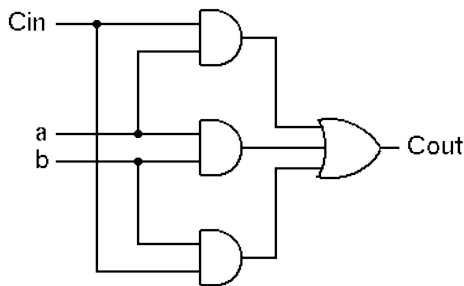
$$c_{out} = c_{in}(a_i + b_i) + a_i b_i$$



Boolean Algebra

Defined as:

Set of elements B , binary operators $\{+, \bullet\}$ unary operation $\{ '\}$ such that the following axioms hold :

1. B contains at least two elements a, b such that $a \neq b$.
2. Closure : a, b in B ,
 $a + b$ in B , $a \bullet b$ in B , a' in B .
3. Communitive laws :
 $a + b = b + a$, $a \bullet b = b \bullet a$.
4. Identities : $0, 1$ in B
 $a + 0 = a$, $a \bullet 1 = a$.
5. Distributive laws :
 $a + (b \bullet c) = (a + b) \bullet (a + c)$, $a \bullet (b + c) = a \bullet b + a \bullet c$.
6. Complement :
 $a + a' = 1$, $a \bullet a' = 0$.

Logic Functions

$B = \{0,1\}$, $+$ = OR, \bullet = AND, $'$ = NOT

is a valid Boolean Algebra.



00		0
01		1
10		1
11		1



00		0
01		0
10		0
11		1



0		1
1		0

Do the axioms hold?

- Ex: communitive law: $0+1 = 1+0$?

Other logic functions of 2 variables (x,y)

xy	f0	f1													
00	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1
01	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1
10	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1
11	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0



↙ ↘
↙ ↘
↙ ↘
↙ ↘
↙ ↘
↙ ↘
↙ ↘
↙ ↘
↙ ↘
↙ ↘
↙ ↘
↙ ↘
↙ ↘
↙ ↘
↙ ↘
↙ ↘

Look at NOR and NAND:



- Theorem:** Any Boolean function that can be expressed as a truth table can be expressed using NAND and NOR.

- Proof sketch:

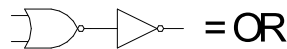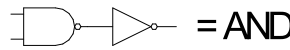

- How would you show that either NAND or NOR is sufficient?

Laws of Boolean Algebra

Duality: A dual of a Boolean expression is derived by interchanging OR and AND operations, and 0s and 1s (literals are left unchanged).

$$\{F(x_1, x_2, \dots, x_n, 0, 1, +, \bullet)\}^D = \{F(x_1, x_2, \dots, x_n, 1, 0, \bullet, +)\}$$

Any law that is true for an expression is also true for its dual.

Operations with 0 and 1:

1. $x + 0 = x$ $x \bullet 1 = x$
2. $x + 1 = 1$ $x \bullet 0 = 0$

Idempotent Law:

3. $x + x = x$ $x \bullet x = x$

Involution Law:

4. $[x']' = x$

Laws of Complementarity:

5. $x + x' = 1$ $x \bullet x' = 0$

Commutative Law:

6. $x + y = y + x$ $x \bullet y = y \bullet x$

Laws of Boolean Algebra (cont.)

Associative Laws:

$$(x + y) + z = x + (y + z) \quad x y z = x (y z)$$

Distributive Laws:

$$x (y + z) = (x y) + (x z) \quad x + (y z) = (x + y)(x + z)$$

"Simplification" Theorems:

$$x y + x y' = x \quad (x + y) (x + y') = x$$

$$x + x y = x \quad x (x + y) = x$$

DeMorgan's Law:

$$(x + y + z + \dots)' = x' y' z' \quad (x y z \dots)' = x' + y' + z'$$

Theorem for Multiplying and Factoring:

$$(x + y) (x' + z) = x z + x' y$$

Consensus Theorem:

$$x y + y z + x' z = (x + y) (y + z) (x' + z)$$

$$x y + x' z = (x + y) (x' + z)$$

Proving Theorems via axioms of Boolean Algebra

Ex: prove the theorem: $x y + x y' = x$

$$x y + x y' = x (y + y') \quad \text{distributive law}$$

$$x (y + y') = x (1) \quad \text{complementary law}$$

$$x (1) = x \quad \text{identity}$$

Ex: prove the theorem: $x + x y = x$

$$x + x y = x 1 + x y \quad \text{identity}$$


$$x 1 + x y = x (1 + y) \quad \text{distributive law}$$

$$x (1 + y) = x (1) \quad \text{identity}$$

$$x (1) = x \quad \text{identity}$$

DeMorgan's Law


$$(x + y)' = x' y'$$

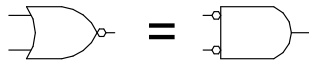

Exhaustive
Proof

x	y	x'	y'	(x+y)'	x'y'
0	0	1	1	1	1
0	1	1	0	0	0
1	0	0	1	0	0
1	1	0	0	0	0

$$(x y)' = x' + y'$$

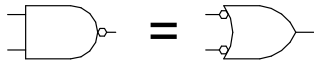


Exhaustive
Proof

x	y	x'	y'	(xy)'	x'+y'
0	0	1	1	1	1
0	1	1	0	1	1
1	0	0	1	1	1
1	1	0	0	0	0

Relationship Among Representations

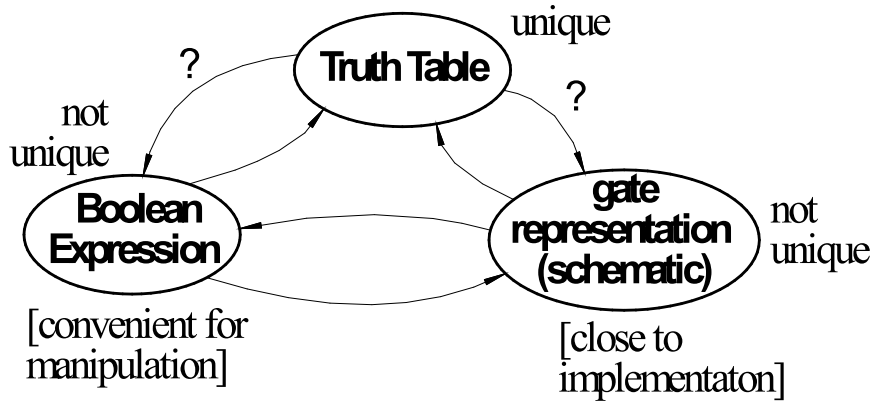- * Theorem: Any Boolean function that can be expressed as a truth table can be written as an expression in Boolean Algebra using AND, OR, NOT.



How do we convert from one to the other?

Canonical Forms

- Standard form for a Boolean expression - unique algebraic expression directly from a true table (TT) description.
- Two Types:
 - * Sum of Products (SOP)
 - * Product of Sums (POS)
- **Sum of Products** (disjunctive normal form, minterm expansion).

Example:

minterms	a	b	c	f	f'
a'b'c'	0	0	0	0	1
a'b'c	0	0	1	0	1
a'bc'	0	1	0	0	1
a'bc	0	1	1	1	0
ab'c'	1	0	0	1	0
ab'c	1	0	1	1	0
abc'	1	1	0	1	0
abc	1	1	1	1	0

One product (**and**) term for each 1 in f:

$$f = a'bc + ab'c' + ab'c + abc' + abc$$

$$f' = a'b'c' + a'b'c + a'bc'$$

Sum of Products (cont.)

Canonical Forms are usually not minimal:

Our Example:

$$f = a'bc + ab'c' + ab'c + abc' + abc \quad (xy' + xy = x)$$

$$= a'bc + ab' + ab$$

$$= a'bc + a \quad (x'y + x = y + x)$$

$$= a + bc$$

$$f' = a'b'c' + a'b'c + a'bc'$$

$$= a'b' + a'bc'$$

$$= a' (b' + bc')$$

$$= a' (b' + c')$$

Canonical Forms

- **Product of Sums** (conjunctive normal form, maxterm expansion). Example:

maxterms	a	b	c	f	f'
$a+b+c$	0	0	0	0	1
$a+b+c'$	0	0	1	0	1
$a+b'+c$	0	1	0	0	1
$a+b'+c'$	0	1	1	1	0
$a'+b+c$	1	0	0	1	0
$a'+b+c'$	1	0	1	1	0
$a'+b'+c$	1	1	0	1	0
$a'+b'+c'$	1	1	1	1	0

One sum (**or**) term for each 0 in f:

$$f = (a+b+c)(a+b+c')(a+b'+c)$$

$$f' = (a+b'+c')(a'+b+c)(a'+b+c') \\ (a'+b'+c)(a+b+c')$$

Mapping from SOP to POS (or POS to SOP): Derive truth table then proceed.

Algebraic Simplification Example

Ex: full adder (FA) carry out function (in canonical form):

$$C_{out} = a'bc + ab'c + abc' + abc$$

Algebraic Simplification

$$\begin{aligned} \text{Cout} &= a'bc + ab'c + abc' + abc \\ &= a'bc + ab'c + abc' + \mathbf{abc} + \mathbf{abc} \\ &= a'bc + \mathbf{abc} + ab'c + abc' + \mathbf{abc} \\ &= \mathbf{(a' + a)bc} + ab'c + abc' + abc \\ &= \mathbf{(1)bc} + ab'c + abc' + abc \\ &= bc + ab'c + abc' + \mathbf{abc} + \mathbf{abc} \\ &= bc + ab'c + \mathbf{abc} + abc' + \mathbf{abc} \\ &= bc + \mathbf{a(b' + b)c} + abc' + abc \\ &= bc + \mathbf{a(1)c} + abc' + abc \\ &= bc + ac + \mathbf{ab(c' + c)} \\ &= bc + ac + \mathbf{ab(1)} \\ &= bc + ac + ab \end{aligned}$$

Outline for remaining CL Topics

- K-map method of two-level logic simplification
- Multi-level Logic
- NAND/NOR networks
- EXOR revisited

Algorithmic Two-level Logic Simplification

Key tool: The Uniting Theorem:

$$xy' + xy = x(y' + y) = x(1) = x$$

ab	f
00	0
01	0
10	1
11	1


$f = ab' + ab = a(b'+b) = a$
 b values change within the on-set rows
 a values don't change
 b is eliminated, a remains

ab	g
00	1
01	0
10	1
11	0

$g = a'b' + ab' = (a'+a)b' = b'$
 b values stay the same
 a values changes
 b' remains, a is eliminated

Karnaugh Map Method

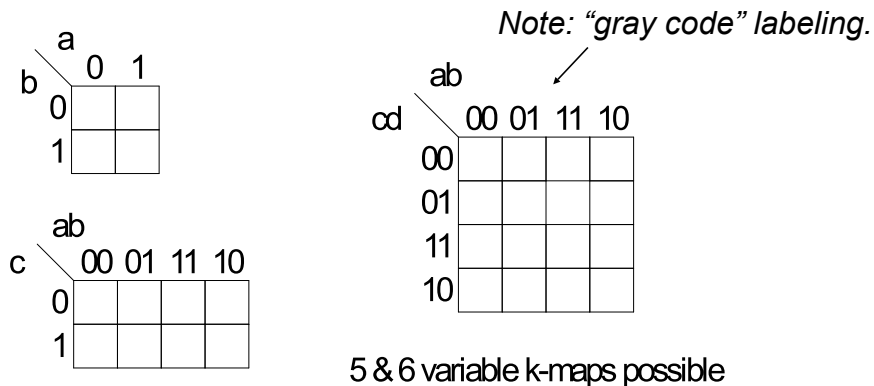- K-map is an alternative method of representing the TT and to help visual the adjacencies.



Karnaugh Map Method

- Adjacent groups of 1's represent product terms

	a	0	1
b	0	0	1
	1	0	1

$f = a$

	a	0	1
b	0	1	1
	1	0	0

$g = b'$

	ab	00	01	11	10
c	0	0	0	1	0
	1	0	1	1	1

$cout = ab + bc + ac$

	ab	00	01	11	10
c	0	0	0	1	1
	1	0	0	1	1

$f = a$

K-map Simplification

1. Draw K-map of the appropriate number of variables (between 2 and 6)
2. Fill in map with function values from truth table.
3. Form groups of 1's.
 - ✓ Dimensions of groups must be even powers of two (1x1, 1x2, 1x4, ..., 2x2, 2x4, ...)
 - ✓ Form as large as possible groups and as few groups as possible.
 - ✓ Groups can overlap (this helps make larger groups)
 - ✓ Remember K-map is periodical in all dimensions (groups can cross over edges of map and continue on other side)
4. For each group write a product term.
 - the term includes the "constant" variables (use the uncomplemented variable for a constant 1 and complemented variable for constant 0)
5. Form Boolean expression as sum-of-products.

K-maps (cont.)

		ab			
		00	01	11	10
c	0	1	0	0	1
	1	0	0	1	1

$$f = b'c' + ac$$

		ab			
		00	01	11	10
cd	00	1	0	0	1
	01	0	1	0	0
	11	1	1	1	1
	10	1	1	1	1

$$f = c + a'bd + b'd'$$

(bigger groups are better)

Product-of-Sums Version

1. Form groups of 0's instead of 1's.
2. For each group write a sum term.
 - the term includes the "constant" variables (use the uncomplemented variable for a constant 0 and complemented variable for constant 1)
3. Form Boolean expression as product-of-sums.


		ab			
		00	01	11	10
cd	00	1	0	0	1
	01	0	1	0	0
	11	1	1	1	1
	10	1	1	1	1

$$f = (b' + c + d)(a' + c + d')(b + c + d')$$

BCD incrementer example

Binary Coded Decimal

	a	b	c	d	w	x	y	z
0	0	0	0	0	0	0	0	1
1	0	0	0	1	0	0	1	0
2	0	0	1	0	0	0	1	1
3	0	0	1	1	0	1	0	0
4	0	1	0	0	0	1	0	1
5	0	1	0	1	0	1	1	0
6	0	1	1	0	0	1	1	1
7	0	1	1	1	1	0	0	0
8	1	0	0	0	1	0	0	1
9	1	0	0	1	0	0	0	0
	1	0	1	0	-	-	-	-
	1	0	1	1	-	-	-	-
	1	1	0	0	-	-	-	-
	1	1	0	1	-	-	-	-
	1	1	1	0	-	-	-	-
	1	1	1	1	-	-	-	-

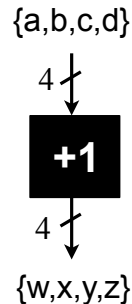

BCD Incrementer Example

- Note one map for each output variable.
- Function includes "don't cares" (shown as "-" in the table).
 - These correspond to places in the function where we don't care about its value, because we don't expect some particular input patterns.
 - We are free to assign either 0 or 1 to each don't care in the function, as a means to increase group sizes.
- In general, you might choose to write product-of-sums or sum-of-products according to which one leads to a simpler expression.



BCD incrementer example

	W	X	
cd \ ab	00 01 11 10	00 01 11 10	
00	0 0 - 1	0 1 - 0	w =
01	0 0 - 0	0 1 - 0	
11	0 1 - -	1 0 - -	x =
10	0 0 - -	0 1 - -	
cd \ ab	y	Z	
00	0 0 - 0	1 1 - 1	y =
01	1 1 - 0	0 0 - 0	
11	0 0 - -	0 0 - -	z =
10	1 1 - -	1 1 - -	

BCD incrementer example

	W	X	
cd \ ab	00 01 11 10	00 01 11 10	
00	0 0 - 1	0 1 - 0	w =
01	0 0 - 0	0 1 - 0	
11	0 1 - -	1 0 - -	x =
10	0 0 - -	0 1 - -	
cd \ ab	y	Z	
00	0 0 - 0	1 1 - 1	y =
01	1 1 - 0	0 0 - 0	
11	0 0 - -	0 0 - -	z =
10	1 1 - -	1 1 - -	

Higher Dimensional K-maps

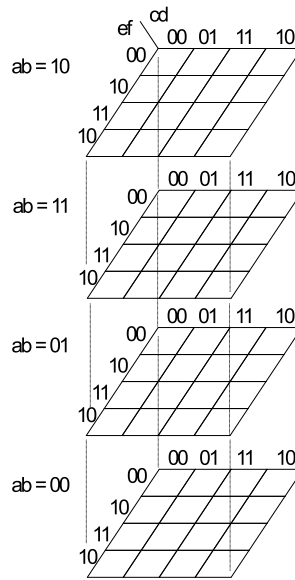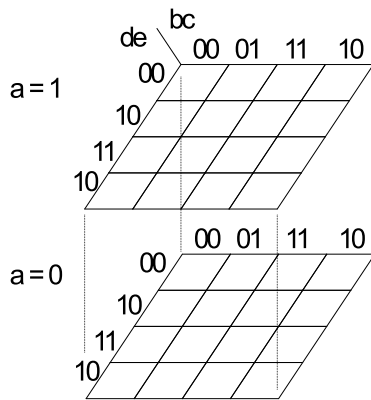

Multi-level Combinational Logic


- Example: reduced sum-of-products form
 $x = adf + aef + bdf + bef + cdf + cef + g$

- Implementation in 2-levels with gates:

cost: 1 7-input OR, 6 3-input AND

=> 50 transistors

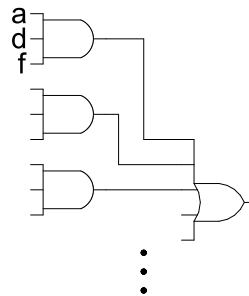delay: 3-input OR gate delay + 7-input AND gate delay




- Factored form:

$$x = (a + b + c)(d + e)f + g$$

cost: 1 3-input OR, 2 2-input OR, 1 3-input AND

=> 20 transistors

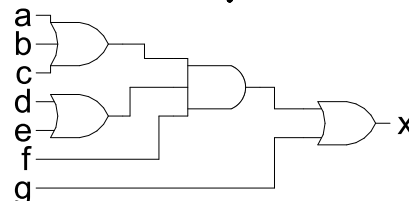delay: 3-input OR + 3-input AND + 2-input OR




Footnote: NAND would be used in place of all ANDs and ORs.

Which is faster?

In general: Using multiple levels (more than 2) will reduce the cost. Sometimes also delay. Sometimes a tradeoff between cost and delay.


Multi-level Combinational Logic

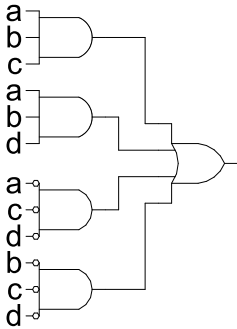Another Example: $F = abc + abd + a'c'd' + b'c'd'$



let $x = ab$ $y = c+d$

$$f = xy + x'y'$$

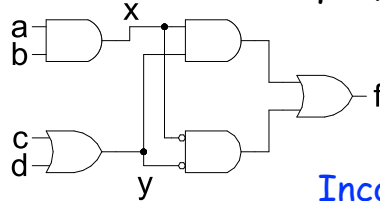

Incorporates fanout.

No convenient hand methods exist for multi-level logic simplification:

- a) CAD Tools use sophisticated algorithms and heuristics
- b) Humans and tools often exploit some special structure (example adder)

Are these optimizations still relevant for LUT implementations?

NAND-NAND & NOR-NOR Networks





DeMorgan's Law Review:

$$(a + b)' = a' b'$$

$$(a b)' = a' + b'$$

$$a + b = (a' b')'$$

$$(a b) = (a' + b')'$$

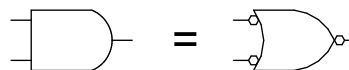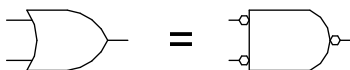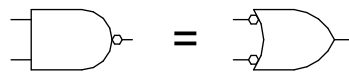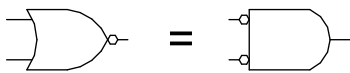


push bubbles or introduce in pairs or remove pairs:

$$(x')' = x.$$


NAND-NAND & NOR-NOR Networks

- Mapping from AND/OR to NAND/NAND

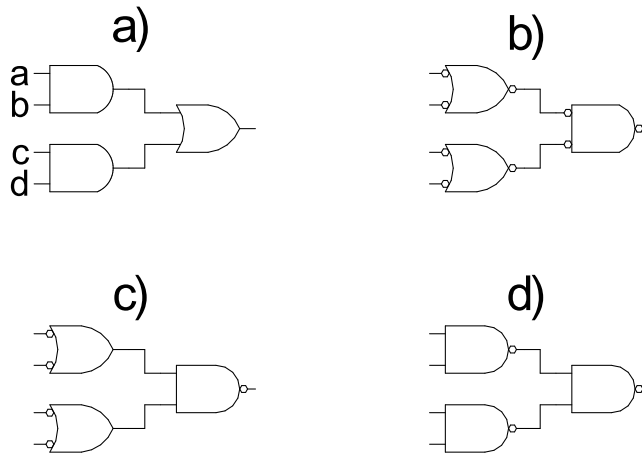


NAND-NAND & NOR-NOR Networks

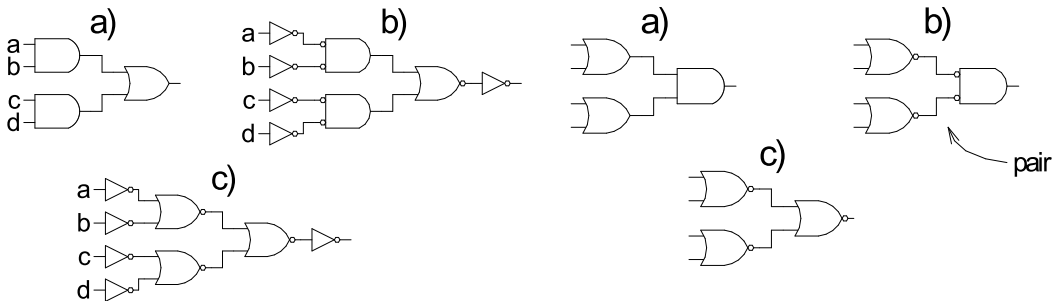- Mapping AND/OR to NOR/NOR
- Mapping OR/AND to NOR/NOR



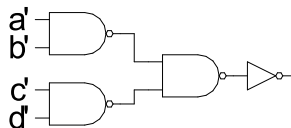
- OR/AND to NAND/NAND (by symmetry with above)




Multi-level Networks

Convert to NANDs:

$$F = a(b + cd) + bc'$$

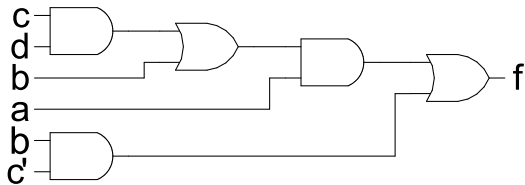

(note fanout)



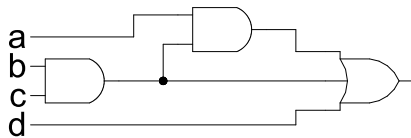


EXOR Function

Parity, addition mod 2

$$x \oplus y = x'y + xy'$$

x	y	xor	xnor
0	0	0	1
0	1	1	0
1	0	1	0
1	1	0	1

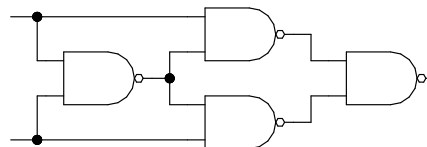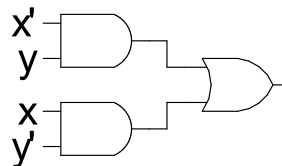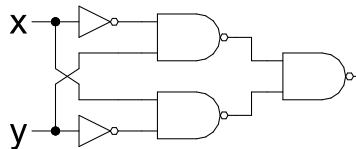

Another approach:

