

CS 61C: Great Ideas in Computer Architecture *Building Blocks for Datapaths*

Instructor:

Randy H. Katz

<http://inst.eecs.Berkeley.edu/~cs61c/fa13>

10/27/13

Fall 2013 -- Lecture #18

1

You are Here!

Software | *Hardware*

- **Parallel Requests**
Assigned to computer
e.g., Search "Katz"
- **Parallel Threads**
Assigned to core
e.g., Lookup, Ads
- **Parallel Instructions**
>1 instruction @ one time
e.g., 5 pipelined instructions
- **Parallel Data**
>1 data item @ one time
e.g., Add of 4 pairs of words
- **Hardware descriptions**
All gates @ one time
- **Programming Languages**


Harness Parallelism & Achieve High Performance

10/27/13

Fall 2013 -- Lecture #18

2

Levels of Representation/ Interpretation

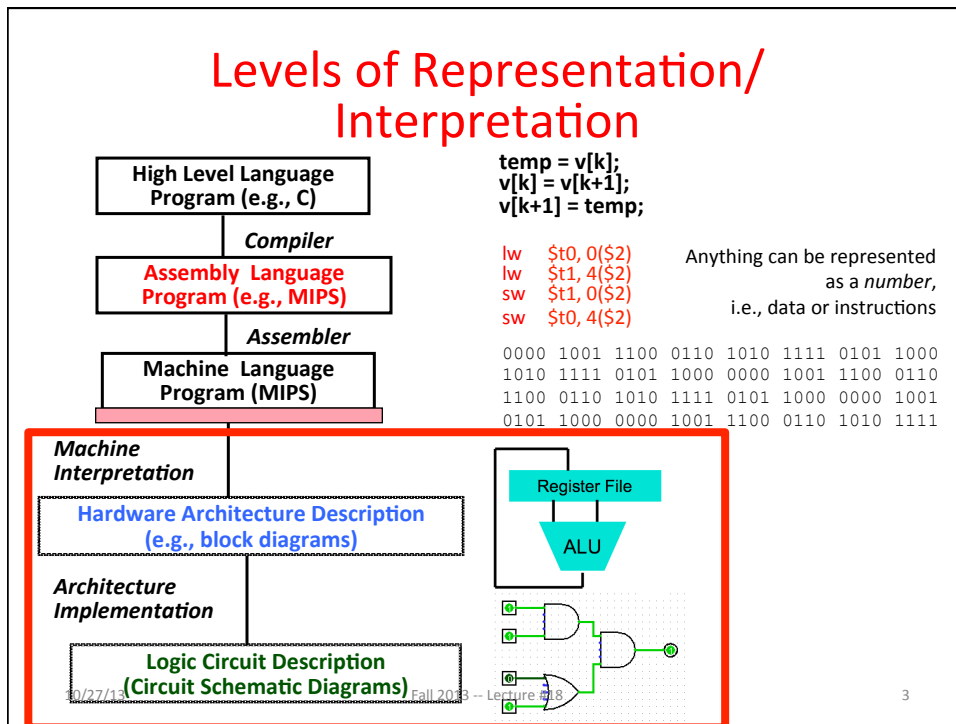

Agenda

- Timing and State Machines
- Datapath Elements: Mux + ALU
- MIPS-lite Datapath
- CPU Timing
- MIPS-lite Control
- And, in Conclusion, ...

Agenda


- Timing and State Machines
- Datapath Elements: Mux + ALU
- MIPS-lite Datapath
- CPU Timing
- MIPS-lite Control
- And, in Conclusion, ...

10/29/13

Fall 2013 -- Lecture #18

5

Last Time: Summation Circuit

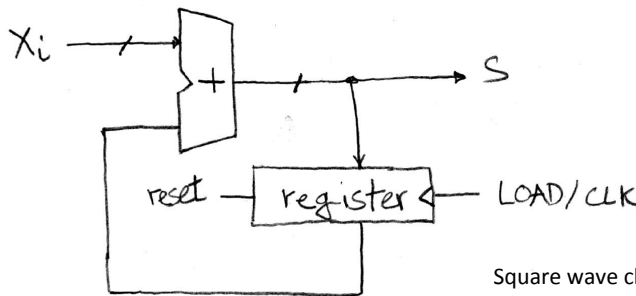

Register is used to hold up the transfer of data to adder

Square wave clock sets when things change

Rough timing ...

High (1)
Low (0)
LOAD/CLK
S
High (1)
Low (0)
Xi
High (1)
Low (0)
Time


Rounded Rectangle per clock means could be 1 or 0
Xi must be ready **before** clock edge due to adder delay

10/29/13

Fall 2013 -- Lecture #18

6

Register Internals

 

- n instances of a “Flip-Flop”
- Flip-flop name because the output flips and flops between 0 and 1
- D is “data input”, Q is “data output”
- Also called “D-type Flip-Flop”

10/29/13

Fall 2013 -- Lecture #18

7

Camera Analogy Timing Terms

- Want to take a portrait – timing right before and after taking picture
- *Set up time* – don’t move since about to take picture (open camera shutter)
- *Hold time* – need to hold still after shutter opens until camera shutter closes
- *Time click to data* – time from open shutter until can see image on output (viewfinder)

10/29/13

Fall 2013 -- Lecture #18

8

Hardware Timing Terms

- **Setup Time:** when the input must be stable *before* the edge of the CLK
- **Hold Time:** when the input must be stable *after* the edge of the CLK
- **“CLK-to-Q” Delay:** how long it takes the output to change, measured from the edge of the CLK


10/29/13

Fall 2013 -- Lecture #18

9

FSM Maximum Clock Frequency

 - What is the maximum frequency of this circuit?



Hint:
Frequency = 1/Period

Max Delay = Setup Time + CLK-to-Q Delay + CL Delay


10/29/13

Fall 2013 -- Lecture #18

10

Another Great (Theory) Idea: Finite State Machines (FSM)

 - You may have seen FSMs in other classes (e.g., CS70)
- Same basic idea
- Function can be represented with a "state transition diagram"
- With combinational logic and registers, any FSM can be implemented in hardware




10/29/13

Fall 2013 -- Lecture #18


11

 Example: 3 Ones FSM

FSM to detect the occurrence of 3 consecutive 1's in the Input



Draw the FSM ...

 

Assume state transitions are controlled by the clock: On each clock cycle the machine checks the inputs and moves to a new state and produces a new output ...

10/29/13

Fall 2013 -- Lecture #18

12

Hardware Implementation of FSM

Register needed to hold a representation of the machine's state.
Unique bit pattern for each state.

Combinational logic circuit is used to implement a function maps from *present state (PS)* and *input* to *next state (NS)* and *output*.


The register is used to break the feedback path between Next State (NS) and Prior State (PS), controlled by the clock

10/29/13

Fall 2013 -

Hardware for FSM: Combinational Logic

 Can look at its functional specification, truth table form




Truth table ...

PS	Input	NS	Output
00	0	00	0
00	1	01	0
01	0	00	0
01	1	10	0
10	0	00	0
10	1	00	1

10/29/13

Fall 2013 -- Lecture #18

14

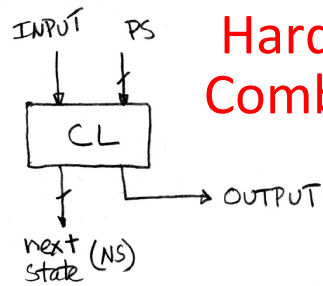

Hardware for FSM: Combinational Logic


Truth table ...

PS	Input	NS	Output
00	0	00	0
00	1	01	0
01	0	00	0
01	1	10	0
10	0	00	0
10	1	00	1

10/29/13

Fall 2013 -- Lecture #18

15

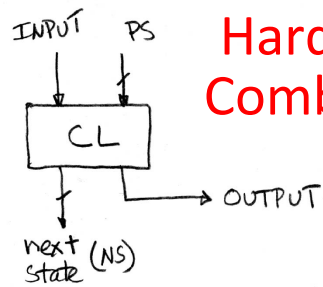

Hardware for FSM: Combinational Logic

Alternative Truth Table format: list only cases where value is a 1. Then restate as logic equations using PS1, PS0, Input

Truth table ...


PS	Input	NS	Output
00	0	00	0
00	1	01	0
01	0	00	0
01	1	10	0
10	0	00	0
10	1	00	1

10/29/13

Fall 2013 -- Lecture #18

16

Hardware for FSM: Combinational Logic

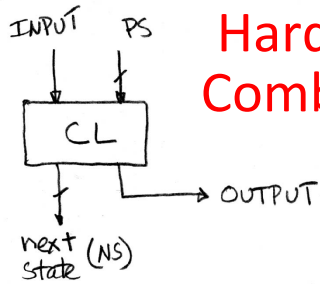

Alternative Truth Table format: list only cases where value is a 1. Then restate as logic equations using PS1, PS0, Input

NS bit 0 is 1

PS	Input
00	1

NS bit 1 is 1

PS	Input
01	1

Output is 1


PS	Input
10	1

Truth table ...

PS	Input	NS	Output
00	0	00	0
00	1	01	0
01	0	00	0
01	1	10	0
10	0	00	0
10	1	00	1

10/29/13 Fall 2013 -- Lecture #18 17

Hardware for FSM: Combinational Logic

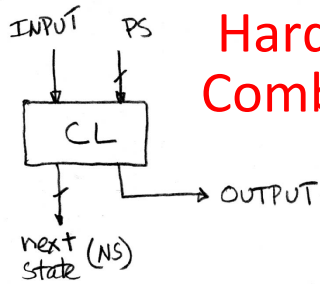

Alternative Truth Table format: list only cases where value is a 1. Then restate as logic equations using PS1, PS0, Input

NS bit 0 is 1

PS	Input
00	1

NS bit 1 is 1

PS	Input
01	1

Output is 1

PS	Input
10	1

- $NS0 = \overline{PS1} \cdot \overline{PS0} \cdot Input$
- $NS0 = \sim PS1 \cdot \sim PS0 \cdot Input$
- $NS1 = \overline{PS1} \cdot PS0 \cdot Input$
- $NS1 = \sim PS1 \cdot PS0 \cdot Input$
- $Output = PS1 \cdot \overline{PS0} \cdot Input$
- $Output = PS1 \cdot \sim PS0 \cdot Input$

Truth table ...

PS	Input	NS	Output
00	0	00	0
00	1	01	0
01	0	00	0
01	1	10	0
10	0	00	0
10	1	00	1

10/29/13 Fall 2013 -- Lecture #18 18

Administrivia

10/29/13

Fall 2013 -- Lecture #18

19

Agenda


- Timing and State Machines
- **Datapath Elements: Mux + ALU**
- MIPS-lite Datapath
- CPU Timing
- MIPS-lite Control
- And, in Conclusion, ...

10/29/13

Fall 2013 -- Lecture #18

20

Design Hierarchy

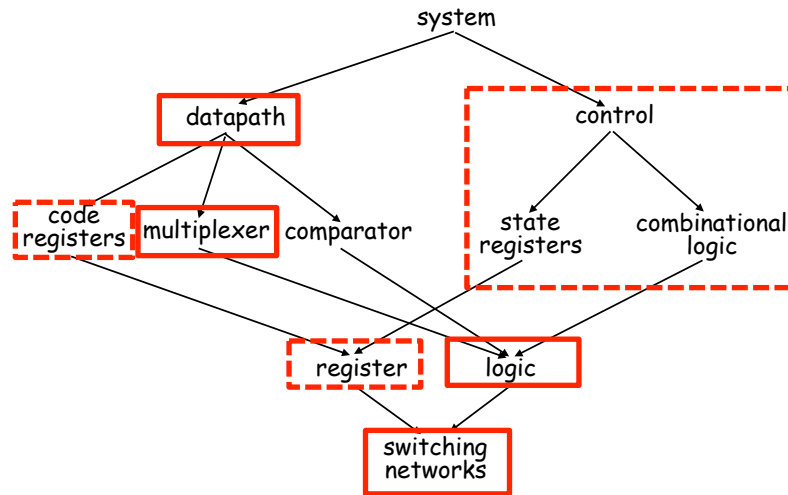


10/27/13

Fall 2013 -- Lecture #18

21

Conceptual MIPS Datapath

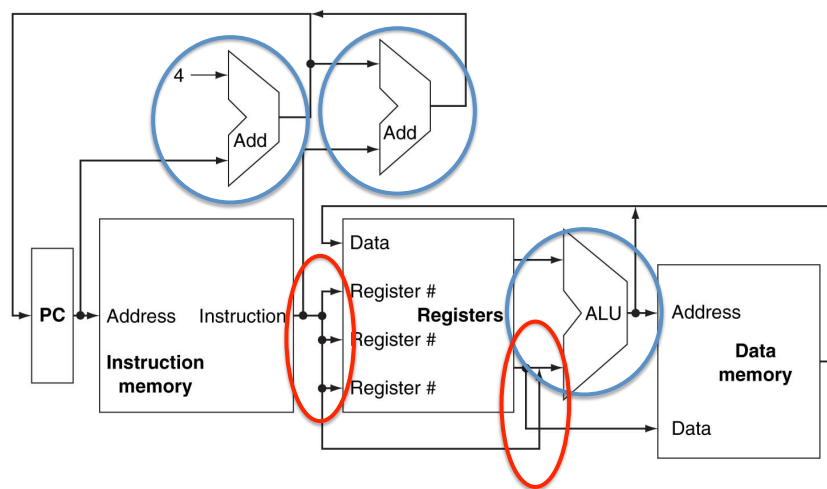


10/27/13

Fall 2013 -- Lecture #18

22

 Data Multiplexer (e.g., 2-to-1 x n-bit-wide)




10/27/13

Fall 2013 -- Lecture #18

23

N Instances of 1-bit-Wide Mux

 

$$\begin{aligned}
 c &= \bar{s}a\bar{b} + \bar{s}ab + s\bar{a}b + sab \\
 &= \bar{s}(a\bar{b} + ab) + s(\bar{a}b + ab) \\
 &= \bar{s}(a(\bar{b} + b)) + s((\bar{a} + a)b) \\
 &= \bar{s}(a(1) + s((1)b) \\
 &= \bar{s}a + sb
 \end{aligned}$$




s	ab	c
0	00	0
0	01	0
0	10	1
0	11	1
1	00	0
1	01	1
1	10	0
1	11	1

10/27/13

Fall 2013 -- Lecture #18

24

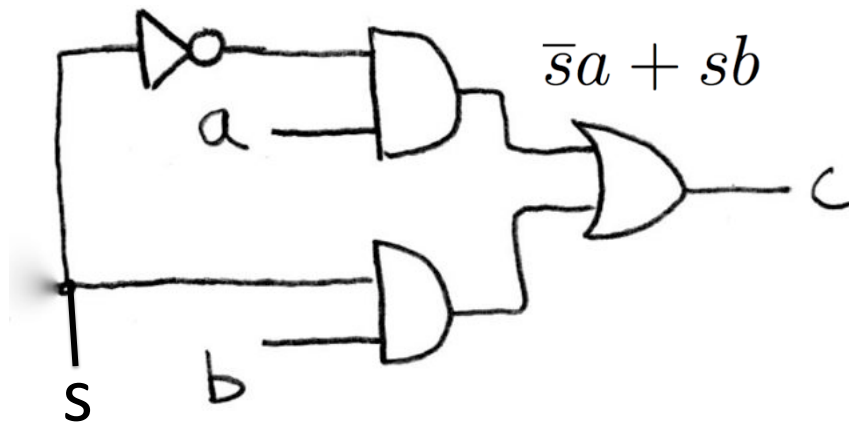How Do We Build a 1-bit-Wide Mux (in Logisim)?




10/27/13

Fall 2013 -- Lecture #18

25

4-to-1 Multiplexer

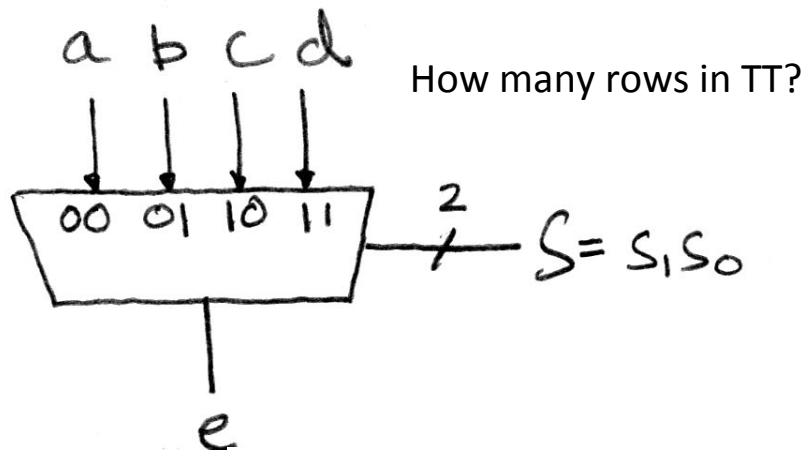


$$e = \bar{s}_1 \bar{s}_0 a + \bar{s}_1 s_0 b + s_1 \bar{s}_0 c + s_1 s_0 d$$

10/27/13

Fall 2013 -- Lecture #18

26

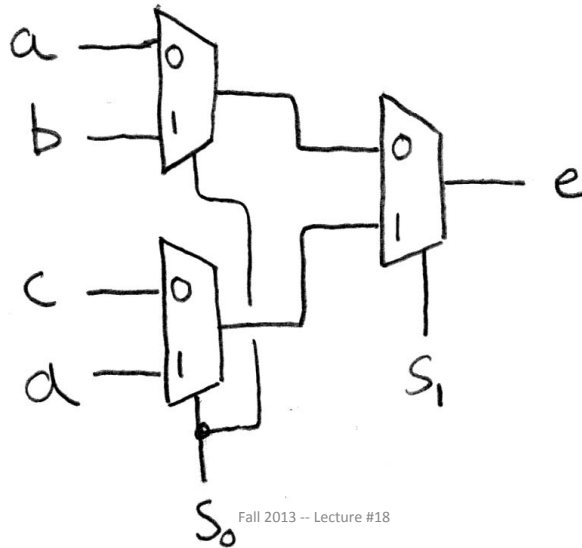Alternative Hierarchical Approach (in Logisim)




10/27/13

Fall 2013 -- Lecture #18

27

Logisim

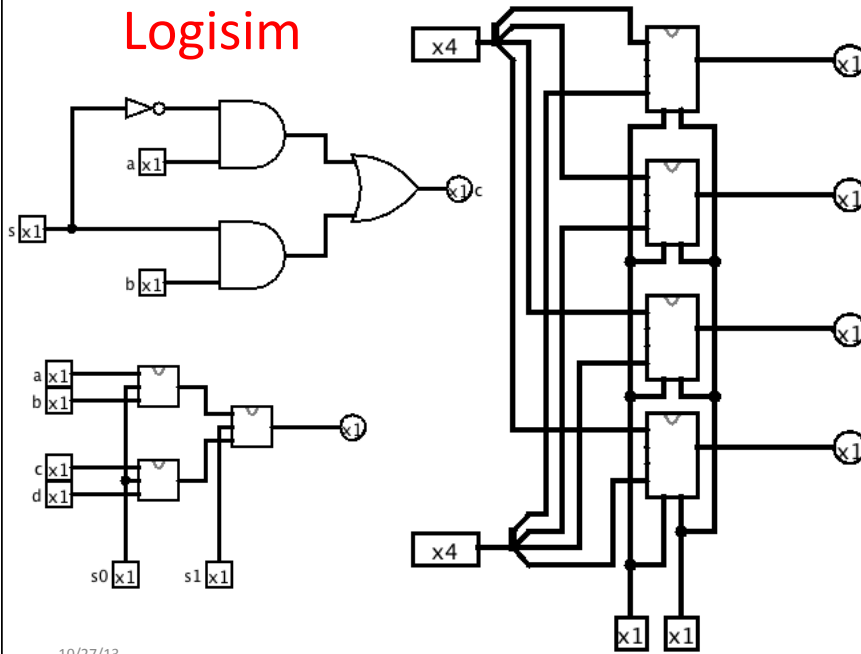

10/27/13

28

Subcircuits


- Subcircuit: Logisim equivalent of procedure or method
 - Every project is a hierarchy of subcircuits

10/27/13

Fall 2013 -- Lecture #18

29

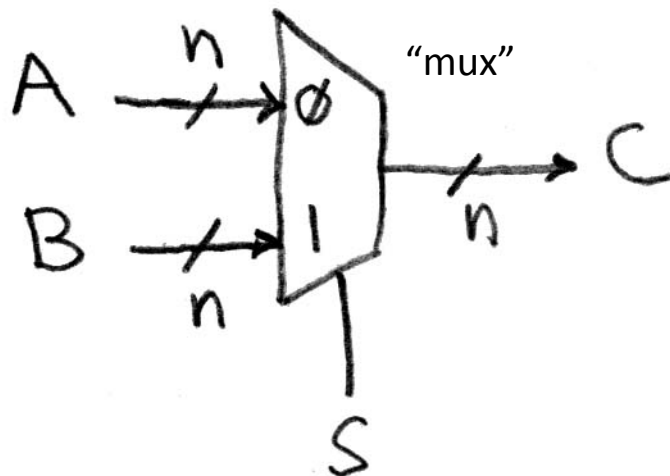N-bit-wide Data Multiplexer (in Logisim + tunnel)




10/27/13

Fall 2013 -- Lecture #18

30

Arithmetic and Logic Unit

 - Most processors contain a special logic block called “Arithmetic and Logic Unit” (ALU)
- We’ll show you an easy one that does ADD, SUB, bitwise AND, bitwise OR




when $S=00$, $R=A+B$
 when $S=01$, $R=A-B$
 when $S=10$, $R=A \text{ AND } B$
 when $S=11$, $R=A \text{ OR } B$

10/27/13

Fall 2013 -- Lecture #18

31

Simple ALU

 

10/27/13

Fall 2013 -- Lecture #18

32

Adder/Subtractor: One-bit adder Least Significant Bit

	a_3	a_2	a_1	a_0
+	b_3	b_2	b_1	b_0
	s_3	s_2	s_1	s_0

a_0	b_0	s_0	c_1
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$s_0 = a_0 \text{ XOR } b_0$$

$$c_1 = a_0 \text{ AND } b_0$$

Adder/Subtractor: One-bit adder (1/2)


	a_3	a_2	a_1	a_0
+	b_3	b_2	b_1	b_0
	s_3	s_2	s_1	s_0

...	a_i	b_i	c_i	s_i	c_{i+1}
	0	0	0	0	0
	0	0	1	1	0
	0	1	0	1	0
	0	1	1	0	1
	1	0	0	1	0
	1	0	1	0	1
	1	1	0	0	1
	1	1	1	1	1

$$s_i =$$

$$c_{i+1} =$$

Adder/Subtractor: One-bit Adder (2/2)

 

$$s_i = \text{XOR}(a_i, b_i, c_i)$$

$$c_{i+1} = \text{MAJ}(a_i, b_i, c_i) = a_i b_i + a_i c_i + b_i c_i$$


10/27/13

Fall 2013 -- Lecture #18

35

N x 1-bit Adders \Rightarrow 1 N-bit Adder

Connect Carry Out $i-1$ to Carry in i :

 


10/27/13

Fall 2013 -- Lecture #18

36

Twos Complement Adder/Subtractor

 

10/27/13

Fall 2013 -- Lecture #18

37

Critical Path

- When setting clock period in synchronous systems, must allow for worst case
- Path through combinational logic that is worst case called “critical path”
 - Can be estimated by number of “gate delays”:
 - Number of gates must go through in worst case
- Idea: Doesn't matter if speedup other paths if don't improve the critical path
- What might critical path of ALU?

10/27/13

Fall 2013 -- Lecture #18

38

Agenda

- Multiplexer
- ALU Design
- **MIPS-lite Datapath**
- CPU Timing
- MIPS-lite Control
- And, in Conclusion, ...

10/27/13

Fall 2013 -- Lecture #18

39

Agenda

- Timing and State Machines
- Datapath Elements: Mux + ALU
- **MIPS-lite Datapath**
- CPU Timing
- MIPS-lite Control
- And, in Conclusion, ...

10/29/13


Fall 2013 -- Lecture #18

40

Processor Design Process

- Five steps to design a processor:

 1. Analyze instruction set → datapath requirements
2. Select set of datapath components & establish clock methodology
3. Assemble datapath meeting the requirements
4. Analyze implementation of each instruction to determine setting of control points that effects the register transfer.
5. Assemble the control logic
 - Formulate Logic Equations
 - Design Circuits



10/27/13

Fall 2013 -- Lecture #18

41

The MIPS-lite Subset

- **ADDU and SUBU**

31	26	21	16	11	6	0						
<table style="width: 100%; border-collapse: collapse;"> <tr> <td style="border: 1px solid black; text-align: center; width: 12.5%;">op</td> <td style="border: 1px solid black; text-align: center; width: 12.5%;">rs</td> <td style="border: 1px solid black; text-align: center; width: 12.5%;">rt</td> <td style="border: 1px solid black; text-align: center; width: 12.5%;">rd</td> <td style="border: 1px solid black; text-align: center; width: 12.5%;">shamt</td> <td style="border: 1px solid black; text-align: center; width: 12.5%;">funct</td> </tr> </table>							op	rs	rt	rd	shamt	funct
op	rs	rt	rd	shamt	funct							
	6 bits	5 bits	5 bits	5 bits	5 bits	6 bits						

 - addu rd,rs,rt
 - subu rd,rs,rt
- **OR Immediate:**

31	26	21	16	0					
<table style="width: 100%; border-collapse: collapse;"> <tr> <td style="border: 1px solid black; text-align: center; width: 12.5%;">op</td> <td style="border: 1px solid black; text-align: center; width: 12.5%;">rs</td> <td style="border: 1px solid black; text-align: center; width: 12.5%;">rt</td> <td colspan="2" style="border: 1px solid black; text-align: center;">immediate</td> </tr> </table>					op	rs	rt	immediate	
op	rs	rt	immediate						
	6 bits	5 bits	5 bits	16 bits					

 - ori rt,rs,imm16
- **LOAD and STORE Word**

31	26	21	16	0					
<table style="width: 100%; border-collapse: collapse;"> <tr> <td style="border: 1px solid black; text-align: center; width: 12.5%;">op</td> <td style="border: 1px solid black; text-align: center; width: 12.5%;">rs</td> <td style="border: 1px solid black; text-align: center; width: 12.5%;">rt</td> <td colspan="2" style="border: 1px solid black; text-align: center;">immediate</td> </tr> </table>					op	rs	rt	immediate	
op	rs	rt	immediate						
	6 bits	5 bits	5 bits	16 bits					

 - lw rt,rs,imm16
 - sw rt,rs,imm16
- **BRANCH:**

31	26	21	16	0					
<table style="width: 100%; border-collapse: collapse;"> <tr> <td style="border: 1px solid black; text-align: center; width: 12.5%;">op</td> <td style="border: 1px solid black; text-align: center; width: 12.5%;">rs</td> <td style="border: 1px solid black; text-align: center; width: 12.5%;">rt</td> <td colspan="2" style="border: 1px solid black; text-align: center;">immediate</td> </tr> </table>					op	rs	rt	immediate	
op	rs	rt	immediate						
	6 bits	5 bits	5 bits	16 bits					

 - beq rs,rt,imm16

10/27/13

Fall 2013 -- Lecture #18

42

Register Transfer Language (RTL)

- RTL gives the meaning of the instructions

```
{op , rs , rt , rd , shamt , funct} ← MEM[ PC ]
```

```
{op , rs , rt , Imm16} ← MEM[ PC ]
```

- All start by fetching the instruction

Inst Register Transfers

```
ADDU R[rd] ← R[rs] + R[rt]; PC ← PC + 4
```

```
SUBU R[rd] ← R[rs] - R[rt]; PC ← PC + 4
```

```
ORI R[rt] ← R[rs] | zero_ext(Imm16); PC ← PC + 4
```

```
LOAD R[rt] ← MEM[ R[rs] + sign_ext(Imm16) ]; PC ← PC + 4
```

```
STORE MEM[ R[rs] + sign_ext(Imm16) ] ← R[rt]; PC ← PC + 4
```

```
BEQ if ( R[rs] == R[rt] )
     then PC ← PC + 4 + (sign_ext(Imm16) || 00)
     else PC ← PC + 4
```

10/27/13

Fall 2013 -- Lecture #18

43

Step 1: Requirements of the Instruction Set


- Memory (MEM)
 - Instructions & data (will use one for each: really caches)
- Registers (R: 32 x 32)
 - Read *rs*
 - Read *rt*
 - Write *rt* or *rd*
- PC
- Extender (sign/zero extend)
- Add/Sub/OR unit for operation on register(s) or extended immediate
- Add 4 (+ maybe extended immediate) to PC
- Compare if registers equal?

10/27/13

Fall 2013 -- Lecture #18

44

Generic Steps of Datapath

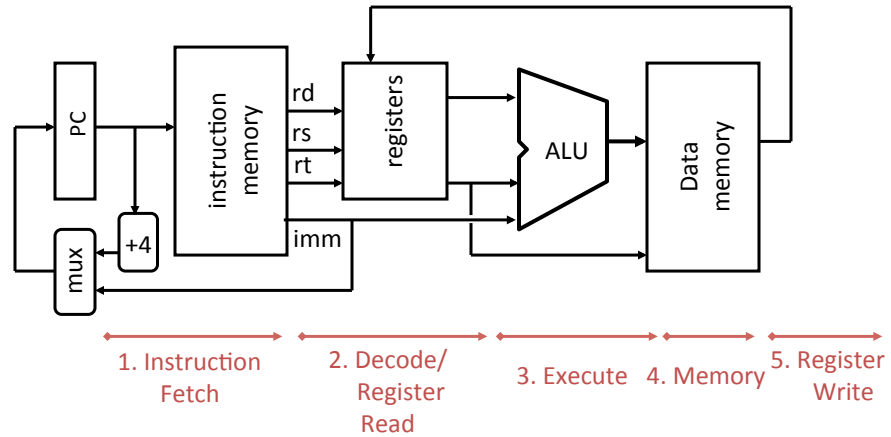


10/27/13

Fall 2013 -- Lecture #18

45

Step 2: Components of the Datapath

 - Combinational Elements
- State Elements + Clocking Methodology
- Building Blocks



10/27/13

Fall 2013 -- Lecture #18

46

ALU Needs for MIPS-lite + Rest of MIPS

- Addition, subtraction, logical OR, ==:


```
ADDU  R[rd] = R[rs] + R[rt]; ...
SUBU  R[rd] = R[rs] - R[rt]; ...
ORI   R[rt] = R[rs] | zero_ext(Imm16)...
BEQ   if ( R[rs] == R[rt] )...
```
- Test to see if output == 0 for any ALU operation gives == test. How?
- P&H also adds AND, Set Less Than (1 if $A < B$, 0 otherwise)
- ALU from Appendix C, section C.5


10/27/13

Fall 2013 -- Lecture #18

47

Storage Element: Idealized Memory

- Memory (idealized)
 - One input bus: Data In
 - One output bus: Data Out
- Memory word is found by:
 - Address selects the word to put on Data Out
 - Write Enable = 1: address selects the memory word to be written via the Data In bus
- Clock input (CLK)
 - CLK input is a factor ONLY during write operation
 - During read operation, behaves as a combinational logic block: Address valid \Rightarrow Data Out valid after “access time”

 


10/27/13

Fall 2013 -- Lecture #18

48

Storage Element: Register (Building Block)

 - Similar to D Flip Flop except
 - N-bit input and output
 - Write Enable input
- Write Enable:
 - Negated (or deasserted) (0): Data Out will not change
 - Asserted (1): Data Out will become Data In on rising edge of clock




10/27/13

Fall 2013 -- Lecture #18

49

Storage Element: Register File

- Register File consists of 32 registers:
 - Two 32-bit output busses: busA and busB
 - One 32-bit input bus: busW
- Register is selected by:
 - RA (number) selects the register to put on busA (data)
 - RB (number) selects the register to put on busB (data)
 - RW (number) selects the register to be written via busW (data) when Write Enable is 1
- Clock input (clk)
 - Clk input is a factor ONLY during write operation
 - During read operation, behaves as a combinational logic block:
 - RA or RB valid \Rightarrow busA or busB valid after "access time."

 


10/27/13

Fall 2013 -- Lecture #18

50

Step 3: Assemble DataPath Meeting Requirements

 - Register Transfer Requirements
⇒ Datapath Assembly
- Instruction Fetch
- Read Operands and Execute Operation
- Common RTL operations
 - Fetch the Instruction: $mem[PC]$
 - Update the program counter:
 - Sequential Code: $PC \leftarrow PC + 4$
 - Branch and Jump: $PC \leftarrow \text{“something else”}$




10/27/13

Fall 2013 -- Lecture #18


51

Step 3: Add & Subtract

 - $R[rd] = R[rs] \text{ op } R[rt]$ (`addu rd, rs, rt`)
 - Ra, Rb, and Rw come from instruction's Rs, Rt, and Rd fields



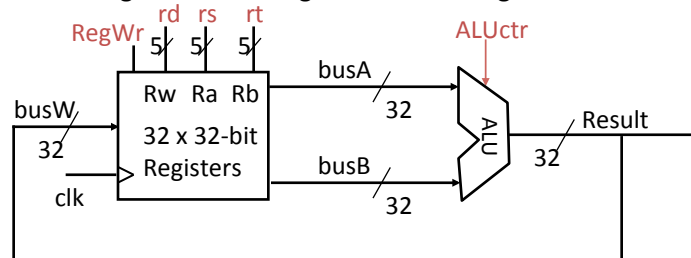- ALUctr and RegWr: control logic after decoding the instruction



- ... Already defined the register file & ALU

10/27/13

Fall 2013 -- Lecture #18

52

Agenda


- Timing and State Machines
- Datapath Elements: Mux + ALU
- MIPS-lite Datapath
- **CPU Timing**
- MIPS-lite Control
- And, in Conclusion, ...

10/29/13

Fall 2013 -- Lecture #18

53

Clocking Methodology

 


- Storage elements clocked by same edge
- “**Critical path**” (longest path through logic) determines length of clock period
- Have to allow for Clock-to-Q and Setup Times too
- This lecture (and P&H sections) 4.3-4.4 do whole instruction in 1 clock cycle for pedagogic reasons
 - Project 4 will do it in 2 clock cycles via simple pipelining
 - Soon explain pipelining and use 5 clock cycles per instruction

10/27/13

Fall 2013 -- Lecture #18


54

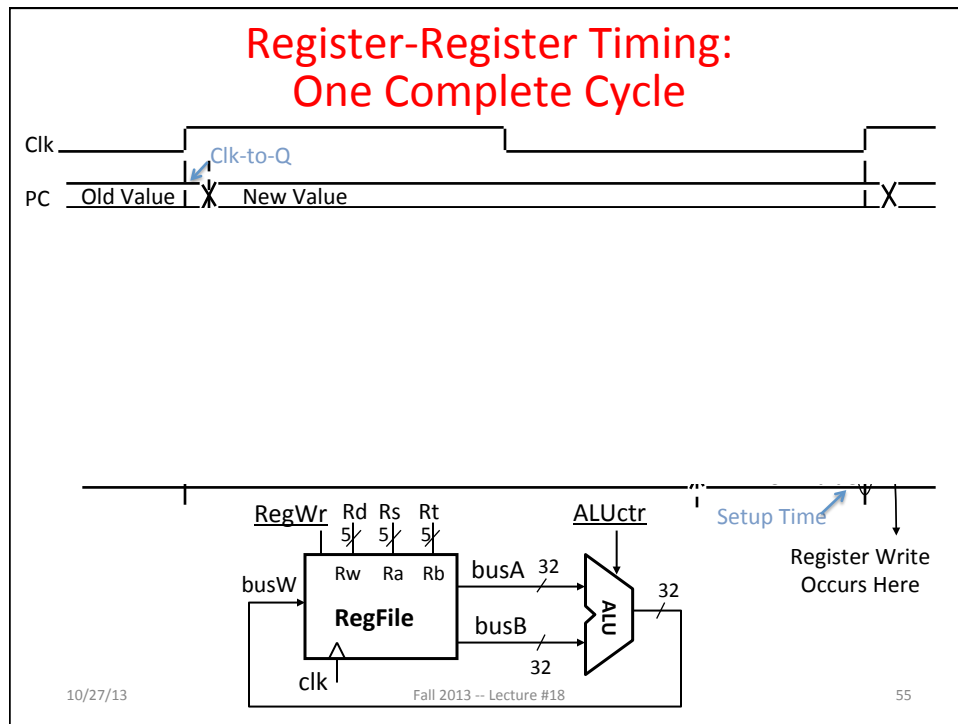

Agenda


- Timing and State Machines
- Datapath Elements: Mux + ALU
- MIPS-lite Datapath
- CPU Timing
- **MIPS-lite Control**
- And, in Conclusion, ...

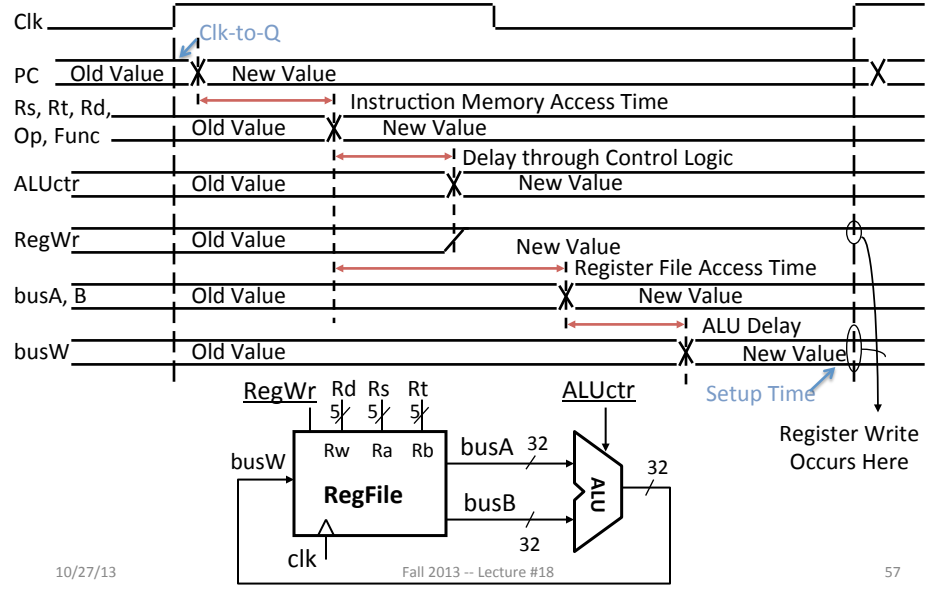Register-Register Timing: One Complete Cycle




Logical Operations with Immediate

 - $R[rt] = R[rs] \text{ op } \text{ZeroExt}[\text{imm16}]$




 **But we're writing to Rt register??
And immediate ALU input??**



Logical Operations with Immediate

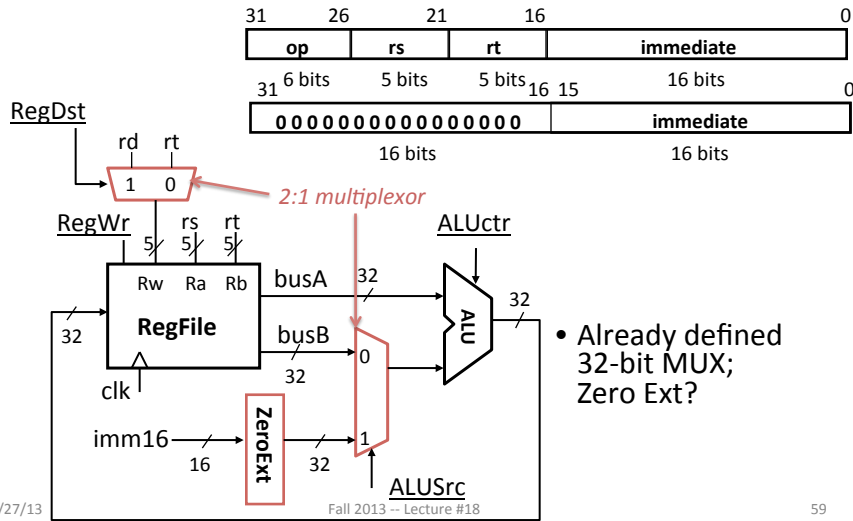
- $R[rt] = R[rs] \text{ op ZeroExt}[imm16]$



Load Operations

- $R[rt] = \text{Mem}[R[rs] + \text{SignExt}[imm16]]$

Example: `lw rt, rs, imm16`

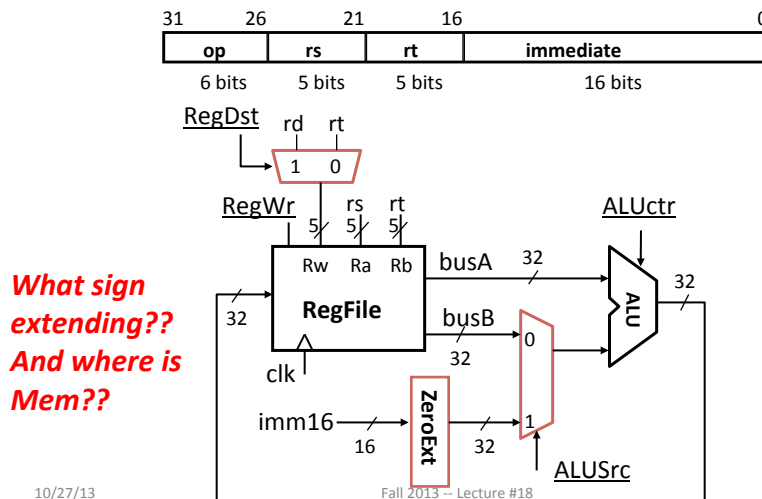


*What sign extending??
And where is Mem??*


Load Operations

- $R[rt] = \text{Mem}[R[rs] + \text{SignExt}[\text{imm16}]]$

Example: `lw rt, rs, imm16`

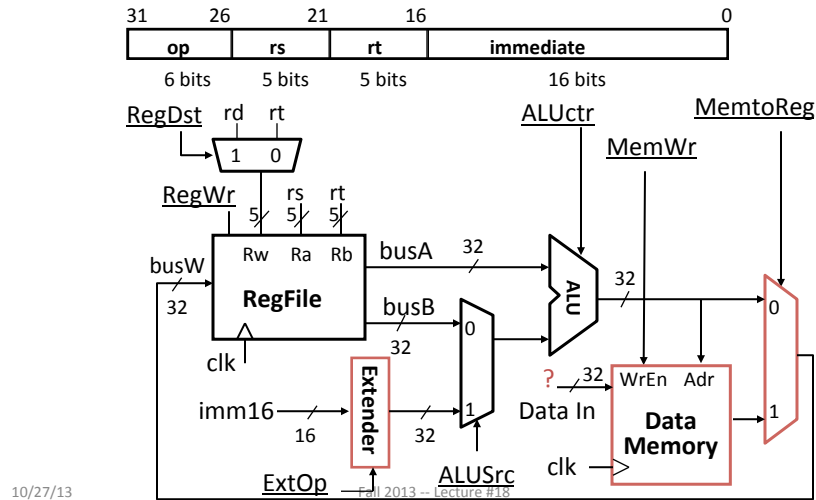

RTL: The Add Instruction

 


`add rd, rs, rt`

- $\text{MEM}[\text{PC}]$ Fetch the instruction from memory
- $R[\text{rd}] = R[\text{rs}] + R[\text{rt}]$ The actual operation
- $\text{PC} = \text{PC} + 4$ Calculate the next instruction's address

Instruction Fetch Unit at Beginning of Add

 - Fetch the instruction from Instruction memory:
 $\text{Instruction} = \text{MEM}[\text{PC}]$
 – same for all instructions




10/27/13


Fall 2013 -- Lecture #18

63

Single Cycle Datapath during Add

 
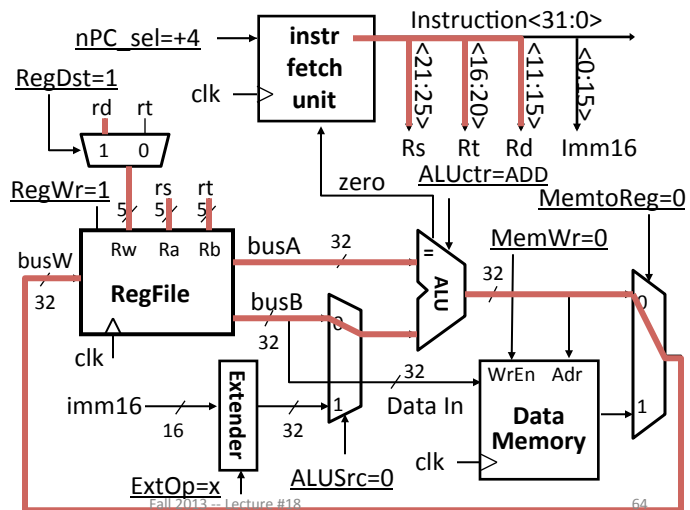
$$R[\text{rd}] = R[\text{rs}] + R[\text{rt}]$$




10/27/13

Fall 2013 -- Lecture #18

64

Instruction Fetch Unit at End of Add

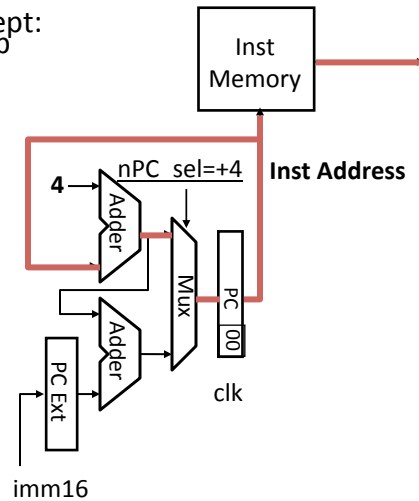- PC = PC + 4
 - Same for all instructions except: Branch and Jump




10/27/13


Fall 2013 -- Lecture #18

65

 Single Cycle Datapath during OR Immediate



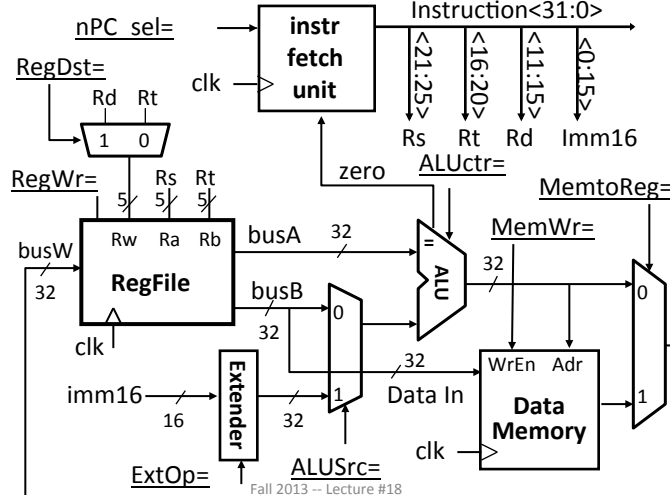- $R[rt] = R[rs] \text{ OR } \text{ZeroExt}[Imm16]$




10/27/13

Fall 2013 -- Lecture #18

66

Single Cycle Datapath during OR Immediate

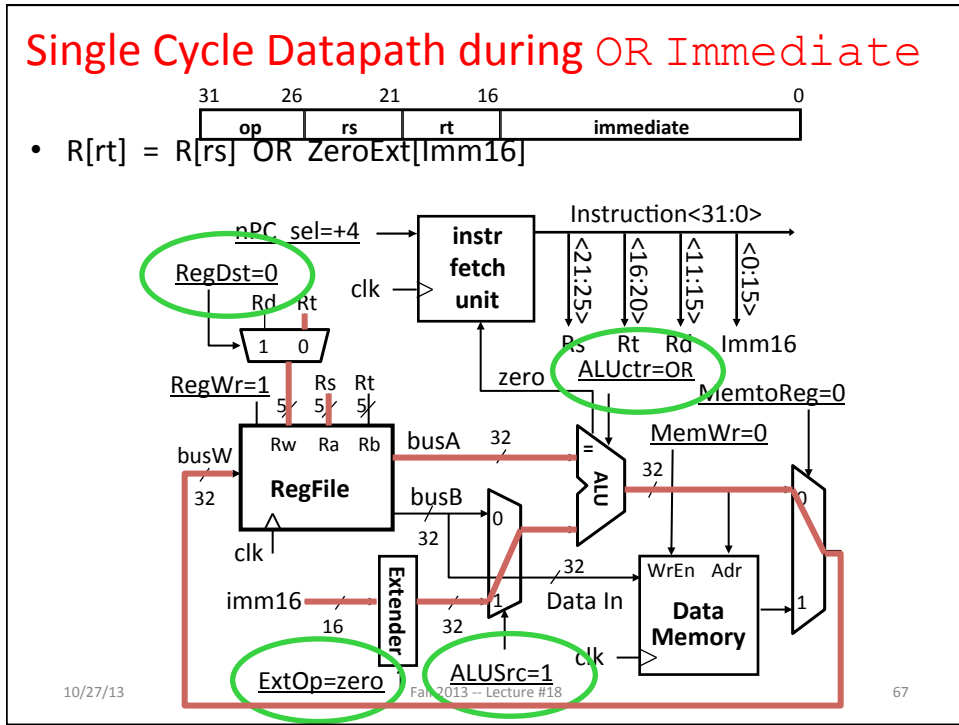
- $R[rt] = R[rs] \text{ OR } \text{ZeroExt}[Imm16]$




Single Cycle Datapath during Load

- $R[rt] = \text{Data Memory} \{R[rs] + \text{SignExt}[imm16]\}$


[Student Roulette](#)

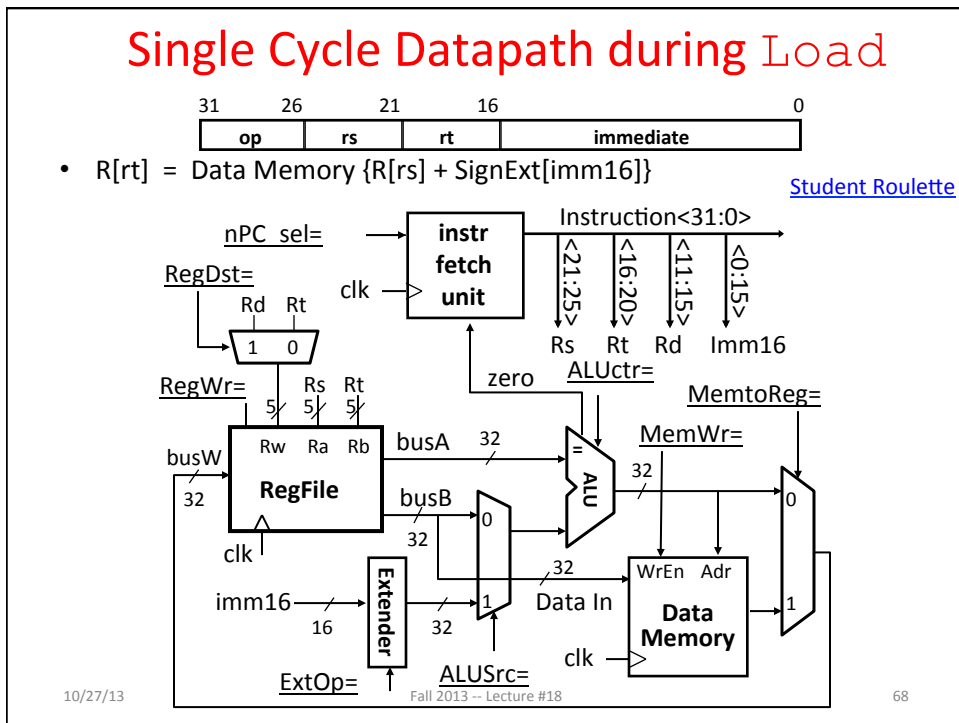

Single Cycle Datapath during Load

 

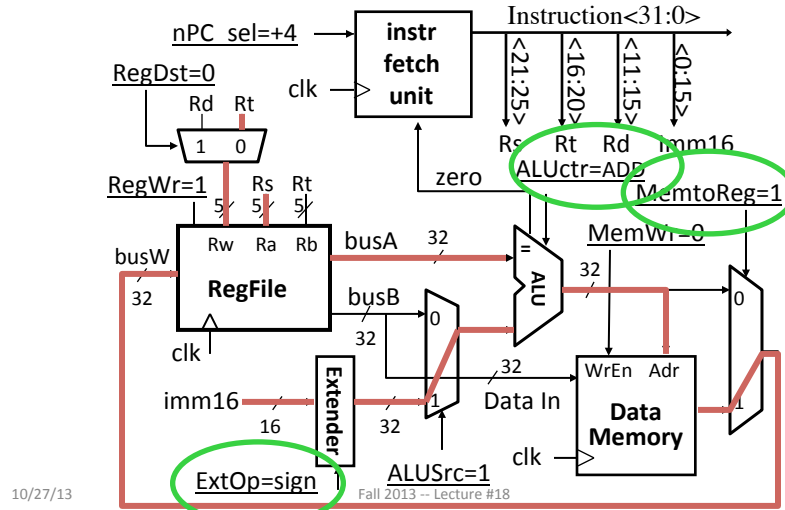- $R[rt] = \text{Data Memory} \{R[rs] + \text{SignExt}[\text{imm16}]\}$




10/27/13


Fall 2013 -- Lecture #18

69

Single Cycle Datapath during Store

 

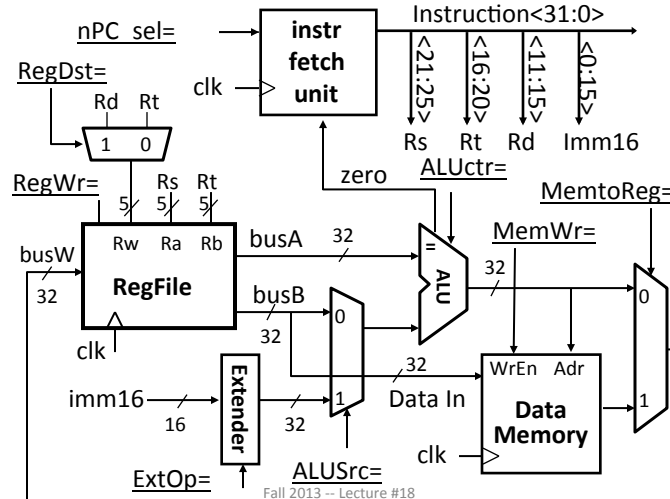- $\text{Data Memory} \{R[rs] + \text{SignExt}[\text{imm16}]\} = R[rt]$




10/27/13


Fall 2013 -- Lecture #18

70

Single Cycle Datapath during Store

 

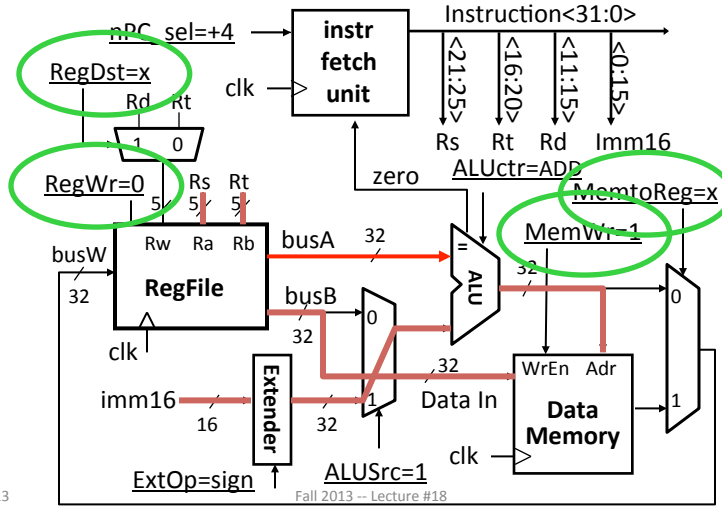- Data Memory $\{R[rs] + \text{SignExt}[imm16]\} = R[rt]$




10/27/13


Fall 2013 -- Lecture #18

71

Single Cycle Datapath during Branch

 

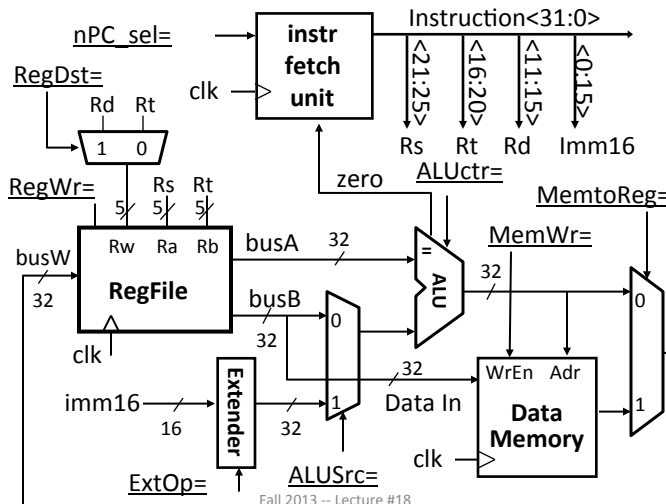- if $(R[rs] - R[rt]) == 0$ then Zero = 1 ; else Zero = 0




10/27/13


Fall 2013 -- Lecture #18

72

Single Cycle Datapath during Branch

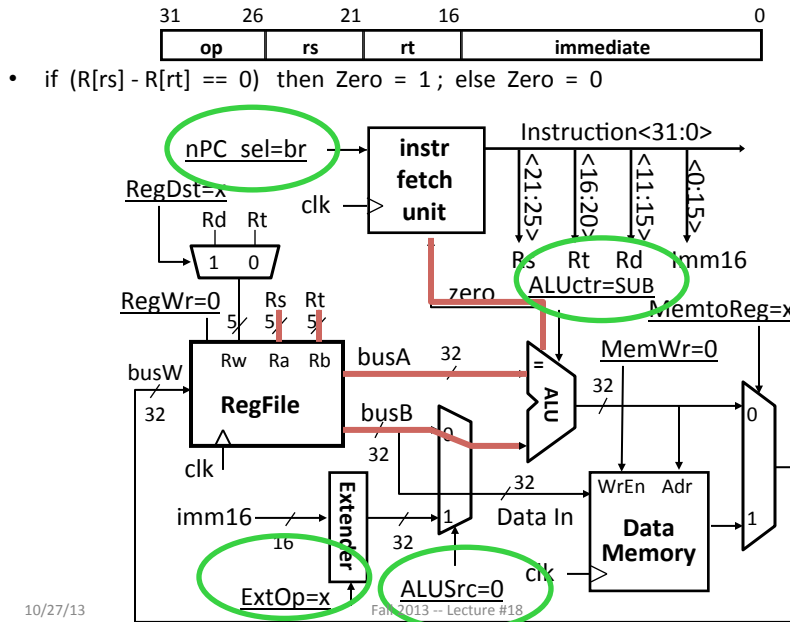


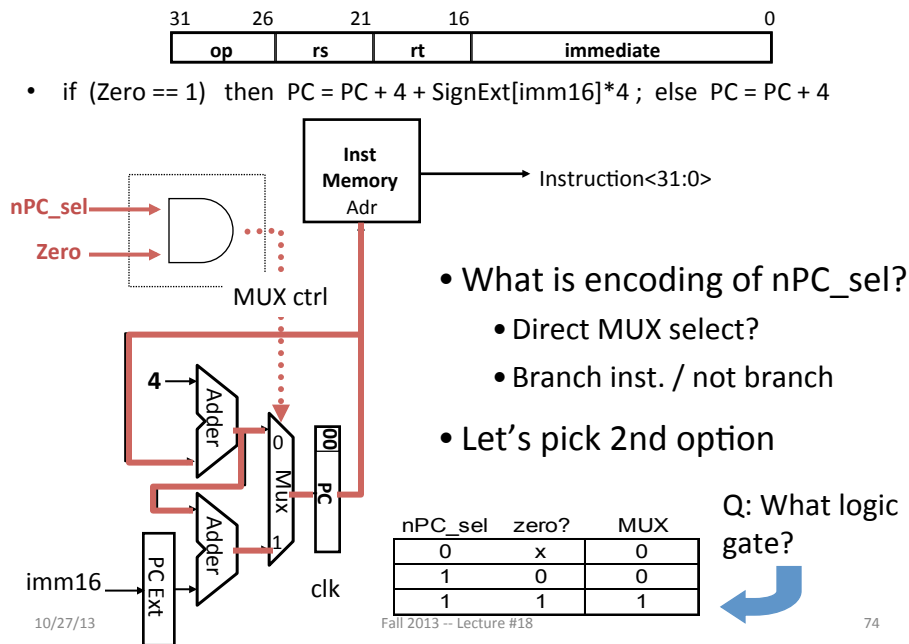Instruction Fetch Unit at the End of Branch



Summary: Datapath's Control Signals

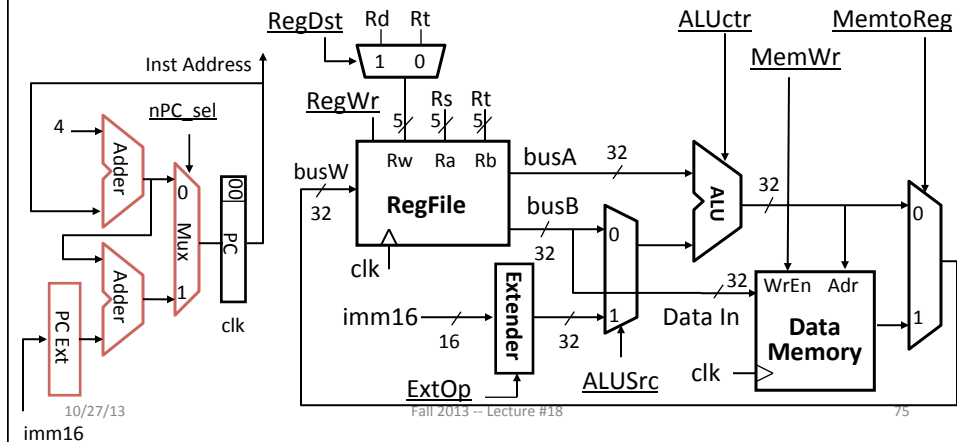- ExtOp: "zero", "sign"
- ALUSrc: 0 \Rightarrow regB;
1 \Rightarrow immed
- ALUctr: "ADD", "SUB", "OR"
- MemWr: 1 \Rightarrow write memory
- MemtoReg: 0 \Rightarrow ALU; 1 \Rightarrow Mem
- RegDst: 0 \Rightarrow "rt"; 1 \Rightarrow "rd"
- RegWr: 1 \Rightarrow write register




Agenda

- Timing and State Machines
- Datapath Elements: Mux + ALU
- MIPS-lite Datapath
- CPU Timing
- MIPS-lite Control
- And, in Conclusion, ...

And. in Conclusion, ... Single-Cycle Processor

- Use muxes to select among input
 - S input bits selects 2^S inputs
 - Each input can be n-bits wide, independent of S
- Can implement muxes hierarchically
- Arithmetic circuits are a kind of combinational logic
- Five steps to processor design:
 1. Analyze instruction set → datapath requirements
 2. Select set of datapath components & establish clock methodology
 3. Assemble datapath meeting the requirements
 4. Analyze implementation of each instruction to determine setting of control points that effects the register transfer.
 5. Assemble the control logic
 - Formulate Logic Equations
 - Design Circuits

 

10/27/13

Fall 2013 -- Lecture #18

77