

CS61C : Machine Structures

Lecture #15: Combinational Logic Blocks



2005-07-14

Andy Carle




Outline

- CL Blocks
- Latches & Flip Flops – A Closer Look




Review (1/3)

 - Use this table and techniques we learned to transform from 1 to another



 (2/3): Circuit & Algebraic Simplification




original circuit

$$\begin{aligned}
 y &= ((ab) + a) + c \\
 &= ab + a + c \\
 &= a(b + 1) + c \\
 &= a(1) + c \\
 &= a + c
 \end{aligned}$$

equation derived from original circuit

algebraic simplification

 

simplified circuit



(3/3): Laws of Boolean Algebra

$x \cdot \bar{x} = 0$	$x + \bar{x} = 1$	complementarity
$x \cdot 0 = 0$	$x + 1 = 1$	laws of 0's and 1's
$x \cdot 1 = x$	$x + 0 = x$	identities
$x \cdot x = x$	$x + x = x$	idempotent law
$x \cdot y = y \cdot x$	$x + y = y + x$	commutativity
$(xy)z = x(yz)$	$(x + y) + z = x + (y + z)$	associativity
$x(y + z) = xy + xz$	$x + yz = (x + y)(x + z)$	distribution
$xy + \bar{x}z = x(y + z) + \bar{x}z$	$(x + y)z = xz + yz$	uniting theorem
$\overline{\overline{x}} = x$	$\overline{(x + y)} = \bar{x} \cdot \bar{y}$	DeMorgan's Law




CL Blocks

- Let's use our skills to build some CL blocks:

- Multiplexer (mux)
- Adder
- ALU



 Data Multiplexor (here 2-to-1, n-bit-wide)




Cal

CS 61C L15 Blocks (7)

A Carlo, Summer 2005 © UCB

N instances of 1-bit-wide mux

 

s	ab	c
0	00	0
0	01	0
0	10	1
0	11	1
1	00	0
1	01	1
1	10	0
1	11	1

$$\begin{aligned}
 c &= \bar{s}a\bar{b} + \bar{s}ab + s\bar{a}b + sab \\
 &= \bar{s}(a\bar{b} + ab) + s(\bar{a}b + ab) \\
 &= \bar{s}(a(\bar{b} + b)) + s((\bar{a} + a)b) \\
 &= \bar{s}(a(1) + s((1)b) \\
 &= \bar{s}a + sb
 \end{aligned}$$


Cal

CS 61C L15 Blocks (8)

A Carlo, Summer 2005 © UCB

How do we build a 1-bit-wide mux?

$$\bar{s}a + sb$$

 


Cal

CS 61C L15 Blocks (9)

A Carlo, Summer 2005 © UCB

4-to-1 Multiplexor?

 


$$e = \bar{s}_1\bar{s}_0a + \bar{s}_1s_0b + s_1\bar{s}_0c + s_1s_0d$$

Cal

CS 61C L15 Blocks (10)

A Carlo, Summer 2005 © UCB

An Alternative Approach

 

Hierarchically!


Cal

CS 61C L15 Blocks (11)

A Carlo, Summer 2005 © UCB

Arithmetic and Logic Unit

 - Most processors contain a logic block called "Arithmetic/Logic Unit" (ALU)
- We'll show you an easy one that does ADD, SUB, bitwise AND, bitwise OR




when S=00, R=A+B
 when S=01, R=A-B
 when S=10, R=A AND B
 when S=11, R=A OR B

Cal

CS 61C L15 Blocks (12)

A Carlo, Summer 2005 © UCB

Our simple ALU

 

Cal

CS 61C L15 Blocks (13)

A. Carle, Summer 2005 © UC Berkeley

Adder/Subtractor Design -- how?


- Truth-table, then determine canonical form, then minimize and implement as we've seen before
- Look at breaking the problem down into smaller pieces that we can cascade or hierarchically layer

Cal

CS 61C L15 Blocks (14)

A. Carle, Summer 2005 © UC Berkeley

N 1-bit adders ⇒ 1 N-bit adder

 

Cal

CS 61C L15 Blocks (15)

A. Carle, Summer 2005 © UC Berkeley

Adder/Subtractor – One-bit adder LSB...

	a ₃	a ₂	a ₁	a ₀
+	b ₃	b ₂	b ₁	b ₀
	s ₃	s ₂	s ₁	s ₀

a ₀	b ₀	s ₀	c ₁
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$s_0 =$$

$$c_1 =$$

Cal

CS 61C L15 Blocks (16)

A. Carle, Summer 2005 © UC Berkeley

Adder/Subtractor – One-bit adder (1/2)...

	a ₃	a ₂	a ₁	a ₀
+	b ₃	b ₂	b ₁	b ₀
	s ₃	s ₂	s ₁	s ₀

a _i	b _i	c _i	s _i	c _{i+1}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$s_i =$$


$$c_{i+1} =$$

Cal

CS 61C L15 Blocks (17)

 A. Carle, Summer 2005 © UC Berkeley

Adder/Subtractor – One-bit adder (2/2)...



$$s_i = \text{XOR}(a_i, b_i, c_i)$$

$$c_{i+1} = \text{MAJ}(a_i, b_i, c_i) = a_i b_i + a_i c_i + b_i c_i$$

Cal


CS 61C L15 Blocks (18)

A. Carle, Summer 2005 © UC Berkeley

What about overflow?

• Consider a 2-bit signed # & overflow:

 - 10 = -2 + -2 or -1
- 11 = -1 + -2 only
- 00 = 0 NOTHING!
- 01 = 1 + 1 only



• Highest adder

- $C_1 = \text{Carry-in} = C_{in}$, $C_2 = \text{Carry-out} = C_{out}$
- No C_{out} or $C_{in} \Rightarrow$ NO overflow!
- C_{in} , and $C_{out} \Rightarrow$ NO overflow!

What op?


- C_{in} , but no $C_{out} \Rightarrow$ A,B both > 0, overflow!
- C_{out} , but no $C_{in} \Rightarrow$ A,B both < 0, overflow!



What about overflow?

• Consider a 2-bit signed # & overflow:

- 10 = -2
- 11 = -1
- 00 = 0
- 01 = 1

 


• Overflows when...

- C_{in} , but no $C_{out} \Rightarrow$ A,B both > 0, overflow!
- C_{out} , but no $C_{in} \Rightarrow$ A,B both < 0, overflow!

$$\text{overflow} = c_n \text{ XOR } c_{n-1}$$



Extremely Clever Subtractor

 


Administrivia

- We're now halfway through the semester... yikes
- HW 45 Due Monday
- Proj2 coming...
- Logisim!



State Circuits Overview

• State circuits have feedback, e.g.

 


- Output is function of inputs + fed-back signals.
- Feedback signals are the circuit's state.
- What aspects of this circuit might cause complications?



A simpler state circuit: two inverters



 - When started up, it's internally stable.
- Provide an or gate for coordination:



What's the result? How do we set to 0?

An R-S latch (cross-coupled NOR gates)

- S means “set” (to 1), R means “reset” (to 0).

A	B	NOR
0	0	1
0	1	0
1	0	0
1	1	0

- Adding Q' gives standard RS-latch:

S	R	Q
0	0	hold (keep value)
0	1	0
1	0	1
1	1	unstable

CS 61C L15 Blocks (25) A Carlo, Summer 2005 © UCB

An R-S latch (in detail)

S	R	Q	Q'	Q(t+Δt)
0	0	0	1	hold
0	0	1	0	hold
0	1	0	1	reset
0	1	1	0	reset
1	0	0	1	set
1	0	1	0	set
1	1	0	1	x x unstable
1	1	1	0	x x unstable

A	B	NOR
0	0	1
0	1	0
1	0	0
1	1	0

CS 61C L15 Blocks (26) A Carlo, Summer 2005 © UCB

Controlling R-S latch with a clock

- Can't change R and S while clock is active.

A	B	NOR
0	0	1
0	1	0
1	0	0
1	1	0

- Clocked latches are called *flip-flops*.

CS 61C L15 Blocks (27) A Carlo, Summer 2005 © UCB

D flip-flop are what we really use

- Inputs C (clock) and D.
- When C is 1, latch open, output = D (even if it changes, “transparent latch”)
- When C is 0, latch closed, output = stored value.

C	D	AND
0	0	0
0	1	0
1	0	0
1	1	1

CS 61C L15 Blocks (28) A Carlo, Summer 2005 © UCB

D flip-flop details

- We don't like transparent latches
- We can build them so that the latch is only open for an instant, on the rising edge of a clock (as it goes from 0⇒1)

Timing Diagram

CS 61C L15 Blocks (29) A Carlo, Summer 2005 © UCB

Edge Detection

A	B	O
0	0	1
0	1	1
1	0	1
1	1	1

- This is a “rising-edge D Flip-Flop”
- When the CLK transitions from 0 to 1 (rising edge) ...
 - Q ← D; Qbar ← not D
- All other times: Q ← Q; Qbar ← Qbar

CS 61C L15 Blocks (30) A Carlo, Summer 2005 © UCB

Peer Instruction

- A. Truth table for mux with 4 control signals has 2^4 rows
- B. We could cascade N 1-bit shifters to make 1 N-bit shifter for sll, srl
- C. If 1-bit adder delay is T, the N-bit adder delay would also be T



"And In conclusion..."

- Use muxes to select among input
 - S input bits selects 2^S inputs
 - Each input can be n-bits wide, indep of S
- Implement muxes hierarchically
- ALU can be implemented using a mux
 - Coupled with basic block elements
- N-bit adder-subtractor done using N 1-bit adders with XOR gates on input
 - XOR serves as conditional inverter

