




CS61CL Machine Structures

Lec 8 – State and Register Transfers

David Culler
Electrical Engineering and Computer Sciences
University of California, Berkeley





CS61CL Road Map

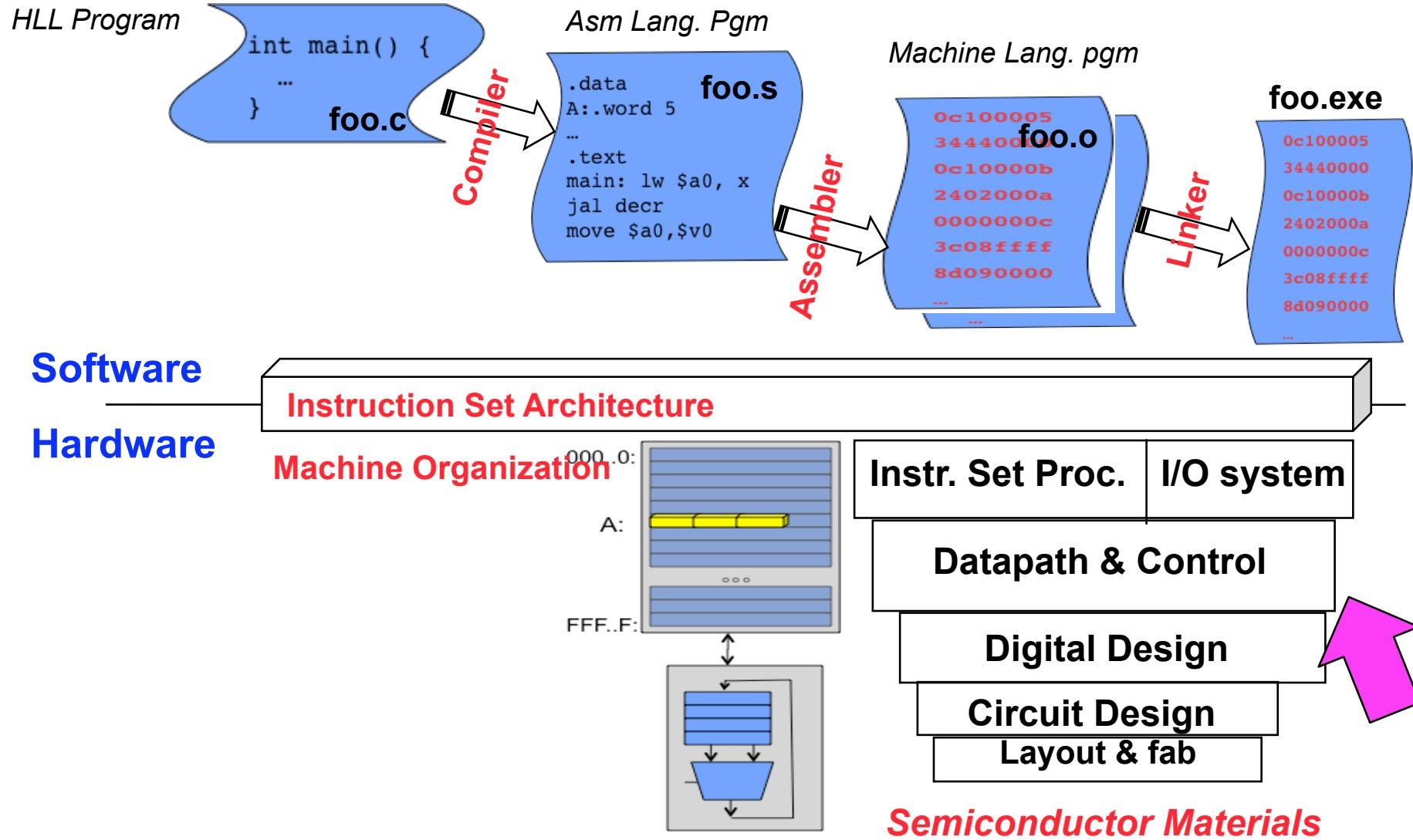



Review: Combinational Logic





 
 
- Any boolean function can be expressed as an acyclic connection of gates
- Often specified by a truth table



- Outputs are purely a function of the inputs
 - no history, no state



Examples: Logical Operations

     
 




Example: Multiplexor



$$C = S ? A : B$$

$$C = (S \& A) | (\sim S \& B)$$

  




Example: Adder

  




Example: Arithmetic Logic Unit

 




ALU

 




Element of Time

 

- Logical change is not instantaneous
- Broader digital design methodology has to make it appear as such
 - Clocking, delay estimation, glitch avoidance



What makes Digital Systems tick?

 




Administrative Issues

- HW 6 due tonight
- Project 2 dues Monday 10/26
 - bimodal check-off
 - testing tools available tomorrow
 - they are really picky
- Project 1 grading almost done
 - Friday
- HW 7 – discuss

- Midterm 2 on 11/9 as in original schedule
 - 11/11 is holiday



 A Bit of state: D-type edge-triggered flip-flop




- The edge of the clock is used to *sample* the "D" input & send it to "Q" (positive edge triggering).
 - At all other times the output Q is independent of the input D (just stores previously sampled value).
 - The input must be stable for a short time before the clock edge.



Registers

 - Collections of flip-flops with similar controls and logic
 - Stored values somehow related (e.g., form binary value)
 - Share clock, reset, and set lines
 - Similar logic at each stage



13



What “registers” do we need?

r0	0
r1	
o	
o	
r31	
PC	
lo	
hi	

Programmable storage

$2^{32} \times \text{bytes}$

31 x 32-bit GPRs (R0=0)


32 x 32-bit FP regs (paired DP)

HI, LO, PC

- “read” vs use the output
- “write” on the clock edge => Load
- Load Control




Register with Load Control

 




Register File

 




Towards a Data Path

 




Exercise a Data Path

 



 
What about RAM - Randomly Accessed Memory?



- Like a **HUGE register file**
 - dense, slower, low-cost storage cell (6T)
 - fewer ports
 - wider address lines
 - accessed over a “bus”
- **Bus: means of composition in hardware system**
 - logically related collection of wires
 - interfacing one or more sources to one or more destinations



Recall: Instruction Cycle

 



Register Transfers

MIPS Instruction Format

R: Reg-Reg

op	rs	rt	rd	shamt	funct
6	5	5	5	5	6

I: Reg-Immed

op	rs	rt	immediate
6	5	5	16

J: Jump

op	immediate
6	26

- **Reg-Reg instructions (op == 0)**

- add, sub, and, or, nor, xor, slt
- sll, srl, sra

$R[rd] := R[rs]$ *funct* $R[rt]$; $pc := pc + 4$
 $R[rd] := R[rt]$ *shift* *shamt*

- **Reg-Immed (op != 0)**

- addi, andi, ori, xori, lui,
- addiu, slti, sltiu
- lw, lh, lhu, lb, lbu
- sw, sh, sb

$R[rt] := R[rs]$ op *Im16*
 $R[rt] := \text{Mem}[R[rs] + \text{signEx}(Im16)]^*$
 $\text{Mem}[R[rs] + \text{signEx}(Im16)] := R[rt]$


10/21/09

cs61cl f09 lec 5

12



Synchronous Circuit Design

 

- **Combinational Logic Blocks (CL)**
 - Acyclic
 - no internal state (no feedback)
 - output only a function of inputs
- **Registers (reg)**
 - collections of flip-flops
- **clock**
 - distributed to all flip-flops
- **ALL CYCLES GO THROUGH A REG!**