



Implementing an Instruction Set

David E. Culler


CS61CL

Oct 28, 2009

Lecture 9



Review: Synchronous Circuit Design

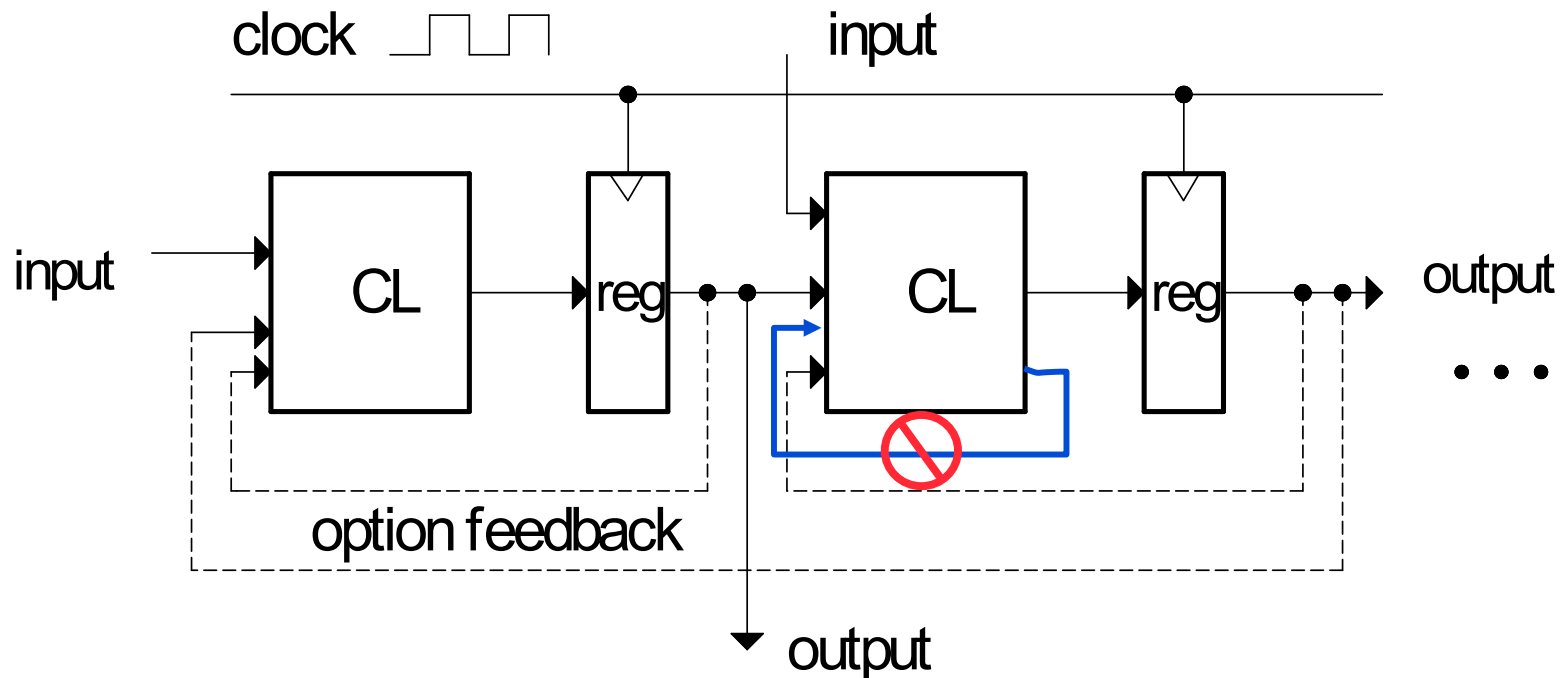


- **Combinational Logic Blocks (CL)**
 - Acyclic
 - no internal state (no feedback)
 - output only a function of inputs
- **Registers (reg)**
 - collections of flip-flops
- **clock**
 - distributed to all flip-flops
- **ALL CYCLES GO THROUGH A REG!**



MIPS: Register Transfers

MIPS Instruction Format

 

• Reg-Reg instructions (op == 0)

- add, sub, and, or, nor, xor, slt $R[rd] := R[rs] \text{ funct } R[rt]; pc:=pc+4$
- sll, srl, sra $R[rd] := R[rt] \text{ shft shamt}$

• Reg-Immed (op != 0)

- addi, andi, ori, xori, lui $R[rt] := R[rs] \text{ op } Im16$
- addiu, slti, sltiu
- lw, lh, lhu, lb, lbu $R[rt] := Mem[R[rs] + signEx(Im16)]^*$
- sw, sh, sb $Mem[R[rs] + signEx(Im16)] := R[rt]$

10/21/09

cs61cl f09 lec 5

12



MIPS: Register Transfers

MIPS Instruction Format



- **Reg-Reg instructions (op == 0)**

- **Reg-Immed (op != 0)**

- **Jumps**

- j

PC := PC_{31..28} || addr || 00

- jal

PC := PC_{31..28} || addr || 00; R[31] := PC + 4

- jr

PC := R[rs]

10/27/09


cs61cl f09 lec 5

19



MIPS: Register Transfers

MIPS Instruction Format

 

- Reg-Reg instructions ($op == 0$)
- Reg-Immed ($op \neq 0$)
- Jumps
- Branches
 - BEQ, BNE $PC := (R[rs] == R[rt]) ? PC + \text{signEx}(\text{im16}) : PC+4$
 - BLT, BGT, BLE, BGTE are pseudo ops
 - Move and LI are pseudo ops too


10/27/09

cs61cl f09 lec 5


20



A Standard High-level Organization

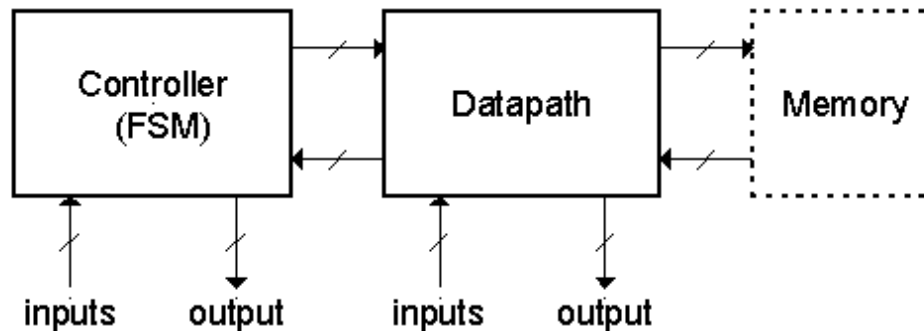


- **Controller**
 - accepts external and control input, generates control and external output and sequences the movement of data in the datapath.
- **Datapath**
 - is responsible for data manipulation. Usually includes a limited amount of storage.
- **Memory**
 - optional block used for long term storage of data structures.
- **Standard model for CPUs, micro-controllers, many other digital sub-systems.**
- **Usually *not* nested.**
- **Often cascaded:**

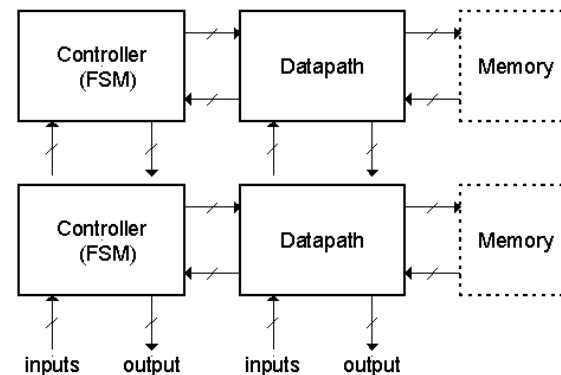



Datapath vs Control

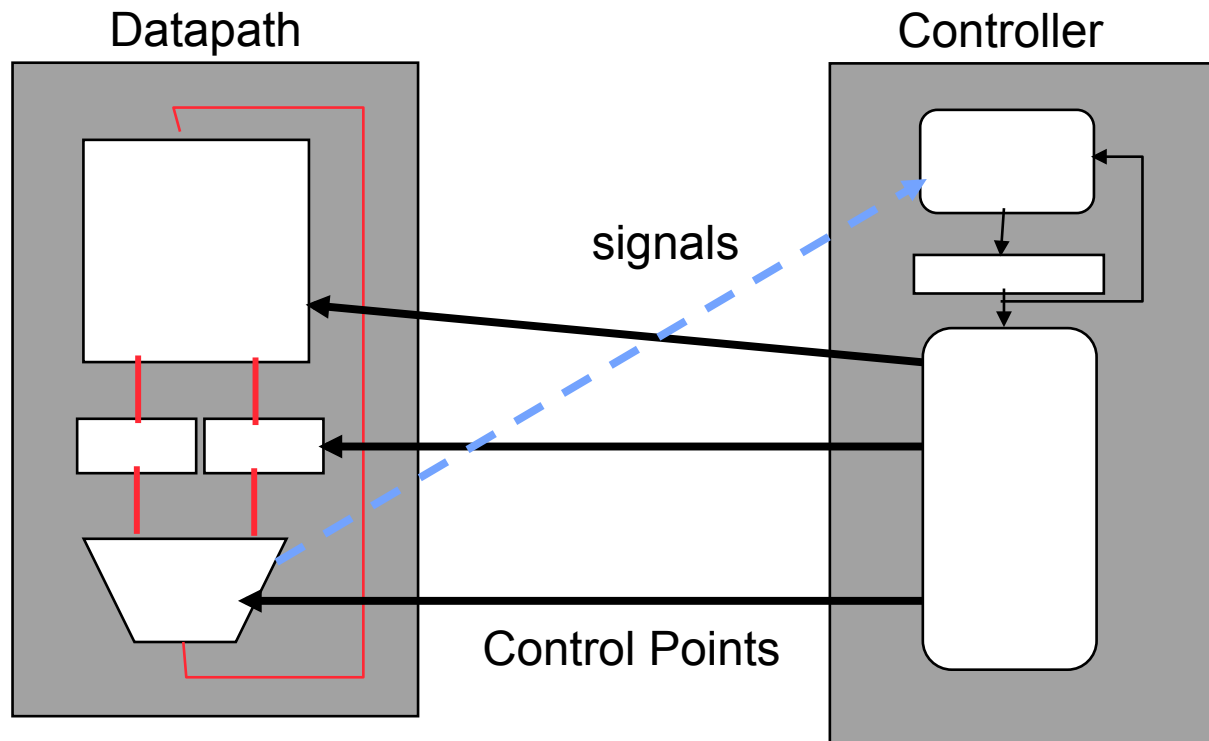


- **Datapath: Storage, FU, interconnect sufficient to perform the desired functions**
 - Inputs are Control Points
 - Outputs are signals
- **Controller: State machine to orchestrate operation on the data path**
 - Based on desired function and signals



Register Transfer Level Descriptions

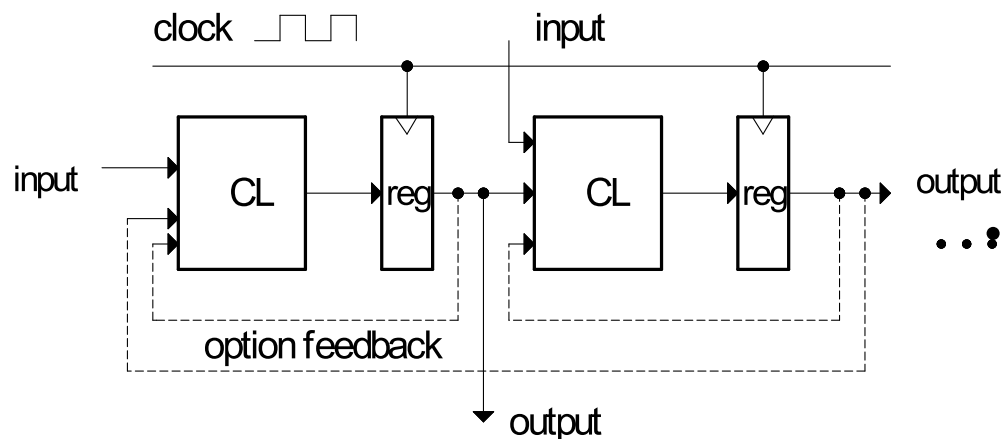- A standard high-level representation for describing systems.
- It follows from the fact that all synchronous digital system can be described as a set of state elements connected by combination logic (CL) blocks:



- RTL comprises a set of *register transfers* with optional operators as part of the transfer.

- Example:

regA ← regB

regC ← regA + regB

if (start==1) regA ← regC

- Personal style:

- use “;” to separate transfers that occur on separate cycles.

- Use “,” to separate transfers that occur on the same cycle.

... Example (2 cycles):

regA ← regB, regB ← 0;

regC ← regA;




The Methodology

- 1. Identify state and operations visible in the ISA**
 - register transfer level operations of the ISA
- 2. Select a set of storage elements, function units, and interconnections that**
 - realize all the “architected” state & operations
 - plus internal state and operations
- 3. Map each instruction to register transfers on the data path**
- 4. Identify the control points that cause the specified data transfers**
- 5. Implement a controller that asserts those control points**
 - as a function of instruction, controller state, and signals from the data path



MIPS R3000 – tiny subset

 

Programmable storage

2^{32} x bytes

31 x 32-bit GPRs (R0=0)

32 x 32-bit FP regs (paired DP)

HI, LO, PC

Arithmetic logical

Add, AddU, Sub, SubU, And, Or, Xor, Nor, SLT, SLTU,
AddI, AddIU, SLTI, SLTIU, AndI, OrI, XorI, *LUI*
SLL, SRL, SRA, SLLV, SRLV, SRAV

Memory Access

LB, LBU, LH, LHU, LW, LWL, LWR
SB, SH, SW, SWL, SWR

Control

J, JAL, JR, JALR
BEQ, BNE, BLEZ, BGTZ, BLTZ, BGEZ, BLTZAL, BGEZAL



TinyMIPS

- **Reg-Reg instructions (op == 0)**

- addu $R[rd] := R[rs] + R[rt]; pc:=pc+4$
- subu $R[rd] := R[rs] - R[rt]; pc:=pc+4$

- **Reg-Immed (op != 0)**

- lw $R[rt] := Mem[R[rs] + signEx(Im16)]$
- sw $Mem[R[rs] + signEx(Im16)] := R[rt]$

- **Jumps**

- j $PC := PC_{31..28} || addr || 00$
- jr $PC := R[rs]$

- **Branches**

- BEQ $PC := (R[rs] == R[rt]) ? PC + signEx(im16) : PC+4$
- BLTZ $PC := (R[rs] < 0) ? PC + signEx(im16) : PC+4$




Administration

- **Project 3 is out – due Sun 11/15**
- **Homework 7 is out – due Wed 11/4**
- **Midterm 2 is Monday 11/9**




Starting Point

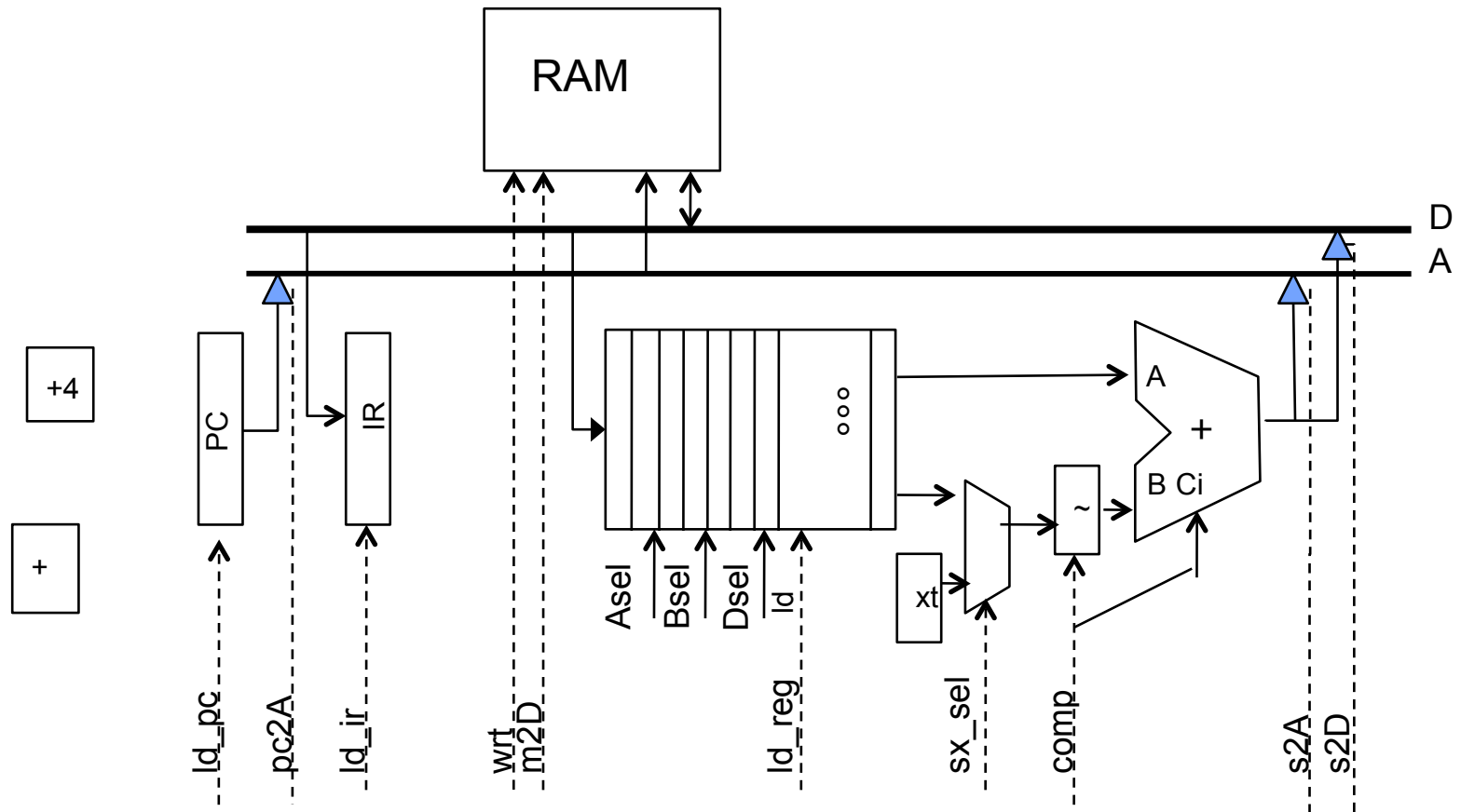




Exec: LW

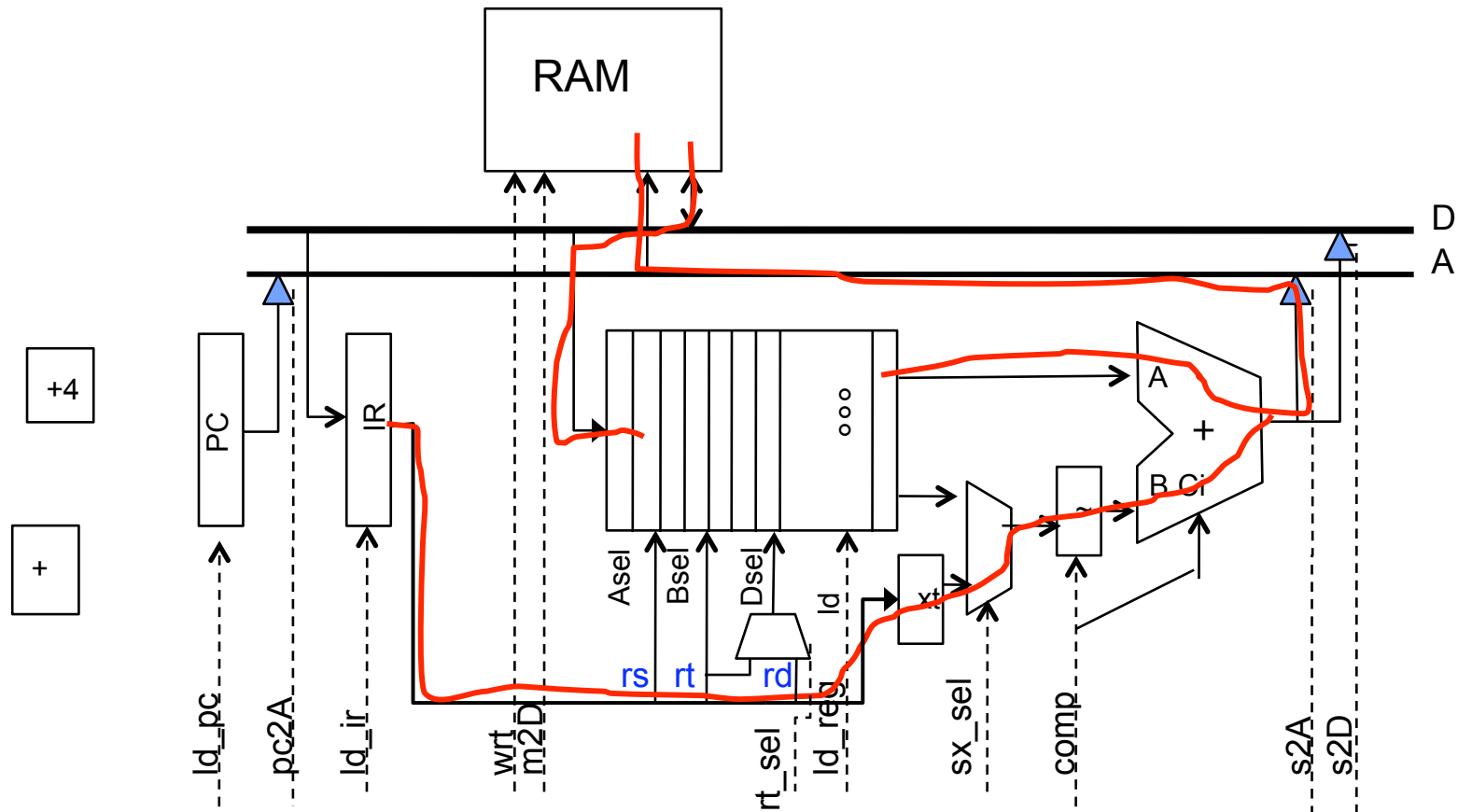

- $R[rt] := Mem[R[rs] + SXim16];$
- $sx_sel, \sim comp, s2A, \sim pc2A, \sim wrt, m2D, ld_reg$
- rt_sel




Exec: SW

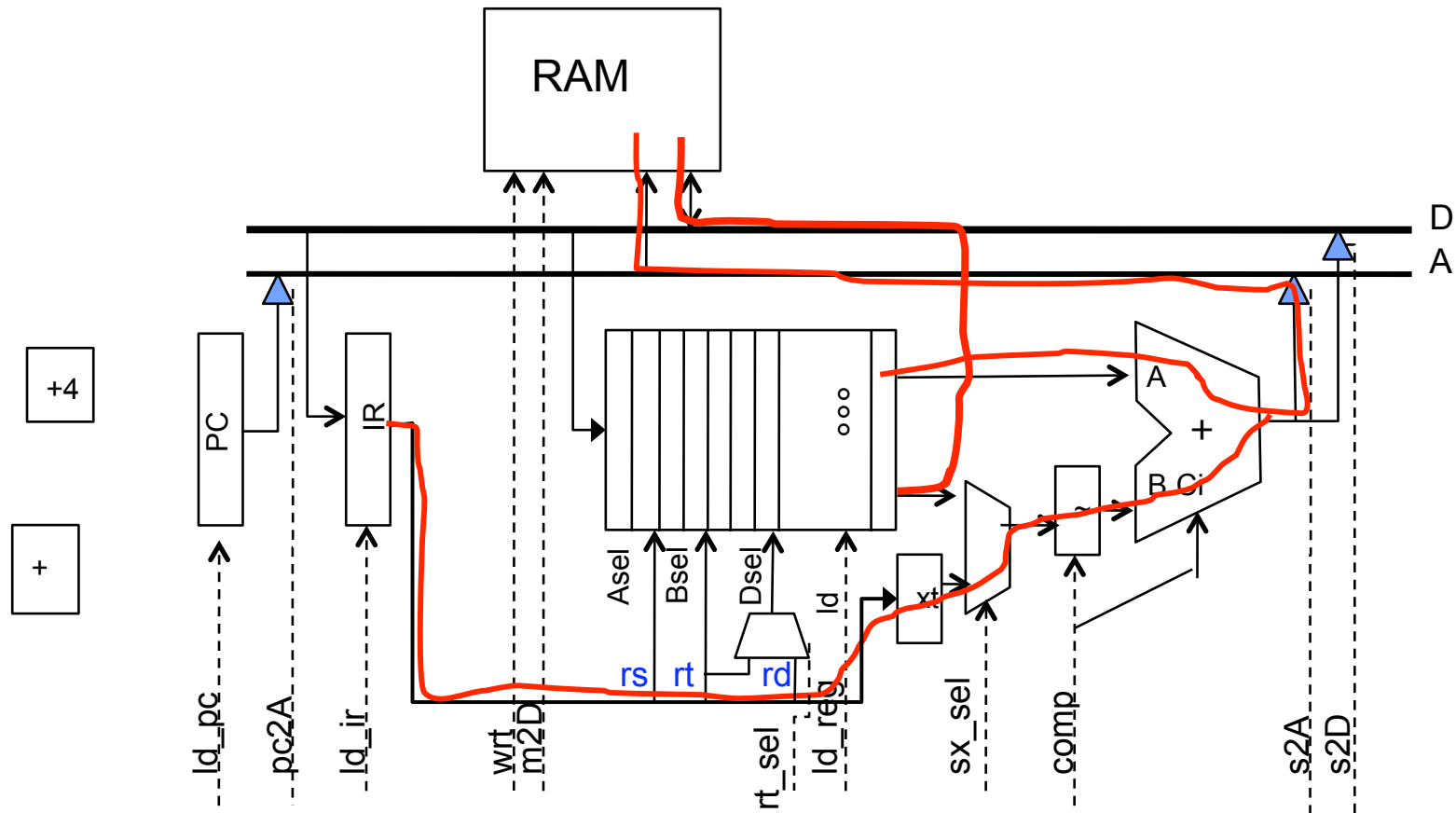

- $\text{Mem}[\text{R}[\text{rs}] + \text{SXim16}] := \text{R}[\text{rt}];$



Exec: SW

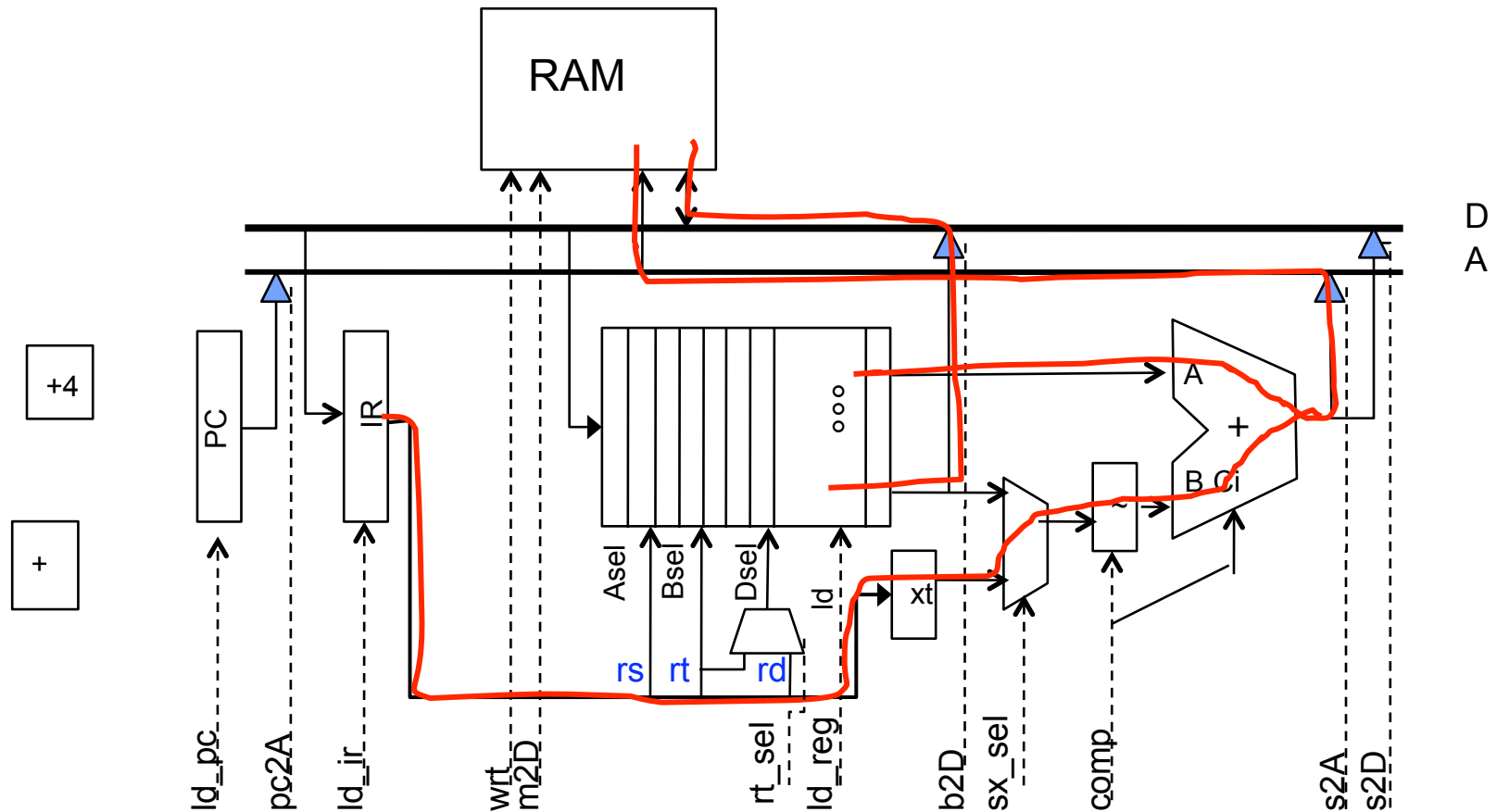


D
A

- $Mem[R[rs]+SXim16] := R[rt];$
- $b2D, sx_sel, \sim comp, s2A, \sim s2D, \sim m2D, wrt, \sim ld_reg, \sim pc2A$



Exec: $PC := PC + 4$

 


D
A

- ld_pc



Exec: $PC := PC + 4$

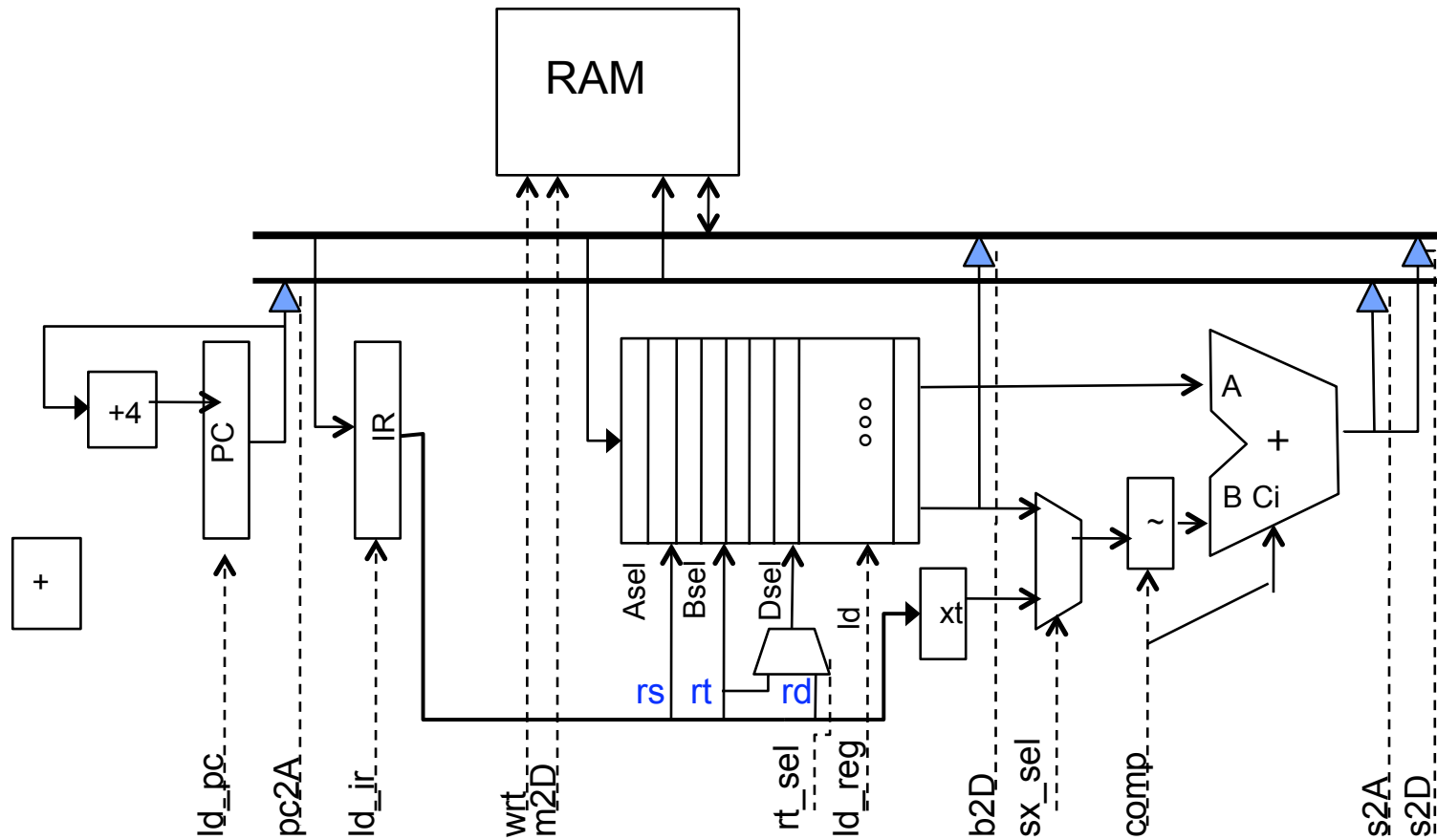


D
A

- **ld_pc**



Exec: Jump

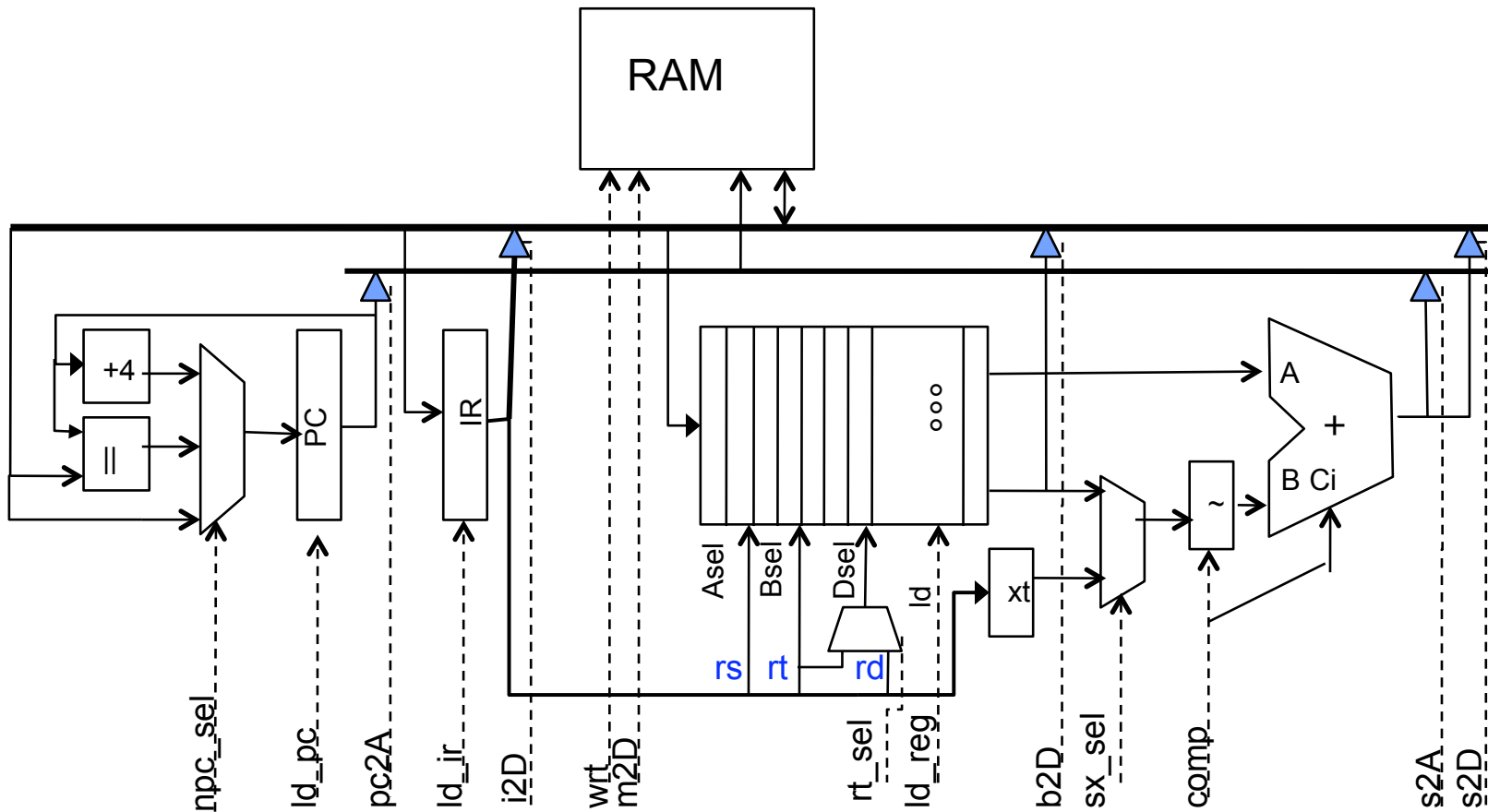


D
A

- **j** $PC := PC_{31..28} || \text{addr} || 00$
- **jr** $PC := R[rs]$



Exec: Branch

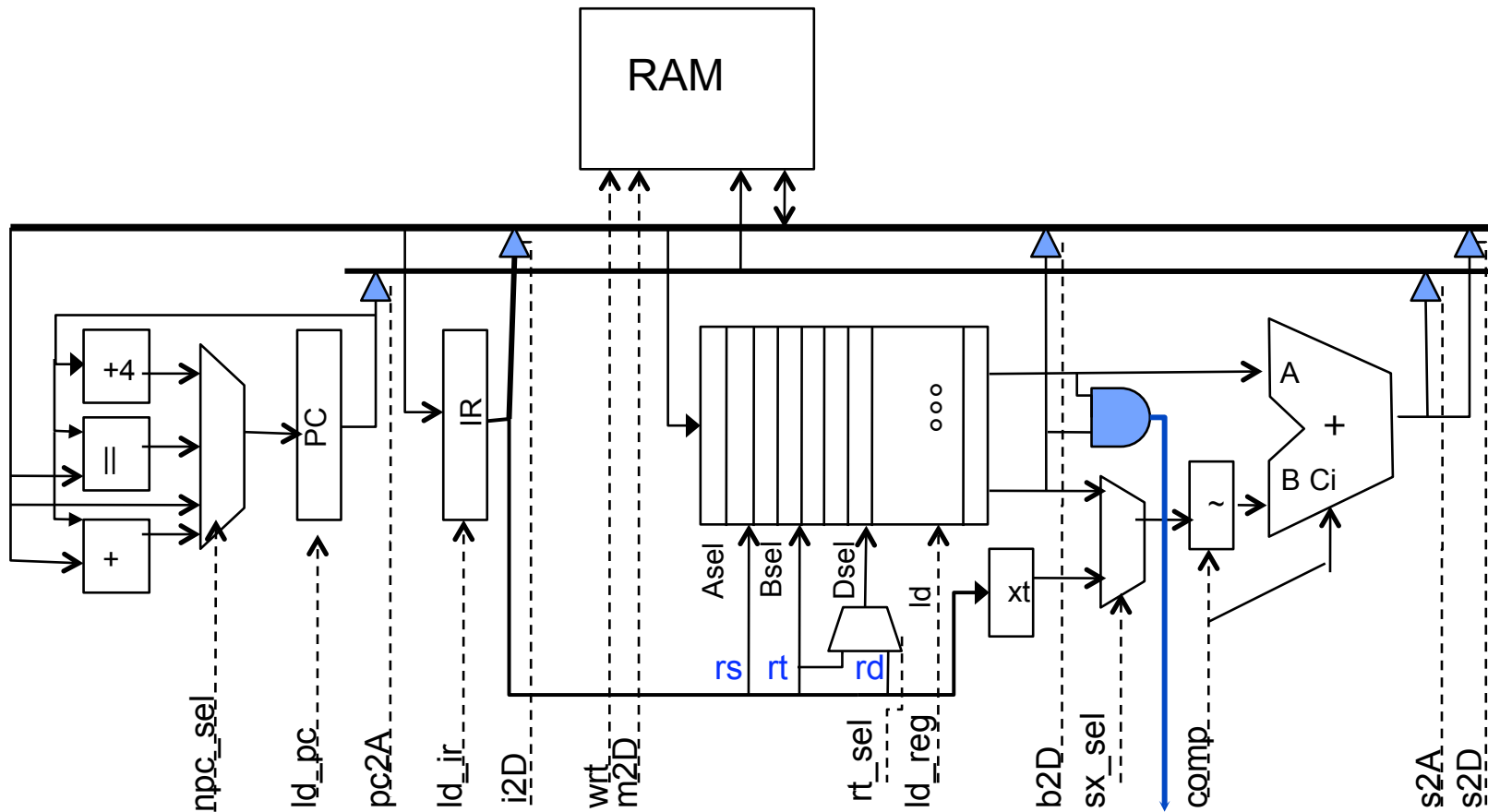


D
A

- **BEQ** $PC := (R[rs] == R[rt]) ? PC + \text{signEx}(im16) : PC+4$
- **BLTZ** $PC := (R[rs] < 0) ? PC + \text{signEx}(im16) : PC+4$



Exec: Branch

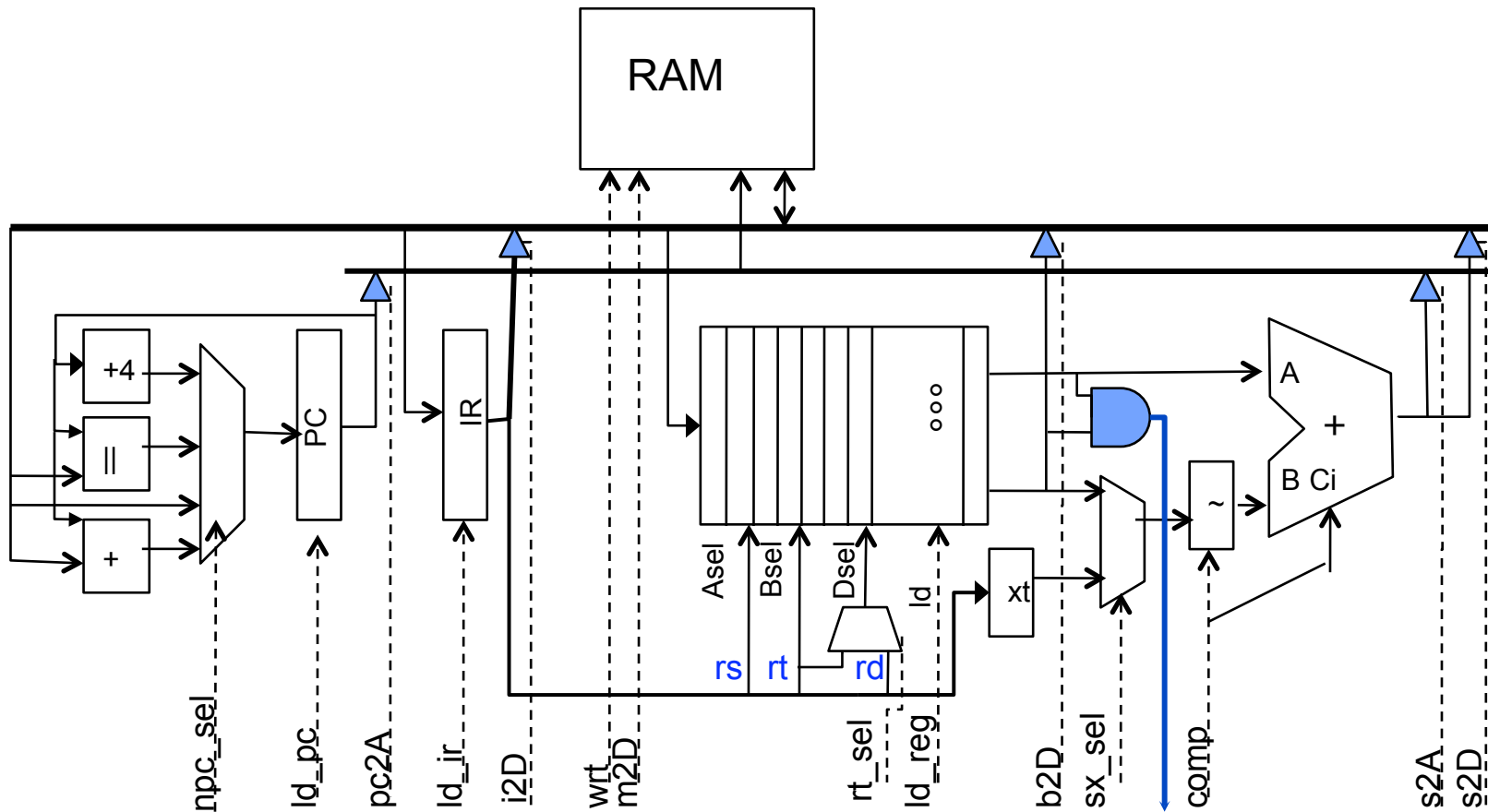


D
A

- $PC := (R[rs] == R[rt]) ? PC + \text{signEx}(im16) : PC+4$
 - $nPC_sel = EQ ? pcAdd : PCInc$
- **BLTZ** $PC := (R[rs] < 0) ? PC + \text{signEx}(im16) : PC+4$



DataPath + Control

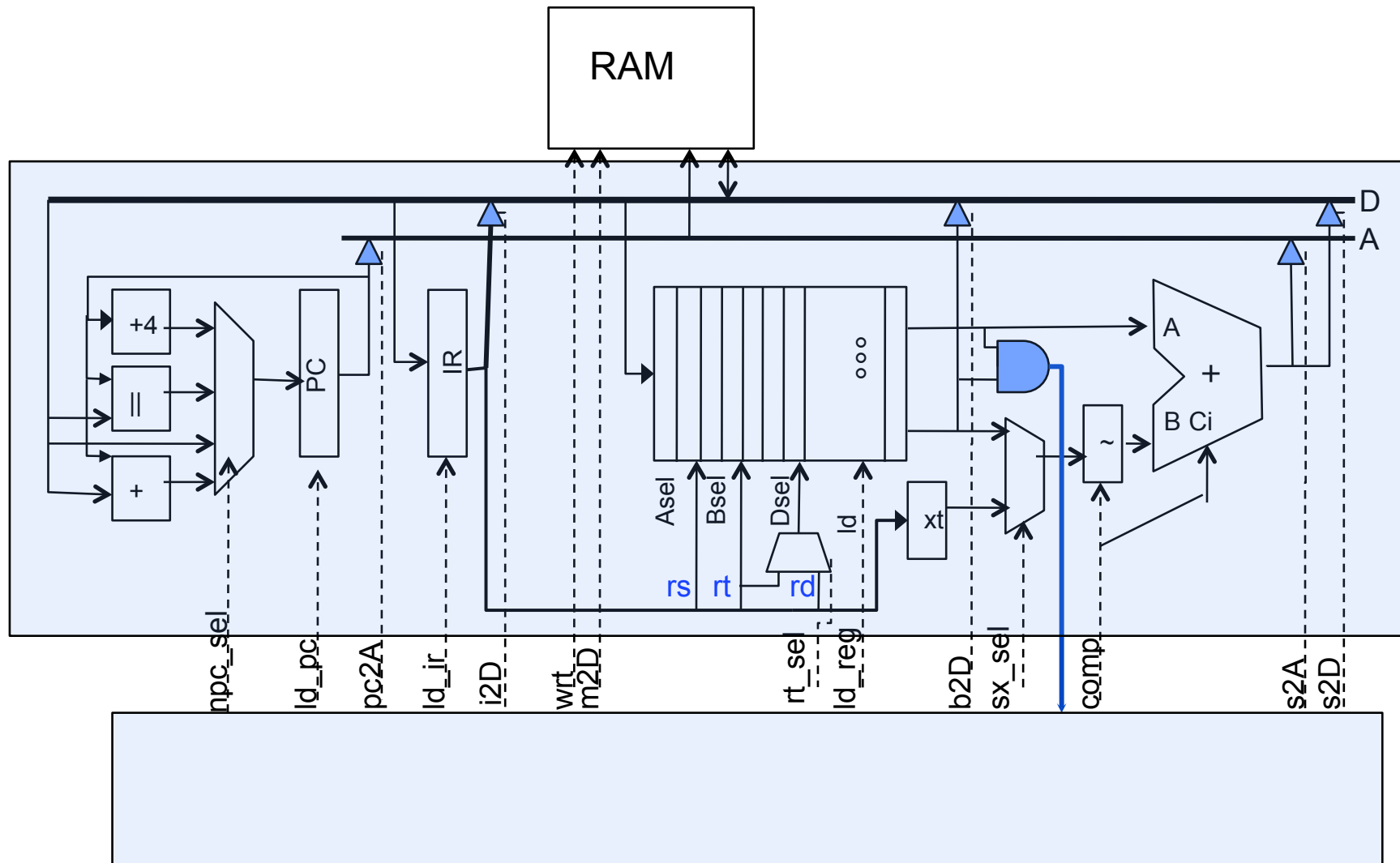



Levels of Design Representation

