

## Solutions

2.

a. Electrons move from bottom to top in the resistor.


b. Current flows from top to bottom in the resistor.

c.  $V = I \cdot R \Rightarrow I = V / R = 1.5 \text{ V} / 1 \text{ k}\Omega = \boxed{1.5 \text{ mA}}$

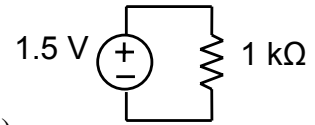d. charge of one electron =  $-1.602 \cdot 10^{-19} \text{ C}$

$1.5 \text{ mA} = 1.5 \text{ mC/s}$  (positive charges) =  $-1.5 \text{ mC/s}$  (negative charges)

$-1.5 \text{ mC/s} / (-1.602 \cdot 10^{-19} \text{ C/electron}) = \boxed{9.363 \cdot 10^{15} \text{ electrons/s}}$



3.

$\boxed{I_1 = 0 \text{ A}}$  (open circuit)

$I_3 = I_S + I_0 = 8 \text{ A} + -2 \text{ A} = \boxed{I_3 = 6 \text{ A}}$

$I_S = I_2 + I_3 \Rightarrow I_2 = I_S - I_3 = 8 \text{ A} - 6 \text{ A} = \boxed{I_2 = 2 \text{ A}}$

4.

Recall that ground nodes are connected to each other.

$I_1 = I_2 + I_3 \Rightarrow I_3 = I_1 - I_2 = 5 \text{ mA} - 3 \text{ mA} = \boxed{8 \text{ mA}}$

5.

a. Voltage divider

$V_1 = V_{IN} \cdot 20 \Omega / (20 \Omega + 30 \Omega) = 15 \text{ V} \cdot 20 \Omega / (20 \Omega + 30 \Omega) = \boxed{V_1 = 6 \text{ V}}$

$I_2 = (15 \text{ V} - V_1) / 30 \Omega = (15 \text{ V} - 6 \text{ V}) / 30 \Omega = \boxed{I_2 = 0.3 \text{ A}}$

$I_1 + I_2 = 0 \Rightarrow I_1 = -I_2 = \boxed{I_1 = -0.3 \text{ A}}$

b.

$V_1 = 1/4 \text{ A} \cdot 20 \Omega = \boxed{V_1 = 5 \text{ V}}$

$V_1 = -I_2 \cdot 30 \Omega \Rightarrow I_2 = -5 \text{ V} / 30 \Omega = \boxed{I_2 = -1/6 \text{ A}}$

c.

$-0.5 \text{ A} \cdot 30 \Omega = -I_2 \cdot 20 \Omega \Rightarrow I_2 = -0.5 \text{ A} \cdot 30 \Omega / 20 \Omega = \boxed{I_2 = 0.75 \text{ A}}$

$-0.5 \text{ A} = I_1 + I_2 \Rightarrow I_1 = -0.5 \text{ A} - 0.75 \text{ A} = \boxed{I_1 = -1.25 \text{ A}}$

$V_1 = -I_1 \cdot 30 \Omega + -0.5 \text{ A} \cdot 30 \Omega = -(-1.25 \text{ A}) \cdot 30 \Omega + 15 \text{ V} = \boxed{V_1 = 52.5 \text{ V}}$

6.

a.  $V_{OUT} = V_{IN} \cdot R_a / (R_1 + R_a) \Rightarrow (R_1 + R_a) \cdot V_{OUT} = V_{IN} \cdot R_a$

$\Rightarrow R_a \cdot (V_{IN} - V_{OUT}) = R_1 \cdot V_{OUT} \Rightarrow R_a = R_1 \cdot V_{OUT} / (V_{IN} - V_{OUT})$

$R_a = 15 \text{ k}\Omega \cdot 20 \text{ V} / (50 \text{ V} - 20 \text{ V}) = \boxed{R_a = 10 \text{ k}\Omega}$

$P = V \cdot I = V^2 / R$

$P_a = V_{OUT}^2 / R_a = (20 \text{ V})^2 / 10 \text{ k}\Omega = 40 \text{ mW} \Rightarrow \boxed{\text{use } 1/8 \text{ W rating for } R_a}$

$P_1 = (V_{IN} - V_{OUT})^2 / R_1 = (50 \text{ V} - 20 \text{ V})^2 / 15 \text{ k}\Omega = 60 \text{ mW} \Rightarrow \boxed{\text{use } 1/8 \text{ W rating for } R_1}$

b. Answers vary

$$\text{Let } R_a = 2.25 \Omega$$

$$R_b = R_a \cdot V_{\text{OUT}} / (V_{\text{IN}} - V_{\text{OUT}}) = 1 \Omega \cdot 2.25 \text{ V} / (5 \text{ V} - 2.25 \text{ V}) = R_b = 2.75 \Omega$$

$$P_a = V_{\text{OUT}}^2 / R_a = (2.25 \text{ V})^2 / 2.25 \text{ k}\Omega = 225 \text{ mW} \Rightarrow \text{use } 1/4 \text{ W rating for } R_a$$

$$P_b = (V_{\text{IN}} - V_{\text{OUT}})^2 / R_b = (5 \text{ V} - 2.25 \text{ V})^2 / 2.75 \text{ k}\Omega = 275 \text{ mW} \Rightarrow \text{use } 1/2 \text{ W rating for } R_b$$

$$\text{c. } V_{\text{OUT}} = V_{\text{IN}} \cdot R_4 / (R_3 + R_L + R_4) \Rightarrow (R_3 + R_L + R_4) \cdot V_{\text{OUT}} = V_{\text{IN}} \cdot R_4$$

$$\Rightarrow R_L \cdot V_{\text{OUT}} = V_{\text{IN}} \cdot R_4 - (R_3 + R_4) \cdot V_{\text{OUT}}$$

$$\Rightarrow R_L = V_{\text{IN}} \cdot R_4 / V_{\text{OUT}} - R_3 + R_4$$

$$= 110 \text{ V} \cdot 2.7 \text{ k}\Omega / 28.3 \text{ V} - 1 \text{ k}\Omega - 2.7 \text{ k}\Omega = R_L = 6.795 \text{ k}\Omega$$

$$P_4 = V_{\text{OUT}}^2 / R_4 = (28.3 \text{ V})^2 / 2.7 \text{ k}\Omega = 296.6 \text{ mW} \Rightarrow \text{use } 1/2 \text{ W rating for } R_4$$

$$I = V_{\text{OUT}} / R_4 = (28.3 \text{ V})^2 / 2.7 \text{ k}\Omega = 10.48 \text{ mA}$$

$$P = V \cdot I = I^2 \cdot R$$

$$P_3 = I^2 / R_3 = (10.48 \text{ mA})^2 \cdot 1 \text{ k}\Omega = 109.9 \text{ mW} \Rightarrow \text{use } 1/8 \text{ W rating for } R_3$$

$$P_L = I^2 / R_L = (10.48 \text{ mA})^2 \cdot 6.795 \text{ k}\Omega = 746.5 \text{ mW} \Rightarrow \text{use } 1 \text{ W rating for } R_L$$

7.

a.

$$v = -I_1 \cdot R_2 \Rightarrow I_1 = -v / R_2$$

$$I_1 + I_2 + 3 = 0 \Rightarrow I_2 = -I_1 - 3 \text{ A} = -v / R_2 - 3 \text{ A} = (12 \text{ V} - v) / R_3$$

$$\Rightarrow v \cdot (1 / R_3 + 1 / R_2) = 12 \text{ V} / R_3 + 3$$

$$\Rightarrow v = (12 \text{ V} / R_3 + 3 \text{ A}) / (1 / R_3 + 1 / R_2) = (12 \text{ V} / 5 \Omega + 3 \text{ A}) / (1 / 5 \Omega + 1 / 10 \Omega)$$

$$v = 18 \text{ V}$$

$$I_1 = -18 \text{ V} / 10 \Omega = I_1 = -1.8 \text{ A}$$

$$I_2 = -1.8 \text{ A} - 3 \text{ A} = I_2 = -1.2 \text{ A}$$

b.

$$P_{\text{IS}} = V_{\text{IS}} \cdot I_{\text{IS}} = (R_1 \cdot 3 \text{ A} - v) \cdot 3 \text{ A} = (25 \Omega \cdot 3 \text{ A} - 18 \text{ V}) \cdot 3 \text{ A} = -279 \text{ W}$$

$$\Rightarrow \text{current source delivers } 279 \text{ W}$$

$$P_{\text{VS}} = V_{\text{VS}} \cdot I_{\text{VS}} = 12 \text{ V} \cdot (-I_2 - 12 \text{ V} / R_4) = 12 \text{ V} \cdot (-1.2 \text{ A} - 12 \text{ V} / 7 \Omega)$$

$$\Rightarrow \text{voltage source delivers } 6.171 \text{ W}$$

c.

$$P_{\text{DISSIPATED}} = P_{\text{DELIVERED}} = -(P_{\text{IS}} + P_{\text{VS}}) = -(279 \text{ W} + 6.171 \text{ W}) = P_{\text{DISSIPATED}} = 285.171 \text{ W}$$