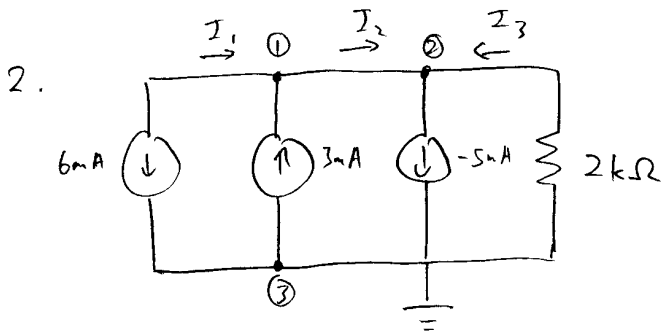


EE 42/100 Problem Set 2 Solutions



by inspection, $I_1 = -6\text{mA}$

at node ①: $I_1 + 3\text{mA} = I_2$


$$I_2 = -3\text{mA}$$

at node ②: $I_2 + I_3 = -5\text{mA}$

$$I_3 = -2\text{mA}$$

} Kirchhoff's Current Law

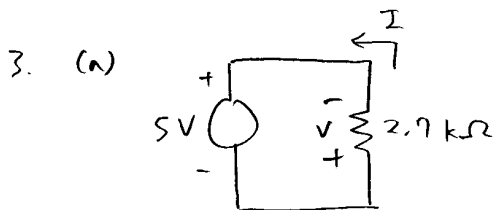
$I_1 = -6\text{mA}, I_2 = -3\text{mA}, I_3 = -2\text{mA}$



$$I = \frac{V}{R} \text{ (Ohm's Law)}$$


$$V = -5\text{V}, R = 2.7\text{k}\Omega$$

$I = -1.85\text{mA}$

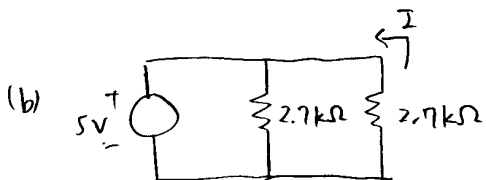

this is the same as part (a) because the resistors are in parallel with voltage source
 → same voltage across resistor as in part (a)

$I = -1.85\text{mA}$

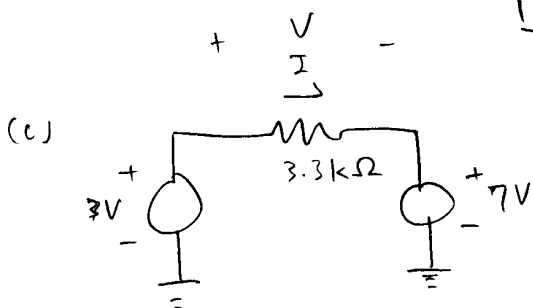


$$I = \frac{V}{R}$$

$$V = 3\text{V} - 7\text{V} = -4\text{V}$$

$I = -1.21\text{mA}$

4.

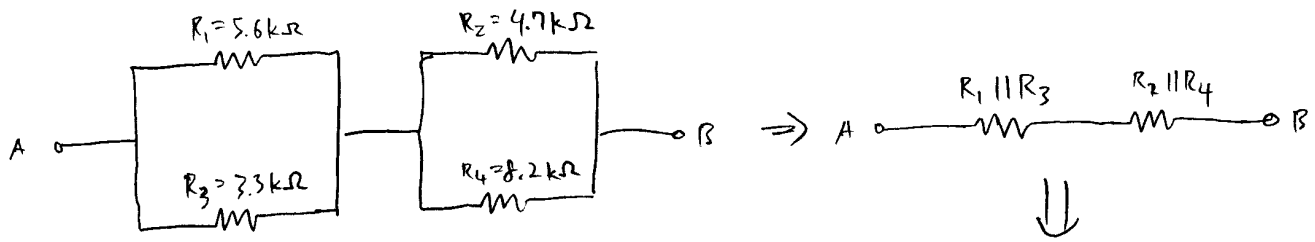


$$R_1 \parallel R_3 = \left(\frac{1}{R_1} + \frac{1}{R_3} \right)^{-1} = \frac{R_1 R_3}{R_1 + R_3} = 2.07 \text{ k}\Omega$$

$$R_2 \parallel R_4 = \left(\frac{1}{R_2} + \frac{1}{R_4} \right)^{-1} = \frac{R_2 R_4}{R_2 + R_4} = 2.99 \text{ k}\Omega$$

$$R_{eq} = (R_1 \parallel R_3) + (R_2 \parallel R_4) = \boxed{5.06 \text{ k}\Omega}$$

5.

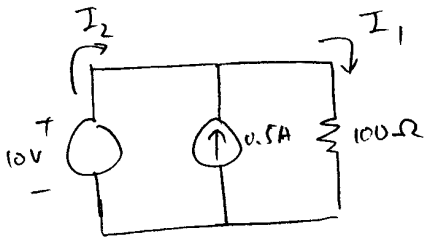

$$I_1 = \frac{V}{R} = \frac{10 \text{ V}}{100 \Omega} = 0.1 \text{ A} \quad (\text{Ohm's Law})$$

$$I_2 + 0.5 \text{ A} = I_1 \Rightarrow I_2 = -0.4 \text{ A} \quad (\text{KCL})$$

$$\boxed{I_1 = 0.1 \text{ A}, I_2 = -0.4 \text{ A}}$$

6. (a) R_1 and R_2 are parallel \Rightarrow same voltage across R_1, R_2

Power dissipated through resistor $R = \frac{V^2}{R}$

$$P = \frac{V^2}{R_1} + \frac{V^2}{R_2} = \text{total power dissipated through both resistors}$$

$$P = V^2 \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$P(R_1 \parallel R_2) = V^2$$

$$P_1 = \frac{V^2}{R_1} = \frac{P(R_1 \parallel R_2)}{R_1}$$

$$= \boxed{P \cdot \frac{R_2}{R_1 + R_2}} \quad \leftarrow \text{power dissipated in } R_1$$

(b) R_1, R_2 in series \rightarrow same current through R_1, R_2

Power dissipated in resistor $R = I^2 R$


$$P = I^2 R_1 + I^2 R_2$$

$$P = I^2 (R_1 + R_2)$$

$$I^2 = \frac{P}{R_1 + R_2}$$

$$P_1 = I^2 R_1$$

$$P_1 = P \cdot \frac{R_1}{R_1 + R_2}$$

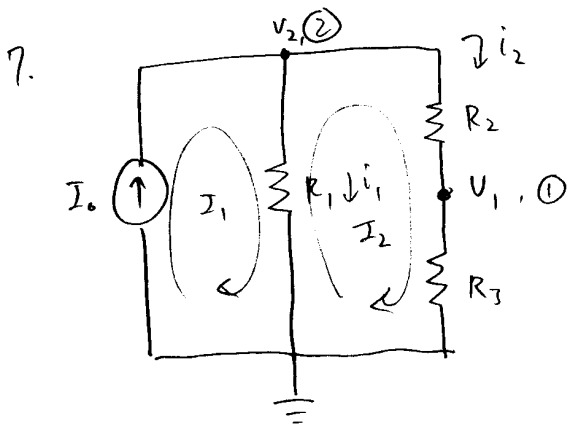

at node ①: $\frac{V_1}{R_3} = \frac{V_2 - V_1}{R_2}$

at node ②: $\frac{V_2}{R_1} + \frac{V_2 - V_1}{R_2} = I_0$

$$\text{②} - \text{①} = \frac{V_2}{R_1} = I_0 - \frac{V_1}{R_3}$$

from ①: $V_1 = V_2 \cdot \frac{R_3}{R_2 + R_3}$ (which is just a voltage divider)

$$\frac{V_2}{R_1} = I_0 - \frac{V_2}{R_2 + R_3} \Rightarrow V_2 = I_0 \cdot \left(\frac{1}{R_1} + \frac{1}{R_2 + R_3} \right)^{-1}$$

$$V_2 = 2.61 \text{ V}$$

$$V_1 = V_2 \cdot \frac{R_3}{R_2 + R_3} \Rightarrow V_1 = 1.43 \text{ V}$$

* this can more easily be solved using the concepts of current and voltage dividers

8. by inspection: $I_1 = I_0$

around mesh current I_2 : $(I_2 - I_1) R_1 + I_2 R_2 + I_2 R_3 = 0$


replacing $I_1 = I_0$: $(I_2 - I_0) R_1 + I_2 R_2 + I_2 R_3 = 0$

$$I_2 = I_0 \cdot \frac{R_1}{R_1 + R_2 + R_3}$$

by ohm's Law: $V_1 = I_2 R_3 = I_0 \cdot \frac{R_1 R_3}{R_1 + R_2 + R_3}$

$$V_1 = 1.43 \text{ V}$$

9.

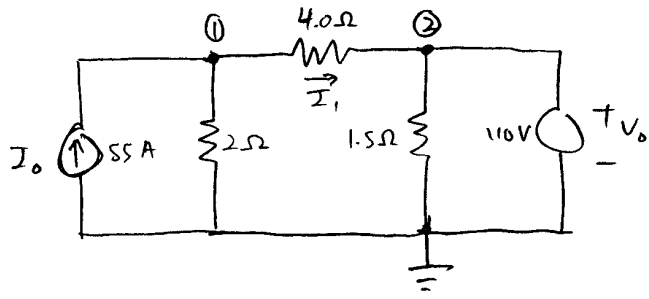

at node ① : $I_0 = \frac{V_1}{2\Omega} + I_1$

$$I_1 = \frac{V_1 - V_2}{4.0\Omega}$$


by inspection, $V_2 = V_0 \Rightarrow I_0 = \frac{V_1}{2\Omega} + \frac{V_1 - V_0}{4.0\Omega}$

$$V_1 = \left(I_0 + \frac{V_0}{4.0\Omega} \right) \left(\frac{1}{2\Omega} + \frac{1}{4.0\Omega} \right)^{-1}$$

$$V_1 = 110 \text{ V}$$

$$\therefore I_1 = \frac{V_1 - V_2}{4.0\Omega} = \boxed{\phi \text{ A}}$$

10.

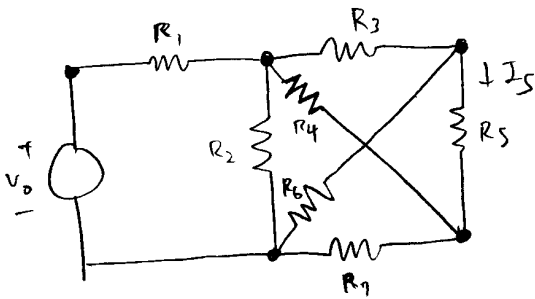

(a) 5 nodes

(b) 8 branches

(c) mesh currents = branches - nodes + 1
 $= 8 - 5 + 1$

4 mesh currents