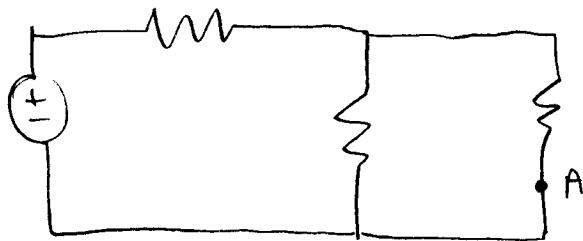




$$V_0 = 10V, R_1 = 4.7k\Omega, R_2 = 2.2k\Omega, R_3 = 3.3k\Omega$$

At DC Steady state, capacitors = open
inductors = short

Circuit simplifies to:



$$V_A = 0V?$$

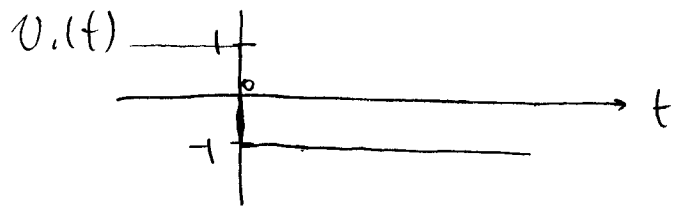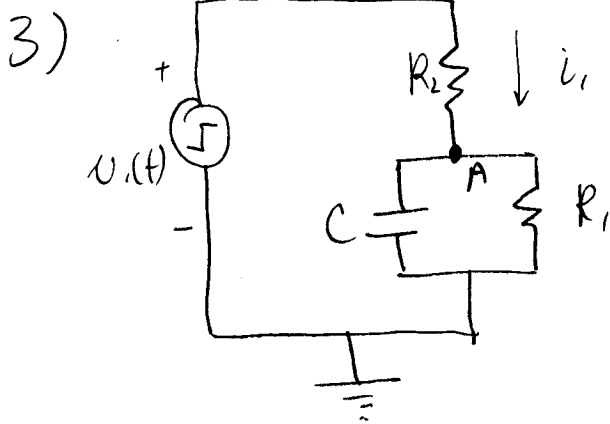


$$R_1 = 1k\Omega, R_2 = 2k\Omega, C = 10\mu F$$

a) $V_A(t=0^-) \Rightarrow$ At steady state, $C = \text{open}$;
thus
$$V_A = \frac{R_1}{R_1 + R_2} V_1 = \frac{1k}{1k + 2k} (1) = \frac{1}{3} V$$

b) $V_A(t=0^+) \Rightarrow$ Since the voltage across a capacitor cannot change instantaneously,
$$V_A(t=0^+) = V_A(t=0^-) = \frac{1}{3} V$$

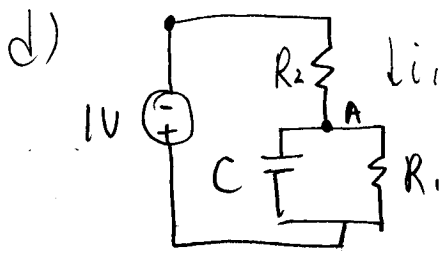
3) c) As the C is open, i_1 is simply:

$$\frac{V_1(t=0^-)}{R_1 + R_2} = \frac{1V}{1k + 2k} = \frac{1}{3} mA$$




$V_A = \frac{1}{3} V$ as shown in part (a)
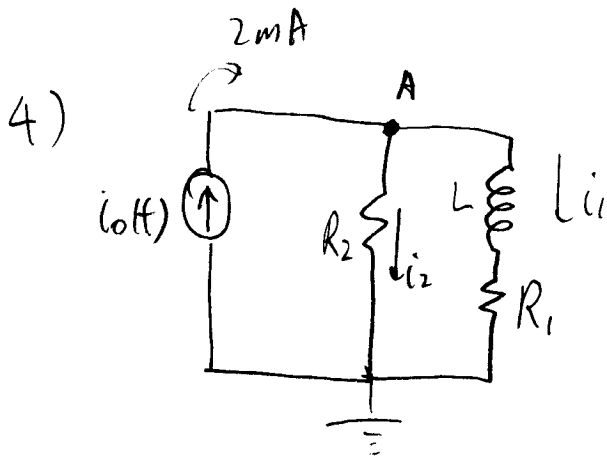
$$i_1 = \frac{\frac{1}{3} V}{2k} = \frac{-2}{3} mA$$



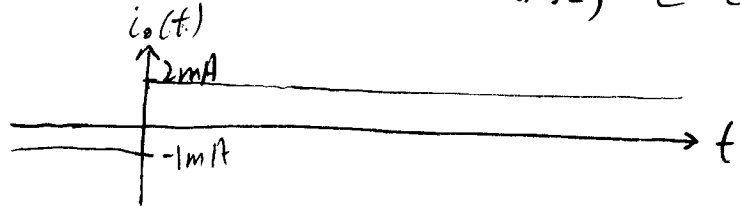$R_1 = 2k \Omega, R_2 = 3k \Omega, L = 20mH$



a) $i_1(0^-) \Rightarrow L$ becomes short in steady state
 $= \frac{R_2}{R_1 + R_2} i_0(0^-) = \frac{3k}{3k + 2k} (-1mA) = \frac{-3}{5} mA$

b) $i_1(0^+) \Rightarrow$ Current across L cannot change instantaneously $\Rightarrow i_1(0^+) = \frac{-3}{5} mA$

c) $i_2(0^-) \Rightarrow$ By KCL = $\frac{-2}{5} mA$

d) $i_2(0^+) \Rightarrow$ By KCL = $2mA + \frac{3}{5} mA = 2\frac{3}{5} mA$

$$4) \quad c) \quad V_A(0^-) \Rightarrow i_1 R_1 = \left(\frac{-3}{5} \text{ mA}\right) (2000 \Omega) \\ = -\frac{6}{5} \text{ V}$$

$$f) \quad V_A(0^+) \Rightarrow i_2 R_2 = \left(2 \frac{3}{5} \text{ mA}\right) (3000 \Omega) \\ = 6 \frac{9}{5} \text{ V}$$

5) Want: $\frac{d}{dt}(V_A)$, $t=0^+$

$$V_A = i_2 R_2 = i_1 R_1 + L \frac{di_1}{dt} \Rightarrow \frac{dV_A}{dt} = R_1 \frac{di_1}{dt} + L \frac{d^2 i_1}{dt^2}$$

We know $i_1(0^+) = \frac{-3}{5} \text{ mA}$

$$\text{and as } t \rightarrow \infty \quad i_1 = \frac{R_2}{R_1 + R_2} (2 \text{ mA}) = \frac{3k}{2k + 3k} = \frac{6}{5} \text{ mA}$$

We have

$$i_1(t) = i_{\text{final}} + (i_0 - i_{\text{final}}) e^{-t/\tau}$$

$$= \frac{6}{5} \text{ mA} + \left(\frac{-3}{5} - \frac{6}{5}\right) \text{ mA} e^{-t/\tau}$$

$$= \frac{6}{5} \text{ mA} - \frac{9}{5} \text{ mA} e^{-t/4 \times 10^{-6} \text{ s}}$$

$$\tau = \frac{L}{R} = \frac{20 \text{ mH}}{2k + 3k} \\ = 4 \times 10^{-6}$$


$$\frac{di_1}{dt} = -\frac{9}{5} \text{ mA} \left(\frac{-1}{4 \times 10^{-6}}\right) e^{-t/4 \times 10^{-6}}$$

$$\frac{d^2 i_1}{dt^2} = -\frac{9}{5} \text{ mA} \left(\frac{-1}{4 \times 10^{-6}}\right)^2 e^{-t/4 \times 10^{-6}}$$

$$\frac{dV_A}{dt} \Big|_{t=0} = 2k \left(\frac{-9}{5} \text{ mA} \left(\frac{-1}{4 \times 10^{-6}}\right)\right) + 20 \text{ mH} \left(\frac{-9}{5} \text{ mA}\right) \left(\frac{-1}{4 \times 10^{-6}}\right)^2$$

$$= -135.0000 = -1.35 \text{ MV/s}$$

b)

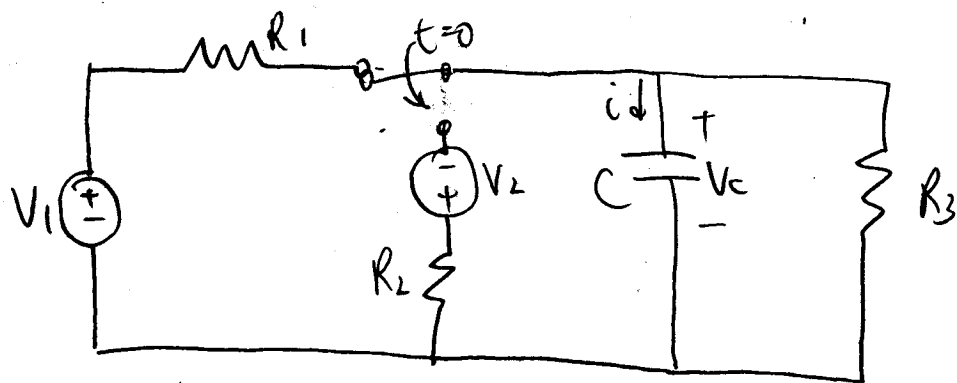

$$V_1 = 4V, V_2 = 3V, R_1 = 50 \Omega, R_2 = 100 \Omega, R_3 = 200 \Omega, C = 60 \mu F$$

a) In steady state, V_c is equal to voltage across R_3 because C is open circuit.

$$V_c(t=0) = \frac{R_3}{R_1 + R_3} V_1 = \frac{200}{50 + 200} (4V) = 3.2V$$

b) Capacitor voltage cannot change instantaneously
 $V_c(0^+) = 3.2V$

c) As $t \rightarrow \infty$, C is again an open circuit, therefore is equal to $-\left(\frac{R_3}{R_2 + R_3}\right) V_2$
 $= -\left(\frac{200}{100 + 200}\right) 3V = -2V$
 (negative because of sign reference)

d) The capacitor sees 2 resistors (R_2, R_3) in parallel, therefore $\tau = R_{eq} C$
 $= (R_2 \parallel R_3) C$
 $= \frac{100(200)}{100 + 200} (60 \times 10^{-6})$
 $= 0.004s$

b) e)

Using formulas in the book / lecture notes,
we have

Initial voltage across cap = 3.2V

As $t \rightarrow 0$, $V_c(t) \rightarrow -2V$


Therefore, we have

$$\begin{aligned}V_c(t) &= V_{\text{final}} + (V_0 - V_{\text{final}}) e^{-t/RC} \\&= -2V + (3 - (-2)) e^{-t/RC} \\&= -2V + 5 e^{-t/0.004} \quad \text{for } t \geq 0\end{aligned}$$

f) For Capacitor, $i_c = C \frac{dV_c}{dt}$


$$\begin{aligned}\text{Therefore } i_c(t) &= \frac{d}{dt} V_c(t) \\&= 5 e^{-t/0.004} \left(-\frac{1}{0.004} \right) \\&= -1250 e^{-t/0.004}\end{aligned}$$

7)

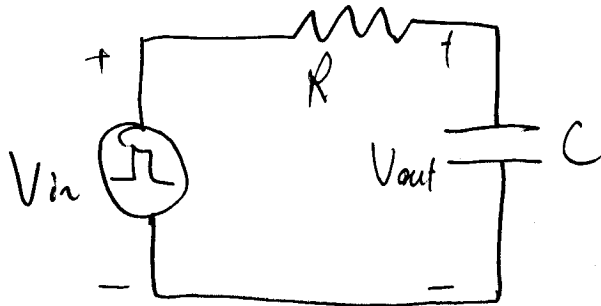

$$R = 400 \Omega$$

$$C = 0.001 \mu\text{F}$$

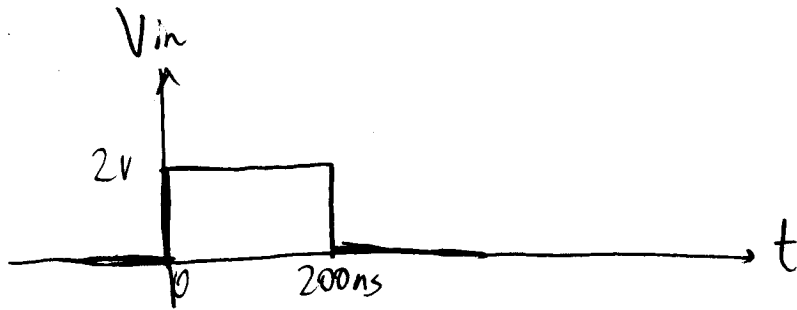

$$\begin{aligned} \text{a) } \tau &= RC = 400 (0.001 \times 10^{-6}) \\ &= 4 \times 10^{-7} \text{ s} \end{aligned}$$

Initially, $V_{\text{out}} = 0 \text{ V}$, therefore we have

$$\begin{aligned} V_{\text{out}}(t) &= V_{\text{in}} (1 - e^{-t/RC}) \\ &= 2 \text{ V} (1 - e^{-t/4 \times 10^{-7} \text{ s}}) \end{aligned}$$

b) We can do this in 2 steps;
we know that for $0 < t < 200 \text{ ns}$,

$$V_{\text{out}}(t) = 2 \text{ V} (1 - e^{-t/4 \times 10^{-7} \text{ s}})$$

Since $200 \text{ ns} = 2 \times 10^{-7} \text{ s}$ is not $\gg \tau$, we need to calculate $V_{\text{out}}(200 \text{ ns})$

$$\begin{aligned} V_{\text{out}}(200 \text{ ns}) &= 2 \text{ V} (1 - e^{-\frac{2 \times 10^{-7}}{4 \times 10^{-7}}}) \\ &= 2 \text{ V} (1 - e^{-\frac{1}{2}}) \approx 0.787 \text{ V} \end{aligned}$$

7) b) (Con't)

After the falling edge of the pulse,
we have $V_{out}(200\text{ns}^+) = 0.787\text{V}$


for $t > 200\text{ns}$, we have

$$\begin{aligned} V_{out}(t) &= 0 + (0.787 - 0) e^{-\frac{(t - 200\text{ns})}{400\text{ns}}} \\ &= 0.787 e^{-\frac{(t - 200\text{ns})}{400\text{ns}}} \end{aligned}$$


Therefore the total voltage is

$$V_{out}(t) = \begin{cases} 2\text{V}(1 - e^{-t/400\text{ns}}), & 0 \leq t \leq 200\text{ns} \\ 0.787 e^{-(t - 200\text{ns})/400\text{ns}}, & t > 200\text{ns} \end{cases}$$

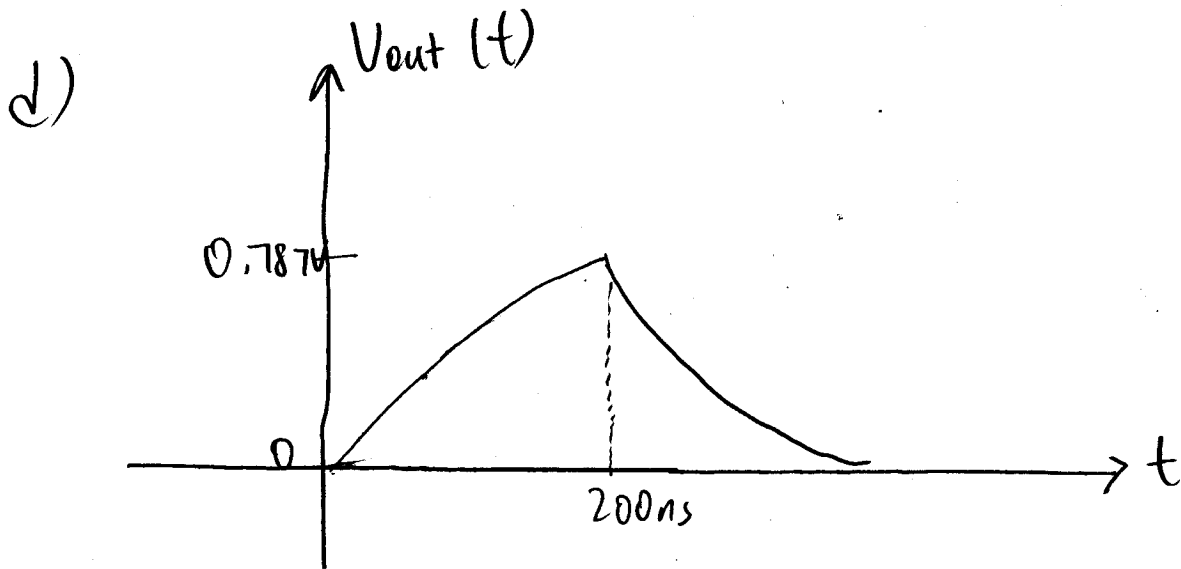c) The maximum voltage occurs at
 $t = 200\text{ns}$, $V_{out} = 0.787\text{V}$



8)

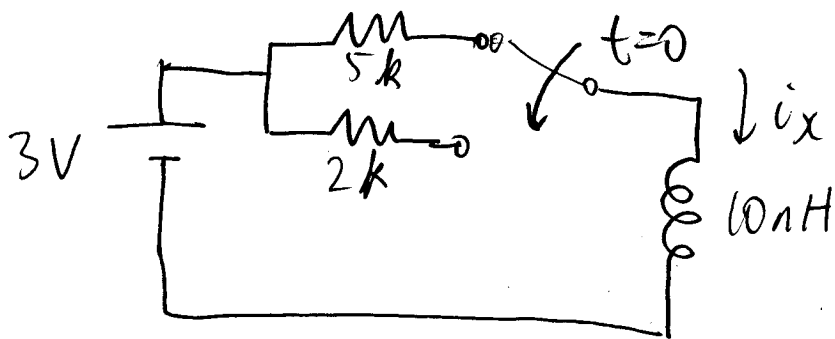

a) In steady state, inductor is short circuit $\Rightarrow i_x = \frac{3V}{5k} = 0.6 \text{ mA}$

b) Current through an inductor cannot change instantaneously, therefore $i_x(0^+) = 0.6 \text{ mA}$

c) for $t < 0$, $\tau = \frac{L}{R_1} = \frac{10 \text{ nH}}{5k} = 2 \times 10^{-12} \text{ s}$

d) for $t > 0$, $\tau = \frac{L}{R_2} = \frac{10 \text{ nH}}{2k} = 5 \times 10^{-12} \text{ s}$