
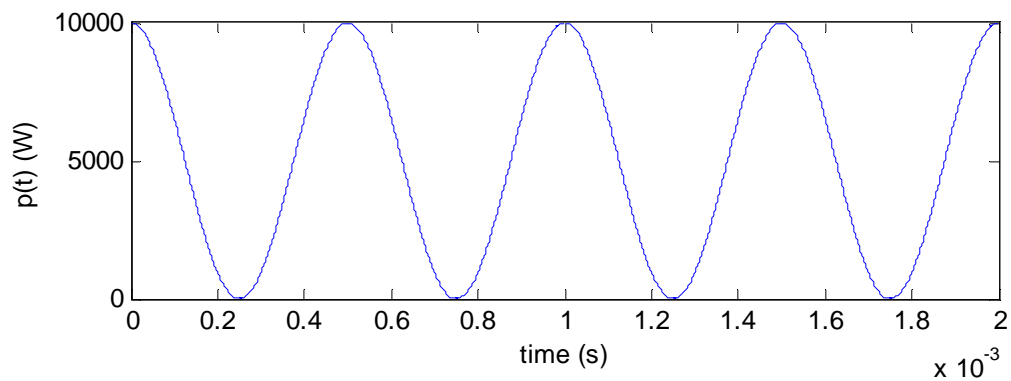


Problem 2

$$i(t) = 10 \cdot \cos(2000 \cdot \pi \cdot t)$$

$$R = 100$$
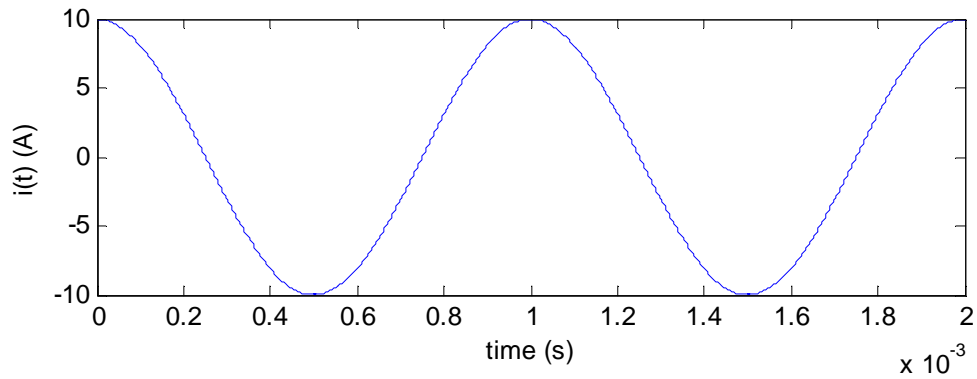
$$p(t) = i^2(t) \cdot R = 10^4 \cdot \cos^2(2000 \cdot \pi \cdot t) = \frac{10^4}{2} (1 + \cos(4000 \cdot \pi \cdot t))$$



$$P_{avg} = \frac{1}{T} \int_T p(t) dt = \frac{1}{0.5 \times 10^{-3}} \int_0^{0.5 \times 10^{-3}} \frac{10^4}{2} (1 + \cos(4000 \cdot \pi \cdot t)) dt$$
$$= \frac{10^4}{2 \cdot 0.5 \times 10^{-3}} (0.5 \times 10^{-3}) = 5000 \text{ W}$$

Problem 3

$$v(t) = 5 + 10 \cdot \cos(20 \cdot \pi \cdot t)$$

$$\begin{aligned}
V_{RMS} &= \sqrt{\frac{1}{T} \int_T v^2(t) dt} = \sqrt{\frac{1}{0.1} \int_0^{0.1} (5 + 10 \cdot \cos(20 \cdot \pi \cdot t))^2 dt} \\
&= \sqrt{10} \cdot \sqrt{\int_0^{0.1} 25 dt + 100 \cdot \int_0^{0.1} \cos(20 \cdot \pi \cdot t) + \frac{100}{2} \int_0^{0.1} (1 + \cos(40 \cdot \pi \cdot t)) dt} \\
&= \sqrt{10} \cdot \sqrt{25 \cdot 0.1 + 0 + (50 \cdot 0.1 + 0)} = \sqrt{75} = 5\sqrt{3} V_{rms}
\end{aligned}$$

Problem 4

$$v(t) = A \cdot \cos(2 \cdot \pi \cdot t) + B \cdot \sin(2 \cdot \pi \cdot t)$$

$$\begin{aligned}
v^2(t) &= A^2 \cdot \cos^2(2 \cdot \pi \cdot t) + 2AB \cdot \cos(2 \cdot \pi \cdot t) \cdot \sin(2 \cdot \pi \cdot t) + B^2 \cdot \sin^2(2 \cdot \pi \cdot t) \\
&= \frac{A^2}{2} (1 + \cos(4 \cdot \pi \cdot t)) + AB \cdot \sin(4 \cdot \pi \cdot t) + \frac{B^2}{2} \cdot (1 - \cos(4 \cdot \pi \cdot t))
\end{aligned}$$

Now, the definition of root-mean-squared:

$$\begin{aligned}
V_{RMS} &= \sqrt{\frac{1}{T} \int_T v^2(t) dt} = \sqrt{\int_0^1 \frac{A^2}{2} (1 + \cos(4 \cdot \pi \cdot t)) + AB \cdot \sin(4 \cdot \pi \cdot t) + \frac{B^2}{2} \cdot (1 - \cos(4 \cdot \pi \cdot t)) dt} \\
&= \sqrt{\frac{A^2}{2} + \frac{B^2}{2}} V_{rms}
\end{aligned}$$

Problem 5

The two voltages can be expressed as:

$$v_a(t) = 8\sqrt{2} \cos(2 \cdot \pi \cdot t + \phi_a)$$

$$v_b(t) = 3\sqrt{2} \cos(2 \cdot \pi \cdot t + \phi_b)$$

If $\phi_a = \phi_b = \phi$, then our voltages have the same phase and they add to give us our maximum voltage:

$$\begin{aligned}
v_a(t) + v_b(t) &= 8\sqrt{2} \cos(2 \cdot \pi \cdot t + \phi) + 3\sqrt{2} \cos(2 \cdot \pi \cdot t + \phi) = 11\sqrt{2} \cos(2 \cdot \pi \cdot t + \phi) \\
\Rightarrow V_{RMS, \max} &= 11
\end{aligned}$$

If $\phi_b = \phi_a \pm \pi$, then our signals are 180° out of phase, and thus our signal subtract directly from each other to give us our minimum voltage:

$$\begin{aligned}
v_a(t) + v_b(t) &= 8\sqrt{2} \cos(2 \cdot \pi \cdot t + \phi_a) + 3\sqrt{2} \cos(2 \cdot \pi \cdot t + \phi_a + \pi) \\
&= 8\sqrt{2} \cos(2 \cdot \pi \cdot t + \phi_a) - 3\sqrt{2} \cos(2 \cdot \pi \cdot t + \phi_a) = 5\sqrt{2} \cos(2 \cdot \pi \cdot t + \phi_a) \\
\Rightarrow V_{\text{RMS, min}} &= 5
\end{aligned}$$

Problem 6

$$\begin{aligned}
v_1(t) &= 10 \cdot \cos(2 \cdot \pi \cdot 200 \times 10^3 \cdot t + 30^\circ) \\
v_2(t) &= 5 \cdot \cos(2 \cdot \pi \cdot 200 \times 10^3 \cdot t + 150^\circ) \\
v_3(t) &= 10 \cdot \cos(2 \cdot \pi \cdot 200 \times 10^3 \cdot t + 90^\circ)
\end{aligned}$$

v_1 lags v_2 by 120° and lags v_3 by 60° . v_2 leads v_1 by 120° and leads v_3 by 60° . v_3 leads v_1 by 60° and lags v_2 by 60° .

Problem 7

Rewrite the sine term as a cosine:

$$4 \cdot \sin(\omega \cdot t) = 4 \cdot \cos(\omega \cdot t - \pi/4)$$

Now we have:

$$\begin{aligned}
&5 \cdot \cos(\omega t + 75^\circ) - 3 \cdot \cos(\omega t - 75^\circ) + 4 \cdot \cos(\omega t - 90^\circ) \\
&= \Re(5 \cdot e^{j(\omega t + 75^\circ)}) - \Re(3 \cdot e^{j(\omega t - 75^\circ)}) + \Re(4 \cdot e^{j(\omega t - 90^\circ)}) \\
&= \Re(e^{j\omega t} (5e^{j75^\circ} - 3e^{-j75^\circ} + 4e^{-j90^\circ}))
\end{aligned}$$

Thus we need only convert the term multiplying the $e^{j\omega t}$ into a single complex number with magnitude and phase:

$$5e^{j75^\circ} - 3e^{-j75^\circ} + 4e^{-j90^\circ} = 1.29 + j4.83 - 0.78 - j4.83 - j4 = 3.76 \angle 82^\circ$$

So our result is:

$$3.76 \cdot \cos(\omega t + 82^\circ)$$

Problem 8

Part a)

Convert the sine term into a cosine term:

$$v(t) = 100 \cdot \sin(200t + 30^\circ) = 100 \cdot \cos(200t + 30^\circ - 90^\circ) = 100 \cdot \cos(200t - 60^\circ)$$

We express the voltage and current as phasors now:

$$v = 100\angle -60^\circ \text{ and } i = 1\angle 30^\circ$$

$$Z = \frac{v}{i} = \frac{100\angle -60^\circ}{1\angle 30^\circ} = 100\angle -90^\circ$$

This is a capacitor. Since we know $\omega = 200$, we calculate the capacitor to be:

$$\frac{1}{\omega C} = 100 \Rightarrow C = 50 \mu F$$

Part b)

$$v = 500\angle 50^\circ \text{ and } i = 2\angle -40^\circ$$

$$Z = 250\angle 90^\circ$$

This is an inductor, with value:

$$\omega L = 250 \Rightarrow L = 1.25 \text{ H}$$

Part c)

$$v = 100\angle 30^\circ \text{ and } i = 1\angle -60^\circ$$

$$Z = 100\angle 90^\circ$$

This is an inductor, with value:

$$\omega L = 100 \Rightarrow L = 0.5 \text{ H}$$

Problem 9

$$Z = R + j\omega L + \frac{1}{j\omega C}$$

If $\omega = 500$:

$$Z = 50 + j(500)(100 \times 10^{-3}) + \frac{1}{j(500)(10 \times 10^{-6})} = 50 - j150 \Omega$$

If $\omega = 1000$:

$$Z = 50 + j(1000)(100 \times 10^{-3}) + \frac{1}{j(1000)(10 \times 10^{-6})} = 50 \Omega$$

If $\omega = 2000$:

$$Z = 50 + j(500)(100 \times 10^{-3}) + \frac{1}{j(500)(10 \times 10^{-6})} = 50 + j150 \Omega$$

Problem 10

The capacitor's impedance is:

$$Z_C = \frac{1}{j \cdot 500 \cdot 2 \times 10^{-6}} = -j1000 = 1000 \angle -90^\circ$$

The overall impedance is:

$$Z = 1000 - j1000 = 1414 \angle -45^\circ$$

The current then is:

$$i = \frac{v}{Z} = \frac{10 \angle 0^\circ}{1414 \angle -45^\circ} = 7.1 \times 10^{-3} \angle 45^\circ$$


The voltage across the resistor is:

$$v_R = iR = (7.1 \times 10^{-3} \angle 45^\circ) \cdot 1000 = 7.07 \angle 45^\circ$$

The voltage across the capacitor:

$$v_C = iZ_C = (7.1 \times 10^{-3} \angle 45^\circ)(1000 \angle -90^\circ) = 7.07 \angle -45^\circ$$

prob 11

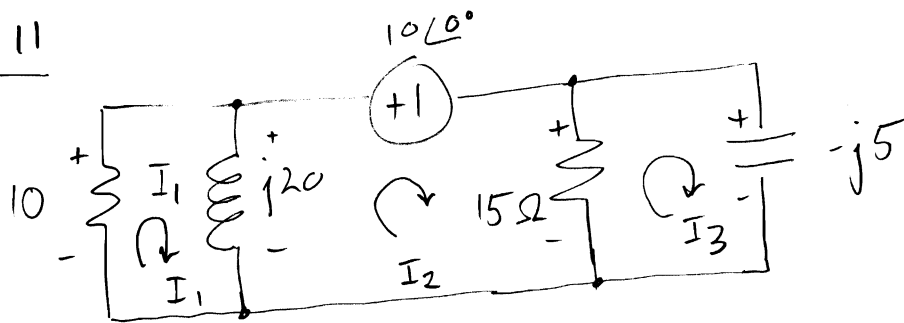

$$10I_1 = j20(I_1 - I_2)$$

$$j20(I_2 - I_1) = 10 + 15(I_2 - I_3)$$

$$15(I_3 - I_2) = -j5 \cdot I_3$$

$$\begin{bmatrix} 10 - j20 & j20 & 0 \\ -j20 & -15 + j20 & 15 \\ 0 & -15 & 15 + j5 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 0 \\ 10 \\ 0 \end{bmatrix}$$

$$\begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 0.94 \angle 150.4^\circ \\ 1.05 \angle 177.0^\circ \\ 0.997 \angle 158.6^\circ \end{bmatrix}$$

$$v_1 = -I_1 \cdot R = -(0.94 \angle 150.4^\circ) 10 = 9.4 \angle -29.6^\circ$$

$$v_2 = I_3 \cdot Z_C = (0.997 \angle 158.6^\circ)(-5 \angle -90^\circ) \\ = 4.99 \angle -111.4^\circ$$

check:

$$v_1 - v_2 = (9.4 \angle -29.6^\circ) - (4.99 \angle -111.4^\circ) = 10 \checkmark$$

Problem 12

Part a)

$$Z = \left(\frac{1}{j\omega C} \right) \parallel (R + j\omega L) = \frac{\left(\frac{1}{j\omega C} \right) (R + j\omega L)}{\frac{1}{j\omega C} + R + j\omega L} = \frac{R + j\omega L}{1 + j\omega RC - \omega^2 LC}$$

Part b)

Remembering that:

$$\frac{1}{a + jb} = \frac{a}{a^2 + b^2} - j \frac{b}{a^2 + b^2}$$

We write:

$$Z = \frac{(R + j\omega L)(1 - \omega^2 LC - j\omega RC)}{(1 - \omega LC)^2 + (\omega RC)^2} = \frac{R(1 - \omega^2 RC) + \omega^2 LRC}{(1 - \omega LC)^2 + (\omega RC)^2} + j \frac{(1 - \omega^2 LC)\omega L - \omega R^2 C}{(1 - \omega LC)^2 + (\omega RC)^2}$$

$$\begin{aligned} |Z| &= \sqrt{\frac{(R(1 - \omega^2 RC) + \omega^2 LRC)^2}{(1 - \omega LC)^2 + (\omega RC)^2} + \frac{((1 - \omega^2 LC)\omega L - \omega R^2 C)^2}{(1 - \omega LC)^2 + (\omega RC)^2}} \\ &= \frac{\sqrt{(R(1 - \omega^2 RC) + \omega^2 LRC)^2 + ((1 - \omega^2 LC)\omega L - \omega R^2 C)^2}}{(1 - \omega LC)^2 + (\omega RC)^2} \end{aligned}$$


Part c)

If we assume that $(RC)^2 \ll LC$, then our denominator becomes zero when:

$$1 - \omega^2 LC = 0 \Rightarrow \omega = \frac{1}{\sqrt{LC}}$$

Part d)

To plot $|Z|$, select $L=1$, $C=1$, and $R=0.01$. This way, our assumption is justified.

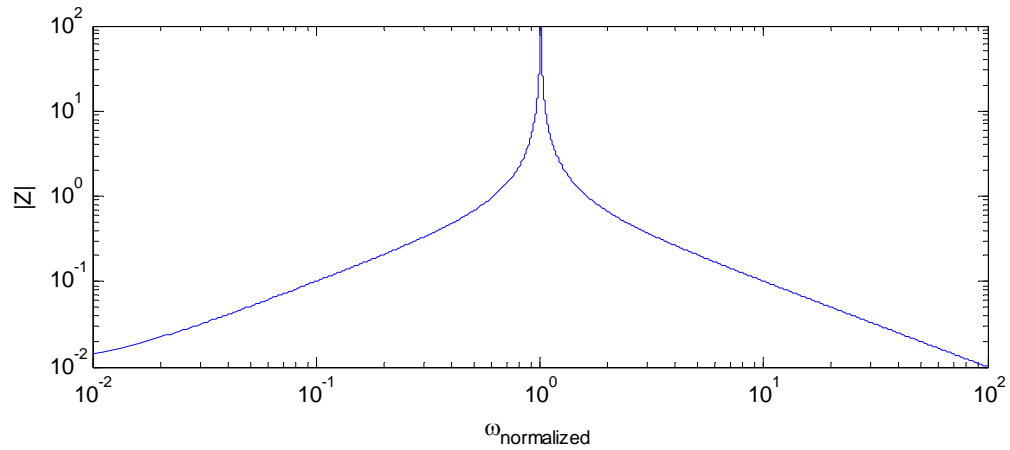

Problem 13

For the circuit in Figure a), the limits are:

$$v_{\omega \rightarrow 0} = 0$$

$$v_{\omega \rightarrow \infty} = \frac{R_2 \parallel R_3}{R_1 + R_2 \parallel R_3}$$

For the circuit in Figure b), the limits are:

$$v_{\omega \rightarrow 0} = 0$$

$$v_{\omega \rightarrow \infty} = 0$$

The parasitics have a greater effect at higher frequencies.