

Homework #7 Solutions

Prepared by Lynn Wang



Ting 918 @ eecs.berkeley.edu

P 11. 2

An amplifier can be characterized by:

- (1) input impedance
- (2) output impedance
- (3) gain (i.e. open-circuit voltage gain)

P 11.6 The equivalent circuit is:

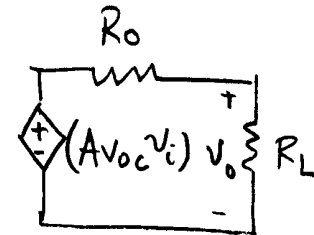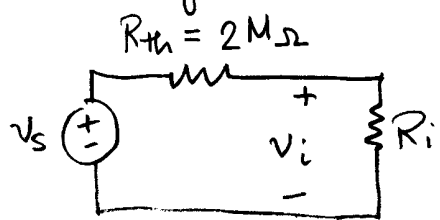

Given:

$$\left\{ \begin{array}{l} R_i = 1 \text{ M}\Omega \\ R_o = 1 \text{ k}\Omega \\ R_L = 1 \text{ k}\Omega \end{array} \right. \quad \begin{array}{l} V_s = 3 \cos(200\pi t) \text{ mV} \\ A_{voc} = -10^4 \end{array}$$

$$V_i(t) = \frac{R_i}{R_i + R_{th}} \cdot V_s = \frac{10^6}{10^6 + 2 \times 10^6} (3 \times 10^{-3} \cos(200\pi t))$$

$$= 10^{-3} \cos(200\pi t) \text{ V} = \cos(200\pi t) \text{ mV}$$

$$V_o(t) = A_{voc} V_i \cdot \frac{R_L}{R_o + R_L} = -10^4 [10^{-3} \cos(200\pi t)] \left(\frac{1000}{1000 + 1000} \right)$$



$$\boxed{V_o(t) = -5 \cos(200\pi t) \text{ V}}$$

$$P_i = \frac{V_i^2(\text{rms})}{R_i} = \frac{(10^{-3}/\sqrt{2})^2}{10^6} = \frac{1}{2} \text{ pW}$$

$$P_o = \frac{V_o^2(\text{rms})}{R_L} = \frac{(5/\sqrt{2})^2}{10^3} = 12.5 \text{ mW}$$

$$G = \frac{P_o}{P_i} = \boxed{25 \times 10^9}$$

P 11.12

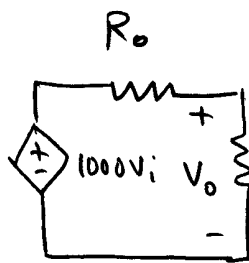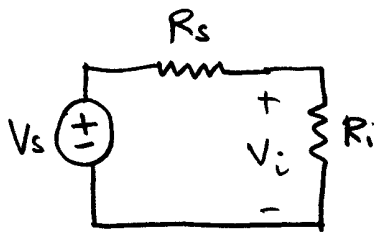

$$\left\{ \begin{array}{l} A_{voc} = 1000 \\ R_i = 20 \text{ k}\Omega \\ R_o = 2 \Omega \\ R_s = 10 \text{ k}\Omega \\ R_L = 8 \Omega \end{array} \right.$$

$$V_o = 1000 V_i \left(\frac{R_L}{R_o + R_L} \right)$$

$$A_v = \frac{V_o}{V_i} = 1000 \left(\frac{R_L}{R_o + R_L} \right) = 1000 \left(\frac{8}{2 + 8} \right) = \boxed{800}$$

$$V_i = V_s \left(\frac{R_i}{R_s + R_i} \right)$$

$$\frac{V_i}{V_s} = \frac{R_i}{R_s + R_i} = \frac{20 \times 10^3}{20 \times 10^3 + 10 \times 10^3} = \frac{2}{3}$$

$$A_{vs} = \frac{V_o}{V_s} = \frac{V_i}{V_s} \cdot \frac{V_o}{V_i} = \frac{V_i}{V_s} \cdot A_v = \left(\frac{2}{3} \right) (800) = \boxed{533.3}$$

$$A_i = \frac{V_o / R_L}{V_i / R_i} = \frac{V_o}{V_i} \cdot \frac{R_i}{R_L} = A_v \cdot \frac{R_i}{R_L} = 800 \left(\frac{20 \text{ k}}{8} \right)$$

$$= \boxed{2 \times 10^6}$$


$$G = A_v \cdot A_i = 800 (2 \times 10^6) = \boxed{1.6 \times 10^9}$$

P 14.8 Inverting Amplifier


$$A_v = -\frac{R_2}{R_1} = -3$$

$$V_o(t) = -3(2 \cos(2000\pi t)) = -6 \cos(2000\pi t) \text{ V}$$

$v_{in}(t)$

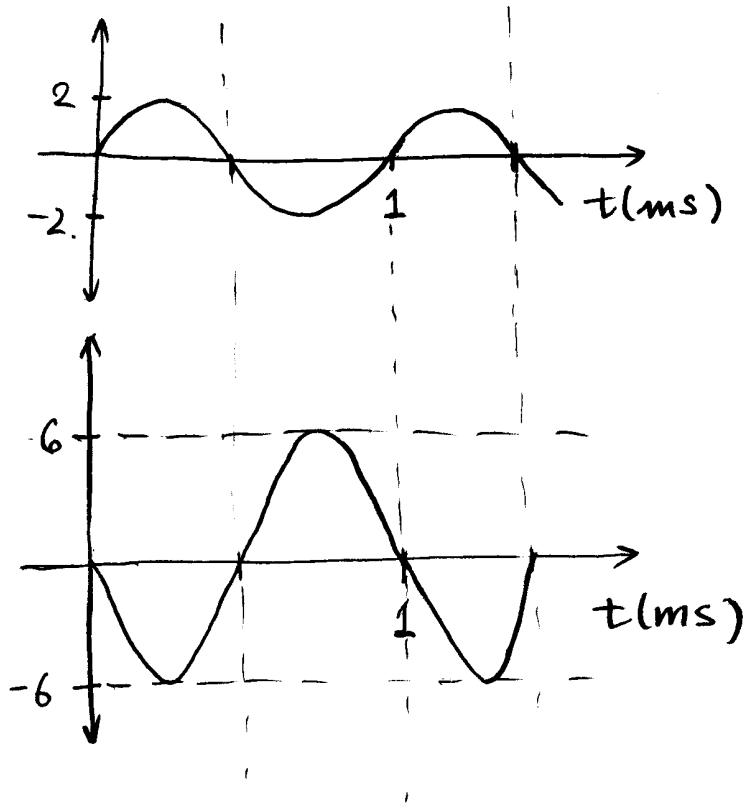

P 14.9

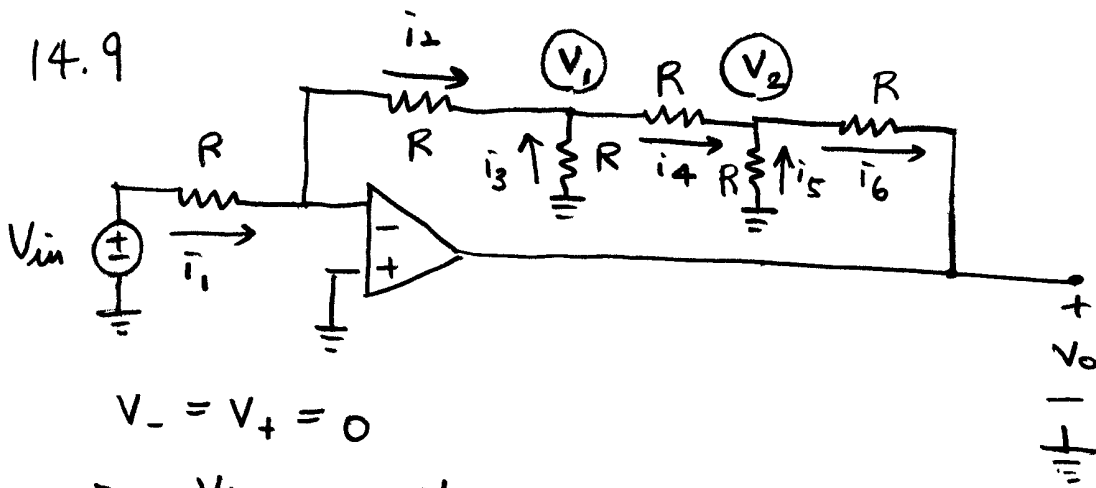

$$V_- = V_+ = 0$$

$$\bar{i}_1 = \frac{V_{in} - 0}{R} = \frac{V_{in}}{R}$$

$$\bar{i}_1 = i_2$$

$$i_2: \frac{0 - V_1}{R} = \frac{V_{in}}{R}$$

$$V_1 = -V_{in}$$

$$\bar{i}_3 = \frac{0 - V_1}{R} = \frac{-V_1}{R} = \frac{V_{in}}{R}$$

$$\bar{i}_4 = \bar{i}_2 + i_3 = \frac{V_{in}}{R} + \frac{V_{in}}{R} = \frac{2V_{in}}{R}$$

$$i_4: \frac{V_1 - V_2}{R} = \frac{2V_{in}}{R} \Rightarrow V_1 - V_2 = 2V_{in}$$

$$V_2 = V_1 - 2V_{in} = -V_{in} - 2V_{in} = -3V_{in}$$

$$i_5: \frac{0 - V_2}{R} = \frac{3V_{in}}{R}$$


$$\bar{i}_6 = \bar{i}_4 + i_5 = \frac{2V_{in}}{R} + \frac{3V_{in}}{R} = \frac{5V_{in}}{R}$$

$$i_6: \frac{V_2 - V_o}{R} = \frac{5V_{in}}{R}$$

$$V_2 - V_o = 5V_{in} \Rightarrow V_o = V_2 - 5V_{in} = -3V_{in} - 5V_{in} = -8V_{in}$$

$$A_v = \frac{V_o}{V_{in}} = -8$$

P 14.10

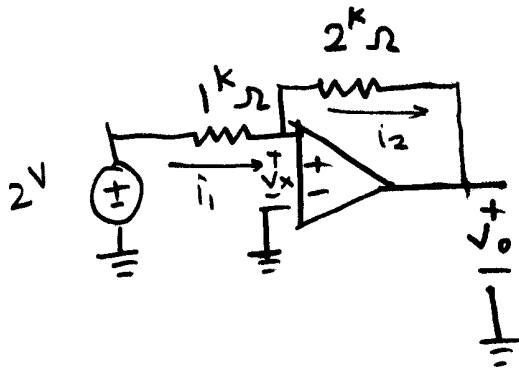

This circuit has positive feedback, and the output swings from -10^V to $+10^V$.

Writing a current equation in terms of v_x and v_o :

$$i_1 = i_2$$

$$\frac{2 - v_x}{1k} = \frac{v_x - v_o}{2k}$$

$$\frac{2}{1k} - \frac{v_x}{1k} = \frac{v_x}{2k} - \frac{v_o}{2k}$$

$$\frac{2}{1k} + \frac{v_o}{2k} = \frac{v_x}{1k} + \frac{v_x}{2k}$$

$$v_x \left(\frac{1}{1k} + \frac{1}{2k} \right) = \frac{2}{1k} + \frac{v_o}{2k}$$

$$v_x = \frac{\frac{2}{1k} + \frac{v_o}{2k}}{\frac{1}{1k} + \frac{1}{2k}} = 1.3333 + 0.3333 v_o$$




For $v_o = 10^V$

$$v_x = 1.3333 + 0.3333(10^V) \approx \boxed{4.6^V} \quad (4.3^V \text{ o.k.})$$


For $v_o = -10^V$

$$v_x = 1.3333 + 0.3333(-10^V) \approx \boxed{-2^V}$$

P 14.17

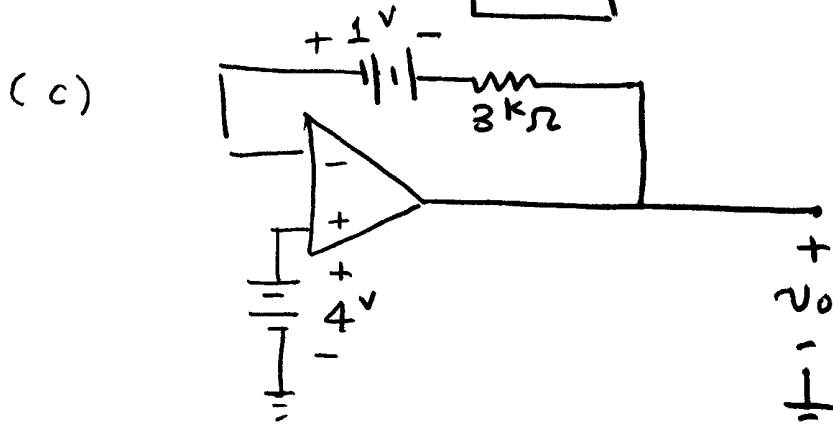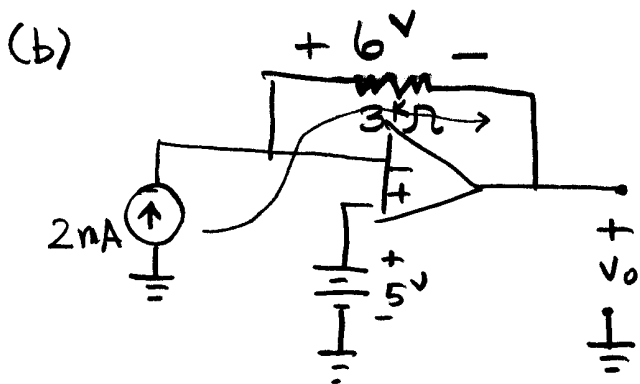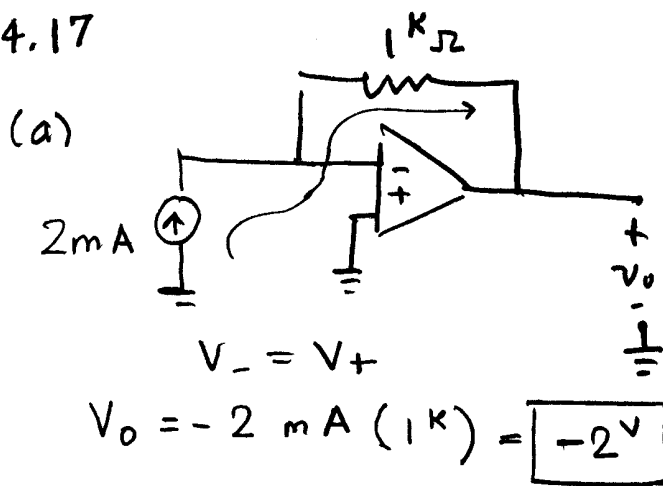


(d)

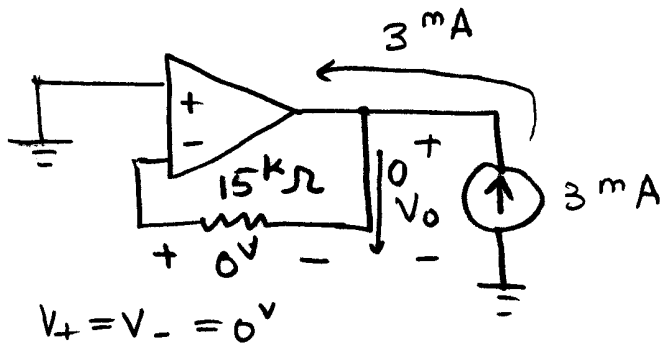

- \therefore No current may flow into V_+ and V_- terminals.
Thus, there is no current flowing across the $15\text{ k}\Omega$ resistor.


$$V_0 = 0\text{ V}$$

(e)

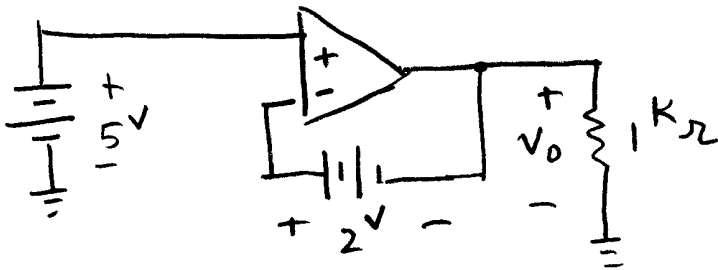

$$V_0 = 5 - 2 = 3\text{ V}$$

P 14.18

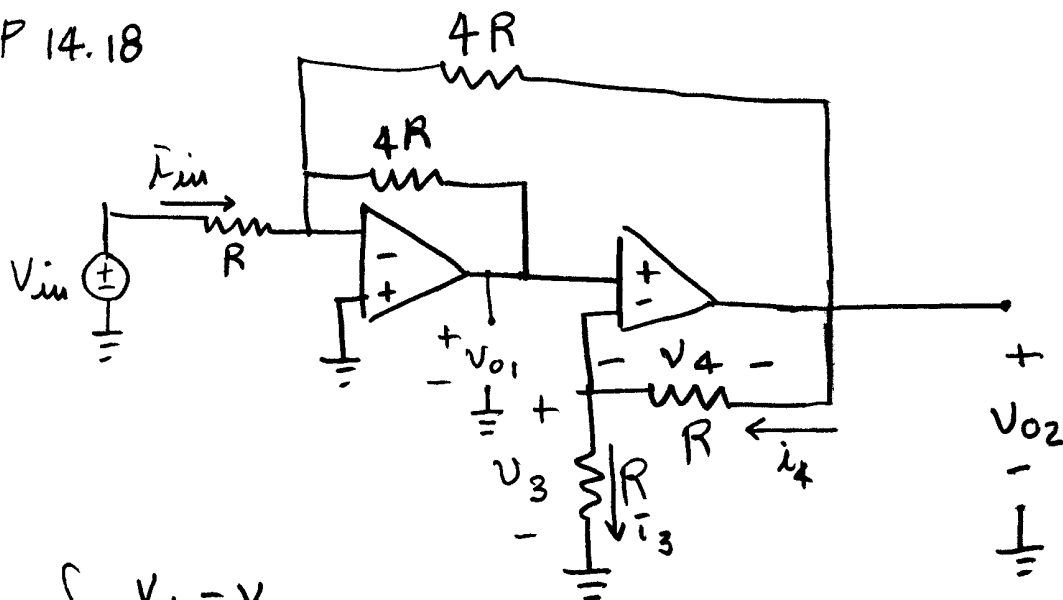

$$\begin{cases} v_+ = v_- \\ v_{o1} = v_3 \end{cases}$$

$$\begin{cases} i_4 = i_3 = \frac{v_{o1}}{R} \\ v_4 = v_3 = v_{o1} \end{cases}$$

$$v_{o2} = v_3 + v_4 = 2v_{o1} \quad (1)$$

$$i_{in} + \frac{v_{o1}}{4R} + \frac{v_{o2}}{4R} = 0$$

$$i_{in} = \frac{v_{in}}{R}$$

$$\frac{v_{in}}{R} + \frac{v_{o1}}{4R} + \frac{v_{o2}}{4R} = 0 \quad (2)$$

For A_1 :

Substitute into (2): $v_{o2} = 2v_{o1} \quad (1)$

$$\frac{v_{in}}{R} + \frac{v_{o1}}{4R} + \frac{2v_{o1}}{4R} = 0$$

$$\frac{v_{in}}{R} = -\frac{3v_{o1}}{4R}$$


$$A_1 = \frac{v_{o1}}{v_{in}} = -\frac{4}{3}$$

For A_2 :

$$A_2 = \frac{v_{o2}}{v_{in}} = \frac{2v_{o1}}{v_{in}} = 2 \left(-\frac{4}{3} \right)$$

$$A_2 = -\frac{8}{3}$$

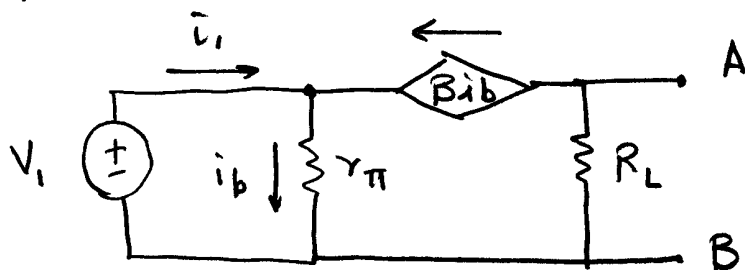(4.9) $V_i = 2V$
 $Y_{\pi} = 2.5k\Omega$
 $R_L = 5k\Omega$
 $\beta = 100$




Find i_1 .

$$\bar{i}_1 + \beta i_b = i_b$$


$$\bar{i}_1 = i_b - \beta i_b = i_b (1 - \beta)$$

$$i_b = \frac{V_i}{Y_{\pi}} = \frac{2V}{2.5k\Omega}$$
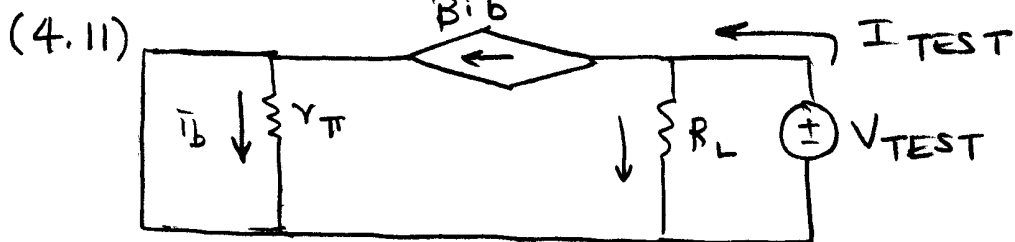
$$\bar{i}_1 = \frac{2V}{2.5k\Omega} (1 - 100) = \boxed{-79.2 \text{ mA}}$$



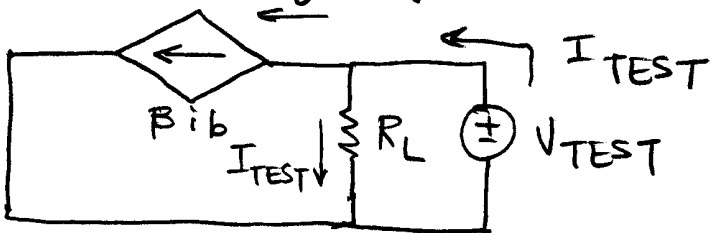
$i_b = 0$, since voltage supply is shorted.




$$V_{TEST} = I_{TEST} \cdot R_L$$

$$R_{th} = \frac{V_{TEST}}{I_{TEST}} = R_L$$

(4.12)

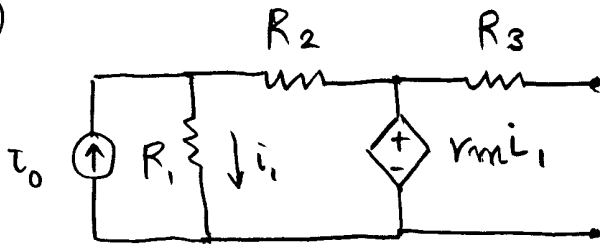

open current sources.

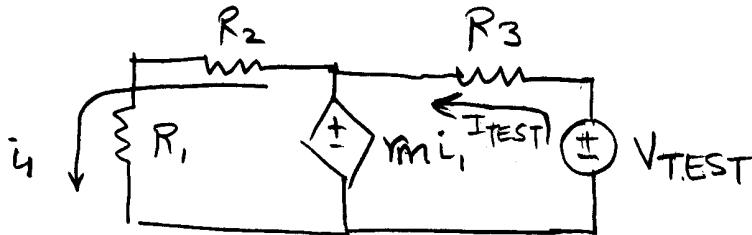

$$\text{KVL: } V_{\text{TEST}} - I_{\text{TEST}} R_3 - y_m i_1 = 0$$

i_1 must flow through R_2 :

$$y_m i_1 - i_1 R_2 - i_1 R_1 = 0$$


$$\textcircled{1} \quad y_m = R_1 + R_2 \quad \underline{\text{OK.}}$$

$\textcircled{2}$ If assume $y_m \neq R_1 + R_2$

$$i = 0$$

$$\boxed{R_{\text{th}} = R_3}$$

Circuit could be represented as:

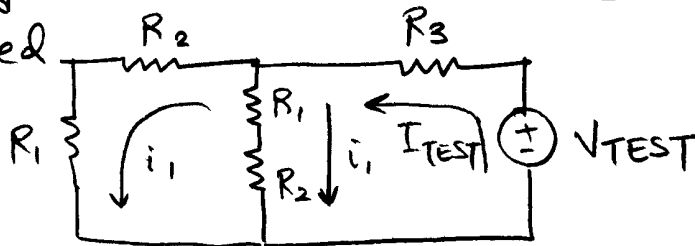


$$I_{\text{TEST}} = i_1 + i_1 = 2i_1$$

$$i_1 = \frac{I_{\text{TEST}}}{2}$$

$$V_{\text{TEST}} - I_{\text{TEST}} R_3 - y_m \left(\frac{I_{\text{TEST}}}{2} \right) = 0$$

$$V_{\text{TEST}} = I_{\text{TEST}} \left(R_3 + \frac{y_m}{2} \right)$$
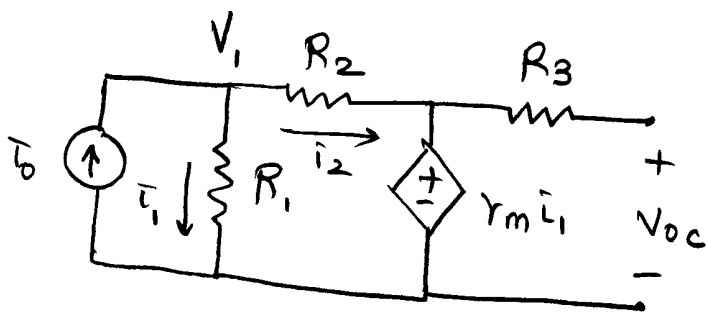
$$R_{\text{th}} = \frac{V_{\text{TEST}}}{I_{\text{TEST}}} = \boxed{R_3 + \frac{y_m}{2}}$$



No current flowing across R_3 , open circuit.

$$\therefore V_{oc} = y_m i_1$$

$$i_0 = i_1 + i_2$$

$$i_0 = \frac{V_1}{R_1} + \frac{V_1 - y_m i_1}{R_2}$$

$$V_1 = i_1 R_1$$

$$i_0 = \frac{i_1 R_1}{R_1} + \frac{i_1 R_1 - y_m i_1}{R_2}$$

$$i_0 = i_1 \left(1 + \frac{R_1 - y_m}{R_2} \right)$$

$$i_0 = i_1 \left(\frac{R_2 + R_1 - y_m}{R_2} \right)$$

$$i_1 = i_0 \left(\frac{R_2}{R_2 + R_1 - y_m} \right)$$

$$\therefore V_{oc} = y_m i_1 = y_m \left(\frac{R_2}{R_2 + R_1 - y_m} \right) i_0$$

$$V_{Th} = V_{oc} = \frac{i_0 y_m R_2}{R_1 + R_2 - y_m}$$