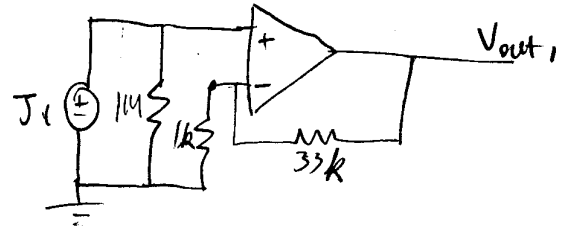


EE100 Problem Set 9 - Soln

2) IC1-a



$$\frac{J_1}{1k} + \frac{J_1 - V_{out1a}}{33k} = 0$$

$$J_1 \left( 1 + \frac{1}{33} \right) = \frac{V_{out1a}}{33}$$

$$V_{out1a} = 34 J_1 \Rightarrow A_{1a} = 34$$

IC1-b

By symmetry, this is the same as IC1-a


$$A_{1b} = 34$$

IC2-b

By symmetry again, this is the same as IC2-a

$$A_{2b} = -1$$

IC2-a

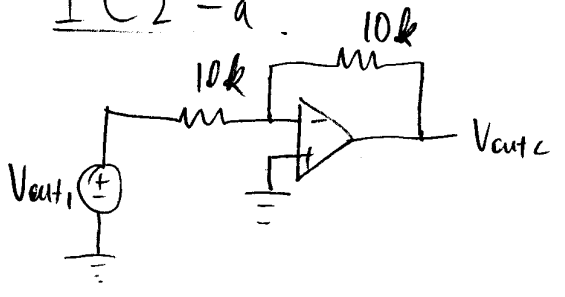

$$\frac{0 - V_{out1a}}{10k} + \frac{0 - V_{out2}}{10k} = 0$$

$$V_{out2} = -V_{out1a} \Rightarrow A_{2a} = -1$$


IC3-b

By symmetry, this is the same as IC3-a

IC3-a

$$A_{3a} = -10$$

IC3-a

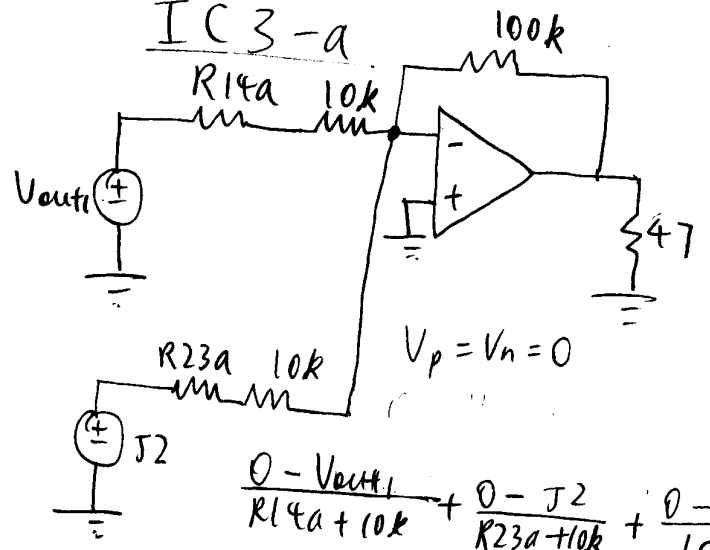

$$\frac{0 - V_{out1}}{R14a + 10k} + \frac{0 - J2}{R23a + 10k} + \frac{0 - V_{out}}{100k} = 0$$

$$V_{out} = -100k \left( \frac{V_{out1}}{R14a + 10k} + \frac{J2}{R23a + 10k} \right)$$

Gain from  $V_{out1a}/V_{out2a} = \frac{-100k}{R14a + 10k}$

Gain from  $J2 = \frac{-100k}{R23a + 10k}$






For maximum signal amplitude

$$R14a/R14b \rightarrow 0k \Rightarrow \frac{-100k}{10k} = -10$$


$$R23a/R23b \rightarrow 0k \Rightarrow \frac{-100k}{10k} = -10$$

$$A_{3a} = -10$$

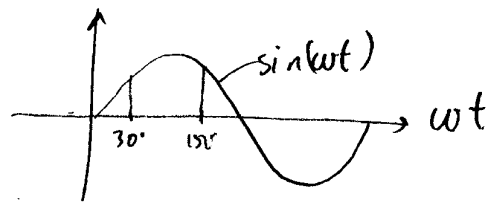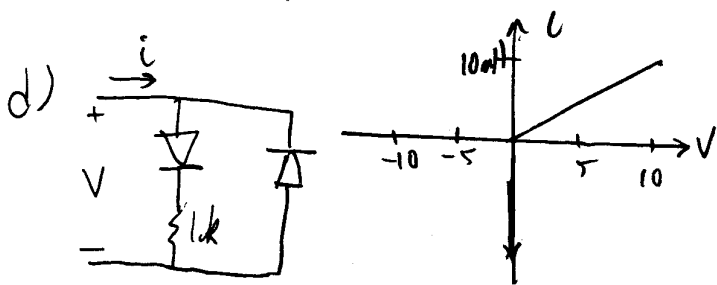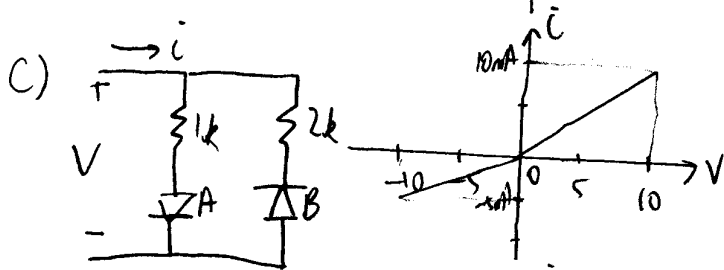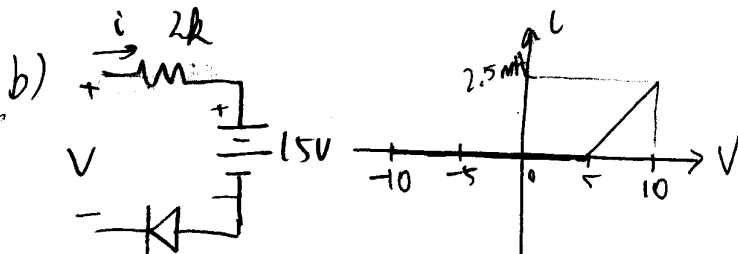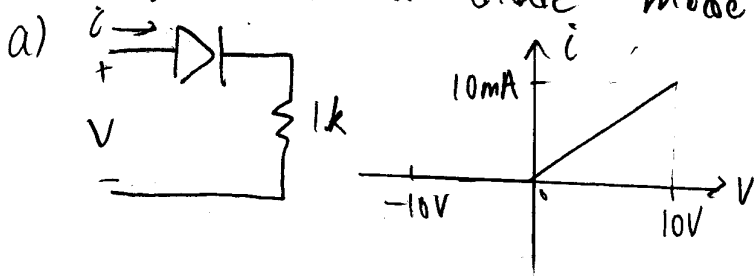3) P10.35  $\Rightarrow$  Ideal diode model,  $V$  ranges from  $-10V$  to  $10V$



4) 10.44

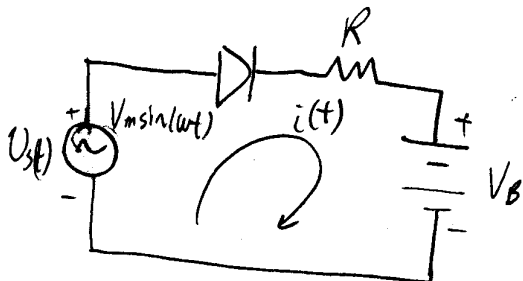

$V_m = 24V$ ,  $f = 60Hz$ ,  $R = 2\Omega$ ,  $V_B = 12V$ ,  
Ideal diode

$\Rightarrow$  Diode on when  $V_m \sin(\omega t) > V_B$

$$24 \sin(\omega t) \geq 12V$$

$$\sin(\omega t) \geq \frac{1}{2} \Rightarrow \omega t \geq 30^\circ / \frac{\pi}{6}$$

$$i(t) = \frac{24 \sin(\omega t) - 12V}{2\Omega} = 12 \sin(\omega t) - 6 A$$

$$2\pi f = \omega \Rightarrow \omega = 120\pi$$

4) (Cont)

$$\begin{aligned} \text{The } Q(t) \text{ is } & \int_{0/6}^{5\pi/6} 12 \sin(120\pi t) - 6 dt \\ & = \left[ -\frac{12}{120\pi} \cos(120\pi t) - 6t \right]_{0/6}^{5\pi/6} = \frac{12\sqrt{3} - 4\pi}{120\pi} \end{aligned}$$

$$\begin{aligned} \text{Total Charge in 1 sec } \Rightarrow Q(t) \text{ (60 sec)} \\ & = \frac{12\sqrt{3} - 4\pi}{2\pi} = \frac{6\sqrt{3}}{\pi} - 2 \approx 1.308 A \end{aligned}$$


$$\begin{aligned} \text{Time required for} \\ \text{battery } T & = \frac{100}{1.308} = 76.45 \text{ hr} \end{aligned}$$

5) 10.46

$$\begin{aligned} \text{a) } V_{\text{avg}} & = \frac{1}{T} \int_0^T v(t) dt \quad T = \frac{1}{f} = \frac{2\pi}{\omega} \\ & = \frac{1}{2\pi} \int_0^{2\pi/\omega} V_m \sin(\omega t) dt \\ & = \frac{1}{2\pi} V_m [\cos(\omega t)]_0^{2\pi/\omega} = 0 \end{aligned}$$

b) Half-wave rectified  $\Rightarrow$  only half period


$$\begin{aligned} V_{\text{avg}} & = \frac{\omega}{2\pi} \int_0^{\pi/\omega} V_m \sin(\omega t) dt \\ & = \frac{1}{2\pi} V_m [\cos(\omega t)]_0^{\pi/\omega} \\ & = \frac{2V_m}{2\pi} = \frac{V_m}{\pi} \end{aligned}$$

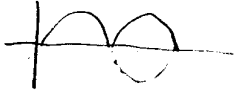c) Full-wave  $\Rightarrow$    
2 times the half-wave version

$$V_{\text{avg}} = \frac{2V_m}{\pi}$$

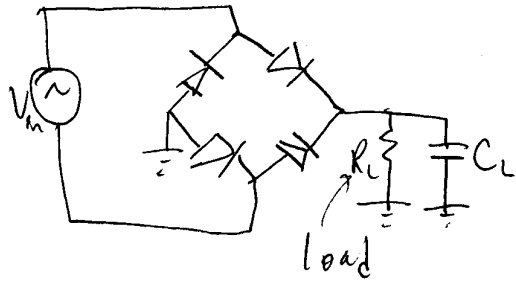6) 10.48

$V_{avg} = 9V$ ,  $V_r = 2V$ ,  $I_{avg} = 100mA$   
 Ideal diodes,  $f = 60Hz$




Using equation from P. 464,

$$C_L = \frac{I_c T}{2V_r} = \frac{(100mA) (\frac{1}{60})}{2(2)} = 417 \mu F$$


7) 10.53

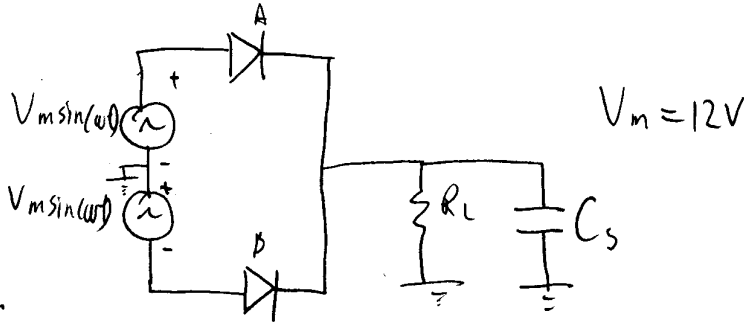a) The maximum voltage on the capacitor is  $V_m$ , and the minimum voltage on the source is





$-V_m \Rightarrow$  total reverse bias  $= 2V_m$ .

b)

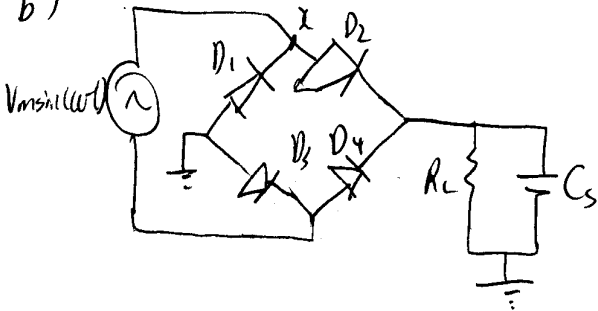

lets assume  $D_1$  and  $D_3$  are on, that means the max voltage at  $x$  is  $V_m$  and the max reverse bias is  $V_m \Rightarrow$  by symmetry this is true for all diodes

8) 10.55

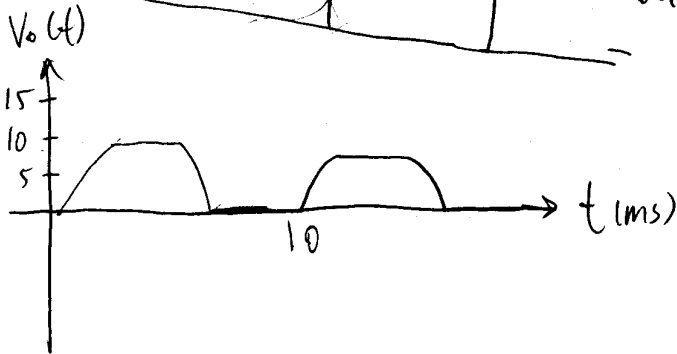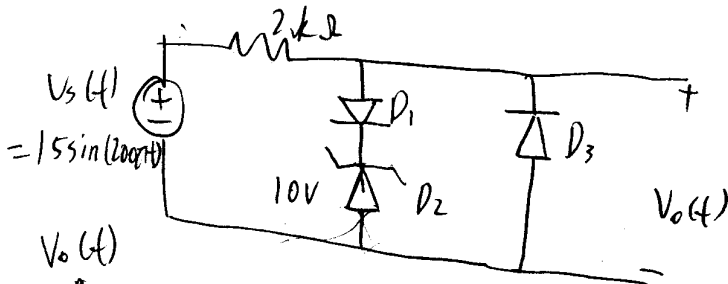


for  $V_s(t) < 0$ ,  $D_3$  turns on  $\rightarrow$  shorts  $\Rightarrow V_o(t) \rightarrow 0$

for  $V_s(t) > 0$ , we have 2 regions of operation  $\Rightarrow 0 < V_s < 10$  and  $V_s \geq 10$

for  $0 < V_s < 10$ , the Zener diode is off and thus  $V_o(t) = V_s(t)$

for  $V_s \geq 10$ , the  $D_1$  is on and  $D_2$  has 10V across it for breakdown mode operation  $V_o(t) \rightarrow 10V$

a) 10.61

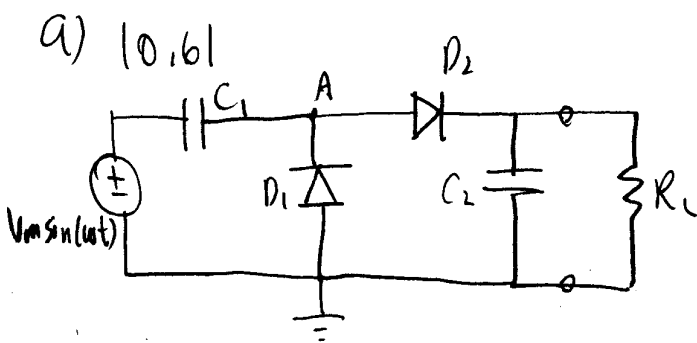

By looking at the combination of  $C_1$  and  $D_1$ , we can see that the diode conducts if  $V_{in} < 0$ , therefore we know the minimum voltage at the output is  $0V$ . (Center point moved to  $V_m$ )  
 $D_2$  and  $C_2$  together forms a half-wave rectifier and thus  $V_L(t) \approx 2V_m$ . This is called a voltage-doubler because the load voltage is twice  $V_m$ . The PIV for both diodes are  $2V_m$  also.