

# **Quick introduction to phasor analysis for the RC filter lab**

**Very brief introduction to phasors**

**Using phasors to analyze a low-pass  
RC filter circuit**

# “PHASORS”

**You can solve AC circuit analysis problems that involve Circuits with linear elements (R, C, L) plus independent and dependent voltage and/or current sources operating at a single angular frequency  $\omega = 2\pi f$  (radians/s) such as  $v(t) = V_0 \cos(\omega t)$  or  $i(t) = I_0 \cos(\omega t)$**

**By using any of Ohm's Law, KVL and KCL equations, doing superposition, nodal or mesh analysis, AND**

**Using instead of the functions of time below on the left, the phasor expressions below on the right:**

## RESISTOR I-V relationship in terms of

$v(t)$  and  $i(t)$  OR phasor voltage  $V_R$  and phasor current  $I_R$  (not functions of time)

$$v_R = i_R R$$

$$V_R = I_R R \text{ where } R \text{ is the resistance in ohms,}$$

$V_R$  = phasor voltage,  $I_R$  = phasor current  
(boldface indicates complex quantity)

## CAPACITOR I-V relationship in terms of

$v(t)$  and  $i(t)$  OR phasor voltage  $V_C$  and phasor current  $I_C$  (not functions of time)

$$i_C = C dv_C / dt$$

$$I_C = V_C / Z_C, \text{ with capacitive impedance } Z_C = 1 / j\omega C, \text{ where}$$

$j = (-1)^{1/2}$  and boldface type indicates a complex quantity

$$\text{Thus, } I_C = j\omega C V_C$$

[We'll see later that the  $\omega$  comes from the time derivative of a sinusoidal voltage  $v_c(t) = V_C \cos(\omega t)$ , etc.]

## INDUCTOR I-V relationship in terms of

$v(t)$  and  $i(t)$  OR phasor voltage  $V_L$  and phasor current  $I_L$  (not functions of time)

$$v_L = L di_L / dt$$

$$V_L = I_L Z_L, \text{ with inductive impedance } Z_L = j\omega L, \text{ where}$$

$j = (-1)^{1/2}$  and boldface type indicates a complex quantity

$$\text{Thus, } V_L = j\omega L I_L$$

[We'll see later that the  $\omega$  comes from the time derivative of a sinusoidal current  $i_L(t) = I_L \cos(\omega t)$ , etc.]

$$\begin{aligned} v_R &= i_R R \\ i_C &= C dv_C / dt \\ v_L &= L di_L / dt \end{aligned}$$


Use with steady  
or transient  
sources

$$\begin{aligned} V_R &= I_R R \\ I_C &= V_C / Z_C = (j\omega C) V_C \\ V_L &= I_L Z_L = (j\omega L) I_L \end{aligned}$$

Use with single-  
frequency  
sinusoidal sources

## Using phasors to analyze a low-pass RC filter

Consider the circuit shown below. We want to use phasors and complex impedances to find how the ratio  $|V_{\text{out}}/V_{\text{in}}|$  varies as the frequency of the input sinusoidal source changes. This circuit is a filter; how does it treat the low frequencies and the high frequencies?

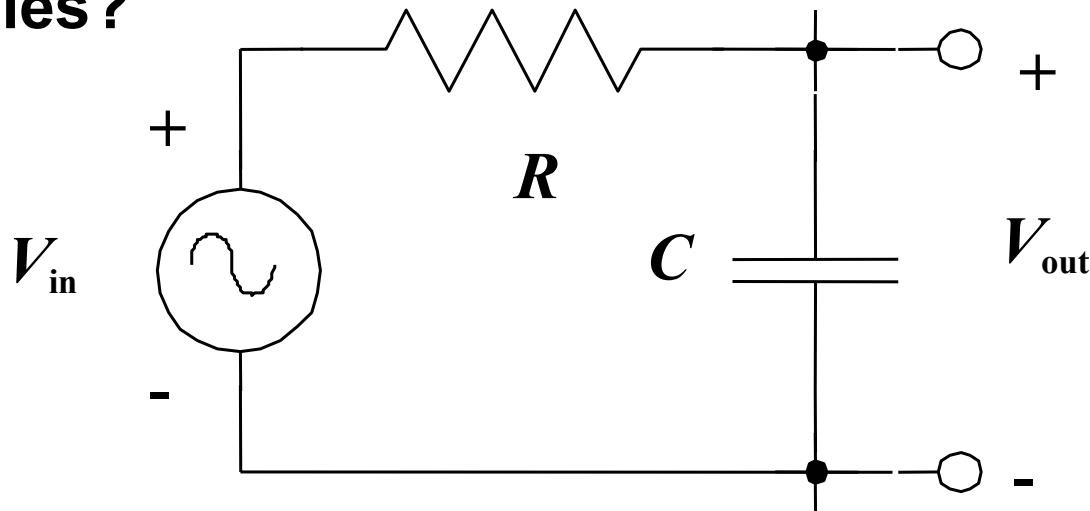

Assume the input voltage is  $v_{\text{in}}(t) = V_{\text{in}} \cos(\omega t)$  and represent it by the phasor  $\mathbf{V}_{\text{in}}$ . A phasor current  $\mathbf{I}$  flows clockwise in the circuit.

Write KVL:  $-\mathbf{V}_{in} + \mathbf{I}R + \mathbf{I}\mathbf{Z}_C = 0 = -\mathbf{V}_{in} + \mathbf{I}(R + \mathbf{Z}_C)$

The phasor current is thus  $\mathbf{I} = \mathbf{V}_{in}/(R + \mathbf{Z}_C)$

The phasor output voltage is  $\mathbf{V}_{out} = \mathbf{I}\mathbf{Z}_C$ .

Thus  $\mathbf{V}_{out} = \mathbf{V}_{in}[\mathbf{Z}_C/(R + \mathbf{Z}_C)]$

If we are only interested in the dependence upon frequency of the magnitude of  $(\mathbf{V}_{out} / \mathbf{V}_{in})$ , we can write

$$|\mathbf{V}_{out} / \mathbf{V}_{in}| = |\mathbf{Z}_C/(R + \mathbf{Z}_C)| = 1/|1 + R/\mathbf{Z}_C|$$

Substituting for  $\mathbf{Z}_C$ , we have  $1 + R/\mathbf{Z}_C = 1 + j\omega RC$ , whose magnitude is the square root of  $(\omega RC)^2 + 1$ . Thus,


$$\left| \frac{\mathbf{V}_{out}}{\mathbf{V}_{in}} \right| = \frac{1}{\sqrt{(\omega RC)^2 + 1}}$$

# Explore the Result

If  $\omega RC \ll 1$  (low frequency) then  $| \mathbf{V}_{out} / \mathbf{V}_{in} | = 1$

If  $\omega RC \gg 1$  (high frequency) then  $| \mathbf{V}_{out} / \mathbf{V}_{in} | \sim 1/\omega RC$

If we plot  $| \mathbf{V}_{out} / \mathbf{V}_{in} |$  vs.  $\omega RC$  we obtain roughly the plot below, which was plotted on a log-log plot:

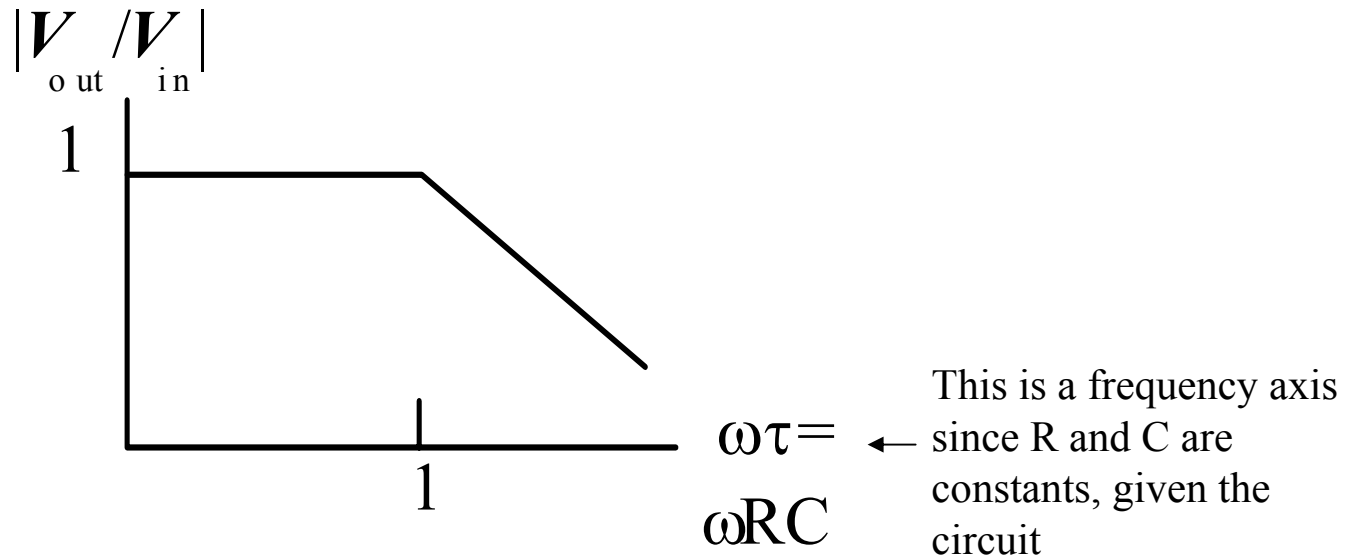

The plot shows that this is a **low-pass filter**. Its cutoff frequency is at the frequency  $\omega$  for which  $\omega RC = 1$ .

# Decibel: Logarithmic measure for power, voltage and current ratios

**Power:** To express a power,  $P$ , relative to a reference power,  $P_{\text{reference}}$ , we define the power in decibels as:  $\text{Power } P \text{ in decibels (dB)} = 10 \log_{10}(P/P_{\text{reference}})$ . [E.g., if  $P = 2 \text{ mW}$  and  $P_{\text{reference}} = 1 \text{ mW}$ ,  $P = 10 \log_{10}(2/1) = 10 \log_{10}(2) = 10 \times 0.301 = 3 \text{ dB re } 1 \text{ mW}$ .]

**Voltage and current:** Suppose that the voltage  $V$  (or current  $I$ ) appears across (or flows in) a resistance whose value is  $R$ . The corresponding power dissipated,  $P$ , is then  $V^2/R$  or  $I^2R$ . We can similarly relate the reference voltage or reference current to the reference power as

$$P_{\text{reference}} = (V_{\text{reference}})^2/R \text{ or } P_{\text{reference}} = (I_{\text{reference}})^2R..$$

Hence

$$\begin{aligned} \text{Voltage } V \text{ in dB} &= 20 \log_{10}(V/V_{\text{reference}}) \\ \text{Current } I \text{ in dB} &= 20 \log_{10}(I/I_{\text{reference}}) \end{aligned}$$

Similarly, the **power, voltage or current gain of an amplifier or a filter** can be represented in terms of input and output quantities as

$$\begin{aligned} \text{Power gain} &= 10 \log_{10}(P_{\text{out}}/P_{\text{in}}) \\ \text{Voltage gain} &= 20 \log_{10}(V_{\text{out}}/V_{\text{in}}) \\ \text{Current gain} &= 20 \log_{10}(I_{\text{out}}/I_{\text{in}}). \end{aligned}$$

[E.g., a voltage amplifier whose output voltage is 1000 times its input voltage has a voltage gain of  $20 \log_{10}(1000) = 60 \text{ dB}$ , and a filter whose output voltage is 1/10 of its input voltage has a voltage gain of  $-20 \text{ dB}$  (or a voltage loss of  $20 \text{ dB}$  (or a).]