

Lab 3: Phase-Locked Loop

The Phase-Locked Loop (PLL) circuit is widely used in communication and control systems. A typical PLL circuit consists of three main components: a voltage-controlled oscillator (VCO), a phase comparator, and a low-pass filter as shown in Figure 1. When used as a FM demodulator, the input to the PLL circuit is a FM signal and the output (demodulated signal) is the output from the low-pass filter. The operation of this demodulator is described as follows:

The phase comparator detects the difference between the phase (or frequency) of the VCO output and that of the input signal. The phase error is first filtered by the low-pass filter and then used to adjust the VCO so that the phase of the VCO phase locks on the phase of the input signal.

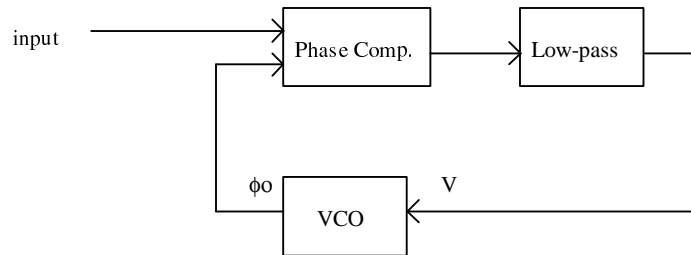


Figure 1 Phase-Locked Loop

Voltage-Controlled Oscillator (VCO)

The VCO output frequency (Freq) is linearly related to the control voltage (V), i.e., $\text{Freq} = K_o * V$ where K_o is a constant. If the phase of the VCO output square wave is considered as the output variable, the VCO can be modeled as an integrator i.e.,

$$\phi_o = K_o * V / s$$

Figure 2 shows the VCO output with a unit step input V. Note that while the VCO output frequency undergoes a step change, its phase (with respect to the reference signal) increases linearly at rate of ϕ_o .

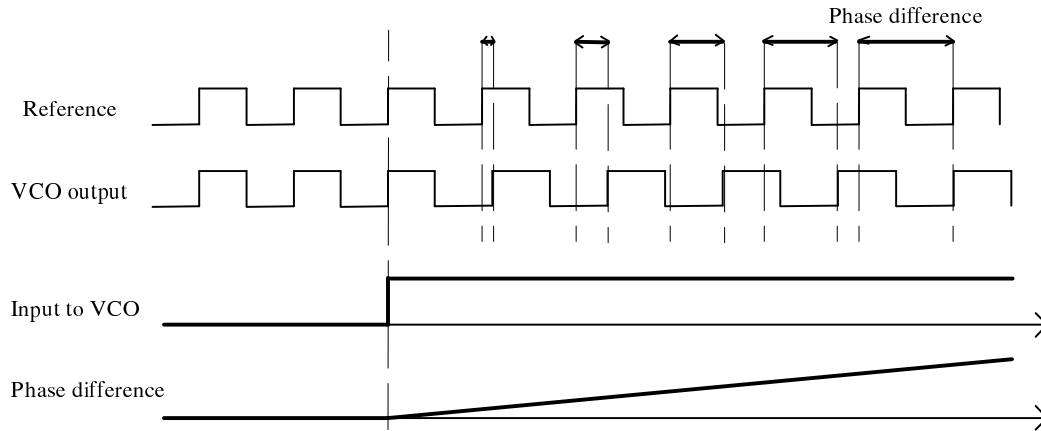


Figure 2 Step response of the VCO and the phase comparator

Phase Comparator

An Exclusive-Or (XOR) function can be used as a phase comparator. As shown in Figure 3, if the phase difference between two input signals is exactly 90 degrees, the output of the XOR gate is a square wave of twice the input frequency and has exactly 50% duty cycle. Note that, if one of the input signal's phase is shifted, the duty cycle of the output changes accordingly.

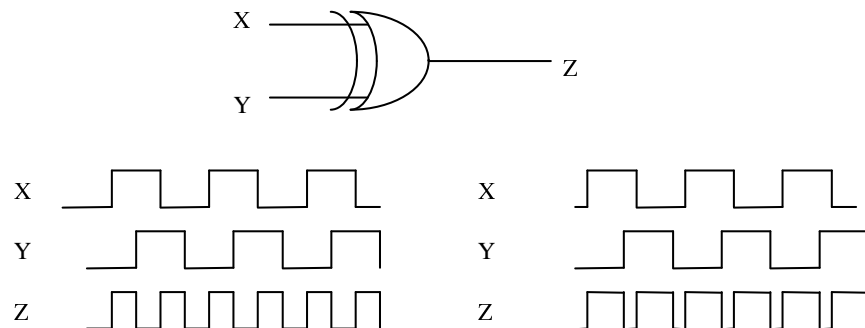


Figure 3. A simple phase comparator

This simple phase comparator has two drawbacks:

- (1) It can only detect ± 90 degrees of phase difference.
- (2) It needs a duty-cycle detector to convert the duty cycle of the output square wave to an analog signal.

While the first problem has no simple solution, the second problem can be solved by a low-pass filter as explained below.

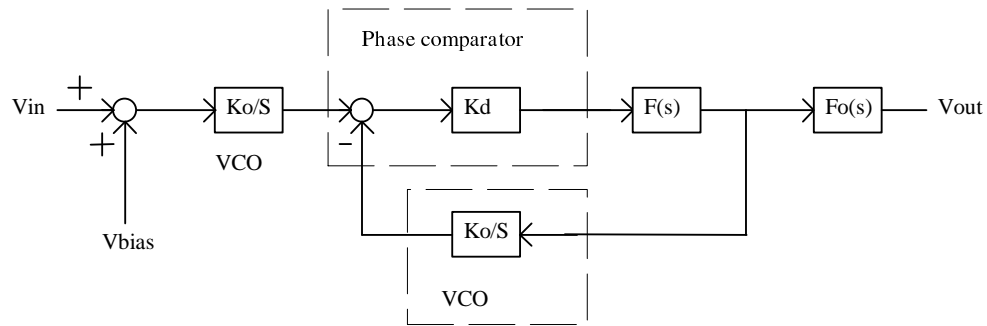


Figure 6 Block diagram of the circuit in Figure 5.

Pre-lab:

1. Using Fig 5 and 6, determine the transfer functions for the RC networks $F(s)$ and $F_o(s)$.
2. Determine the transfer function from V_{in} to V_{out} . It will be in terms of K_d and K_o . Simplify it to a polynomial in powers of s such that it can be entered into MATLAB.

Tasks to be completed in lab:

1. Calculate the constant K_d from Figure 4 and the fact that the voltage of the logic level high is 10v. The scale of K_d is v/rad.
2. Measure the constant K_o by finding the relationship between the VCO input voltage and its output frequency. Note that K_o is in (rad/s)/v.
3. Measure the step response of the circuit using a 0.2V peak-to-peak 2KHz square wave as input.
4. Experimentally generate a Bode plot for this system (magnitude and phase). Use a sinewave with 0.2 peak-to-peak amplitude for this.
5. Now that you know K_o and K_d , plug these values into the transfer function from V_{in} to V_{out} . Plot the step response of this transfer function using MATLAB. What is the damping ratio and the natural frequency of the complex poles?
6. Using MATLAB, generate a Bode plot for this system.
7. Show that, with an additional resistor in series with the capacitor C , the damping ratio of the closed loop circuit can be adjusted. Determine the value of the resistor for a damping ratio of 0.5 and experimentally verify your design. Note that a low damping ratio renders an undesirable peaking in the frequency response. High damping ratio, on the other hand, means slow frequency tracking. With only 90 degree dynamic range, the circuit should not have a high damping ratio.
8. What is the purpose of the voltage follower? How would the circuit operation be affected if this voltage-follower is replaced by a wire?