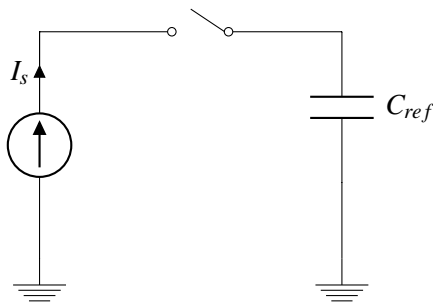


Design Example Continued


Continuing our analysis for "countdown timer" circuit.



We know for a capacitor C :


$$I = C \frac{dV}{dt} \quad (1)$$

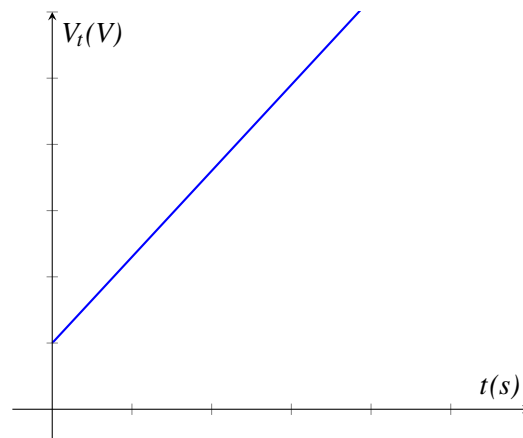There is a linear relationship between the voltage across capacitor $V(t)$ and charging time t .




When a button is pressed, we want to turn on some circuit after 2s. Given that voltage is linearly dependent on charging time, we can use a comparator and a reference voltage V_{ref} to decide if 2s has already passed

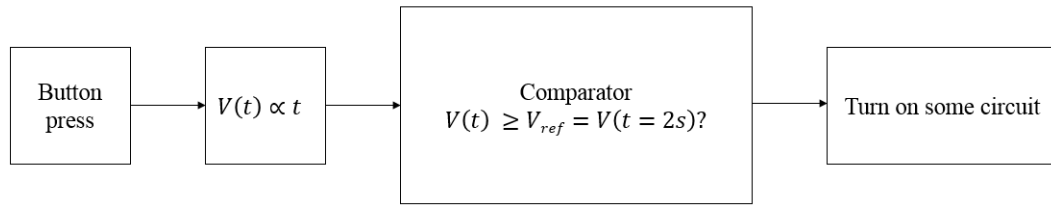after the button press to decide whether or not to turn on some circuit.




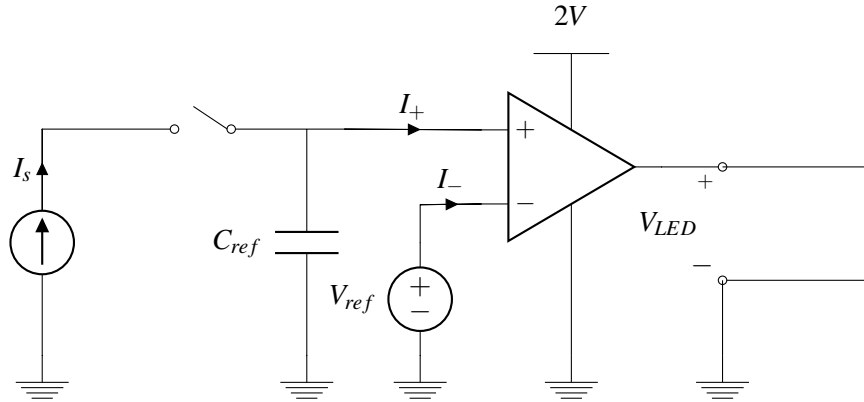Adding an op-amp comparator and a voltage source V_{ref} to the "countdown timer" circuit:



Obviously, V_{ref} should be set equal to the voltage of C_{ref} after charging for 2s. After 2s since the button is pressed, if the voltage across C_{ref} becomes higher than V_{ref} , the comparator outputs 2V to the output of the op-amp to turn on the LED.

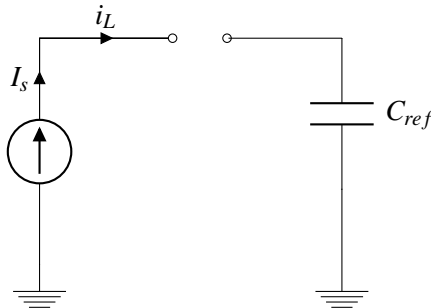
Step 4: design verification Now, let's actually analyze the design completely to make sure it works. Before the button is pressed, the circuit on the current source side looks like:




According to KCL,

$$I_s = I_L \quad (2)$$

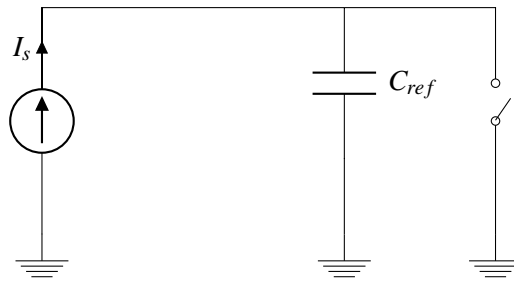
I_s is the constant current supplied by the current source, I_L is the current flow into the switch. Before touch, I_L must equal 0 since there is an open circuit. However, the current source guarantees that I_s is nonzero. It is very easy to see that mathematically this is problematic, how do we solve the problem? We can add another switch in the circuit:



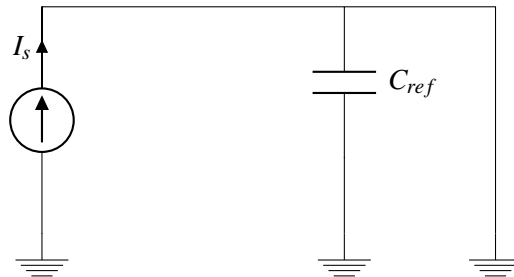Before touch, the switch is on and can be replaced by a wire:



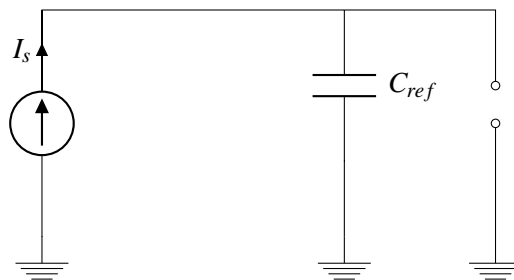After touch, the switch is off and can be replaced by an open circuit:



In either cases, there is a loop in the circuit for I_s to flow. Now, there is a remaining mystery to be answered, how do we build that current source?

22.1 "Almost" current source

In this section, we will use resistors, voltage sources and op amps to build a current source. We know by Ohm's law,

$$I = \frac{V}{R} \quad (3)$$


If we have a voltage source V_s , we can scale it by a resistance value R , then we should get a constant current I_s .

Now let's use our design procedures to build a current source.

Step 1 restate design goal: we want to build a current source that can output constant current regardless of whatever elements we hook up to it.

Step 2 Let's now take a voltage source and connect it to a resistor to output a current:

Attempt #1

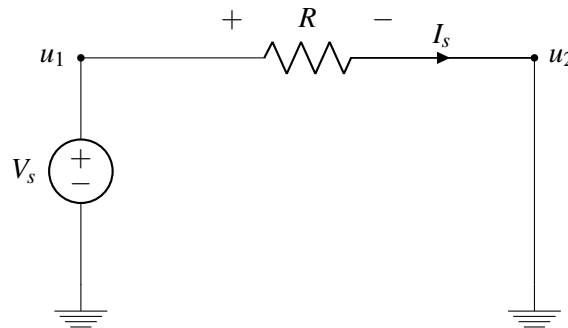


In the above circuit,

$$u_1 = V_s \quad (4)$$


$$I_s = \frac{V_s}{R} \quad (5)$$

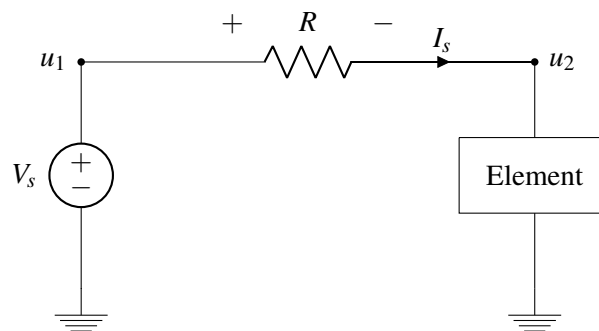However, if we hook up an element between u_2 and ground, we can tell immediately that the current through R_s is no longer the constant $I_s = \frac{V_s}{R}$.



Recall that it is important to guarantee a constant current output from the current source regardless of the element added to the circuit.

Attempt #2 Although our attempt 1 has failed, we have learned an important lesson: if we can somehow set u_2 to $0V$ without physically connecting it to ground. The current through R will always equal $\frac{V_s}{R}$ ($I_R = \frac{u_1 - u_2}{R} = \frac{V_s - 0}{R}$)! According to golden rule #2, we can set both V_+ and V_- to $0V$ if an op amp circuit is in negative feedback. Indeed, we will now use an op amp to build a current source!

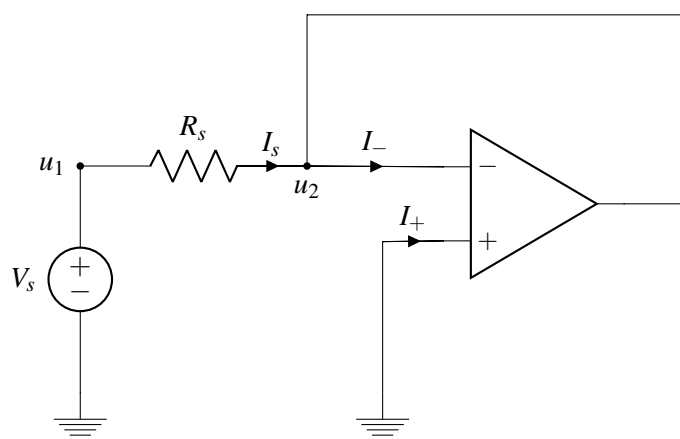

According to golden rules:

$$I_- = 0 \quad (6)$$

$$V_- = V_+ = 0V \quad (7)$$


We also know that the current across R will always be:

$$I_s = \frac{u_1 - u_2}{R} \quad (8)$$


Solving the above equations, we can get the value of I_s :

$$I_s = \frac{V}{R} \quad (9)$$

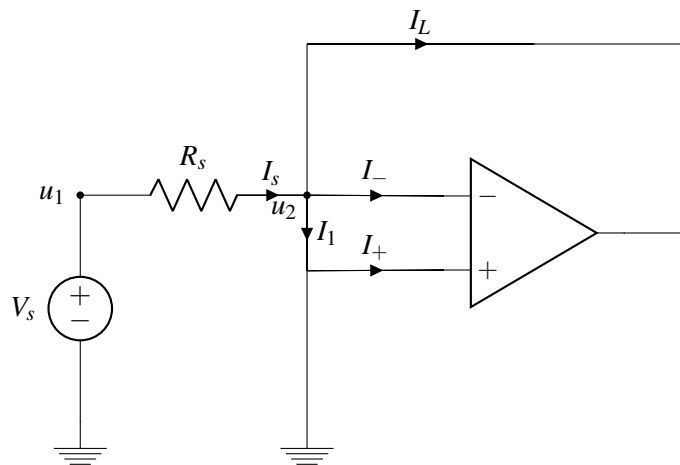By setting u_2 (V_-) to $0V$ by using a negative feedback circuit, we have successfully built a current source! It is important to keep in mind setting u_2 to $0V$ by using a negative feedback circuit is very different from physically connecting the node of u_2 to ground. If we physically connect u_2 to ground by adding a wire between V_- and V_+ :



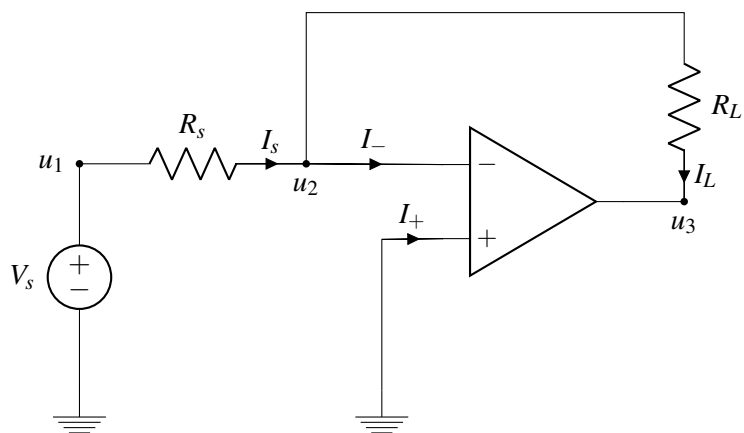If we physically connect both V_- and V_+ to ground, I_L will become $0A$ because it is shorted by the wire between V_- and V_+ . Instead, now we have $I_1 = I_s$. So we must not physically connect V_- to ground. Let's now hook up a resistor R_L to the circuit and prove that current flow through R_L is constant:



According to KCL:


$$I_L = I_s = \frac{V}{R_s} \quad (10)$$

From I_L equation, we can see immediately that I_L is not affected by changes in R_L . How does the circuit maintain the constant current flow through R_L ?


The op-amp outputs a negative V_{out} to maintain a constant current flow through R_L . In other words, the voltage drop across R_L is always given by

$$V_{R_L} = \frac{V}{R_s} \times R_L \quad (11)$$

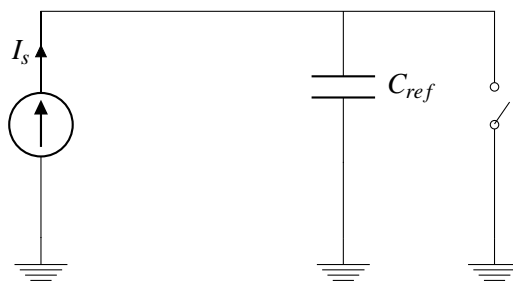Now let us plug in the current source to the following circuit:




The circuit becomes:

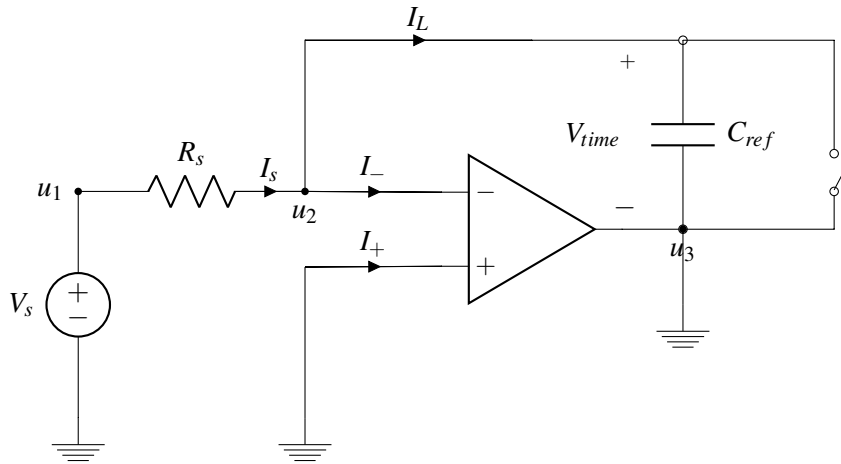

Now u_3 is connected to ground. By doing this, the voltage across C_{ref} becomes:

$$V_{time} = u_2 - u_3 = 0V - 0V = 0V \quad (12)$$

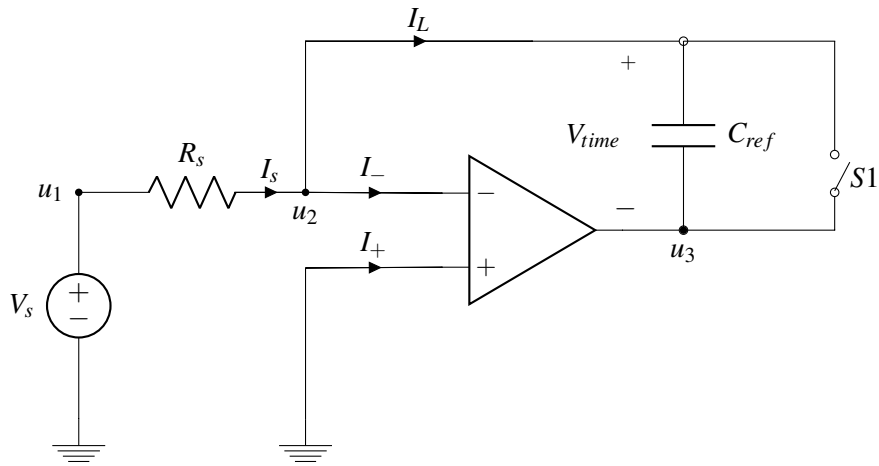There is even a worse problem, recall that there is an controlled voltage source inside the op-amp, this op-amp wants to set u_3 to some nonzero value $A \cdot V_c$ but u_3 is also manually connected to $0V$. The fix to solve this problem is to simply get rid of the ground connection.



$$I_s = C_{ref} \frac{dV}{dt} \quad (13)$$

$$I_s = C_{ref} \frac{d(u_2 - u_3)}{dt} \quad (14)$$

According to golden rule #2, $u_2 = 0V$.

$$I_s = C_{ref} \frac{d(0V - u_3)}{dt} = C_{ref} \frac{d(-u_3)}{dt} \quad (15)$$

Solving the above equation:

$$u_3(t) = -\frac{I_s}{C_{ref}} \times t + u_3(t=0s) \quad (16)$$

$u_3(t)$ is associated with the initial value $u_3(t=0s)$. Before touch, the switch $S1$ is on, which sets $u_3(t=0s)$ to $0V$. Therefore,

$$u_3(t) = -\frac{I_s}{C_{ref}} \times t = -\frac{V_s}{R_s C_{ref}} \times t \quad (17)$$

Note there is a term $R_s C_{ref}$ in the denominator, what is the unit of $R_s C_{ref}$?

$$\text{Unit for } R_s C_{ref} = \frac{V}{A} \times CV = \frac{C}{A} = \text{second} \quad (18)$$

It is good to know that this multiplication result of RC is very useful and common in the timing analysis for circuits, this is an indicator of how fast a circuit is.

There are 2 important points to keep in mind when this current source:

- Do not connect the circuit element that we want to supply the constant current to with ground externally. Doing so may force V_{out} of the op-amp to $0V$ and lead to nonidealities.
- The circuit element we hook up to the current source must still keep the op-amp circuit in its negative feedback state. Being in negative feedback allows us to set the node u_2 to $0V$ without physically connecting it to ground and hence allows a constant current output.