


UNIVERSITY OF CALIFORNIA
College of Engineering
Department of Electrical Engineering
and Computer Sciences

H. Khorramabadi


Homework 6
Due Tues. November 23, 2010

EECS 247
FALL 2010

 
1. A basic NMOS track and hold circuit is shown below. The clock applied to the gate of the transistor swings from $V_{SS}=0V$ to $V_{DD}=1.5V$. Assume an ideal square law model for the transistor with $V_{TH}=0.2V$ and $\mu C_{ox}=250\mu A/V^2$. Ignore body effect.
 - a) Suppose this circuit precedes a 14-bit ADC. How large should we choose C so that the input referred rms noise from the sampler is equal to 0.25LSB of the ADC at $T = 27^\circ C$? Compared to the case where only quantization noise is present, how much is the overall SNR degraded by the input-referred kT/C noise.
 - b) If the clock has a 50% duty cycle, calculate the maximum clock frequency at which inputs between $0 \dots 1.0V$ input can be sampled to within 1/8 LSB accuracy at 14 bit resolution. Assume $C = 15pF$. You can use the average resistance for $M1$.
 - c) In practice, what are the other factors affecting the accuracy of this sampling front-end?



 
2. Consider a 6-bit flash ADC with an ideal reference resistor string and $V_{ref}=1V$. Assume that the comparators have an offset voltage with standard deviation $\sigma_{OS}=3mV$. What are the standard deviations of the converter's worst case DNL and INL?
3. Shown below is the block diagram of a pipelined ADC. Note that the input voltage is centered around ground level.



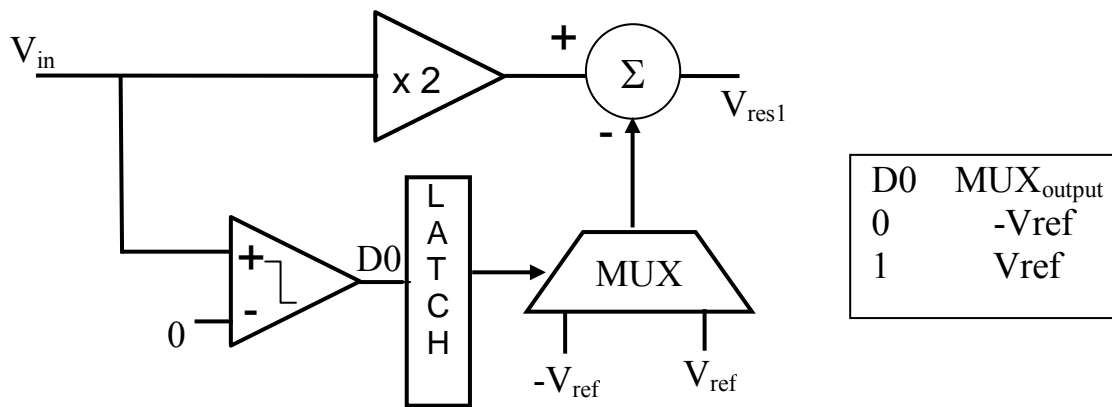The first stage has the following block diagram:



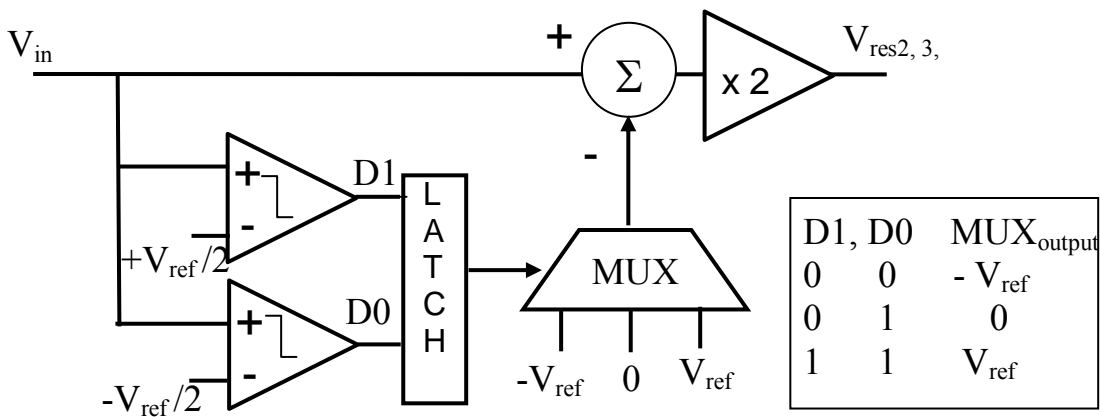The rest of the stages have the block diagram shown below:



- What is the effective number of bits for stage 1 and the following stages? What is the raw number of bits for each stage?
- How many stages are needed to implement a 12bit ADC?
- If each stage takes one clock cycle per conversion, what is the minimum signal latency from the analog input to the digital output?
- Derive the residue plot for the first and the following stages.
- What is the maximum tolerable comparator offset in the 1st stage (assume all other stages are ideal)? Show your derivation on the residue plot/s.
- What is the maximum tolerable comparator offset in the 2nd stage (assume all other stages are ideal)? Show your derivation on the residue plot/s. b