

EE247

Lecture 17

- Administrative issues
 - Midterm exam postponed to **Thurs. Oct. 28th**
 - o You can *only* bring one 8x11 paper with your own written notes (please do not photocopy)
 - o No books, class or any other kind of handouts/notes, calculators, computers, PDA, cell phones....
 - o Midterm includes material covered to **end of lecture 14**

EE247

Lecture 17

ADC Converters

- Sampling (continued)
 - Sampling switch considerations
 - Clock voltage boosters
 - Sampling switch charge injection & clock feedthrough
 - Complementary switch
 - Use of dummy device
 - Bottom-plate switching
- Track & hold
 - T/H circuits
 - T/H combined with summing/difference function
 - T/H circuit incorporating gain & offset cancellation
 - T/H aperture uncertainty

Practical Sampling Summary So Far!

- kT/C noise

$$C \geq 12k_B T \frac{2^{2B}}{V_{FS}^2}$$


- Finite $R_{sw} \rightarrow$ limited bandwidth

$$R \ll \frac{0.72}{B f_s C}$$


- $g_{sw} = f(V_{in}) \rightarrow$ distortion

$$g_{ON} = g_o \left(1 - \frac{V_{in}}{V_{DD} - V_{th}} \right) \quad \text{for} \quad g_o = \mu C_{ox} \frac{W}{L} (V_{DD} - V_{th})$$

 - Allowing long enough settling time \rightarrow reduce distortion due to switch non-linear behavior



Constant V_{GS} Sampling Circuit

 


This Example: All device sizes: $W/L=10\mu/0.35\mu$

All capacitor size: 1pF (except for Chold)

Note: Each critical switch requires a separate clock booster


Ref: A. Abo et al, "A 1.5-V, 10-bit, 14.3-MS/s CMOS Pipeline Analog-to-Digital Converter," JSSC May 1999, pp. 599.

Constant V_{GS} Sampler: Φ High

 


- C3 previously charged to VDD
- M8 & M9 are on: C3 across G-S of M11
- M11 on with constant $V_{GS} = V_{DD}$
- Mission accomplished!?

Constant V_{GS} Sampling

 

Constant V_{GS} Sampling?

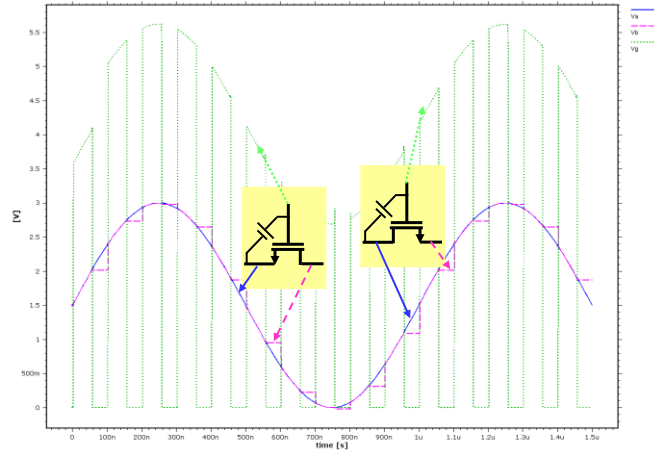

Constant V_{GS} Sampling?



- During the time period:
 $V_{in} < V_{out}$
 $\rightarrow V_{GS} = \text{constant} = V_{DD}$

- Larger $V_{GS} - V_{th}$ compared to no boost
- $V_{GS} = \text{cte}$ and not a function of input voltage
 \rightarrow Significant linearity improvement




- During the time period:
 $V_{in} > V_{out}$:
 $\rightarrow V_{GS} = V_{DD} - IR$

- Larger $V_{GS} - V_{th}$ compared to no boost
- V_{GS} is a function of IR and hence input voltage
 \rightarrow Linearity improvement not as pronounced as for $V_{in} < V_{out}$

Boosted Clock Sampling Design Considerations

Choice of value for C3:

 - C3 too large → large charging current → large dynamic power dissipation
- C3 too small →
 $(V_{gate} - V_s)_{M11} = \frac{V_{DD} \cdot C3}{C3 + Cx}$
 → Loss of $V_{GS_{M11}}$ due to low ratio of C3/Cx
 Cx includes C_{GS} of M11 plus all other parasitics caps....




Ref: A. Abo et al, "A 1.5-V, 10-bit, 14.3-MS/s CMOS Pipeline Analog-to-Digital Converter," JSSC May 1999, pp. 599.

Boosted Clock Sampling Design Considerations

- Reliability issues:
 - Avoid having any of the G-S and G-D, and D-S terminal voltages for ALL circuit devices exceed the maximum V_{DD} prescribed by the SI processing firm.
 - In particular, the thin MOS device gate oxide could gradually sustain damage through getting exposed to higher than prescribed voltage.

Boosted Clock Sampling Complete Circuit

 


M7 & M13 for reliability

Remaining issues:

- V_{GS} constant only for $V_{in} < V_{out}$
- Nonlinearity due to V_{th} dependence of M11 on body-source voltage

Ref: A. Abo et al, "A 1.5-V, 10-bit, 14.3-MS/s CMOS Pipeline Analog-to-Digital Converter," JSSC May 1999, pp. 599.


Advanced Clock Boosting Technique

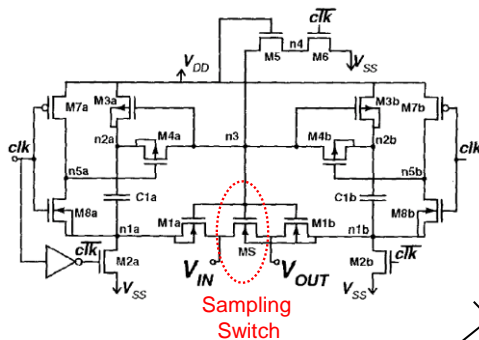

Ref: M. Waltari et al., "A self-calibrated pipeline ADC with 200MHz IF-sampling frontend," ISSCC 2002, Dig. Tech. Papers, pp. 314


Two floating voltages sources generated and connected to Gate and S & D

Advanced Clock Boosting Technique

 


- clk → low
 - Capacitors C1a & C1b → charged to VDD
 - MS → off
 - Hold mode

Advanced Clock Boosting Technique

 

- clk → high
 - Top plate of C1a & C1b connected to gate of sampling switch
 - Bottom plate of C1a connected to V_{IN}
 - Bottom plate of C1b connected to V_{OUT}
 - VGS & VGD of sampling switch (MS) both @ VDD & ac signal on G of MS
→ average of V_{IN} & V_{OUT}


Advanced Clock Boosting Technique

 

Ref: M. Waltari et al., "A self-calibrated pipeline ADC with 200MHz IF-sampling frontend," ISSCC 2002, Dig. Tech. Papers, pp. 314


- Gate tracks *average* of input and output, reduces effect of I-R drop at high frequencies
- Bulk also tracks signal \Rightarrow reduced body effect (technology used allows connecting bulk to S)
- Reported measured SFDR = 76.5dB at $f_{in}=200\text{MHz}$

Constant Conductance Switch

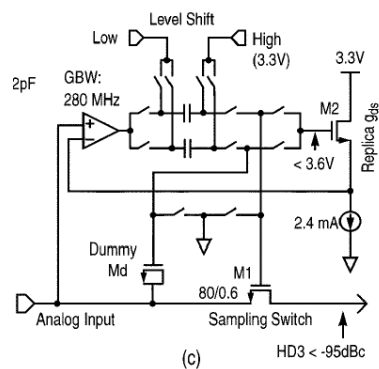


Ref: H. Pan et al., "A 3.3-V 12-b 50-MS/s A/D converter in 0.6 μm CMOS with over 80-dB SFDR," *IEEE J. Solid-State Circuits*, pp. 1769-1780, Dec. 2000

Constant Conductance Switch

 

Ref: H. Pan et al., "A 3.3-V 12-b 50-MS/s A/D converter in 0.6 μ m CMOS with over 80-dB SFDR," *IEEE J. Solid-State Circuits*, pp. 1769-1780, Dec. 2000

Constant Conductance Switch

 


M2 \rightarrow Constant current

M1 \rightarrow replica of M2
& same V_{GS}
as M2
 \rightarrow M1 also
constant current


- Note: Authors report requirement of 280MHz GBW for the opamp for 12bit 50Ms/s ADC
- Also, opamp common-mode compliance for full input range required

Ref: H. Pan et al., "A 3.3-V 12-b 50-MS/s A/D converter in 0.6 μ m CMOS with over 80-dB SFDR," *IEEE J. Solid-State Circuits*, pp. 1769-1780, Dec. 2000

Switch Off-Mode Feedthrough Cancellation

 

 
High-pass feedthrough paths past an open switch



Feedthrough cancellation with a dummy switch



Ref: M. Waltari et al., "A self-calibrated pipeline ADC with 200MHz IF-sampling frontend," ISSCC 2002, Dig. Techn. Papers, pp. 314

Practical Sampling Issues

 

- Switch induced noise due to M1 finite channel resistance
- Clock jitter
- Finite $R_{sw} \rightarrow$ limited bandwidth \rightarrow finite acquisition time
- $R_{sw} = f(V_{in}) \rightarrow$ distortion
- ➔ • Switch charge injection & clock feedthrough

  
Sampling Switch Charge Injection & Clock Feedthrough Switching from Track to Hold




- First assume V_i is a DC voltage
- When switch turns off \rightarrow unwanted offset voltage induced on C_s
- Why?

Sampling Switch Charge Injection

 MOS xtor operating in triode region
Cross section view





 Distributed channel resistance &
gate & junction capacitances





- Channel \rightarrow distributed RC network formed between G, S, and D
- Channel to substrate junction capacitance \rightarrow distributed & voltage dependant
- Drain/Source junction capacitors to substrate \rightarrow voltage dependant
- Over-lap capacitance $C_{ov} = L_D \cdot W \cdot C_{ox}$ associated with G-S & G-D overlap

Switch Charge Injection Slow Clock

  

- Slow clock \rightarrow clock fall time \gg device speed
 \rightarrow During the period $(t- \text{ to } t_{off})$ current in channel discharges channel charge into low impedance signal source
- Only source of error \rightarrow Clock feedthrough from C_{ov} to C_s

Switch Clock Feedthrough Slow Clock

  

$$\Delta V = -\frac{C_{ov}}{C_{ov} + C_s} (V_i + V_{th} - V_L)$$

$$\approx -\frac{C_{ov}}{C_s} (V_i + V_{th} - V_L)$$



$$V_o = V_i + \Delta V$$

$$V_o = V_i - \frac{C_{ov}}{C_s} (V_i + V_{th} - V_L) = V_i \left(1 - \frac{C_{ov}}{C_s} \right) - \frac{C_{ov}}{C_s} (V_{th} - V_L)$$

$$V_o = V_i (1 + \varepsilon) + V_{os}$$

$$\text{where } \varepsilon = -\frac{C_{ov}}{C_s}; V_{os} = -\frac{C_{ov}}{C_s} (V_{th} - V_L)$$

  Switch Charge Injection & Clock Feedthrough Slow Clock- Example





$$C'_{ov} = 0.1fF / \mu \quad C_{ox} = 9fF / \mu^2 \quad V_{th} = 0.4V \quad V_L = 0$$

$$\varepsilon = -\frac{C_{ov}}{C_s} = -\frac{10\mu \times 0.1fF / \mu}{1pF} = -0.1\%$$

Allowing $\varepsilon = 1/2LSB \rightarrow$ ADC resolution $< \sim 9bit$

$$V_{os} = -\frac{C_{ov}}{C_s} (V_{th} - V_L) = -0.4mV$$

  Switch Charge Injection & Clock Feedthrough Fast Clock



- Sudden gate voltage drop \rightarrow no gate voltage to establish current in channel \rightarrow channel charge has no choice but to escape out towards S & D

Switch Charge Injection & Clock Feedthrough Fast Clock

Clock Fall-Time \ll Device Speed:


$$\Delta V_o = -\frac{C_{ov}}{C_{ov} + C_s}(V_H - V_L) - \left(\frac{1}{2}\right) \times \frac{Q_{ch}}{C_s}$$

$$\approx -\frac{C_{ov}}{C_{ov} + C_s}(V_H - V_L) - \frac{1}{2} \times \frac{WC_{ox}L((V_H - V_i - V_{th}))}{C_s}$$

$$V_o = V_i(1 + \varepsilon) + V_{os}$$


where $\varepsilon = -\frac{1}{2} \times \frac{WC_{ox}L}{C_s}$
 
$$V_{os} = -\frac{C_{ov}}{C_s}(V_H - V_L) - \frac{1}{2} \times \frac{WC_{ox}L(V_H - V_{th})}{C_s}$$



- For simplicity it is assumed channel charge divided equally between S & D
- Source of error \rightarrow channel charge transfer + clock feedthrough via C_{ov} to C_s

 
Switch Charge Injection & Clock Feedthrough Fast Clock- Example




$$C_{ov} = 0.1 \frac{fF}{\mu}, C_{ox} = 9 \frac{fF}{\mu^2}, V_{th} = 0.4V, V_{DD} = 1.8V, V_L = 0$$

$$\varepsilon = 1/2 \times \frac{WLC_{ox}}{C_s} = \frac{10\mu \times 0.18\mu \times 9fF / \mu^2}{1pF} = 1.6\% \rightarrow \sim 5\text{-bit}$$
 
$$V_{os} = -\frac{C_{ov}}{C_s}(V_H - V_L) - \frac{1}{2} \times \frac{WC_{ox}L(V_H - V_{th})}{C_s} = -1.8mV - 14.6mV = -16.4mV$$



 Switch Charge Injection & Clock Feedthrough Example-Summary



Error function of:

- Clock fall time
- Input voltage level
- Source impedance
- Sampling capacitance size
- Switch size

⚡ → Clock fall/rise should be controlled not to be faster (sharper) than necessary

Switch Charge Injection Error Reduction

- How do we reduce the error?
 - Reduce switch size to reduce channel charge?

$$\Delta V_o = -\frac{1}{2} \frac{Q_{ch}}{C_s} \downarrow$$

$$\tau = R_{ON} C_s = \frac{C_s}{\mu C_{ox} \frac{W}{L} (V_{GS} - V_{th})} \uparrow \quad (\text{note: } \frac{T_s}{2} = k\tau)$$

Consider the figure of merit (FOM):

$$FOM = \frac{I}{\tau \times \Delta V_o} \approx \frac{\mu C_{ox} \frac{W}{L} (V_{GS} - V_{th})}{C_s} \times 2 \times \frac{C_s}{W C_{ox} L ((V_H - V_i - V_{th}))}$$



$$\rightarrow FOM \propto \mu / L^2$$

- ❖ Reducing switch size increases τ → increased distortion → not a viable solution
- ❖ Small τ and small ΔV → use minimum channel length (mandated by technology)
- ❖ For a given technology $\tau \times \Delta V \sim \text{constant}$

Sampling Switch Charge Injection & Clock Feedthrough Summary

- Extra charge injected onto sampling capacitor @ switch device turn-off
 - Channel charge injection
 - Clock feedthrough to C_s via C_{ov}
- Issues due to charge injection & clock feedthrough:
 - DC offset induced on hold C
 - Input dependant error voltage \rightarrow distortion
- Solutions:
 - Slowing down clock edges as much as possible
 - Complementary switch?
 - Addition of dummy switches?
 - Bottom-plate sampling?

  Switch Charge Injection & Clock Feedthrough Complementary Switch



- In slow clock case if area of n & p devices & widths are equal ($W_n = W_p$) \rightarrow effect of overlap capacitor for n & p devices to first order cancel (cancellation accuracy depends on matching of n & p width and overlap length L_D)
- Since in CMOS technologies $\mu_n \sim 2.5\mu_p$ choice of $W_n = W_p$ not optimal from linearity perspective ($W_p > W_n$ preferable)

Switch Charge Injection Complementary Switch Fast Clock

$$|Q_{ch-n}| = W_n C_{ox} L_n (V_H - V_i - |V_{th-n}|)$$



$$|Q_{ch-p}| = W_p C_{ox} L_p (V_i - V_L - |V_{th-p}|)$$

$$\Delta V_o \approx -\frac{I}{2} \left(\frac{|Q_{ch-n}|}{C_s} - \frac{|Q_{ch-p}|}{C_s} \right)$$



$$V_o = V_i (1 + \varepsilon) + V_{os}$$

$$\varepsilon \approx \frac{1}{2} \times \frac{W_n C_{ox} L_n + W_p C_{ox} L_p}{C_s}$$

  - In fast clock case
 - To 1st order, offset due to overlap caps cancelled for equal device width
 - Input voltage dependant error worse!



Switch Charge Injection Dummy Switch

  


$$Q_1 \approx \frac{I}{2} Q_{ch}^{M1} + Q_{ov}^{M1}$$

$$Q_2 \approx Q_{ch}^{M2} + 2Q_{ov}^{M2}$$


$$\text{For } W_{M2} = \frac{1}{2} W_{M1} \rightarrow Q_2 = -Q_1 \quad \& \quad Q_{ov}^{M1} = 2Q_{ov}^{M2}$$

Switch Charge Injection Dummy Switch

 


- Dummy switch same L as main switch but half W
- Main device clock goes low, dummy device gate goes high → dummy switch acquires same amount of channel charge main switch needs to lose
- Effective only if exactly half of the charge stored in M1 is transferred to M2 (depends on input/output node impedance) and requires good matching between clock fall/rise

Switch Charge Injection Dummy Switch

 

- To guarantee half of charge goes to each side → create the same environment on both sides
 - ❖ Add capacitor equal to sampling capacitor to the other side of the switch
 - + add fixed resistor to emulate input resistance of following circuit
 - Issues: Degrades sampling bandwidth

Dummy Switch Effectiveness Test

 


V_{in}	UNCOMPENSATED SWITCH	COMPENSATED WITH DUMMY	BALANCED SWITCH
0v	-160mV	-45mV	6mV
5v	-105mV	-30mV	1mV
10v	-40mV	-11mV	0.5mV

- Dummy switch
→ $W=1/2W_{main}$
- As V_{in} is increased $V_{c1}-V_{in}$ is decreased → channel charge decreased → less charge injection
- Note large L_s
→ good device area matching

Ref: L. A. Bienstman et al, "An Eight-Channel 8 13it Microprocessor Compatible NMOS D/A Converter with Programmable Scaling", IEEE JSSC, VOL. SC-15, NO. 6, DECEMBER 1980

 Switch Charge Injection Differential Sampling



$$V_{o+} - V_{o-} = V_{od} \quad V_{i+} - V_{i-} = V_{id}$$

$$V_{oc} = \frac{V_{o+} + V_{o-}}{2} \quad V_{ic} = \frac{V_{i+} + V_{i-}}{2}$$


$$V_{o+} = V_{i+} (1 + \epsilon_1) + V_{os1}$$

$$V_{o-} = V_{i-} (1 + \epsilon_2) + V_{os2}$$

$$V_{od} = V_{id} + V_{id} \frac{(\epsilon_1 + \epsilon_2)}{2} + (\epsilon_1 - \epsilon_2) V_{ic} + V_{os1} - V_{os2}$$


- To 1st order, offset terms cancel
- Note gain error ϵ still about the same
- Has the advantage of better immunity to noise coupling and cancellation of even order harmonics

 Avoiding Switch Charge Injection Bottom Plate Sampling




- Switches M2 opened slightly earlier compared to M1
→ Injected charge due to turning off M2 is constant since its GS voltage is constant & eliminated when used differentially
- Since C_s bottom plate is already open when M1 is switched off:
→ No signal dependant charge injected on C_s

Flip-Around Track & Hold

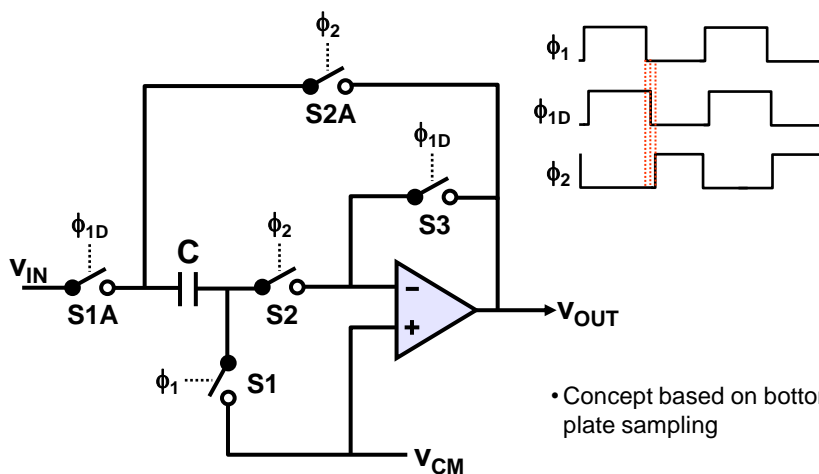


- Concept based on bottom-plate sampling


Flip-Around T/H-Basic Operation

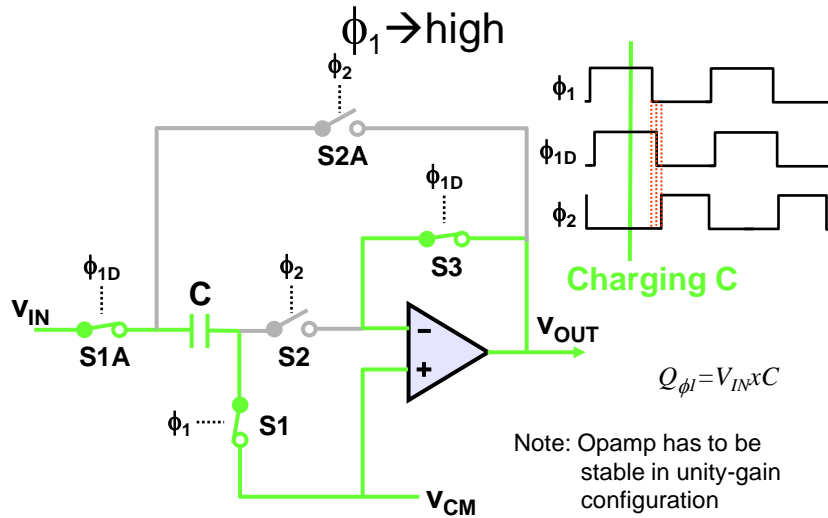

Flip-Around T/H-Basic Operation

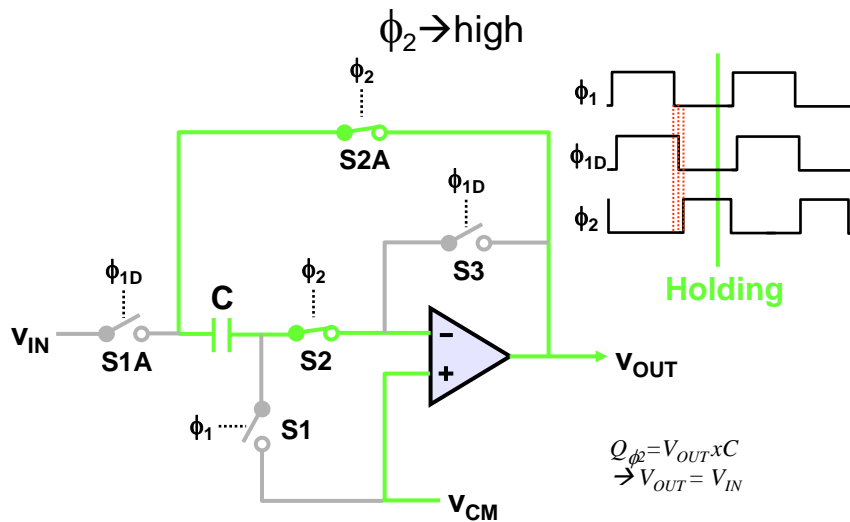


Flip-Around T/H - Timing

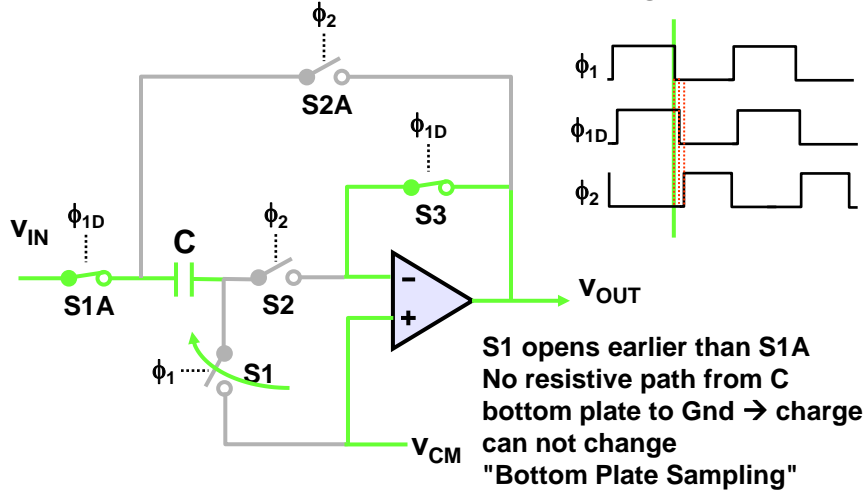

Charge Injection

- At the instant of transitioning from track to hold mode, some of the charge stored in sampling switch $S1$ is dumped onto C
- With "Bottom Plate Sampling", only charge injection component due to opening of $S1$ and is to first-order independent of v_{IN}
 - Only a dc offset is added. This dc offset can be removed with a differential architecture



Flip-Around T/H

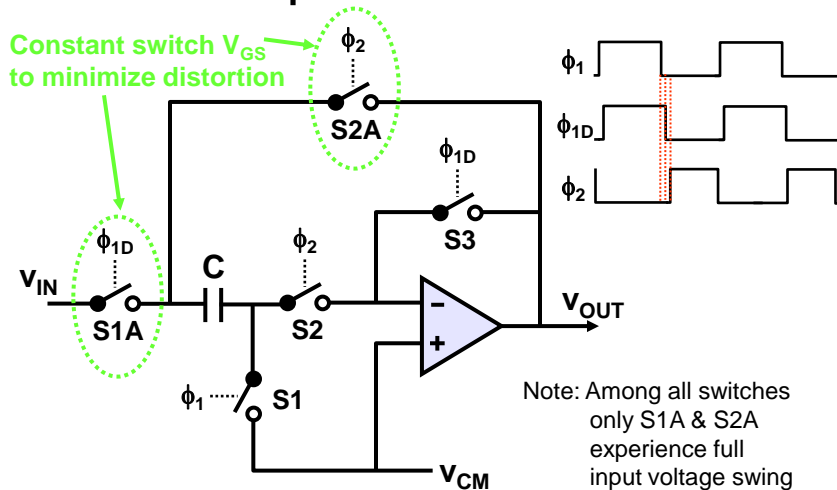

Flip-Around T/H

- S1 is chosen to be an n-channel MOSFET
- Since it always switches the same voltage, it's on-resistance, R_{S1} , is signal-independent (to first order)
- Choosing $R_{S1} \gg R_{S1A}$ minimizes the non-linear component of $R = R_{S1A} + R_{S1}$
 - Typically, S1A is a wide (much lower resistance than S1) & constant V_{GS} switch
 - In practice size of S1A is limited by the (nonlinear) S/D capacitance that also adds distortion
 - If S1A's resistance is negligible \rightarrow delay depends only on S1 resistance
 - S1 resistance is independent of $V_{IN} \rightarrow$ error due to finite time-constant \rightarrow independent of V_{IN}

  
Differential Flip-Around T/H Choice of Sampling Switch Size



- THD simulated w/o sampling switch boosted clock \rightarrow -45dB
- THD simulated with sampling switch boosted clock (see graph)

Ref: K. Vleugels et al, "A 2.5-V Sigma-Delta Modulator for Broadband Communications Applications" IEEE JSSC, VOL. 36, NO. 12, DECEMBER 2001, pp. 1887

Differential Flip-Around T/H

 


Offset voltage associated with charge injection of S11 & S12 cancelled by differential nature of the circuit

During input sampling phase \rightarrow amp outputs shorted together


Ref: W. Yang, et al. "A 3-V 340-mW 14-b 75-Msample/s CMOS ADC With 85-dB SFDR at Nyquist Input," IEEE JOURNAL OF SOLID-STATE CIRCUITS, VOL. 36, NO. 12, DECEMBER 2001 1931

Differential Flip-Around T/H

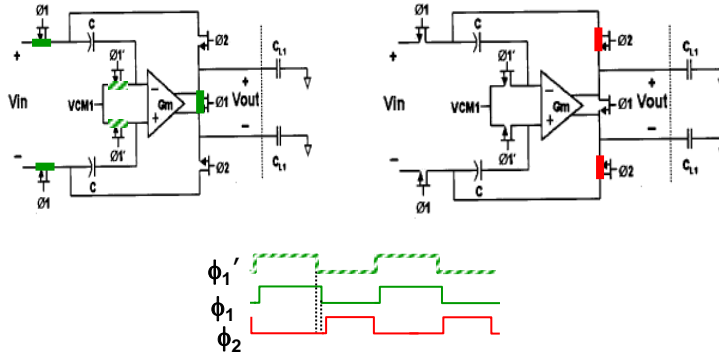


- Gain=1
- Feedback factor=1 \rightarrow high operating speed

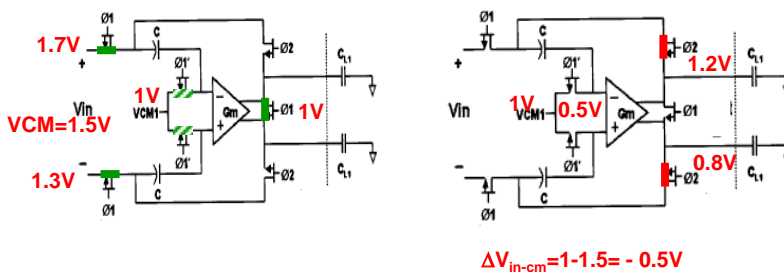Differential Flip-Around T/H Issues: Input Common-Mode Range



- $\Delta V_{in-cm} = V_{out-com} - V_{sig-com}$
 \rightarrow Drawback: Amplifier needs to have large input common-mode compliance


Input Common-Mode Cancellation

 

- Note: Shorting switch M3 added

Ref: R. Yen, *et al.* "A MOS Switched-Capacitor Instrumentation Amplifier," IEEE JOURNAL OF SOLID-STATE CIRCUITS, VOL. SC-17, NO. 6., DECEMBER 1982 1008

Input Common-Mode Cancellation

 

Track mode (ϕ high)
 $V_{C1}=V_{I1}$, $V_{C2}=V_{I2}$
 $V_{O1}=V_{O2}=0$


Hold mode (ϕ low)
 $V_{O1}+V_{O2} = 0$
 $V_{O1}-V_{O2} = -(V_{I1}-V_{I2})(C_1/(C_1+C_3))$

→ Input common-mode level removed

Switched-Capacitor Techniques Combining Track & Hold with Other Functions

- T/H + Charge redistribution amplifier
- T/H & Input difference amplifier
- T/H & summing amplifier
- Differential T/H combined with gain stage
- Differential T/H including offset cancellation

T/H + Charge Redistribution Amplifier

 

Track mode: (S1, S3 → on S2 → off)

$$V_{C1} = V_{os} - V_{IN}, \quad V_{C2} = 0$$

$$V_o = V_{os}$$

T/H + Charge Redistribution Amplifier Hold Mode

**S1 & S3 open
S2 closed**

$$V_{C1} \rightarrow V_{os}$$

$$\Delta V_{C1} = V_{os} - (V_{os} - V_{IN}) = V_{IN}$$

$$\Delta Q_1 = C_1 \Delta V_{C1} = C_1 V_{IN}$$


$$\Delta Q_2 = C_2 \Delta V_{C2} = \Delta Q_1$$

$$\Delta V_{C2} = \left(\frac{C_1}{C_2}\right) V_{C1} = V_{C2}$$

$$V_O = V_{C2} + V_{os} = \left(\frac{C_1}{C_2}\right) V_{IN} + V_{os}$$



→ Offset NOT cancelled, but not amplified

 → Input-referred offset = $(C_2/C_1) \times V_{OS}$, & often $C_2 < C_1$



Hold/amplify mode (S1, S3 → off S2 → on)

T/H & Input Difference Amplifier

  

Sample mode:

(S1, S3 → on S2 → off)

$$V_{C1} = V_{os} - V_{I1}, V_{C2} = 0$$

$$V_O = V_{os}$$

Input Difference Amplifier Cont'd

Subtract/Amplify mode (S1, S3 → off S2 → on)

During previous phase:

$$V_{C1} = V_{os} - V_{I1}, \quad V_{C2} = 0$$

$$V_o = V_{os}$$

$$V_{C1} = V_{os} - V_{I2}$$


$$\Delta V_{C1} = (V_{os} - V_{I2}) - (V_{os} - V_{I1}) = V_{I1} - V_{I2}$$

$$\Delta V_{C2} = \left(\frac{C_1}{C_2}\right) \Delta V_{C1} = \left(\frac{C_1}{C_2}\right) (V_{I1} - V_{I2})$$


$$V_o = \left(\frac{C_1}{C_2}\right) (V_{I1} - V_{I2}) + V_{os}$$

→ Offset NOT cancelled, but not amplified

 
→ Input-referred offset = $(C_2/C_1) \times V_{os}$, & $C_2 < C_1$



T/H & Summing Amplifier

 

T/H & Summing Amplifier Cont'd

 


Sample mode (S1, S3, S5 → on, S2, S4 → off)

$$V_{C1} = V_{0S} - V_{11}, \quad V_{C2} = V_{0S} - V_{14}, \quad V_{C3} = 0$$

$$V_O = V_{0S}$$

T/H & Summing Amplifier Cont'd

 Amplify mode (S1, S3, S5 → off, S2, S4 → on)



$$V_{C1} = V_{0S} - V_{12} \Rightarrow \Delta V_{C1} = V_{11} - V_{12}$$


$$V_{C2} = V_{0S} - V_{14} \Rightarrow \Delta V_{C2} = V_{13} - V_{14}$$

$$\Delta Q_3 = \Delta Q_1 + \Delta Q_2 = C_1 \Delta V_{C1} + C_2 \Delta V_{C2}$$

$$\Delta V_{C3} = \frac{\Delta Q_3}{C_3} = \left(\frac{C_1}{C_3} \right) (V_{11} - V_{12}) + \left(\frac{C_2}{C_3} \right) (V_{13} - V_{14})$$

$$V_O = \left(\frac{C_1}{C_3} \right) (V_{11} - V_{12}) + \left(\frac{C_2}{C_3} \right) (V_{13} - V_{14}) + V_{0S}$$

 Differential T/H Combined with Gain Stage




Employs the previously discussed technique to eliminate the problem associated with high common-mode voltage excursion at the input of the opamp

Ref: S. H. Lewis, et al., "A Pipelined 5-Msample/s 9-bit Analog-to-Digital Converter" IEEE JSSC, VOL. SC-22, NO. 6, DECEMBER 1987


Differential T/H Combined with Gain Stage

$\phi_1 \rightarrow$ High

 

Ref: S. H. Lewis, et al., "A Pipelined 5-Msample/s 9-bit Analog-to-Digital Converter" IEEE JSSC, VOL. SC-22, NO. 6, DECEMBER 1987

 Differential T/H Combined with Gain Stage



- $Gain = 4C/C = 4$
- Input voltage common-mode level removed \rightarrow opamp can have low input common-mode compliance
- Amplifier offset NOT removed

Ref: S. H. Lewis, et al., "A Pipelined 5-Msample/s 9-bit Analog-to-Digital Converter" IEEE JSSC, VOL. SC-22, NO. 6, DECEMBER 1987