

EE247

Lecture 18

ADC Converters


- Track & hold
 - T/H circuits
 - T/H combined with summing/difference function
 - T/H circuit incorporating gain & offset cancellation
 - T/H aperture uncertainty
- ADC architectures and design
 - Serial- slope type
 - Successive approximation
 - Flash ADC and its sources of error: comparator offset, sparkle code & meta-stability
- Comparator design
 - Single-stage open-loop amplifier
 - Cascade of open-loop amplifiers

Summary of Last Lecture


ADC Converters

- Sampling (continued)
 - Sampling switch considerations
 - Clock voltage boosters
 - Sampling switch charge injection & clock feedthrough
 - Complementary switch
 - Use of dummy device
 - Bottom-plate switching
- Track & hold
 - Flip around T/H


Flip-Around T/H-Basic Operation

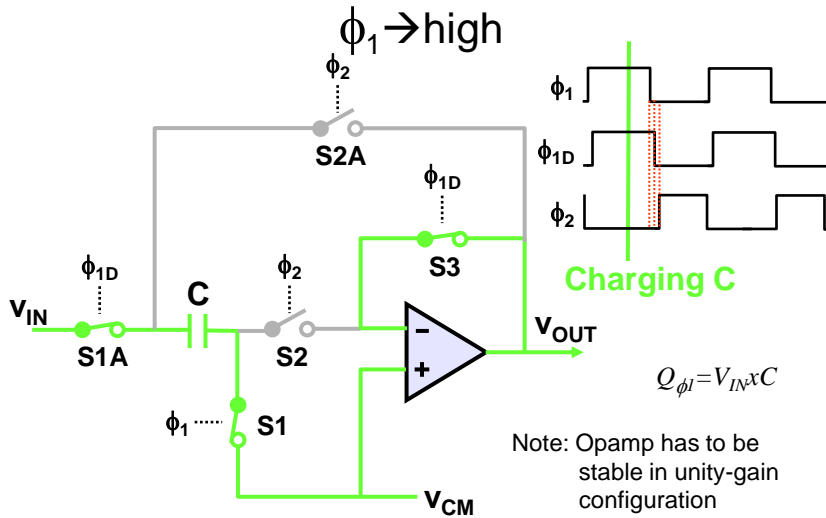

Flip-Around T/H-Basic Operation

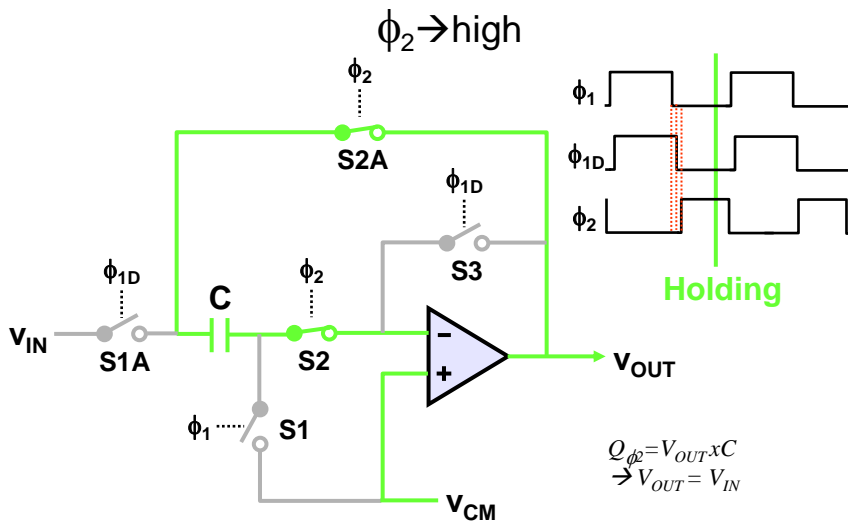


Differential Flip-Around T/H

 

Offset voltage associated with charge injection of S11 & S12 cancelled by differential nature of the circuit

Ref: W. Yang, *et al.* "A 3-V 340-mW 14-b 75-Msample/s CMOS ADC With 85-dB SFDR at Nyquist Input,"
 IEEE JOURNAL OF SOLID-STATE CIRCUITS, VOL. 36, NO. 12, DECEMBER 2001 1931


Differential Flip-Around T/H

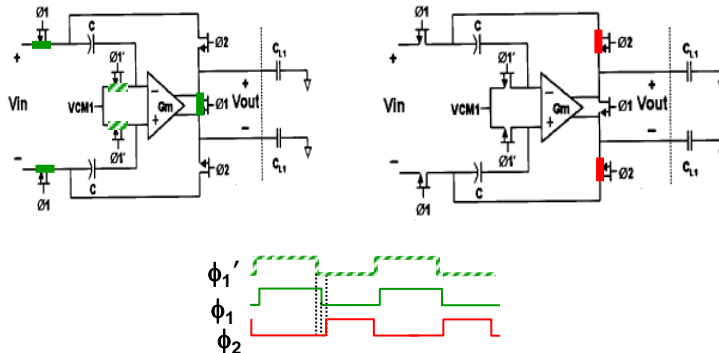

- Gain=1
- Issue: Large input common-mode compliance required


Differential Flip-Around T/H

 Issues: Large Input Common-Mode Compliance



- $\Delta V_{in-cm} = V_{out-com} - V_{sig-com}$
 → Drawback: Amplifier needs to have large input common-mode compliance


Input Common-Mode Cancellation

 

- Note: Shunting switch M3 added

Ref: R. Yen, *et al.* "A MOS Switched-Capacitor Instrumentation Amplifier," IEEE JOURNAL OF SOLID-STATE CIRCUITS, VOL. SC-17, NO. 6., DECEMBER 1982 1008

Input Common-Mode Cancellation

 

Track mode (ϕ high)

$$V_{C1} = V_{I1}, \quad V_{C2} = V_{I2}$$

$$V_{O1} = V_{O2} = 0$$

Hold mode (ϕ low)

$$V_{O1} + V_{O2} = 0$$


$$V_{O1} - V_{O2} = -(V_{I1} - V_{I2})(C_1 / (C_1 + C_3))$$

- Input common-mode level removed
- Will introduce active version in page 18

Switched-Capacitor Techniques Combining Track & Hold with Various other Functions

- T/H + Charge redistribution amplifier
- T/H & Input difference amplifier
- T/H & summing amplifier
- Differential T/H combined with gain stage
- Differential T/H including offset cancellation

T/H + Charge Redistribution Amplifier

 

Track mode: (S1, S3 → on S2 → off)

$$V_{C1} = V_{OS} - V_{IN}, V_{C2} = 0$$

$$V_O = V_{OS}$$

T/H + Charge Redistribution Amplifier Hold Mode

$$V_{C1} \rightarrow V_{OS}$$


$$\Delta V_{C1} = V_{OS} - (V_{OS} - V_{IN}) = V_{IN}$$

$$\Delta Q_1 = C_1 \Delta V_{C1} = C_1 V_{IN}$$

$$\Delta Q_2 = C_2 \Delta V_{C2} = \Delta Q_1$$

$$\Delta V_{C2} = \left(\frac{C_1}{C_2}\right) V_{C1} = V_{C2}$$
 
$$V_O = V_{C2} + V_{OS} = \left(\frac{C_1}{C_2}\right) V_{IN} + V_{OS}$$





Hold/amplify mode (S1, S3 → off S2 → on)

→ Offset NOT cancelled, but not amplified

→ Input-referred offset = $(C_2/C_1) \times V_{OS}$, & often $C_2 < C_1$

→ Can incorporate gain by having $C_1 > C_2$

T/H & Input Difference Amplifier

  

Sample mode:

(S1, S3 → on S2 → off)

$$V_{C1} = V_{os} - V_{I1}, V_{C2} = 0$$

$$V_o = V_{os}$$

Input Difference Amplifier Cont'd

Subtract/Amplify mode (S1, S3 → off S2 → on)

During previous phase:

$$V_{C1} = V_{os} - V_{I1}, V_{C2} = 0$$


$$V_o = V_{os}$$

$$V_{C1} = V_{os} - V_{I2}$$

$$\Delta V_{C1} = (V_{os} - V_{I2}) - (V_{os} - V_{I1}) = V_{I1} - V_{I2}$$

$$\Delta V_{C2} = \left(\frac{C_1}{C_2}\right) \Delta V_{C1} = \left(\frac{C_1}{C_2}\right) (V_{I1} - V_{I2})$$

 
$$V_o = \left(\frac{C_1}{C_2}\right) (V_{I1} - V_{I2}) + V_{os}$$




→ Offset NOT cancelled, but not amplified

→ Input-referred offset = $(C_2/C_1) \times V_{os}$, & $C_2 < C_1$

T/H & Summing Amplifier

 

T/H & Summing Amplifier Cont'd

 


Sample mode (S1, S3, S5 → on, S2, S4 → off)

$$V_{C1} = V_{os} - V_{11}, \quad V_{C2} = V_{os} - V_{13}, \quad V_{C3} = 0$$

$$V_o = V_{os}$$

T/H & Summing Amplifier Cont'd

 Amplify mode (S1, S3, S5 → off, S2, S4 → on)



$$V_{C1} = V_{os} - V_{12} \Rightarrow \Delta V_{C1} = V_{11} - V_{12}$$


$$V_{C2} = V_{os} - V_{14} \Rightarrow \Delta V_{C2} = V_{13} - V_{14}$$

$$\Delta Q_3 = \Delta Q_1 + \Delta Q_2 = C_1 \Delta V_{C1} + C_2 \Delta V_{C2}$$

$$\Delta V_{C3} = \frac{\Delta Q_3}{C_3} = \left(\frac{C_1}{C_3} \right) (V_{11} - V_{12}) + \left(\frac{C_2}{C_3} \right) (V_{13} - V_{14})$$

$$V_O = \left(\frac{C_1}{C_3} \right) (V_{11} - V_{12}) + \left(\frac{C_2}{C_3} \right) (V_{13} - V_{14}) + V_{os}$$

 Differential T/H Combined with Gain Stage




Employs the previously discussed technique to eliminate the problem associated with high common-mode voltage excursion at the input of the opamp

Ref: S. H. Lewis, et al., "A Pipelined 5-Msample/s 9-bit Analog-to-Digital Converter" IEEE JSSC, VOL. SC-22, NO. 6, DECEMBER 1987


Differential T/H Combined with Gain Stage

$\phi_1 \rightarrow \text{High}$

 

Ref: S. H. Lewis, et al., "A Pipelined 5-Msample/s 9-bit Analog-to-Digital Converter" IEEE JSSC, VOL. SC-22, NO. 6, DECEMBER 1987

 
Differential T/H Combined with Gain Stage



- $Gain = 4C/C = 4$
- Input voltage common-mode level removed \rightarrow opamp can have low input common-mode compliance
- Amplifier offset NOT removed

Ref: S. H. Lewis, et al., "A Pipelined 5-Msample/s 9-bit Analog-to-Digital Converter" IEEE JSSC, VOL. SC-22, NO. 6, DECEMBER 1987

 Differential T/H Including Offset Cancellation




- Operation during offset cancellation phase shown
- Auxiliary inputs added with $A_{\text{main}}/A_{\text{aux}}=10$
- During offset cancellation phase:
 - Aux. amp configured in unity-gain mode: \rightarrow offset stored on C_{AZ} & canceled during the signal acquisition phase

Ref: H. Ohara, et al., "A CMOS programmable self-calibrating 13-bit eight-channel data acquisition peripheral," *IEEE Journal of Solid-State Circuits*, vol. 22, pp. 930 - 938, December 1987.

Differential T/H Including Offset Cancellation Operational Amplifier


- Operational amplifier \rightarrow dual input folded-cascode opamp
- M3,4 auxiliary input, M1,2 main input
- To achieve 1/10 gain ratio $W_{M3,4} = 1/10 \times W_{M1,2}$ & current sources are scaled by 1/10
- M5,6,7 \rightarrow common-mode control
- Output stage \rightarrow dual cascode \rightarrow high DC gain
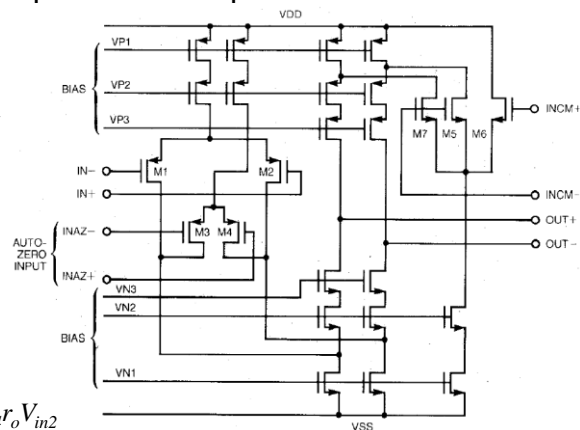
$$V_{out} = g_{m1,2} r_o V_{in1} + g_{m3,4} r_o V_{in2}$$





Ref: H. Ohara, et al., "A CMOS programmable self-calibrating 13-bit eight-channel data acquisition peripheral," *IEEE Journal of Solid-State Circuits*, vol. 22, pp. 930 - 938, December 1987.

 Differential T/H Including Offset Cancellation Phase



- During offset cancellation phase AZ and S1 closed \rightarrow main amplifier offset amplified by g_{m1}/g_{m2} & stored on C_{AZ}
- Auxiliary amp chosen to have lower gain so that:
 - Aux. amp charge injection associated with opening of switch AZ \rightarrow reduced by $A_{aux}/A_{main}=1/10$
 - Insignificant increase in power dissipation resulting from addition of aux. inputs
- Requires an extra auto-zero clock phase

Track & Hold Aperture Time Error

  


Transition from track to hold:
Occurs when device turns fully off

$$\rightarrow V_{CLK} = V_{in} + V_{TH}$$

Sharp fall-time wrt signal change
 \rightarrow no aperture error

Track & Hold Aperture Time Error

 

Slow falling clock \rightarrow aperture error

$$V_{in} = A \sin(2\pi f_{in} t)$$

$$\epsilon = f_{in} \times A \times t_{fall} / V_{CLK}$$

$SDR = -20 \log \epsilon - 4$ [dB] (imperial see Ref.)

Example:

Nyquist rate 10-bit ADC & $A = V_{CLK}/4$

$\rightarrow SQNR = 62$ dB

for distortion due to aperture error

< quant noise

$$\rightarrow t_{fall} < 2 \times 10^{-3} f_{in}$$

$$\rightarrow \text{Worst case: } f_{in} = f_s/2$$

$$\rightarrow t_{fall} < 4 \times 10^{-3} f_s$$

$$\rightarrow \text{e.g. } f_s = 1000 \text{ MHz, } t_{fall} < 4 \text{ psec}$$

Ref: P. J. Lim and B. A. Wooley, "A high-speed sample-and-hold technique using a Miller hold capacitance," *IEEE Journal of Solid-State Circuits*, vol. 26, pp. 643 - 651, April 1991.

Track & Hold Aperture Time Error

- Aperture error analysis applies to simple sampling network
- Bottom plate sampling \rightarrow reduced aperture error
- Boosted clock \rightarrow reduced aperture error

\rightarrow Clock edge fall/rise trade-off between switch charge injection versus aperture error

Ref: P. J. Lim and B. A. Wooley, "A high-speed sample-and-hold technique using a Miller hold capacitance," *IEEE Journal of Solid-State Circuits*, vol. 26, pp. 643 - 651, April 1991.


ADC

Architecture & Design


ADC Architectures

- Slope type converters
- Successive approximation
- Flash
- Time-interleaved / parallel converter
- Folding
- Residue type ADCs
 - Two-step
 - Pipeline
 - ...
- Oversampled ADCs

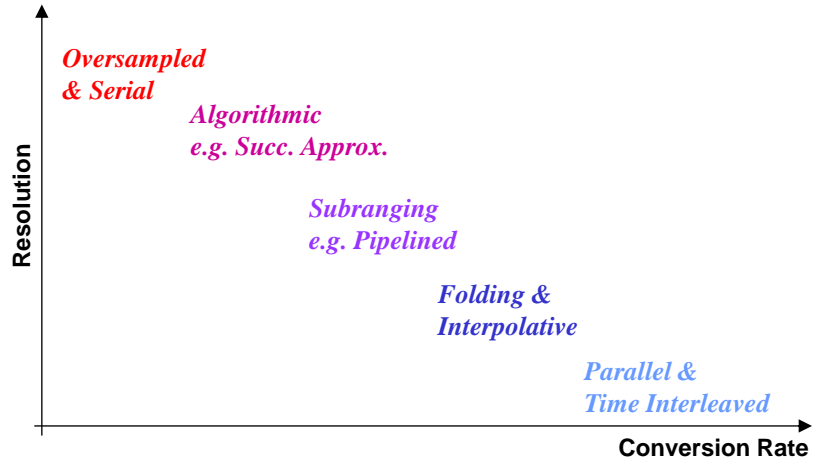Various ADC Architectures Resolution/Conversion Rate




Resolution versus Signal Bandwidth

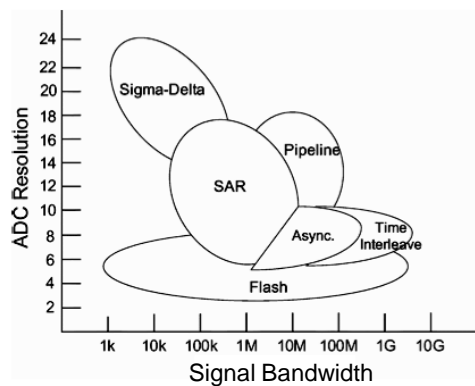


Ref: S. Chen, R. Brodersen, "A 6-bit 600-MS/s 5.3-mW Asynchronous ADC in 0.13- μ m CMOS: *IEEE J. of Solid-State Circuits*, Vol. 41, No. 12, December 2006.

Serial ADC Single Slope

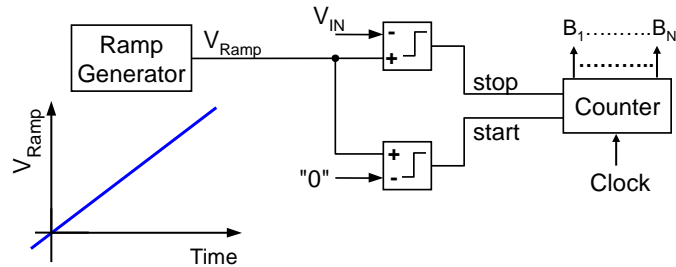

- Counter starts counting @ $V_{\text{Ramp}}=0$
- Counter stops counting for $V_{\text{IN}}=V_{\text{Ramp}}$

Serial ADC Single Slope

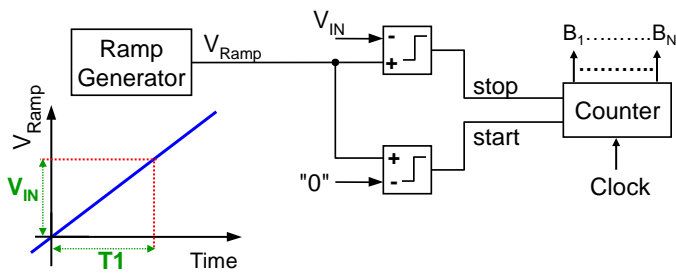


- Note that $T1$ is proportional to V_{IN}
- Counter output proportional to $T1=nT_{\text{clock}}$
 - Counter output proportional to V_{IN}
 - $2^N \times T_{\text{clock}} = V_{\text{FS}}$

Single Slope ADC


- Advantages:
 - Low complexity & simple
 - INL depends on ramp linearity & not component matching
 - Inherently monotonic
- Disadvantages:
 - Slow (2^N clock pulses for N-bit conversion) (e.g. N=16
 $f_{clock}=1MHz \rightarrow$ needs $65000 \times 1\mu s = 65ms$ /conversion)
 - Hard to generate precise ramp required for high resolution ADCs
 - Need to calibrate ramp slope versus V_{IN}
- Better: Dual Slope, Multi-Slope

Serial ADC Dual Slope

 

- First: V_{IN} is integrated for a fixed time ($2^N \times T_{CLK}$)
 $\rightarrow V_o = 2^N \times T_{CLK} \times V_{IN} / \tau_{intg}$
- Next: V_o is de-integrated with V_{REF} until $V_o = 0$
 \rightarrow Counter output = $2^N \times V_{IN} / V_{REF}$

Dual Slope ADC

 

http://www.maxim-ic.com/appnotes.cfm/appnote_number/1041

- Integrate V_{in} for fixed time (T_{INT}), de-integrate with V_{REF} applied $\rightarrow T_{De-Int} \sim 2^N \times T_{CLK} \times V_{in} / V_{REF}$
- Most laboratory DVMs use this type of ADC

Dual Slope ADC



- Advantage:
 - Accuracy to 1st order independent of integrator time-constant and clock period
 - Comparator offset referred to input is attenuated by integrator high DC gain
 - Insensitive to most linear error sources
 - DNL is a function of clock jitter
 - Power line (60Hz) xtalk effect on reading can be canceled by: choosing conversion time multiple of 1/60Hz
 - High accuracy achievable (16+bit)
- Disadvantage:
 - Slow (maximum $2 \times 2^N \times T_{clk}$ per conversion)
 - Integrator opamp offset results in ADC offset (can cancel)
 - Finite opamp gain gives rise to INL

ADC Architectures

- Slope type converters
- ➔ • Successive approximation
- Flash
- Time-interleaved / parallel converter
- Folding
- Residue type ADCs
 - Two-step
 - Pipeline
 - ...
- Oversampled ADCs


Successive Approximation ADC SAR

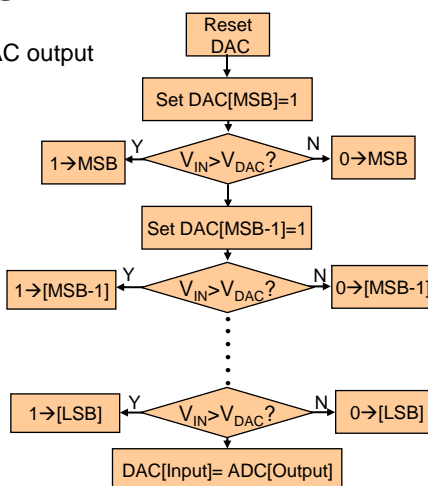 - Algorithmic type ADC
- Based on binary search over DAC output




Successive Approximation ADC

Example: 6-bit ADC & $V_{IN}=5/8V_{REF}$

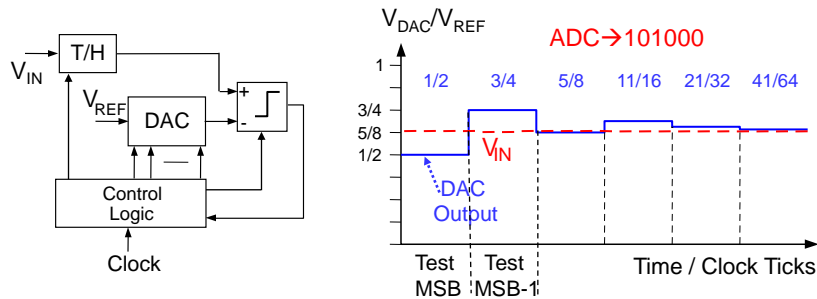


- High accuracy achievable (16+ Bits)
- Need DAC to be accurate enough
- Require N clock cycles for N-bit conversion (much faster than slope type)
- Moderate speed (highest SAR conversion rate 2Ms/sec & 18bits)

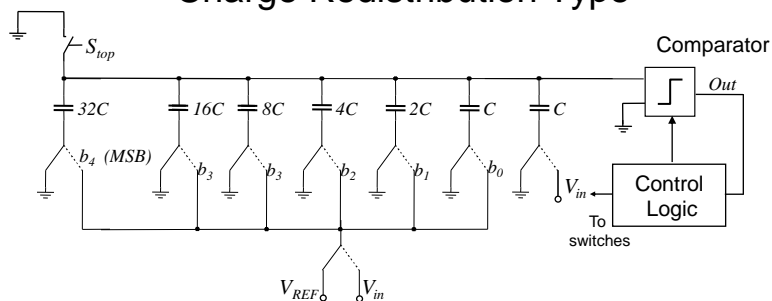Example: SAR ADC Charge Redistribution Type




- Built with binary weighted capacitors, switches, comparator & control logic
- T/H inherent in DAC

 Charge Redistribution Type SAR DAC Operation: Determining the MSB



- Operation starts by connecting all top plate to gnd and all bottom plates to V_{in}
- To test the MSB all top plate are opened bottom plate of 32C connected to V_{REF} & rest of bottom plates connected to ground \rightarrow input to comparator = $-V_{in} + V_{REF}/2$
- Comparator is strobed to determine the polarity of input signal:
 - If negative MSB=1, else MSB=0
- The process continues until all bits are determined

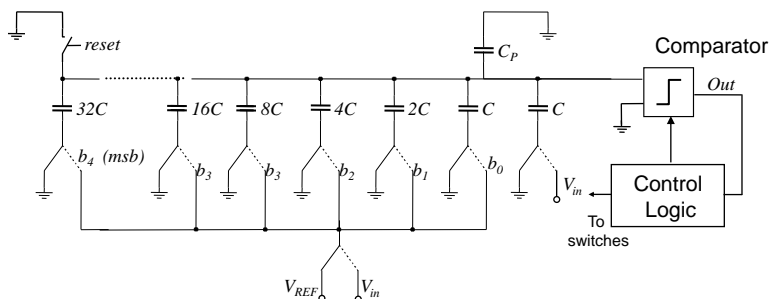Example: SAR ADC Charge Redistribution Type



- To 1st order parasitic (C_p) insensitive since top plate driven from initial 0 to final V_{REF} by the global negative feedback
- Linearity is a function of accuracy of C ratios
- Possible to add a C ratio calibration cycle (see Ref.)


Ref: H. Lee, D. A. Hodges, and P. R. Gray, "A self-calibrating 15 bit CMOS A/D converter," *IEEE Journal of Solid-State Circuits*, vol. 19, pp. 813 - 819, December 1984.



ADC Architectures

- Slope type converters
- Successive approximation
- • Flash
- Time-interleaved / parallel converter
- Folding
- Residue type ADCs
 - Two-step
 - Pipeline
 - ...
- Oversampled ADCs


Flash ADC

 - B-bit flash ADC:
 - DAC generates all possible $2^B - 1$ levels
 - $2^B - 1$ comparators compare V_{IN} to DAC outputs
 - Comparator output:
 - If $V_{DAC} < V_{IN} \rightarrow 1$
 - If $V_{DAC} > V_{IN} \rightarrow 0$
 - Comparator outputs form thermometer code
 - Encoder converts thermometer to binary code
- Application example: 6-bit Flash ADC in Disk Drives with Gs/s conversion rate




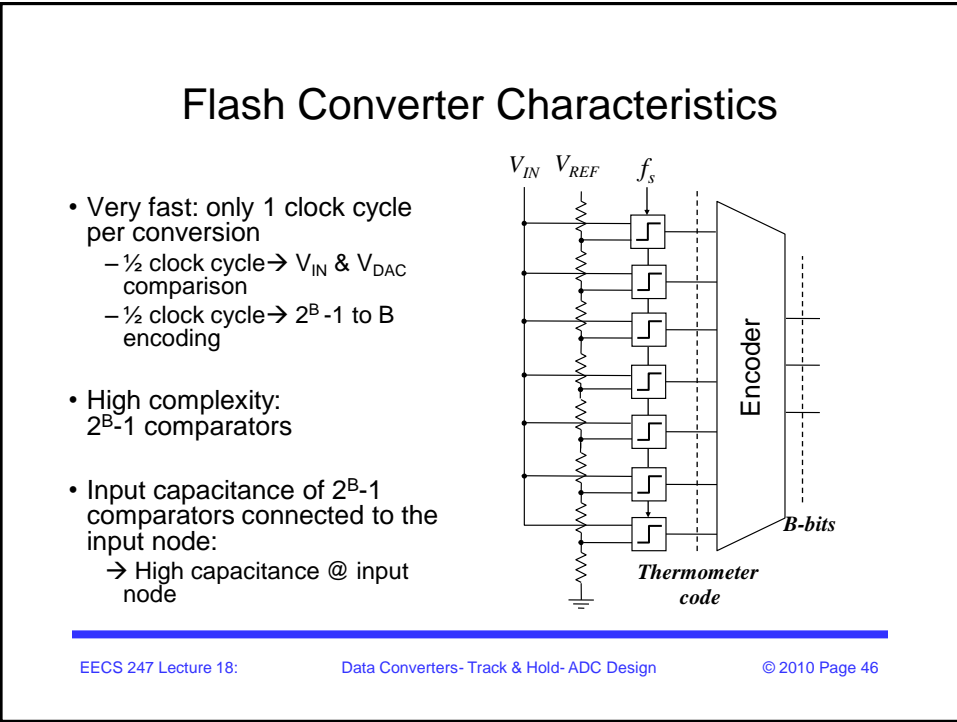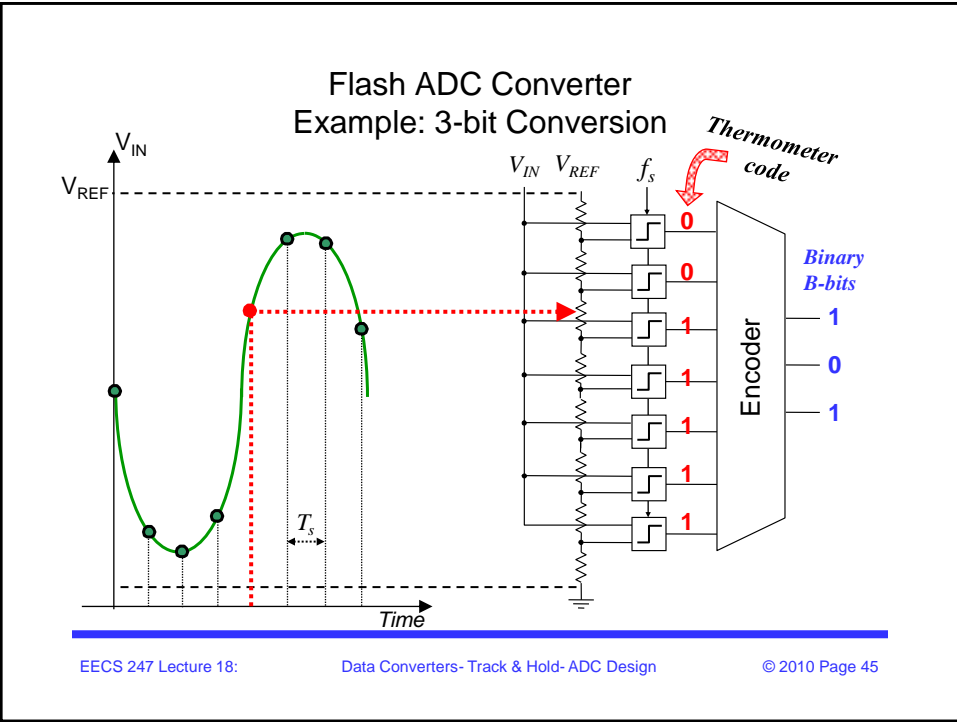

Flash ADC Converter Considerations

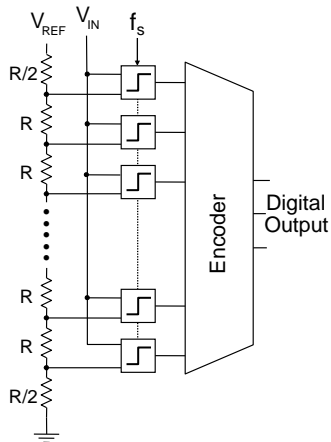


Assume simple comparator design

 

Depending on V_{in} level x_n lower comparators have M1 on & M2 off x_m upper comparators have M1 off & M2 (m+n=2^B-1)
 → Total capacitance experienced by input source a function of V_{in}
 → Also note V_{in} feedthrough to V_{ref} taps via M1 & M2 G-S capacitance & R_s
 → When switches M_x open, charge injection and clock feedthru causes perturbation on R taps

Flash Converter Sources of Error

 


- Comparator input:
 - DC offset
 - Nonlinear input capacitance
 - Feedthrough of input signal to reference ladder
 - Kickback noise (disturbs reference)
 - Signal dependent sampling time (addition of T/H @ the input eliminates this problem)
- Comparator output:
 - Sparkle codes (... 0001011111)
 - Metastability

Flash ADC Converter

 Example: 8-bit ADC Comparator Offset Considerations

- 8-bit → 255 comparators
- $V_{REF}=1V \rightarrow 1LSB=4mV$
- $DNL < 1/2LSB \rightarrow$
Comparator input referred offset $< 2mV$
- Assuming close to 100% yield, $2mV = 6\sigma_{offset}$
 $\rightarrow \sigma_{offset} < 0.33mV$



Flash ADC Converter

Example: 8-bits ADC (continued)

$$\rightarrow 1\sigma_{offset} < 0.33mV$$

- Let us assume in the technology used:

$$- \text{Voffset-per-unit-sqrt}(W \times L) = 3 mV \times \mu$$

$$V_{offset} = \frac{3mV}{\sqrt{W \times L}} = 0.33mV \rightarrow W \times L = 83\mu^2$$

$$\text{Assuming: } C_{ox} = 9 fF / \mu^2 \rightarrow C_{GS} = \frac{2}{3} C_{ox} W \times L = 496 fF$$

$$\rightarrow \text{Total max. input capacitance: } 255 \times 0.496 = 126.5 pF!$$

- Issues:

- Si area quite large
- Large ADC input capacitance
- Since depending on input voltage level different number of comparator input transistors would be on/off- total input capacitance varies as input varies
- \rightarrow Nonlinear input capacitance could give rise to signal distortion

Ref: M. J. M. Pelgrom, A. C. J. Duinmaijer, and A. P. G. Welbers, "Matching properties of MOS transistors," *IEEE Journal of Solid-State Circuits*, vol. 24, pp. 1433 - 1439, October 1989.

Flash ADC Converter Example (continued)


Trade-offs:

- Allowing larger DNL e.g. 1LSB instead of 0.5LSB:
 - Increases the maximum allowable input-referred offset voltage by a factor of 2
 - Decreases the required device WxL by a factor of 4
 - Reduces the input device area by a factor of 4
 - Reduces the input capacitance by a factor of 4!
- Reducing the ADC resolution by 1-bit
 - Increases the maximum allowable input-referred offset voltage by a factor of 2
 - Decreases the required device WxL by a factor of 4
 - Reduces the input device area by a factor of 4
 - Reduce the input capacitance by a factor of 4


Flash Converter Maximum Tolerable Comparator Offset versus ADC Resolution

Assumption:
 $DNL=0.5LSB$

 
Note:
Graph shows max. tolerable offset, note that depending on min acceptable yield, the derived offset numbers are associated with 2σ to 6σ offset voltage




Typical Flash ADC Output Encoder

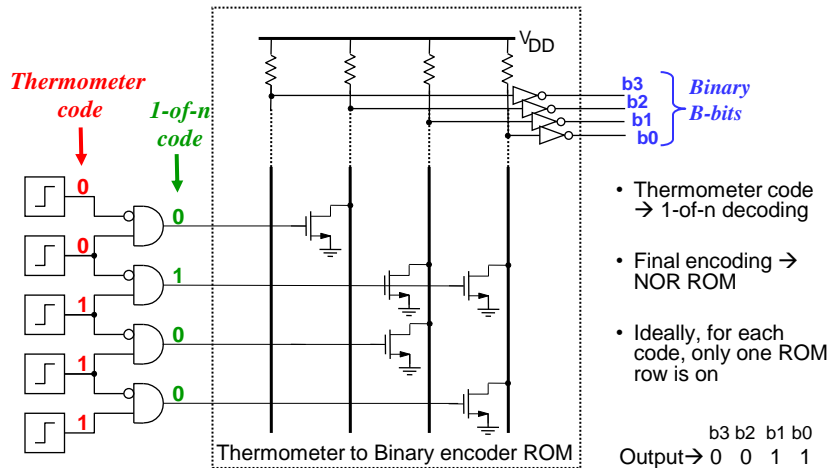

Sparkle Codes

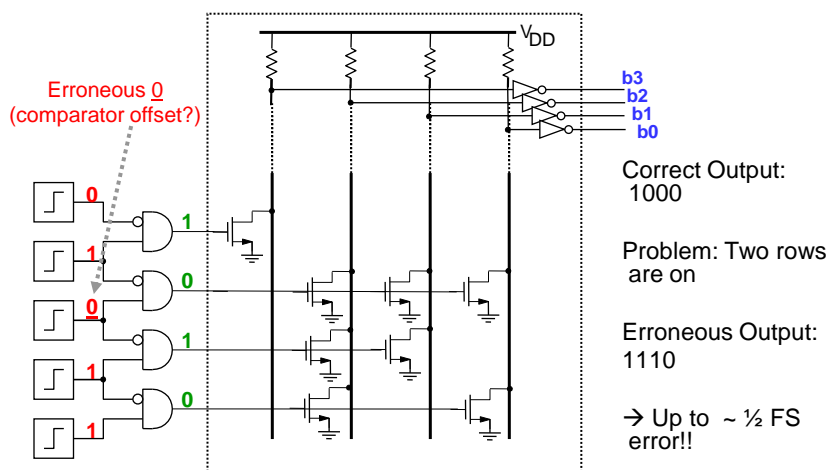


Sparkle Tolerant Encoder

 

- Protects against a *single* sparkle.
- Possible to improve level of sparkle protection by increasing # of NAND gate inputs

Ref: C. Mangelsdorf et al, "A 400-MHz Flash Converter with Error Correction," JSSC February 1990, pp. 997-1002

Meta-Stability

 

Different gates interpret metastable output X differently

Correct output: 1000

Erroneous output: 0000

Solutions:

- Add latches to comparator outputs (high power)
- Gray encoding

Ref: C. Portmann and T. Meng, "Power-Efficient Metastability Error Reduction in CMOS Flash A/D Converters," JSSC August 1996, pp. 1132-40

Gray Encoding Example: 3bit ADC

Thermometer Code							Gray			Binary		
T ₇	T ₆	T ₅	T ₄	T ₃	T ₂	T ₁	G ₃	G ₂	G ₁	B ₃	B ₂	B ₁
0	0	0	0	0	0	0	0	0	0	0	0	0
0	0	0	0	0	0	1	0	0	1	0	0	1
0	0	0	0	0	1	1	0	1	1	0	1	0
0	0	0	0	1	1	1	0	1	0	0	1	1
0	0	0	1	1	1	1	1	1	0	1	0	0
0	0	1	1	1	1	1	1	1	1	1	0	1
0	1	1	1	1	1	1	1	0	1	1	1	0
1	1	1	1	1	1	1	1	0	0	1	1	1


$$G_1 = T_1 \overline{T_3} + T_5 \overline{T_7}$$

$$G_2 = T_2 \overline{T_6}$$

$$G_3 = T_4$$

- Each T_i affects only one G_i
→ Metastability in one T output affects only one of the G bits (unlike binary)
- Protects also against sparkles
- Follow Gray encoder by (latch and) Gray-to-binary encoder

Voltage Comparators

 

Play an important role in majority of ADCs

Function: Compare the instantaneous value of two analog signals & generate a digital output voltage based on the sign of the difference:

$$\text{If } V_{i+} - V_{i-} > 0 \rightarrow V_{out} = "1"$$

$$\text{If } V_{i+} - V_{i-} < 0 \rightarrow V_{out} = "0"$$

Voltage Comparator Architectures

Comparator architecture choices:

- High gain amplifier with differential analog input & single-ended large swing output
 - Output swing has to be compatible with driving digital logic circuits
 - Open-loop amplification → no frequency compensation required
 - Precise or linear transfer function not required
- Latched comparators; in response to a strobe (clock edge), input stage disabled & digital output stored in a latch till next strobe
 - Two options for implementation :
 - Latch-only comparator
 - Low-gain preamplifier + high-sensitivity latch
- Sampled-data comparators
 - T/H input
 - Offset cancellation



Comparator Built with High-Gain Amplifier

Amplify $V_{in(min)}$ to V_{DD}
 → $V_{in(min)}$ determined by ADC resolution

  Example: 12-bit ADC with:
 - $V_{FS} = 1.5V \rightarrow 1LSB = 0.36mV$
 - $V_{DD} = 1.8V$

→ For 1.8V output & 0.5LSB resolution:

$$A_v^{Min} = \frac{1.8V}{0.18mV} \approx 10,000$$



Comparator Design 1-Single-Stage Amplification

- Amplifier maximum Gain-Bandwidth product (f_u) for a given technology, typically a function of maximum device f_t

$$f_u = \text{unity-gain frequency, } f_o = -3\text{dB frequency} \quad f_o = \frac{f_u}{A_v}$$

Example: $f_u = 10\text{GHz}$ & $A_v = 10,000$

$$f_o = \frac{10\text{GHz}}{10,000} \approx 1\text{MHz}$$


$$\tau_{\text{settling}} = \frac{1}{2\pi f_o} = 0.16\mu\text{sec}$$

Allow a few τ for output to settle


$$f_{\text{Clock}}^{\text{Max.}} \rightarrow \frac{1}{5\tau_{\text{settling}}} \approx 1.26\text{MHz}$$

Too slow for majority of applications!

 
→ Try cascade of lower gain stages to broaden frequency of operation



 Comparator Design 2- Cascade of Open Loop Amplifiers



 The stages identical → small-signal model for the cascades:



One stage:

$$|A_v(0)| = g_m R_L$$

$$\omega_o = -3\text{dB frequency} = \frac{1}{R_L C_T}$$

$$\omega_u = -\text{unity gain frequency} = G \times \text{BW} = \frac{g_m}{C_T}$$

$$\therefore \omega_o = \frac{\omega_u}{|A_v(0)|}$$

Open Loop Cascade of Amplifiers

For an N-stage cascade:

$$A_T(j\omega) = [A_V(j\omega)]^N = \frac{[A_V(0)]^N}{\left(1 + j\frac{\omega}{\omega_p}\right)^N}$$

Define

$$\omega_{oN} \equiv \text{-3dB frequency of the N-stage cascade}$$

Then

$$|A_T(j\omega_{oN})| = \frac{|A_V(0)|^N}{\sqrt{2}}$$

and

$$\omega_{oN} = \omega_o \sqrt{2^{1/N} - 1} = \frac{\omega_u}{|A_V(0)|} \sqrt{2^{1/N} - 1}$$

∴ For a specified $|A_T(0)|$

$$|A_V(0)| = |A_T(0)|^{1/N}$$

$$\Rightarrow \omega_{oN} = \frac{\omega_u}{|A_T(0)|^{1/N}} \sqrt{2^{1/N} - 1}$$

Thus,

$$\frac{\omega_{oN}}{\omega_{o1}} = \left[\frac{\omega_u}{|A_T(0)|^{1/N}} \sqrt{2^{1/N} - 1} \right] \bigg/ \left[\frac{\omega_u}{|A_T(0)|} \right]$$

$$= |A_T(0)|^{\left(\frac{N-1}{N}\right)} \sqrt{2^{1/N} - 1}$$

Example: $N=4, A_T=10000 \rightarrow \omega_{oN}=430\omega_{o1}$

Open Loop Cascade of Amplifiers

For $|A_T(\text{DC})|=10,000$

N	ω_{oN}/ω_{o1}	$ A_V(0) $
1	1	10,000
2	64	100
3	236	21.5
4	435	10
5	611	6.3
10	1067	2.5
20	1185	1.6

Example:

$$N=3, f_u=10\text{GHz} \ \& \ |A_T(0)|=10000$$

$$f_{oN} = \frac{10\text{GHz}}{(10,000)^{1/3}} \sqrt{2^{1/3}-1} \approx 237\text{MHz}$$

$$\tau_{\text{settling}} = \frac{1}{2\pi f_o} = 0.7\text{nsec}$$


Allow a few τ for output to settle

$$f_{\text{Clock}}^{\text{Max}} \rightarrow \frac{1}{5\tau_{\text{settling}}} \approx 290\text{MHz}$$


f_{max} improved from 1.26MHz to 290MHz $\rightarrow X236$

Open Loop Cascade of Amplifiers Offset Voltage

 - From offset point of view: high gain/stage is preferred



 - Choice of # of stage
→ bandwidth vs offset tradeoff




$$A_T = A_1 \cdot A_2 \cdot A_3$$

$$\text{Input-referred offset} \rightarrow V_{os} = V_{os1} + \frac{V_{os2}}{A_1} + \frac{V_{os3}}{A_1 \cdot A_2}$$

Open Loop Cascade of Amplifiers Step Response

 - Assuming linear behavior (not slew limited)



$$v_{o1} = \frac{1}{C} \int_0^t g_m v_{in} dt = \frac{g_m}{C} v_{in} t$$


$$v_{o2} = \frac{1}{C} \int_0^t g_m v_{o1} dt = \frac{g_m}{C} \int_0^t \frac{g_m}{C} v_{in} t dt = \frac{1}{2} \left(\frac{g_m}{C} \right)^2 v_{in} t^2$$

$$v_{o3} = \frac{1}{C} \int_0^t g_m v_{o2} dt = \frac{g_m}{C} \int_0^t \left[\frac{1}{2} \left(\frac{g_m}{C} \right)^2 v_{in} t^2 \right] dt$$

$$= \frac{1}{3} \left(\frac{g_m}{C} \right)^3 v_{in} t^3$$

Open Loop Cascade of Amplifiers Step Response

• Assuming linear behavior

 

N Stages

$$v_{oN} = \left(\frac{g_m}{C}\right)^N \left(\frac{t^N}{N!}\right) v_{in}$$

For the output to reach a specified v_{out} (i.e., $v_{oN} = v_{out}$) the delay is

$$\tau_D = \left(\frac{C}{g_m}\right) \left[(N!) \left(\frac{v_{out}}{v_{in}}\right) \right]^{1/N}$$

Open Loop Cascade of Amplifiers Delay/(C/g_m)

$$\tau_D = \left(\frac{C}{g_m}\right) \left[(N!) \left(\frac{V_{out}}{V_{in}}\right) \right]^{1/N}$$

- Minimum total delay broad function of N
- Relationship between # of stages resulting in minimum delay (N_{opt}) and gain (V_{out}/V_{in}) approximately:

$$N_{opt} \approx 1 + \log_2 A_T \quad \text{for } A < 1000$$

$$N_{opt} \approx 1.2 \ln A_T \quad \text{for } A \geq 1000$$

N	Delay/(C/g _m)			
	10	100	1000	10K
1	10	100	1000	10K
2	4.5	14.1	44.7	141
3	3.9	8.4	18.2	39.1
4	3.9	7.0	12.4	22.1
5	4.1	6.5	10.4	16.4
6	4.4	6.4	9.5	13.9
7	4.7	6.5	9.1	12.6
8	5.0	6.7	8.9	11.9
9	5.4	6.9	8.9	11.5
10	5.7	7.2	9.0	11.4
11	6.1	7.5	9.2	11.3
12	6.4	7.8	9.4	11.4
20	9.3	10.5	11.7	13.2

Ref: J.T. Wu, et al., "A 100-MHz pipelined CMOS comparator" *IEEE Journal of Solid-State Circuits*, vol. 23, pp. 1379 - 1385, December 1988.