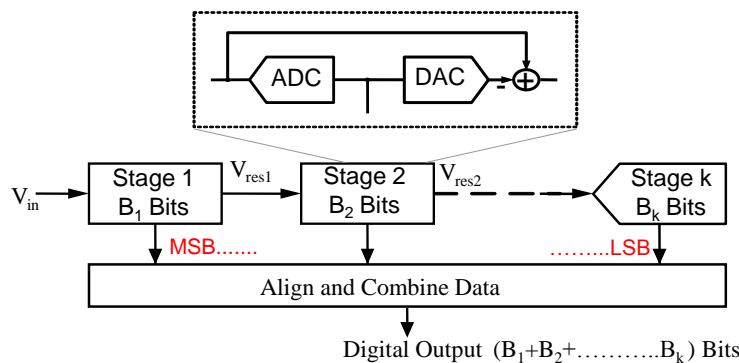


EE247 Lecture 22


- Pipelined ADCs (continued)
 - Effect sub-ADC, gain stage, sub-DAC non-idealities on overall ADC performance (continued)
 - Correction for inter-stage gain nonlinearity
 - Implementation
 - Combining the bits
 - Practical circuits
 - Stage scaling
 - Stage implementation
 - Circuits
 - Noise budgeting
 - How many bits per stage?
 - Algorithmic ADCs utilizing pipeline structure
 - Advanced background calibration techniques
- Time Interleaved Converters
- ADC figures of merit

Pipeline ADC Block Diagram




- Idea: Cascade several low resolution stages to obtain high overall resolution (e.g. 10bit ADC can be built with series of 10 ADCs each 1-bit only!)
- Each stage performs coarse A/D conversion and computes its quantization error, or "residue"

Summary So Far Pipelined A/D Converters

 


- Cascade of low resolution stages
 - By adding inter-stage gain = $2^{B_{\text{eff}}}$
 - No need to scale down V_{ref} for stages down the pipe
 - Reduced accuracy requirement for stages coming after stage 1
 - Addition of Track & Hold function to interstage-gain
 - Stages can operate concurrently
 - Throughput increased to as high as one sample per clock cycle
 - Latency function of number of stages & conversion-per-stage
 - Correction for circuit non-idealities
 - Built-in redundancy compensate for sub-ADC inaccuracies such as comparator offset (interstage gain: $G=2^{B_{\text{neff}}}$, $B_{\text{neff}} < B_n$)
 - Error associated with gain stage and sub-DAC calibrated out

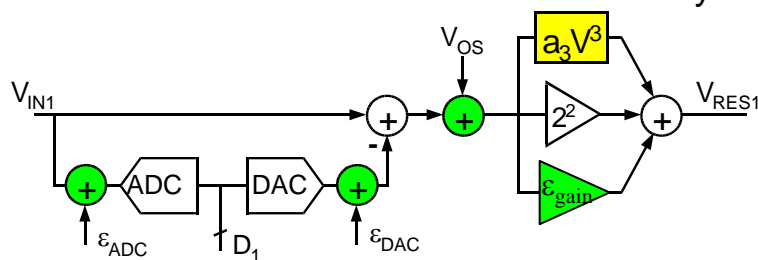Pipelined ADC Error Correction/Calibration Summary



Error	Correction/Calibration
ϵ_{ADC} , V_{OS}	Redundancy either same stage or next stage
ϵ_{gain}	Digital adjustment
ϵ_{DAC}	Either sufficient component matching or digital calibration
Inter-stage amplifier non-linearity	?


Inter-stage Gain Nonlinearity

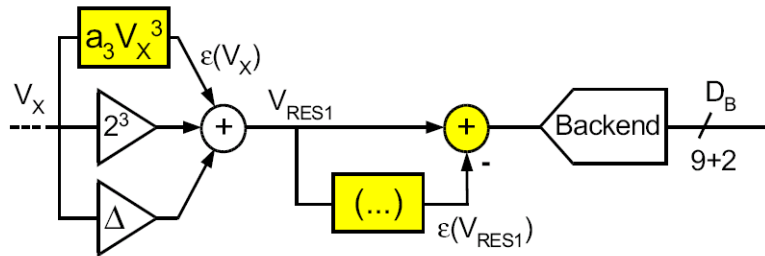

- Invert gain stage non-linear polynomial
- Express error as function of V_{RES1}
- Push error compensator into digital domain through backend ADC

Ref: B. Murmann and B. E. Boser, "A 12-b, 75MS/s Pipelined ADC using Open-Loop Residue Amplification," *ISSCC Dig. Techn. Papers*, pp. 328-329, 2003


Inter-stage Gain Nonlinearity

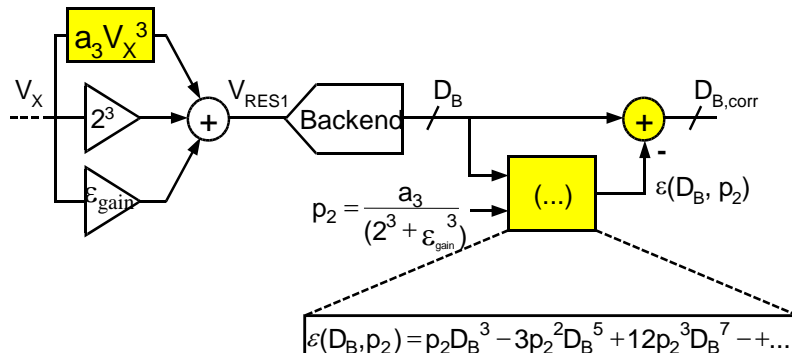

- Pre-measured & stored in table look-up form
- p_2 continuously estimated & updated (account for temp. & other variations)

Ref: B. Murmann and B. E. Boser, "A 12-b, 75MS/s Pipelined ADC using Open-Loop Residue Amplification," *ISSCC Dig. Techn. Papers*, pp. 328-329, 2003

 
Inter-stage Gain Nonlinearity Compensation Proof of Concept Evaluation Prototype



- Re-used 14-bit ADC in 0.35 μ m from Analog Devices [Kelly, ISSCC 2001]
- Modified only 1st stage with 3- b_{eff} \rightarrow open-loop amplifier built with simple diff-pair + resistive load instead of the conventional feedback around high-gain amp
- Conventional 9- b_{eff} backend, 2-bit redundancy in 1st stage
- Real-time post-processor off-chip (FPGA)


Ref: B. Murmann and B. E. Boser, "A 12-b, 75MS/s Pipelined ADC using Open-Loop Residue Amplification," *ISSCC Dig. Techn. Papers*, pp. 328-329, 2003

 Measurement Results 12-bit ADC w Extra 2-bits for Calibration



Combining the Bits

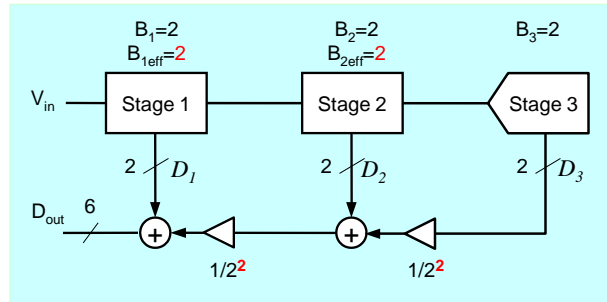
- Example: Three 2-bit stages, no redundancy




$$D_{out} = D_1 + \frac{1}{2^{B_{1eff}}} D_2 + \frac{1}{2^{B_{1eff}} \cdot 2^{B_{2eff}}} D_3$$

$$D_{out} = D_1 + \frac{1}{4} D_2 + \frac{1}{16} D_3$$

Combining the Bits

 


 - Only bit shifts
- No arithmetic circuits needed



Combining the Bits Including Redundancy

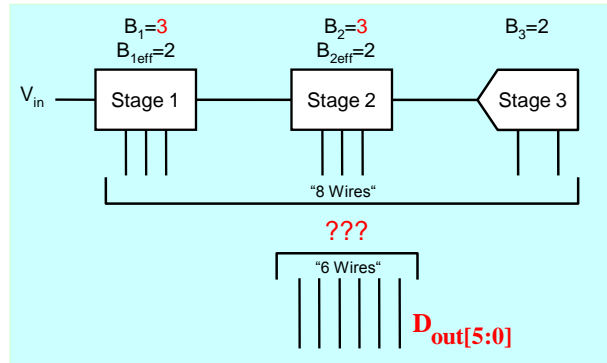- Example: Three 2-bit stages, incorporating 1-bit redundancy in stages 1 and 2





Combining the Bits


$$D_{out} = D_1 + \frac{1}{2^{B_{1eff}}} D_2 + \frac{1}{2^{B_{1eff}} \cdot 2^{B_{2eff}}} D_3$$

$$D_{out} = D_1 + \frac{1}{4} D_2 + \frac{1}{16} D_3$$

- Bits overlap
- Need adders

  


Combining the Bits Example

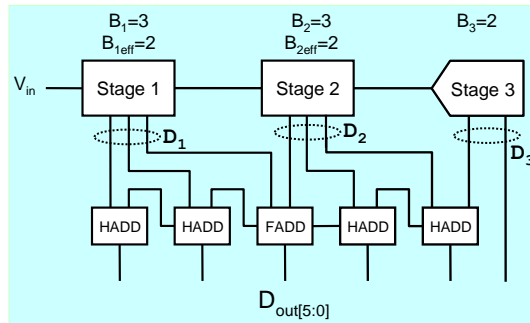


D_1	001
D_2	111
D_3	10
D_{out}	011000

Pipelined ADC Stage Implementation

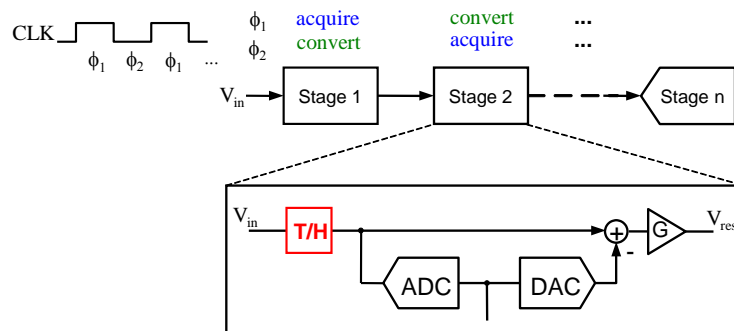


- Each stage needs T/H hold function
- Track phase: Acquire input/residue from previous stage
- Hold phase: sub-ADC decision, compute residue

Stage Implementation

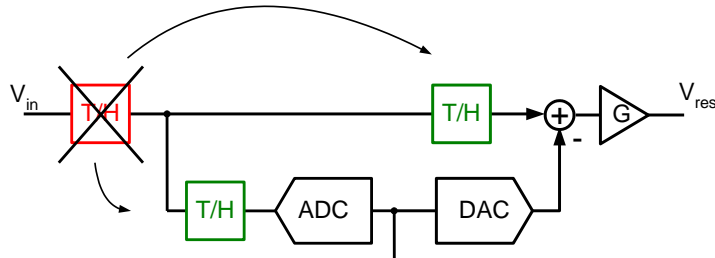


- Usually no dedicated T/H amplifier in each stage (Except first stage in some cases – why?)
- T/H implicitly contained in stage building blocks

Stage Implementation

 


- DAC-subtract-gain function can be lumped into a single switched capacitor circuit
- "MDAC"

1.5-Bit Stage Implementation Example

 


Ref: A. Abo, "Design for Reliability of Low-voltage, Switched-capacitor Circuits," UCB PhD Thesis, 1999

 1.5-Bit Stage Implementation Acquisition Cycle



Ref: A. Abo, "Design for Reliability of Low-voltage, Switched-capacitor Circuits," UCB PhD Thesis, 1999

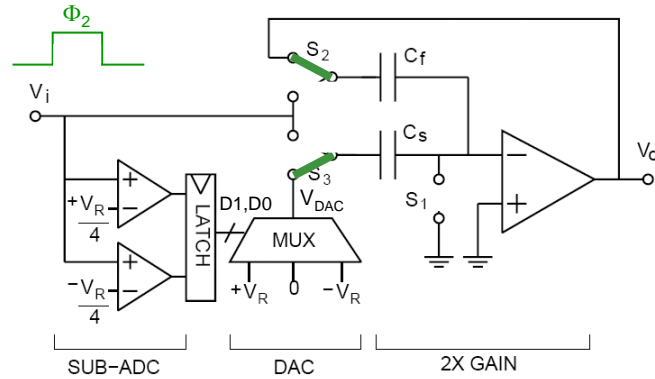1.5-Bit Stage Implementation Conversion Cycle



Ref: A. Abo, "Design for Reliability of Low-voltage, Switched-capacitor Circuits," UCB PhD Thesis, 1999

1.5-Bit Stage Implementation Conversion Cycle

V_{DAC} induces equal currents in C_s and C_f :

$$V_{DAC} \times C_s = -V_o \times C_f$$

$$Q_{Cf} = -V_{DAC} \times C_s$$


$$Q_{Cf}^{Total} \Big|_{\phi_2} = Q_{Cf} \Big|_{\phi_1} + Q_{Cs} \Big|_{\phi_1} - V_{DAC} \times C_s$$

$$V_o \times C_f = V_i \times C_f + V_i \times C_s - V_{DAC} \times C_s$$

$$V_o = V_i \left(1 + \frac{C_s}{C_f} \right) - V_{DAC} \times \frac{C_s}{C_f}$$

$$C_s = C_f$$

$$V_o = 2V_i - V_{DAC}$$

 


	D1, D0	V_{DAC}
$V_i > V_R/4$	1 1	$-V_R$
$-V_R/4 < V_i < V_R/4$	0 1	0
$V_i < -V_R/4$	0 0	$+V_R$

1.5 Bit Stage Implementation Example

$$V_o = \begin{cases} \left(1 + \frac{C_s}{C_f}\right) V_i - \frac{C_s}{C_f} V_{ref} & \text{if } V_i > V_{ref}/4 \\ \left(1 + \frac{C_s}{C_f}\right) V_i & \text{if } -V_{ref}/4 \leq V_i \leq +V_{ref}/4 \\ \left(1 + \frac{C_s}{C_f}\right) V_i + \frac{C_s}{C_f} V_{ref} & \text{if } V_i < -V_{ref}/4 \end{cases}$$


Note:

 - Interstage gain set by C ratios
- Accuracy better than 0.1%
- Up to 10bit level no need for gain calibration





Ref: A. Abo, "Design for Reliability of Low-voltage, Switched-capacitor Circuits," UCB PhD Thesis, 1999

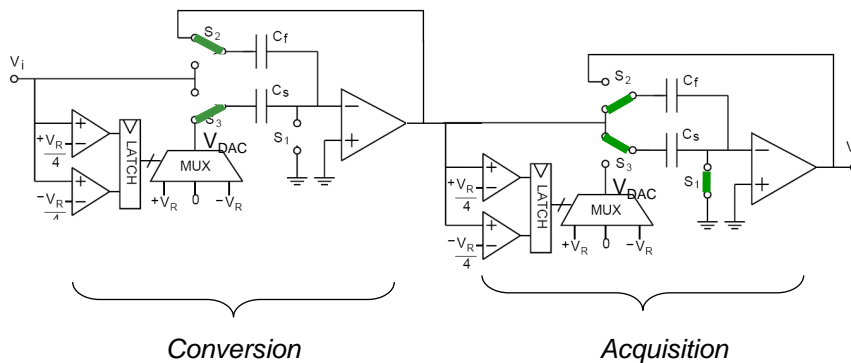1.5-Bit Stage Implementation Timing of Stages



Pipelined ADC Stage Power Dissipation & Noise

 
 
- Typically pipeline ADC noise dominated by inter- stage gain blocks
- Sub-ADC comparator noise translates into comparator threshold uncertainty and is compensated for by redundancy



$$V_{noise}^{in} = \sqrt{V_{n1}^2 + \frac{V_{n2}^2}{G1^2} + \frac{V_{n3}^2}{G1^2 G2^2} + \dots}$$


Pipelined ADC Stage Scaling

  - Example: Pipeline using 1-bit_{eff} stages



- Total input referred noise power: $N_{tot} \propto kT \left[\frac{1}{C_1} + \frac{1}{G1^2 C_2} + \frac{1}{G1^2 G2^2 C_3} + \dots \right]$
- $N_{tot} \propto kT \left[\frac{1}{C_1} + \frac{1}{4C_2} + \frac{1}{16C_3} + \dots \right]$


Pipelined ADC Stage Scaling

 

$$N_{tot} \propto kT \left[\frac{1}{C_1} + \frac{1}{4C_2} + \frac{1}{16C_3} + \dots \right]$$

- If all caps made the same size, backend stages contribute very little noise
 - Wasteful power-wise, because:
 - ❑ Power $\sim G_m$
 - ❑ Speed $\sim G_m/C$
- Fixed speed $\rightarrow G_m/C$ fixed \rightarrow Power $\sim C$

Pipelined ADC Stage Scaling

 


$$N_{tot} \propto kT \left[\frac{1}{C_1} + \frac{1}{4C_2} + \frac{1}{16C_3} + \dots \right]$$


- How about scaling caps down by $G^2=2^2=4x$ per stage?
 - Same amount of noise from every stage
 - All stages contribute significant noise
 - To keep overall noise the same \rightarrow noise/stage must be reduced
 - Power $\sim G_m \sim C$ goes up!

Stage Scaling Example: 2-bit_{eff}/stage

Extreme 1: All Stages the Same Size

 

 Extreme 2: All Stages Contribute the Same Noise




- Optimum capacitor scaling lies approximately midway between these two extremes

Ref: D. W. Cline, P.R. Gray "A power optimized 13-b 5MSamples/s pipelined analog-to-digital converter in 1.2um CMOS," JSSC 3/1996


Pipeline ADC Stage Scaling

 - Power minimum is "shallow"
- Near optimum solution in practice: Scale capacitors by stage gain
- E.g. for effective stage resolution of 1bit (Gain=2):





$$N_{tot} \propto kT \left[\frac{1}{C} + \frac{1}{2C} + \frac{1}{4C} + \dots \right]$$

Stage Scaling Example

 

Note:
Resolution
per stage:
→ 2bits

→ $G=4$

  

Ref: D. W. Cline, P.R Gray "A power optimized 13-b 5 MSamples/s pipelined analog-to-digital converter in 1.2 μ m CMOS," JSSC 3/1996

How Many Bits Per Stage?

- Many possible architectures
 - E.g. $B_{1\text{eff}}=3, B_{2\text{eff}}=1, \dots$
 - vs. $B_{1\text{eff}}=1, B_{2\text{eff}}=1, B_{3\text{eff}}=1, \dots$
 - Complex optimization problem, fortunately optimum tends to be shallow...
 - Qualitative answer:
 - Maximum speed for given technology
 - Use small resolution-per-stage (large feedback factor)
 - Maximum power efficiency for fixed, "low" speed
 - Try higher resolution stages
 - Can help alleviate matching & noise requirements in stages following the 1st stage
- Ref: Singer VLSI 96, Yang, JSSC 12/01 (14bit ADC w/o calibration)


14 & 12-Bit State-of-the-Art Implementations

Reference	Yang (JSSC 12/2001) 0.35 μ /3V	Loloe (ESSIRC 2002) 0.18 μ /3V
Bits	14	12
Architecture	3-1-1-1-1-1-1-1-1-3	1-1-1-1-1-1-1-1-1-1-2
SNR/SFDR	~73dB/88dB	~66dB/75dB
Speed	75MS/s	80MS/s
Power	340mW	260mW

10 & 8-Bit State-of-the-Art Implementations


Reference	Yoshioko et al (ISSCC 2005) 0.18 μ /1.8V	Kim et al (ISSCC 2005) 0.18 μ /1.8V
Bits	10	8
Architecture	1.5bit/stage	2.8 -2.8 - 4
SNR/SFDR	~55dB/66dB	~48dB/56dB
Speed	125MS/s	200MS/s
Power	40mW	30mW

Algorithmic ADC

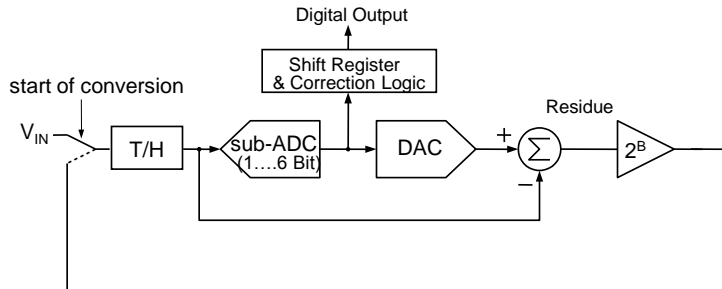

- Essentially same as pipeline, but a single stage is reused for all partial conversions
- For overall B_{overall} bits \rightarrow need $B_{\text{overall}}/B_{\text{stage}}$ clock cycles per conversion
 - \rightarrow Small area, slow
 - \rightarrow Trades conversion time for area

 
Least Mean Square Adaptive Digital Background Calibration of Pipelined Analog-to-Digital Converters



- Slow, but accurate ADC operates in parallel with pipelined (main) ADC
- Slow ADC samples input signal at a lower sampling rate (f_s/n)
- Difference between corresponding samples for two ADCs (e) used to correct fast ADC digital output via an adaptive digital filter (ADF) based on minimizing the Least-Mean-Squared error

Ref: Y. Chiu, *et al*, "Least Mean Square Adaptive Digital Background Calibration of Pipelined Analog-to-Digital Converters," IEEE TRANS. CAS, VOL. 51, NO. 1, JANUARY 2004

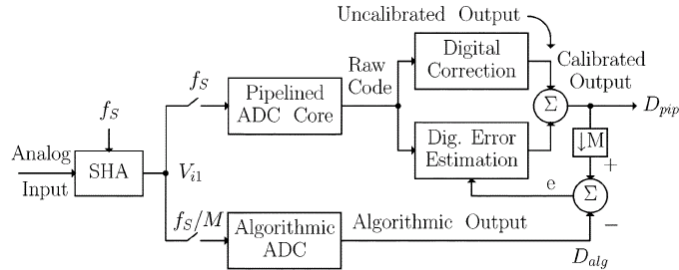
Example: "A 12-bit 20-MS/s pipelined analog-to-digital converter with nested digital background calibration"



- Pipelined ADC operates at 20Ms/s @ has 1.5bit/stage
- Slow ADC → Algorithmic type operating at 20Ms/32=625ks/s
- Digital correction accounts for bit redundancy
- Digital error estimator → minimizes the mean-squared-error

Ref: X. Wang, P. J. Hurst, S. H. Lewis, "A 12-bit 20-Msample/s pipelined analog-to-digital converter with nested digital background calibration", IEEE JSSC, vol. 39, pp. 1799 - 1808, Nov. 2004

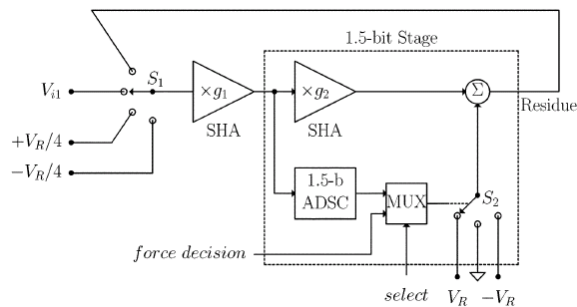
Algorithmic ADC Used for Calibration of Pipelined ADC (continued from previous page)



- Uses replica of pipelined ADC stage
- Requires extra SHA in front to hold residue
- Undergoes a calibration cycle periodically prior to being used to calibrate pipelined ADC

Ref: X. Wang, P. J. Hurst, S. H. Lewis, "A 12-bit 20-MS/s pipelined analog-to-digital converter with nested digital background calibration", IEEE JSSC, vol. 39, pp. 1799 - 1808, Nov. 2004

 12-bit 20-MS/s Pipelined ADC with Digital Background Calibration



Sampling capacitors scaled ($1B_{\text{eff}}/\text{stage}$):



- Input SHA: 6pF
- Pipelined ADC: 2pF, 0.9, 0.4, 0.2, 0.1, 0.1...
- Algorithmic ADC: 0.2pF

Chip area: 13.2mm²

- Does not include digital calibration circuitry estimated ~1.7mm²
- Area of Algorithmic ADC <20%

Ref: X. Wang, P. J. Hurst, S. H. Lewis, "A 12-bit 20-MS/s pipelined analog-to-digital converter with nested digital background calibration", IEEE JSSC, vol. 39, pp. 1799 - 1808, Nov. 2004

 
 
Measurement Results 12-bit 20-MS/s Pipelined ADC with Digital Background Calibration



Ref: X. Wang, P. J. Hurst, S. H. Lewis, "A 12-bit 20-MS/s pipelined analog-to-digital converter with nested digital background calibration", IEEE JSSC, vol. 39, pp. 1799 - 1808, Nov. 2004

Measurement Results

  12-bit 20-MS/s Pipelined ADC with Digital Background Calibration



Ref: X. Wang, P. J. Hurst, S. H. Lewis, "A 12-bit 20-MS/s pipelined analog-to-digital converter with nested digital background calibration", IEEE JSSC, vol. 39, pp. 1799 - 1808, Nov. 2004

Measurement Results

12-bit 20-MS/s Pipelined ADC with Digital Background Calibration

PERFORMANCE SUMMARY (3.3 V, 25 °C)

Process	0.35 μ m 2P4M CMOS	
Sampling rate	20 Msample/s	
Active area	7.5 mm ²	
Full-Scale Input	1.6 Vp-p	
	Without Cal.	With Cal.
Analog Power Diss.	190 mW	226 mW
Total Power Diss.	217 mW	254 mW
Max. INL (Pip. ADC)*	4.21 LSB	0.47 LSB
Max. DNL (Pip. ADC)*	0.60 LSB	0.41 LSB
SNDR (Alg. ADC)*	49.6 dB	59.6 dB
SNDR (Pip. ADC)*	58.2 dB	70.8 dB
SFDR (Pip. ADC)*	59.4 dB	93.3 dB
THD (Pip. ADC) *	-59.4 dB	-92.9 dB
PSRR*	65.0 dB	64.8 dB
CMRR*	73.6 dB	73.4 dB

* f_{in} = 58 kHz

Does not include digital calibration circuitry estimated ~1.7mm²

Alg. ADC SNDR dominated by noise


Ref: X. Wang, P. J. Hurst, S. H. Lewis, "A 12-bit 20-MS/s pipelined analog-to-digital converter with nested digital background calibration", IEEE JSSC, vol. 39, pp. 1799 - 1808, Nov. 2004

ADC Architectures


- Slope type converters
- Successive approximation
- Flash
- Interpolating & Folding
- Residue type ADCs
 - Two-step Flash
 - Pipelined ADCs
- ➔ • Time-interleaved / parallel converter
- Oversampled ADCs

Time Interleaved Converters

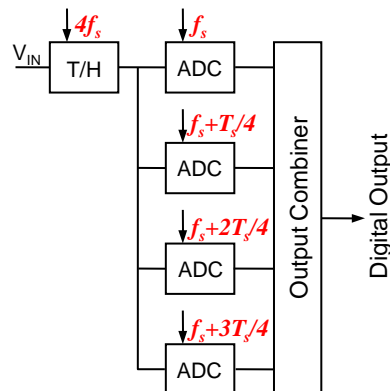- Example:
 - 4 ADCs operating in parallel at sampling frequency f_s
 - Each ADC converts on one of the 4 possible clock phases
 - Overall sampling frequency = $4f_s$
 - Note T/H has to operate at $4f_s$!
- Extremely fast:
Typically, limited by speed of T/H
- Accuracy limited by mismatch among individual ADCs (timing, offset, gain, ...)



Time Interleaved Converters Timing

 

- Note: Effective sampling rate $\rightarrow 4f_s$

ADC Figures of Merit

- Objective: Establish measure/s to compare performance of various ADCs
- Can use FOM to combine several performance metrics to get one single number
- What are reasonable FOM for ADCs?


ADC Figures of Merit

$$FOM_1 = f_s \cdot 2^{ENOB}$$

- This FOM suggests that adding an extra bit to an ADC is just as hard as doubling its bandwidth
- Is this a good assumption?

Ref: R. H. Walden, "Analog-to-digital converter survey and analysis," *IEEE Journal on Selected Areas in Communications*, April 1999

Survey Data

 

Ref: R. H. Walden, "Analog-to-digital converter survey and analysis," *IEEE Journal on Selected Areas in Communications*, April 1999

ADC Figures of Merit

$$FOM_2 = \frac{Power}{f_s \cdot 2^{ENOB}} \quad [J / conv]$$

- Sometimes inverse of this metric is used
- In typical circuits power ~ speed, FOM_2 captures this tradeoff correctly
- How about power vs. ENOB?
 - One more bit 2x in power?

Ref: R. H. Walden, "Analog-to-digital converter survey and analysis," *IEEE Journal on Selected Areas in Communications*, April 1999

ADC Figures of Merit

- One more bit means...
 - 6dB SNR, 4x less noise power, 4x larger C
 - Power ~ G_m ~ C increases **4x**
- Even worse: Flash ADC
 - Extra bit means 2x number of comparators
 - Each of them needs double precision
 - Transistor area 4x, Current 4x to keep same current density
 - Net result: Power increases **8x**

ADC Figures of Merit


- FOM_2 seems not entirely appropriate, but somehow still standard in literature, papers
- "Tends to work" because:
 - Not all power in an ADC is "noise limited"
 - E.g. Digital power, biasing circuits, etc.
- Better use FOM_2 to compare ADCs with same resolution!

ADC Figures of Merit


$$FOM_3 = \frac{Power}{Speed}$$

- Compare only power of ADCs with approximately same ENOB
- Useful numbers:
 - 10b (~9 ENOB) ADCs: 1 mW/MSample/sec
Note the ISSCC 05 example: 0.33mW/MS/sec!
 - 12b (~11 ENOB) ADCs: 4 mW/MSample/sec


10-Bit ADC Power/Speed

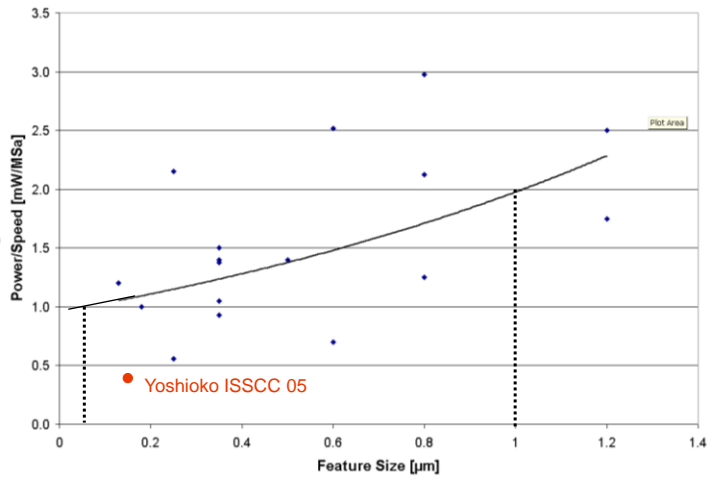

12-Bit ADC Power/Speed

 

Performance Trend

 

ADC Architectures

- Slope type converters
- Successive approximation
- Flash
- Interpolating & Folding
- Residue type ADCs
 - Two-step Flash
 - Pipelined ADCs
- Time-interleaved / parallel converter
- ➡ • Oversampled ADCs

Analog-to-Digital Converters

- Two categories:

- Nyquist rate ADCs $\rightarrow f_{sig}^{max} \sim 0.5x f_{sampling}$


- Maximum achievable signal bandwidth higher compared to oversampled type
 - Resolution limited to max. ~14 to 16bits

- Oversampled ADCs $\rightarrow f_{sig}^{max} \ll 0.5x f_{sampling}$


- Maximum possible signal bandwidth lower compared to nyquist rate ADCs
 - Maximum achievable resolution high (18 to 20bits!)

The Case for Oversampling

Nyquist sampling:

 


Oversampling:

 

- Nyquist rate $f_N \sim 2B$
- Oversampling rate $M = f_s/f_N \gg 1$

 Nyquist v.s. Oversampled Converters Antialiasing Requirements




Oversampling Benefits

- Almost no stringent requirements imposed on analog building blocks
- Takes advantage of the availability of low cost, low power digital filtering
- Relaxed transition band requirements for analog anti-aliasing filters
- Reduced baseband quantization noise power
- Allows trading speed for resolution

ADC Converters Baseband Noise

 - For a quantizer with quantization step size Δ and sampling rate f_s :
 - Quantization noise power distributed uniformly across Nyquist bandwidth ($f_s/2$)



- Power spectral density:

$$N_e(f) = \frac{\overline{e^2}}{f_s} = \left(\frac{\Delta^2}{12}\right) \frac{1}{f_s}$$

- Noise is distributed over the Nyquist band $-f_s/2$ to $f_s/2$

Oversampled Converters Baseband Noise

$$S_B = \int_{-f_B}^{f_B} N_e(f) df = \int_{-f_B}^{f_B} \left(\frac{\Delta^2}{12}\right) \frac{1}{f_s} df$$


$$= \frac{\Delta^2}{12} \left(\frac{2f_B}{f_s}\right)$$

where for $f_B = f_s/2$

$$S_{B0} = \frac{\Delta^2}{12}$$

$$S_B = S_{B0} \left(\frac{2f_B}{f_s}\right) = \frac{S_{B0}}{M}$$

 where $M = \frac{f_s}{2f_B} = \text{oversampling ratio}$



Oversampled Converters Baseband Noise

$$S_B = S_{B0} \left(\frac{2f_B}{f_s} \right) = \frac{S_{B0}}{M}$$

where $M = \frac{f_s}{2f_B} = \text{oversampling ratio}$

2X increase in M

→ 3dB reduction in S_B


→ ½ bit increase in resolution/octave oversampling

To further increase the improvement in resolution:

- Embed quantizer in a feedback loop (patented by Cutler in 1960s!)


→ Noise shaping (sigma delta modulation)

Pulse-Count Modulation

 


Mean of pulse-count signal approximates analog input!

Pulse-Count Output Spectrum

 


- Signal band of interest: low frequencies, $f < B \ll f_s$
- Quantization error: high frequency, $B \dots f_s / 2$
- Separate with digital low-pass filter!

Oversampled ADC Predictive Coding

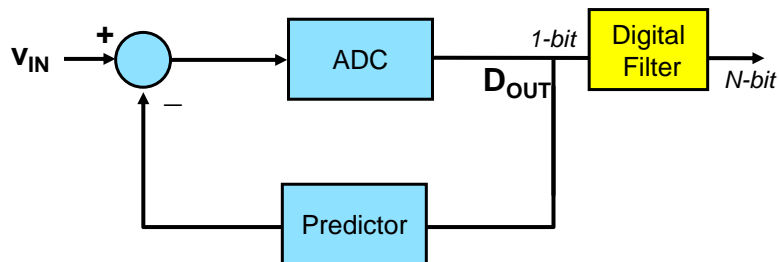

- Quantize the difference signal rather than the signal itself
- Smaller input to ADC \rightarrow Buy dynamic range
- Only works if combined with oversampling
- 1-Bit digital output
- Digital filter computes "average" \rightarrow N-bit output

Oversampled ADC

 

Decimator:

- Digital (low-pass) filter
- Removes quantization noise for $f > B$
- Provides anti-alias filtering for DSP
- Narrow transition band, high-order (digital filters with high order consume significantly smaller power & area compared to analog filters)
- 1-Bit input, N-Bit output (essentially computes “average”)


Modulator or Analog Front End (AFE)

- Objectives:
 - Convert analog input to 1-Bit pulse density stream
 - Move quantization error to high frequencies $f \gg B$
 - Operates at high frequency $f_s \gg f_N$
 - $M = 8 \dots 256$ (typical)....1024
 - Since modulator operated at high frequencies
→ need to keep analog circuitry “simple”

→ $\Sigma\Delta = \Delta\Sigma$ Modulator


Sigma- Delta Modulators

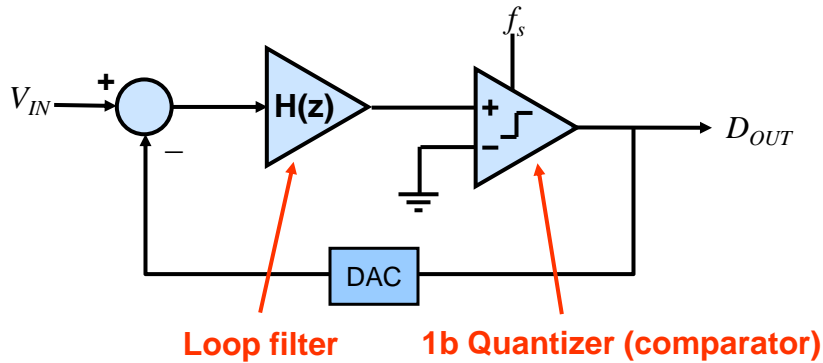Analog 1-Bit $\Sigma\Delta$ modulators convert a continuous time analog input v_{IN} into a 1-Bit sequence D_{OUT}




Sigma-Delta Modulators

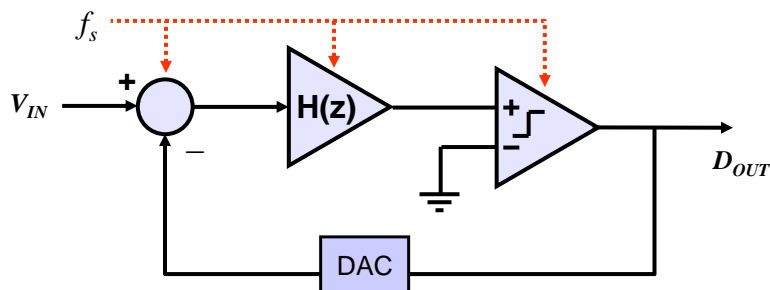- The loop filter H can be either switched-capacitor or continuous time
- Switched-capacitor filters are “easier” to implement + frequency characteristics scale with clock rate
- Continuous time filters provide anti-aliasing protection




Oversampling A/D Conversion

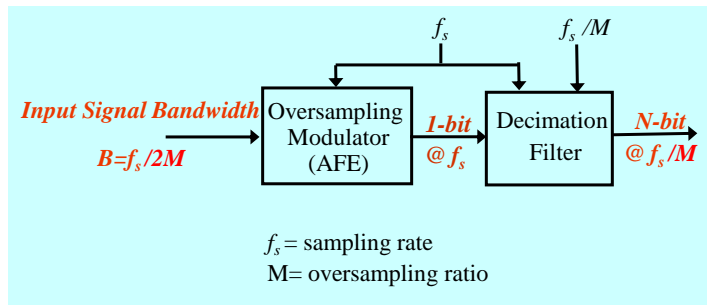

- Analog front-end → oversampled noise-shaping modulator
 - Converts original signal to a 1-bit digital output at the high rate of ($2BXM$)
- Digital back-end → digital filter (decimator)
 - Removes out-of-band quantization noise
 - Provides anti-aliasing to allow re-sampling @ lower sampling rate

1st Order $\Sigma\Delta$ Modulator

 1st order modulator, simplest loop filter → an integrator



Note: Non-linear system with memory → difficult to analyze