

EE247


Lecture 5

- Filters
 - Effect of integrator non-idealities on filter behavior
 - Integrator quality factor and its influence on filter frequency characteristics (brief review for last lecture)
 - Filter dynamic range limitations due to limited integrator linearity
 - Measures of linearity: Harmonic distortion, intermodulation distortion, intercept point
 - Effect of integrator component variations and mismatch on filter response
 - Various integrator topologies utilized in monolithic filters
 - Resistor + C based filters
 - Transconductance (gm) + C based filters
 - Switched-capacitor filters
 - Continuous-time filter considerations
 - Facts about monolithic Rs, gms, & Cs and its effect on integrated filter characteristics


Summary of Lecture 4

- Ladder type RLC filters converted to integrator based active filters
 - All pole ladder type filters
 - Convert RLC ladder filters to integrator based form
 - Example: 5th order Butterworth filter
 - High order ladder type filters incorporating zeros
 - 7th order elliptic filter in the form of ladder RLC with zeros
 - Sensitivity to component mismatch
 - Compare with cascade of biquads
 - *Doubly terminated LC ladder filters* ⇒ *Lowest sensitivity to component variations*
 - Convert to integrator based form utilizing SFG techniques
 - Example: Differential high order filter implementation
 - Effect of integrator non-idealities on continuous-time filter behavior
 - Effect of integrator finite DC gain & non-dominant poles on filter frequency response

Real Integrator Non-Idealities

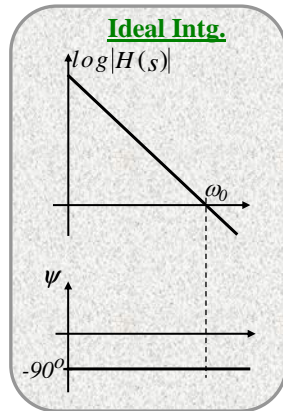


$$H(s) = \frac{-\omega_0}{s}$$

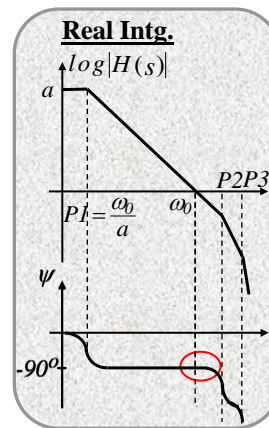

$$H(s) \approx \frac{-a}{\left(1 + s \frac{a}{\omega_0}\right) \left(1 + \frac{s}{p2}\right) \left(1 + \frac{s}{p3}\right) \dots}$$

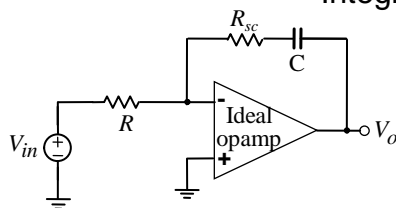Effect of Integrating Capacitor Series Resistance on Integrator Q




Finite R_{sc} adds LHP zero @ $\frac{1}{R_{sc}C}$

$$H(s) = \frac{-\omega_0 (1 + R_{sc}Cs)}{s}$$

$$\rightarrow Q_{intg} \approx \frac{R}{R_{sc}}$$

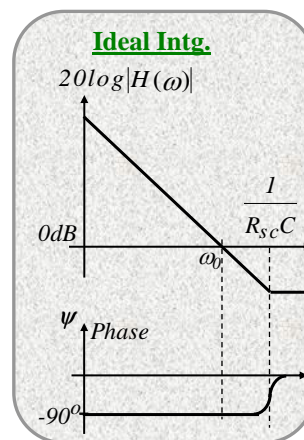Typically, opamp non-idealities dominate Q_{intg}



Summary

Effect of Integrator Non-Idealities on Q

$$Q_{ideal}^{intg.} = \infty$$

$$Q_{real}^{intg.} \approx \frac{1}{\frac{1}{a} - \omega_0 \sum_{i=2}^{\infty} \frac{1}{p_i}}$$

- Amplifier finite DC gain reduces the overall Q in the same manner as series/parallel resistance associated with passive elements
- Amplifier poles located above integrator unity-gain frequency enhance the Q!
 - If non-dominant poles close to unity-gain freq. → Oscillation
- Depending on the location of unity-gain-frequency, the two terms can cancel each other out!
- Overall quality factor of the integrator has to be much higher compared to the filter's highest pole Q

Effect of Integrator Non-Linearities on Overall Integrator-Based Filter Performance

- Dynamic range of a filter is determined by the ratio of maximum signal output with acceptable performance over total noise
- Maximum signal handling capability of a filter is determined by the non-linearities associated with its building blocks
- Integrator linearity function of opamp/R/C (or any other component used to build the integrator) linearity-
- Linearity specifications for active filters typically given in terms of :
 - Maximum allowable harmonic distortion @ the output
 - Maximum tolerable intermodulation distortion
 - Intercept points & compression point referred to output or input


Component Linearity versus Overall Filter Performance 1- Ideal Components

Ideal DC transfer characteristics:

Perfectly linear output versus input transfer function with no clipping

$$V_{out} = \alpha V_{in} \text{ for } -\infty \leq V_{in} \leq \infty$$
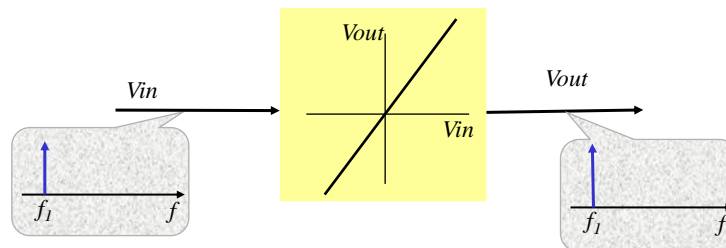
$$\text{If } V_{in} = A \sin(\omega t) \rightarrow V_{out} = \alpha A \sin(\omega t)$$



Component Linearity versus Overall Filter Performance 2- Semi-Ideal Components

Semi-ideal DC transfer characteristics:

Perfectly linear output versus input transfer function with clipping


$$V_{out} = \alpha V_{in} \text{ for } -\Delta \leq V_{in} \leq +\Delta$$

$$V_{out} = -\Delta\alpha \text{ for } V_{in} \leq -\Delta$$

$$V_{out} = \Delta\alpha \text{ for } V_{in} \geq \Delta$$

$$\text{If } V_{in} = A \sin(\omega t) \rightarrow V_{out} = \alpha A \sin(\omega t) \text{ for } -\Delta \leq V_{in} \leq +\Delta$$

Otherwise clipped & distorted

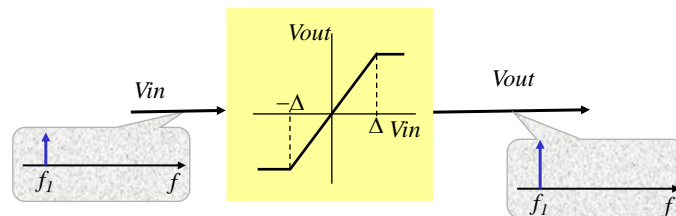


Effect of Component Non-Linearities on Overall Filter Linearity Real Components including Non-Linearities

Real DC transfer characteristics: Both soft non-linearities & hard (clipping)

$$V_{out} = \alpha_1 V_{in} + \alpha_2 V_{in}^2 + \alpha_3 V_{in}^3 + \dots \text{for } -\Delta \leq V_{in} \leq \Delta$$

Clipped otherwise
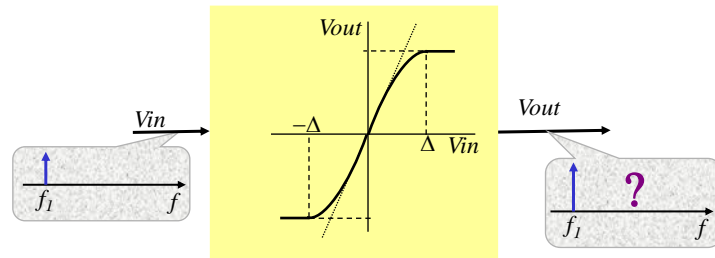
$$\text{If } V_{in} = A \sin(\omega_1 t)$$



Effect of Component Non-Linearities on Overall Filter Linearity Real Components including Non-Linearities


Typical real circuit DC transfer characteristics:

$$V_{out} = \alpha_1 V_{in} + \alpha_2 V_{in}^2 + \alpha_3 V_{in}^3 + \dots \text{ If } V_{in} = A \sin(\omega_1 t) \text{ \& } A < \Delta$$

Then:

$$\rightarrow V_{out} = \alpha_1 A \sin(\omega_1 t) + \alpha_2 A^2 \sin^2(\omega_1 t) + \alpha_3 A^3 \sin^3(\omega_1 t) + \dots$$
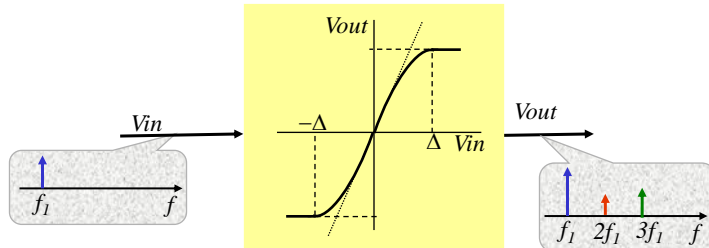
$$\text{or } V_{out} = \alpha_1 A \sin(\omega_1 t) + \frac{\alpha_2 A^2}{2} (1 - \cos(2\omega_1 t)) + \frac{\alpha_3 A^3}{4} (3\sin(\omega_1 t) - \sin(3\omega_1 t)) + \dots$$



Effect of Component Non-Linearities on Overall Filter Linearity Harmonic Distortion

$$V_{out} = \alpha_1 A \sin(\omega t) + \frac{\alpha_2 A^2}{2} (1 - \cos(2\omega t)) + \frac{\alpha_3 A^3}{4} (3\sin(\omega t) - \sin(3\omega t)) + \dots$$

$$HD2 = \frac{\text{amplitude } 2^{\text{nd}} \text{ harmonic distortion component}}{\text{amplitude fundamental}}$$


$$HD3 = \frac{\text{amplitude } 3^{\text{rd}} \text{ harmonic distortion component}}{\text{amplitude fundamental}}$$

$$\rightarrow HD2 = \frac{1}{2} \times \frac{\alpha_2}{\alpha_1} A, \quad HD3 = \frac{1}{4} \times \frac{\alpha_3}{\alpha_1} A^2$$

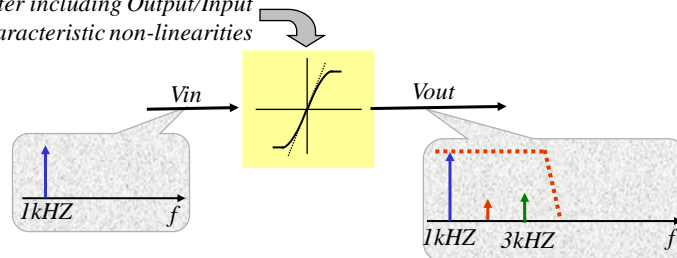Example: Significance of Filter Harmonic Distortion in Voice-Band CODECs

- Voice-band CODEC filter (CODEC stands for coder-decoder, telephone circuitry includes CODECs with extensive amount of integrated active filters)
- Specifications includes limits associated with maximum allowable harmonic distortion at the output (< typically < 1% → -40dB)

CODEC Filter including Output/Input transfer characteristic non-linearities



Example: Significance of Filter Harmonic Distortion in Voice-Band CODECs

- Specifications includes limits associated with maximum allowable harmonic distortion at the output (< typically < 1% → -40dB)
- Let us assume filter output/input transfer characteristic:

$$\frac{\alpha_3}{\alpha_1} = 1/100 \text{ and } \alpha_2 \text{ is negligible}$$

since:

$$HD3 = \frac{1}{4} \times \frac{\alpha_3}{\alpha_1} A^2$$

The requirement of $HD3 < 1/100 \rightarrow A_{\max} \leq 2V_{\text{peak}}$

- Note that with fixed HD3 requirements, larger α_3 would result in smaller acceptable maximum signal levels and therefore reduces the overall dynamic range.
- Maximizing dynamic range requires highly linear circuit components

Effect of Component Non-Linearities on Overall Filter Linearity Intermodulation Distortion

DC transfer characteristics including nonlinear terms, input 2 sinusoidal waveforms:

$$V_{out} = \alpha_1 V_{in} + \alpha_2 V_{in}^2 + \alpha_3 V_{in}^3 + \dots$$

$$\text{If } V_{in} = A_1 \sin(\omega_1 t) + A_2 \sin(\omega_2 t)$$

Then V_{out} will have the following components:

$$\alpha_1 V_{in} \rightarrow \alpha_1 A_1 \sin(\omega_1 t) + \alpha_1 A_2 \sin(\omega_2 t)$$

$$\alpha_2 V_{in}^2 \rightarrow \alpha_2 A_1^2 \sin^2(\omega_1 t) + \alpha_2 A_2^2 \sin^2(\omega_2 t) + 2\alpha_2 A_1 A_2 \sin(\omega_1 t) \sin(\omega_2 t) + \dots$$

$$\rightarrow \frac{\alpha_2 A_1^2}{2} (1 - \cos(2\omega_1 t)) + \frac{\alpha_2 A_2^2}{2} (1 - \cos(2\omega_2 t))$$

$$+ \alpha_2 A_1 A_2 [\cos((\omega_1 - \omega_2)t) - \cos((\omega_1 + \omega_2)t)]$$

$$\alpha_3 V_{in}^3 \rightarrow \alpha_3 A_1^3 \sin^3(\omega_1 t) + \alpha_3 A_2^3 \sin^3(\omega_2 t)$$

$$+ 3\alpha_3 A_1^2 A_2 \sin(\omega_1 t)^2 \sin(\omega_2 t) + 3\alpha_3 A_2^2 A_1 \sin(\omega_2 t)^2 \sin(\omega_1 t)$$


$$+ \frac{3\alpha_3 A_1^2 A_2}{4} [\sin(2\omega_1 + \omega_2)t - \sin(2\omega_1 - \omega_2)t]$$

Effect of Component Non-Linearities on Overall Filter Linearity Intermodulation Distortion

Real DC transfer characteristics, input 2 sin waves:

$$V_{out} = \alpha_1 V_{in} + \alpha_2 V_{in}^2 + \alpha_3 V_{in}^3 + \dots$$
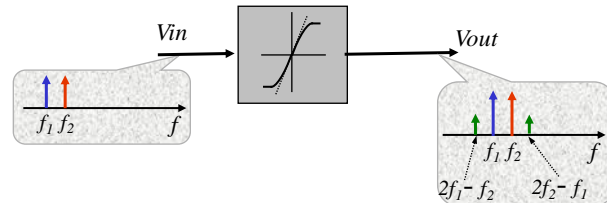
$$\text{If } V_{in} = A_1 \sin(\omega_1 t) + A_2 \sin(\omega_2 t)$$



For f_1 & f_2 close in frequency \rightarrow Components associated with $(2f_1 - f_2)$ & $(2f_2 - f_1)$ are the closest to the fundamental signals on the frequency axis and thus most harmful

Effect of Component Non-Linearities on Overall Filter Linearity Intermodulation Distortion

Intermodulation distortion is measured in terms of IM2 and IM3:

Typically for input two sinusoids with equal amplitude ($A_1 = A_2 = A$)


$$IM2 = \frac{\text{amplitude } 2^{nd} \text{ IM component}}{\text{amplitude fundamental}}$$

$$IM3 = \frac{\text{amplitude } 3^{rd} \text{ IM component}}{\text{amplitude fundamental}}$$

$$IM2 = \frac{\alpha_2}{\alpha_1} A + \dots \quad IM3 = \frac{3}{4} \frac{\alpha_3}{\alpha_1} A^2 + \frac{25}{8} \frac{\alpha_5}{\alpha_1} A^4 + \dots$$


Wireless Communications Measure of Linearity

1dB Compression Point

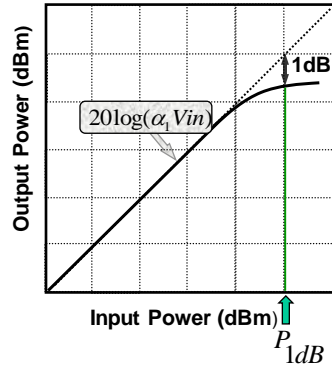

$$V_{out} = \alpha_1 V_{in} + \alpha_2 V_{in}^2 + \alpha_3 V_{in}^3 + \dots$$

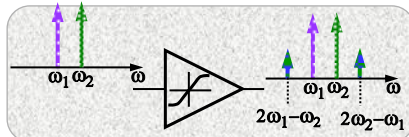Wireless Communications Measure of Linearity Third Order Intercept Point



$$V_{out} = \alpha_1 V_{in} + \alpha_2 V_{in}^2 + \alpha_3 V_{in}^3 + \dots$$


$$\begin{aligned} IM_3 &= \frac{3rd}{1st} \\ &= \frac{3}{4} \frac{\alpha_3}{\alpha_1} V_{in}^2 + \frac{25}{8} \frac{\alpha_5}{\alpha_1} V_{in}^4 + \dots \\ &= 1 @ IIP3 \end{aligned}$$

Typically:

$$IIP_3 - P_{1dB} = 9.6dB$$


Most common measure of linearity for wireless circuits:

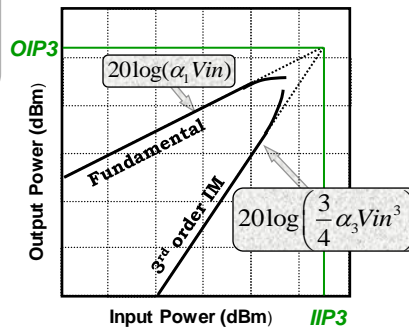→ OIP3 & IIP3, Third order output/input intercept point




Example: Significance of Filter Intermodulation Distortion in Wireless Systems

- Typical wireless receiver architecture

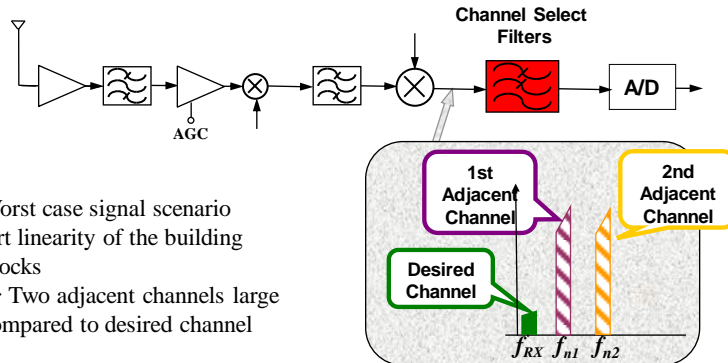


Worst case signal scenario
wrt linearity of the building
blocks
→ Two adjacent channels large
compared to desired channel

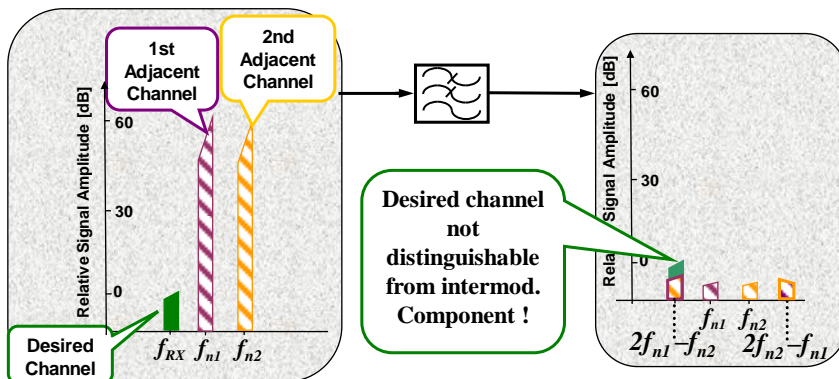Example: Significance of Filter Intermodulation Distortion in Wireless Systems



- Adjacent channels can be as much as 60dB higher compared to the desired RX signal!
- Notice that in this example, 3rd order intermodulation component associated with the two adjacent channel, falls on the desired channel signal!

Filter Linearity

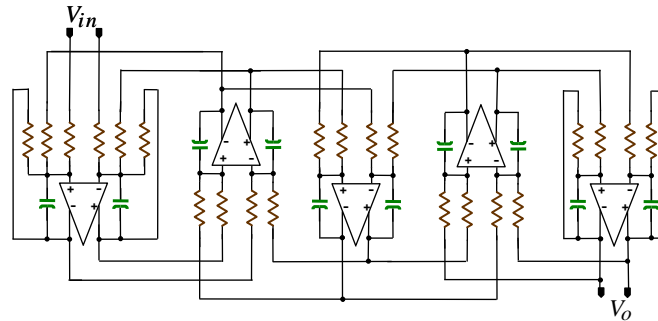


- Maximum signal handling capability is usually determined by the specifications wrt harmonic distortion and /or intermodulation distortion
Distortion in a filter is a function of linearity of the components
- Example: In the above circuit linearity of the filter is mainly a function of linearity of the *opamp* voltage transfer characteristics

Various Types of Integrator Based Filter


- Continuous Time
 - Resistive element based
 - Opamp-RC
 - Opamp-MOSFET-C
 - Opamp-MOSFET-RC
 - Transconductance (G_m) based
 - G_m -C
 - Opamp- G_m -C
- Sampled Data
 - Switched-capacitor Integrator

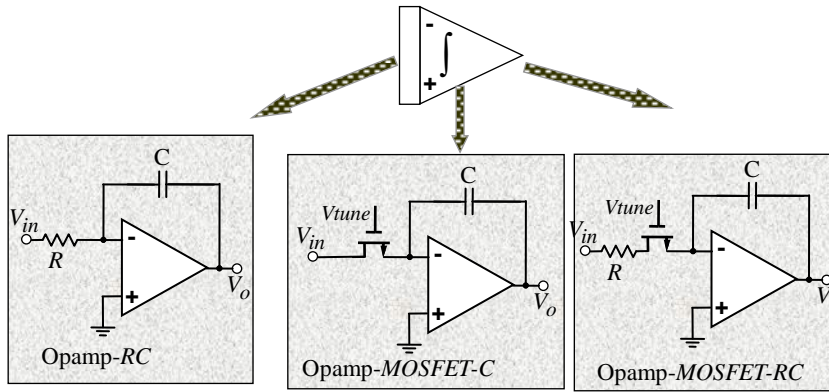Continuous-Time Resistive Element Type Integrators Opamp-RC & Opamp-MOSFET-C & Opamp-MOSFET-RC




Ideal transfer function: $\frac{V_o}{V_{in}} = \frac{-\omega_o}{s}$ where $\omega_o = \frac{1}{R_{eq}C}$

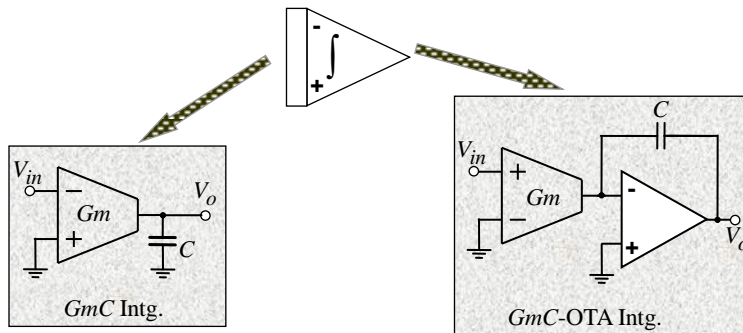Continuous-Time Transconductance Type Integrator Gm-C & Opamp-Gm-C



Ideal transfer function: $\frac{V_o}{V_{in}} = \frac{-\omega_o}{s}$ where $\omega_o = \frac{G_m}{C}$

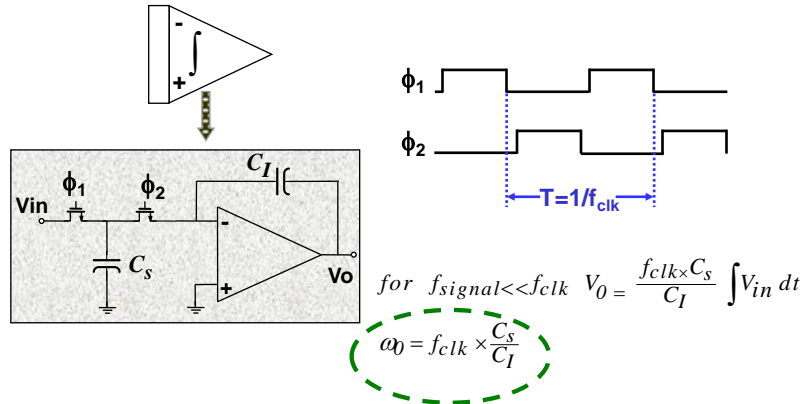Integrator Implementation Switched-Capacitor



Main advantage: Critical frequency function of *ratio* of caps & clock freq.
 → Critical filter frequencies (e.g. LPF -3dB freq.) very accurate


Few Facts About Monolithic R_s & C_s & G_m s

- Monolithic continuous-time filter critical frequency set by $R \times C$ or C/G_m
 - Absolute value of integrated R_s & C_s & G_m s are quite variable
 - R_s vary due to doping and etching non-uniformities
 - Could vary by as much as $\sim +20$ to 40% due to process & temperature variations
 - C_s vary because of oxide thickness variations and etching inaccuracies
 - Could vary $\sim +10$ to 15%
 - G_m s typically function of mobility, oxide thickness, current, device geometry ...
 - Could vary $> \sim +40\%$ or more with process & temp. & supply voltage
- Integrated continuous-time filter critical frequency could vary by over $+50\%$

Few Facts About Monolithic Rs & Cs

- While absolute value of monolithic R_s & C_s and g_m s are quite variable, with special attention paid to layout, C & R & g_m s quite well-matched
 - Ratios very accurate and stable over processing, temperature, and time
- With special attention to layout (e.g. interleaving, use of dummy devices, common-centroid geometries...):
 - Capacitor mismatch $\ll 0.1\%$
 - Resistor mismatch $< 0.1\%$
 - G_m mismatch $< 0.5\%$

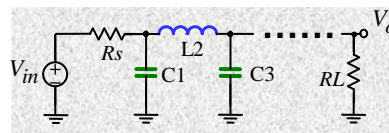Impact of Component Variations on Filter Characteristics



RLC Filters

Facts about RLC filters

- ω_{-3dB} determined by absolute value of L_s & C_s
- Shape of filter depends on ratios of normalized L & C


$$C_1^{RLC} = C_r \times C_1^{Norm} = \frac{C_1^{Norm}}{R^* \times \omega_{-3dB}}$$

$$L_2^{RLC} = L_r \times L_2^{Norm} = \frac{L_2^{Norm} \times R^*}{\omega_{-3dB}}$$

Effect of Monolithic R & C Variations on Filter Characteristics

- Filter shape (whether Elliptic with 0.1dB Rpass or Butterworth..etc) is a function of *ratio* of *normalized Ls & Cs* in RLC filters
 - Critical frequency (e.g. ω_{-3dB}) function of *absolute value* of *Ls xCs*
 - Absolute value of integrated *Rs & Cs & Gms* are quite variable
 - *Ratios* very accurate and stable over time and temperature
- What is the effect of on-chip component variations on monolithic filter frequency characteristics?

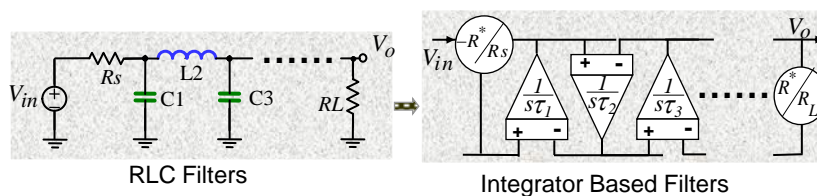Impact of Process Variations on Filter Characteristics




$$\tau_1 = C_1^{RLC} R^* = \frac{C_1^{Norm}}{\omega_{-3dB}}$$

$$\tau_2 = \frac{L_2^{RLC}}{R^*} = \frac{L_2^{Norm}}{\omega_{-3dB}}$$

$$\frac{\tau_1}{\tau_2} = \frac{C_1^{Norm}}{L_2^{Norm}}$$

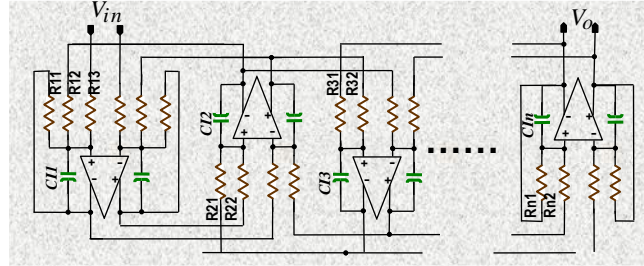Impact of Process Variations on Filter Characteristics



$$\tau_1^{intg} = C_{I1} \cdot R_1 = \frac{C_1^{Norm}}{\omega_{-3dB}}$$


$$\tau_2^{intg} = C_{I2} \cdot R_2 = \frac{L_2^{Norm}}{\omega_{-3dB}}$$

$$\frac{\tau_1^{intg}}{\tau_2^{intg}} = \frac{C_{I1} \cdot R_1}{C_{I2} \cdot R_2} = \frac{C_1^{Norm}}{L_2^{Norm}}$$

Variation in absolute value of integrated
 \rightarrow Rs & Cs \rightarrow change in critical freq. (ω_{-3dB})

Since ratios of Rs & Cs very accurate
 \rightarrow Continuous-time monolithic filters retain their shape due to good component matching even with variability in absolute component values

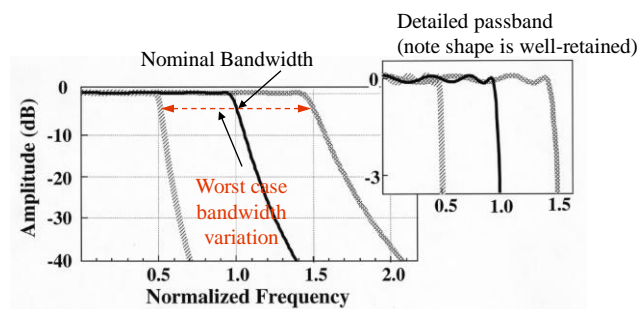
Example: LPF Worst Case Corner Frequency Variations



- While absolute value of on-chip RC (gm-C) time-constants could vary by as much as 100% (process & temp.)
- With proper precautions, excellent component matching can be achieved:
 - \rightarrow Well-preserved relative amplitude & phase vs freq. characteristics
 - \rightarrow Need to only adjust (tune) continuous-time filter critical frequencies

Tunable Opamp-RC Filters Example

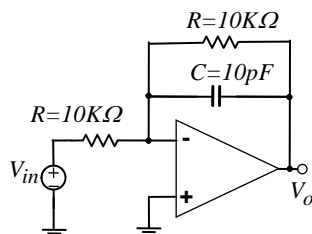- 1st order Opamp-RC filter is designed to have a corner frequency of 1.6MHz
- Assuming process variations of:
 - C varies by $\pm 10\%$
 - R varies by $\pm 25\%$
- Build the filter in such a way that the corner frequency can be adjusted post-manufacturing.



*Nominal R & C values
for 1.6MHz corner frequency*

Filter Corner Frequency Variations

- Assuming expected process variations of:
 - Maximum C variations by $\pm 10\%$
 $C_{\text{nom}}=10\text{pF} \rightarrow C_{\text{min}}=9\text{pF}, C_{\text{max}}=11\text{pF}$
 - Maximum R variations by $\pm 25\%$
 $R_{\text{nom}}=10\text{K} \rightarrow R_{\text{min}}=7.5\text{K}, R_{\text{max}}=12.5\text{K}$
 - Corner frequency ranges from
 $\rightarrow 2.357\text{MHz}$ to 1.157MHz

 \rightarrow Corner frequency varies by $+48\%$ & -27%

Variable Resistor or Capacitor

- In order to make provisions for filter to be tunable either R or C should be made adjustable (this example → adjustable R)
- Monolithic Rs can only be made adjustable in discrete steps (not continuous)

$$\frac{R_{nom}^{max}}{R_{nom}} = \frac{f_{max}}{f_{nom}} = 1.48$$


$$R_{nom} \quad f_{nom}$$

$$\rightarrow R_{nom}^{max} = 14.8k\Omega$$

$$\frac{R_{nom}^{min}}{R_{nom}} = \frac{f_{min}}{f_{nom}} = 0.72$$

$$R_{nom} \quad f_{nom}$$
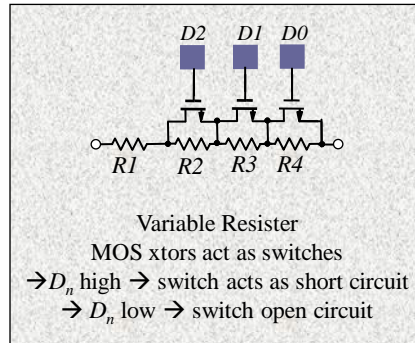
$$\rightarrow R_{nom}^{min} = 7.2k\Omega$$



Tunable Resistor

- Maximum C variations by +-10% → C_{min}=9pF, C_{max}=11pF
- Maximum R variations by +-25% → R_{min}=7.5K, R_{max}=12.5K
→ Corner frequency varies by +48% & -27.%
- Assuming control signal has $n = 3$ bit (0 or 1) for adjustment → R₂=2R₃=4R₄


$$R_1 = R_{nom}^{min} = 7.2k\Omega$$

$$R_2 = (R_{nom}^{max} - R_{nom}^{min}) \times \frac{2^{n-1}}{2^n - 1} = (14.8k - 7.2k) \frac{4}{7} = 4.34k\Omega$$

$$R_3 = (R_{nom}^{max} - R_{nom}^{min}) \times \frac{2^{n-2}}{2^n - 1} = (14.8k - 7.2k) \frac{2}{7} = 2.17k\Omega$$

$$R_4 = (R_{nom}^{max} - R_{nom}^{min}) \times \frac{2^{n-3}}{2^n - 1} = (14.8k - 7.2k) \frac{1}{7} = 1.08k\Omega$$
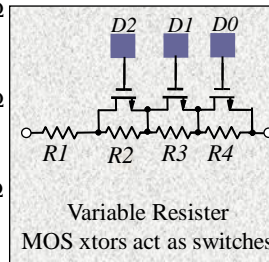
$$\text{Tuning resolution} \approx 1.08k/10k \approx 10\%$$




Tunable Opamp-RC Filter

D2	D1	D0	Rnom
1	1	1	7.2K
1	1	0	8.28K
1	0	1	9.37K
0	0	0	14.8K


Post manufacturing:

- Set all Dx to 100 (mid point)
- Measure -3dB frequency
 - If frequency too high decrement D to D-1
 - If frequency too low increment D to D+1
 - If frequency within 10% of the desired corner frequency → stop
 - else

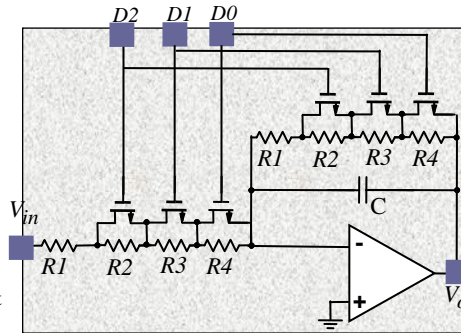For higher order filters, all filter integrators tuned simultaneously




Tunable Opamp-RC Filters Summary

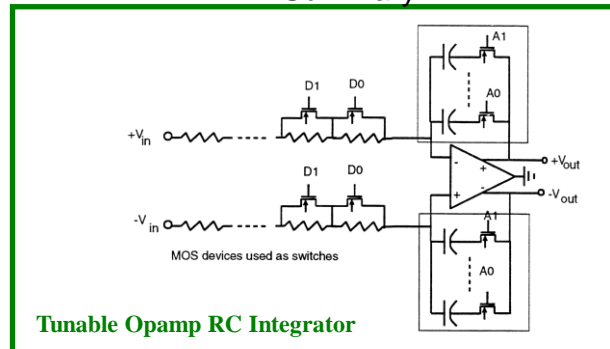


- Program Cs and/or Rs to freq. tune the filter
- All filter integrators tuned simultaneously
- Tuning in discrete steps & not continuous
- Tuning resolution limited
- Switch parasitic C & series R can affect the freq. response of the filter

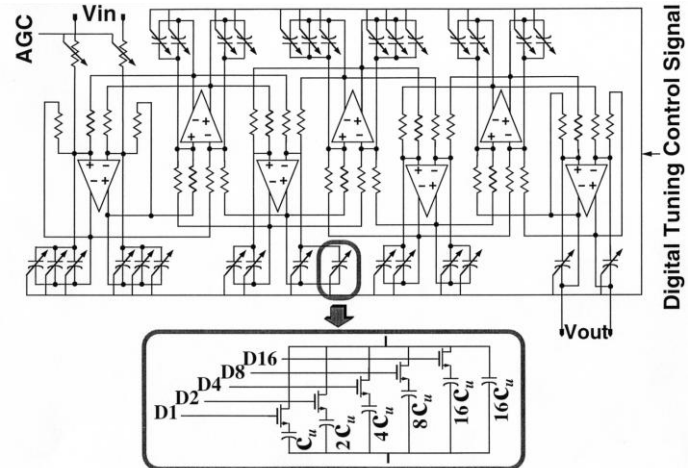Example: Tunable Low-Pass Opamp-RC Filter Adjustable Capacitors




Opamp RC Filters

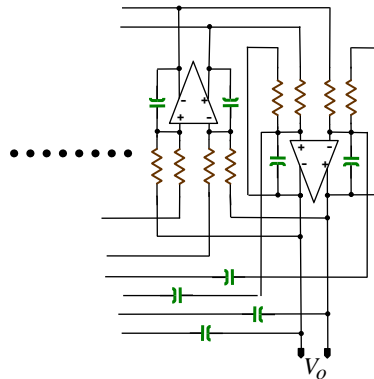- Advantages
 - Since resistors are quite linear, linearity only a function of opamp linearity
 - good linearity
- Disadvantages
 - Opamps have to drive resistive load, low output impedance is required
 - High power consumption
 - Continuous tuning not possible-tuning only in discrete steps
 - Tuning requires programmable R_s and/or C_s




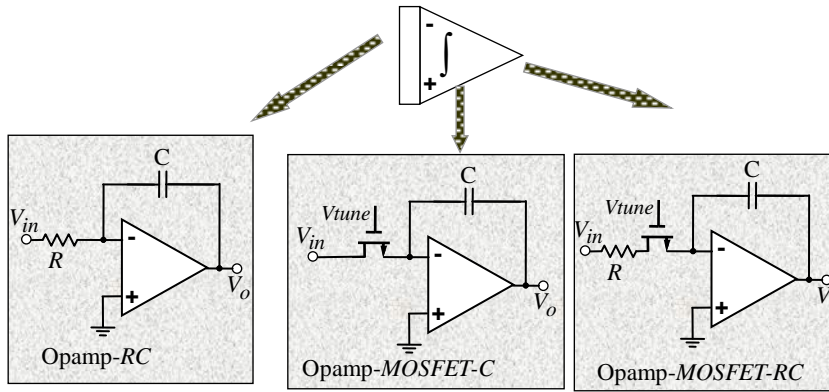Integrator Implementation Opamp-RC & Opamp-MOSFET-C & Opamp-MOSFET-RC




$$\frac{V_o}{V_{in}} = \frac{-\omega_o}{s} \quad \text{where} \quad \omega_o = \frac{1}{R_{eq}C}$$

Use of MOSFETs as Variable Resistors

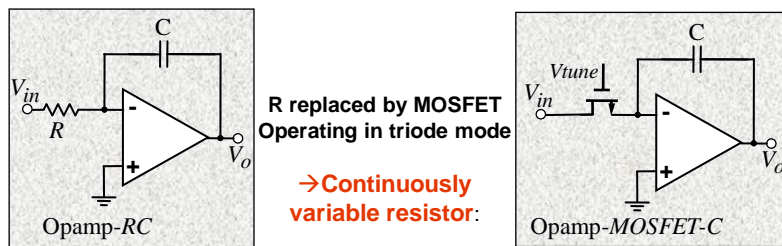

MOSFET IV characteristic:

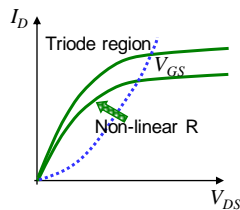


Opamp MOSFET-C Integrator Single-Ended Integrator

$$I_D = \mu C_{ox} \frac{W}{L} \left[(V_{gs} - V_{th}) V_{ds} - \frac{V_{ds}^2}{2} \right]$$

$$I_D = \mu C_{ox} \frac{W}{L} \left[(V_{gs} - V_{th}) V_i - \frac{V_i^2}{2} \right]$$
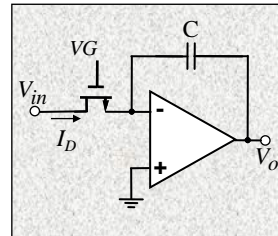
$$G = \frac{\partial I_D}{\partial V_i} = \mu C_{ox} \frac{W}{L} (V_{gs} - V_{th} - V_i)$$



→ Tunable by varying VG:

By varying VG effective admittance is tuned
→ Tunable integrator time constant

Problem: Single-ended MOSFET-C Integrator → Effective R non-linear
Note that the non-linearity is mainly 2nd order type

Use of MOSFETs as Resistors Differential Integrator


$$I_D = \mu C_{ox} \frac{W}{L} \left(V_{gs} - V_{th} - \frac{V_{ds}}{2} \right) V_{ds}$$

$$I_{D1} = \mu C_{ox} \frac{W}{L} \left(V_{gs} - V_{th} - \frac{V_i}{4} \right) \frac{V_i}{2}$$

$$I_{D2} = -\mu C_{ox} \frac{W}{L} \left(V_{gs} - V_{th} + \frac{V_i}{4} \right) \frac{V_i}{2}$$

$$I_{D1} - I_{D2} = \mu C_{ox} \frac{W}{L} (V_{gs} - V_{th}) V_i$$
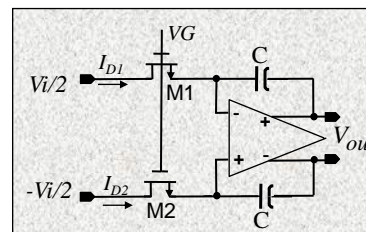
$$G = \frac{\partial (I_{D1} - I_{D2})}{\partial V_i} = \mu C_{ox} \frac{W}{L} (V_{gs} - V_{th})$$




Opamp-MOSFET-C

- Non-linear term is of even order & cancelled!
- Admittance independent of Vi

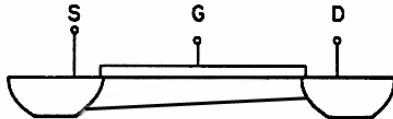
Problem: Threshold voltage dependence

Use of MOSFET as Resistor Issues

MOS xtor operating in triode region
Cross section view



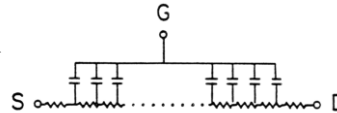
Distributed channel resistance &
gate capacitance




- Distributed nature of gate capacitance & channel resistance results in infinite no. of high-frequency poles:
 - Excess phase @ the unity-gain frequency of the integrator
 - Enhanced integrator Q
 - Enhanced filter Q,
 - Peaking in the filter passband

Use of MOSFET as Resistor Issues

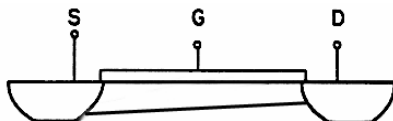MOS xtor operating in triode region
Cross section view



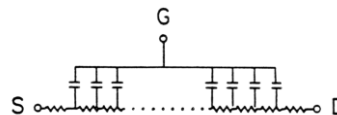
Distributed channel resistance &
gate capacitance



- Tradeoffs affecting the choice of device channel length:
 - Filter performance mandates well-matched MOSFETs → long channel devices desirable
 - Excess phase increases with L^2 → Q enhancement and potential for oscillation!
 - Tradeoff between device matching and integrator Q
 - This type of filter limited to low frequencies

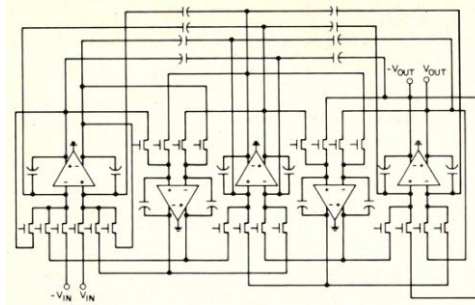Example: Opamp MOSFET-C Filter

- Suitable for low frequency applications
- Issues with linearity
- Linearity achieved ~40-50dB
- Needs tuning
- Continuously tunable



5th Order Elliptic MOSFET-C LPF
with 4kHz Bandwidth

Ref: Y. Tsvividis, M.Banu, and J. Khoury, "Continuous-Time MOSFET-C Filters in VLSI", *IEEE Journal of Solid State Circuits* Vol. SC-21, No.1 Feb. 1986, pp. 15-30

Improved MOSFET-C Integrator

$$I_D = \mu C_{ox} \frac{W}{L} \left(V_{gs} - V_{th} - \frac{V_{ds}}{2} \right) V_{ds}$$

$$I_{D1} = \mu C_{ox} \frac{W}{L} \left(V_{gs1} - V_{th} - \frac{V_i}{4} \right) \frac{V_i}{2}$$

$$I_{D3} = -\mu C_{ox} \frac{W}{L} \left(V_{gs3} - V_{th} + \frac{V_i}{4} \right) \frac{V_i}{2}$$

$$I_{X1} = I_{D1} + I_{D3}$$

$$= \mu C_{ox} \frac{W}{L} \left(V_{gs1} - V_{gs3} - \frac{V_i}{2} \right) \frac{V_i}{2}$$

$$I_{X2} = \mu C_{ox} \frac{W}{L} \left(V_{gs3} - V_{gs1} - \frac{V_i}{2} \right) \frac{V_i}{2}$$


$$I_{X1} - I_{X2} = \mu C_{ox} \frac{W}{L} (V_{gs1} - V_{gs3}) V_i$$

$$G = \frac{\partial (I_{X1} - I_{X2})}{\partial V_i} = \mu C_{ox} \frac{W}{L} (V_{gs1} - V_{gs3})$$

No threshold voltage dependence


Linearity achieved in the order of 50-70dB

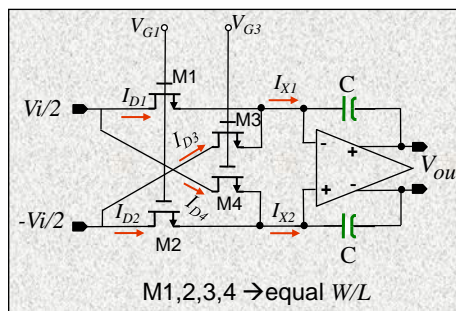Ref: Z. Czarnul, "Modification of the Banu-Tsvividis Continuous-Time Integrator Structure," *IEEE Transactions on Circuits and Systems*, Vol. CAS-33, No. 7, pp. 714-716, July 1986.



M1,2,3,4 → equal W/L


R-MOSFET-C Integrator

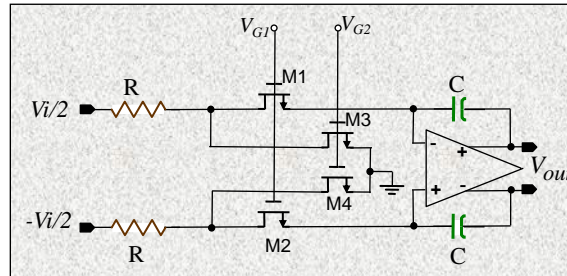

- Improvement over MOSFET-C by adding resistor in series with MOSFET
- Voltage drop primarily across fixed resistor \rightarrow small MOSFET V_{ds} \rightarrow improved linearity & reduced tuning range
- Generally low frequency applications

Ref: U-K Moon, and B-S Song, "Design of a Low-Distortion 22-kHz Fifth Order Bessel Filter," *IEEE Journal of Solid State Circuits*, Vol. 28, No. 12, pp. 1254-1264, Dec. 1993.


R-MOSFET-C Lossy Integrator

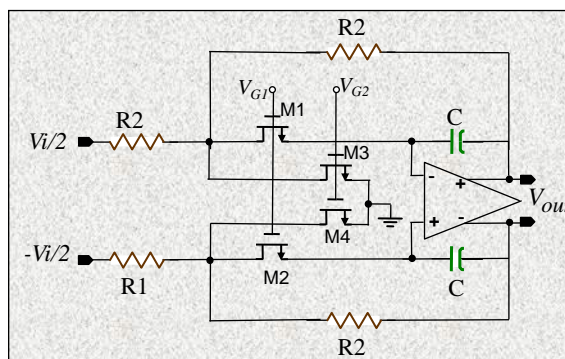

- Negative feedback around the non-linear MOSFETs improves linearity but compromises frequency response accuracy

Ref: U-K Moon, and B-S Song, "Design of a Low-Distortion 22-kHz Fifth Order Bessel Filter," *IEEE Journal of Solid State Circuits*, Vol. 28, No. 12, pp. 1254-1264, Dec. 1993.

Example: Opamp MOSFET-RC Filter

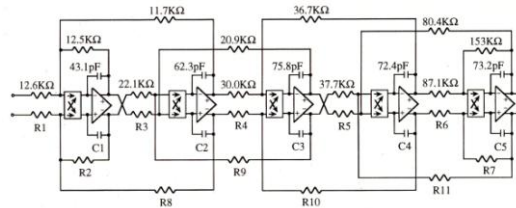


**5th Order Bessel MOSFET-RC LPF 22kHz bandwidth
THD \rightarrow -90dB for 4Vp-p, 2kHz input signal**

- Suitable for low frequency, low Q applications
- Significant improvement in linearity compared to MOSFET-C
- Needs tuning

Ref: U-K Moon, and B-S Song, "Design of a Low-Distortion 22-kHz Fifth Order Bessel Filter," *IEEE Journal of Solid State Circuits*, Vol. 28, No. 12, pp. 1254-1264, Dec. 1993.


Operational Amplifiers (Opamps) versus Operational Transconductance Amplifiers (OTA)

Opamp
Voltage controlled
voltage source

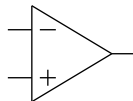


- Output in the form of voltage
- Low output impedance
- Can drive R-loads
- Good for RC filters, OK for SC filters
- Extra buffer adds complexity, power dissipation

OTA
Voltage controlled
current source

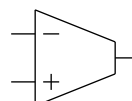

- Output in the form of current
- High output impedance
- In the context of filter design called *gm-cells*
- Cannot drive R-loads
- Good for SC & gm-C filters
- Typically, less complex compared to opamp \rightarrow higher freq. potential
- Typically lower power

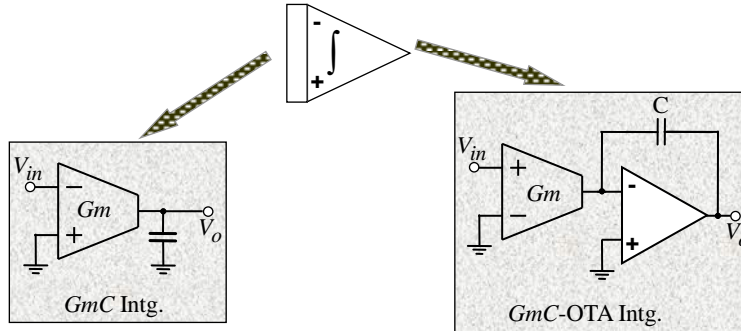Integrator Implementation Transconductance-C & Opamp-Transconductance-C




$$\frac{V_o}{V_{in}} = \frac{-\omega_o}{s} \quad \text{where} \quad \omega_o = \frac{G_m}{C}$$

Gm-C Filters Simplest Form of CMOS Gm-C Integrator


- Transconductance element formed by the source-coupled pair *M1* & *M2*
- All MOSFETs operating in saturation region
- Current in *M1* & *M2* can be varied by changing $V_{control}$

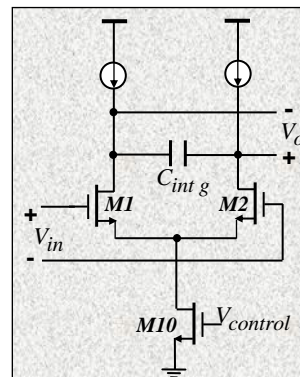→ Transconductance of *M1* & *M2* varied through $V_{control}$



Ref: H. Khorramabadi and P.R. Gray, "High Frequency CMOS continuous-time filters," IEEE Journal of Solid-State Circuits, Vol.-SC-19, No. 6, pp.939-948, Dec. 1984.

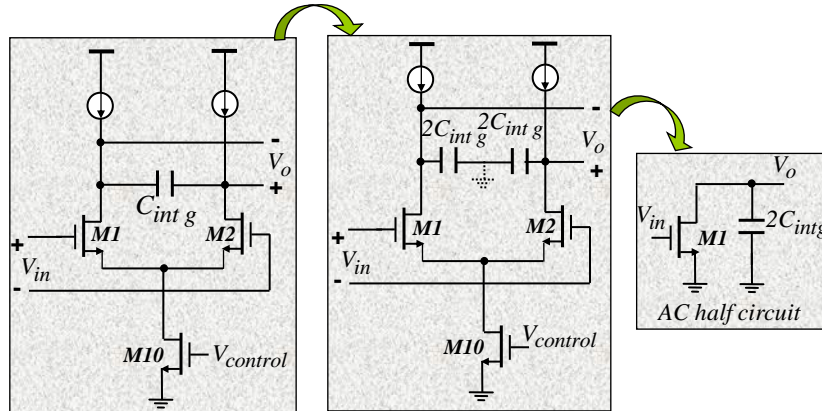Simplest Form of CMOS Gm-C Integrator AC Half Circuit



Gm-C Filters Simplest Form of CMOS Gm-C Integrator



- Use ac half circuit & small signal model to derive transfer function:

$$V_o = -g_m^{M1,2} \times V_{in} \times 2C_{intg} g s$$

$$\frac{V_o}{V_{in}} = -\frac{g_m^{M1,2}}{2C_{intg} g s}$$

$$\frac{V_o}{V_{in}} = \frac{-\omega_o}{s}$$
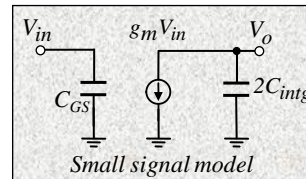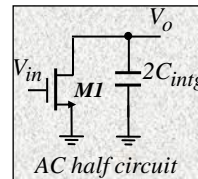
$$\rightarrow \omega_o = \frac{g_m^{M1,2}}{2 \times C_{intg} g}$$



Gm-C Filters

Simplest Form of CMOS Gm-C Integrator

- MOSFET in saturation region:

$$I_d = \frac{\mu C_{ox} W}{2 L} (V_{gs} - V_{th})^2$$

- Gm is given by:


$$g_m^{M1 \& M2} = \frac{\partial I_d}{\partial V_{gs}} = \mu C_{ox} \frac{W}{L} (V_{gs} - V_{th})$$

$$= 2 \frac{I_d}{(V_{gs} - V_{th})}$$

$$= 2 \left(\frac{1}{2} \mu C_{ox} \frac{W}{L} I_d \right)^{1/2}$$

I_d varied via V_{control}


→ g_m tunable via V_{control}

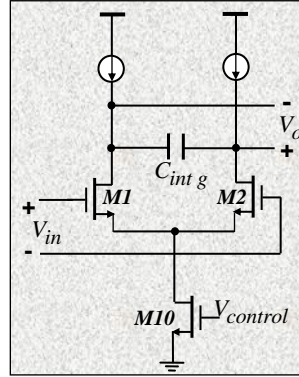


Gm-C Filters

2nd Order Gm-C Filter

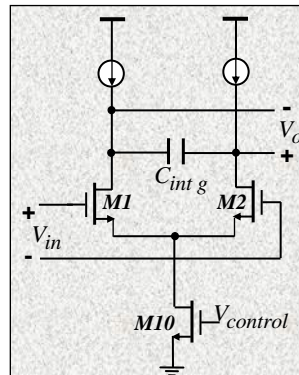- Use the Gm-cell to build a 2nd order bandpass filter



2nd Order Bandpass Filter

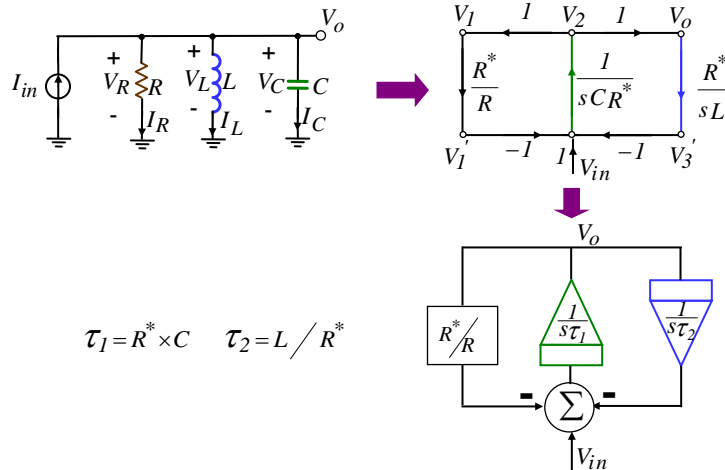

2nd Order Integrator-Based Bandpass Filter

$$\frac{V_{BP}}{V_{in}} = \frac{\tau_2 s}{\tau_1 \tau_2 s^2 + \beta \tau_2 s + 1}$$

$$\tau_1 = R^* \times C \quad \tau_2 = L / R^*$$


$$\beta = R^* / R$$

$$\omega_0 = 1 / \sqrt{\tau_1 \tau_2} = 1 / \sqrt{L C}$$

$$Q = 1 / \beta \times \sqrt{\tau_1 / \tau_2}$$

From matching point of view desirable:

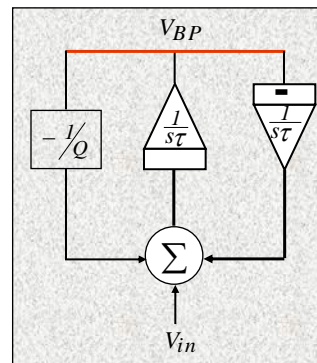
$$\tau_1 = \tau_2 = \tau \rightarrow Q = R / R^*$$





2nd Order Integrator-Based Bandpass Filter

First implement this part
With transfer function:


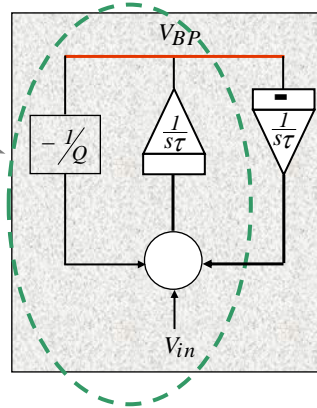
$$\frac{V_0}{V_{in}} = \frac{-1}{\frac{s}{\omega_0} + \frac{1}{Q}}$$



Terminated Gm-C Integrator

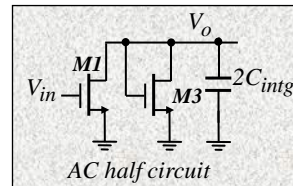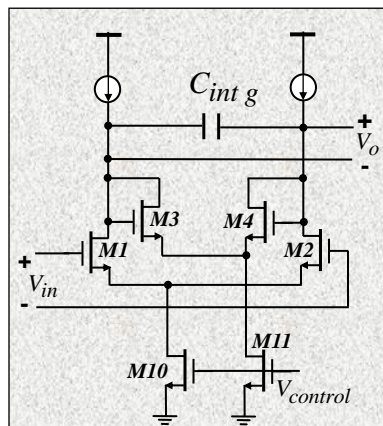



Terminated Gm-C Integrator

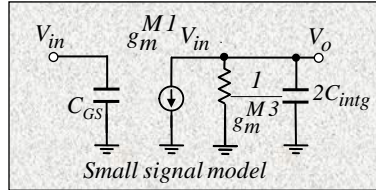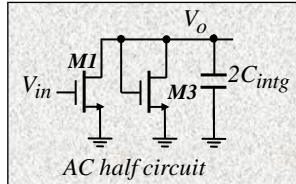

$$\frac{V_o}{V_{in}} = \frac{-I}{s \frac{2C_{int} g}{M1} + \frac{g_m M^3}{M1}}$$

Compare to: $\frac{V_0}{V_{in}} = \frac{-I}{\frac{s}{\omega_0} + \frac{1}{Q}}$

Terminated Gm-C Integrator

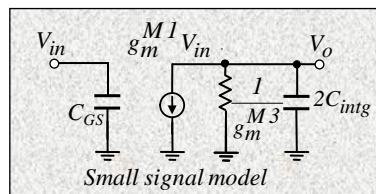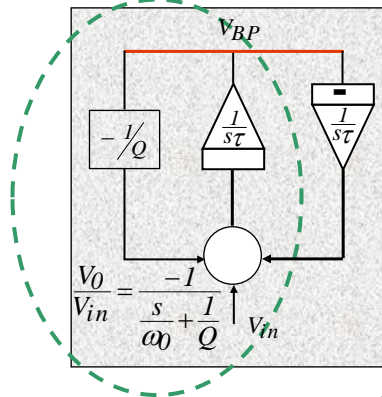

$$\frac{V_o}{V_{in}} = \frac{-I}{s \times 2C_{int} g + \frac{g_m M^3}{M1}}$$

$$\rightarrow \omega_0 = \frac{g_m M1}{2C_{int} g} \quad \& \quad Q = \frac{g_m M1}{g_m M^3}$$

Question: How to define Q accurately?


Terminated Gm-C Integrator

$$g_m^{M1} = 2 \left(\frac{1}{2} \mu C_{ox} \frac{W_{M1}}{L_{M1}} I_d^{M1} \right)^{1/2}$$

$$g_m^{M3} = 2 \left(\frac{1}{2} \mu C_{ox} \frac{W_{M3}}{L_{M3}} I_d^{M3} \right)^{1/2}$$

Let us assume equal channel lengths for M1, M3 then:
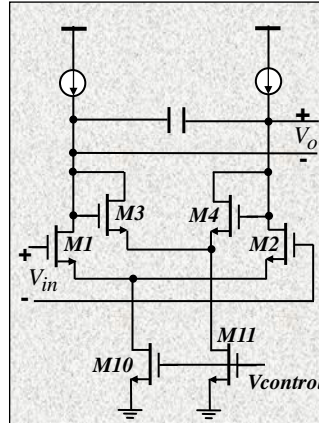
$$\frac{g_m^{M1}}{g_m^{M3}} = \left(\frac{I_d^{M1}}{I_d^{M3}} \times \frac{W_{M1}}{W_{M3}} \right)^{1/2}$$



Terminated Gm-C Integrator


Note that:

$$\frac{I_d^{M1}}{I_d^{M3}} = \frac{I_d^{M10}}{I_d^{M11}}$$


Assuming equal channel lengths for M10, M11:

$$\frac{I_d^{M10}}{I_d^{M11}} = \frac{W_{M10}}{W_{M11}}$$
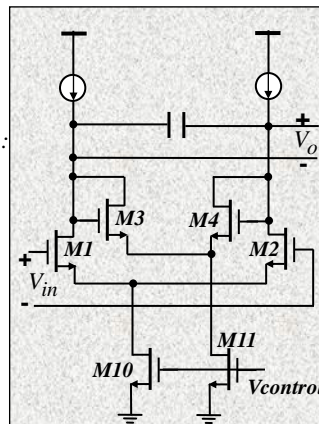
$$\rightarrow \frac{g_m^{M1}}{g_m^{M3}} = \left(\frac{W_{M10}}{W_{M11}} \times \frac{W_{M1}}{W_{M3}} \right)^{1/2}$$



2nd Order Gm-C Filter

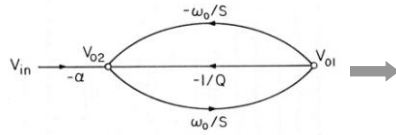

- Simple design
- Tunable
- Q function of device ratios:

$$Q = \frac{g_{m1,2}}{g_{m3,4}}$$

