

EE247 Lecture 9

- **Switched-capacitor filters**
 - Introduction to S.C. filters
 - Issue of aliasing mandating use of anti-aliasing prefilters
 - Example of anti-aliasing prefilter for S.C. filters
 - Switched-capacitor network electronic noise
 - Switched-capacitor integrators
 - DDI integrators
 - LDI integrators

EE247 Summary of Last Lecture

- **Continuous-time filter design considerations**
 - Monolithic highpass filters
 - Active bandpass filter design
 - Lowpass to bandpass transformation
 - Example: 6th order bandpass filter
 - Gm-C bandpass filter using simple diff. pair
 - Various Gm-C filter implementations
- **Performance comparison of various continuous-time filter topologies**
- **Introduction to switched-capacitor filters**

Switched-Capacitor Resistors

$$i = f_s C (v_{IN} - v_{OUT})$$

With the current through the switched-capacitor resistor proportional to the voltage across it, the equivalent “switched capacitor resistance” is:


$$R_{eq} = \frac{v_{IN} - v_{OUT}}{i} = \frac{1}{f_s C}$$

Example:

$$f_s = 100 \text{ KHz}, C = 0.1 \text{ pF}$$

$$\rightarrow R_{eq} = 100 \text{ Mega}\Omega$$

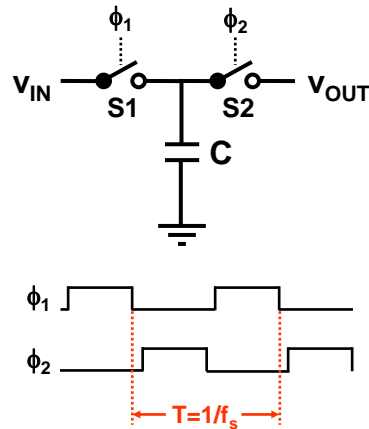Note: Can build large time-constant in small area




Switched-Capacitor Filter



- Let's build a “switched-capacitor” filter ...
- Start with a simple RC LPF
- Replace the physical resistor by an equivalent switched-capacitor resistor
- 3-dB bandwidth:

$$\omega_{-3dB} = \frac{1}{R_{eq} C_2} = f_s \times \frac{C_1}{C_2}$$
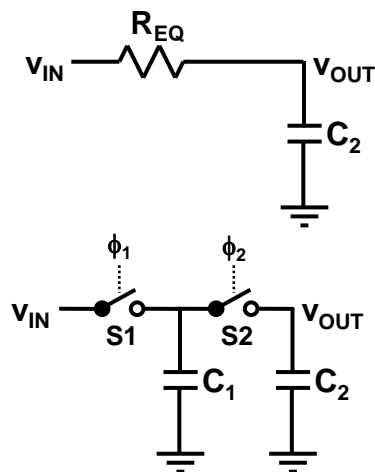
$$f_{-3dB} = \frac{1}{2\pi} f_s \times \frac{C_1}{C_2}$$




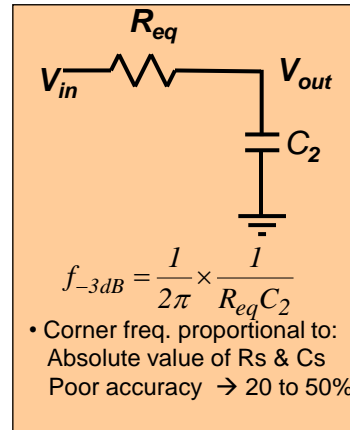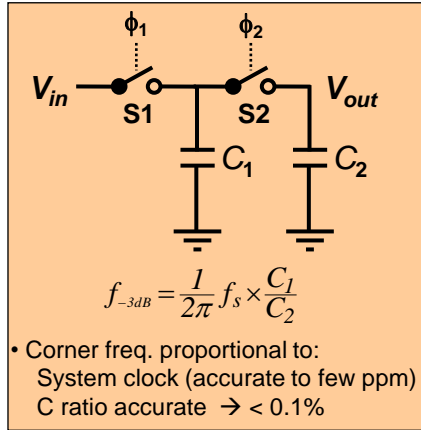Switched-Capacitor Filter Advantage versus Continuous-Time Filter



➔ **Main advantage of SC filters \rightarrow inherent critical frequency accuracy**

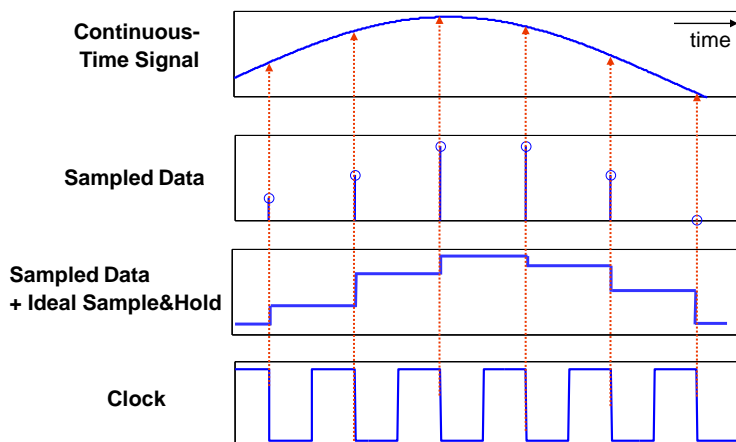Typical Sampling Process Continuous-Time(CT) \Rightarrow Sampled Data (SD)




Uniform Sampling


Nomenclature:

Continuous time signal $x_c(t)$
 Sampling interval T
 Sampling frequency $f_s = 1/T$
 Sampled signal $x_d(kT) = x(k)$

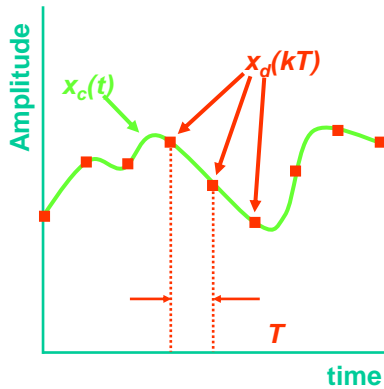- Samples are the waveform values at kT instances and undefined in between
- Problem: Multiple continuous time signals can yield exactly the same discrete time signal
- Let's examine samples taken at $1\mu\text{s}$ intervals of several sinusoidal waveforms ...



Sampling Sine Waves

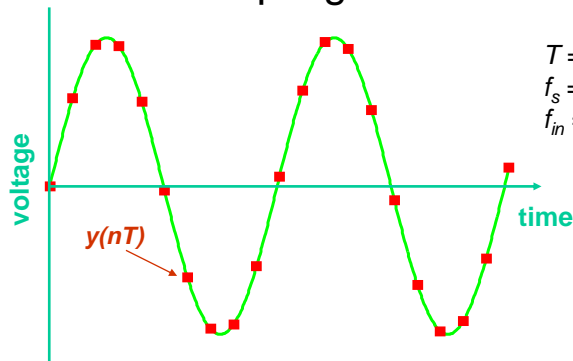


$T = 1\mu\text{s}$
 $f_s = 1/T = 1\text{MHz}$
 $f_{in} = 101\text{kHz}$

$$v(t) = \cos(2\pi \cdot f_{in} \cdot t)$$

Sampled-data domain $\rightarrow t \rightarrow n \cdot T$ or $t \rightarrow n/f_s$ (n integer)

$$v(n) = \cos\left(2\pi \cdot \frac{f_{in}}{f_s} \cdot n\right) = \cos\left(2\pi \cdot \frac{101\text{kHz}}{1\text{MHz}} \cdot n\right)$$

Sampling Sine Waves Aliasing

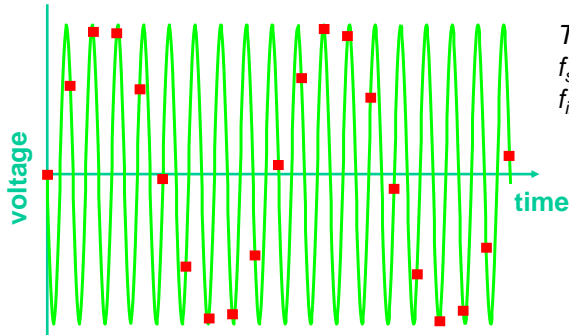


$$\begin{aligned} T &= 1\mu\text{s} \\ f_s &= 1/T = 1\text{MHz} \\ f_{in} &= 899\text{kHz} \end{aligned}$$

$$v(n) = \cos\left(2\pi \frac{899\text{kHz}}{1\text{MHz}} n\right) = \cos\left(2\pi \frac{(1000\text{kHz} - 101\text{kHz})}{1\text{MHz}} n\right) = \cos\left(2\pi - 2\pi \frac{101\text{kHz}}{1\text{MHz}} n\right)$$

$$= \cos\left(2\pi \frac{101\text{kHz}}{1\text{MHz}} n\right)$$

Sampling Sine Waves Aliasing

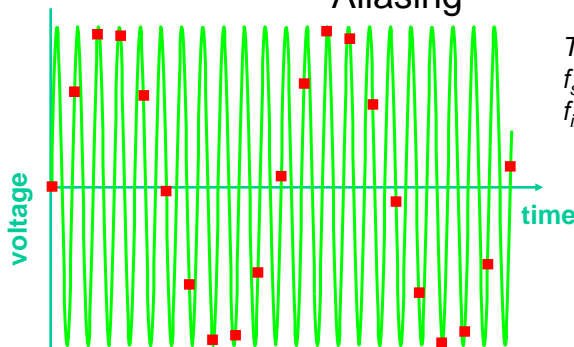

$$\begin{aligned} T &= 1\mu\text{s} \\ f_s &= 1/T = 1\text{MHz} \\ f_{in} &= 1101\text{kHz} \end{aligned}$$

$$v(n) = \cos\left(2\pi \frac{1101\text{kHz}}{1\text{MHz}} n\right) = \cos\left(2\pi \frac{(1000\text{kHz} + 101\text{kHz})}{1\text{MHz}} n\right)$$

$$= \cos\left(2\pi \frac{101\text{kHz}}{1\text{MHz}} n\right)$$

Sampling Sine Waves

Problem:

Sampled data domain \rightarrow identical samples for:

$$v(t) = \cos [2\pi f_{in} t]$$


$$v(t) = \cos [2\pi (f_{in} + n \cdot f_s) t]$$

$$v(t) = \cos [2\pi (f_{in} - n \cdot f_s) t]$$

* (n-integer)

\rightarrow Multiple continuous time signals can yield exactly the same discrete time signal


Sampling Sine Waves Frequency Spectrum

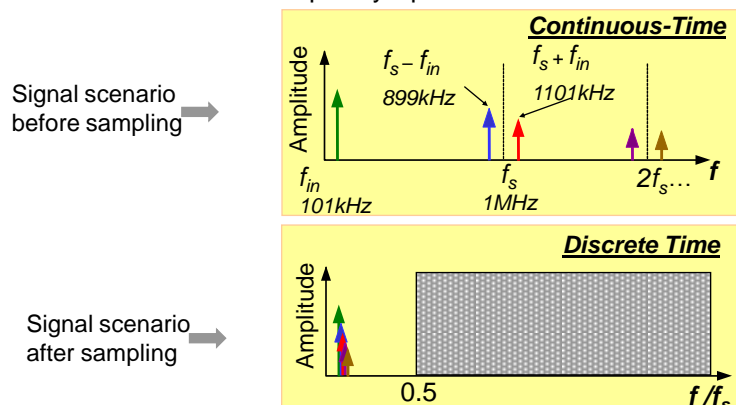


Key point: Signals @ $nf_s \pm f_{max_signal}$ fold back into band of interest \rightarrow **Aliasing**

Sampling Sine Waves Frequency Spectrum

Signal scenario
before sampling →

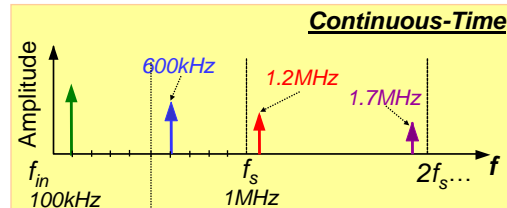

Signal scenario
after sampling →

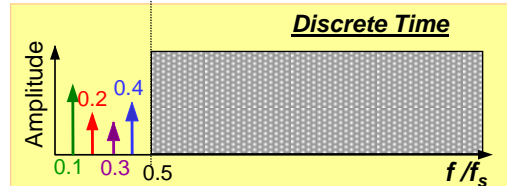

Key point: Signals @ $nf_s \pm f_{max_signal}$ fold back into band of interest → **Aliasing**

Aliasing

- Multiple continuous time signals can produce identical series of samples
- The folding back of signals from $nf_s \pm f_{sig}$ (n integer) down to the band f_{in} is called aliasing
 - Sampling theorem: $f_s > 2f_{max_Signal}$
- If aliasing occurs, no signal processing operation downstream of the sampling process can recover the original continuous time signal

How to Avoid Aliasing?

- Must obey sampling theorem:


$$f_{max-signal} < f_s/2$$

*Note:

Minimum sampling rate of $f_s = 2 \times f_{max-Signal}$ is called Nyquist rate

- Two possibilities:
 1. Sample fast enough to cover all spectral components, including "parasitic" ones outside band of interest
 2. Limit $f_{max-Signal}$ through filtering → attenuate out-of-band components prior to sampling


How to Avoid Aliasing? 1-Sample Fast

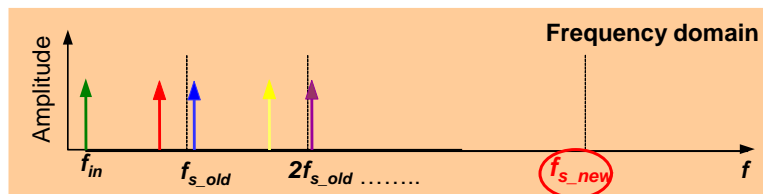

Push sampling frequency to x2 of the highest frequency signal to cover all unwanted signals as well as wanted signals


→ In vast majority of cases not practical

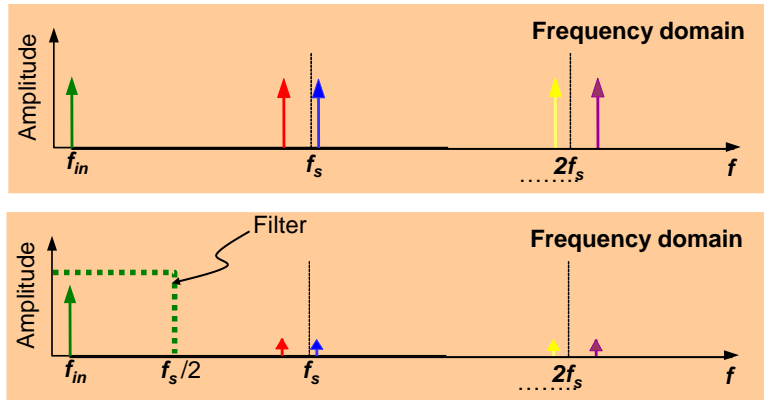How to Avoid Aliasing? 2-Filter Out-of-Band Signal Prior to Sampling



Pre-filter signal to eliminate/attenuate signals above $f_s/2$ - then sample


Anti-Aliasing Filter Considerations

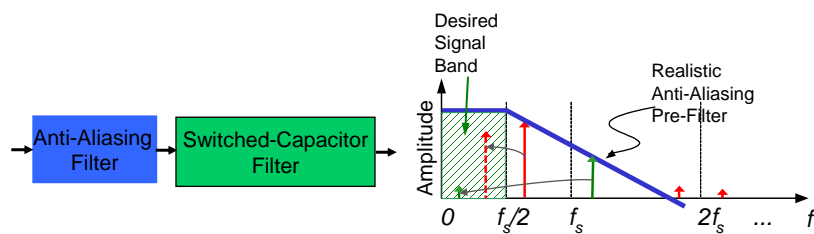

Case1- $B = f_{sig}^{max} = f_s/2$

- Practical anti-aliasing filter → Non-zero filter "transition band"
- Note out-of-band signal close to $f_s/2$ aliases down to the band of interest without much attenuation


Anti-Aliasing Filter Considerations

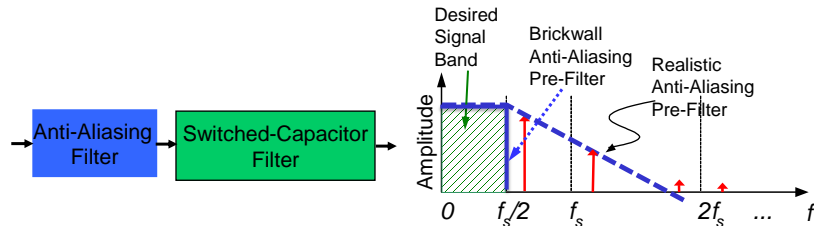

Case1- $B = f_{sig}^{max} = f_s/2$

- To achieve adequate out-of-band attenuation → extremely high order anti-aliasing filter (close to an ideal brickwall filter) is required
- Not practical anti-aliasing filter
- In order to make this work, we need to sample much faster than 2x the signal bandwidth
→ "Oversampling"


Practical Anti-Aliasing Filter

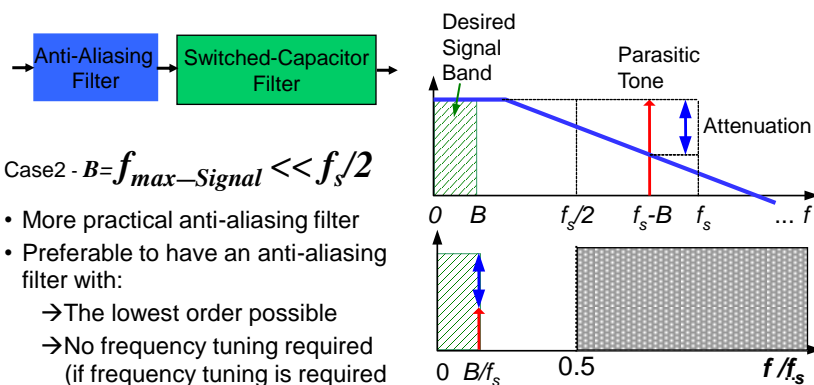

Case2 - $B = f_{max-Signal} \ll f_s/2$

- More practical anti-aliasing filter
- Preferable to have an anti-aliasing filter with:
 - The lowest order possible
 - No frequency tuning required (if frequency tuning is required then why use switched-capacitor filter, just use the prefilter!?)

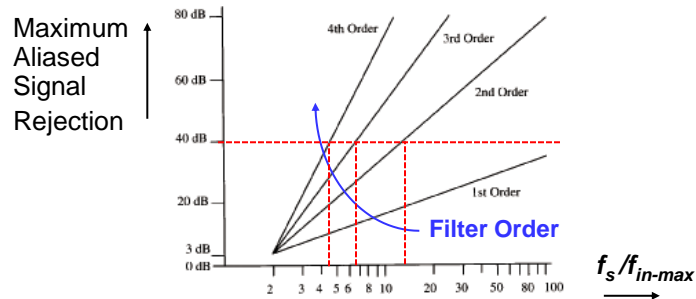Tradeoff Oversampling Ratio versus Anti-Aliasing Filter Order




* Assumption \rightarrow anti-aliasing filter is Butterworth type (not a necessary requirement)

Example:

Assume that a S.C. filter has 40dB in-band dynamic range and that out-of-band signals can have magnitude equal to in-band signals at the input \rightarrow Find the minimum required anti-aliasing filter order versus oversampling rate

Ref: R. v. d. Plassche, *CMOS Integrated Analog-to-Digital and Digital-to-Analog Converters*, 2nd ed., Kluwer publishing, 2003, p.41

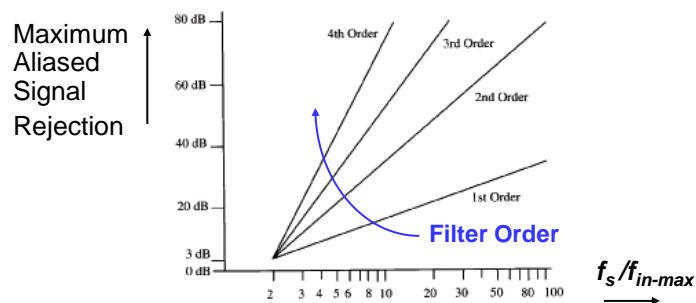Tradeoff Oversampling Ratio versus Anti-Aliasing Filter Order




* Assumption \rightarrow anti-aliasing filter is Butterworth type (not a necessary requirement)

\rightarrow Tradeoff: Sampling frequency versus anti-aliasing filter order

Ref: R. v. d. Plassche, *CMOS Integrated Analog-to-Digital and Digital-to-Analog Converters*, 2nd ed., Kluwer publishing, 2003, p.41

Effect of Sample & Hold

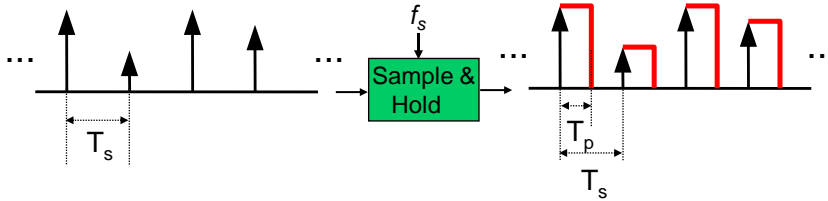


- Using the Fourier transform of a rectangular impulse:

$$|H(f)| = \frac{T_p}{T_s} \frac{\sin(\pi f T_p)}{\pi f T_p} \rightarrow \frac{\sin x}{x} \text{ shape}$$

In literature also called Sinc function

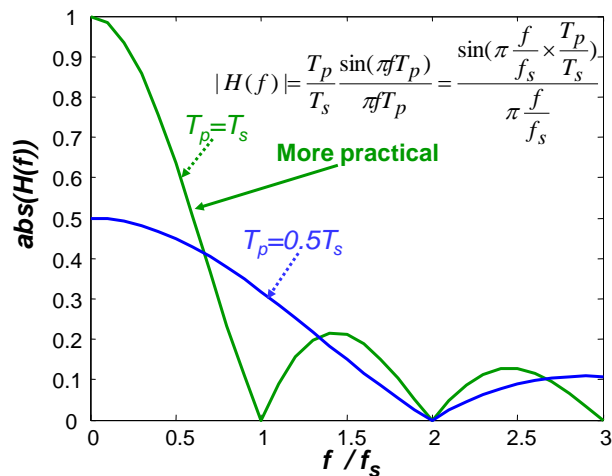Effect of Sample & Hold on Frequency Response




$$|H(f)| = \frac{T_p}{T_s} \frac{\sin(\pi f T_p)}{\pi f T_p} = \frac{\sin(\pi \frac{f}{f_s} \times \frac{T_p}{T_s})}{\pi \frac{f}{f_s}}$$

$$|H(f=0)| = \frac{T_p}{T_s}$$


$$|H(f = n f_s \frac{T_s}{T_p})| = 0$$

$n \rightarrow$ integer

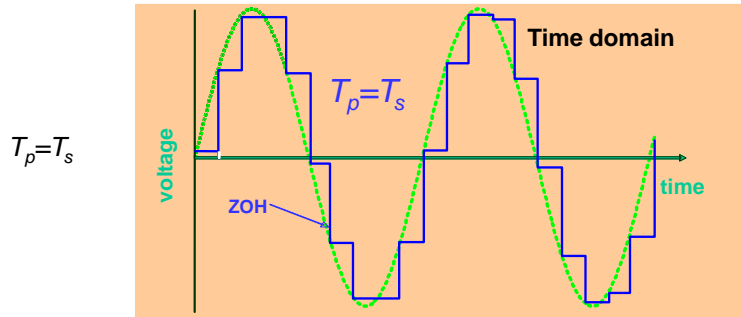Sample & Hold Effect (Reconstruction of Analog Signals)




Magnitude droop due to sinc/x effect

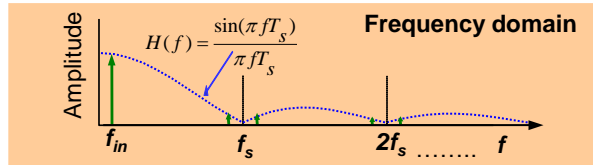


Sample & Hold Effect (Reconstruction of Analog Signals)

Magnitude droop due to sinc/x effect:

Case 1) $f_{sig} = f_s / 4$

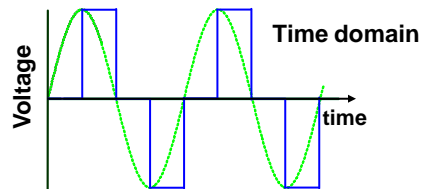

Droop = -1dB

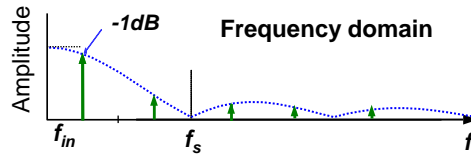

Sample & Hold Effect (Reconstruction of Analog Signals)


Magnitude droop due to ***sinx/x*** effect:

Case 2)
 $f_{sig} = f_s / 32$


Droop = -0.0035dB

• **Insignificant droop**
→ **High oversampling ratio desirable**


Time domain

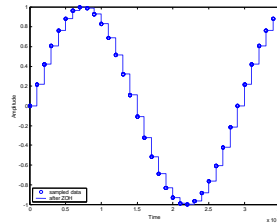


Frequency domain

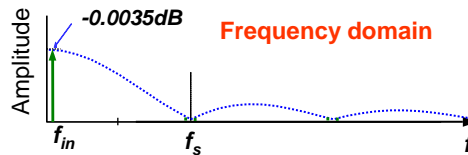

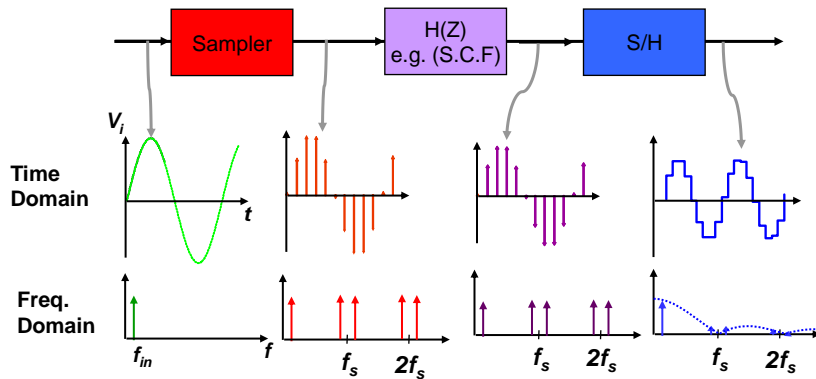Sampling Process Including S/H Input: Single In-Band Sinusoid




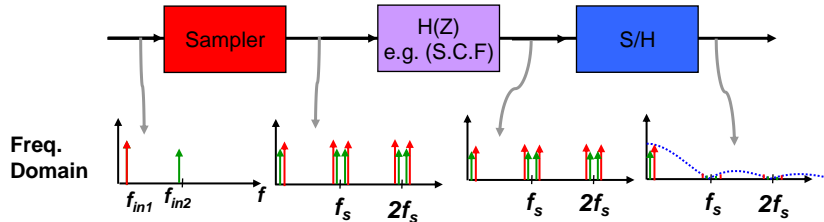Sampling Process Including S/H Input: In-Band Sinusoid + One Out-of-Band Sinusoid



Key: *Aliasing occurs prior to sinc/x shaping and hence sinc/x effect does not attenuate aliased components*

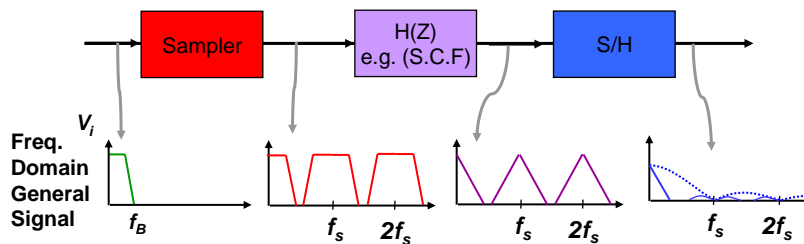Sampling Process Including S/H Input: General In-Band Signal





Key: *Beware of sinc/x shaping (droop) of in-band signals*



1st Order Filter S.C. versus C.T. Transient Analysis

1st Order RC versus SC LPF

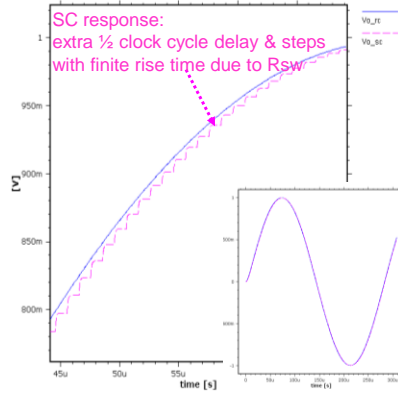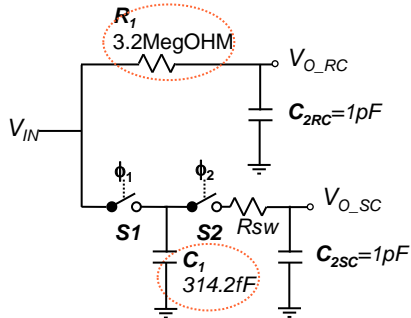$f_s = 1\text{MHz}$
 $f_{-3dB} = 50\text{kHz}$
 $f_{in} = 3.6\text{kHz}$



1st Order Filter Transient Analysis

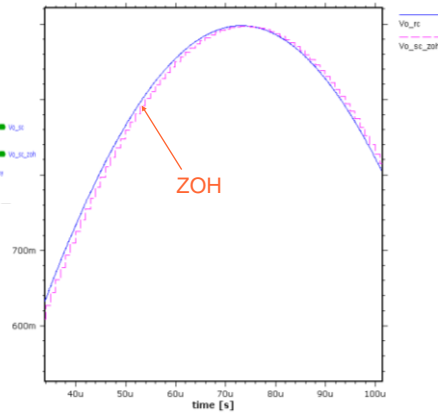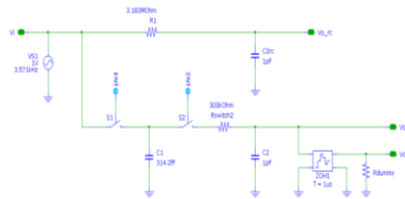

- ZOH: Emulates an ideal S/H → pick signal after output is fully settled (usually at end of clock phase)
- Adds delay and $\sin(x)/x$ shaping


Periodic AC Analysis

1st Order RC / SC LPF


$f_s = 1\text{MHz}$
 $f_c = 50\text{kHz}$
 $f_r = 9.571\text{kHz}$

Periodic AC Analysis: PAC1
 log sweep from 1 to 3.1M (1001 steps)

Netlist
 ah2_include "zoh.def"

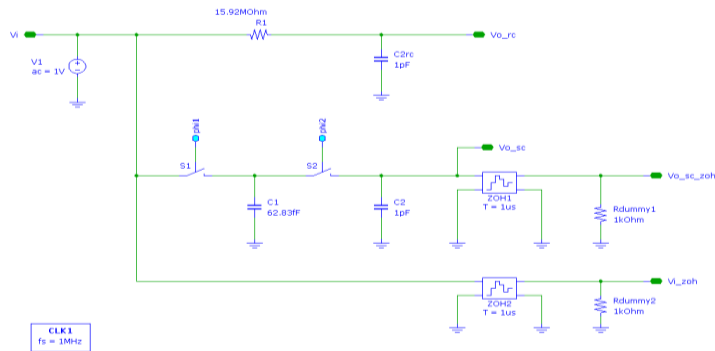

1st Order Filter Magnitude Response

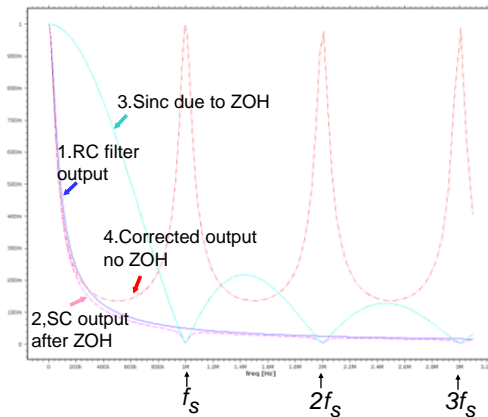

1. RC filter output
2. SC output after ZOH
3. Output after single ZOH
4. S.C. filter output w/o effect of ZOH
 - (2) over (3)
 - Repeats filter shape around nf_s
 - Identical to RC for $f \ll f_s/2$

Periodic AC Analysis

- SPICE frequency analysis
 - ac linear, **time-invariant** circuits
 - pac linear, **time-variant** circuits
- SpectreRF statements

```
V1 ( Vi 0 ) vsource type=dc dc=0 mag=1
pacmag=1
PSS1 pss period=1u errpreset=conservative
PAC1 pac start=1 stop=1M lin=1001
```
- Output
 - Divide results by $\text{sinc}(f/f_s)$ to correct for ZOH distortion

SpectreRF Circuit File

```
rc_pac
simulator lang=spectre
ahdl_include "zoh.def"

S1 ( Vi c1 phi1 0 ) relay ropen=100G rclosed=1 vt1=-500m vt2=500m
S2 ( c1 Vo_sc phi2 0 ) relay ropen=100G rclosed=1 vt1=-500m vt2=500m
C1 ( c1 0 ) capacitor c=314.159f
C2 ( Vo_sc 0 ) capacitor c=1p
R1 ( Vi Vo_rc ) resistor r=3.1831M
C2rc ( Vo_rc 0 ) capacitor c=1p
CLK1_Vphi1 ( phi1 0 ) vsource type=pulse val0=-1 vall=1 period=1u
width=450n delay=50n rise=10n fall=10n
CLK1_Vphi2 ( phi2 0 ) vsource type=pulse val0=-1 vall=1 period=1u
width=450n delay=550n rise=10n fall=10n
V1 ( Vi 0 ) vsource type=dc dc=0 mag=1 pacmag=1
PSS1 pss period=1u errpreset=conservative
PAC1 pac start=1 stop=3.1M log=1001
ZOH1 ( Vo_sc_zoh 0 Vo_sc 0 ) zoh period=1u delay=500n aperture=1n tc=10p
ZOH2 ( Vi_zoh 0 Vi 0 ) zoh period=1u delay=0 aperture=1n tc=10p
```

ZOH Circuit File

```

// Copy from the SpectreRF Primer
module zoh (Pout, Nout, Pin, Nin) (period,
    delay, aperture, tc)

node [V,I] Pin, Nin, Pout, Nout;
parameter real period=1 from (0:inf);
parameter real delay=0 from (0:inf);
parameter real aperture=1/100 from (0:inf);
parameter real tc=1/500 from (0:inf);
{
integer n; real start, stop;
node [V,I] hold;
analog {
// determine the point when aperture
begins
n = ($time() - delay + aperture) / period
+ 0.5;
start = n*period + delay - aperture;
$break_point(start);

// determine the time when aperture ends
n = ($time() - delay) / period + 0.5;
stop = n*period + delay;
$break_point(stop);
}

// Implement switch with effective series
// resistance of 1 Ohm
if ( ($time() > start) && ($time() <=
stop))
I(hold) <- V(hold) - V(Pin, Nin);
else
I(hold) <- 1.0e-12 * (V(hold) - V(Pin,
Nin));


// Implement capacitor with an effective
// capacitance of tc
I(hold) <- tc * dot(V(hold));

// Buffer output
V(Pout, Nout) <- V(hold);

// Control time step tightly during
// aperture and loosely otherwise
if (($time() >= start) && ($time() <=
stop))
$bound_step(tc);
else
$bound_step(period/5);
}
}


```

First Order S.C. Filter

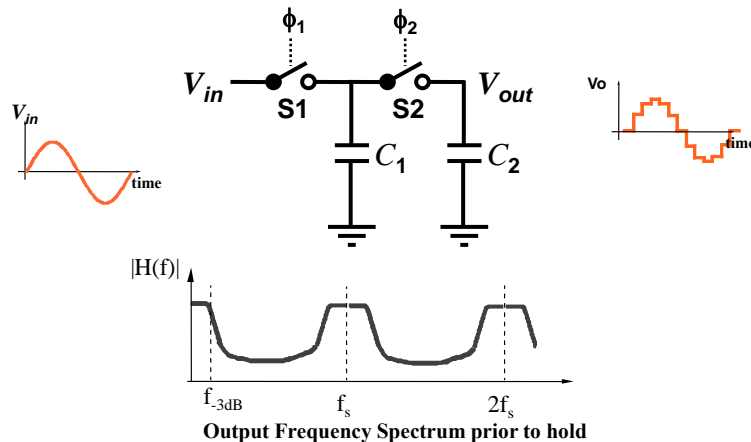

Switched-Capacitor Filters → problem with aliasing

First Order S.C. Filter

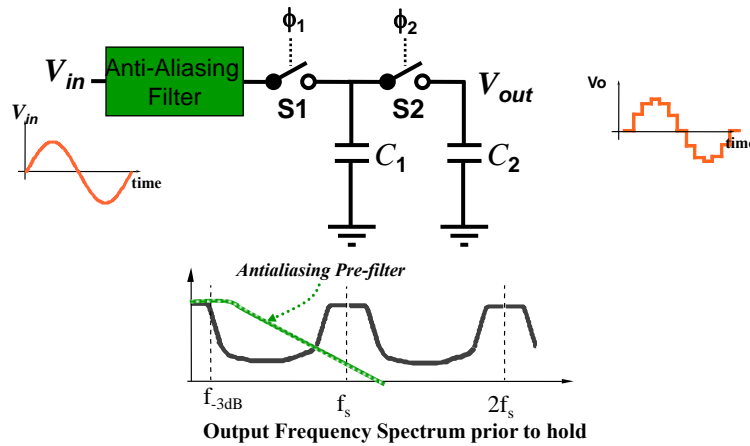


Switched-Capacitor Filters → problem with aliasing

Sampled-Data Systems (Filters) Anti-aliasing Requirements


- Frequency response repeats at $f_s, 2f_s, 3f_s, \dots$
- High frequency signals close to $f_s, 2f_s, \dots$ folds back into passband (aliasing)
- Most cases must pre-filter input to sampled-data systems (filter) to attenuate signal at:
 $f > f_s/2$ (nyquist $\rightarrow f_{max} < f_s/2$)
- Usually, anti-aliasing filter \rightarrow included on-chip as continuous-time filter with relaxed specs. (no tuning)

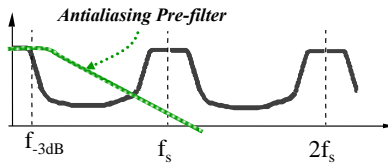Example : Anti-Aliasing Filter Requirements



- Voice-band CODEC S.C. filter high order low-pass with $f_{-3dB}=4kHz$ & $f_s=256kHz$
- Anti-aliasing continuous-time pre-filter requirements:
 - Need at least 40dB attenuation of all out-of-band signals which can alias inband
 - Incur no phase-error from 0 to 4kHz
 - Gain error due to anti-aliasing filter \rightarrow 0 to 4kHz $< 0.06dB$
 - Allow $\pm 30\%$ variation for anti-aliasing filter corner frequency (no tuning) **Need to find minimum required filter order**

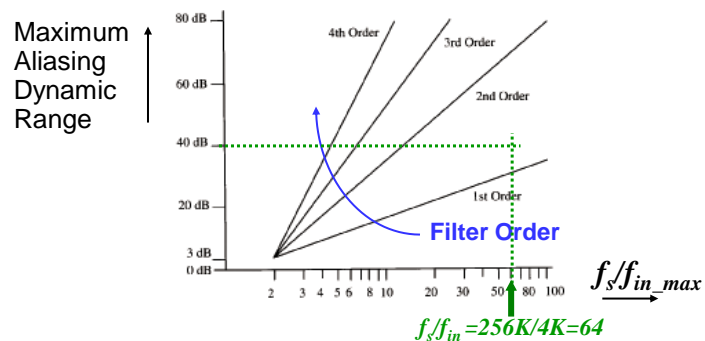Oversampling Ratio versus Anti-Aliasing Filter Order




* Assumption \rightarrow anti-aliasing filter is Butterworth type

\rightarrow 2nd order Butterworth

\rightarrow Need to find minimum corner frequency for mag. droop $< 0.06dB$

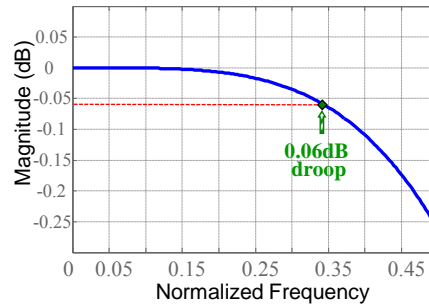
Example : Meeting the Anti-Aliasing Filter Specifications

- Note that since the anti-aliasing filter is not tuned have to make sure all specifications are met under worst-case conditions
- Worst case passband droop occurs at narrowest possible anti-aliasing filter bandwidth
- Find the AA filter bandwidth for with droop $< 0.06\text{dB}$
- Normalized frequency for 0.06dB droop: need perform passband simulation \rightarrow normalized $\omega = 0.34$
- Narrowest AA filter bandwidth \rightarrow $4\text{kHz}/0.34 = \underline{12\text{kHz}}$




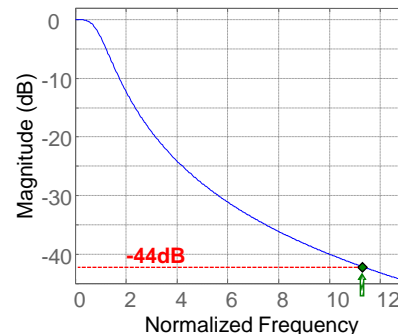Example : Anti-Aliasing Filter Specifications

- Since $\pm 30\%$ variation of AA filter corner frequency is expected
- Set anti-aliasing filter corner frequency for minimum corner frequency $\underline{12\text{kHz}}$ \rightarrow Find nominal corner frequency: $12\text{kHz}/0.7 = \underline{17.1\text{kHz}}$
- Check if min. attenuation requirement is satisfied for widest filter bandwidth \rightarrow $17.1 \times 1.3 = \underline{22.28\text{kHz}}$
- Find $(f_s \cdot f_{sig})/f_{3dB}^{\max}$
 $\rightarrow 252/22.2 = 11.35 \rightarrow$ make sure enough attenuation
- Check phase-error within 4kHz signal band for min. filter bandwidth via simulation



Example : Anti-Aliasing Filter

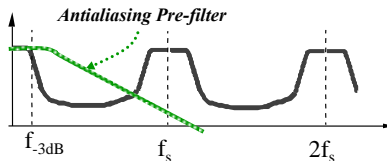

- Voice-band S.C. filter $f_{-3dB} = 4kHz$ & $f_s = 256kHz$
 - Anti-aliasing filter requirements:
 - Need 40dB attenuation at clock freq.
 - Incur no phase-error from 0 to 4kHz
 - Gain error 0 to 4kHz < 0.06dB
 - Allow +30% variation for anti-aliasing corner frequency (no tuning)
- 2-pole Butterworth LPF with nominal corner freq. of 17kHz & no tuning (min.=12kHz & max.=22kHz corner frequency)


Summary

- Sampling theorem $\rightarrow f_s > 2f_{max_Signal}$
- Signals at frequencies $nf_s \pm f_{sig}$ fold back down to desired signal band, f_{sig}
 - This is called aliasing & usually mandates use of anti-aliasing pre-filters combined with oversampling
- Oversampling helps reduce required order for anti-aliasing filter
- S/H function shapes the frequency response with $\sin x/x$ shape
 - Need to pay attention to droop in passband due to $\sin x/x$
- If the above requirements are not met, CT signals can NOT be recovered from sampled-data networks without loss of information

Switched-Capacitor Network Noise

- During ϕ_1 high: Resistance of switch S1 (R_{on}^{S1}) produces a noise voltage on C with variance kT/C (lecture 1- first order filter noise)
- The corresponding noise charge is:

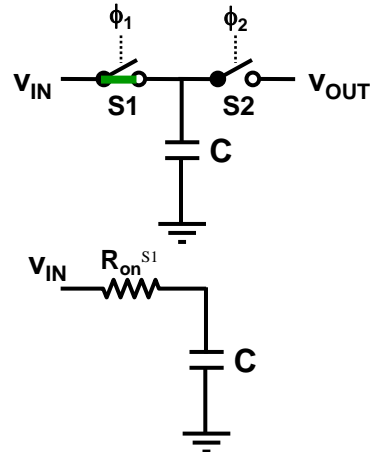
$$Q^2 = C^2 V^2 = C^2 \cdot kT/C = kTC$$
- ϕ_1 low: S1 open \rightarrow This charge is sampled



Switched-Capacitor Noise

- During ϕ_2 high: Resistance of switch S2 contributes to an uncorrelated noise charge on C at the end of ϕ_2 : with variance kT/C
- Mean-squared noise charge transferred from v_{IN} to v_{OUT} per sample period is:

$$Q^2 = 2kTC$$

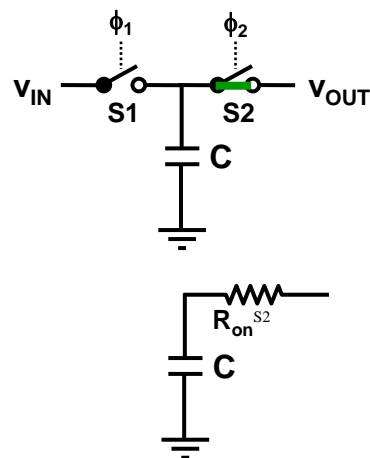

Switched-Capacitor Noise

- The mean-squared noise current due to S1 and S2's kT/C noise is :

$$\text{Since } i = Q/t \text{ then } \rightarrow \overline{i^2} = (Qf_s)^2 = 2k_B T C f_s^2$$

- This noise is approximately white and distributed between 0 and $f_s/2$ (noise spectra \rightarrow single sided by convention)
The spectral density of the noise is found:

$$\frac{\overline{i^2}}{\Delta f} = \frac{2k_B T C f_s^2}{f_s/2} = 4k_B T C f_s$$


$$\text{Since } R_{EQ} = \frac{1}{f_s C} \text{ then:}$$

$$\frac{\overline{i^2}}{\Delta f} = \frac{4k_B T}{R_{EQ}}$$

\rightarrow S.C. resistor noise = a physical resistor noise with same value!


Periodic Noise Analysis SpectreRF

Sampling Noise from SC S/H

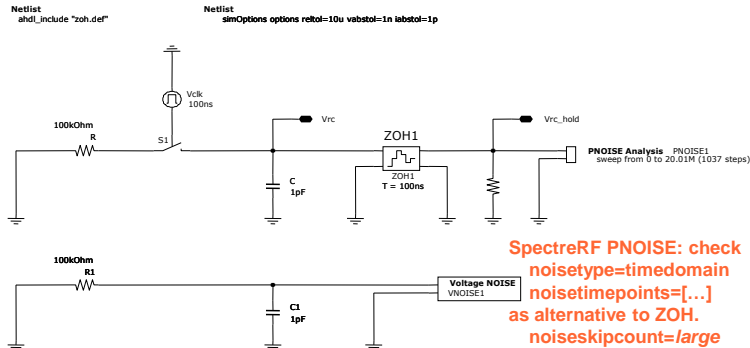


PSS pss period=100n maxacfreq=1.5G errpreset=conservative
PNOISE (Vrc_hold 0) pnoise start=0 stop=20M lin=500 maxsideband=10

Sampled Noise Spectrum

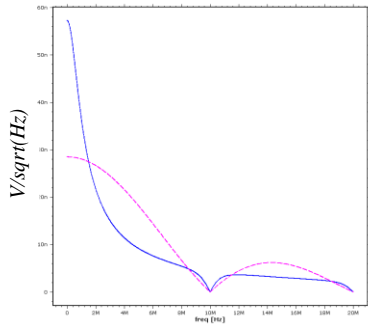


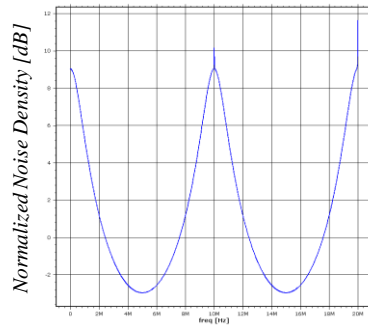Spectral density of sampled noise including sinc/x effect



Noise spectral density with sinc/x effect taken out



Total Noise

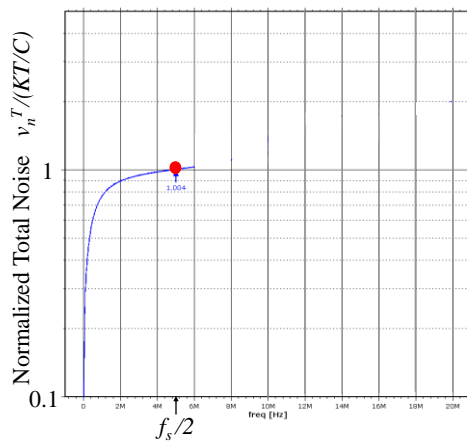

Sampled simulated noise in $0 \dots f_s/2$: $62.2\mu\text{V rms}$

(expect $64\mu\text{V}$ for 1pF)

Switched-Capacitor Integrator

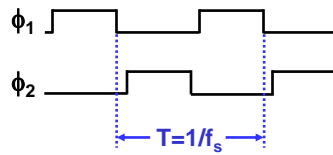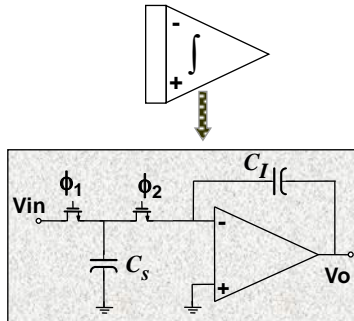





for $f_{signal} \ll f_{sampling}$

$$\rightarrow V_o = \frac{f_s \times C_s}{C_I} \int V_{in} dt$$

$$\omega = f_s \times \frac{C_s}{C_I}$$

Main advantage: No tuning needed
 → Critical frequency function of ratio of capacitors & clock freq.

Switched-Capacitor Integrator

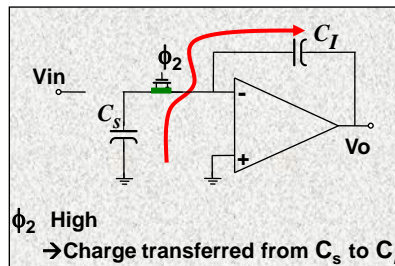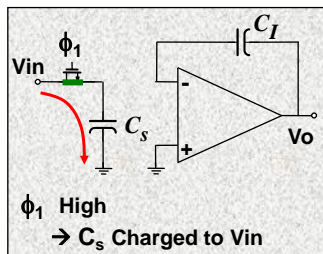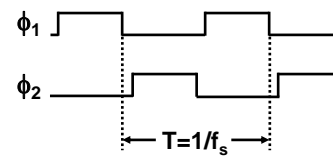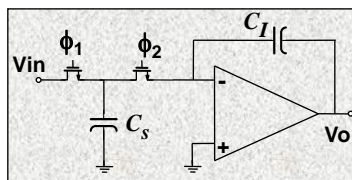

Continuous-Time versus Discrete-Time Analysis Approach

Continuous-Time

- Write differential equation
- Laplace transform ($F(s)$)
- Let $s=j\omega \rightarrow F(j\omega)$
- Plot $|F(j\omega)|$, $\text{phase}(F(j\omega))$

Discrete-Time

- Write difference equation \rightarrow relates output sequence to input sequence

$$V_o(nT_s) = V_i[(n-1)T_s] - \dots$$

- Use delay operator z^{-1} to transform the recursive realization to algebraic equation in z domain

$$V_o(z) = z^{-1}V_i(z) - \dots$$

- Set $z = e^{j\omega T}$
- Plot mag./phase versus frequency


Discrete Time Design Flow

- Transforming the recursive realization to algebraic equation in z domain:
 - Use delay operator z :


$$\begin{aligned}
 nT_s &\dots\dots\dots \rightarrow 1 \\
 [(n-1)T_s] &\dots\dots\dots \rightarrow z^{-1} \\
 [(n-1/2)T_s] &\dots\dots\dots \rightarrow z^{-1/2} \\
 [(n+1)T_s] &\dots\dots\dots \rightarrow z^{+1} \\
 [(n+1/2)T_s] &\dots\dots\dots \rightarrow z^{+1/2}
 \end{aligned}$$

* Note: $z = e^{j\omega T_s} = \cos(\omega T_s) + j \sin(\omega T_s)$

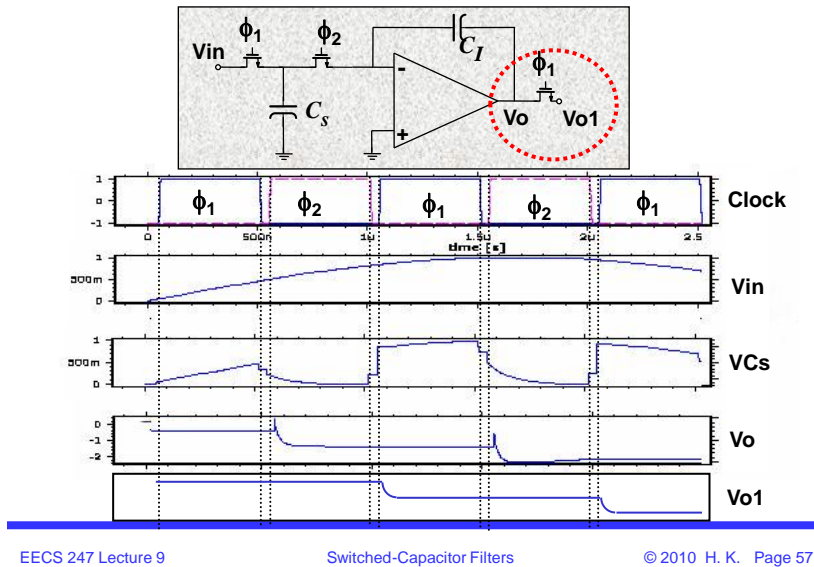Switched-Capacitor Integrator Output Sampled on ϕ_1




Switched-Capacitor Integrator

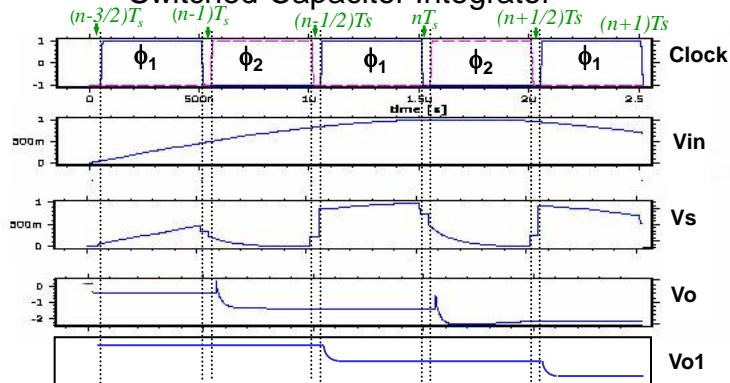

$$\begin{aligned} \Phi_1 \rightarrow Q_s [(n-1)T_s] &= C_s V_i [(n-1)T_s], & Q_I [(n-1)T_s] &= Q_I [(n-3/2)T_s] \\ \Phi_2 \rightarrow Q_s [(n-1/2)T_s] &= 0, & Q_I [(n-1/2)T_s] &= Q_I [(n-1)T_s] + Q_s [(n-1)T_s] \\ \Phi_1 \rightarrow Q_s [nT_s] &= C_s V_i [nT_s], & Q_I [nT_s] &= Q_I [(n-1)T_s] + Q_s [(n-1)T_s] \end{aligned}$$

Since $V_{o1} = -Q_I / C_I$ & $V_i = Q_s / C_s \rightarrow C_I V_{o1}(nT_s) = C_I V_{o1}[(n-1)T_s] - C_s V_i [(n-1)T_s]$

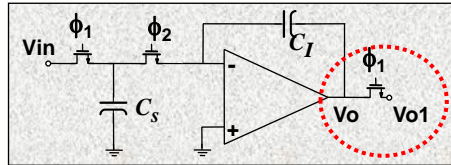Switched-Capacitor Integrator Output Sampled on ϕ_1



$$C_I V_o(nT_s) = C_I V_o[(n-1)T_s] - C_S V_{in}[(n-1)T_s]$$

$$V_o(nT_s) = V_o[(n-1)T_s] - \frac{C_S}{C_I} V_{in}[(n-1)T_s]$$


$$V_o(Z) = Z^{-1}V_o(Z) - Z^{-1}\frac{C_S}{C_I}V_{in}(Z)$$

$$\frac{V_o}{V_{in}}(Z) = -\frac{C_S}{C_I} \times \frac{Z^{-1}}{1-Z^{-1}}$$

DDI (Direct-Transform Discrete Integrator)

z-Domain Frequency Response

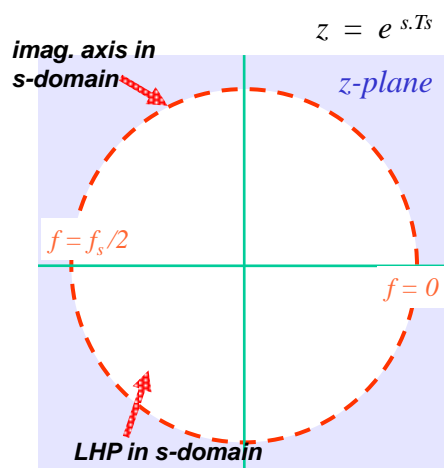- Sampled-data systems \rightarrow z plane singularities analyzed via z-plane
- The s-plane $j\omega$ axis maps onto the unit-circle
- LHP singularities in s-plane map into inside of unit-circle in z-domain
- RHP singularities in s-plane map into outside of unit-circle in z-domain
- Particular values:
 - $f = 0 \rightarrow z = 1$
 - $f = f_s/2 \rightarrow z = -1$




z-Domain Frequency Response

- The frequency response is obtained by evaluating $H(z)$ on the unit circle at:


$$z = e^{j\omega T} = \cos(\omega T_s) + j \sin(\omega T_s)$$

- Once $z = -1$ ($f_s/2$) is reached, the frequency response repeats, as expected

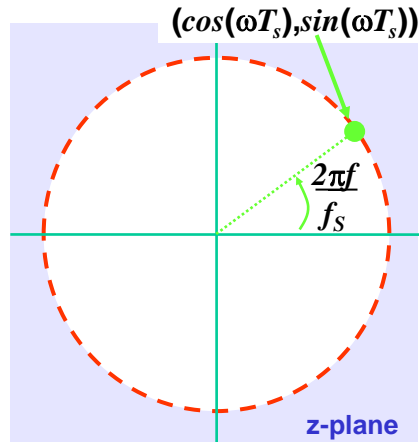- The angle to the pole is equal to 360° (or 2π radians) times the ratio of the pole frequency to the sampling frequency



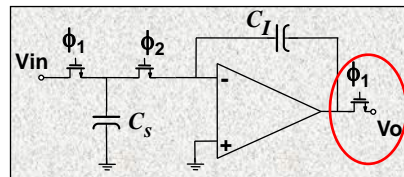Switched-Capacitor Direct-Transform Discrete Integrator



$$\begin{aligned} \frac{V_o}{V_{in}}(z) &= -\frac{C_s}{C_I} \times \frac{z^{-1}}{1-z^{-1}} \\ &= -\frac{C_s}{C_I} \times \frac{1}{z-1} \end{aligned}$$


DDI Integrator Pole-Zero Map in z-Plane

$z - 1 = 0 \rightarrow z = 1$
on unit circle


Pole from $f \rightarrow 0$
in s-plane mapped to $z = +1$

As frequency increases z
domain point moves on unit
circle (CCW)

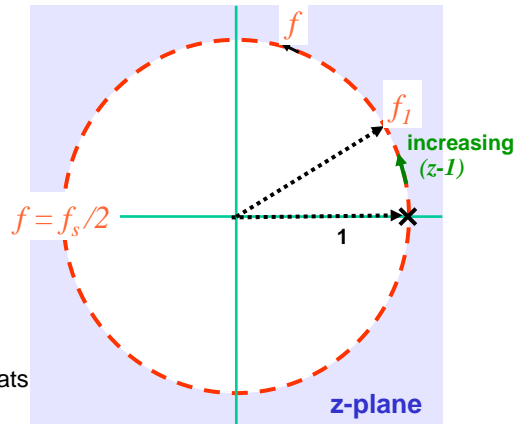Once frequency gets to:
 $z = -1$ ($f = f_s/2$)
 \rightarrow frequency response repeats




DDI Switched-Capacitor Integrator

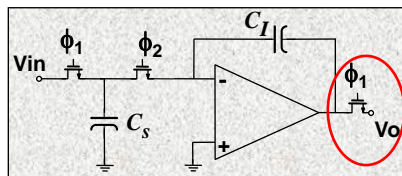

$$\begin{aligned} \frac{V_o}{V_{in}}(z) &= -\frac{C_s}{C_f} \times \frac{z^{-1}}{1-z^{-1}} = \frac{C_s}{C_f} \times \frac{-1}{1-z} \quad , \quad z = e^{j\omega T} \\ &= \frac{C_s}{C_f} \times \frac{1}{1-e^{j\omega T}} = \frac{C_s}{C_f} \times \frac{e^{-j\omega T/2}}{e^{-j\omega T/2} - e^{j\omega T/2}} \quad \text{since: } \sin \alpha = \frac{e^{j\alpha} - e^{-j\alpha}}{2j} \\ &= -j \frac{C_s}{C_f} \times e^{-j\omega T/2} \times \frac{1}{2 \sin(\omega T/2)} \\ &= \underbrace{-\frac{C_s}{C_f} \frac{1}{j\omega T}}_{\text{Ideal Integrator}} \times \underbrace{\frac{\omega T/2}{\sin(\omega T/2)}}_{\text{Magnitude Error}} \times \underbrace{e^{-j\omega T/2}}_{\text{Phase Error}} \end{aligned}$$

DDI Switched-Capacitor Integrator

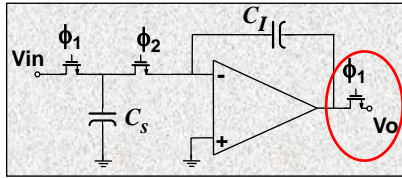

$$\frac{V_o}{V_{in}}(z) = -\frac{C_s}{C_I} \frac{1}{j\omega T} \times \frac{\omega T / 2}{\sin(\omega T / 2)} \times e^{-j\omega T / 2}$$

Example: Mag. & phase error for:

$$1-f/f_s=1/12 \rightarrow \text{Mag. error} = 1\% \text{ or } 0.1\text{dB}$$

$$\text{Phase error} = 15 \text{ degree}$$

$$Q_{\text{intg}} = -3.8$$

Magnitude Error

Phase Error

$$2-f/f_s=1/32 \rightarrow \text{Mag. error} = 0.16\% \text{ or } 0.014\text{dB}$$


$$\text{Phase error} = 5.6 \text{ degree}$$

$$Q_{\text{intg}} = -10.2$$


DDI Integrator:

→ magnitude error no problem
phase error major problem

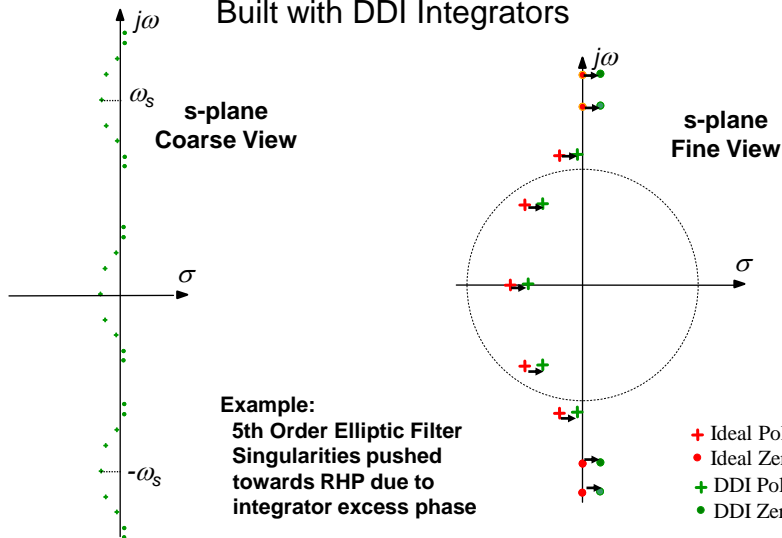
5th Order Low-Pass Switched Capacitor Filter Built with DDI Integrators



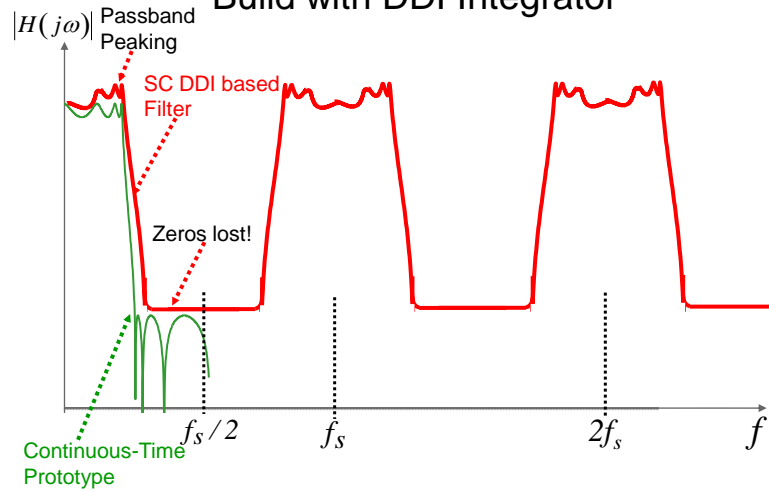Switched Capacitor Filter Build with DDI Integrator




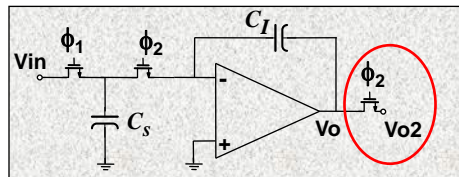Switched-Capacitor Integrator Output Sampled on ϕ_2



Sample output $\frac{1}{2}$ clock cycle earlier
 → Sample output on ϕ_2

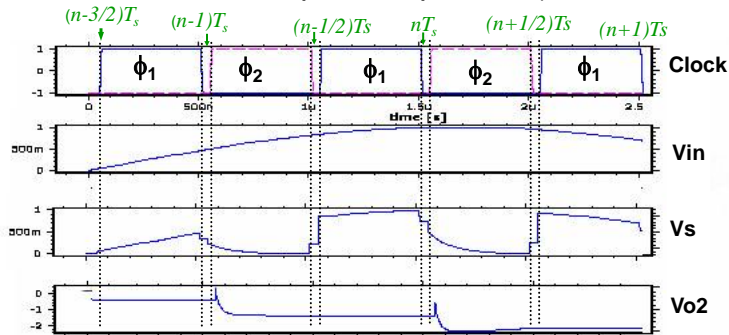Switched-Capacitor Integrator Output Sampled on ϕ_2




$$\Phi_1 \rightarrow Q_s [(n-1)T_s] = C_s V_i [(n-1)T_s], \quad Q_i [(n-1)T_s] = Q_i [(n-3/2)T_s]$$

$$\Phi_2 \rightarrow Q_s [(n-1/2)T_s] = 0, \quad Q_i [(n-1/2)T_s] = Q_i [(n-3/2)T_s] + Q_s [(n-1)T_s]$$

$$\Phi_1 \rightarrow Q_s [nT_s] = C_s V_i [nT_s], \quad Q_i [nT_s] = Q_i [(n-1)T_s] + Q_s [(n-1)T_s]$$

$$\Phi_2 \rightarrow Q_s [(n+1/2)T_s] = 0, \quad Q_i [(n+1/2)T_s] = Q_i [(n-1/2)T_s] + Q_s [nT_s]$$

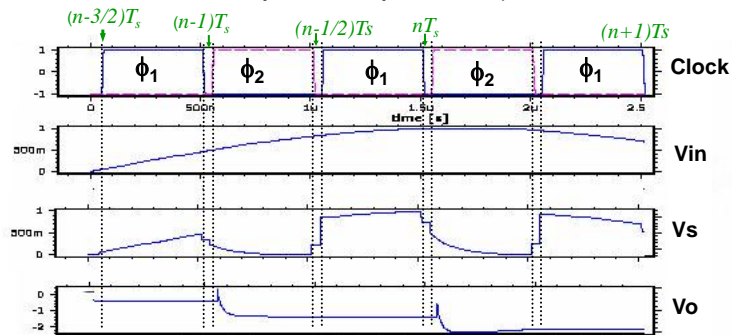Switched-Capacitor Integrator Output Sampled on ϕ_2



$$Q_i [(n+1/2)T_s] = Q_i [(n-1/2)T_s] + Q_s [nT_s]$$

$$V_{o2} = -Q_i / C_1 \quad \& \quad V_i = Q_s / C_s \rightarrow C_1 V_{o2} [(n+1/2)T_s] = C_1 V_{o2} [(n-1/2)T_s] - C_s V_i [nT_s]$$

Using the z operator rules:

$$\rightarrow C_1 V_{o2} z^{1/2} = C_1 V_{o2} z^{-1/2} - C_s V_i$$

$$\frac{V_{o2}}{V_{in}}(z) = -\frac{C_s}{C_1} \times \frac{z^{-1/2}}{1-z^{-1}}$$

LDI Switched-Capacitor Integrator

LDI (Lossless Discrete Integrator) → same as DDI but output is sampled 1/2 clock cycle earlier

LDI

$$\frac{V_{o2}(z)}{V_{in}} = -\frac{C_s}{C_I} \times \frac{z^{-1/2}}{1-z^{-1}}, \quad z = e^{j\omega T}$$


$$= -\frac{C_s}{C_I} \times \frac{e^{-j\omega T/2}}{1-e^{-j\omega T}} = \frac{C_s}{C_I} \times \frac{1}{e^{-j\omega T/2} - e^{+j\omega T/2}}$$

$$= -j \frac{C_s}{C_I} \times \frac{1}{2 \sin(\omega T/2)}$$

$$= -\frac{C_s}{C_I} \frac{1}{j\omega T} \times \frac{\omega T/2}{\sin(\omega T/2)}$$

Ideal Integrator

Magnitude Error

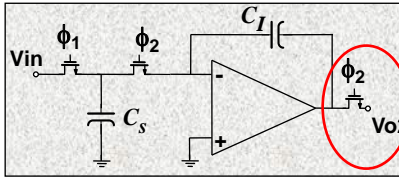

No Phase Error!
For signals at frequencies \ll sampling freq.
→ Magnitude error negligible

Switched-Capacitor Filter Built with LDI Integrators

