

EECS 40, Fall 2006
Prof. Chang-Hasnain
Midterm #3

November 29, 2006
 Total Time Allotted: 50 minutes
Total Points: 100 pts

1. This is a closed book exam. However, you are allowed to bring one page (8.5" x 11"), single-sided notes PLUS your 1-page notes from midterm 1 and 2.
2. No electronic devices, i.e. calculators, cell phones, computers, etc.
3. Slide rules are allowed.
4. SHOW all the steps on the exam. **Answers without steps will be given only a small percentage of credits.** Partial credits will be given if you have proper steps but no final answers.
5. **Remember to put down units.** Points will be taken off for answers without units.


Last (Family) Name: _____

First Name: _____

Student ID: _____ Discussion Session: _____

Signature: _____

Score:	
Problem 1 (30 pts) Op Amp Circuit	
Problem 2 (40 pts): Diode Circuit	
Problem 3 (30 pts): Semiconductor Physics	
Total	

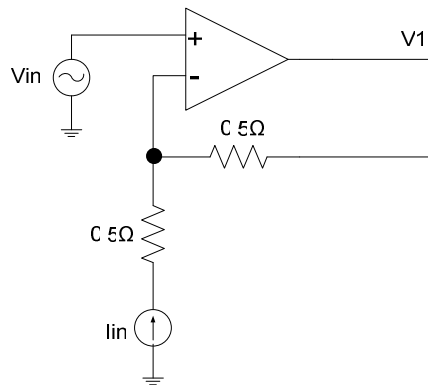
1. [30 points] Op. Amp. Circuita) [8 pts] Find V_1 in terms of V_{in} and I_{in} .

By the summing point constraint:

$$V_- = V_+ = V_{in}$$

By Ohm's Law:

$$V_1 = V_{in} - I_{in}(0.5\Omega)$$

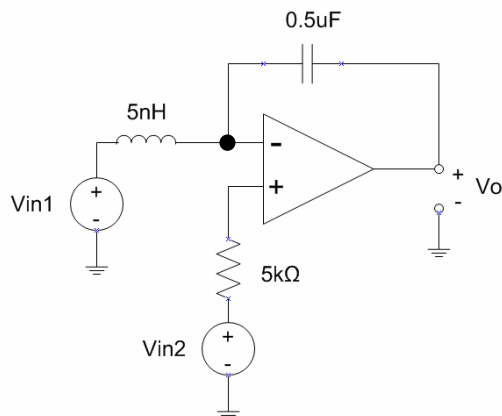b) [12 pts] Find V_0 in terms of V_{in1} , V_{in2} , and ω . Use complex impedances. Assume V_{in1} and V_{in2} are AC signals.

Since no current flows into the (+) terminal:

$$V_+ = V_{in2}$$

By the summing point constraint:


$$V_- = V_{in2}$$

By KCL:

$$V_0 = V_{in2} - \frac{Z_C}{Z_L}(V_{in1} - V_{in2}), Z_C = \frac{1}{j\omega 0.5\mu F}, Z_L = j\omega 5nH$$

$$V_0 = V_{in2} + \frac{1}{\omega^2(0.5\mu F)(5nH)}(V_{in1} - V_{in2})$$

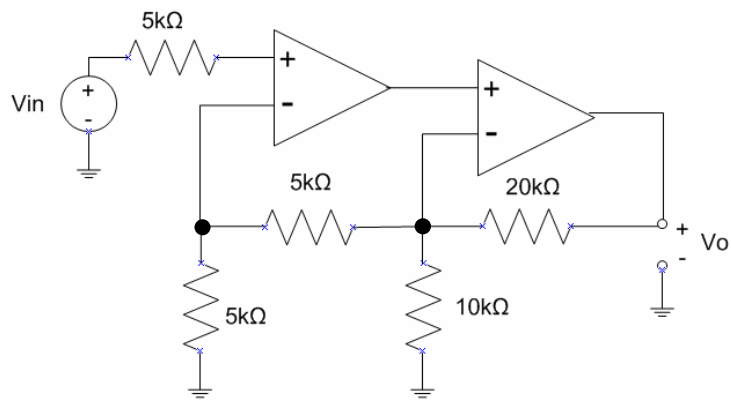c) [10 pts] Find V_o in terms of V_{in} .



Since no current flows into the (+,1) terminal:

$$V_{+,1} = V_{in}$$

By the summing point constraint:

$$V_{-,1} = V_{in}$$

Since no current flows into the (-,1) terminal:

$$V_{-,2} = 2(V_{-,1}) \text{ by voltage divider across 2 resistors}$$

Since no current flows into the (-,2) terminal:

$$V_{-,2} = V_o [5k\Omega / (5k\Omega + 20k\Omega)]$$

$$V_o = 5V_{-,2} = 5(2V_{-,1}) = 10V_{in}$$

2. [40 points] Diode Circuit:

Given the following circuit and input. Assume $C_1 \gg C_2$. Use the Ideal Diode model:

If $V_D < 0$, then the diode is OFF and does not pass current ($I_D=0$)


If $I_D \geq 0$, then the diode is ON and $V_D=0$

V_D is the voltage drop across the diode and I_D is current through the diode.

$$V_{IN}(t) = -V_m \sin(2\pi t/T) \text{ for } t > 0,$$

and

$$V_{C1}(t=0^+) = V_{C2}(t=0^+) = 0.$$

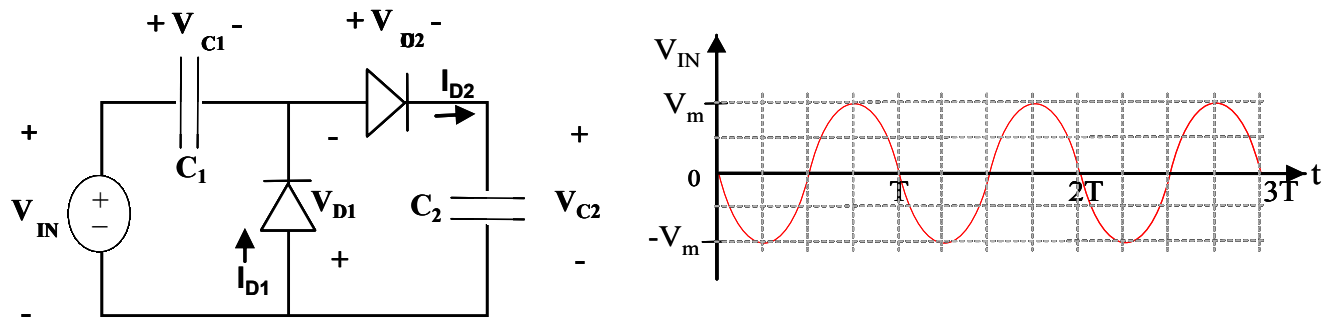

(a) (20 pts) **For the time period** $0 \leq t \leq \frac{T}{4}$

Is Diode 1 on or off? *On, V_{in} is -, so Diode 1 is turned on, charging C_1*

$V_{D1}=?$ *0V (on, Ideal)*

$V_{C1}=?$ *$V_{in}(t)$, Diode 1 on grounds the node above the diode, ($V_{C1} = V_{in} - 0$)*

$I_{D1}=?$ *$C_1 \frac{2\pi}{T} V_m \cos\left(\frac{2\pi t}{T}\right)$, I_{D1} enters negative reference of C_1 , $I_{D1} = -C_1 \frac{dV_{C1}}{dt}$*

If this was done in the frequency domain, $I = -\frac{V_{in}}{\left(\frac{1}{j\omega C_1}\right)}$

Is Diode 2 on or off? *On, node between diodes is ground (0V), V_{C2} is 0V above the ground*

$V_{D2}=?$ *0V (on, Ideal)*

$V_{C2}=?$ *0V (ground on both sides of C_2)*

$I_{D2}=?$ 0 A, no current flows through capacitor, all current is through D1 and C1

(b) (20 pts) **For the period** $\frac{T}{4} \leq t \leq \frac{3T}{4}$

Is Diode 1 on or off? *Off, Voltage begins decreasing on + reference of diode. (At $t = T/4$, treat VC1+ node as ground, Voltage on both sides of diode is +Vm. This magnitude begins decreasing, shutting off diode, since $V_{D+} < V_{D-}$)*

$V_{D1}=?$ $-V_{in} + V_{c1}$, KVL requires $V_{in} - V_{c1} + V_{d1} = 0$

$V_{C1}=?$ $-V_m$, (If you assume that $C1 \gg C2$, the same current through both will charge C2 without significantly discharging C1)

$I_{D1}=?$ 0A, Diode off

Is Diode 2 on or off? on

$V_{D2}=?$ 0V (on, Ideal)

$V_{C2}=?$ $V_{in} + V_m$ (KVL: $V_{in} - V_{c1} - V_{d2} - V_{c2} = 0$)

$I_{D2}=?$ $-C_2 \frac{2\pi}{T} V_m \cos\left(\frac{2\pi t}{T}\right)$, $I_{D2} = C_2 \frac{dV_{C2}}{dt}$

In the frequency domain, $I = \frac{V_{in}}{\left(\frac{1}{j\omega C_2}\right)}$

3. [30 points] Semiconductor Physics

Suppose two doped blocks of silicon, one with an N-dopant concentration of $5 \times 10^{18} \text{ cm}^{-3}$, and the other with a P-dopant concentration of $1 \times 10^{17} \text{ cm}^{-3}$.

a) (5 pts) What is the concentration of majority charge carriers in N-block? What type of charge carriers is in the majority?

Answer:

$5 \times 10^{18} \text{ cm}^{-3}$
Electrons

b) (5 pts) What is the concentration of majority charge carriers in P-block? What type of charge carriers is in the majority?


Answer:

$1 \times 10^{17} \text{ cm}^{-3}$
Holes

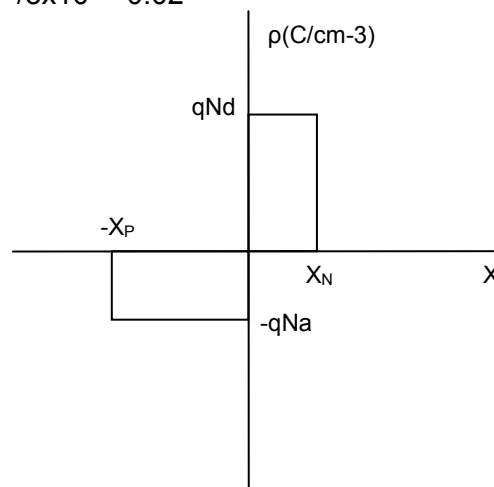c) (6 pts) Suppose the two regions are connected together to form a PN junction with the junction as $x = 0$, p-side on the left ($x < 0$) and n-side on the right ($x > 0$). Use depletion approximation and assume the depletion region in the N side is $x \in [0, x_N]$ and P side is $x \in [-x_P, 0]$. Plot the charge density $\rho(x)$ over the pn junction. What is x_N/x_P ?


Answer:

$$x_N/x_P = N_A/N_D = 1 \times 10^{17} / 5 \times 10^{18} = 0.02$$




d) (7 pts) Plot electric field $E(x)$ vs. distance x . Assuming the ϵ is the permittivity of the material. Label your plot. Write E_{\max} as a function of x_N .

Answer:

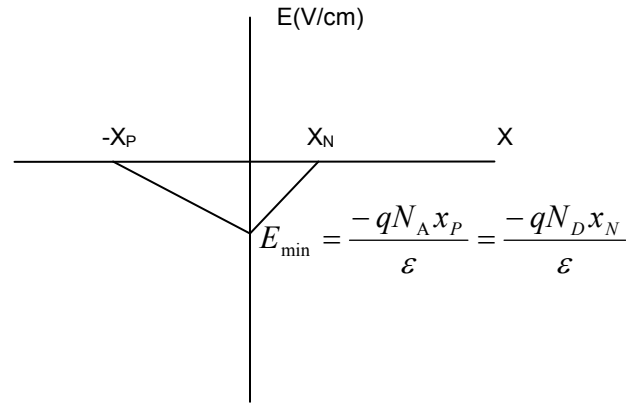

e) (7 pts) Plot electrostatic potential $V(x)$ vs. distance x . Assume the reference point $V=0$ at p -side $x \ll -x_p$. Label your plot and write V_{\max} as a function of x_N .

Answer:

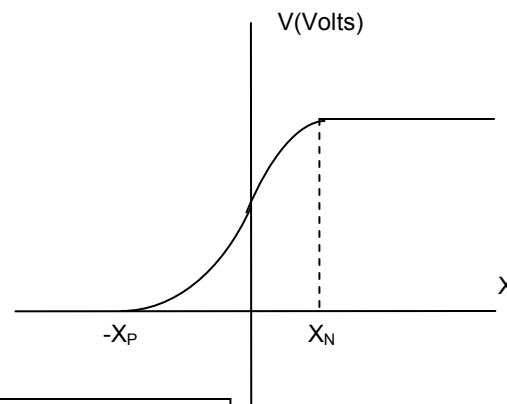

$$V_{\max} = \frac{qN_D(x_N)^2}{2\epsilon} + \frac{qN_A(x_p)^2}{2\epsilon}$$

where

$$x_p = \frac{N_D x_N}{N_A}$$

so

$$V_{\max} = \frac{qN_D(x_N)^2}{2\epsilon} \left(1 + \frac{N_D}{N_A} \right)$$