

## Administrivia

- Op-amps handout is the same as the theory handout for lab
  - Note about lab #4:
    - Bring a check made out to UC Regents. \$240/group. Post date to August 15th 2003.
- DO NOT FORGET THE CHECK!
- To receive your calbot kit, please bring the check!
  - How is HW #2 going?

**Last Time...**

- Thevenin's Theorem
- Do you have questions on Thevenin's theorem?


## This Time...

- The Operational Amplifier
  - General Amplifier Model
  - The Op Amp model
  - Amplifier circuits
    - \* Voltage follower
    - \* Non inverting Amplifier
    - \* Inverting Amplifier
    - \* Integrator
  - Introduction to frequency response
  - Practical applications of op-amp

# The Operational Amplifier


- Op-amp for short.
- A device that amplifies as well as perform other functions like integration, differentiation and evaluating the logarithm.
- We are going to be using the “ideal circuit model”. Op-amp is very complicated (take EECS 140 @ UC Berkeley):

## Schematic Diagram

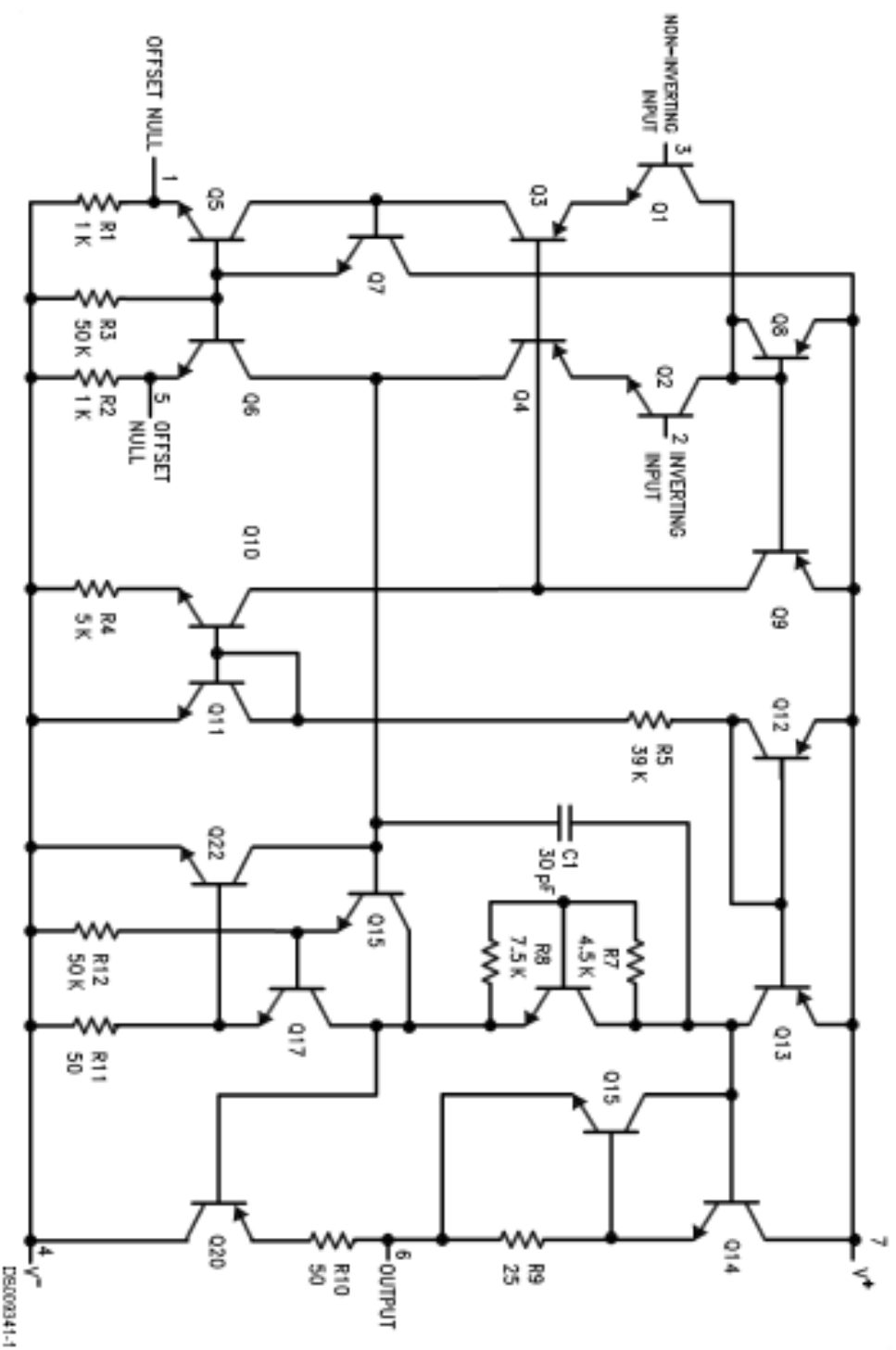

- Source: <http://www.national.com/ds/LM/LM741.pdf>


# General Amplifier Model

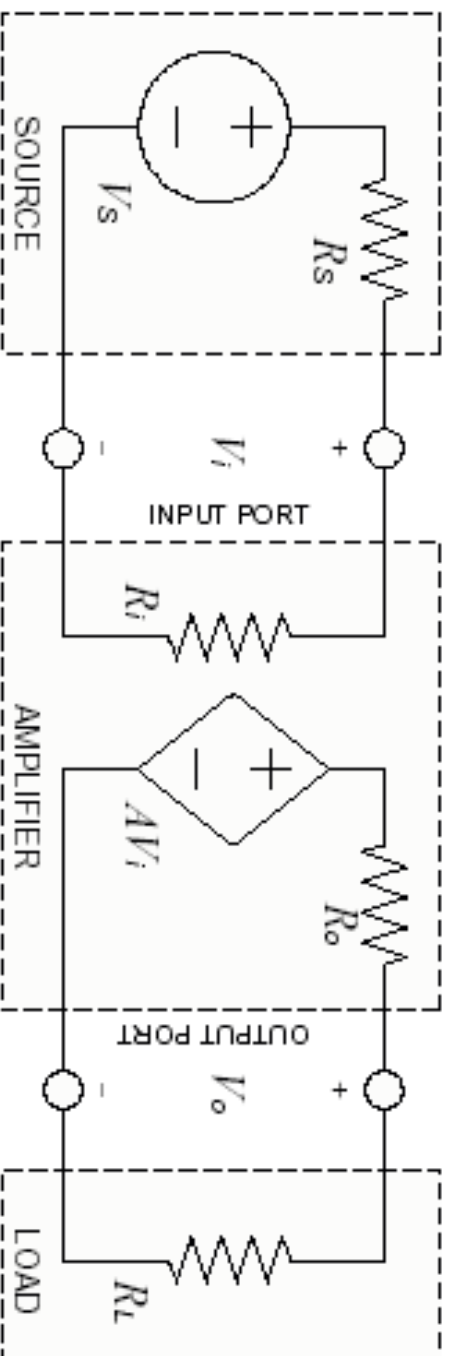


**Figure 1:** Circuit model of an amplifier circuit.

# The Op Amp

- Symbol and notations (don't forget the power supply)
- Non-ideal vs ideal:

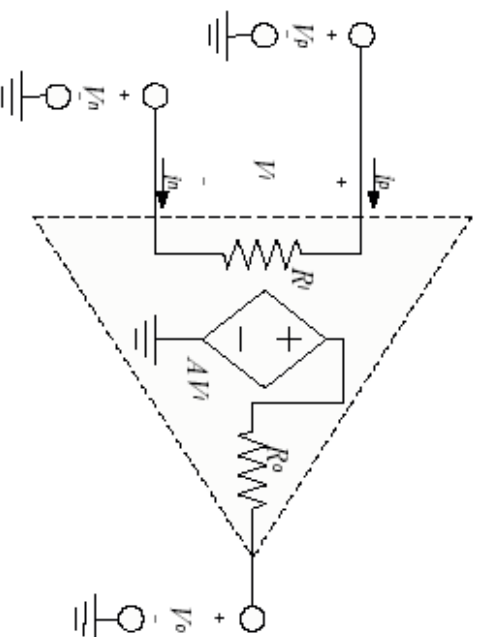

**Figure 2:** Standard op-amp

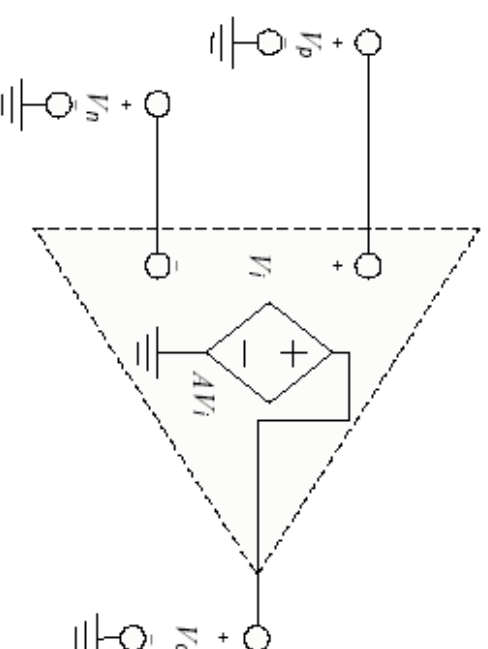

**Figure 3:** Ideal op-amp

## Ideal Op Amp Assumptions

- Remember these ideal op-amp assumptions:

Gain is infinite:  $A \rightarrow \infty$

Input resistance is infinite:  $R_i \rightarrow \infty$

Output resistance is zero:  $R_o = 0$

- Practically important:


$$i_n = i_p$$

$$V_p = V_n$$



# Voltage Transfer Characteristic

- Voltage Transfer Characteristic (VTC) is a plot of  $V_{out}$  vs.  $V_{in}$
- Ideal versus non-ideal op-amp VTC:

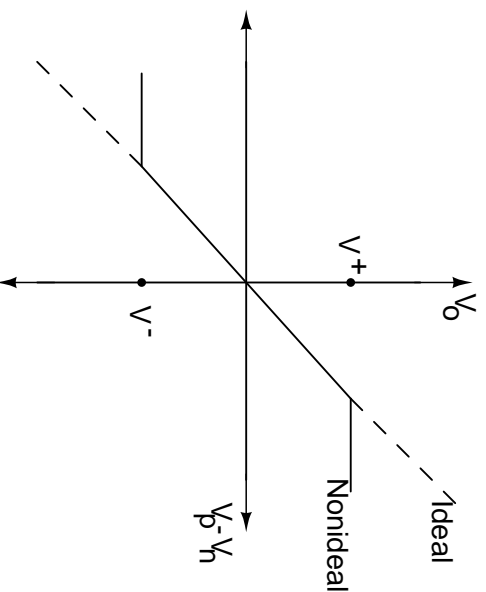

**Graph 1.** Op-amp voltage transfer characteristic

- Now we look at op-amp circuits.

# Voltage Follower

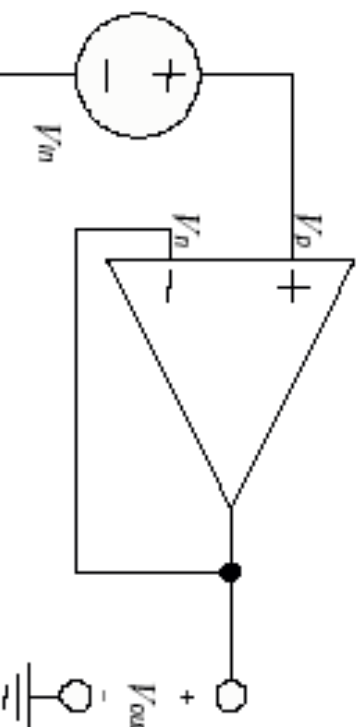


Figure 5a: Voltage follower

## Non inverting Amplifier

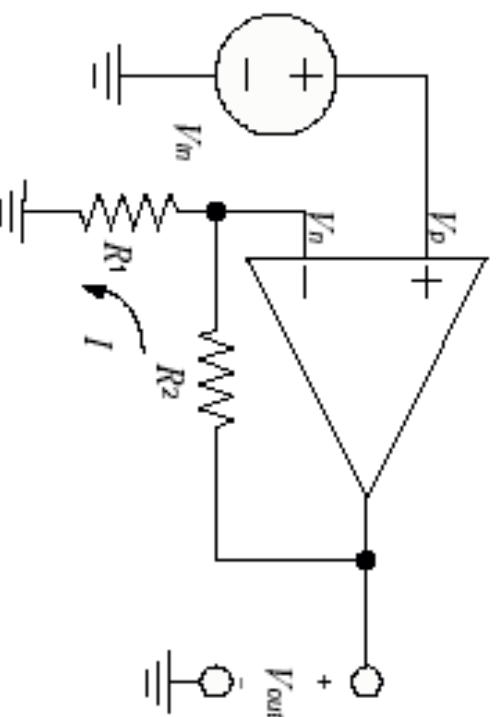


Figure 4a: Non-inverting amplifier

## Inverting Amplifier

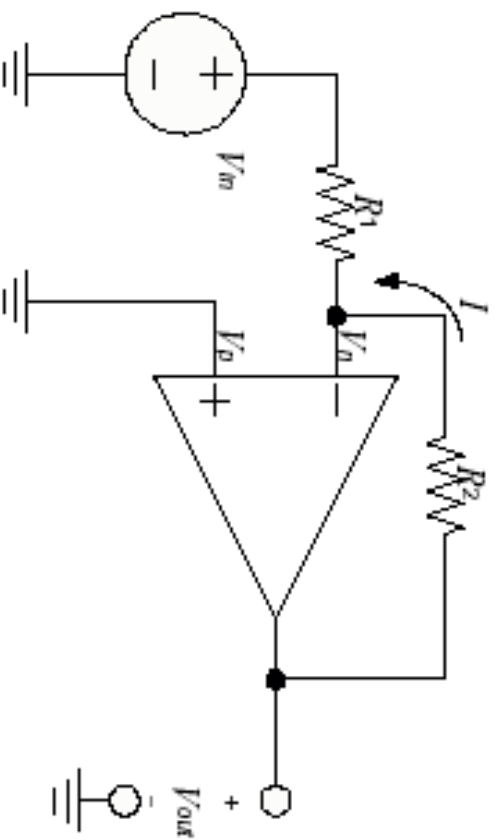


Figure 6a: Inverting amplifier

# Integrator


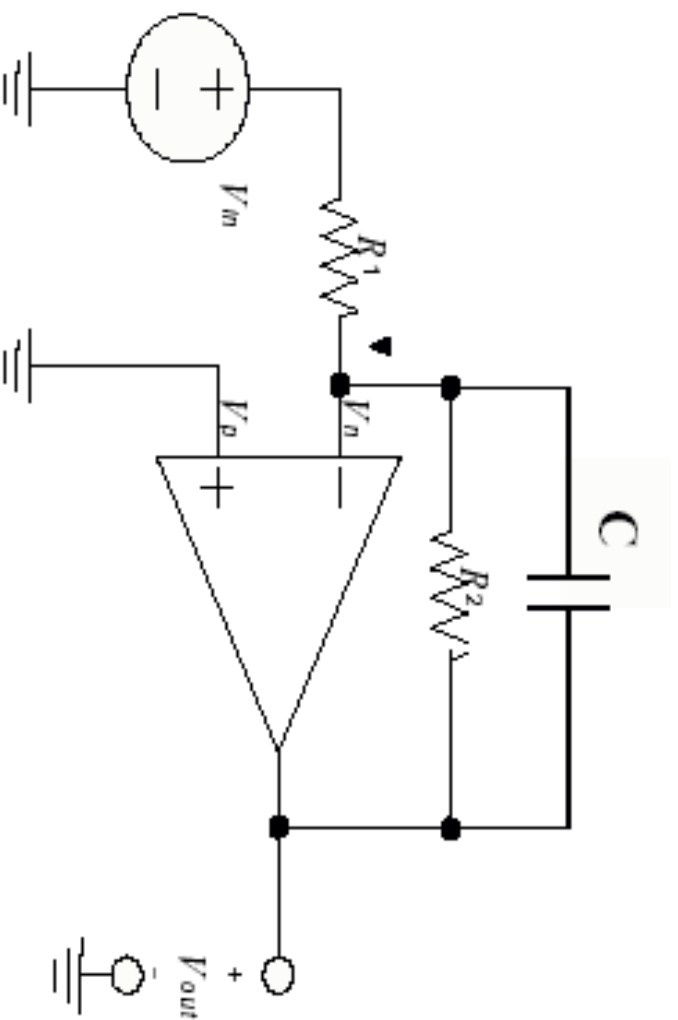


Figure 8: Integrator
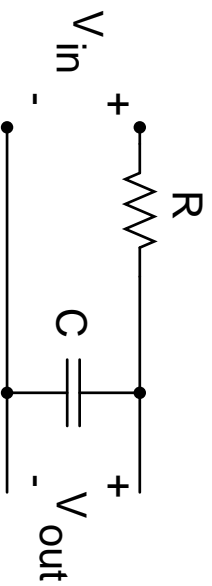
## Intro. to Frequency Response

- Out of the scope of this class. Just give a hand-wavy intro using a low pass filter:



## Op-Amp Practical Applications

- My EECS 192 race car:
  - Op-amp used to amplify magnetic signals from track

## Summary

- Another tool added to our toolbox: the op-amp
  - REMEMBER THE IDEAL OP-AMP ASSUMPTIONS!
  - Some typical op-amp configurations: voltage buffer, inverting amplifier, non-inverting amplifier and the integrator
  - Practice them circuits!



## In Conclusion...

- Next time: Official end of circuit analysis - Source transformations
- Introduction to IC fabrication - prelude to guest lecture
- Reading: Finish chapter 4 of the reader - source transforms and maximum power transfer theorem.
- Lab 3 should help you understand op-amps better
- REMEMBER CHECK FOR CALBOT KIT!
- I will talk a little bit about the calbot project...
- Questions?