

EE 40

Lecture 8



Thevenin and Norton Equivalent Circuits

We have been studying the current-voltage relationships for several devices, like resistors and capacitors, for example.



$$V = RI$$

$$I = C \frac{dV}{dt}$$

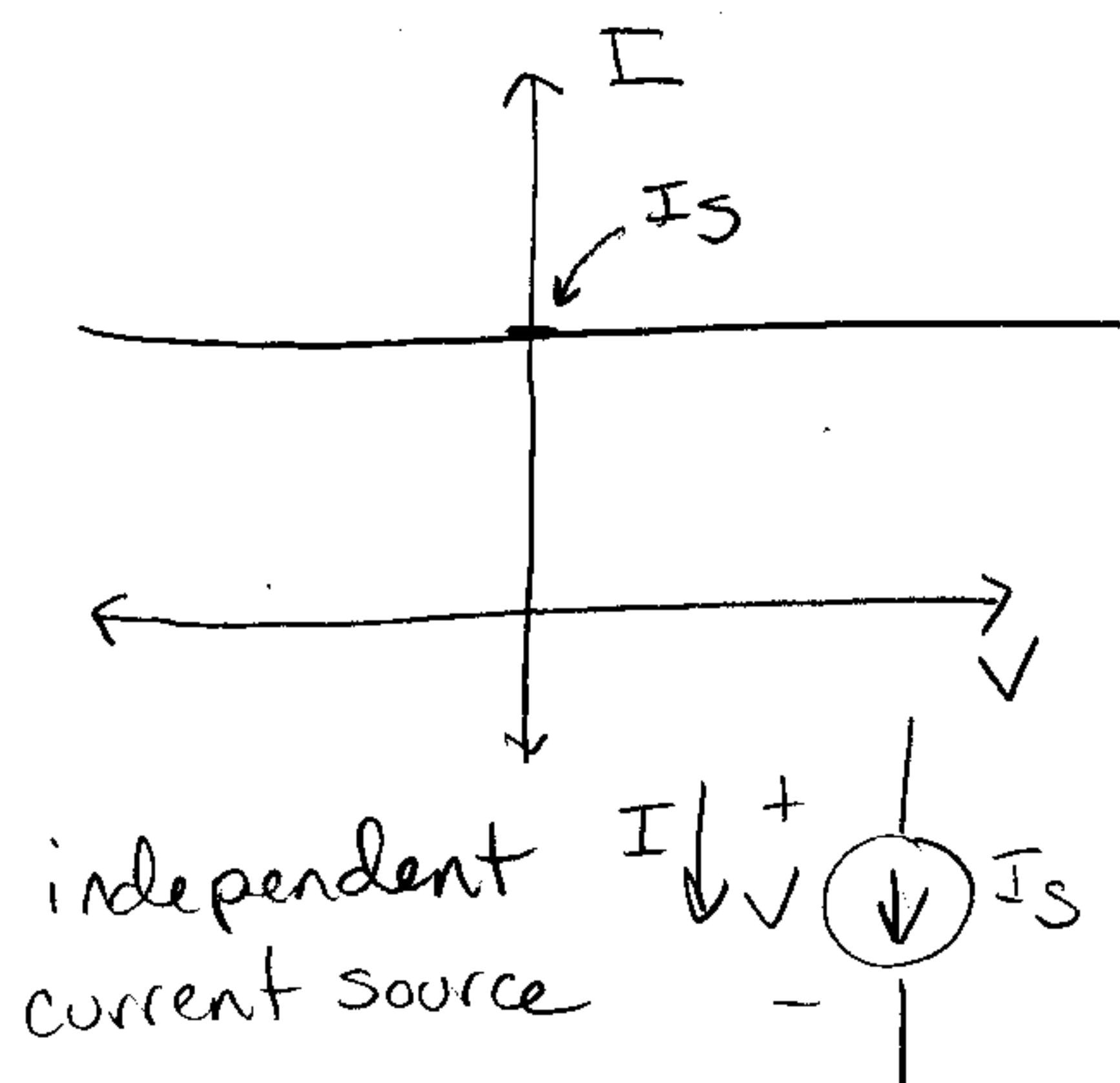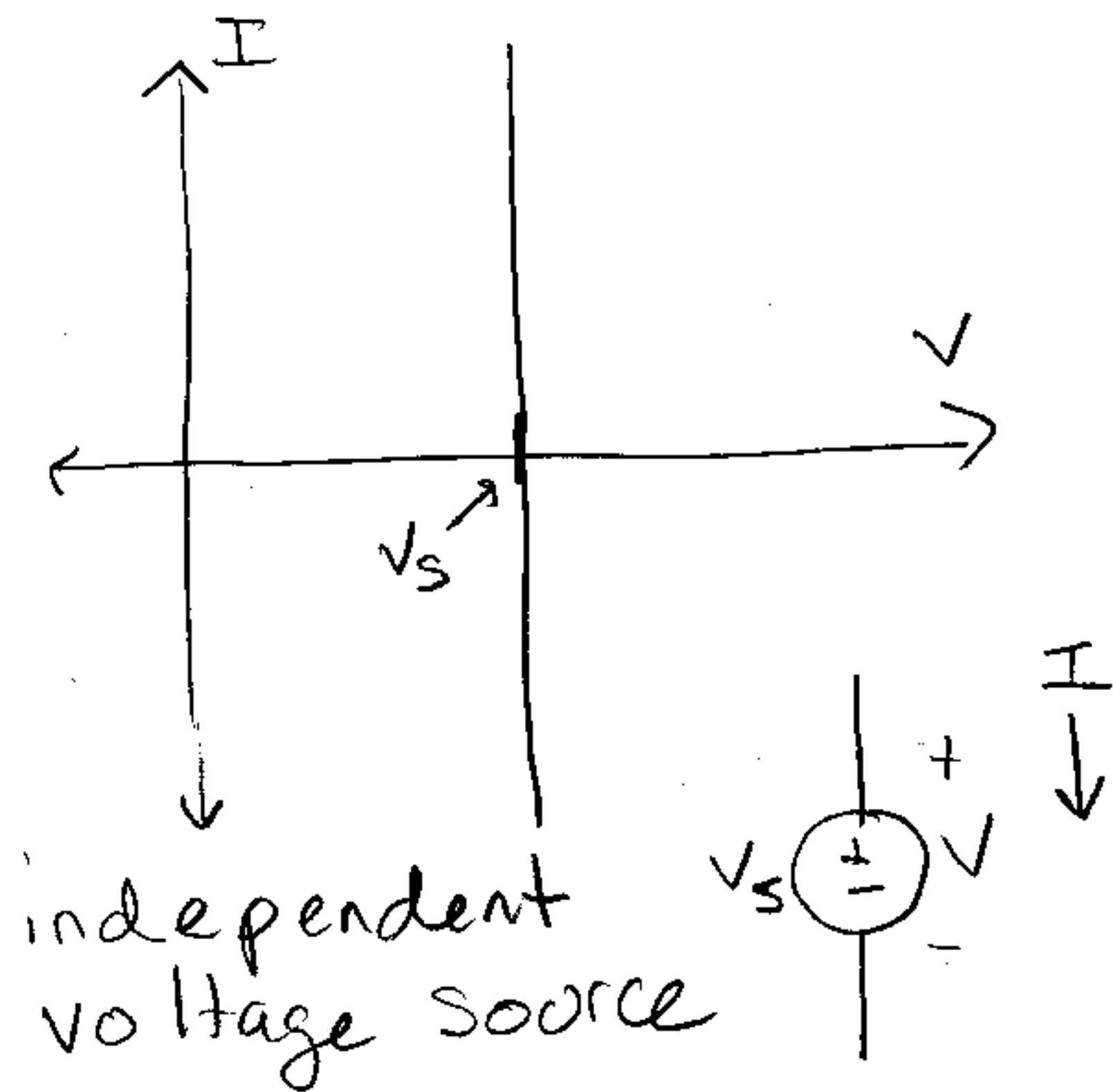We can characterize the I-V relationship that an entire chunk of circuit contributes to the rest of the system, by drawing a graph. Simple examples:




Q2

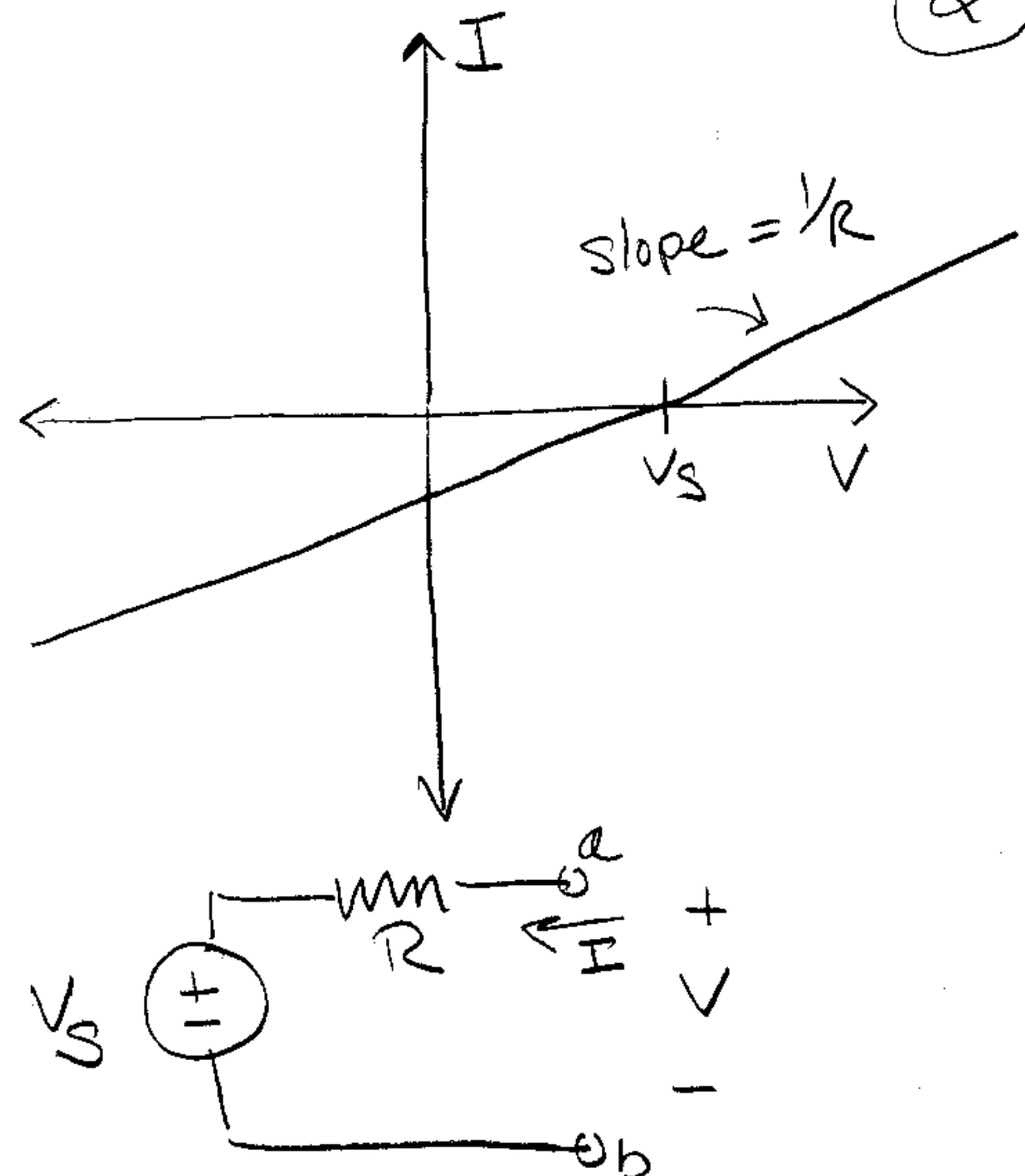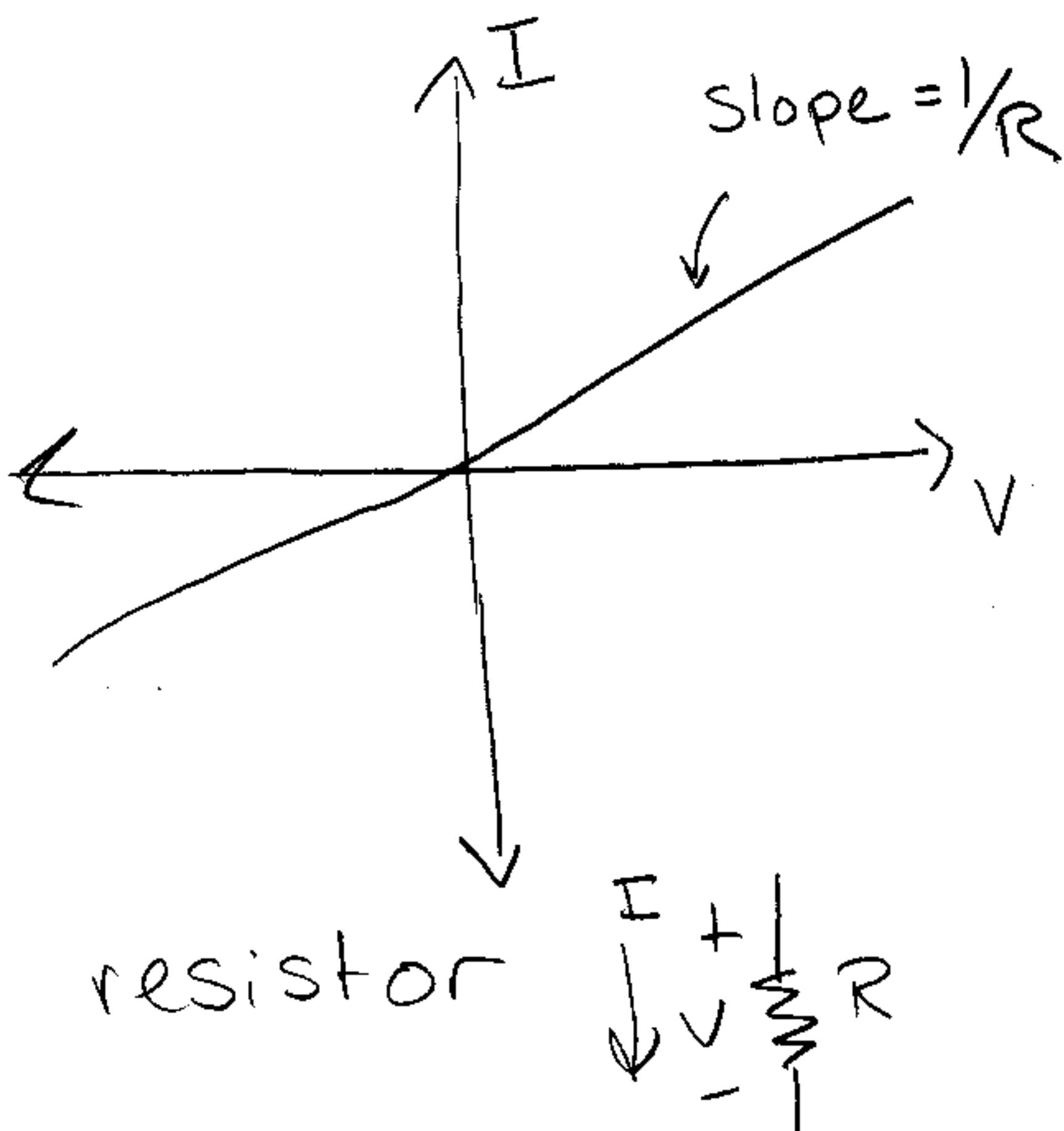


Derive the graph for the voltage source w/resistor's
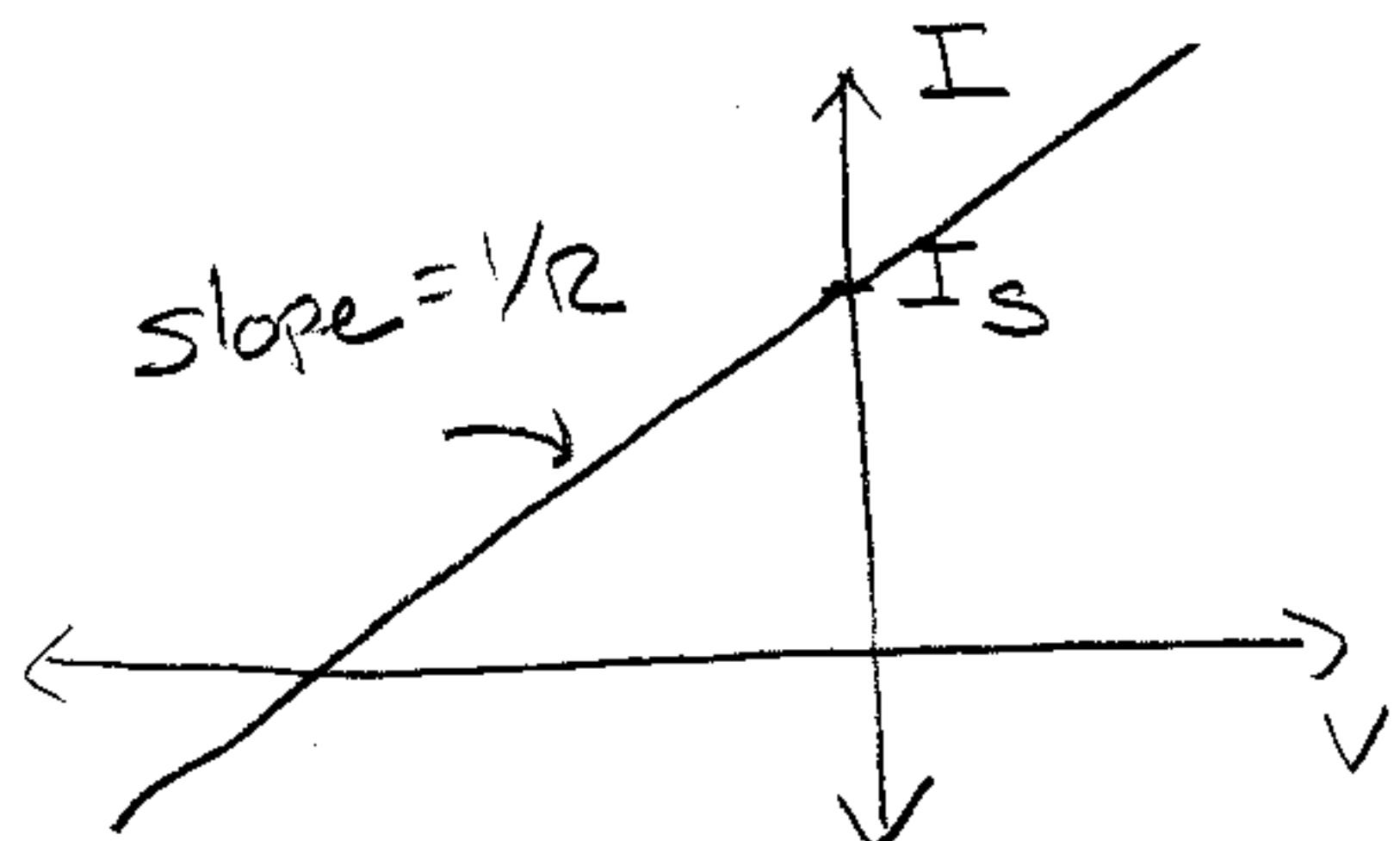
$$-V + IR + V_s = 0 \quad I = \frac{V - V_s}{R}$$



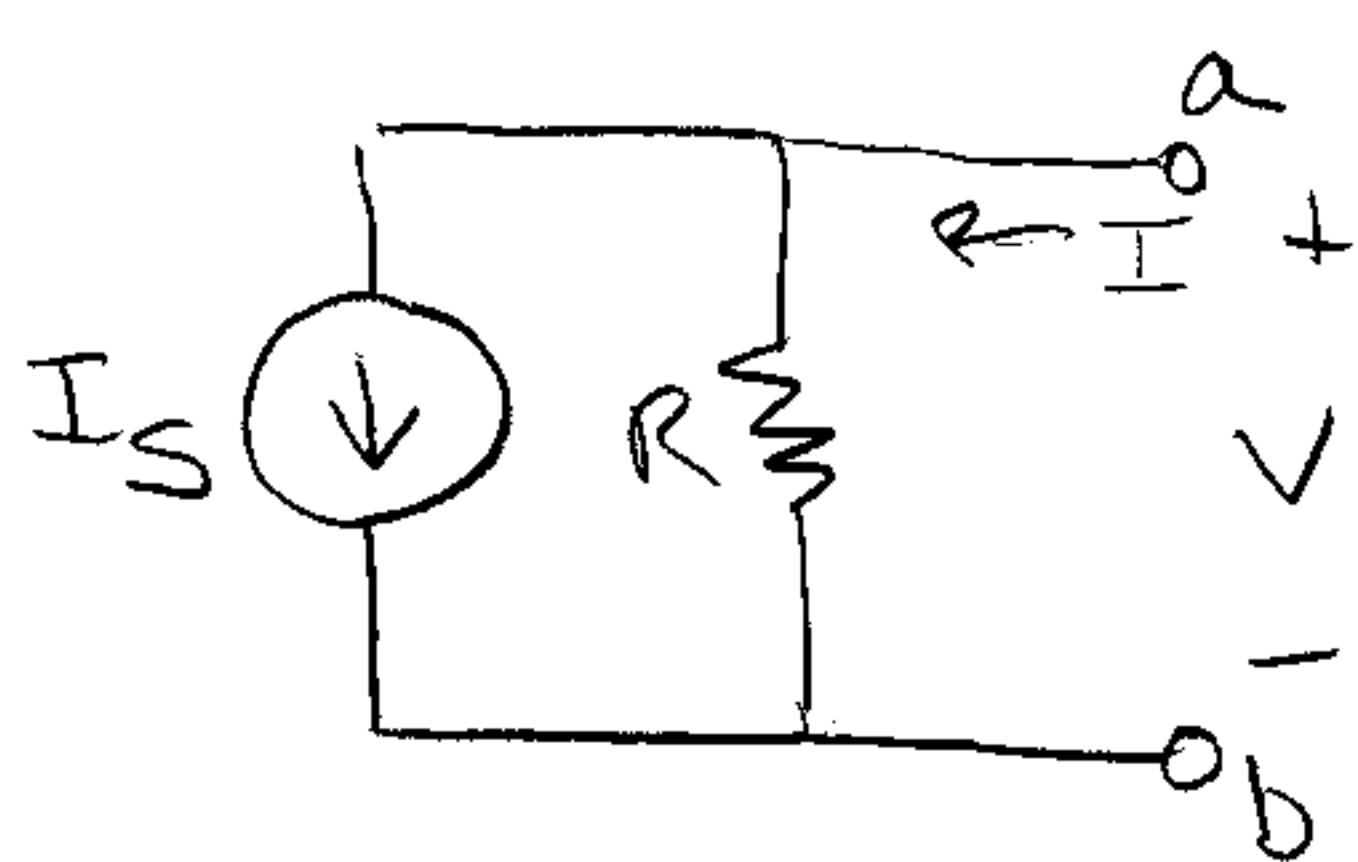Derive the graph for
the current source in parallel
with resistor's






$$I = I_s + \frac{V}{R}$$

③



If a chunk of a circuit contains only resistors, independent sources, and linear dependent sources, then its I-V relationship will be linear.

You can graph the I-V relationship then, using only 2 current-voltage measurements.

Example:

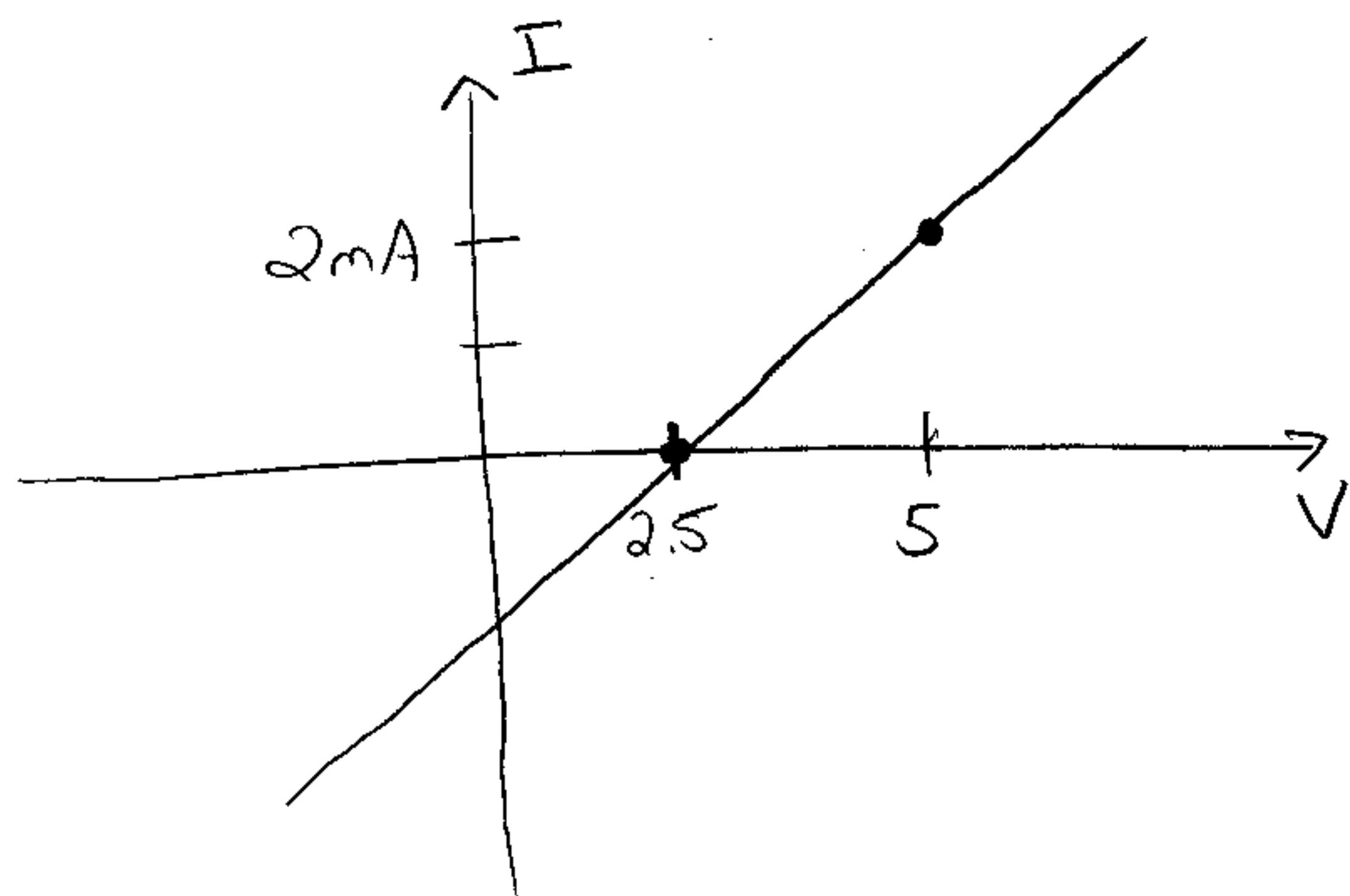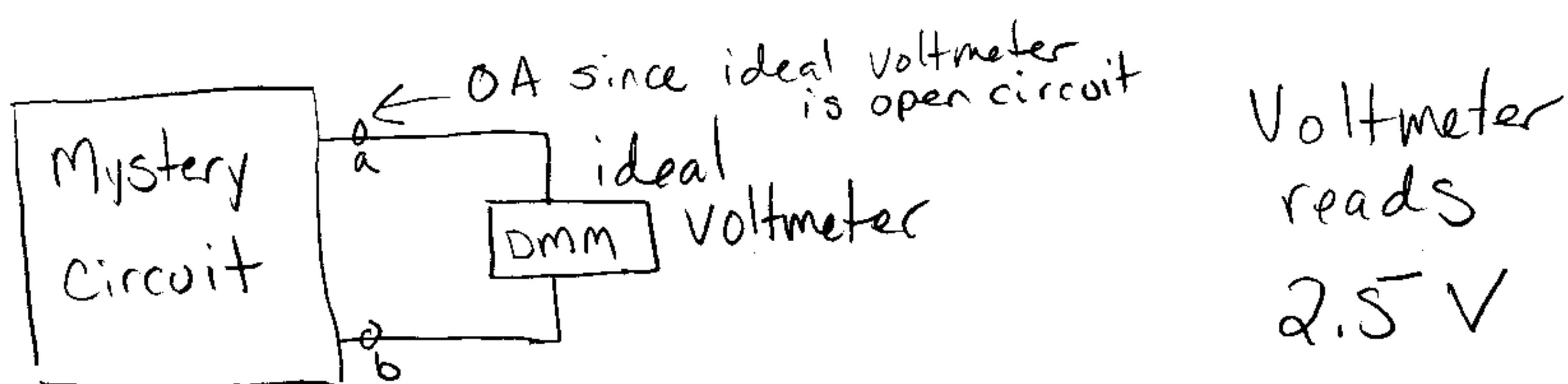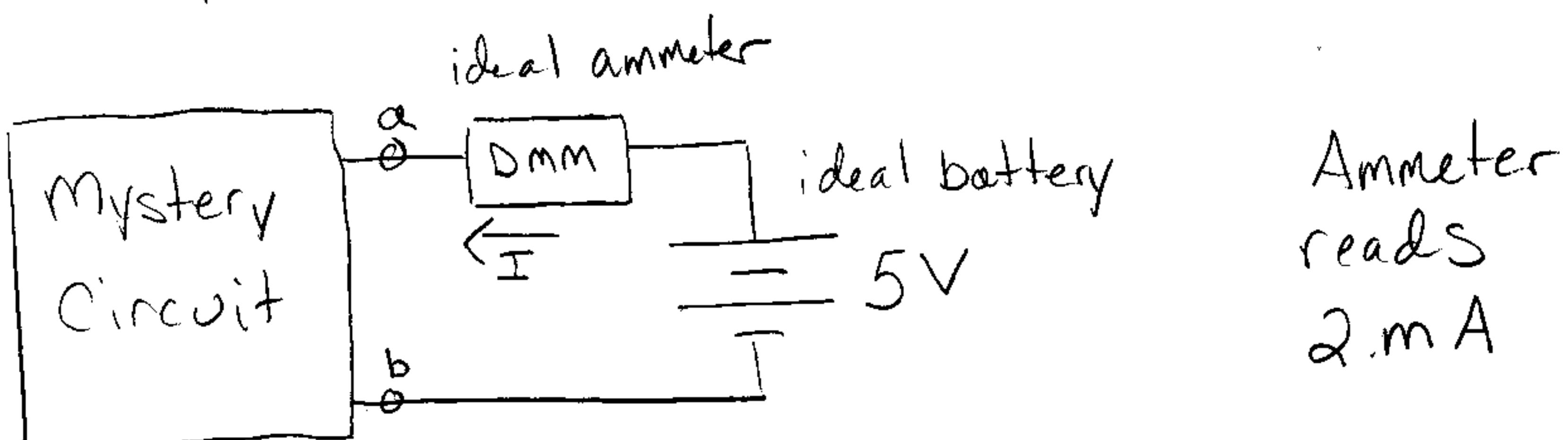

Let's look back at the I-V relationship

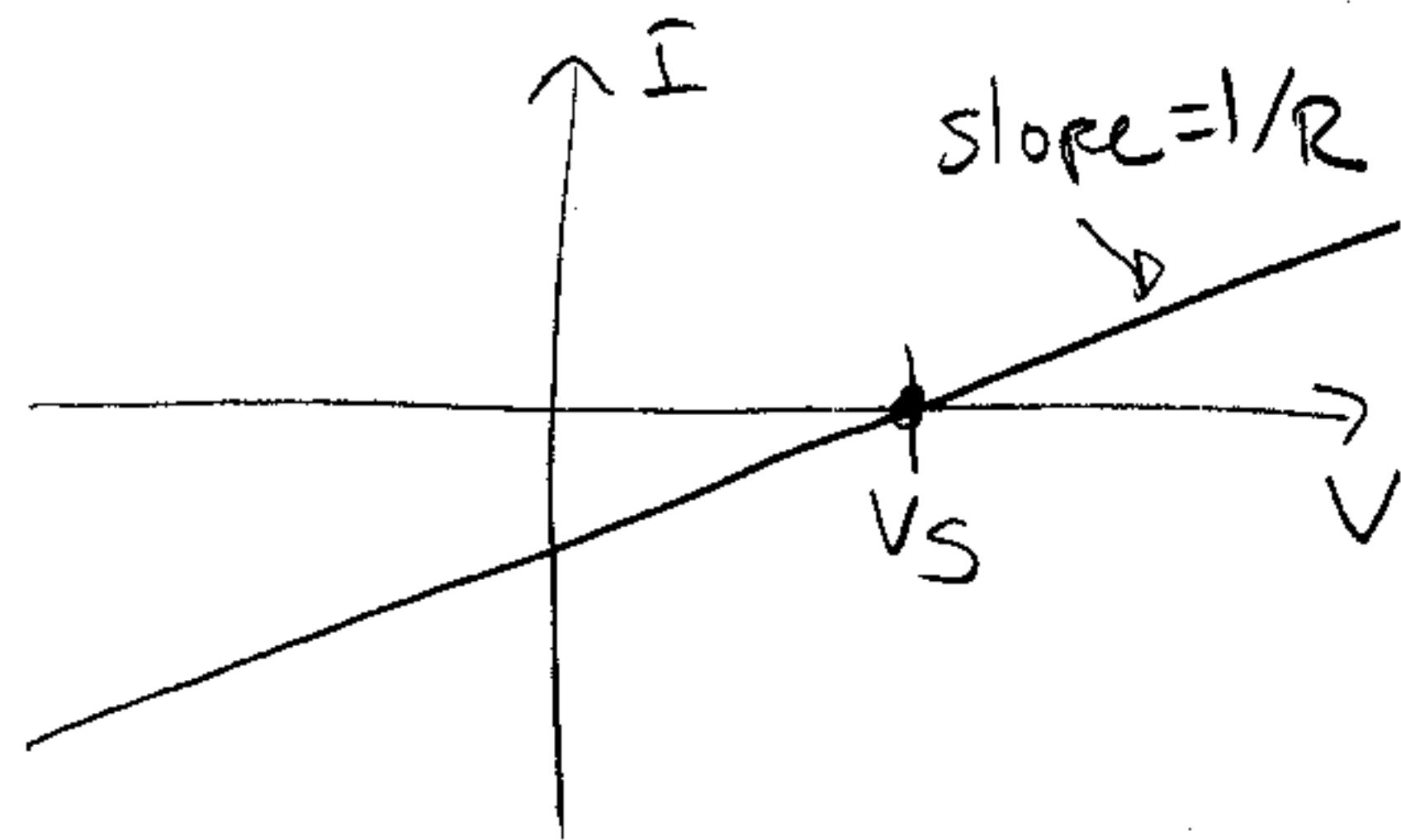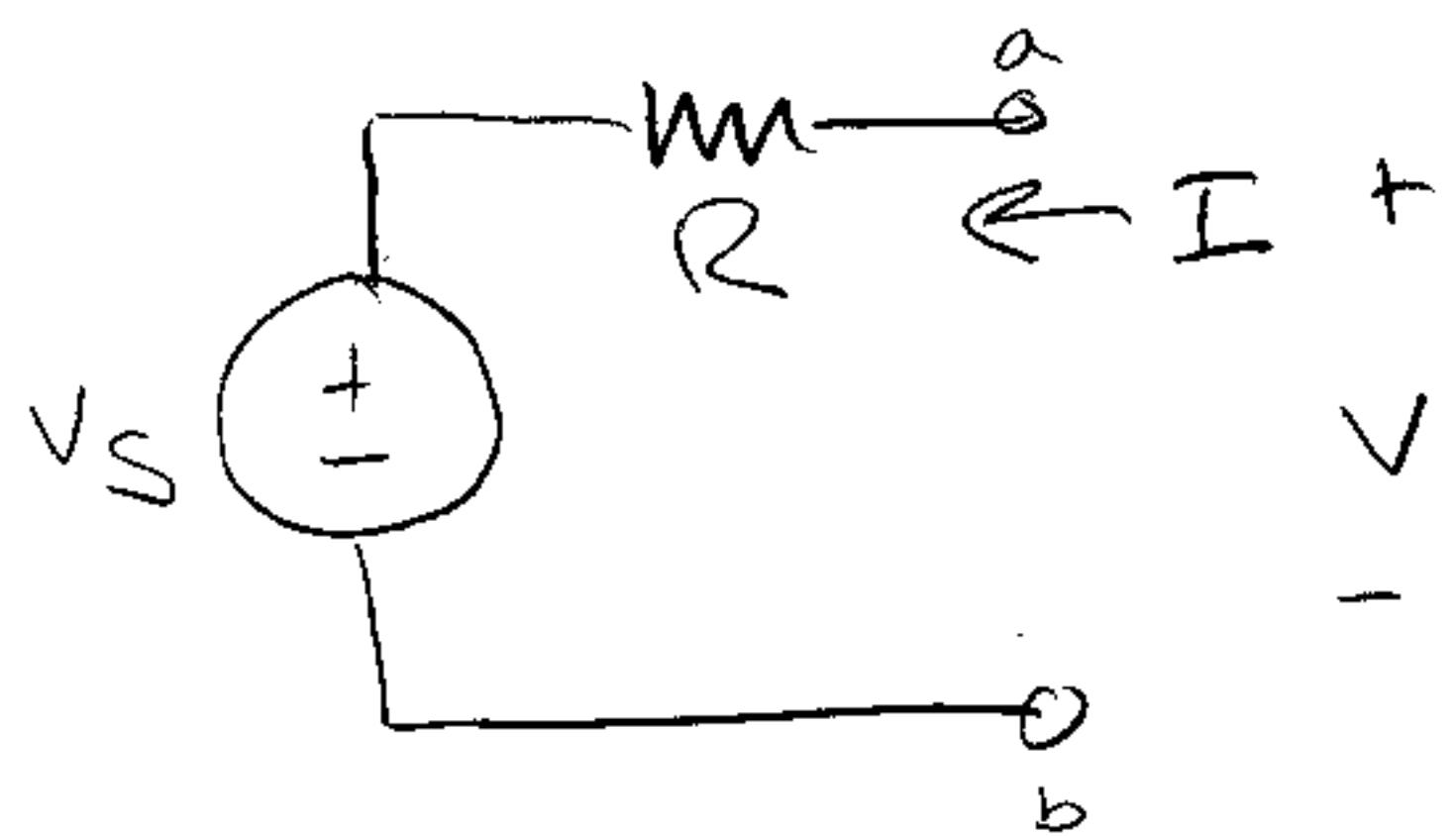

We can replicate any* linear I-V characteristic graph through choice of V_s and R .

This is the Thevenin equivalent circuit.



So the way that a complicated linear circuit interacts with the outside world can be simplified down to the behavior of a voltage source in series with a resistor!

Example: Voltage source in lab. Inside, very complicated! But you only care how it interacts with your circuit. To you, it is an ideal voltage source in series with a small resistance.

* What is the exception?

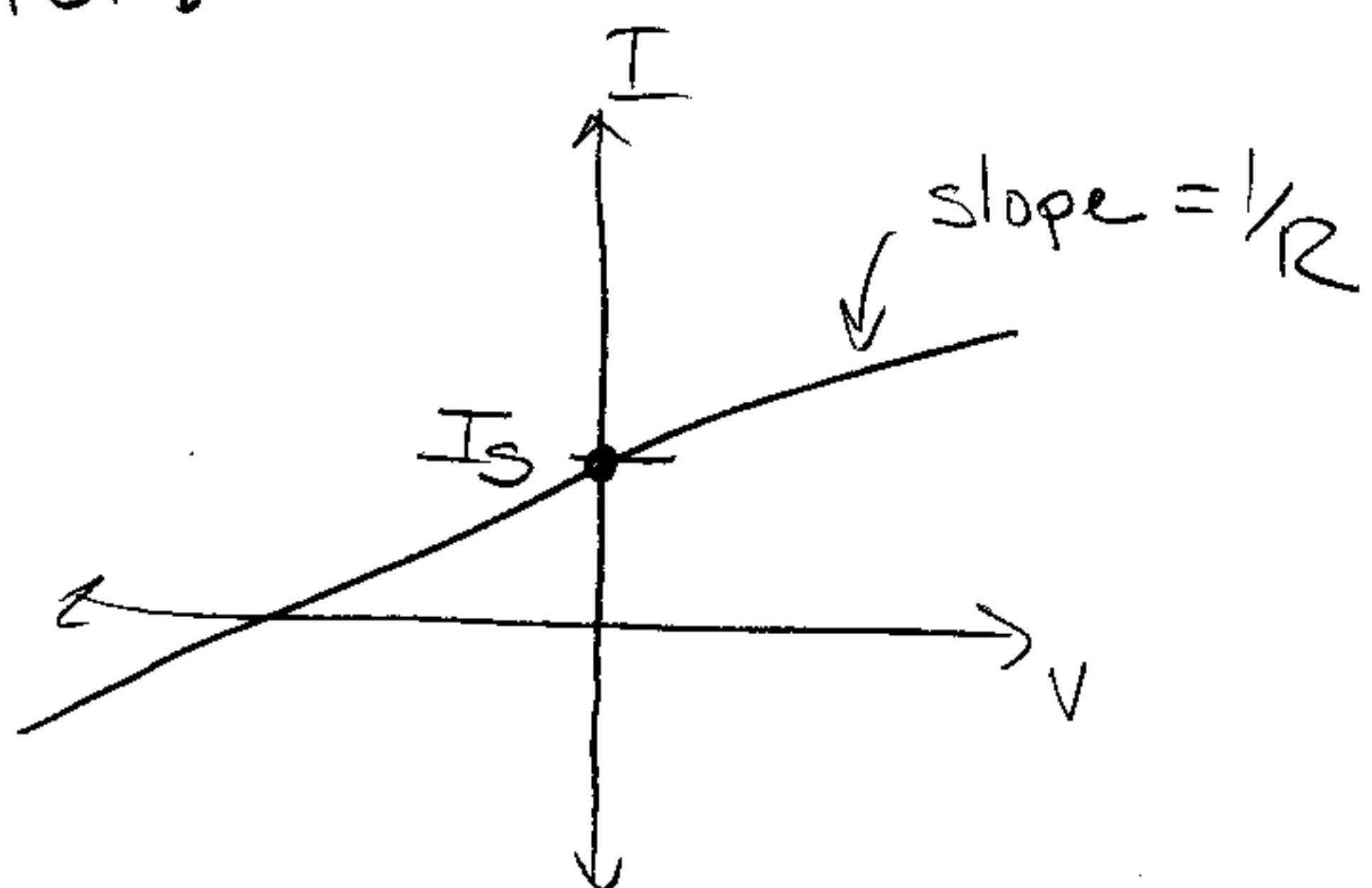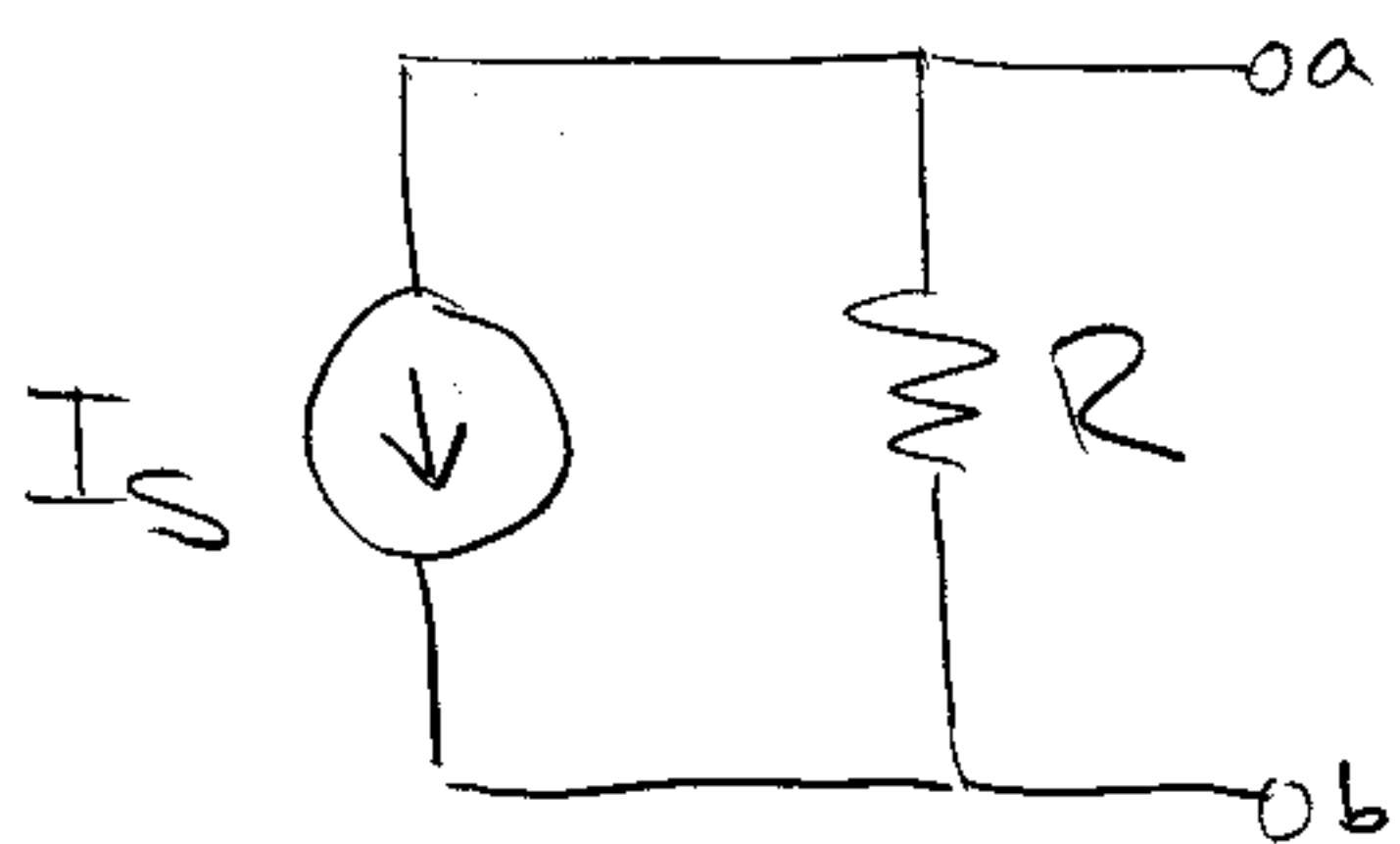(5)

Let's also revisit the current source in parallel with the resistor.




We can also replicate any* linear circuit through choice of I_S and R .

This is the Norton equivalent circuit.

The Thevenin equivalent voltage and resistance are called V_T and R_T , respectively.

The Norton equivalent current and resistance are called I_N and R_N , respectively.

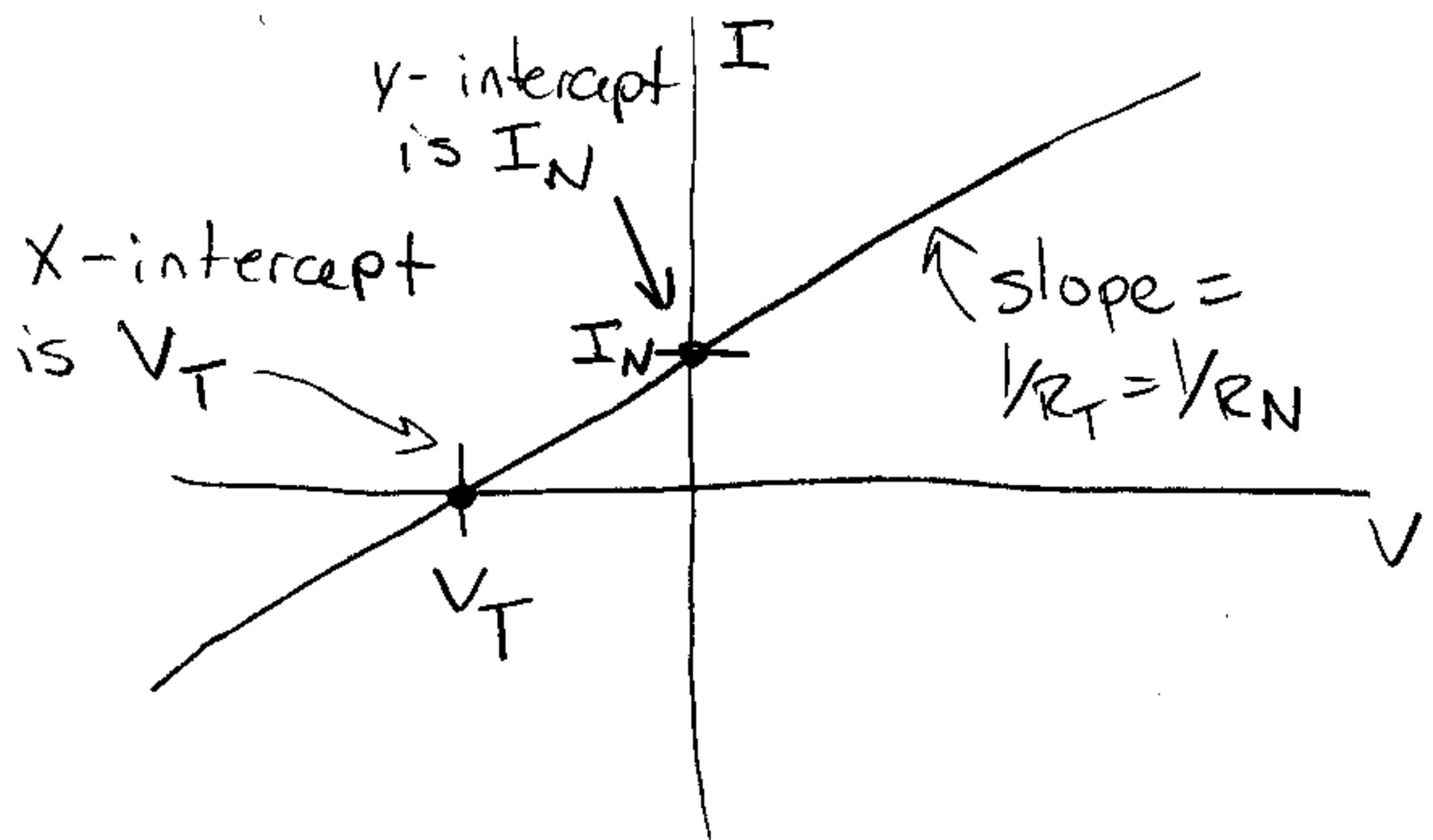Find them on the graph or analytically or measuring:



$$V_T = V_{ab} \text{ when } a-b \text{ open}$$

(then $I = 0$)


$$I_N = I_{b \rightarrow a} \text{ when } a-b \text{ shorted}$$

(then $V = 0$)

$$R_T = R_N = -\frac{V_T}{I_N}$$

(6)

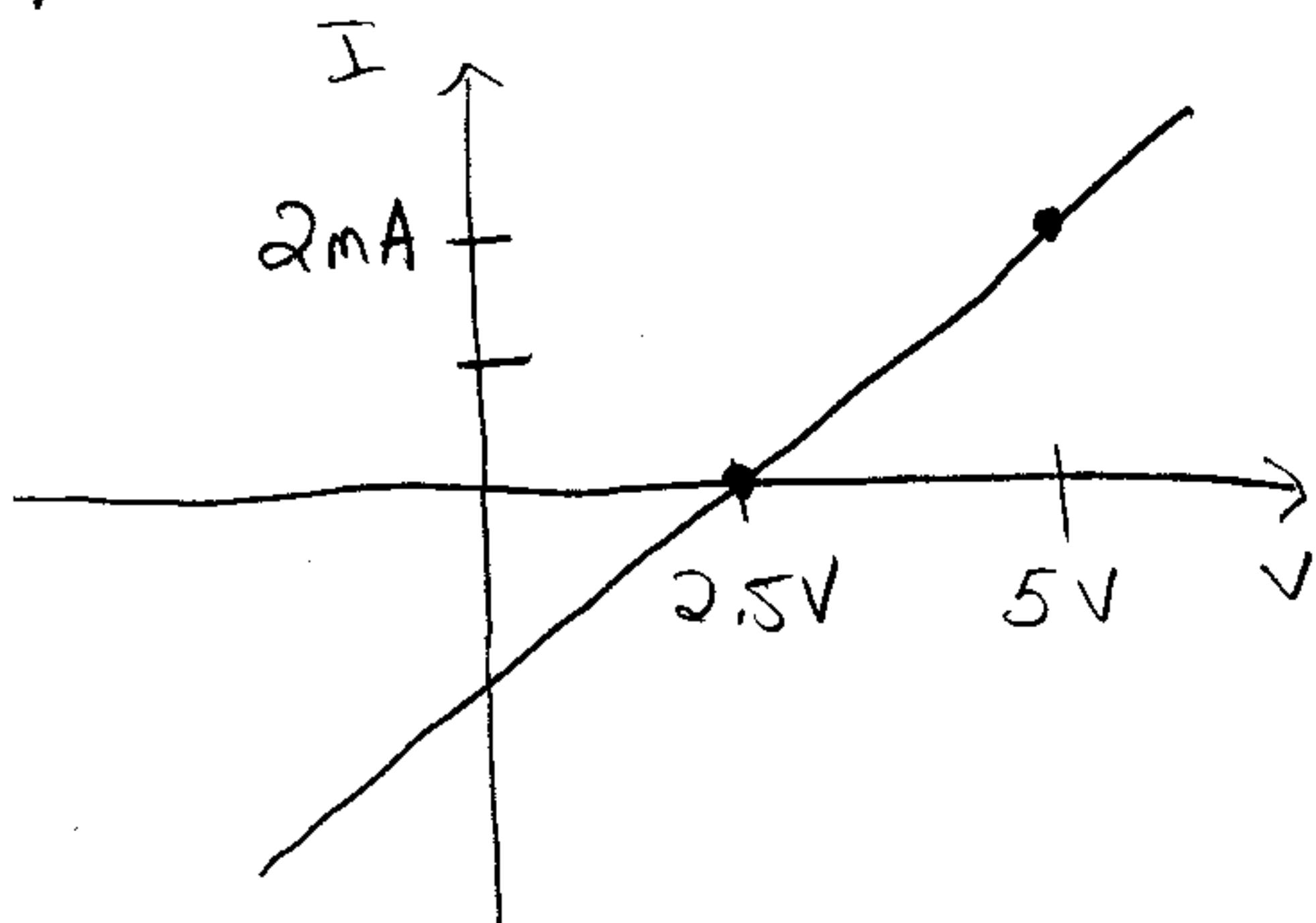Example: Find the Thevenin and Norton equivalents for our "mystery circuit" from before.





Equation for line:

$$I = \frac{2\text{mA}}{5-2.5\text{V}}(V - 2.5\text{V}) \\ = 0.8\text{mS}V - 2\text{mA}$$

$$x\text{-intercept} = V_T = 2.5\text{V}$$


$$y\text{-intercept} = I_N = -2\text{mA}$$
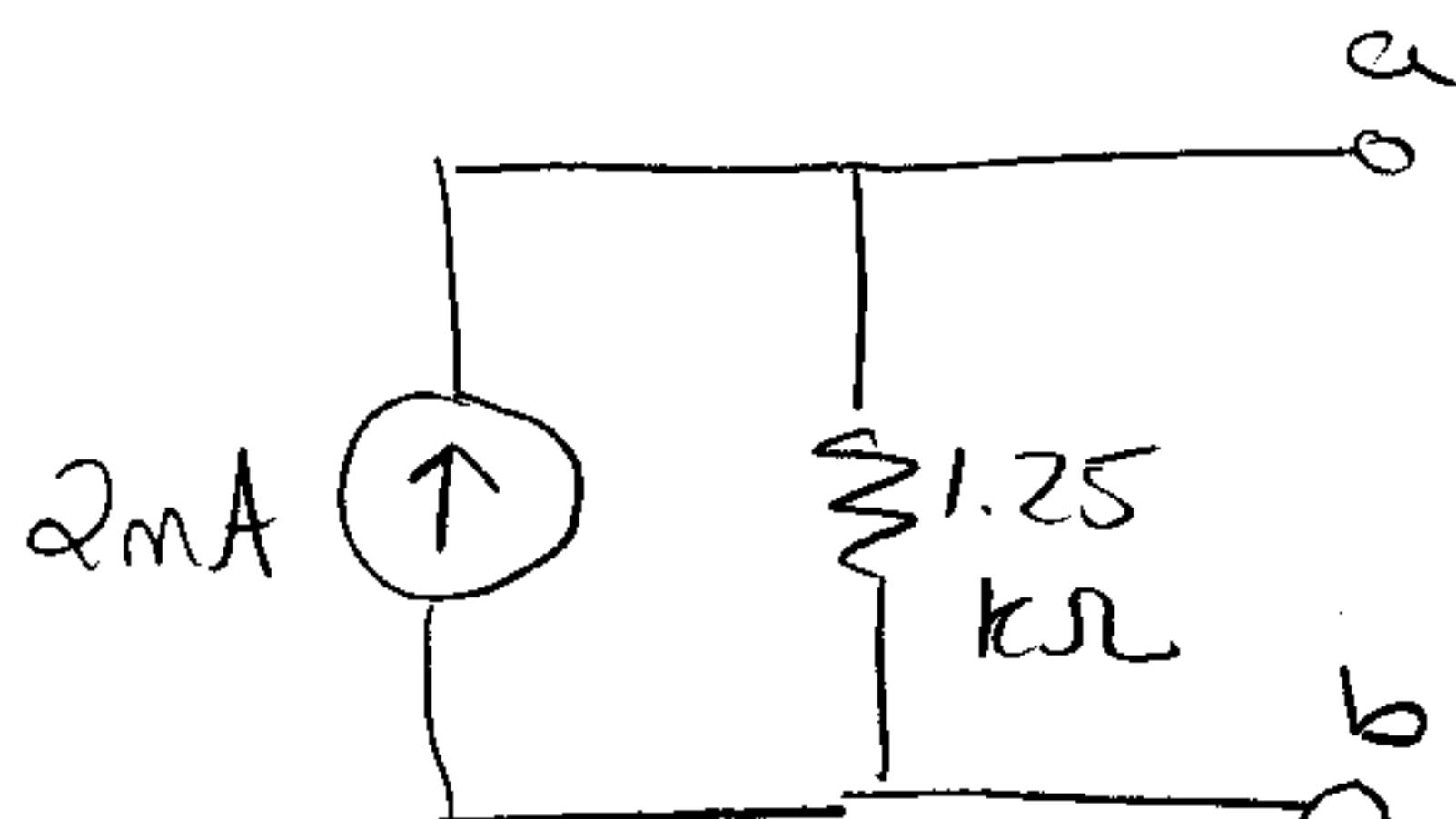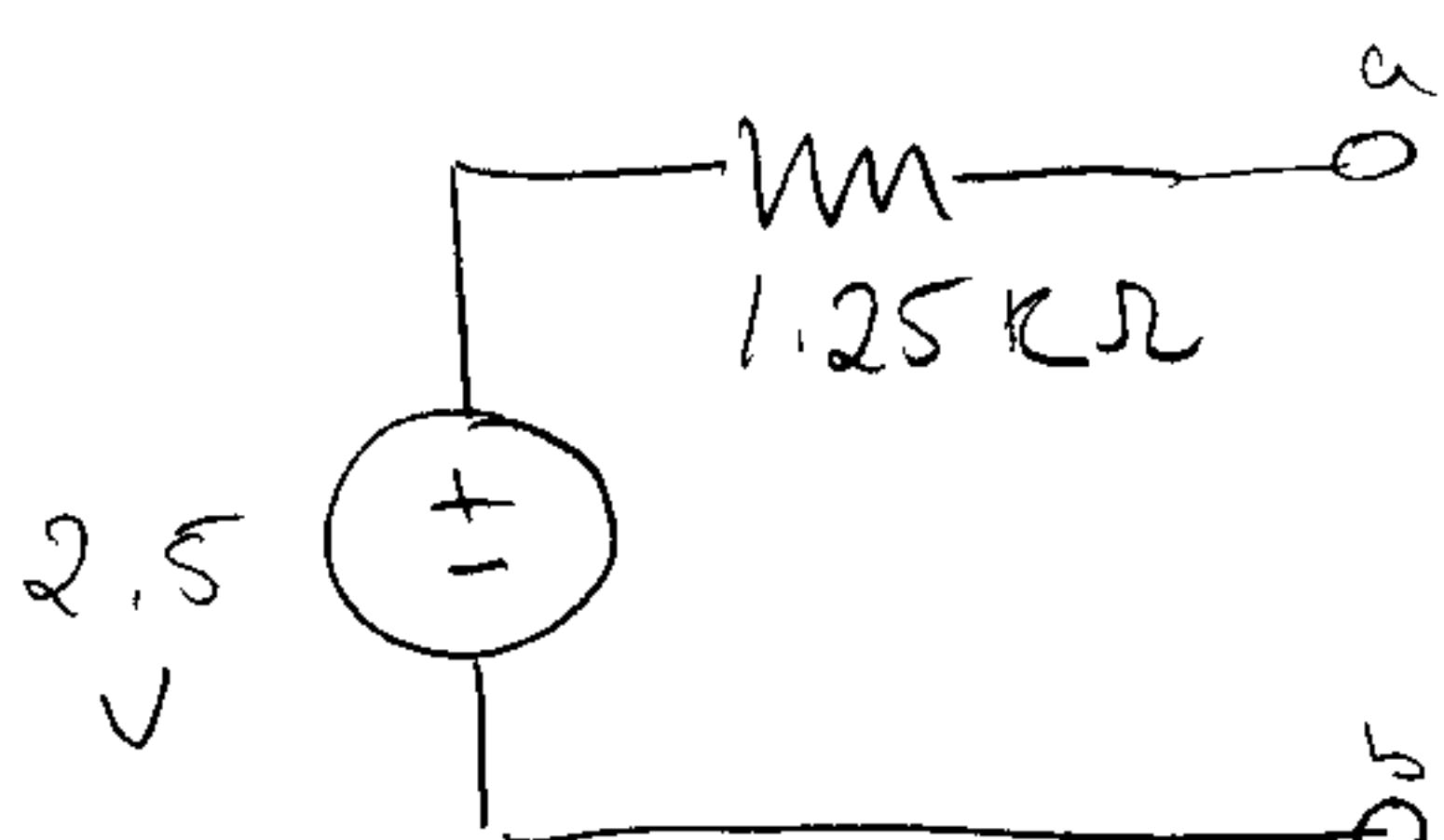
$$\text{slope} = \frac{1}{R_N} = \frac{1}{R_T} = 0.8\text{mS} \Rightarrow R_N = R_T = 1.25\text{k}\Omega$$



7

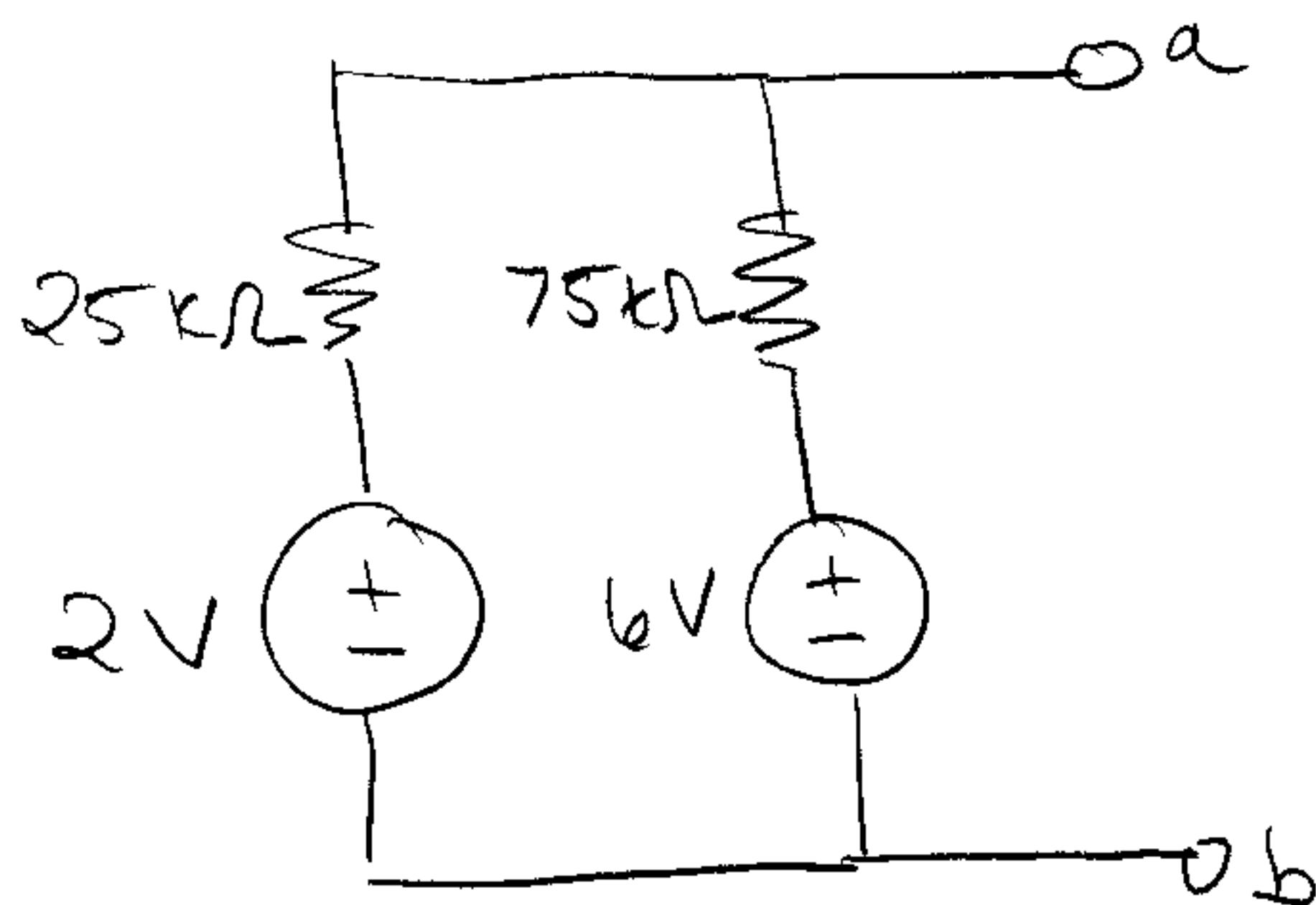Example: Find the Thevenin and Norton equivalents for the following:



$$V_T = V_{ab} \text{ when } a-b \text{ open}$$

Nodal analysis: b is ground

$$\frac{V_a - 2}{25k} + \frac{V_a - 6}{75k} = 0 \quad V_a = V_{ab} = 3V$$

$$I_N = I_{b \rightarrow a} \text{ when } a-b \text{ shorted}$$

$$\text{KVL: } 25I_1 + 2 = 0 \quad 75I_2 + 6 = 0$$


$$I_1 = -80\mu A \quad I_2 = -80\mu A$$

$$I_N = I_1 + I_2 = -160\mu A$$

$$R_T = R_N = -\frac{V_T}{I_N} = -\frac{3V}{-160\mu A} = 18.75k\Omega$$

8

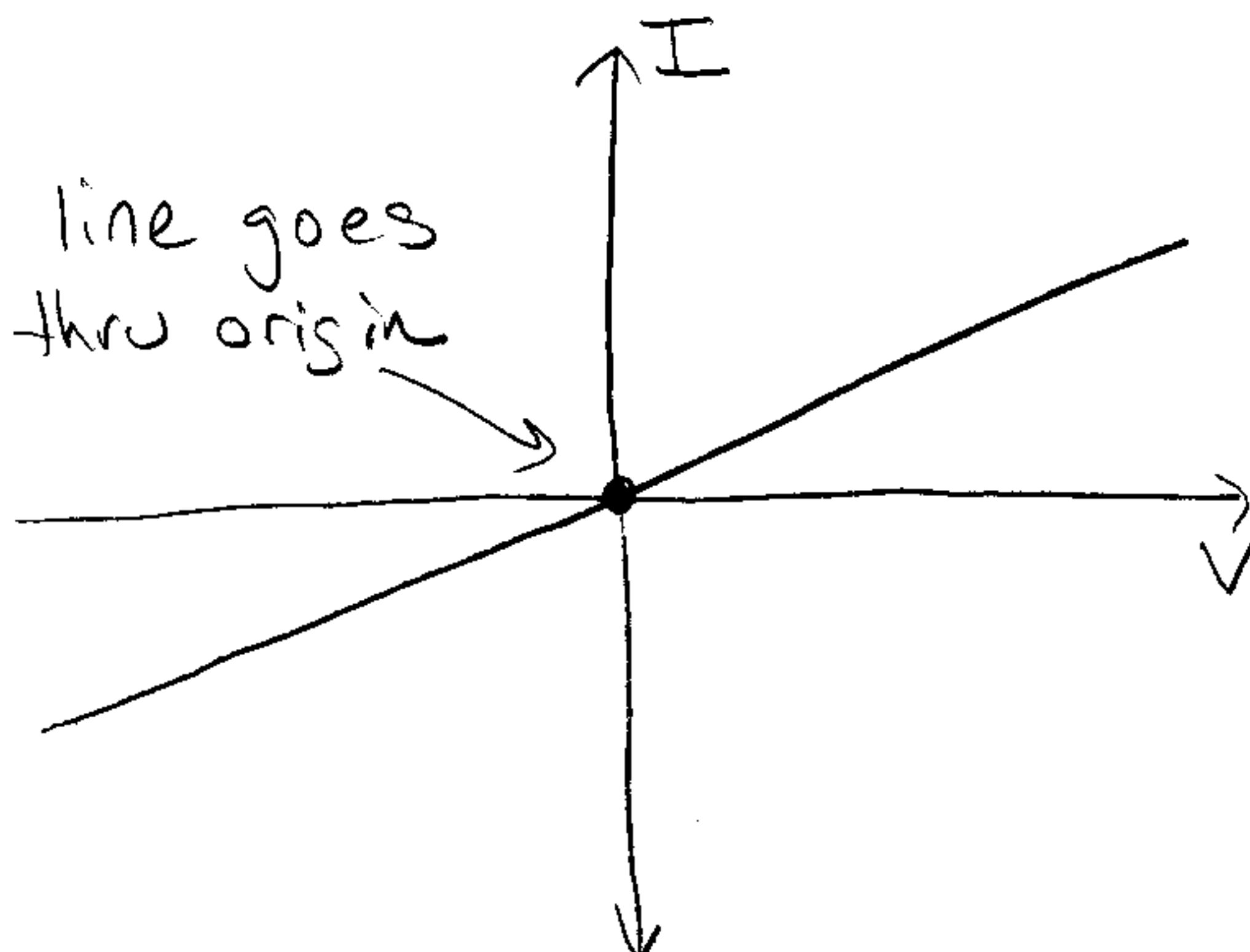
What happens when there are no independent sources?



$$I_N = V_T = 0$$


$$\text{so } R_T = R_N = -\frac{V_T}{I_N}$$

is undefined.

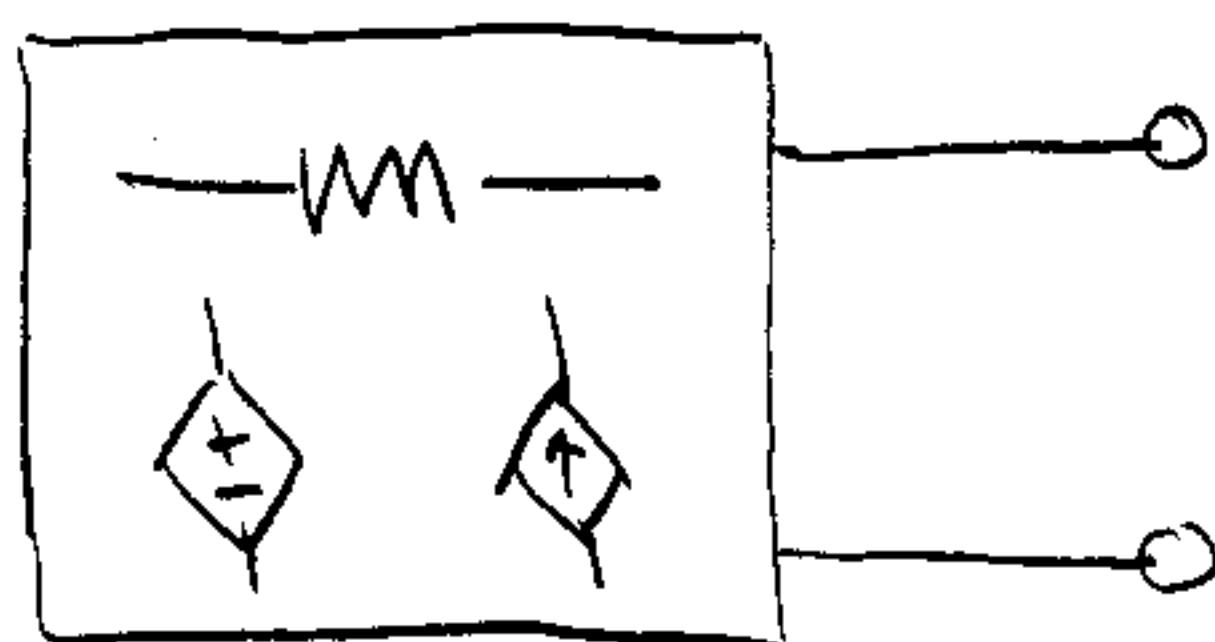

No current, no voltage when left alone.

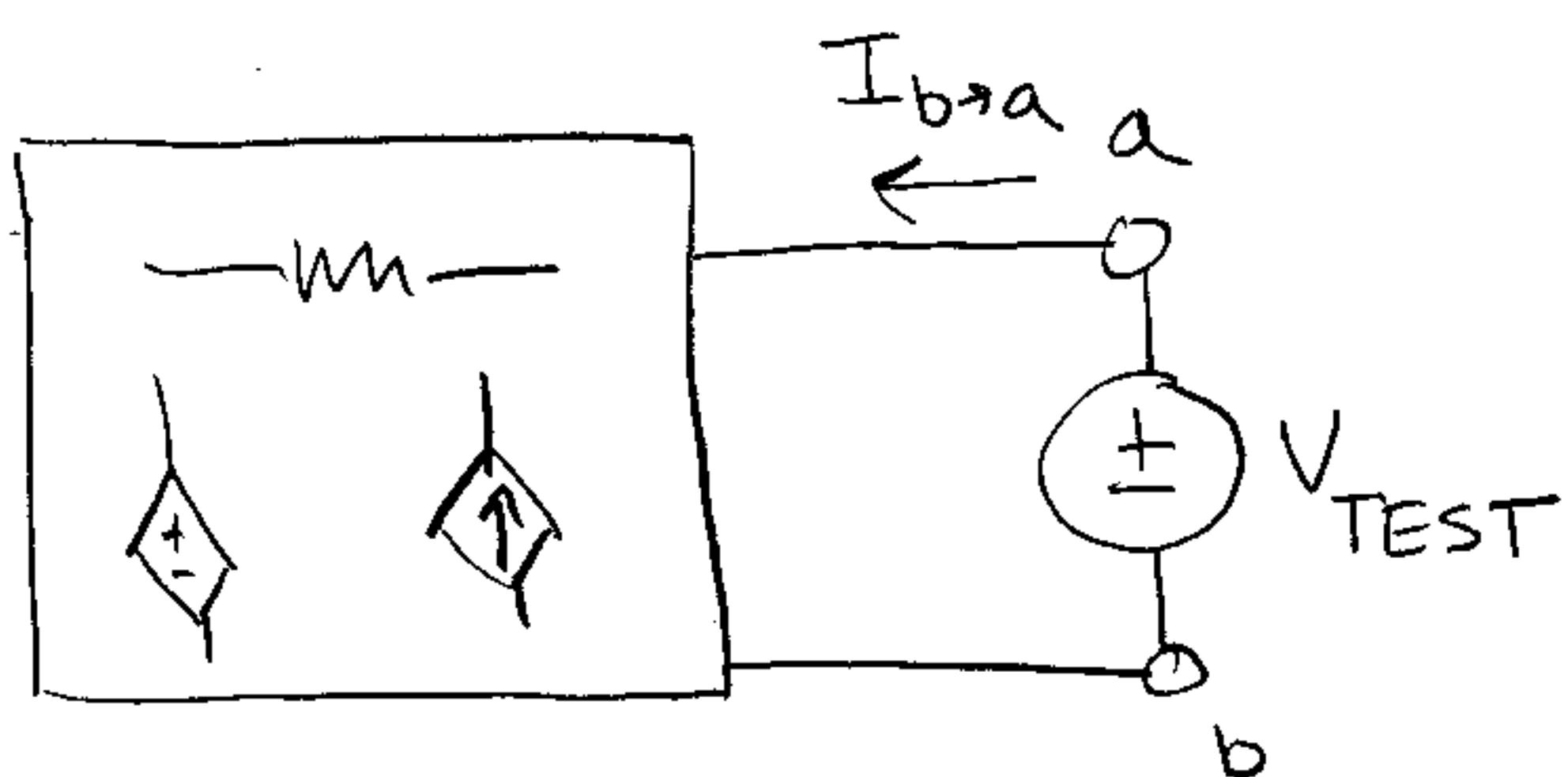Most "excite" circuit with external voltage to see how circuit works!



Apply a "test" voltage, measure $I_{b>a}$.


This gives us a second point on the line.

$$R_T = R_N = \frac{V_{TEST}}{I_{b>a}}$$


If just resistors, easier to find Req.

9

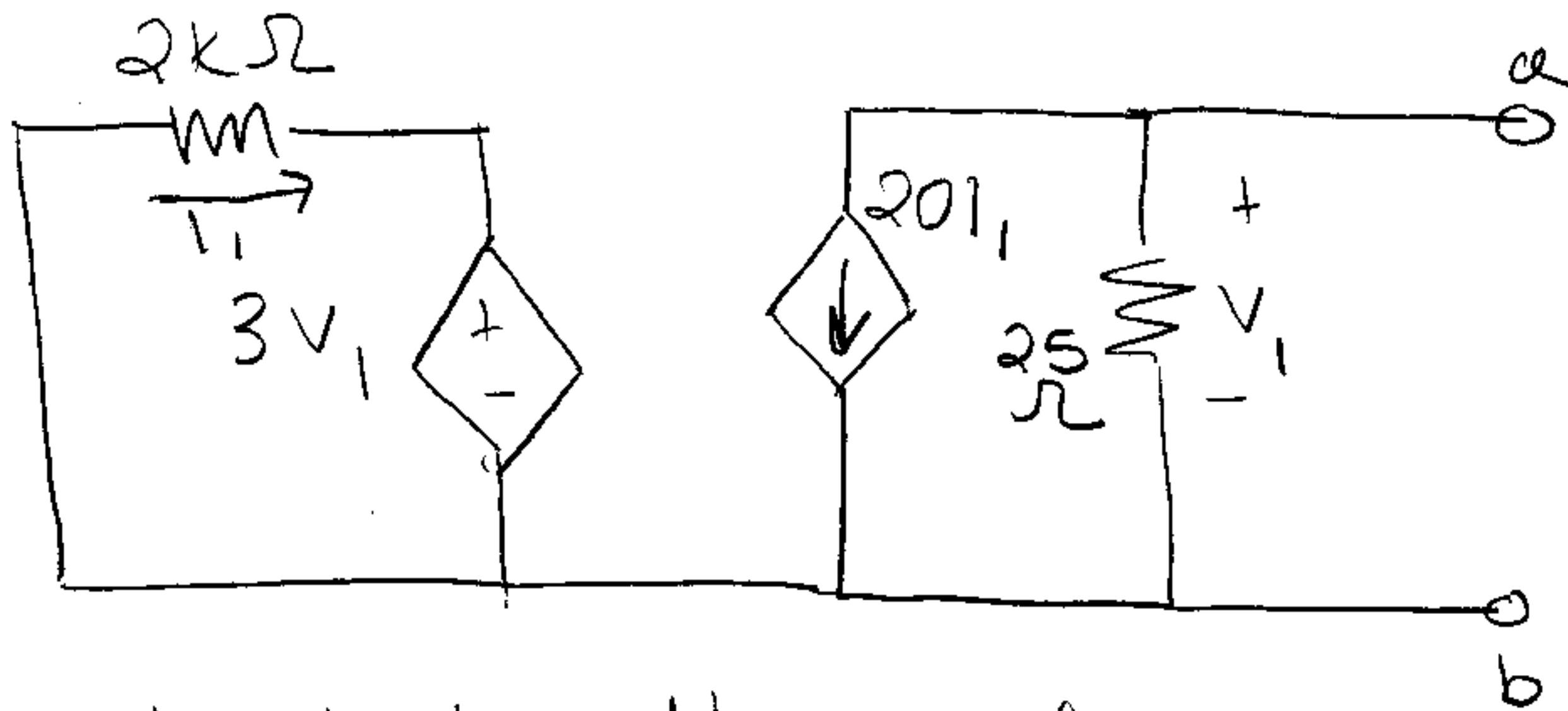Example: Find the Thevenin and Norton equivilents.



Apply test voltage of 1V.

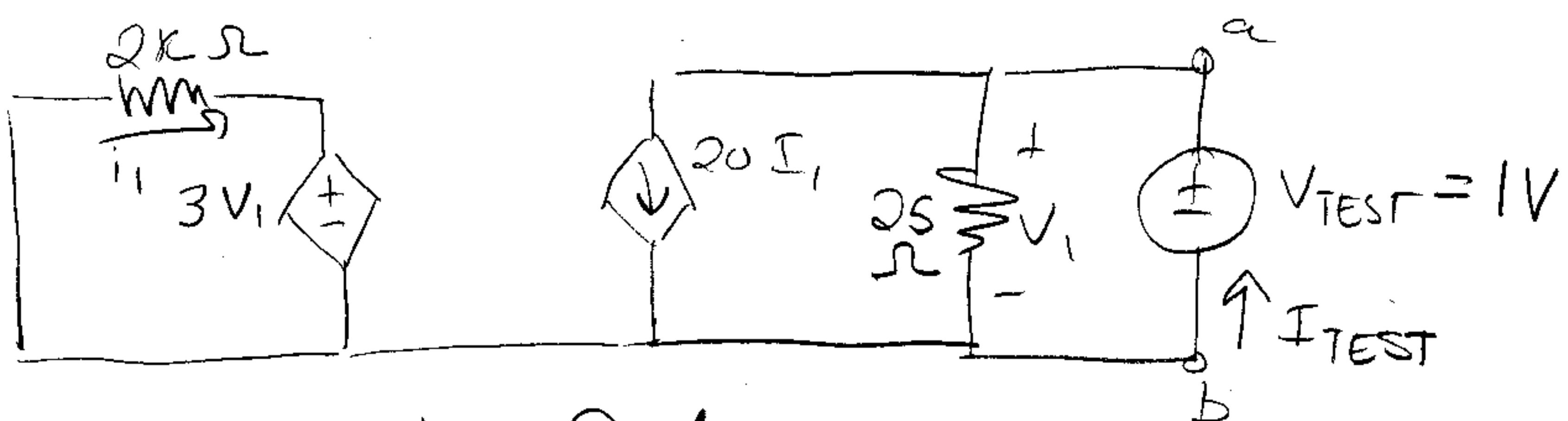

We want to find I_{TEST} .

KCL @ node "a":

$$20I_1 + \frac{V_1}{25} = I_{TEST}$$

$$V_1 = V_{TEST} = 1V$$

How to find I_1 ? KVL at left loop:

$$3V_1 + 2kI_1 = 0 \quad I_1 = -\frac{3}{2k} V_1 = -\frac{3}{2k}$$



$$I_{TEST} = 20\left(-\frac{3}{2k}\right) + \frac{1}{25} = 10mA$$

$$\frac{V_{TEST}}{I_{TEST}} = \frac{1V}{10mA} = \boxed{100\Omega = R_T = R_N}$$



$$V_T = 0V \quad I_N = 0A$$

Some tricks to make things easier:

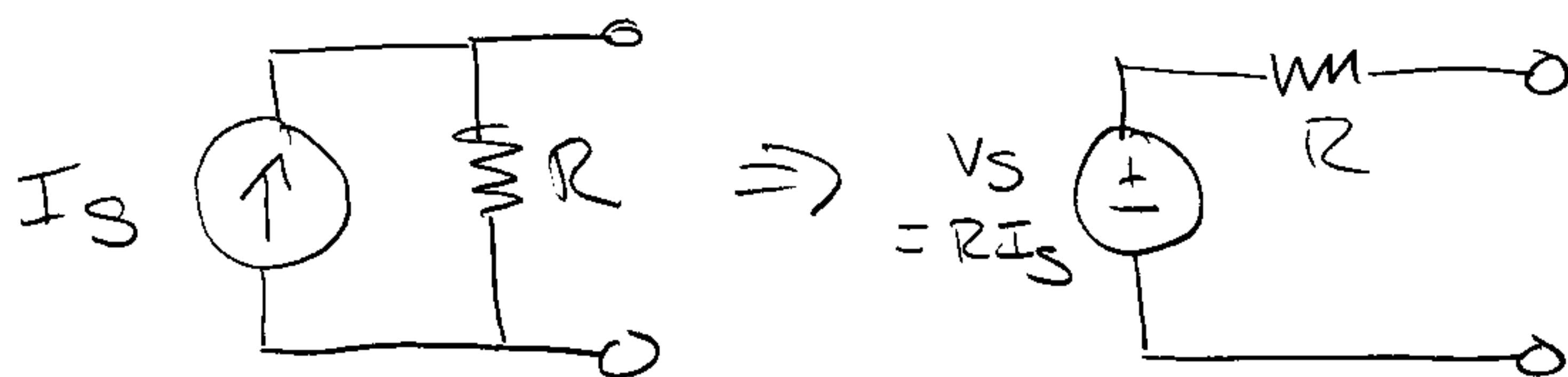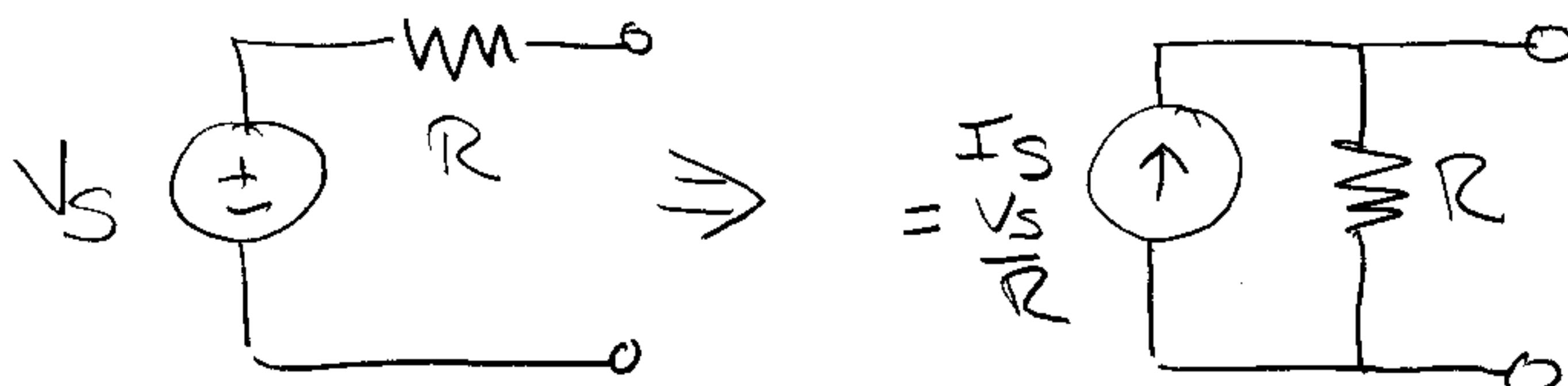Trick #1: Exploit the "duality" of the voltage source-resistor series and the current source-resistor parallel combo to simplify circuits, aka "Source Transformations"



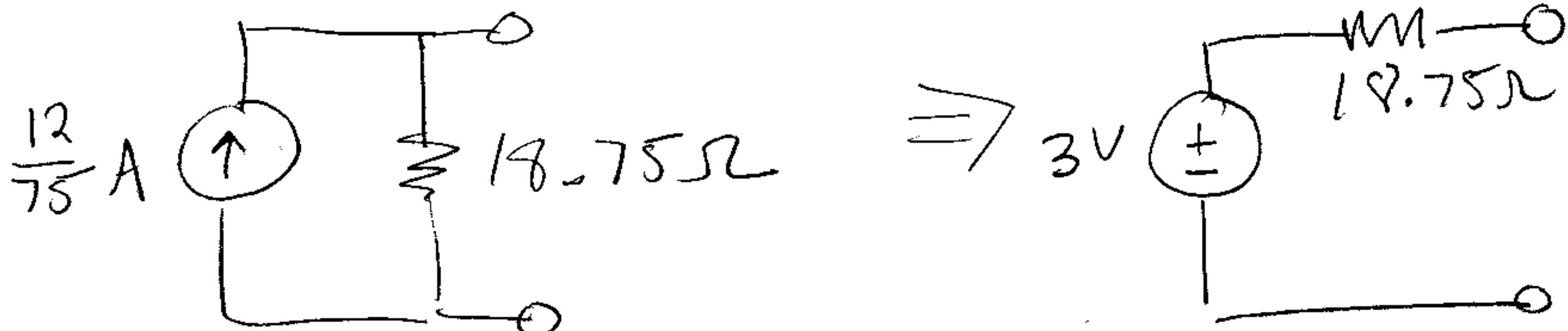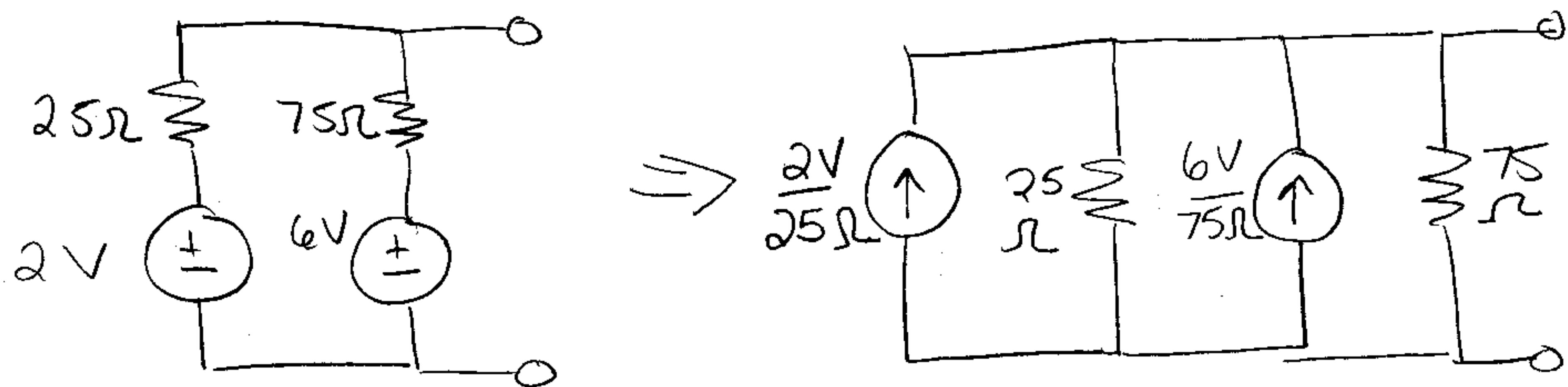Example: Revisit earlier Thevenin/Norton example.



Trick #2: Instead of finding R_T or R_N


Via $- \frac{V_T}{I_N}$, turn off independent

Sources and find R_T or R_N for remainder
of circuit.

This works because the slope of the I-V graph
is not affected by the values of the independent
sources! It depends on resistances/dep sources only.

Suggested use: When there are no dep sources.


Turning off a voltage source:

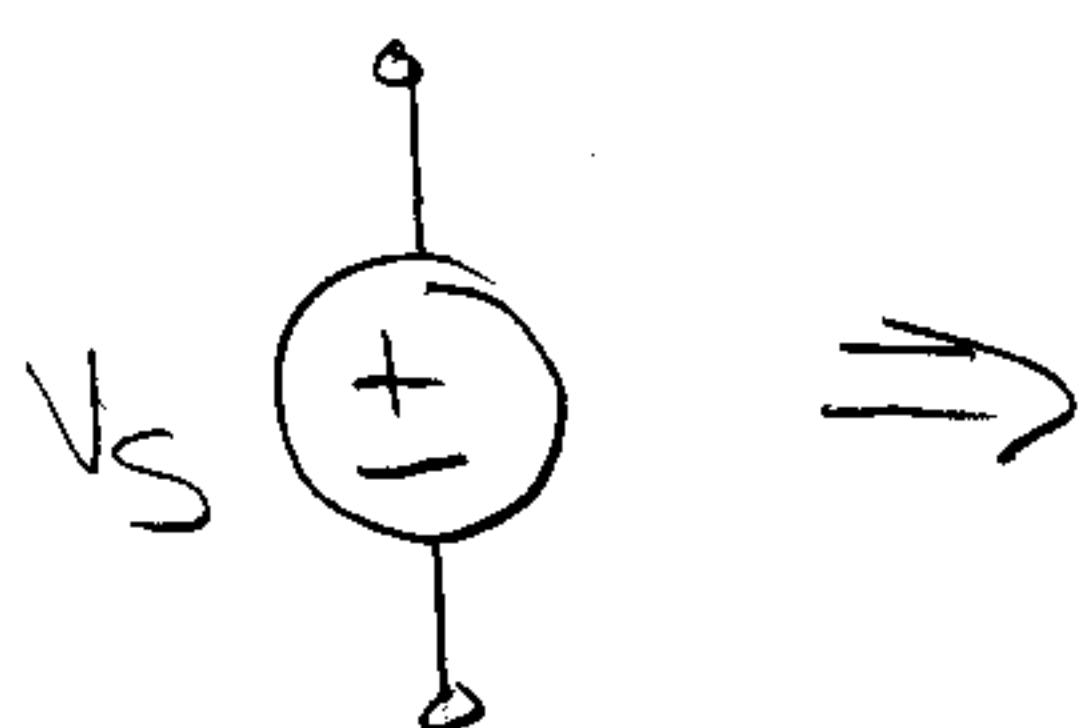

Voltage sources \Rightarrow Short circuit

A wire has zero voltage!

Turning off a current source:


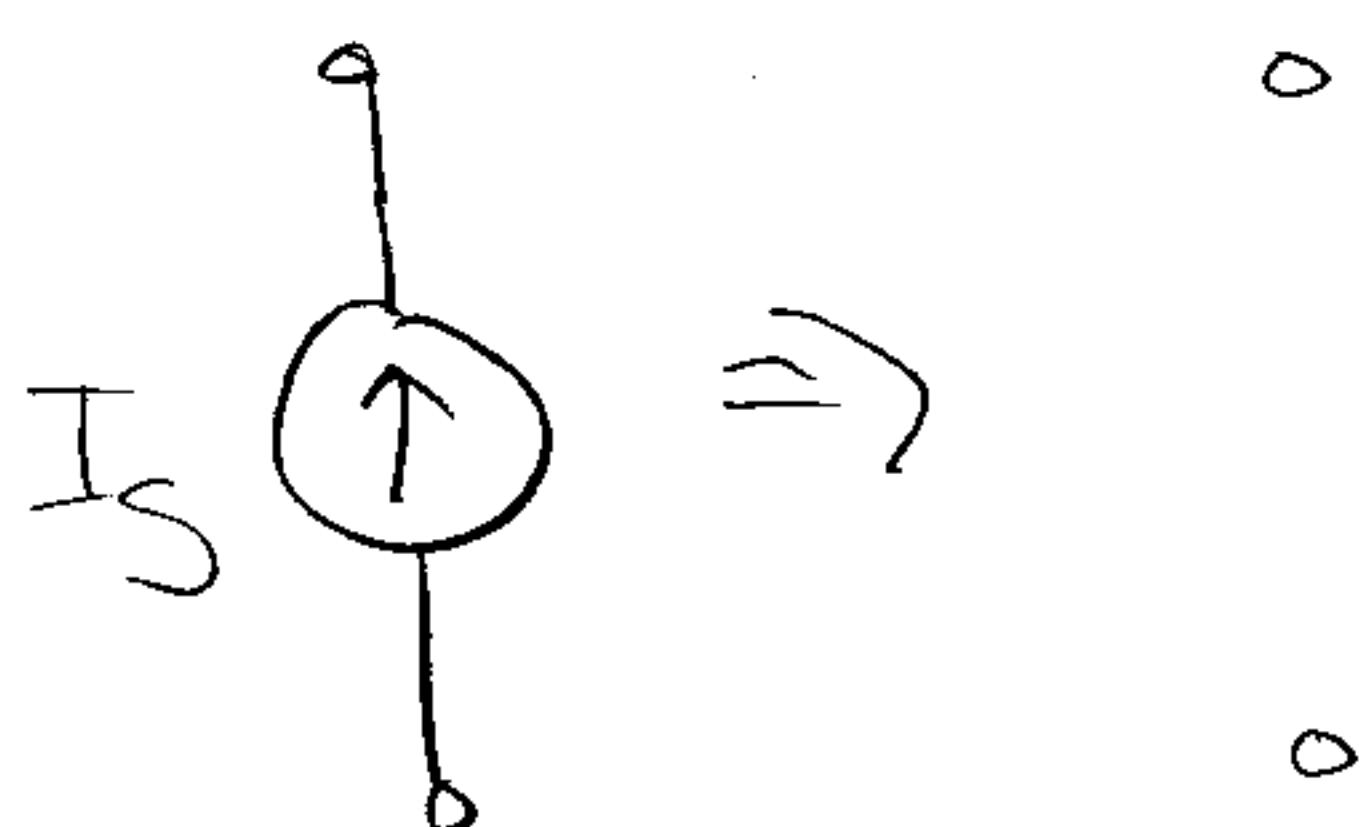


Current sources \Rightarrow open circuit


Air has zero current!

12

Example: Find R_T .

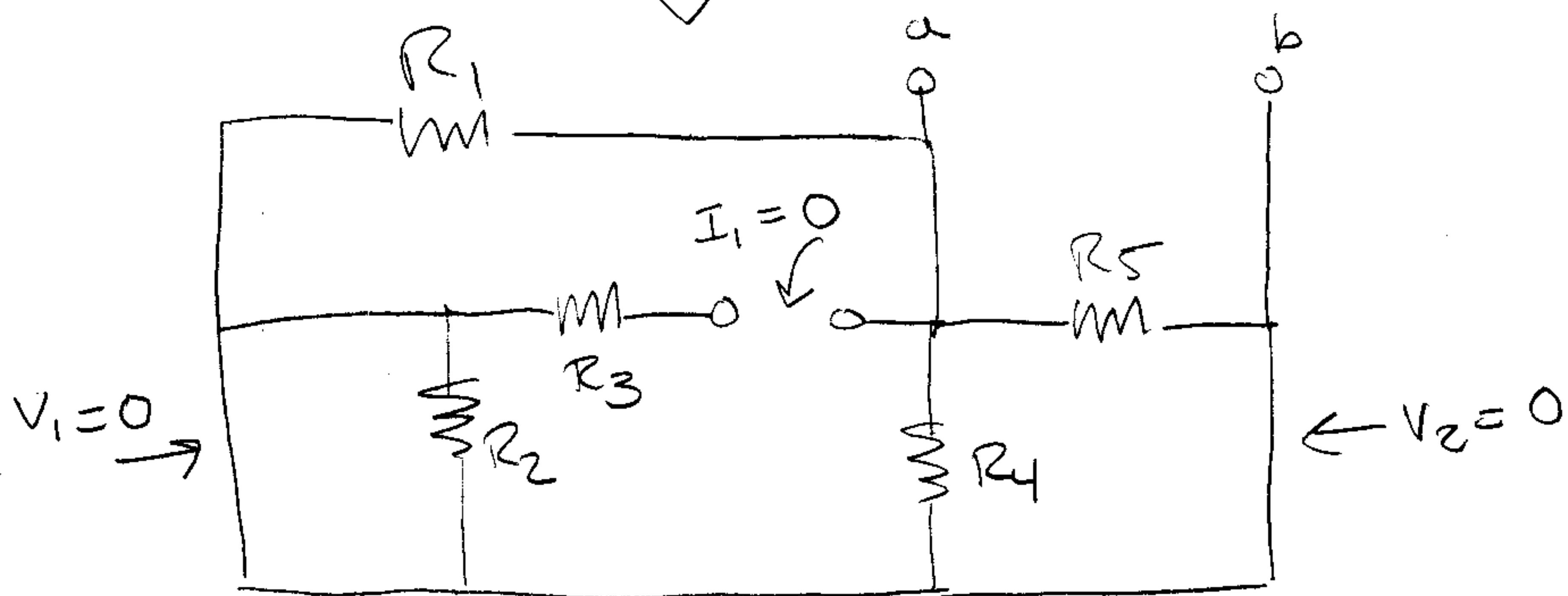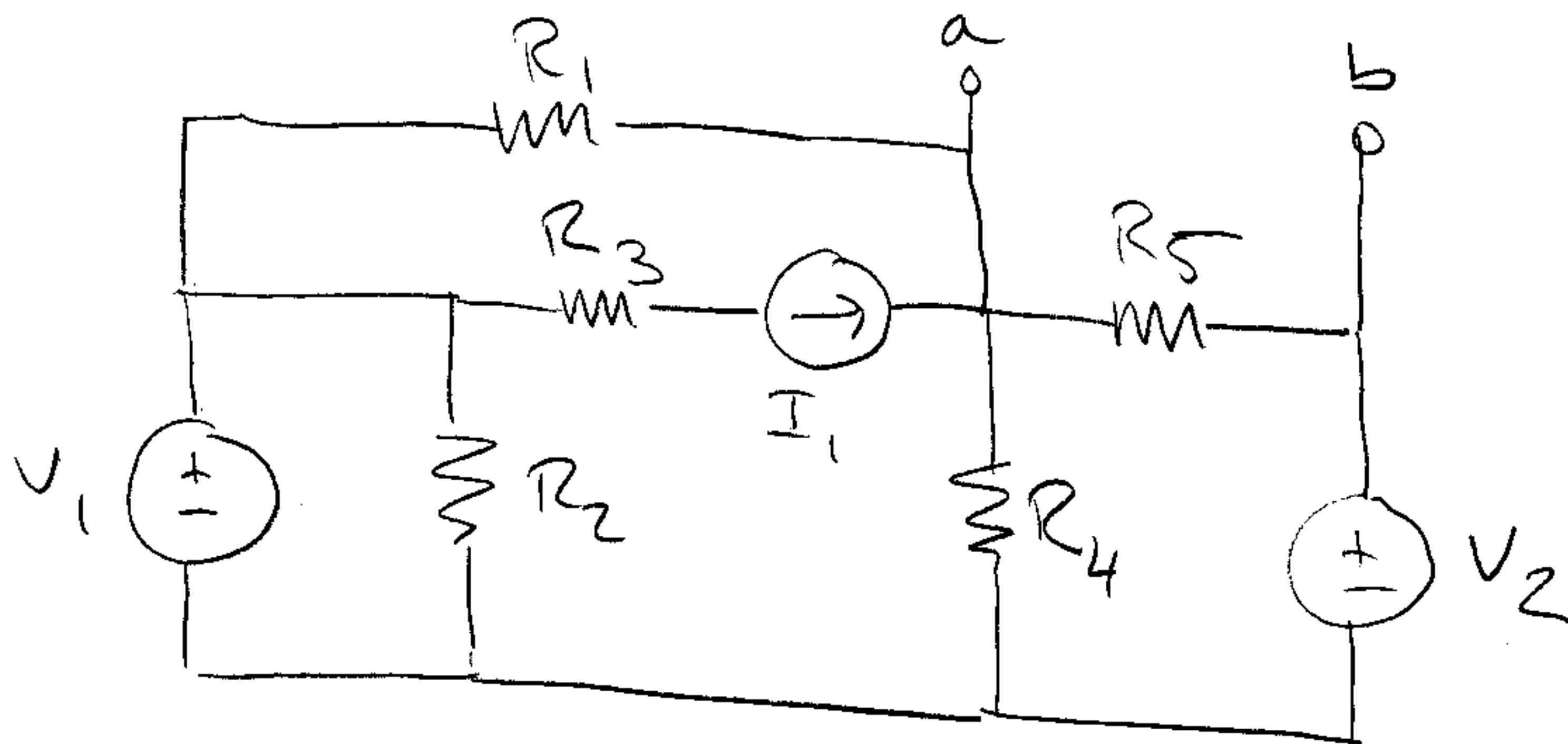


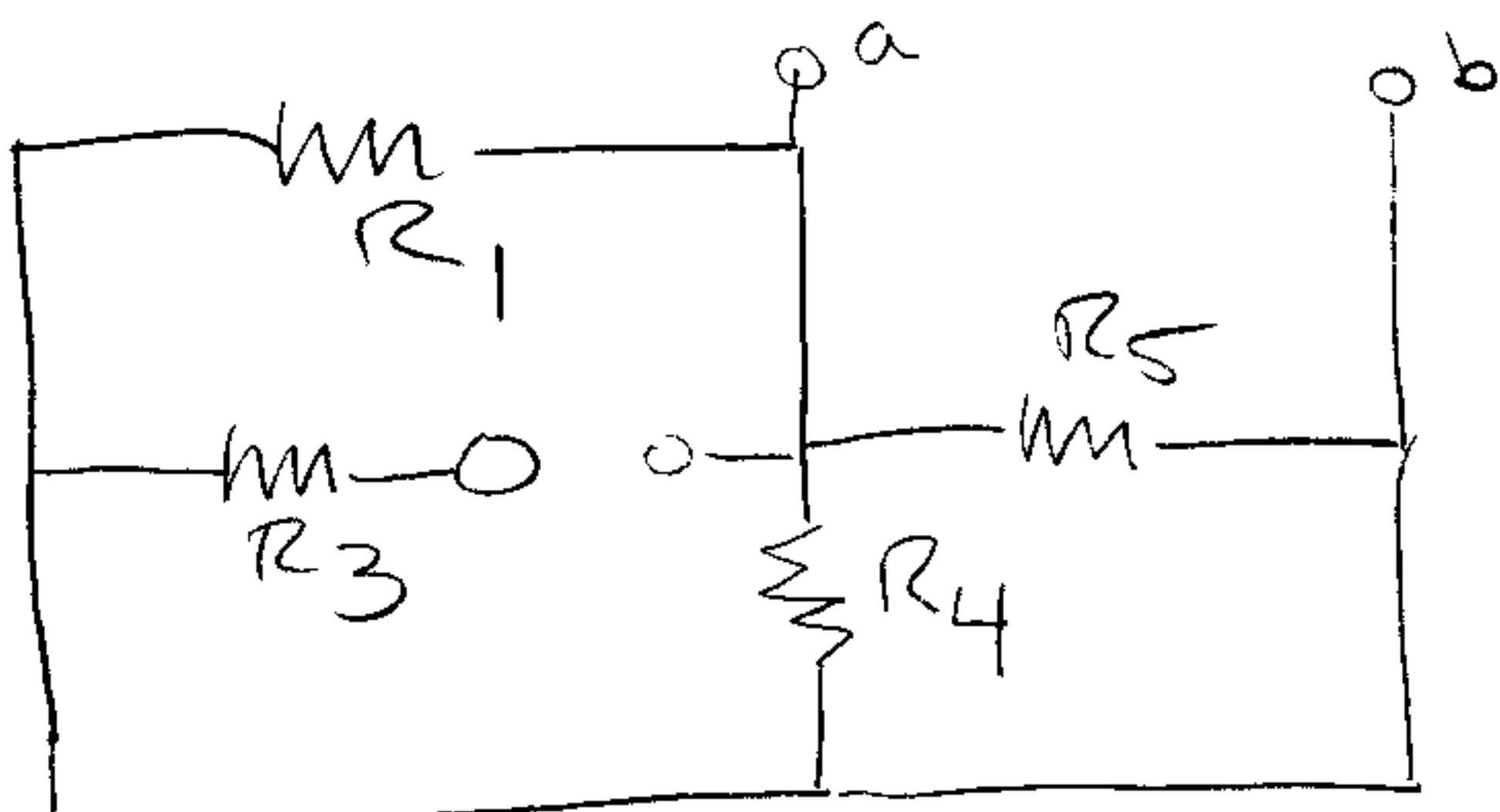R_2 is in parallel with a wire (0Ω).
The parallel combination is 0Ω .



We want to find out how this network of resistors affects a device connected to a+b, i.e., the I-V characteristic.

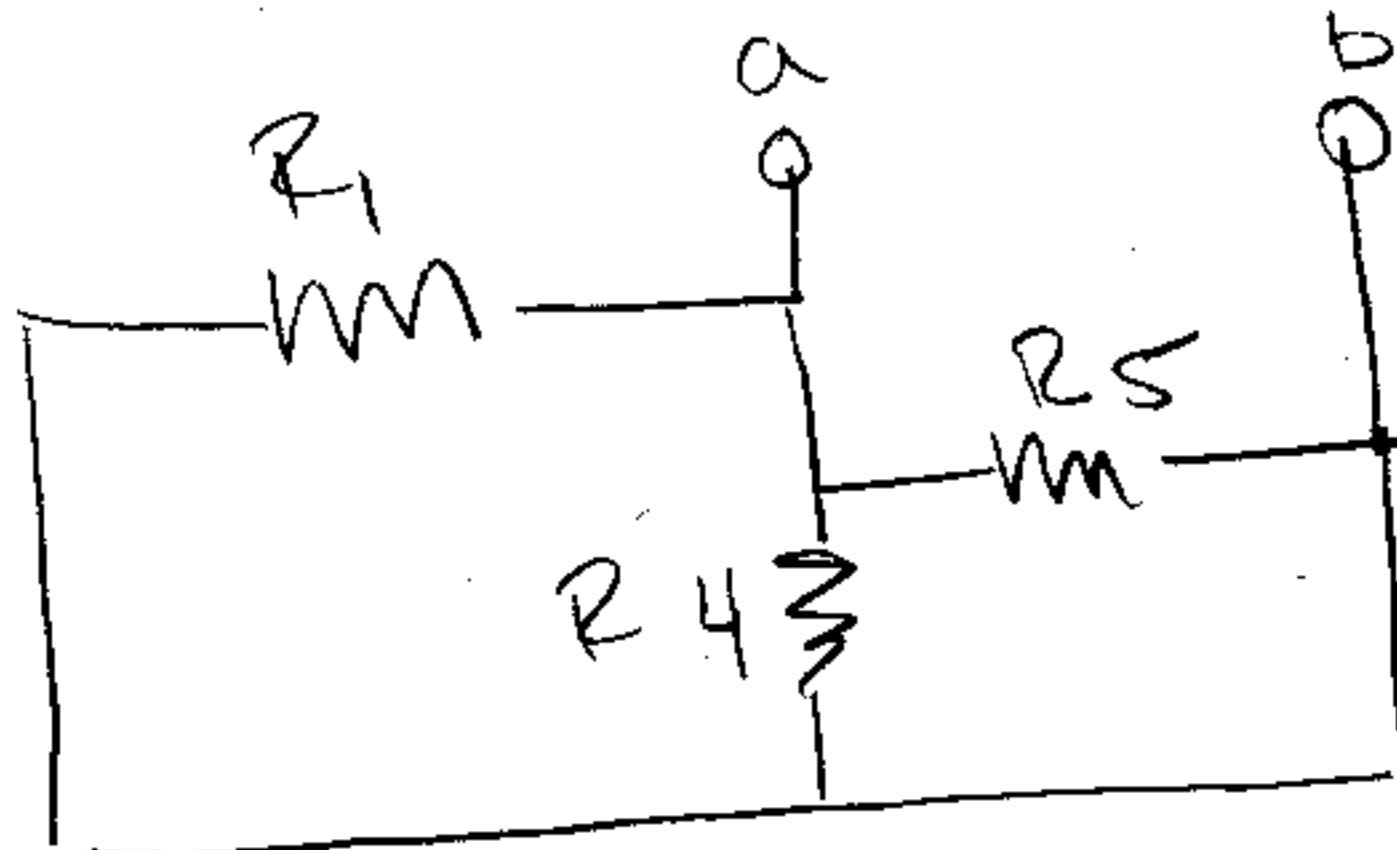Since R_3 is disconnected on one end, it does not carry current or contribute to the I-V relationship. We can leave it out.



Each resistor is connected at point a, and point b.

The resistors are in parallel.



$$R_{eq} = R_T = \left(R_1^{-1} + R_4^{-1} + R_5^{-1} \right)^{-1}$$