



OPERATIONAL AMPLIFIERS: REVIEW

- We use differential amplifiers with **feedback** (output and input connected) to perform mathematical operations
- We also use amplifiers to provide predictable voltage and additional current to output “loads”
- We can analyze amplifier circuits using the circuit model

Differential Amplifier


$$V_0 = A(V_+ - V_-)$$

Circuit Model *in linear region*

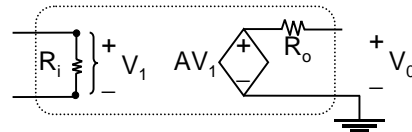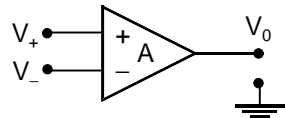


- Or, we can analyze using the simpler “ideal” assumptions
- We can design an amplifier to perform a certain operation by choosing the right form and then choosing resistor values

OPERATIONAL AMPLIFIER: USES

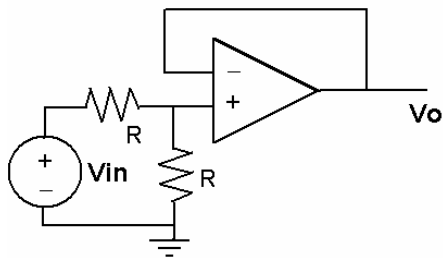

V_o is $V_{in}/2$ **regardless** of what is attached to output.


Not true without voltage follower!

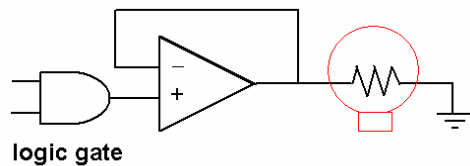

Output of logic gate will turn light bulb on or off.



Light bulb connected directly to logic gate may draw too much current from logic gate!

INTEGRATING AMPLIFIER

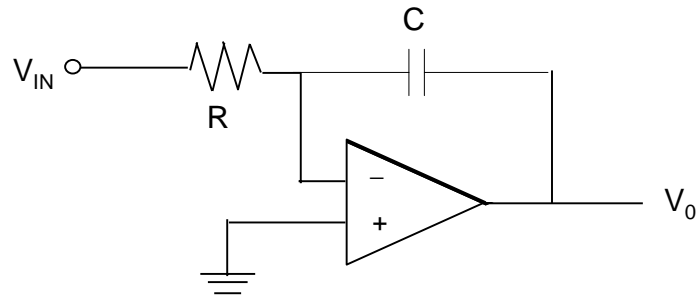

$$V_O(t) = -\frac{1}{RC} \int_0^t V_{IN}(T) dT + V_C(0)$$


ANALOG VS. DIGITAL

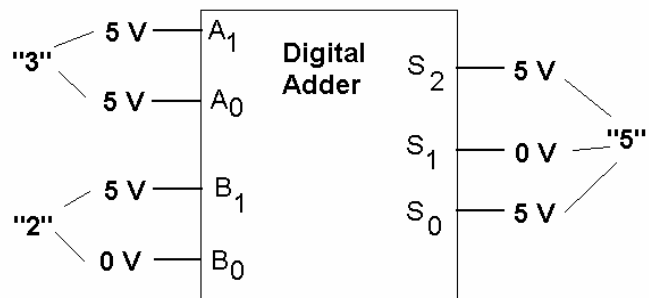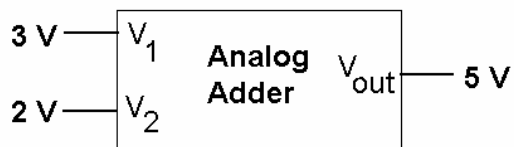

D/A CONVERSION

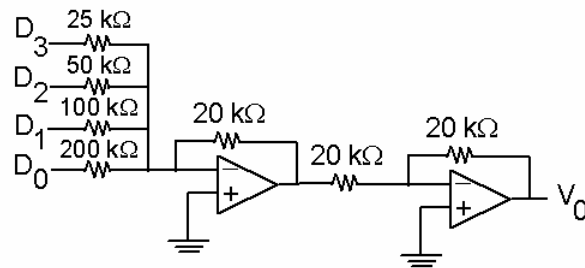Example: Digital sound (CD) to analog (speaker)

Let's have each "1" on the CD translate to 0.5 V at the speaker.




Another way is to sum **charges** instead of current with capacitor networks

Binary number	Analog output (volts)
0000	0
0001	0.5
0010	1
0011	1.5
0100	2
0101	2.5
0110	3
0111	3.5
1000	4
1001	4.5
1010	5
1011	5.5
1100	6
1101	6.5
1110	7
1111	7.5

↑ ↑
MSB LSB

COMPARATORS

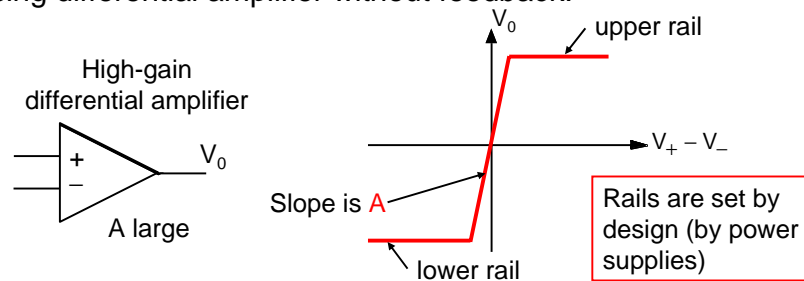Using differential amplifier without feedback:



If $V_+ > V_-$, the output V_0 will be at the upper rail.



If $V_+ < V_-$, the output V_0 will be at the lower rail.

UNLESS...



V_+ is very close to V_- , such that $A(V_+ - V_-)$ is between the rails.

COMPARATORS


Comparator with 2V threshold

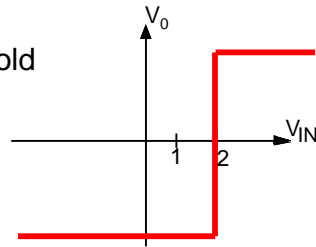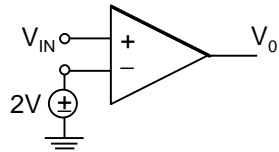

Comparator
transfer
curve

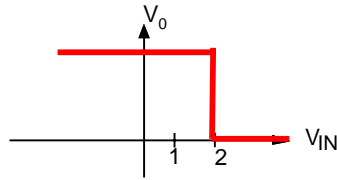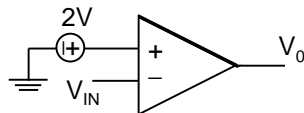


Inverter
transfer
curve

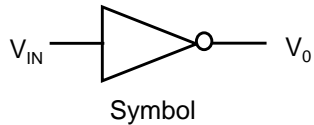

To function as logic gate, set upper rail to logic 1 and lower rail to logic 0.

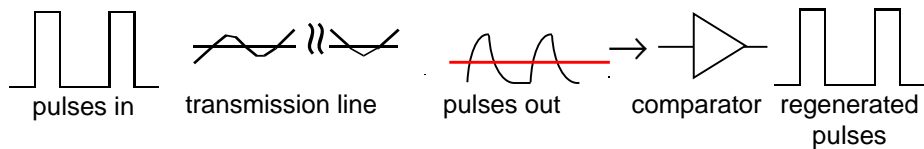ONE-BIT A/D CONVERSION IN DIGITAL SYSTEMS



Set comparator **threshold** at a suitable value
(border between logic 0 and logic 1)

Comparator output goes to +rail (logic 1) if

$$V_{IN} > V_{THRESHOLD}$$

and to -rail (logic 0) if

$$V_{IN} < V_{THRESHOLD}$$

