EECS 40 Spring 2003 Lecture 3	W. G. Oldham and S. Ross	EECS 40 Spring 2003 Lecture 3	W. G. Oldham and S. Ross
Lecture 3			
<ul> <li>Definitions: Circuits, Nodes, Bran</li> <li>Kirchoff's Voltage Law (KVL)</li> <li>Kirchoff's Current Law (KCL)</li> <li>Examples and generalizations</li> <li>RC Circuit Solution</li> </ul>	nches		
EECS 40 Spring 2003 Lecture 3	W. G. Oldham and S. Ross	EECS 40 Spring 2003 Lecture 3	W. G. Oldham and S. Ross
BRANCHES AND NO Branch: elements connected end-to-e nothing coming off in between A single branch NOT a single branch NOT a single branch node	DES nd, n (in series) single branch ned—entire wire		

# NOTATION: NODE VOLTAGES

The voltage drop from node X to a reference node (ground) is called the **node voltage**  $V_x$ .

#### Example:



EECS 40 Spring 2003 Lecture 3

W. G. Oldham and S. Ross

EECS 40 Spring 2003 Lecture 3

W. G. Oldham and S. Ross

#### KIRCHOFF'S VOLTAGE LAW (KVL)

The sum of the voltage drops around any closed loop is zero.

We must return to the same potential (conservation of energy).



Closed loop: Path beginning and ending on the same node

Our trick: to sum voltage drops on elements, look at the first sign you encounter on element when tracing path W. G. Oldham and S. Ross

# KVL EXAMPLE

Examples of three closed paths:



Path 1:

Path 2:

Path 3:

EECS 40 Spring 2003 Lecture 3

W. G. Oldham and S. Ross

EECS 40 Spring 2003 Lecture 3

W. G. Oldham and S. Ross

## UNDERLYING ASSUMPTIONS OF KVL

Assume no time-varying magnetic flux through the loop ... If there was, Faraday's Law  $\rightarrow$  induced emf (voltage) Antennas are designed to "pick up" electromagnetic waves

"Regular circuits" often do the same thing  $\rightarrow$  not desirable!

+  $\underbrace{\downarrow}_{v(t)}$ 

Avoid these loops!

How do we deal with antennas (EECS 117A)?

Include a voltage source as the circuit representation of the emf or "noise" pickup.

We have a lumped model rather than a distributed (wave) model.

EECS 40 Spring 2003 Lecture 3

W. G. Oldham and S. Ross

W. G. Oldham and S. Ross

# ALTERNATIVE STATEMENTS OF KIRCHHOFF'S VOLTAGE LAW

1) For any node sequence A, B, C, D, ..., M around a closed path, the voltage drop from A to M is given by

 $\mathbf{V}_{\mathsf{A}\mathsf{M}} = \mathbf{V}_{\mathsf{A}\mathsf{B}} + \mathbf{V}_{\mathsf{B}\mathsf{C}} + \mathbf{V}_{\mathsf{C}\mathsf{D}} + \dots + \mathbf{V}_{\mathsf{L}\mathsf{M}}$ 

2) For all pairs of nodes i and j, the voltage drop from i to j is

 $\mathbf{V}_{ij} = \mathbf{V}_i - \mathbf{V}_j$ 

where the node voltages are measured with respect to the common node.

EECS 40 Spring 2003 Lecture 3

W. G. Oldham and S. Ross

EECS 40 Spring 2003 Lecture 3

W. G. Oldham and S. Ross

# MAJOR IMPLICATION

KVL tells us that any set of elements which are **connected at both ends** carry the **same voltage**.

We say these elements are in parallel.



W. G. Oldham and S. Ross

W. G. Oldham and S. Ross

EECS 40 Spring 2003 Lecture 3

#### KIRCHOFF'S CURRENT LAW

Circuit with several branches connected at a node:



#### KIRCHOFF's CURRENT LAW "KCL":

(Sum of currents <u>entering</u> node) – (Sum of currents <u>leaving</u> node) = 0

Charge stored **in node** is zero (e.g. entire capacitor is part of a branch)

EECS 40 Spring 2003 Lecture 3

**USING KCL** 

#### Kirchhoff's Current Law (KCL)

Formulation 1:

Sum of currents **entering** node = sum of currents **leaving** node

Use/write reference directions to determine "entering" and "leaving" currents--no concern about actual current directions W. G. Oldham and S. Ross

# ALTERNATIVE KCL FORMULATIONS

Formulation 2:

"Algebraic sum" of currents **entering** node = 0

where "algebraic sum" means currents **leaving** are included with a **minus sign** 

Formulation 3:

"Algebraic sum" of currents **leaving** node = 0

currents entering are included with a minus sign

EECS 40 Spring 2003 Lecture 3

W. G. Oldham and S. Ross

EECS 40 Spring 2003 Lecture 3

W. G. Oldham and S. Ross

## **MAJOR IMPLICATION**

KCL tells us that all of the elements in a single branch carry the same current.

We say these elements are in series.



Current entering node = Current leaving node

 $i_1 = i_2$ 

EECS 40 Spring 2003 Lecture 3	W. G. Oldnam and S. Ross	EECS 40 Spring 2003 Lecture 3	W. G. Olulialit and S. Ross
KIRCHHOFF'S CURRENT LAW EXAN	IPLE		
10 µА -4 µА			
Currents entering the node:			
Currents leaving the node:			
Three formulations of KCL:			
EECS 40 Spring 2003 Lecture 3	W. G. Oldham and S. Ross	EECS 40 Spring 2003 Lecture 3	W. G. Oldham and S. Ross
EECS 40 Spring 2003 Lecture 3 GENERALIZATION OF KCL	W. G. Oldham and S. Ross	EECS 40 Spring 2003 Lecture 3	W. G. Oldham and S. Ross
EECS 40 Spring 2003 Lecture 3 GENERALIZATION OF KCL Sum of currents entering/leaving a closed surf	W. G. Oldham and S. Ross	EECS 40 Spring 2003 Lecture 3	W. G. Oldham and S. Ross

W. G. Oldham and S. Ross

EECS 40 Spring 2003 Lecture 3

W. G. Oldham and S. Ross

#### **KIRCHOFF'S CURRENT LAW USING SURFACES**

