

Lecture 6

FINDING VOLTAGES IN A CIRCUIT

So far, we have been applying KVL and KCL “haphazardly” to find voltages and currents in a circuit.

Good for developing intuition, finding things quickly...

...but what if the circuit is complicated? What if you get stuck?

Systematic way to find all node voltages in a circuit:

Nodal Analysis


1

2

NOTATION: NODE VOLTAGES

The voltage drop from node X to a reference node (ground) is called the **node voltage** V_x .

Example:

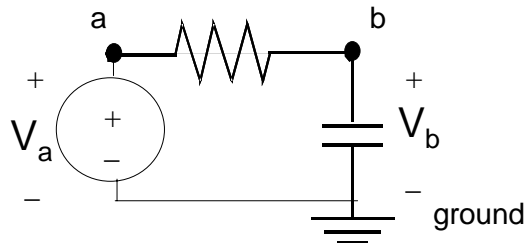


3

4

FORMAL CIRCUIT ANALYSIS USING KCL: NODAL ANALYSIS

(Memorize these steps and apply them rigorously!)


- 1 Choose a reference node (ground, node 0)
(look for the one with the most connections!) 
- 2 Define unknown node voltages (those not fixed by voltage sources)
- 3 Write KCL at each unknown node, expressing current in terms of the node voltages (using the I-V relationships of branch elements*)
- 4 Solve the set of equations (N equations for N unknown node voltages)

* with floating voltages we will use a modified Step 3

5

6

EXAMPLE OF NODE ANALYSIS

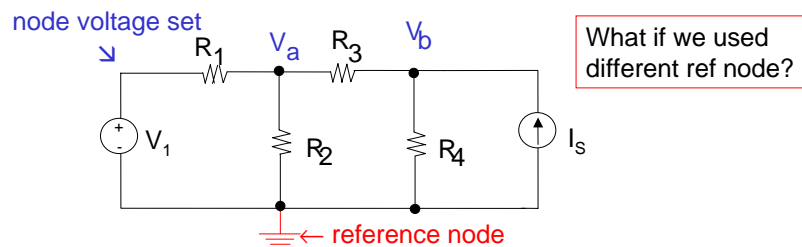


1. Choose a reference node.
2. Define the node voltages (except reference node and the one set by the voltage source).
3. Apply KCL at the nodes with unknown voltage.
4. Solve for V_a and V_b in terms of circuit parameters.

7

8

EXAMPLE OF NODE ANALYSIS

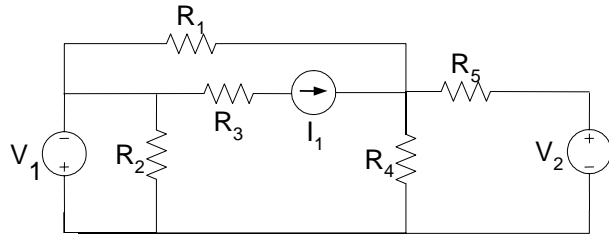


9

10

NODAL ANALYSIS WITH “FLOATING” VOLTAGE SOURCES

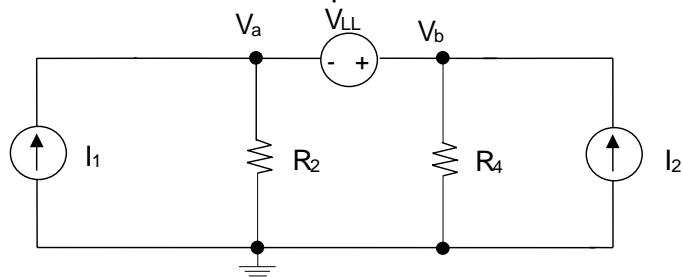A “floating” voltage source is a voltage source for which neither side is connected to the reference node. V_{LL} in the circuit below is an example.




Problem: We cannot write KCL at node a or b because there is no way to express the current through the voltage source in terms of $V_a - V_b$.

Solution: Define a “supernode” – that chunk of the circuit containing nodes a and b. Express KCL at this supernode. 11

12

FLOATING VOLTAGE SOURCES (cont.)

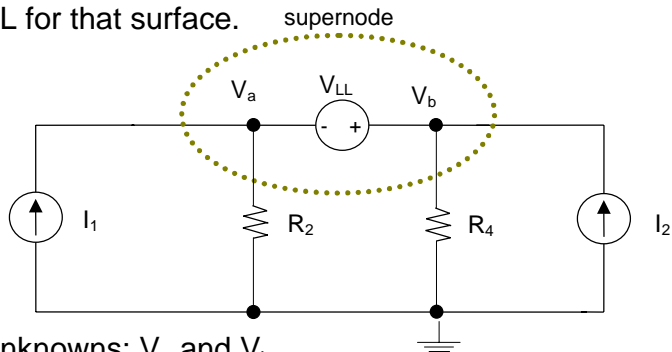Use a Gaussian surface to enclose the floating voltage source;
write KCL for that surface.



Two unknowns: V_a and V_b .


Get one equation from KCL at supernode:

Get a second equation from the property of the voltage source:

13

14

ANOTHER EXAMPLE

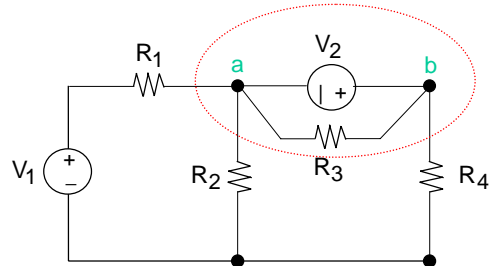

15

16