

Electrical Quantities, Circuit Elements, KCL

EE40, Summer 2004

Alessandro Pinto

apinto@eecs.berkeley.edu

Announcements

- ✓ **New schedule** has been posted on-line
- ✓ **Office hours** moved in 463 Cory Hall
- ✓ No discussions no labs this week!
- ✓ Would you **move lectures** in 247 Cory Hall?
- ✓ **HW** will be posted on Friday and will be due by 5PM in 463 Cory Hall the following friday

About Labs

010	10		010	18
012	3			
013	27	→	013	19
014	3			
015	13		015	19

Missing e-mail addresses

name [BAN, IL HYUN]

name [BAZARRAGCHAA, ZORIGT]

name [BESTORY, CORINNE]

name [BROWNING, JASON]

name [CHUNG, HYE WON]

name [JANG, WEON WI]

name [JWA, TAI WOOK]

name [KIM, JU HYUN]

name [KIM, KI SANG]

name [LEEPER, ANDREW ALAN]

name [LIM, SANG HO]

name [NORONA, CHARLES EDWARD]

name [RYU, SEONG WAN]

neilg@uclink.berkeley.edu

psyrex@uclink4.berkeley.edu

Outline

- ✓ Basic quantities
 - ✓ Charge
 - ✓ Current
 - ✓ Voltage
 - ✓ Power
- ✓ Basic elements
 - ✓ Resistor
 - ✓ Voltage Source
 - ✓ Current Source
 - ✓ Capacitor
 - ✓ Inductor
- ✓ Kirchoff's Current Law


Charge

- ✓ Charge are quantized
 - ✓ Multiple of $1.602 \cdot 10^{-19}$ *Coulomb*
- ✓ Charge conservation principle
 - ✓ Electric charge is neither created nor destroyed
- ✓ Rubbing amber and fur separates charges but the system is still neutral

Voltage

- ✓ Work done per unit charge to move against an electric field

$$v = \frac{dw}{dq}$$

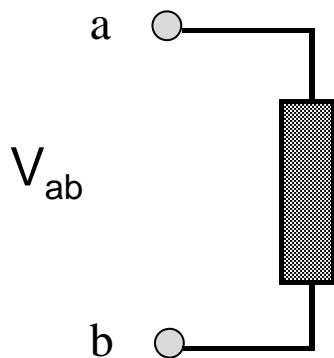


$$V_{ab} = V_a - V_b$$

- ✓ Remember that voltage is defined with respect to a reference point
- ✓ Unit of measure Volt (V) = Joule/Coulomb (in honor of Alessandro Volta)

Current

- ✓ Rate of flow of electric charge

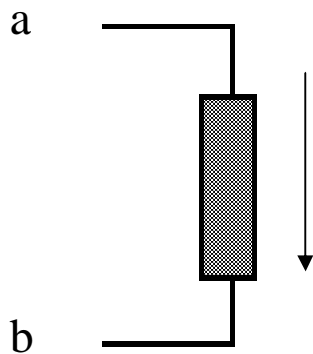


The diagram shows a vertical resistor connected to a circuit. The top terminal is labeled 'a' and the bottom terminal is labeled 'b'. A downward-pointing arrow is positioned to the right of the resistor, indicating the direction of current flow.

$$i = \frac{dq}{dt} \left[\frac{\text{Coulomb}}{\text{sec}} = \text{Ampere} \right]$$


- ✓ Unit of measure Ampere (A) (in honor of André-Marie Ampère)
- ✓ Current has polarity and direction

Reference direction

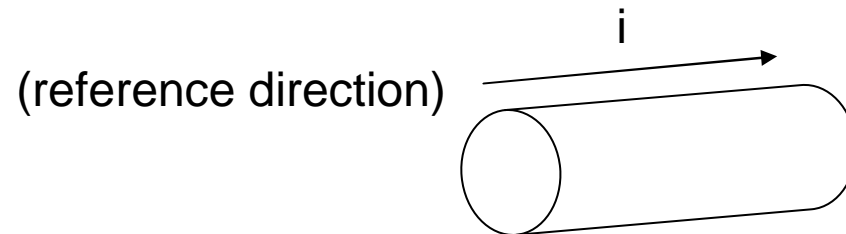


- ✓ Count charges flowing in the conductor
 - ✓ Positive charges flowing in the reference direction contribute as positive
 - ✓ Positive charges flowing against the reference direction contribute as negative
 - ✓ Negative charges flowing in the reference direction contribute as negative
 - ✓ Negative charges.....

Reference direction

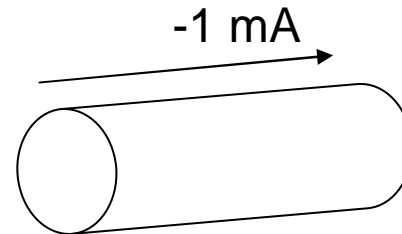

- ✓ It means that there is a flow of 1 mC of positive charges per second **against the reference direction**

Reference Polarities

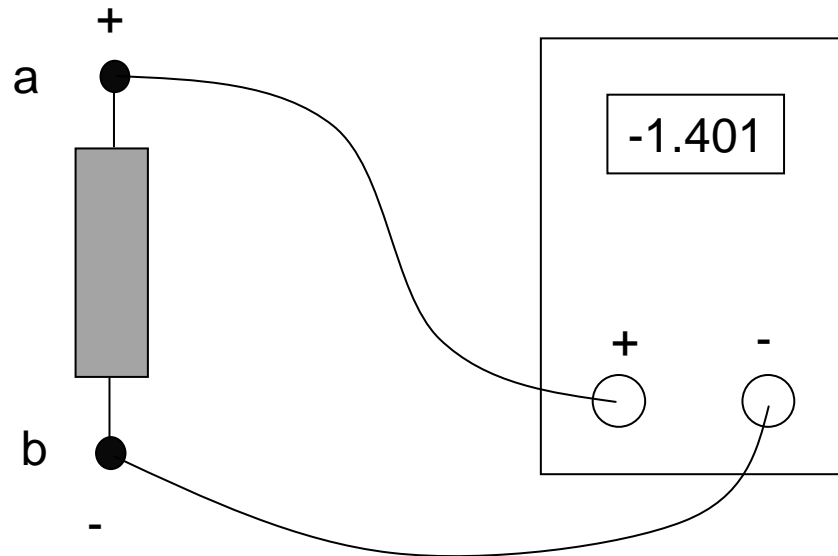

$$v_{ab} = v_a - v_b = -1.401$$

$$v_{ba} = v_b - v_a = 1.401$$

Power

- ✓ Change in energy over time


$$p = \frac{dw}{dt} = \frac{dw}{dq} \frac{dq}{dt} = vi \quad [\text{Volt} \cdot \text{Ampere} = \text{Watt}]$$

- ✓ A charge q moving through a drop in voltage V loses energy qV
- ✓ Rate of energy loss depends on number of charges per second, which is current


Sign Convention for Power

Passive sign convention

$$p = vi$$

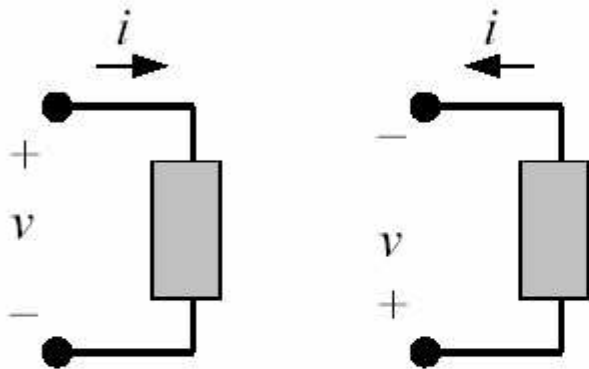

$$p = -vi$$

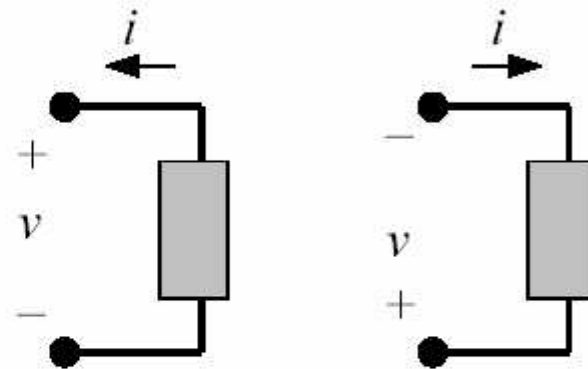


- If $p > 0$, power is being delivered to the box.
- If $p < 0$, power is being extracted from the box.

Resistor

Resistance is the capacity of a material to impede the flow of electric charge. The circuit element used to model this behavior is the **resistor**.

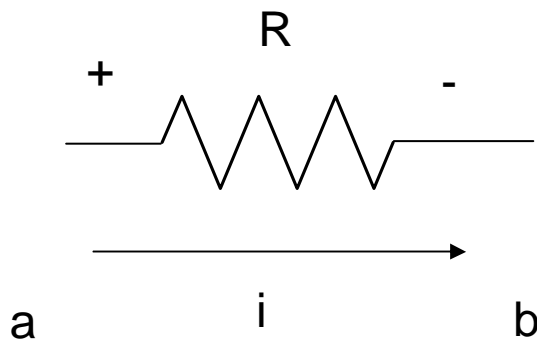With the reference direction and polarities shown we get the Ohm's law




$$v_{ab} = Ri \quad [V = \Omega A]$$

A resistor always absorb power,
R is always positive

Voltage Sources

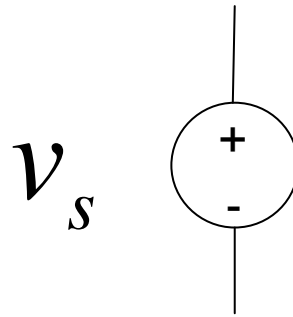
- ✓ **Independent ideal voltage source**
 - ✓ Circuit element that maintains a prescribed voltage across its terminals, **regardless of the current flowing in those terminals.**
 - ✓ Voltage is known, but current is determined by the circuit to which the source is connected.





Voltage Sources

✓ Dependent ideal voltage source

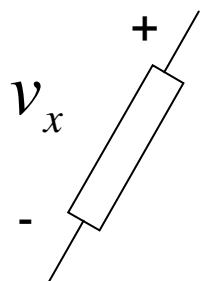
- ✓ It is a voltage source whose voltage depends on a voltage or current elsewhere in the circuit



Voltage-controlled

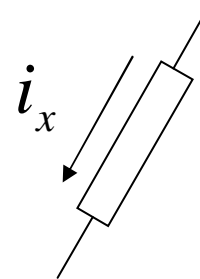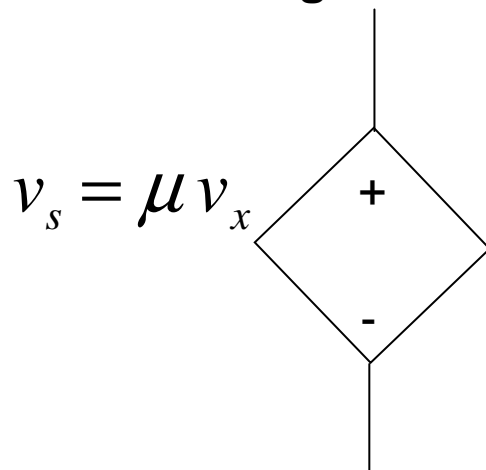


Current-controlled

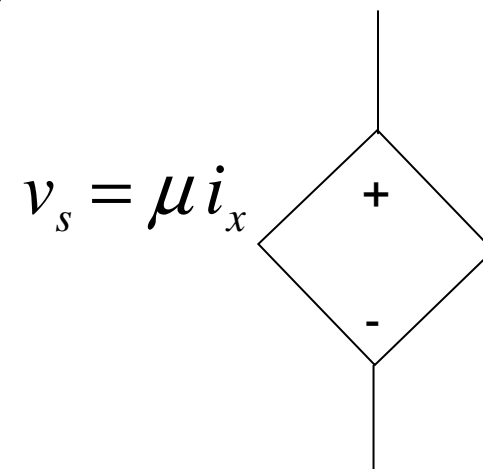

Current Sources


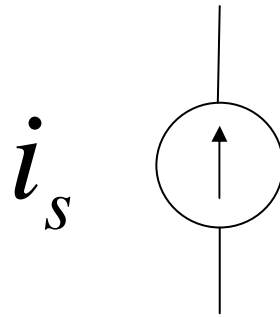
- ✓ **Independent ideal current source**
 - ✓ Circuit element that maintains a prescribed current through its terminals, **regardless of the voltage across those terminals.**
 - ✓ Current is known, but voltage is determined by the circuit to which the source is connected.



Current Sources


✓ Dependent ideal current source

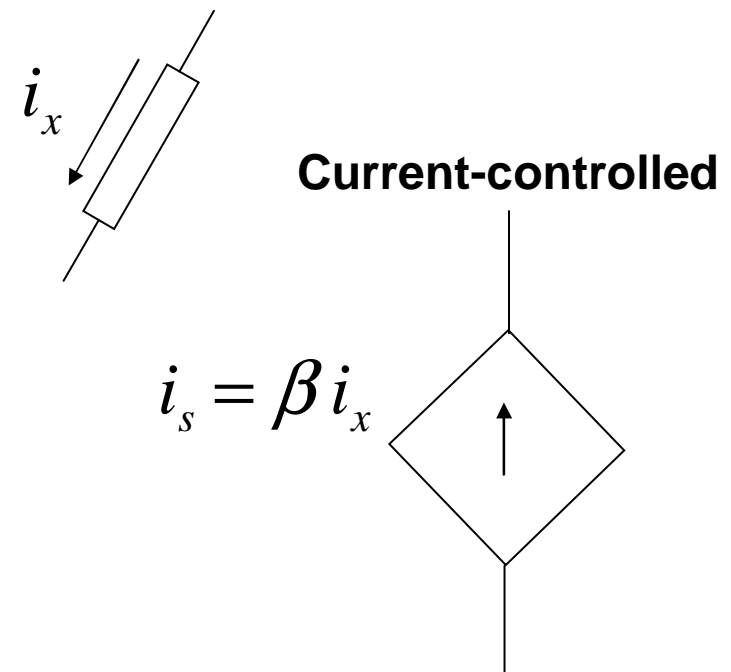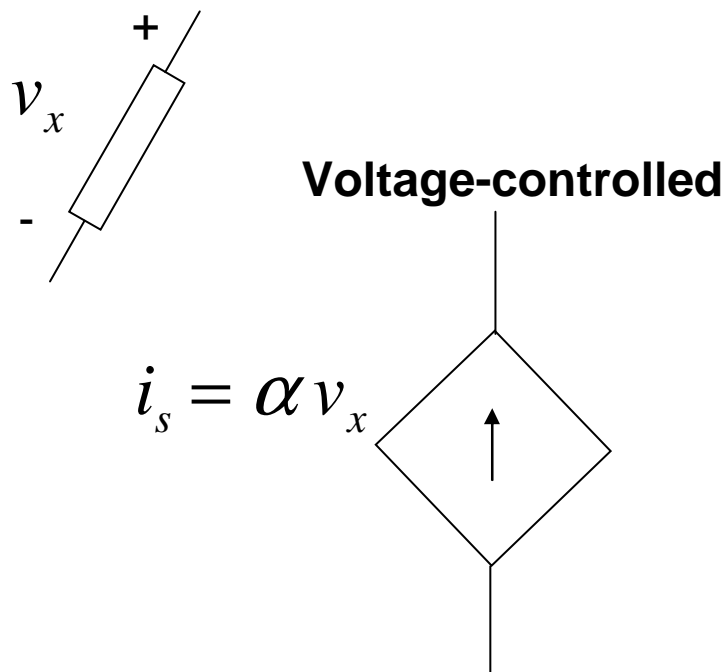- ✓ It is a current source whose current depends on a voltage or current elsewhere in the circuit



Circuit Nodes and Loop

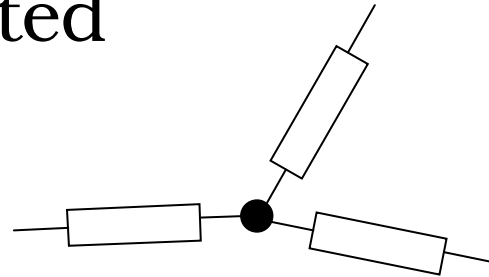
- ✓ A node is a point where two or more circuit elements are connected



- ✓ A loop is a path of circuit elements that starts and ends at the same node and includes other nodes at most once

Kirchoff's Current Law

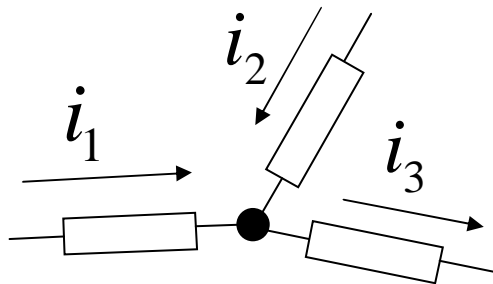- ✓ The algebraic sum of all the currents at any node in a circuit equals zero.
- ✓ The sum of all currents entering a node is equal to the sum of all currents leaving a node



$$i_1 + i_2 - i_3 = 0$$

$$i_1 + i_2 = i_3$$