

DIODES: APPROXIMATIONS

The current/voltage relation for a diode is:

$$I = I_0 \left(e^{\frac{V}{V_T}} - 1 \right)$$


where $V_T \approx 26 \text{ mV} @ 300 \text{ K}$ (remember that V_T depends on the temperature and its value is actually $V_T = \frac{kT}{q}$ where k is the Boltzmann constant, q is the charge of an electron and T is the Temperature in Kelvin degrees).

η is a constant that depends on the semiconductor: $\eta = 1$ for Germanium (Ge) and 2 for silicon (Si).

Finally I_0 is the reverse saturation current. For instance for the 1N4002, $I_0 \approx 0.05 \mu\text{A} @ 25^\circ\text{C}$. Figure 1 on the next page shows the I/V plot obtained using these numbers.

$$V_T = 25 \text{ mV}$$

$$I_0 = 0.05 \mu\text{A}$$

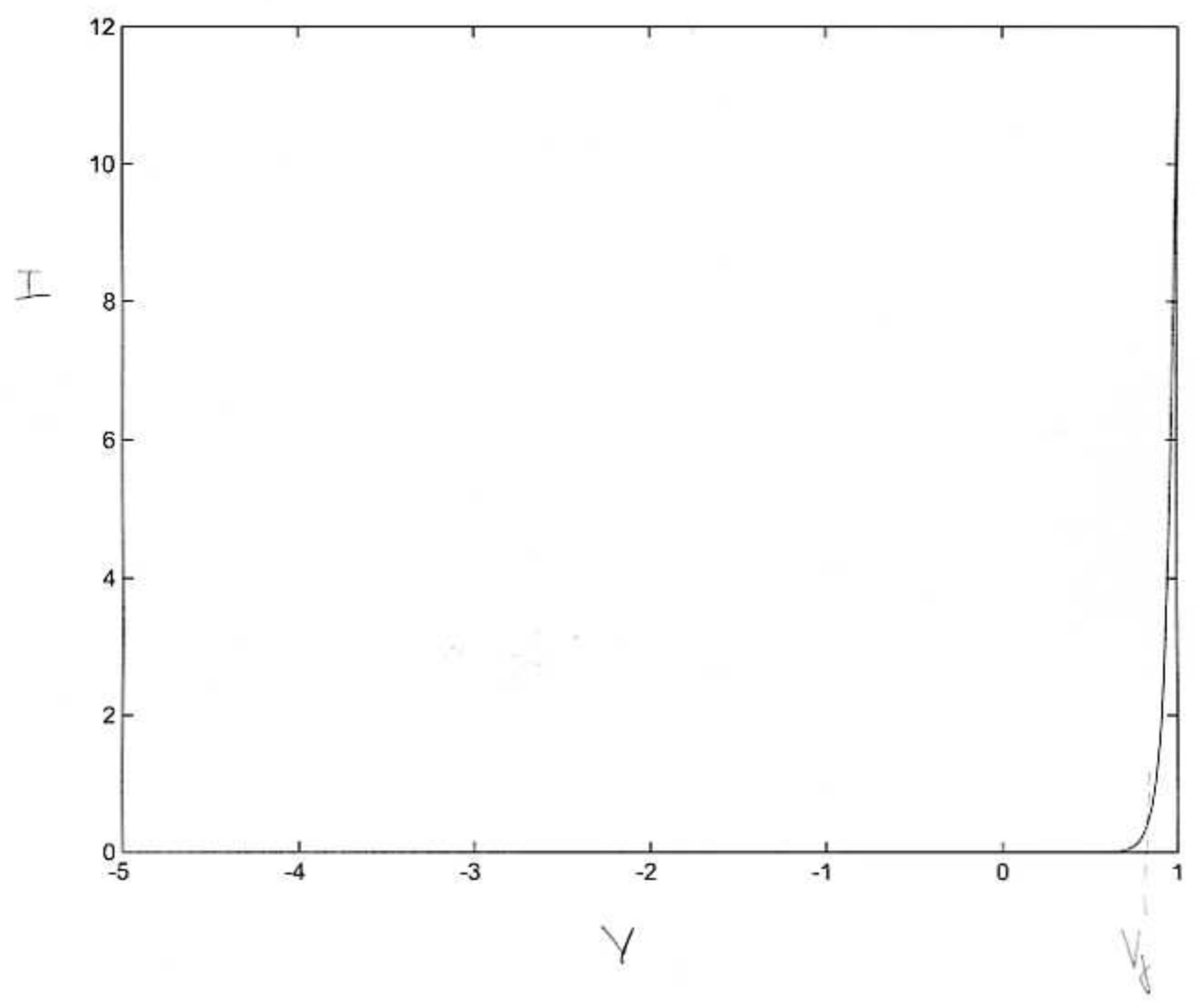

The circuit symbol that we use for diodes is like the following:




For $V < V_f$, I is very small and if $V < 0$ then $I \approx -I_0$ which is a very small reverse current.

If $V > V_f$ then $\frac{\partial I}{\partial V}$ is very high meaning that G (the conductance) is high and hence $R = \frac{1}{G}$ is very small. The diode behaves like a short circuit.


We want to abstract this behaviour. The first rough approximation is the following:

- $V \leq 0$ open circuit
- $V \geq 0$ short circuit

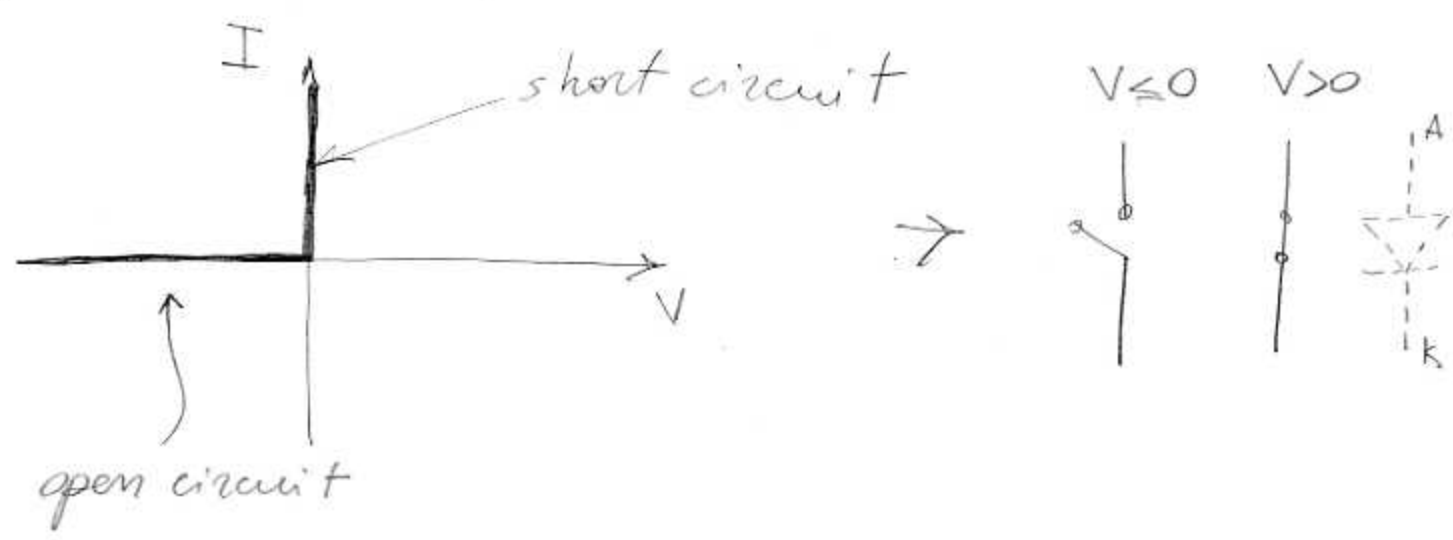This behaviour can be graphically represented as follows:



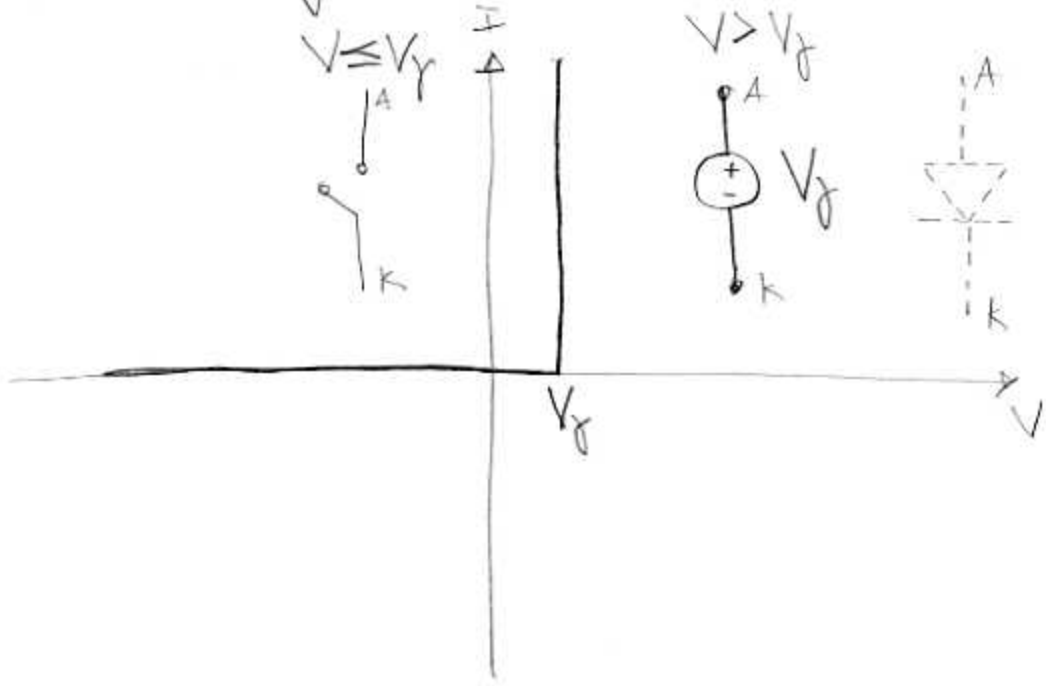This model is an approximation because it doesn't consider I_0 , in reverse polarization, and V_f in forward polarization. We could take into account V_f using the following model:




This model considers the diode an open circuit for $V \leq V_f$, and a voltage source for $V > V_f$.

Actually this is not the correct description of this model. We should say: $I=0$ for $V \leq V_f$ and $V=V_f$ otherwise, which means $V=V_f$ for forward polarization. The reason is that in this model V across the diode cannot be greater than V_f . When the diode is in forward polarization then not only the voltage is V_f but also the current can assume any value greater than 0.

This is basically a voltage source.

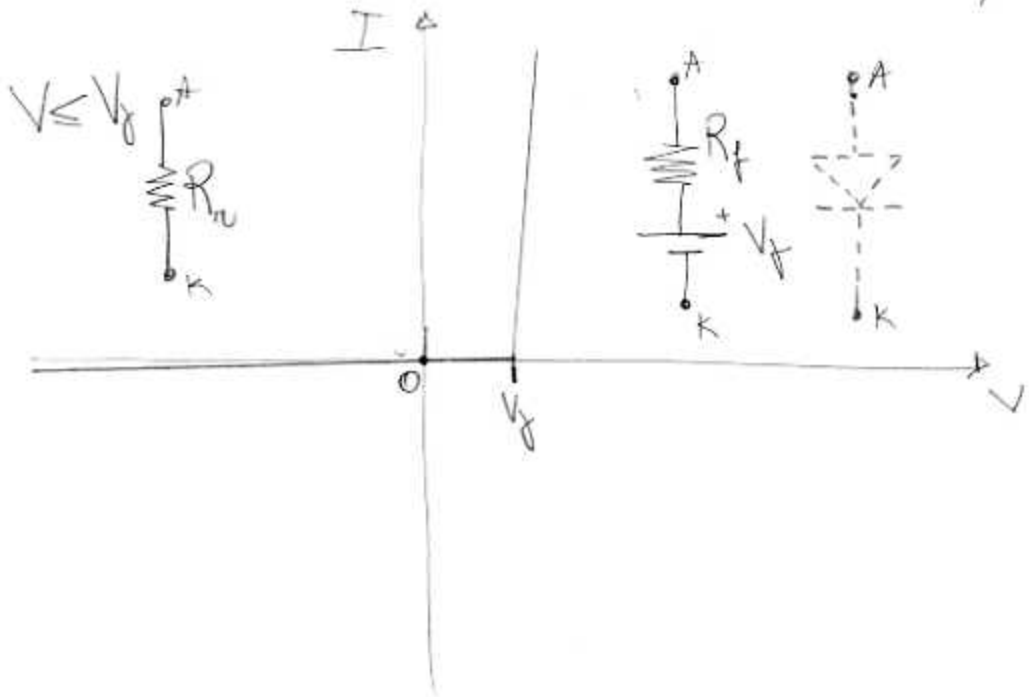a more refined approximation is the following



In reverse polarization, the diode can be considered as a resistor with a very high resistance. This situation can be graphically represented by a line that passes through the origin of the $I-V$ plane.

The angular coefficient of this line is :

$$\frac{dI}{dV} = \frac{1}{R}$$

In forward polarization, the diode can be considered as a very small resistor R_r but we have to use a voltage source V_f to consider the fact that the line doesn't pass through the origin.

- TRANSCONDUCTANCE CHARACTERISTIC

Consider a circuit with an input and an output :




The question we want to answer is : what is the value of the output

if the value of the input is x Volts? 11.7

Of course we want to characterize the output V values x .

We can build a graph then:

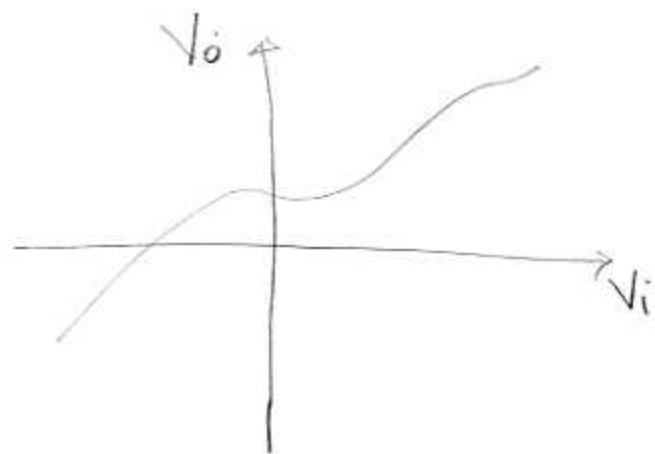

for each value of V_i we can look at the graph and find the value of the output V_o .



For linear circuits that graph will always be something like:

$$V_o = aV_i + b$$

Unfortunately, diodes are non linear circuits element. The relation between current and voltage is not linear, it is indeed exponential.

If we are given a circuit and we are asked to find the transfer then if the circuit is linear

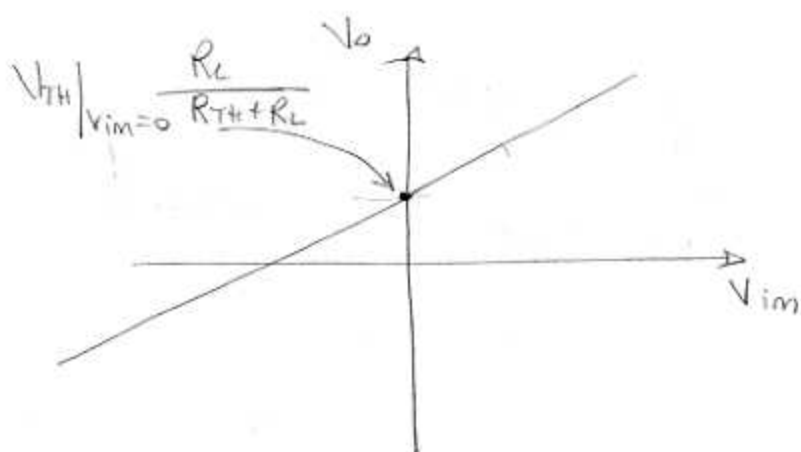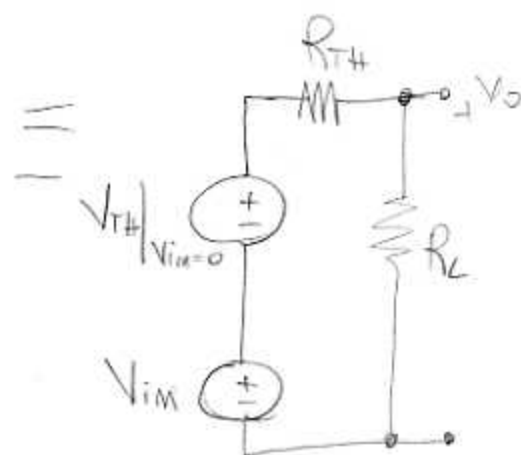
we can just find the thevenin equivalent circuit :



If the circuit is non linear then we cannot apply the methods that we know directly.

- STATES METHOD

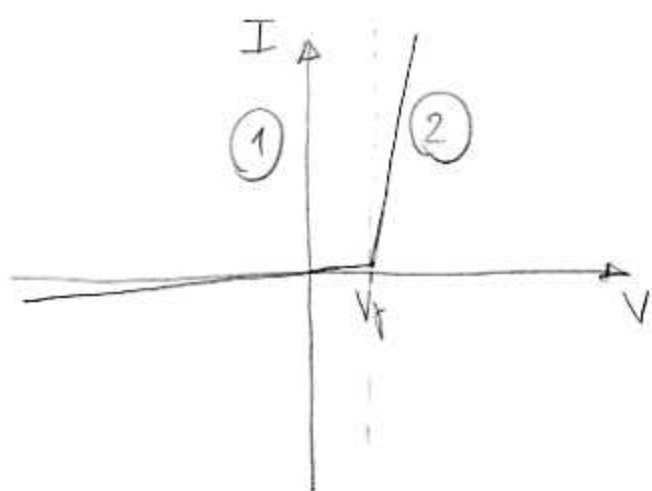Even if diodes are non linear devices, we have built approximations that are piecewise linear. We define a state of the device the portion of its I-V characteristic which is linear:



① and ② are the two states. They are defined by:

$$\textcircled{1} \left\{ V \leq V_f ; I = \frac{V}{R_r} \right\}$$

$$\textcircled{2} \left\{ V > V_f ; I = \frac{V - V_f}{R_f} \right\}$$

If a circuit has D diodes, then its state is a D -tuple S where $S[i]$ (the i -th element of the tuple)

represent the state of the i -th diode.

11.10

We can use the following method for analyzing a circuit containing diodes:

1 - Pick an initial state S

2 - While a solution is not found

2.1 - \forall diodes D_i


2.1.1 - substitute D_i with its equivalent circuit based on state $S[i]$

2.2 - Analyze the resulting linear circuit

2.3 - If all voltages across the diodes are compliant with the state S then this is the solution

2.4 - otherwise pick a state S that has not been visited already

EXAMPLE:

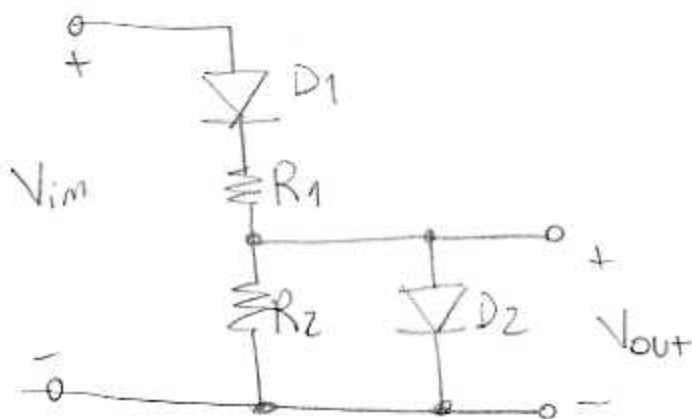

$$R_1 = 100 \Omega$$

$$R_2 = 50 \Omega$$


$$R_{in} = 100 M\Omega$$

$$R_f = 5 \Omega$$

$$V_f = 0.7$$

Since there are two diodes then we have to explore at most 4 states:

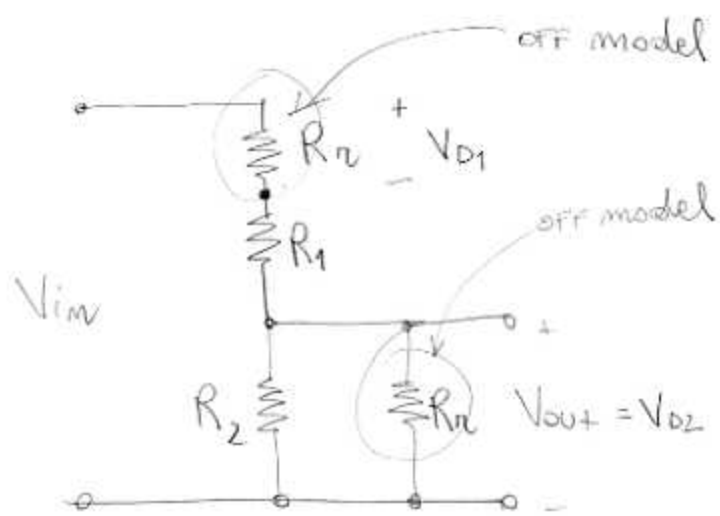We start with the initial state {OFF, OFF}



$$V_{out} = V_{D2} = V_{in} \frac{R_2 // R_2}{R_2 // R_2 + R_1 + R_2}$$

$$V_{D1} = V_{in} \frac{R_2}{R_2 + R_1 + R_2 // R_2}$$


$$V_{D2} \approx V_{in} \frac{R_2}{R_2} \approx 0$$

$$V_{D1} \approx V_{in}$$

If $V_{in} \leq V_f$ then this state is valid because

both V_{D1} and V_{D2} are less than V_f and the two diodes are both off which matches our original assumption.

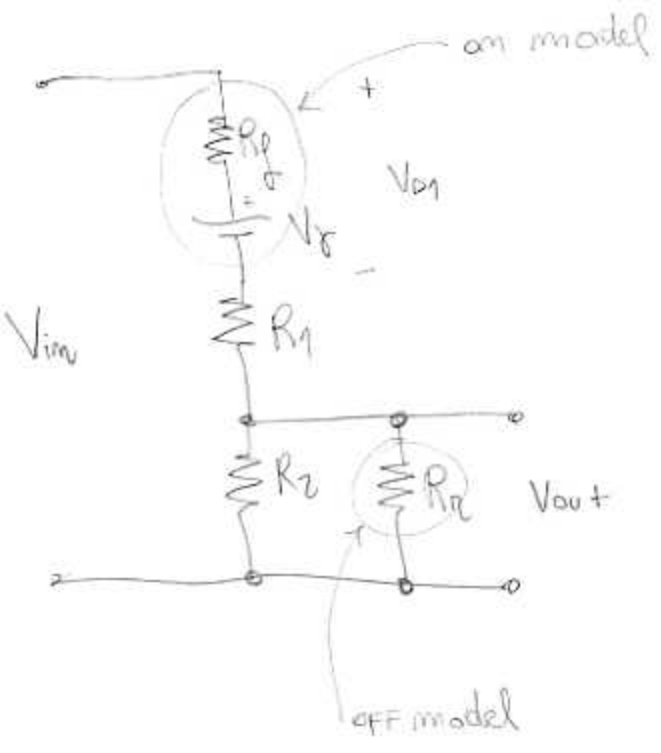When $V_{in} > V_f$, then $D1$ switches to ON and we can try then with the new state {ON, OFF}



$$V_{o2} = V_{o1} = (V_{im} - V_f) \frac{R_2 // R_o}{R_2 // R_o + R_1 + R_f}$$

$$V_{o1} = V_f + (V_{im} - V_f) \frac{R_f}{R_f + R_1 + R_2 // R_o}$$

$$V_{o2} \approx (V_{im} - V_f)$$

$$V_{o1} \approx V_f + \frac{(V_{im} - V_f) R_f}{R_o}$$


Sim $V_{im} = V_f \Rightarrow V_{o2} = 0$ and $V_{o1} > V_f$ hence this model is valid.

It will be valid until $V_{o2} \geq V_f$ meaning

$$V_{im} - V_f > V_f \Rightarrow V_{im} > 2V_f$$

At this point also

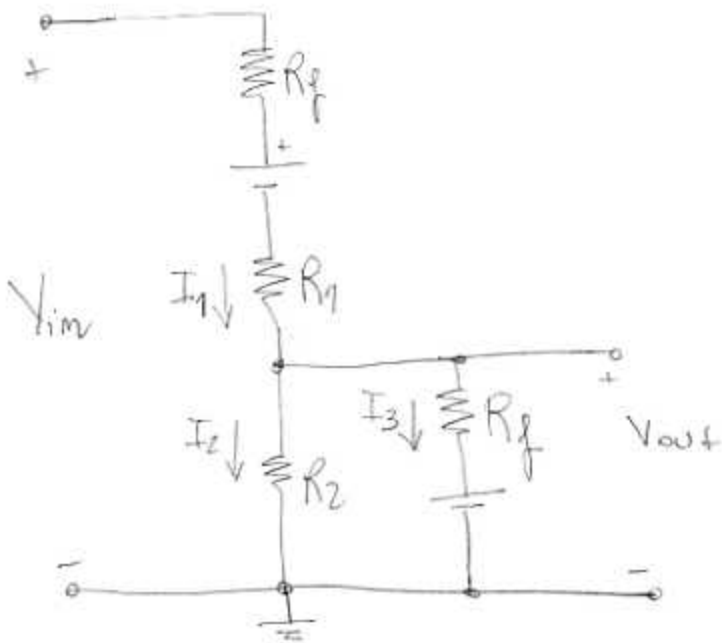D_1 switches. We can then try the new state {ON, ON}



$$I_1 = \frac{V_{in} - V_{out} - V_f}{R_f + R_1}$$

$$I_2 = \frac{V_{out}}{R_2} ; I_3 = \frac{V_{out} - V_f}{R_f}$$

$$I_1 = I_2 + I_3 \Rightarrow \frac{V_{in} - V_{out} - V_f}{R_f + R_1} = \frac{V_{out}}{R_2} + \frac{V_{out} - V_f}{R_f}$$


$$\frac{V_{in}}{R_f + R_1} = V_{out} \left(\frac{1}{R_2} + \frac{1}{R_f} + \frac{1}{R_f + R_1} \right) + V_f \left(\frac{1}{R_f + R_1} - \frac{1}{R_f} \right)$$

$$V_{out} = \frac{\frac{V_{in}}{R_f + R_1} + V_f \left(\frac{R_1}{(R_f + R_1) R_f} \right)}{\frac{R_f(R_f + R_1) + R_2(R_f + R_1) + R_2 R_f}{R_f R_2 (R_f + R_1)}}$$

$$= \frac{V_{in} R_2 R_f}{(R_2 + R_f)(R_f + R_1) + R_2 R_f} + V_f \frac{R_1 R_2}{(R_2 + R_f)(R_1 + R_f) + R_2 R_f}$$

$$V_{out} \approx V_{in} \cdot 0.041 + V_f \cdot 0.83$$

So the transcharacteristic is:

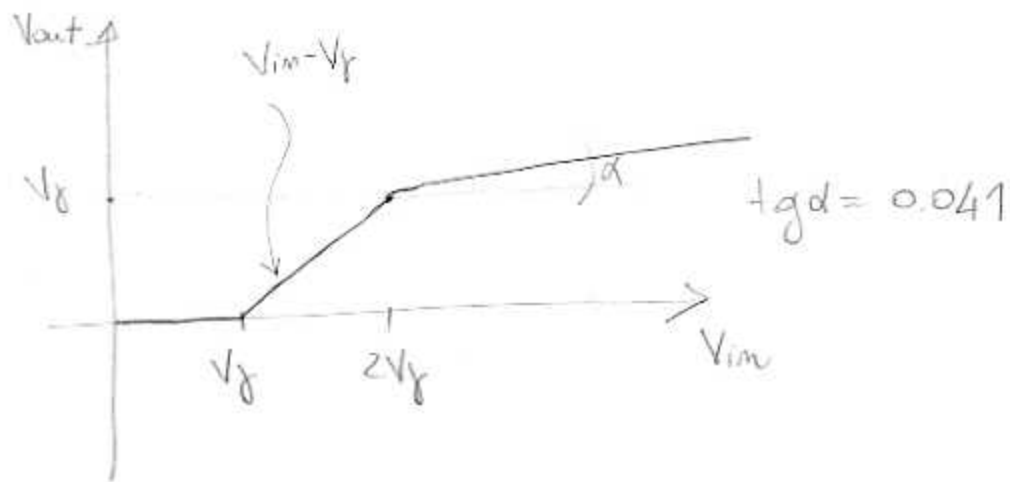

The solution is an approximate solution.


In fact if you compute $V_{out} = 2V_f \cdot 0.041 + V_f \cdot 0.83$

The result is not exactly V_f . The reason is that we have made a lot of approximation in our computation. For instance considering $R_2 \parallel R_2 = R_2$ and $R_2 + R_f + R_1 = R_2$ and so on.

- APPLICATIONS

In your texbook you can find classical applications of diodes. Here I will give you other applications that you might like.


- LOGIC GATES

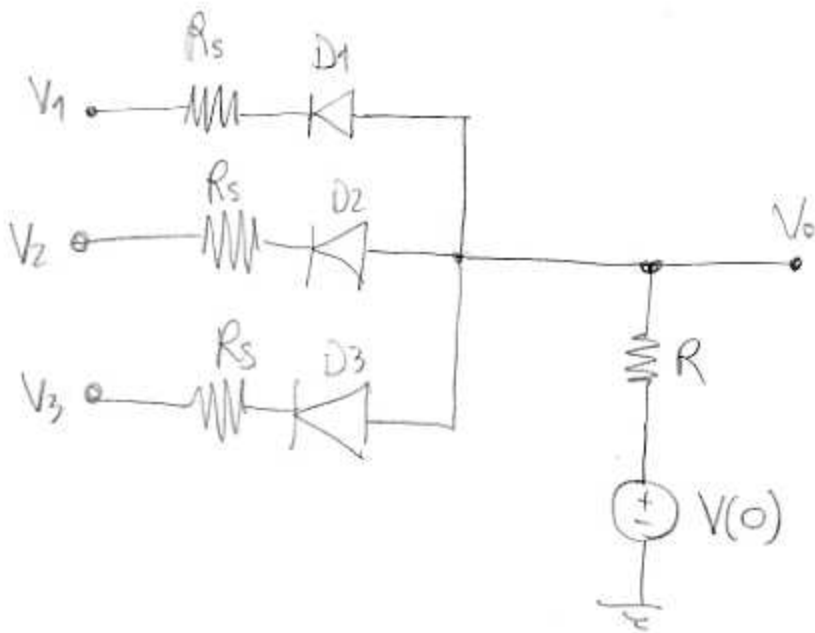

V_i can take
 on two values
 $V(1) = 0 \text{ V} \rightarrow$ binary 1
 $V(0) > V_f \rightarrow$ binary 0

If $V_1 = V_2 = V_3 = V(0) \Rightarrow V_o = V(0)$

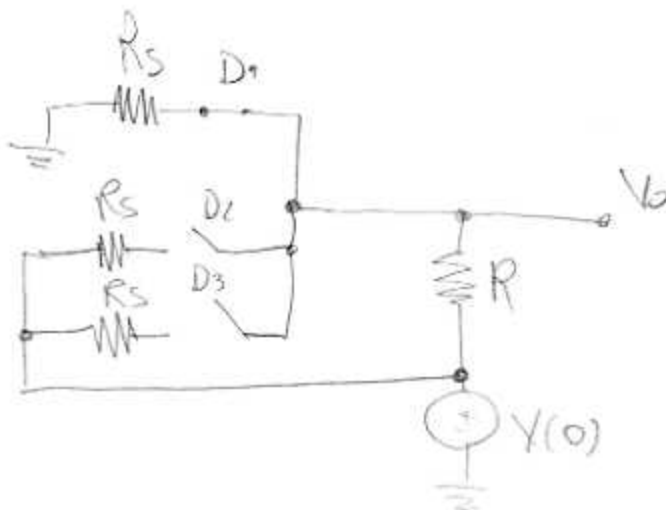If $V_1 = V(1) = 0$ and $V_2 = V_3 = V(0)$ then




$$V_o = V(0) - (V(0) - V(1)) \frac{R}{R + R_s}$$


$$= V(0) \left(1 - \frac{R}{R + R_s} \right) + V(1) \frac{R}{R + R_s}$$

if $R \gg R_s \Rightarrow V_o \approx V(1)$

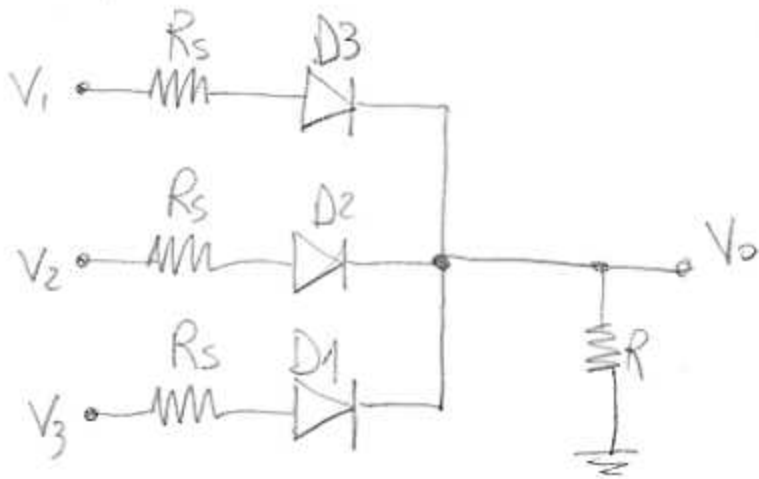This is an OR logic gate. Using the same method, we can build an AND logic gate: 11.16



— COMPUTING THE LOGARITHM

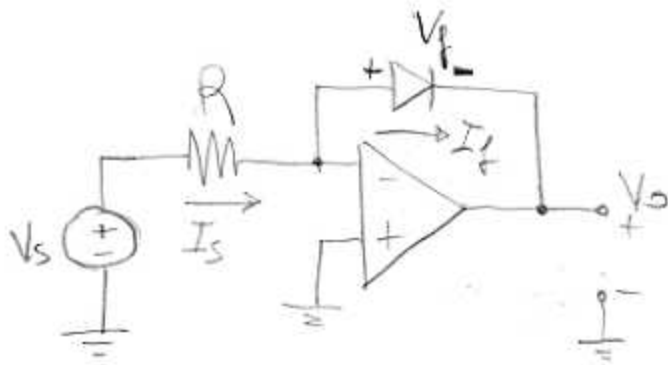

$$V_o = -V_f = -\eta V_T (\ln I_f - \ln I_o) =$$

$$= -\eta V_T \left(\ln \frac{V_s}{R} - \ln I_o \right)$$

$$I_s = \frac{V_s}{R} = I_f$$

$$I_f = I_o \left(e^{\frac{V_f}{\eta V_T}} - 1 \right)$$

In forward polarization


$$e^{\frac{V_f}{\eta V_T}} \gg 1 \quad \text{so:}$$

$$I_f \approx I_o e^{\frac{V_f}{\eta V_T}} \Rightarrow$$

$$\Rightarrow V_f = \eta V_T \ln \frac{I_f}{I_o}$$

$$= \eta V_T (\ln I_f - \ln I_o)$$

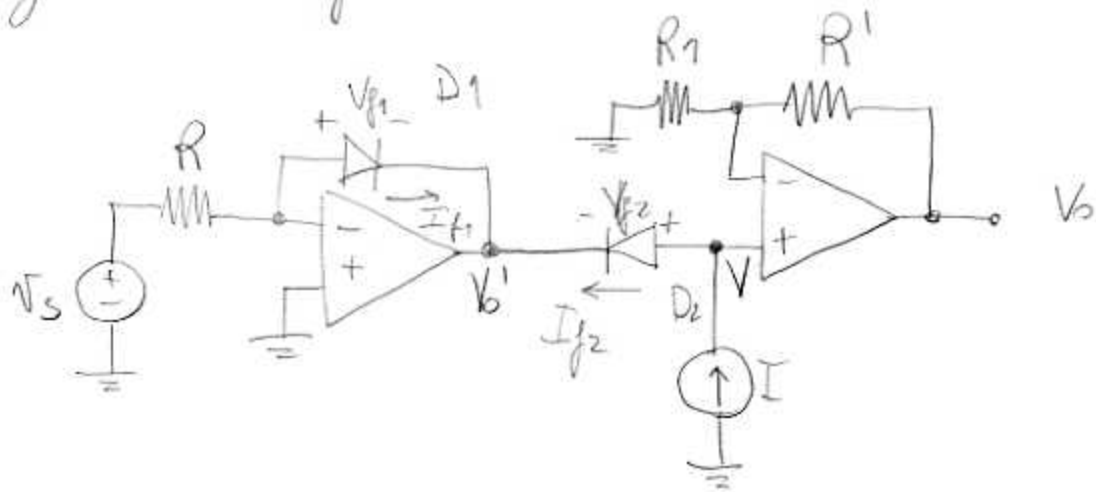The problem with our log. is the constant factor $\ln I_0$ which we want to get rid of:



We use another diode that generate a V_{f2} that is going to be removed from V_{f1} :

$$V = V_{f2} + V_b' = \eta V_T \left(\underbrace{\ln \frac{I}{I_0}}_{\text{from } D_2} - \underbrace{\ln \frac{V_s}{R} + \ln I_0}_{V_b'} \right) =$$

$$= -\eta V_T \ln \frac{V_s}{RI}$$

The output voltage is then: $V_o = \eta V_T \frac{R' + R_1}{R_1} \ln \frac{V_s}{RI}$

We can choose $\frac{R' + R_1}{R_1}$ and RI in such a way

that $V_o = \ln V_s$


- AM DEMODULATOR

11.18

We first introduce the AM (Amplitude Modulation)
Consider a message $m(t)$ (for instance voice) that we want to send over the air. One technique that is used is the amplitude modulation. For simplicity we consider $m(t) = \sin(\omega_m t)$. We can use another sinusoidal signal at a much higher frequency, that we call carrier, and we change the carrier amplitude using $m(t)$:


$$c(t) = (C + m(t)) \sin(\omega_c t) \quad \leftarrow \text{this is the modulated carrier}$$

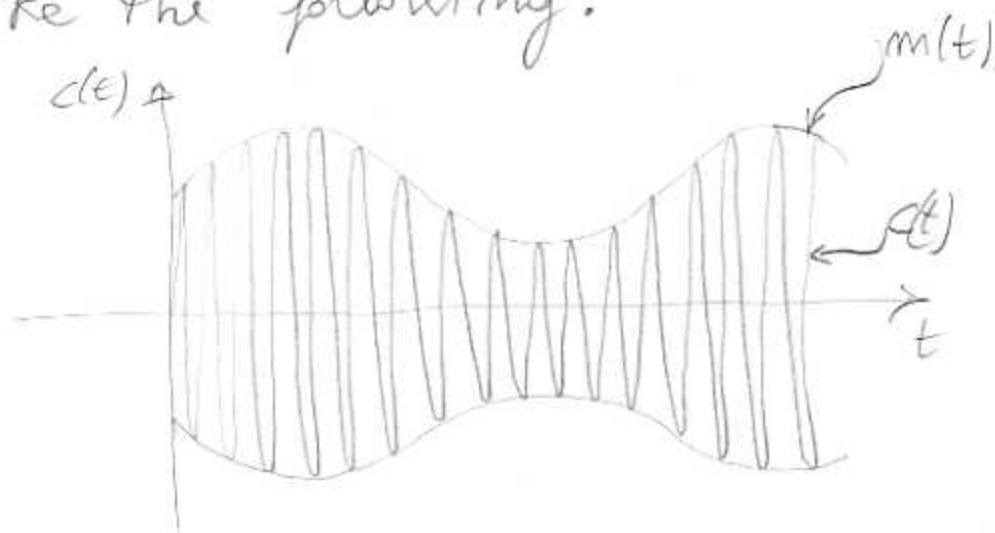C is a constant, without going into details let's pick $C = 2$. The modulated signal looks like the following:



The amplitude of the signal $\sin(\omega_c t)$ is modulated by $m(t)$.

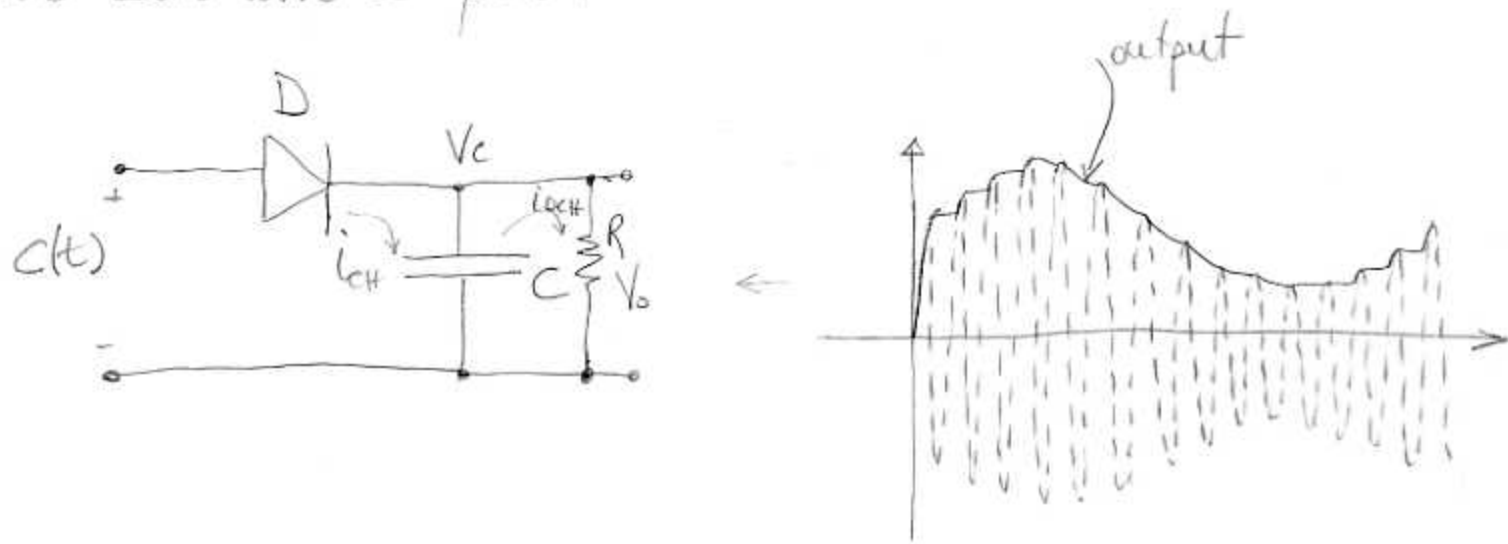If we want to obtain the original signal $m(t)$ we have to follow the peak voltage of $c(t)$. We can use a peak detector:




When $c(t) > V_c$ the current will charge the capacitor, when $c(t) < V_c$ the capacitor will be discharged by R .

The value of RC depends on ω_m and ω_c and it is chosen during the demodulator design. The problem with this circuit is that $c(t) \gg V_f$ otherwise the diode will be always OFF.

But $c(t)$ is the signal received from an antenna or (even after amplification)

is usually very small.

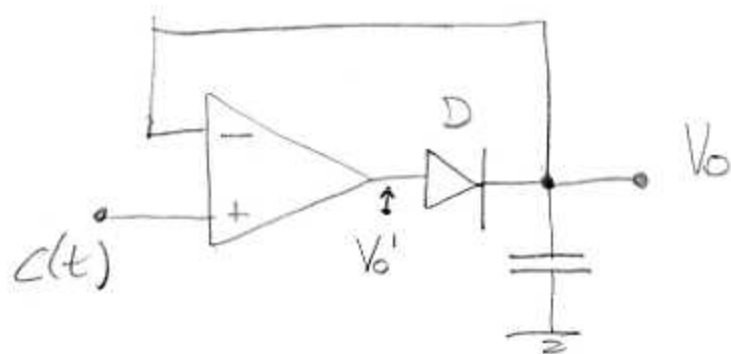To eliminate V_f we can use a different peak detector that uses an op-amp:



$$V_o' = K(c(t) - V_o)$$

In order for D to be on, $V_o' - V_o > V_f$

which means


$$Kc(t) - KV_o - V_o > V_f$$

$$\Rightarrow Kc(t) - (K+1)V_o > V_f$$

And since $K \gg 1$

$$Kc(t) - KV_o > V_f \Rightarrow c(t) - V_o > \frac{V_f}{K}$$

It is equivalent to

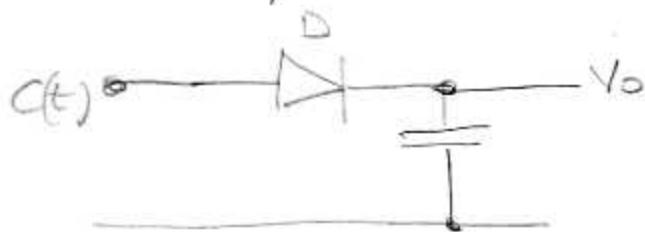


Where D has a threshold voltage $V_o' = \frac{V_f}{K} \approx 0$

because K is very high



- V_{pp} DOUBLER

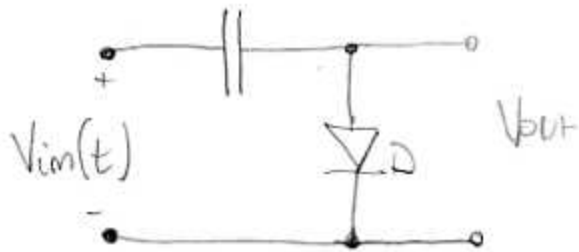Diodes can be used to multiply the peak voltage of a sinusoidal waveform:



$$V_{in}(t) = A \sin(\omega t)$$

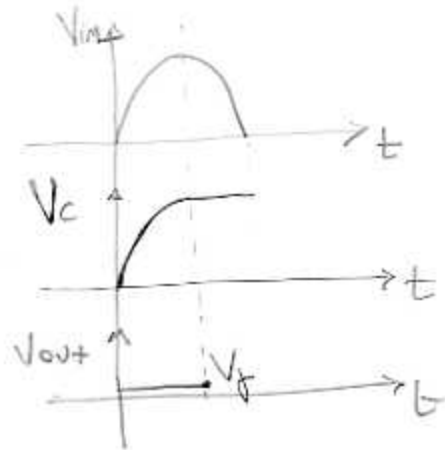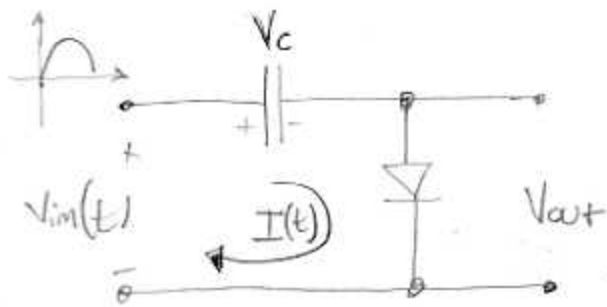During the positive half of the wave the diode is ON and the capacitor charges to A :




V_{out} is equal to the voltage across the diode that is V_f since the diode is ON.

During the negative half the diode is OFF. $V_{out} = V_{in}(t) - V_c$ and since V_{in} is negative the output will reach 0


value equal to $2A$

11.27

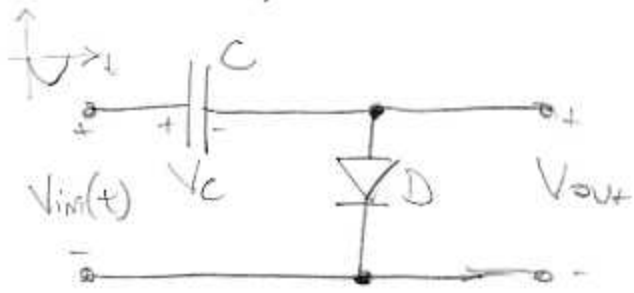


The maximum negative voltage is now $-2A$.

This circuit is used for instance

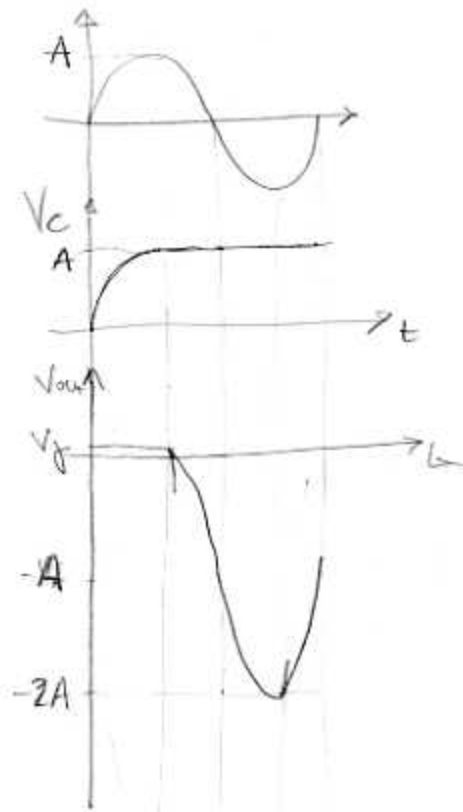


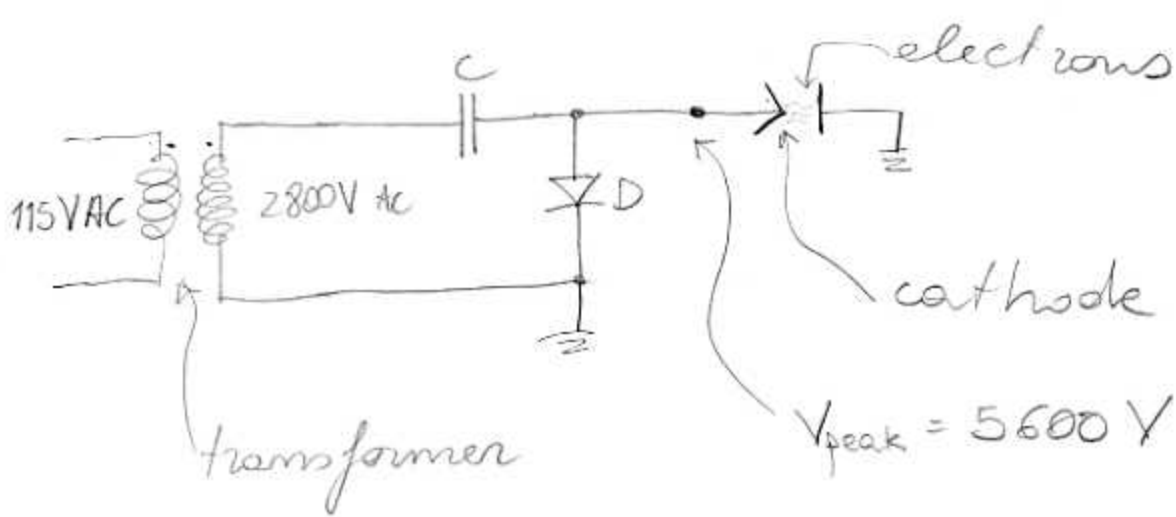in microwave ovens. Microwave ovens cook food using waves at very high frequency (2450 MHz). This device has a cathode which emits electrons that are then subject to a permanent magnetic field. The electrons will move in a resonant cavity and generate the microwave. The cathode requires a very high peak voltage to work. The circuit that is used is like the following.



Using the same strategy we can build a full wave doubler, a tripler a quadrupler and so on.

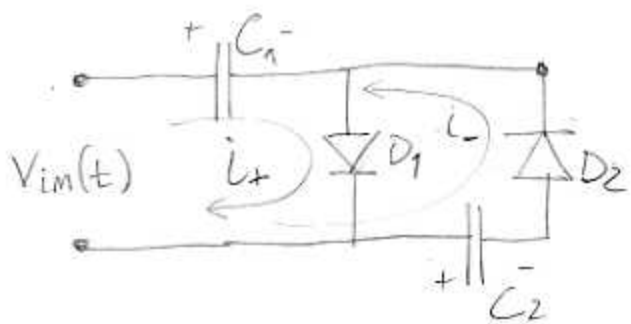The following circuit is a full wave doubler



the simulation result for

$V_{in}(t) = 15 \sin(2\pi 60t)$ is shown in

figure dbl on the following page.

During the first quarter of period D_1 is on and C_1 charges to 15.

Then V_{im} start decreasing and D_1 switches to OFF because the voltage $V_{D1} = V_{im} - V_{C1}$ becomes negative. 11.24

At this point D_2 switches to ON and C_2 charges to 15.

When V_{im} becomes positive again
Then D_1 switches to ON and C_1 charges to 15 again. Now when V_{im} becomes negative again we have the following situation:

$$V_{C1} = 15$$


$$V_{D1} < 0 \Rightarrow D_1 = \text{OFF}$$

$$V_{C2} = 15$$

$$V_{D2} = -V_{im} \Rightarrow D_2 = \text{ON}$$

$$V_{im} < 0$$

The circuit is like this:

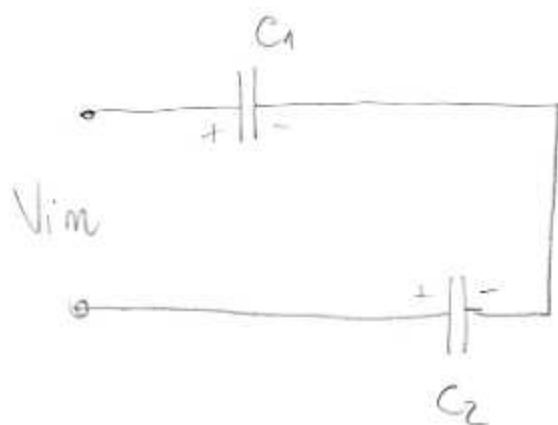


$$V_{C1}(0) = 15 = \frac{Q_1}{C_1}$$

$$V_{C2}(0) = 15 = \frac{Q_2}{C_2}$$




these are the initial conditions

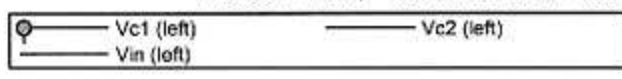Transient - New, halfdoubler2.Sch + halfdoubler2.Anl, 17 July 2004



y	1.43534E+1
x	2.00000E-1

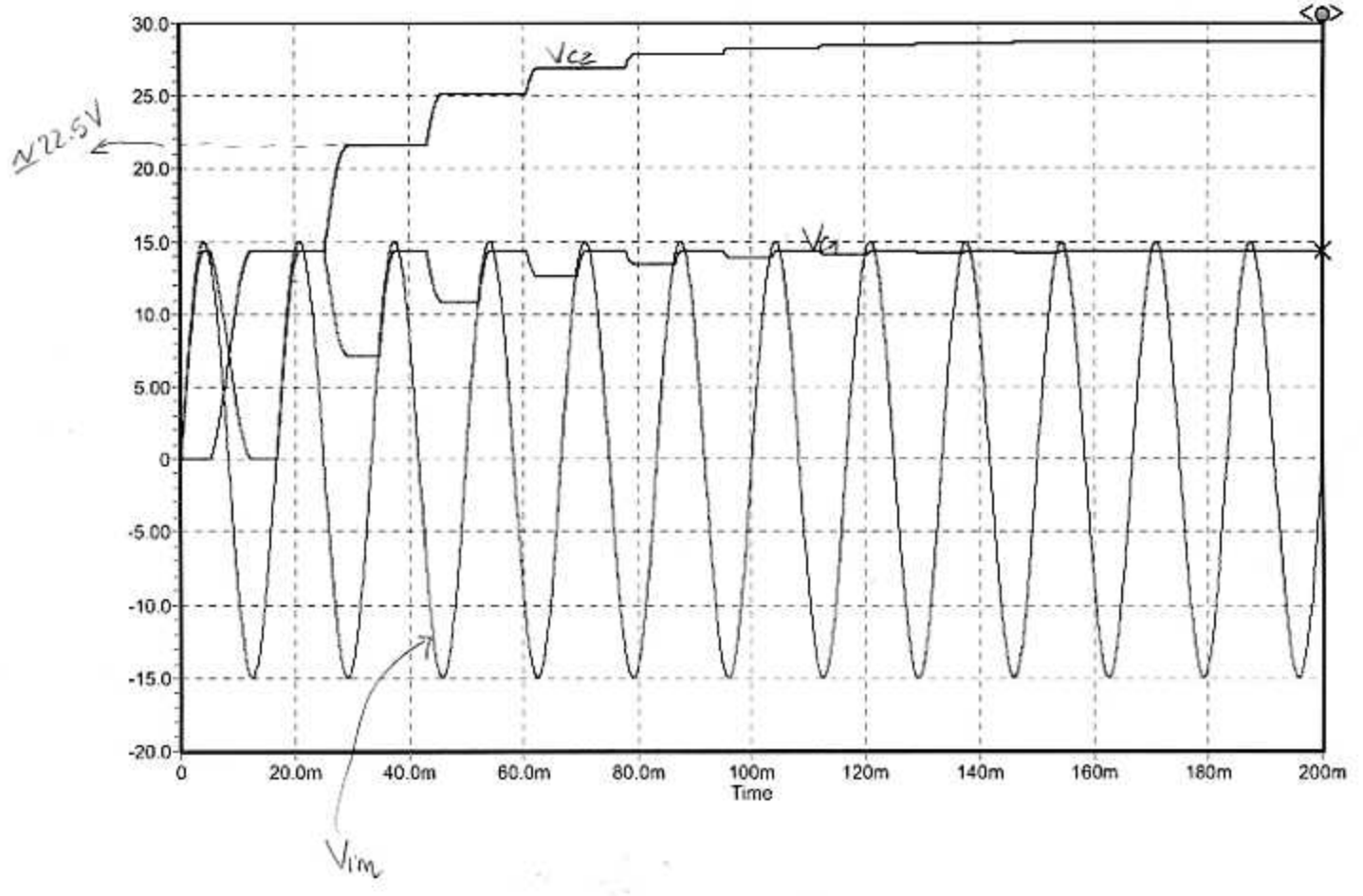

The final conditions are

11.26

$$V_{c1} - V_{c2} = -15$$

$$\frac{Q_1}{C_1} - \frac{Q_2}{C_2} = -15$$



but the total charge has to be the same to the beginning

$$\Rightarrow Q_1 + Q_2 = 15 \cdot C_1 + 15 \cdot C_2$$

$$\Rightarrow Q_1 = 15C_1 + 15C_2 - Q_2$$


$$-\frac{Q_2}{C_1} + 15 + 15\frac{C_2}{C_1} - \frac{Q_2}{C_2} = -15$$

$$-Q_2 \left(\frac{1}{C_1} + \frac{1}{C_2} \right) = -30 - 15\frac{C_2}{C_1}$$

$$\text{If } C_1 = C_2 \Rightarrow 2\frac{Q_2}{C} = +45 \Rightarrow V_{c2} = \frac{45}{2} = 22.5V$$

You can go ahead and compute V_{c1} and then repeat the reasoning for the next cycle.

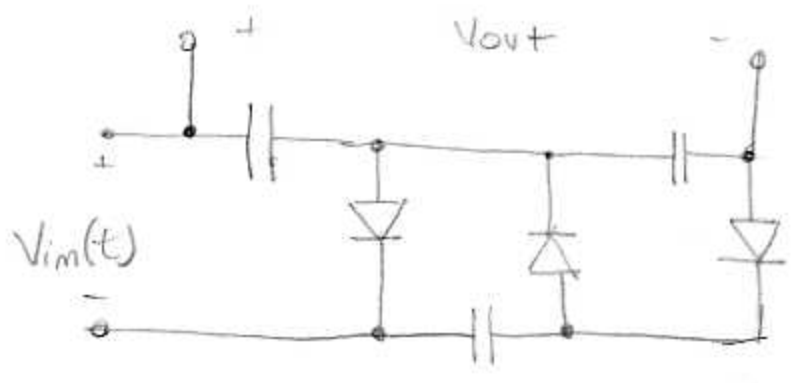If we add another diode and capacitor pair we obtain a voltage tripler:



This circuit is used in CRT
to drive the guides that are used
to focus the electrons beam.