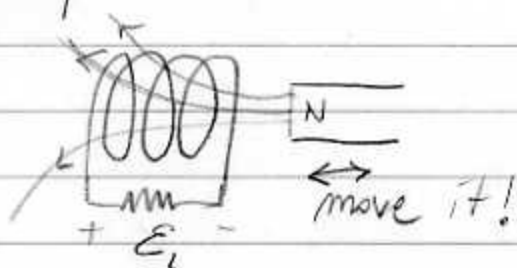


## INDUCTORS

To understand current-voltage relation in an inductor we need to go back to Faraday and Lenz.

Faraday made the following experiment



He moved a magnet in and out a solenoid (coil).

He observed an induced voltage whose value was proportional to the change in magnetic flux:

$$\mathcal{E}_L \propto \frac{d\Phi_B}{dt}$$

Lenz's law says that the voltage that gets generated is such that the current generates a magnetic field which is opposite to the one generating the voltage

This law introduces a minus sign in the equation


$$\mathcal{E}_L = - \frac{d\Phi_B}{dt}$$

The flux is proportional to the current so the induced voltage is proportional to the current

$$\mathcal{E}_L = - L \frac{dI}{dt} \quad L \text{ is called inductance}$$

and its unit of measure is Henry = H.

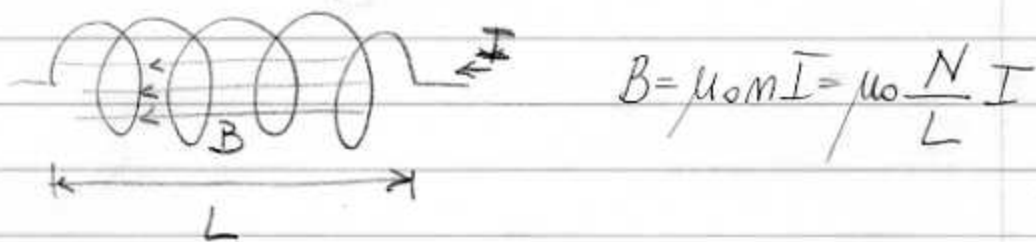The solution of Maxwell's equations for a solenoid gives the following magnetic field



$$B = \mu_0 n I = \mu_0 \frac{N}{L} I$$

where  $N$  is the number of turns. The flux is


$$\Phi_B = N B A = N \mu_0 \frac{N}{L} I A$$

where  $A$  is the area of one turn.

$$\mathcal{E}_L = - \frac{d\Phi_B}{dt} = - \frac{\mu_0 N^2 A}{L} \frac{dI}{dt}$$

$$\Rightarrow L = \frac{\mu_0 N^2 A}{L}$$

Current and voltage in an inductor

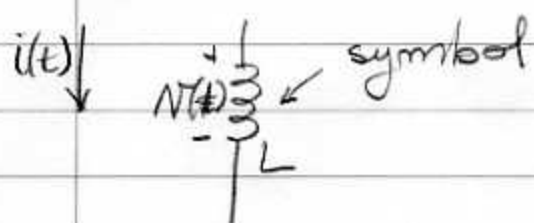

$$V(t) = L \frac{di(t)}{dt}$$

In steady state  $\frac{di(t)}{dt} = 0 \Rightarrow V(t) = 0$

an inductor behaves like a short circuit.

Note that the relation is linear!

Integrating the expression we have

$$i(t) = \frac{1}{L} \int_{t_0}^t V(t) dt + i(t_0)$$

Power and energy in an inductor

$$p(t) = v(t) i(t) = \\ = L i(t) \frac{di(t)}{dt}$$

The energy is the integral:

$$e(t) = \int_{t_0}^t p(t) dt = L \int_{t_0}^t i(t) di(t) =$$


$$= \frac{1}{2} L i^2(t) - \frac{1}{2} L i^2(t_0)$$

This is the energy stored in the inductor at time  $t$ .

## - ANALYSIS OF CIRCUITS IN PRESENCE OF INDUCTORS

As in the case of capacitors, we can apply node-voltage or mesh-current analysis to obtain a system of differential equations.

Consider the following circuit:

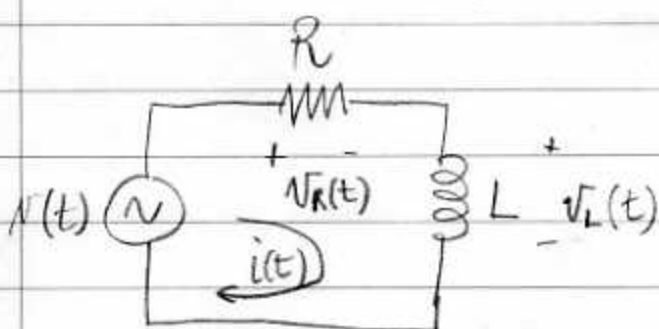

$$v(t) = \sin(2\pi f_0 t) \\ = \sin(\omega_0 t)$$

Using KVL:

$$Ri(t) + v_L(t) = v(t)$$

$$Ri(t) + L \frac{di(t)}{dt} = v(t)$$

Again we can compute  $i(t)$

homogeneous equation:

$$Ri(t) + L \frac{di(t)}{dt} = 0$$

considering  $i(t) = e^{\alpha t}$

$$Re^{\alpha t} + L\alpha e^{\alpha t} = 0 \Rightarrow R + \alpha L = 0$$

$$\Rightarrow \alpha = -\frac{R}{L}$$

$$i(t) = e^{-\frac{R}{L}t}$$

Considering  $\eta(t) = A \sin(\omega_0 t) + B \cos(\omega_0 t)$

$$RA \sin(\omega_0 t) + RB \cos(\omega_0 t) - LA\omega_0 \cos(\omega_0 t) +$$

$$+ LB\omega_0 \sin(\omega_0 t) = \sin(\omega_0 t)$$

$$\begin{cases} RA + LB\omega_0 = 1 \\ RB - LA\omega_0 = 0 \end{cases} \begin{cases} RA + \frac{L^2 A \omega_0^2}{R} = 1 \\ B = \frac{L}{R} A \omega_0 \end{cases}$$

$$\begin{cases} A = \frac{1}{R + \frac{\omega_0^2 L^2}{R}} = \frac{R}{R^2 + \omega_0^2 L^2} \\ B = \frac{L}{R} \frac{R}{R^2 + \omega_0^2 L^2} \quad \omega_0 = \frac{\omega_0 L}{R^2 + \omega_0^2 L^2} \end{cases}$$

call  $L/R = \tau$

$$A = \frac{1}{R(1 + \omega_0^2 \tau^2)} \quad B = \frac{\omega_0 \tau}{R(1 + \omega_0^2 \tau^2)}$$

a particular solution of the differential equation is:

$$i(t) = \frac{1}{R(1 + \omega_0^2 \tau^2)} \sin(\omega_0 t) + \frac{\omega_0 \tau}{R(1 + \omega_0^2 \tau^2)} \cos(\omega_0 t) =$$

$$= \sqrt{A^2 + B^2} \sin\left(\omega_0 t + \arctg\left(-\frac{B}{A}\right)\right)$$

$$\sqrt{A^2 + B^2} = \frac{1}{1 + \omega_0^2 \tau^2} \sqrt{\frac{1}{R^2} + \frac{\omega_0^2 \tau^2}{R^2}} =$$

$$= \frac{1}{R \sqrt{1 + \omega_0^2 \tau^2}}$$

$$i(t) = \frac{1}{R \sqrt{1 + \omega_0^2 \tau^2}} \sin(\omega_0 t + \alpha)$$

↑  
phase

$$V_L(t) = L \frac{di(t)}{dt} = -\frac{L}{R} \frac{\omega_0}{\sqrt{1 + \omega_0^2 \tau^2}} \cos(\omega_0 t + \alpha)$$

$$v_L(t) = \frac{\omega_0 \tau}{\sqrt{1 + \omega_0^2 \tau^2}} \sin(\omega_0 t + \alpha')$$

Again the amplitude depends on the frequency.

If  $\omega_0 = 0 \Rightarrow$

$$\lim_{\omega_0 \rightarrow 0} \frac{\omega_0 \tau}{\sqrt{1 + \omega_0^2 \tau^2}} = 0$$

$$\lim_{\omega_0 \rightarrow \infty} \frac{\omega_0 \tau}{\sqrt{1 + \omega_0^2 \tau^2}} = 1$$

This is an high-pass filter whose cut-off frequency is ( $\omega_0^*$ ):

$$\frac{\omega_0^* \tau}{\sqrt{1 + \omega_0^{*2} \tau^2}} = \frac{1}{\sqrt{2}} \Rightarrow \frac{\omega_0^{*2} \tau^2}{1 + \omega_0^{*2} \tau^2} = \frac{1}{2}$$

$$2\omega_0^{*2} \tau^2 = 1 + \omega_0^{*2} \tau^2 \Rightarrow \omega_0^{*2} \tau^2 = 1 \Rightarrow \omega_0^* = \frac{1}{\tau}$$




## - SECOND ORDER CIRCUITS (ONLY FEW THINGS)

We can combine inductors and capacitors in circuits. Now since

$$i_c(t) = C \frac{dV_c(t)}{dt} \quad V_L(t) = L \frac{di(t)}{dt}$$

it may happen that part (or all) the capacitor current flows into the inductor giving a double derivative.

Consider the following circuit

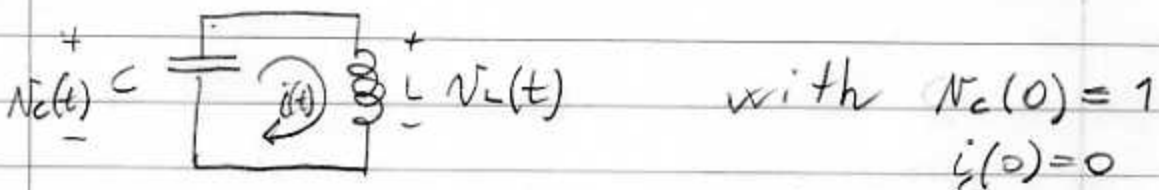

we have  $V_c(t) = V_L(t) = L \frac{di(t)}{dt} =$

$$= LC \frac{d^2 V_c(t)}{dt^2}$$

$$\frac{d^2 v_c(t)}{dt^2} - \frac{1}{LC} v_c(t) = 0$$


consider the solution  $v_c(t) = A \sin(\omega t + \phi)$

$$-A\omega^2 \sin(\omega t + \phi) - \frac{1}{LC} A \sin(\omega t + \phi) = 0$$

$$\omega^2 = \frac{1}{LC} \Rightarrow \omega = \frac{1}{\sqrt{LC}}$$

Since  $v_c(0) = 1$  and  $i_c(0) = 0$   
then it must be  $\phi = \pi/2$  and  $A = 1$

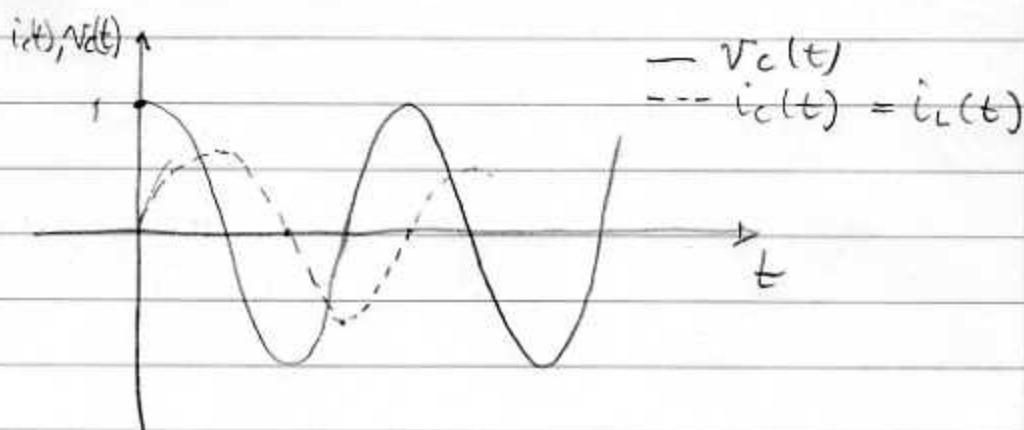The voltage across the capacitor is  
a sinusoid:



what is happening? look at  
the energy:

$$w_c(t) = \frac{1}{2} C v_c^2(t)$$

$$w_L(t) = \frac{1}{2} L i_L^2(t) = \frac{1}{2} L i_c^2(t)$$

so when the energy stored in the capacitor is maximum the energy in the inductor is zero and vice-versa.

The two objects are exchanging energy that was originally stored in the capacitor.

This circuit is lossless because  $C$  and  $L$  do not dissipate (absorb) energy. To see this, compute the total energy absorbed by, for instance,  $C$

$$\begin{aligned} P &= \lim_{T \rightarrow \infty} \frac{1}{T} \int_0^T v(t) i(t) dt \\ &= \lim_{T \rightarrow \infty} \frac{1}{T} \int_0^T \sin(\omega t) \cos(\omega t) dt \end{aligned}$$

and the integral is known to be 0 !!