


EECS 42 Introduction to Electronics for Computer Science Andrew R. Neureuther

Lecture #9 Node Equations

- Recap and Checking Solutions
 - Applications to parallel and bridge
 - Midterm Exam Topics
 - Thevenin/Norton Eq. Cir. Review
- <http://inst.EECS.Berkeley.EDU/~ee42/>

FLOATING VOLTAGE SOURCES (cont.)

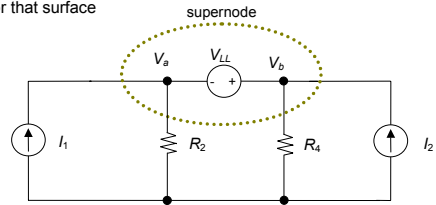Use a Gaussian surface to enclose the floating voltage source; write KCL for that surface



We have two unknowns: V_a and V_b .

We obtain one equation from KCL at supernode: $I_1 - \frac{V_a}{R_2} - \frac{V_b}{R_4} + I_2 = 0$

We obtain a second "auxiliary" equation from the property of the voltage source: $V_{LL} = V_b - V_a$ (often called the "constraint")

⇒ 2 Equations & 2 Unknowns

Game Plan 02/24/03

Monday 02/24/03

- Node Equations: S&O 2.3, 2.5, 2.6; Exam Topics; Thevenin Review

Wednesday 02/26/03: Sheila Ross instructor


- Quiz on Basic Circuit Analysis and Transients
- Logic – Functions, Tables, Circuit Symbols 391-406

Next (7th) Week:

- Monday 3/3: Brief Exam Review; Logic Synthesis
- Monday 3/3: TA Exam Review Session (247 Cory?)
- Wednesday: Midterm In Class, Closed Book

Problem Set #5 – Out 2/19/03 - Due 2/26/03 2:30 in box in 240 Cory; Node Analysis: basic, supernode, advanced; review: circuit analysis, transients
No Problem Set Due 7th week, Problem set #6 out Monday 3/3 and due at 2:30 3/10 in box in 240 Cory

ANOTHER EXAMPLE

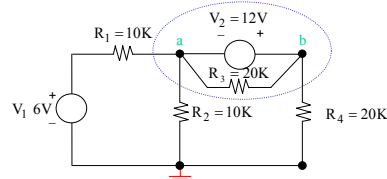

1 Choose reference node (can it be chosen to avoid floating voltage source?)

2 Label unknowns V_a and V_b

3 Equation at supernode: $\frac{V_1 - V_a}{R_1} = \frac{V_b}{R_4} + \frac{V_a}{R_2} \rightarrow V_a \left(\frac{1}{R_1} + \frac{1}{R_2} \right) + \frac{V_b}{R_4} = \frac{V_1}{R_1}$

4 Auxiliary equation: $V_b - V_a = V_2 \rightarrow V_a - V_b = -V_2$

$$\text{Solve: } V_a \left(\frac{R_4}{R_1} + \frac{R_4}{R_2} + 1 \right) = \frac{V_1 R_4}{R_1} - V_2 \quad \text{SOLUTION: } V_a = 0$$

$$V_b = V_a + V_2 \quad V_b = 12$$

FORMAL CIRCUIT ANALYSIS USING KCL: NODAL ANALYSIS


(Memorize these steps and apply them rigorously!)

- 1 Choose a Reference Node ---
- 2 Define unknown node voltages (those not fixed by voltage sources)
- 3 Write KCL at each unknown node, expressing current in terms of the node voltages (using the constitutive relationships of branch elements*)
- 4 Solve the set of equations (N equations for N unknown node voltages)

* With inductors or floating voltages we will use a modified Step 3: The Supernode Method – see slide 10

NODAL ANALYSIS EXAMPLE

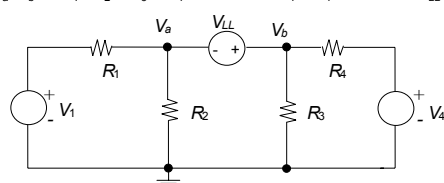Find V_a, V_b if $R_1 = R_2 = R_3 = R_4 = 1\text{M}\Omega$, and $V_1 = V_4 = 1.5\text{V}$ with $V_{LL} = 1\text{V}$




Solution: At supernode enclosing nodes a and b :

$$(V_1 - V_a)/R_1 - V_a/R_2 = V_b/R_3 + (V_b - V_4)/R_4 \quad \text{and}$$

$$V_b = V_a + V_{LL} \quad \text{Thus: } V_a = 0.25 \quad V_b = 1.25 \quad \text{Be sure to check answer with KCL!}$$

CHECK ANSWER WITH KCL Version Date 02/24/03

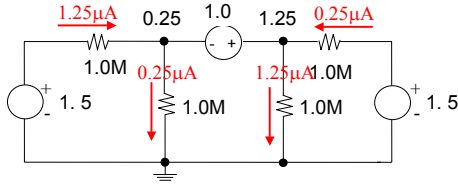Is $V_a = 1.25$ and $V_b = 0.25$ if $R_1 = R_2 = R_3 = R_4 = 1M\Omega$, and $V_1 = V_4 = 1.5V$ with $V_{LL} = 1V$????




KCL at the Supernode: $0.25 - 1.25 + 1.25 - 0.25 = 0$
 Clearly the current into the supernode is zero and we have verified that the solution is correct. :

Version Date 02/24/03

IDENTIFYING SERIES AND PARALLEL COMBINATIONS (cont.)

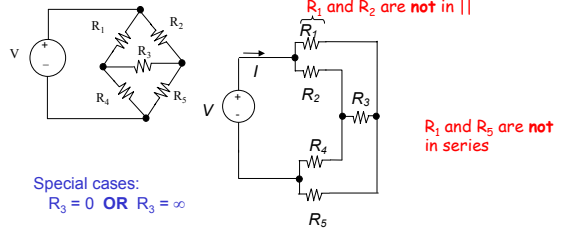Some circuits *must* be analyzed (not amenable to simple inspection)




Special cases:
 $R_3 = 0$ OR $R_3 = \infty$

Example: $R_3 = 0 \Rightarrow R_1 \parallel R_2; R_4 \parallel R_5$ in series; $R_{eq} = R_1 \parallel R_2 + R_4 \parallel R_5$

OR IF $R_3 = \infty \Rightarrow (R_1 + R_2) \parallel (R_4 + R_5)$

RESISTORS IN PARALLEL Version Date 02/24/03

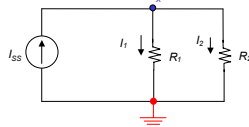- 1 Select Reference Node
- 2 Define unknown node voltages



Note: $I_{SS} = I_1 + I_2$, i.e.,

$$I_{SS} = \frac{V_X}{R_1} + \frac{V_X}{R_2} \Rightarrow V_X = I_{SS} \cdot \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} = I_{SS} \cdot \frac{R_1 R_2}{R_1 + R_2}$$

RESULT 1 EQUIVALENT RESISTANCE: $R_{||} = R_1 \parallel R_2 = \frac{R_1 R_2}{R_1 + R_2}$

RESULT 2 CURRENT DIVIDER: $I_1 = \frac{V_X}{R_1} = I_{SS} \times \frac{R_2}{R_1 + R_2}$

$$I_2 = \frac{V_X}{R_2} = I_{SS} \times \frac{R_1}{R_1 + R_2}$$

Version Date 02/24/03

First Midterm Exam: Topics


- Basic Circuit Analysis (KVL, KCL)
- Equivalent Circuits and Graphical Solutions for Nonlinear Loads
- Transients in Single Capacitor Circuits
- Node Analysis Technique and Checking Solutions

Exam is in class 3:10-4:03 PM, Closed book, Closed notes, Bring a calculator, Paper provided

Version Date 02/24/03

IDENTIFYING SERIES AND PARALLEL COMBINATIONS

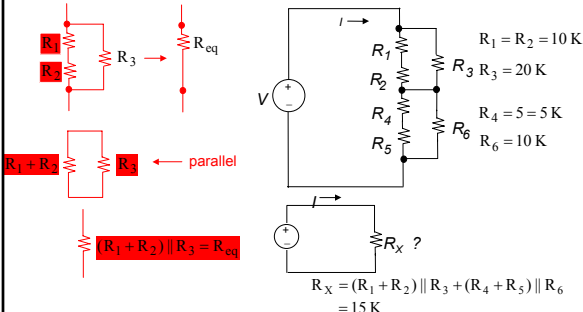
Use series/parallel equivalents to simplify a circuit before starting KVL/KCL



Please note the order of math operators here!


Version Date 02/24/03

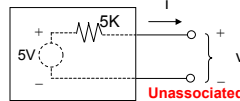I-V CHARACTERISTICS OF LINEAR TWO-TERMINAL NETWORKS



Apply v , measure i , or vice versa

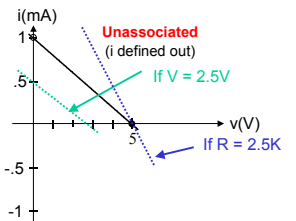Consider how the graph changes with differences in V and R .




First consider change in V , eg $V = 2.5V$, not $5V$

Now consider change in R (with V back at $5V$)

Clearly by varying V and R we can produce an arbitrary linear graph ... in other words this circuit can produce *any* linear graph

FINDING V_T , R_T BY MEASUREMENT

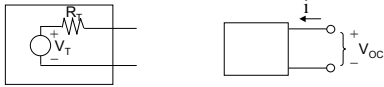1 V_T is the open-circuit voltage V_{OC} (i.e., $i = 0$)



2a) If we short the output clearly $I = -V_T / R_T$ thus R_T is the ratio of V_{OC} to $-i_{SC}$, the short-circuit current



$$R_T = -\frac{V_{OC}}{i_{SC}}$$


2b) If $V_T = 0$, you need to apply test voltage, then



$$R_T = \frac{V_{TEST}}{i}$$

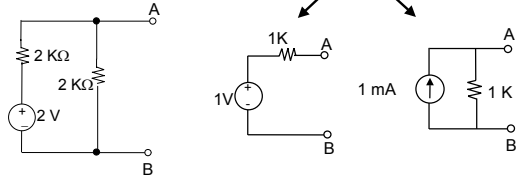EXAMPLE 1, Continued

In what sense is this circuit equivalent to these?




They have identical I-V characteristics and therefore have
The same open circuit voltage
The same short circuit current

FINDING V_T , R_T BY ANALYSIS

- 1 Calculate V_{OC} . $V_T = V_{OC}$
- 2 Turn off all independent sources and find equivalent R at terminals


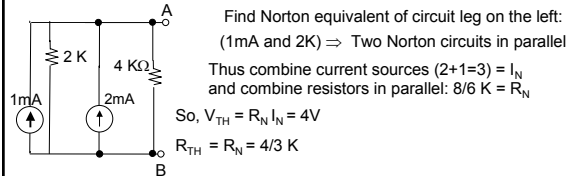
EXAMPLE 2

Find the Thévenin and Norton equivalents of:




Find Norton equivalent of circuit leg on the left:
(1mA and 2K) \Rightarrow Two Norton circuits in parallel
Thus combine current sources ($2+1=3$) = I_N
and combine resistors in parallel: $8/6 K = R_N$

So, $V_{TH} = R_N I_N = 4V$
 $R_{TH} = R_N = 4/3 K$

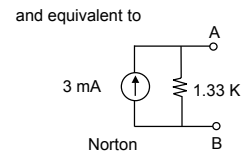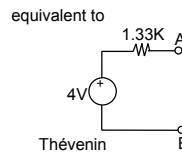

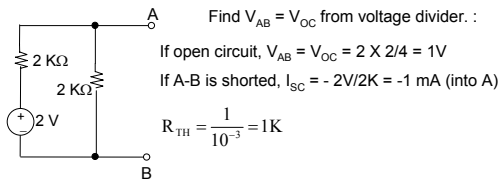EXAMPLE 1



Find the Thévenin and Norton equivalents of:



Find $V_{AB} = V_{OC}$ from voltage divider. :


If open circuit, $V_{AB} = V_{OC} = 2 \times 2/4 = 1V$
If A-B is shorted, $i_{SC} = -2V/2K = -1 mA$ (into A)

$$R_{TH} = \frac{1}{10^{-3}} = 1K$$

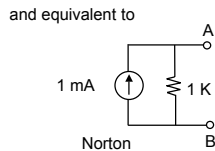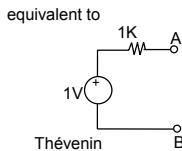

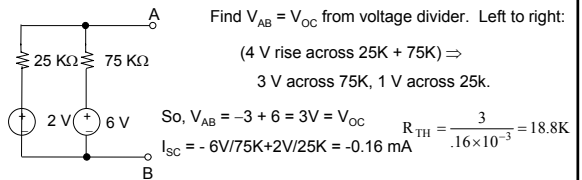EXAMPLE 3

Find the Thévenin and Norton equivalents of:



Find $V_{AB} = V_{OC}$ from voltage divider. Left to right:
(4 V rise across 25K + 75K) \Rightarrow
3 V across 75K, 1 V across 25K.

So, $V_{AB} = -3 + 6 = 3V = V_{OC}$
 $i_{SC} = -6V/75K + 2V/25K = -0.16 mA$
 $R_{TH} = \frac{3}{.16 \times 10^{-3}} = 18.8K$

