

EECS 42 Intro. electronics for CS Spring 2003 Lecture 14: 03/17/03 A.R. Neureuther  
Version Date 03/16/03

## EECS 42 Introduction to Electronics for Computer Science

**Andrew R. Neureuther**

### Lecture # 14 Circuit analysis with dependent sources (4.1-4.3)

- A) Node Equations
- B) Equivalent Sources
- C) Amplifier Parameters:  
Gain,  $R_{IN}$ ,  $R_{OUT}$
- D) Non-Ideal Op-Amp Model

<http://inst.EECS.Berkeley.EDU/~ee42/>

Copyright 2001, Regents of University of California

EECS 42 Intro. electronics for CS Spring 2003 Lecture 14: 03/17/03 A.R. Neureuther  
Version Date 03/16/03

### EXAMPLE OF NODAL ANALYSIS WITH DEPENDENT SOURCES

Standard technique, except an additional equation is needed if the dependent variable is an unknown current as here. Note Vb is redundant.

$$I = V_a / R_2 + (V_a - R_m I_2) / R_3 \quad \text{and} \quad I_2 = V_a / R_2$$

Solving:  $I = V_a (1/R_2 + 1/R_3 - R_m / R_2 R_3)$

$$\text{So } V_a = I R_2 R_3 / (R_2 + R_3 - R_m)$$

Copyright 2001, Regents of University of California

EECS 42 Intro. electronics for CS Spring 2003 Lecture 14: 03/17/03 A.R. Neureuther  
Version Date 03/16/03

## Game Plan 03/17/03

**Monday 03/17/04**

- ☐ Monday: Circuit analysis with dependent sources (4.1-4.2)

**Wednesday 03/19/03:**

- ☐ Comparators and op-amps (Comparator handout)

**Next (10<sup>th</sup>) Week: After Spring Recess**

- ☐ Monday: 3/31/03 Logic with State Dependent Device 593-595, 604-605
- ☐ Wednesday: 4/02/03 Logic Static: Voltage Transfer Characteristic 606, Handout

**Problem set #7: out Wednesday 3/12 and due at 2:30 3/19 in box in 240 Cory – basic dependant sources and Op-Amp circuits**

**Problem set #8: Half-Set - out Monday 3/17 and due at 2:30 4/02 in box in 240 Cory – input/output impedance, comparators**

Copyright 2001, Regents of University of California

EECS 42 Intro. electronics for CS Spring 2003 Lecture 14: 03/17/03 A.R. Neureuther  
Version Date 03/16/03

### THEVENIN EQUIVALENT WITH DEPENDENT SOURCES

Method 1: Use  $V_{oc}$  and  $I_{sc}$  as usual to find  $V_T$  and  $R_T$  (and  $I_N$  as well)

Method 2: To find  $R_T$  by the “ohmmeter method” turn off only the *independent* sources; let the dependent sources just do their thing.

See examples in text (such as Example 4.3).

This method also works when computing **incremental signals** such as a change in the source  $V_S$  (given by  $\Delta V_S$  or  $v_s$ ) produces a change in  $V_{IN}$  or  $V_{OUT}$ , (given by  $\Delta V_{IN}$  or  $\Delta V_{OUT}$  also written  $v_{IN}$  and  $v_{OUT}$ ), and their ratio called the small-signal gain ( $\Delta V_{OUT} / \Delta V_S$ ) or ( $v_{OUT} / v_s$ )

Copyright 2001, Regents of University of California

EECS 42 Intro. electronics for CS Spring 2003 Lecture 14: 03/17/03 A.R. Neureuther  
Version Date 03/16/03

### The 4 Basic Linear Dependent Sources

Constant of proportionality

Parameter being sensed

Output

**Voltage-controlled voltage source ...  $V = A_v V_{cd}$**

**Current-controlled voltage source ...  $V = R_m I_c$**

**Current-controlled current source ...  $I = A_i I_c$**

**Voltage-controlled current source ...  $I = G_m V_{cd}$**

Copyright 2001, Regents of University of California

EECS 42 Intro. electronics for CS Spring 2003 Lecture 14: 03/17/03 A.R. Neureuther  
Version Date 03/16/03

### NODAL ANALYSIS WITH DEPENDENT SOURCES

Example : Find Thévenin equivalent of stuff in red box.

With method 2 we first find open circuit voltage ( $V_T$ ) and then we “measure” input resistance with source  $I_{SS}$  turned off.

You verify the solution:

$$V_{TH} = \frac{-I_{SS} R_6 (R_2 + A R_3)}{R_2 + R_3 + R_6} \quad R_{TH} = \frac{R_2 (R_6 + R_3)}{R_2 + R_3 + R_6}$$

Copyright 2001, Regents of University of California

EECS 42 Intro. electronics for CS Spring 2003 Lecture 14: 03/17/03 A.R. Neureuther  
Version Date 03/16/03

### EXAMPLE CIRCUIT WITH MULTIPLE SOURCES

**Original circuit**

**Circuit with independent sources turned to zero**

Note  $R_L$  has been rotated down.

Copyright 2001, Regents of University of California

EECS 42 Intro. electronics for CS Spring 2003 Lecture 14: 03/17/03 A.R. Neureuther  
Version Date 03/16/03

### EXAMPLE CIRCUIT: INCREASED INPUT RESISTANCE

Add resistor  $R_E$

The output has been assumed to be shorted  $V_{OUT} = 0$

**Analysis:** apply  $i_{TEST}$  and evaluate  $v_{TEST}$

$$v_{IN} = R_{IN}i_{TEST} \quad v_{TEST} = R_{IN}i_{TEST} + v_E$$

**KCL**  $\frac{v_E}{R_E} + \frac{v_E}{R_O} - i_{TEST} - G_m v_{IN} = 0$

**Intuitive Explanation:**  $R_E$  puts  $R_{IN}$  on a node whose voltage increases in response to current in  $R_{IN}$ .

Check for special case for  $R_O$  infinite  $\frac{v_{TEST}}{i_{TEST}} = R_{IN} + (1 + G_m R_{IN})R_E$

Finish this in the homework

Copyright 2001, Regents of University of California

EECS 42 Intro. electronics for CS Spring 2003 Lecture 14: 03/17/03 A.R. Neureuther  
Version Date 03/16/03

### EXAMPLE CIRCUIT: GAIN = $(\Delta V_{OUT} / \Delta V_S) = (v_{OUT}/v_S)$

$$R_{IN} = \frac{R_a R_b}{R_a + R_b} \quad v_{IN} = \frac{R_{IN}}{R_S + R_{IN}} v_S$$

$$v_{OUT} = -G_m v_{IN} \frac{R_O R_L}{R_O + R_L} = -G_m \frac{R_{IN}}{R_S + R_{IN}} \frac{R_O R_L}{R_O + R_L} v_S$$

**Input voltage divider and output current divider reduce the gain**

Copyright 2001, Regents of University of California

EECS 42 Intro. electronics for CS Spring 2003 Lecture 14: 03/17/03 A.R. Neureuther  
Version Date 03/16/03

### EXAMPLE CIRCUIT: INCREASED OUTPUT RESISTANCE

Add resistor  $R_E$

The input has been assumed to be shorted  $v = 0$

**Analysis:** apply  $i_{TEST}$  and evaluate  $v_{TEST}$

Unknowns:  $i_{TEST}$ ,  $v_{TEST}$ ,  $v_{IN}$ ,  $v_E$

Need 3 equations to find the ratio of  $i_{TEST} / v_{TEST}$

$v_{IN} = -v_E$  and is **not zero!**

KCL at  $v_E$   
KVL at  $v_{OUT}$

**Intuitive Explanation:**  $G_m v_{IN}$  burps current which has to also go through  $R_O$ . This raises  $v_{TEST}$  and the output impedance  $v_{TEST}/i_{TEST}$

Try a bag. It is even easier

Finish this in the homework

Copyright 2001, Regents of University of California

EECS 42 Intro. electronics for CS Spring 2003 Lecture 14: 03/17/03 A.R. Neureuther  
Version Date 03/16/03

### EXAMPLE CIRCUIT: INPUT/OUTPUT RESISTANCE

$$R_{IN} = \frac{R_a R_b}{R_a + R_b}$$

Output does not feed back to input

$$R_{OUT} = R_O$$

Assume  $v_S = 0 \Rightarrow v_{IN} = 0 \Rightarrow$  no current in dependent source

Can circuit design improve  $R_{IN}$  and  $R_{OUT}$  or do we need better devices?

Copyright 2001, Regents of University of California

EECS 42 Intro. electronics for CS Spring 2003 Lecture 14: 03/17/03 A.R. Neureuther  
Version Date 03/16/03

### NON-IDEAL OP-AMPS

JUST ANOTHER CASE OF ANALYSIS WITH DEPENDENT SOURCES

Example:

Circuit (assume  $\infty$ )

**Analysis:** Outline your circuit analysis strategy here.

**Hint:** 1) Find  $V_+$  in terms of  $V_0$ , 2) plug into expression for  $V_0$  and then 3) solve for  $V_0$  which appears on both sides of the equation.

**Answer:**  $V_0 = V_{IN} \frac{A(R_1 + R_2)}{(A+1)R_1 + R_2} \approx V_{IN} \frac{R_1 + R_2}{R_1} = 10V_{IN}$  if  $A \rightarrow \infty$

Copyright 2001, Regents of University of California