

# EECS 42 Introduction to Electronics for Computer Science Andrew R. Neureuther

## Lecture # 20 Logic Transients

Handout of Monday Lecture.

**A) 2<sup>nd</sup> Midterm Review (Cont.)**

**B) Latch circuit to hold/release signals**

**C) Cascade CMOS elements with latches**

**D) Logic Feedback creates memory**

<http://inst.EECS.Berkeley.EDU/~ee42/>

## Game Plan 04/14/03

**Last Week: Logic Delay; resistor model, CMOS operation and delay**

**Monday 4/14/03:**

- 2<sup>nd</sup> Midterm review (Cont.)
- CMOS Latch and use in logic cascade
- Feedback in logic to produce memory

**Wednesday 04/09/03:**


- 2<sup>nd</sup> Midterm

**Next (13th) Week: Diodes and MOS Operation**


**No Problem set for 4/16 as Midterm 4/16: Lectures 1-17 with emphasis on Lectures 10-17; Review Session Monday 5:30-7PM**

**Problem set #10 for 4/23: Logic Delay**
 
## Composite Current Plot for the 42S\_NMOS Circuit with 200kΩ Load to Ground



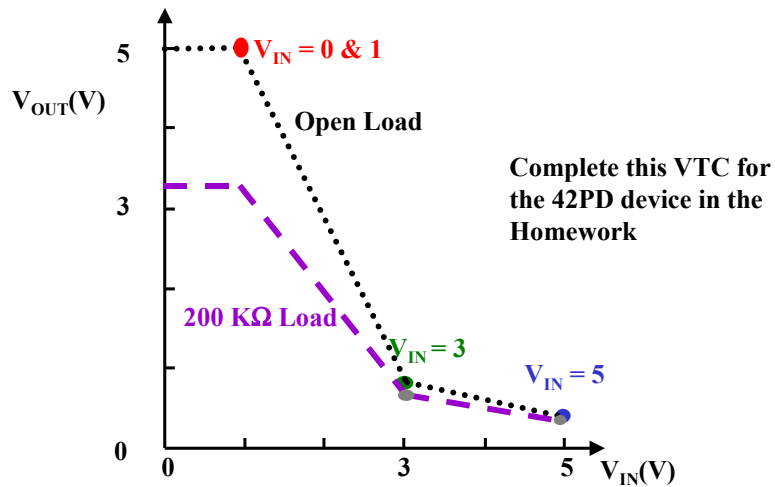
## Voltage Transfer Function for the 42S\_NMOS Logic Circuit w/wo Load



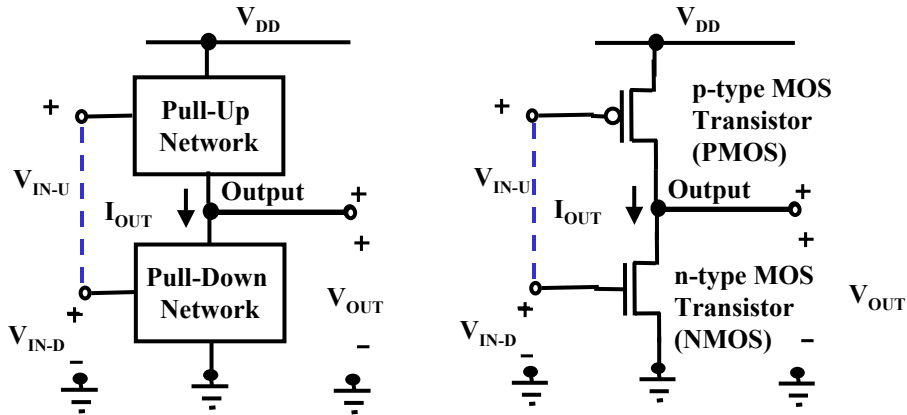
## Transistor Inverter Example

It may be simpler to just **think of PMOS and NMOS transistors** instead of a general 3 terminal pull-up or pull-down devices or networks.




Copyright 2001, Regents of University of California
 
## Composite $I_{OUT}$ vs. $V_{OUT}$ to Find Points That Satisfies Both Devices for Each $V_{IN}$



Copyright 2001, Regents of University of California

 
## Voltage Transfer Function for the Complementary Logic Circuit



Copyright 2001, Regents of University of California
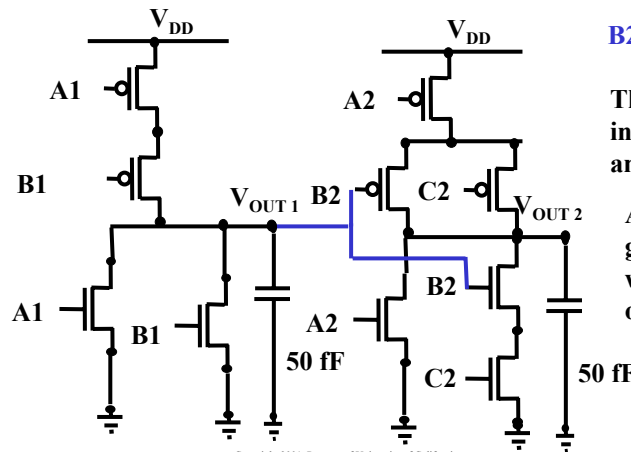
## Logic Gate Cascade

To avoid large resistance due to many gates in series, logic functions with 4 or more inputs are usually made from cascading two or more 2-4 input blocks.




Copyright 2001, Regents of University of California

## Data Synchronization problem

- Combinatorial logic gates can give incorrect answers prematurely and may take several gate propagation delays produce an answer.
- Clocks (signals as to when to proceed) and latches (which capture and hold the correct outputs) can provide synchronization.

## Latch Controlled by a Clock

 


An inverter with clocked devices in series can form a latch.

When the clock  $\phi$  is high its complement  $\bar{\phi}$  is low and the inverter operates.

To synchronize the data the clock remains low until the data is correct at all locations on the chip. When the clock goes high the inverse of the data is passed.

## Latch Work Best In Pairs

 


The first stage operates while the clock is low and inverts and amplifies the arriving signal and charges or discharges  $C_{L1}$ .

The second stage operates while the clock is high and inverts the signal on  $C_{L1}$  to charge or discharge  $C_{L2}$  and downstream logic gate inputs.

Copyright 2001, Regents of University of California
 
## A Double Latch is an Edge-Triggered D Type Flip-Flop




During the low part of the clock cycle this circuit records the input value and when the clock goes high drives  $V_{OUT2}$  to the voltage level that arrived. (This is the classic function of a D flip-flop.)


Note that this circuit is not fooled by noise on the input and makes its decision on the rising edge of the clock (**edge-triggered**).

Copyright 2001, Regents of University of California

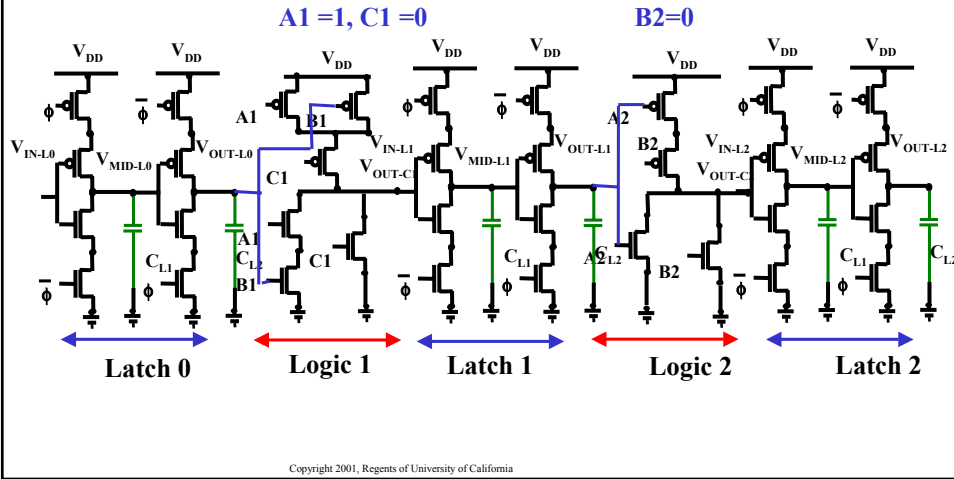
### Combinatorial Logic and Clocked Latches: Wiring


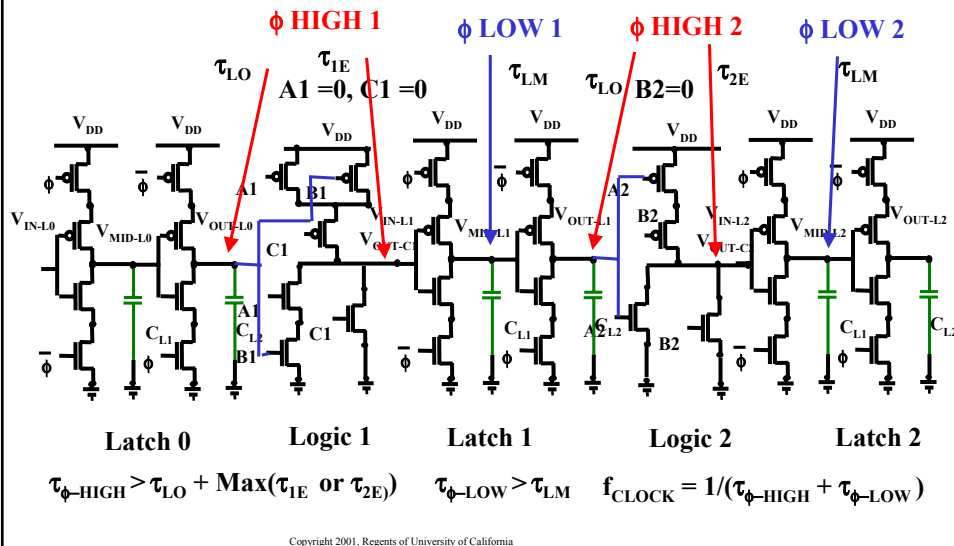
### Combinatorial Logic and Clocked Latches: Signal Flow




## Feedback Can Provide Memory

 

Copyright 2001, Regents of University of California


## Example of the Opposite State

 

Copyright 2001, Regents of University of California




## Adding Memory Controls

 

Set-Reset Flip-Flop

Copyright 2001, Regents of University of California

## Adding a Clock

 

Clocked S-R Flip-Flop

Copyright 2001, Regents of University of California