

**EECS 42 Introduction to Electronics for
Computer Science
Andrew R. Neureuther**

Lecture # 21 Clock Operation of Latches

Handout of Monday Lecture.

- A) 2nd Midterm Returned**
- B) Latch circuit to hold/release signals**
- C) Cascade CMOS elements with latches**

<http://inst.EECS.Berkeley.EDU/~ee42/>

Game Plan 04/21/03

Last Week: Logic Delay; resistor model, CMOS operation and delay

Monday 4/14/03:

- 2nd Midterm returned
- CMOS Latch and use in logic cascade

Wednesday 04/09/03:


- Clocked Latch and Timing Diagram
- Latency and Throughput
- Feedback in logic to produce memory

Next (13th) Week: Diodes and MOS Devices

Problem set #10 for 4/303: Logic Delay; Cascade; Latches and Clock frequency

CMOS Logic Gate: Example Inputs

A = 0
B = 1
C = 1

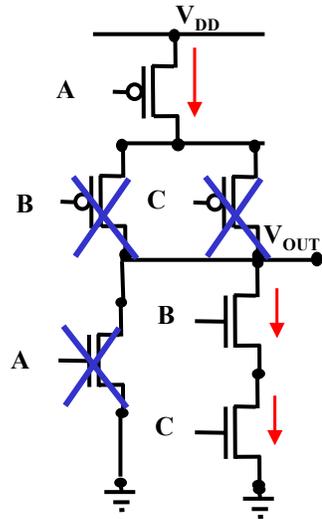

PMOS A conducts; B and C Open

Output is High


= 0

NMOS B and C conduct; A open

Logic is Complementary and produces F = 0

Copyright 2001, Regents of University of California

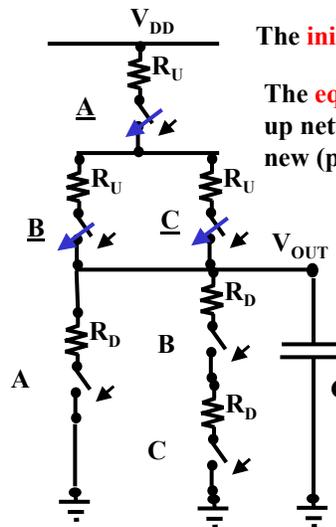Logic Gate Propagation Delay: Initial State



The **initial state** depends on the old (previous) inputs.

The **equivalent resistance** of the pull-down or pull-up network for the transient phase depends on the new (present) input state.


Example: A=0, B=0, C=0 for a long time.

These inputs provided a path to V_{DD} for a long time and the capacitor has precharged up to $V_{DD} = 5V$.

$C_{OUT} = 50 \text{ fF}$

Copyright 2001, Regents of University of California

Logic Gate: Worst Case Scenarios

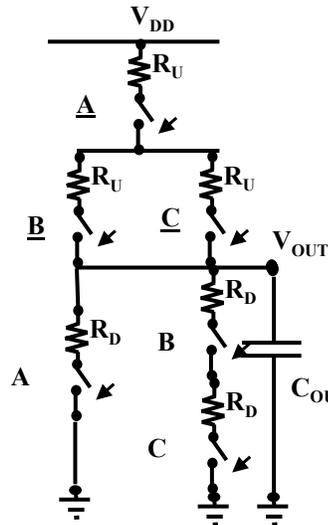

What combination of previous and present logic inputs will make the Pull-Up the **fastest**?

Fastest overall?

What combination of previous and present logic inputs will make the Pull-Up the **slowest**?

Slowest overall?


What combination of previous and present logic inputs will make the Pull-Down the **fastest**?

What combination of previous and present logic inputs will make the Pull-Down the **slowest**?

Copyright 2001, Regents of University of California

Logic Gate Cascade

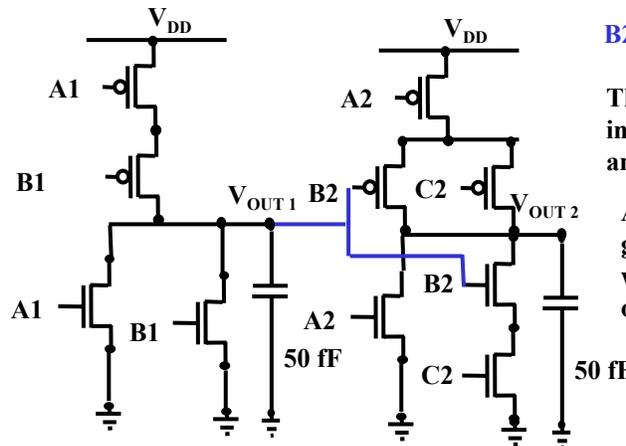To avoid large resistance due to many gates in series, logic functions with 4 or more inputs are usually made from cascading two or more 2-4 input blocks.



$$B2 = V_{OUT1}$$

The four independent input are A1, B1, A2 and C2.

A2 high discharges gate 2 without even waiting for the output of gate 1.


C2 high and A2 low makes gate 2 wait for Gate 1 output

Copyright 2001, Regents of University of California

Data Synchronization problem

- Combinatorial logic gates can give incorrect answers prematurely and may take several gate propagation delays produce an answer.
- Clocks (signals as to when to proceed) and latches (which capture and hold the correct outputs) can provide synchronization.

Latch Controlled by a Clock

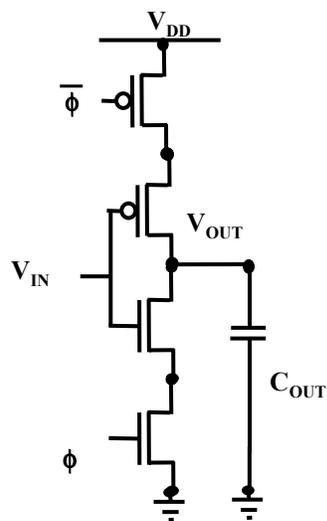


An inverter with clocked devices in series can form a latch.

When the clock ϕ is high its complement $\bar{\phi}$ is low and the inverter operates.

To synchronize the data the clock remains low until the data is correct at all locations on the chip. When the clock goes high the inverse of the data is passed.

Clock Signal Definitions

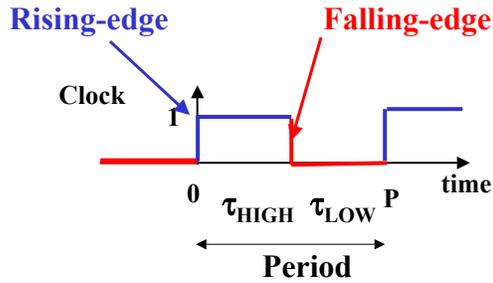


$$\text{Period} = P = \tau_{\text{HIGH}} + \tau_{\text{LOW}}$$

$$\text{Frequency} = 1/P = 1/(\tau_{\text{HIGH}} + \tau_{\text{LOW}})$$

$$\text{Duty Cycle} = (\tau_{\text{HIGH}})/(\tau_{\text{HIGH}} + \tau_{\text{LOW}})$$


Copyright 2001, Regents of University of California

Latch Work Best In Pairs

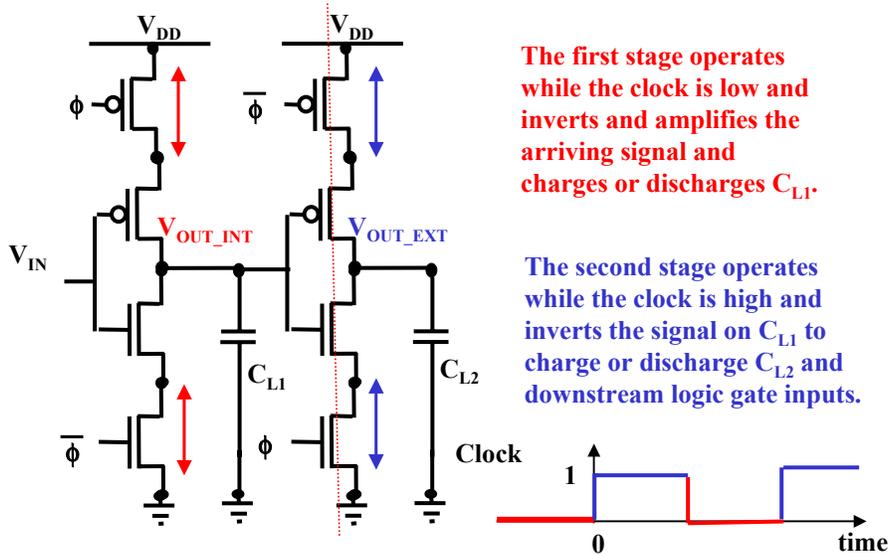

Copyright 2001, Regents of University of California

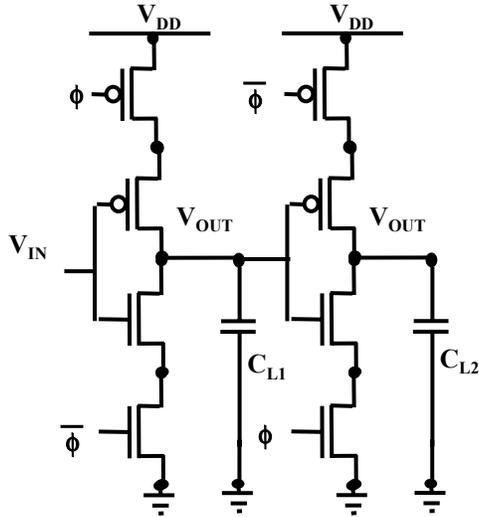
A Double Latch is an Edge-Triggered D Type Flip-Flop




During the low part of the clock cycle this circuit records the input value and when the clock goes high drives V_{OUT2} to the voltage level that arrived. (This is the classic function of a D flip-flop.)

Note that this circuit is not fooled by noise on the input and makes its decision on the rising edge of the clock (**edge-triggered**).

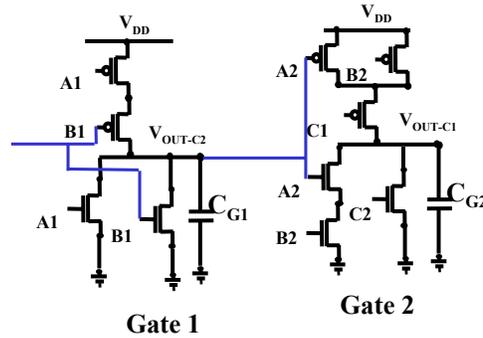Example of Circuits to Integrate with Latches




Latch Implementation: Lumped

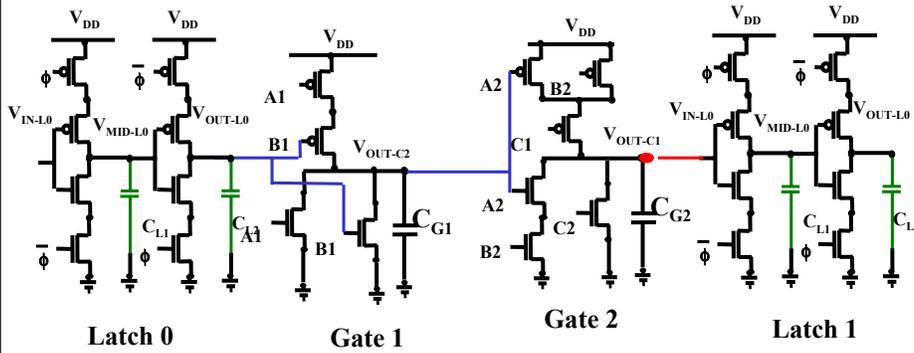

Copyright 2001, Regents of University of California

Latch Operation: Lumped

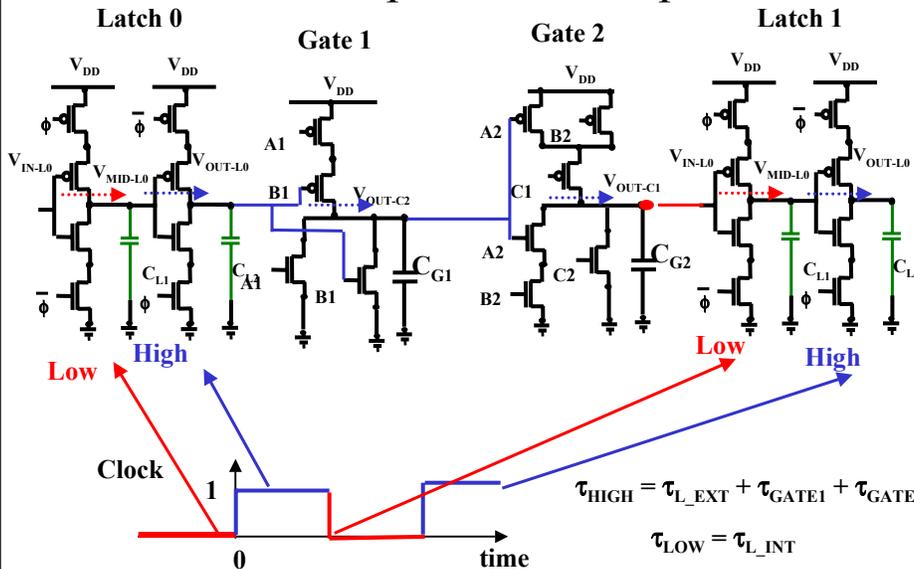

Copyright 2001, Regents of University of California

Latch Implementation: Pipelined

