

EECS 42 Intro. electronics for CS Spring 2003 Lecture 21: 04/21/03 A.R. Neureuther  
Version Date 04/19/03

## EECS 42 Introduction to Electronics for Computer Science

### Andrew R. Neureuther

### Lecture # 21 Clock Operation of Latches

Handout of Monday Lecture.

A) 2<sup>nd</sup> Midterm Returned  
B) Latch circuit to hold/release signals  
C) Cascade CMOS elements with latches

<http://inst.EECS.Berkeley.EDU/~ee42/>

Copyright 2001, Regents of University of California

EECS 42 Intro. electronics for CS Spring 2003 Lecture 21: 04/21/03 A.R. Neureuther  
Version Date 04/19/03

### Logic Gate Propagation Delay: Initial State

The **initial state** depends on the old (previous) inputs.

The **equivalent resistance** of the pull-down or pull-up network for the transient phase depends on the new (present) input state.

Example: A=0, B=0, C=0 for a long time.  
These inputs provided a path to  $V_{DD}$  for a long time and the capacitor has precharged up to  $V_{DD} = 5V$ .

Copyright 2001, Regents of University of California

EECS 42 Intro. electronics for CS Spring 2003 Lecture 21: 04/21/03 A.R. Neureuther  
Version Date 04/19/03

### Game Plan 04/21/03

Last Week: Logic Delay; resistor model, CMOS operation and delay

Monday 4/14/03:

- 2<sup>nd</sup> Midterm returned
- CMOS Latch and use in logic cascade

Wednesday 04/09/03:

- Clocked Latch and Timing Diagram
- Latency and Throughput
- Feedback in logic to produce memory

Next (13th) Week: Diodes and MOS Devices

**Problem set #10 for 4/303: Logic Delay; Cascade; Latches and Clock frequency**

Copyright 2001, Regents of University of California

EECS 42 Intro. electronics for CS Spring 2003 Lecture 21: 04/21/03 A.R. Neureuther  
Version Date 04/19/03

### Logic Gate: Worst Case Scenarios

What combination of previous and present logic inputs will make the Pull-Up the **fastest**? Fastest overall?

What combination of previous and present logic inputs will make the Pull-Up the **slowest**? Slowest overall?

What combination of previous and present logic inputs will make the Pull-Down the **fastest**?

What combination of previous and present logic inputs will make the Pull-Down the **slowest**?

Copyright 2001, Regents of University of California

EECS 42 Intro. electronics for CS Spring 2003 Lecture 21: 04/21/03 A.R. Neureuther  
Version Date 04/19/03

### CMOS Logic Gate: Example Inputs

A = 0  
B = 1  
C = 1

PMOS A conducts; B and C Open  
Output is High = 0

NMOS B and C conduct; A open  
Logic is Complementary and produces  $F = 0$

Copyright 2001, Regents of University of California

EECS 42 Intro. electronics for CS Spring 2003 Lecture 21: 04/21/03 A.R. Neureuther  
Version Date 04/19/03

### Logic Gate Cascade

To avoid large resistance due to many gates in series, logic functions with 4 or more inputs are usually made from cascading two or more 2-4 input blocks.

$B2 = V_{OUT1}$

The four independent input are A1, B1, A2 and C2.

A2 high discharges gate 2 without even waiting for the output of gate 1.

C2 high and A2 low makes gate 2 wait for Gate 1 output


Copyright 2001, Regents of University of California

## Data Synchronization problem

- Combinatorial logic gates can give incorrect answers prematurely and may take several gate propagation delays produce an answer.
- Clocks (signals as to when to proceed) and latches (which capture and hold the correct outputs) can provide synchronization.


Copyright 2001, Regents of University of California

## Latch Work Best In Pairs

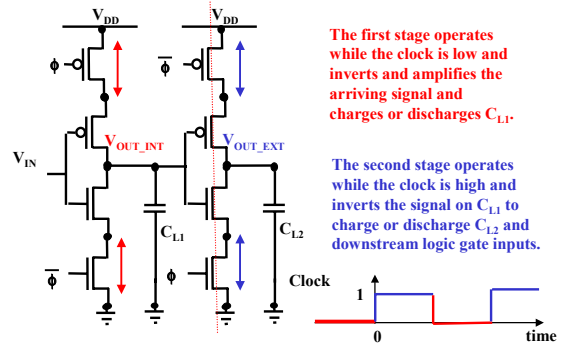

Copyright 2001, Regents of University of California

## Latch Controlled by a Clock

 


An inverter with clocked devices in series can form a latch.

When the clock  $\phi$  is high its complement  $\bar{\phi}$  is low and the inverter operates.

To synchronize the data the clock remains low until the data is correct at all locations on the chip. When the clock goes high the inverse of the data is passed.

Copyright 2001, Regents of University of California
 
## A Double Latch is an Edge-Triggered D Type Flip-Flop




During the low part of the clock cycle this circuit records the input value and when the clock goes high drives  $V_{OUT2}$  to the voltage level that arrived. (This is the classic function of a D flip-flop.)

Note that this circuit is not fooled by noise on the input and makes its decision on the rising edge of the clock (edge-triggered).

Copyright 2001, Regents of University of California

## Clock Signal Definitions

 


$$\text{Period} = P = \tau_{\text{HIGH}} + \tau_{\text{LOW}}$$

$$\text{Frequency} = 1/P = 1/(\tau_{\text{HIGH}} + \tau_{\text{LOW}})$$

$$\text{Duty Cycle} = (\tau_{\text{HIGH}})/(\tau_{\text{HIGH}} + \tau_{\text{LOW}})$$


Copyright 2001, Regents of University of California
 
## Example of Circuits to Integrate with Latches




Copyright 2001, Regents of University of California

### Latch Implementation: Lumped

 


Copyright 2001, Regents of University of California

### Latch Operation: Lumped

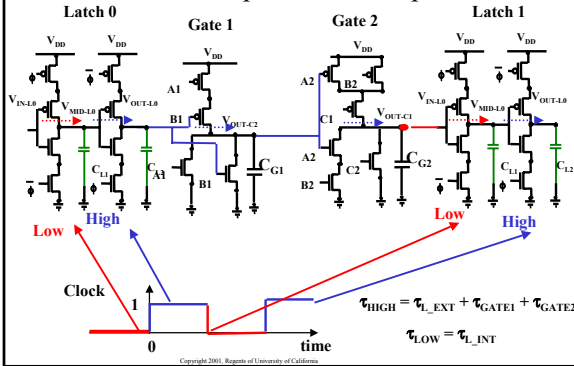

Copyright 2001, Regents of University of California

### Latch Implementation: Pipelined

 

Copyright 2001, Regents of University of California