
 


 

## Logical Effort



# Question #1

- How to best combine logic and drive for a big capacitive load?


  
# Question #2

- All of these are “decoders”
  - Which one is “best”?



## *Method to answer both of these questions*

- ❑ Extension of buffer sizing problem
- ❑ Logical effort


# *Complex Gate Sizing*

# Complex Gate Sizing: NAND-2 Example

$$C_{gnand} = 4C_G = (4/3) C_{ginv}$$

$$C_{dnand} = 6C_D = 6\gamma C_G = 2\gamma C_{ginv}$$
 
$$f = C_L/C_{gnand} = (3/4) C_L/C_{ginv}$$



$$\begin{aligned} t_{pNAND} &= kR_N(C_{dnand} + C_L) \\ &= kR_N(2\gamma C_{ginv} + C_L) \\ &= kR_N C_{ginv} (2\gamma + C_L/C_{ginv}) \\ &= t_{inv} (2\gamma + (4/3)f) \end{aligned}$$

# Logical Effort

- ❑ Defines ease of gate to drive external capacitance
- ❑ Inverter has the smallest logical effort and intrinsic delay of all static CMOS gates
- ❑ Logical effort LE is defined as:
  - $(R_{eq,gate} C_{in,gate}) / (R_{eq,inv} C_{in,inv})$
  - Easiest way to calculate (usually):
    - Size gate to deliver same current as an inverter, take ratio of gate input capacitance to inverter capacitance
- ❑ LE increases with gate complexity

# Logical Effort

$$t_{pgate} = t_{inv} (p + LEf)$$

Measure everything in units of  $t_{inv}$  (divide by  $t_{inv}$ ):

$p$  – intrinsic delay - gate parameter  $\neq f(W)$

$LE$  – logical effort – gate parameter  $\neq f(W)$

$f$  – electrical fanout =  $C_L/C_{in} = f(W)$

Normalize everything to an inverter:

$$LE_{inv} = 1, p_{inv} = \gamma$$



# Delay of a Logic Gate

Gate delay:

$$\text{Delay} = \text{EF} + p \quad (\text{measured in units of } t_{inv})$$

**effective fanout**      **intrinsic delay**


Effective fanout:

$$\text{EF} = \text{LE } f$$

**logical effort**      **electrical fanout** =  $C_L/C_{in}$


Logical effort is a function of topology, independent of sizing  
Effective fanout is a function of load/gate size

# Logical Effort of Gates

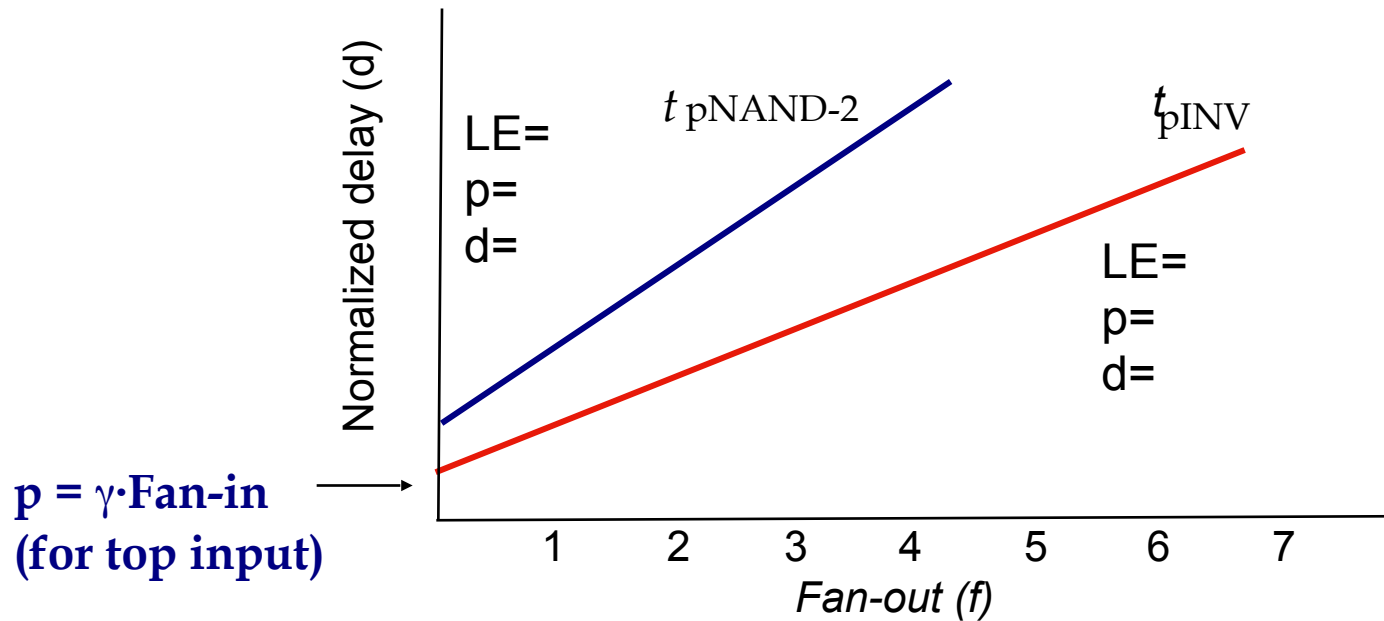

# Delay Of NOR-2 Gate

 1. Size for same resistance as inverter
2. LE = ratio of input cap of gate versus inverter




Intrinsic capacitance ( $C_{dnor}$ ) =  
 $t_{pint} (NOR) =$

# Question

Any logic function can be implemented using NOR gates only or NAND gates only!

Which of the two approaches is preferable in CMOS (from a performance perspective)?

# Logical Effort

 

Gate Type	Number of Inputs			
	1	2	3	n
Inverter	1			
NAND		$4/3$	$5/3$	$(n+2)/3$
NOR		$5/3$	$7/3$	$(2n+1)/3$
Multiplexer		2	2	2
XOR		4	12	

[From Sutherland, Sproull, Harris]



## Optimizing Complex Combinational Logic

# Multistage Networks

$$Delay = \sum_{i=1}^N (p_i + LE_i \cdot f_i)$$

Effective fanout:  $EF_i = LE_i f_i$

*Only for tree networks*


Path delay  $D = \sum d_i = \sum p_i + \sum EF_i$

Path electrical fanout:  $F = C_L / C_{in} = \prod f_i$

Path logical effort:  $\prod LE = LE_1 LE_2 \dots LE_N$

Path effort:  $PE = \prod LE F$

# Adding branching

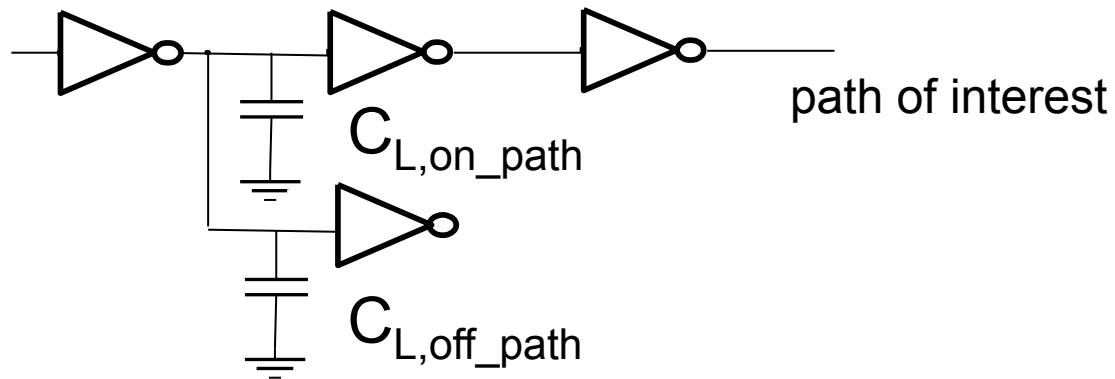

Branching effort: 
$$b = \frac{C_{L,on-path} + C_{L,off-path}}{C_{L,on-path}}$$



# Multistage Networks

$$Delay = \sum_{i=1}^N (p_i + LE_i \cdot f_i)$$

Effective fanout:  $EF_i = LE_i f_i$

Path delay  $D = \sum d_i = \sum p_i + \sum EF_i$

Path electrical fanout:  $F = C_L / C_{in}$

Branching effort:  $\Pi B = b_1 b_2 \dots b_N$

$\Pi f_i = \Pi B F$  (assuming all paths in the tree are important)

Path logical effort:  $\Pi LE = LE_1 LE_2 \dots LE_N$

Path effort:  $PE = \Pi LE \Pi B F$

# Optimum Effort per Stage

When each stage bears the same effort (effective fanout):

$$EF^N = PE$$

$$EF = \sqrt[N]{PE}$$

Effective fanouts:  $LE_1f_1 = LE_2f_2 = \dots = LE_Nf_N$

Minimum path delay

$$\hat{D} = \sum_{i=1}^N (LE_i f_i + p_i) = N \cdot PE^{1/N} + \sum_{i=1}^N p_i$$

# Optimal Number of Stages

For a given load,

and given input capacitance of the first gate

Find optimal number of stages and optimal sizing

$$D = N \cdot PE^{1/N} + \sum p_i$$

*Remember: we can always add inverters to the end of the chain*

The 'best effective fanout'  $EF = PE^{1/\hat{N}}$  is still around 4  
(3.6 with  $\gamma=1$ )

# Method of Logical Effort: Summary


- Compute the path effort:  $PE = (\Pi LE)BF$
- Find the best number of stages  $N \sim \log_4 PE$
- Compute the effective fanout/stage  $EF = PE^{1/N}$
- Sketch the path with this number of stages
- Work either from either end, find sizes:  
$$C_{in} = C_{out} * LE/EF$$

Reference: Sutherland, Sproull, Harris, "Logical Effort", Morgan-Kaufmann 1999.



## Optimizing Complex Combinational Logic: Examples

# Example 1: No branching

 

Electrical fanout,  $F =$

$\prod LE =$

$PE =$

$EF/\text{stage} =$


$a =$

$b =$

$c =$
 
# Example 1: No branching

*a, b, c are input capacitances normalized to the unit inverter*



Electrical fanout,  $F = 5$

$\Pi LE = 25/9$

$PE = 125/9$

$EF/stage = 1.93$

$a = 1.93$

$b = 2.23$

$c = 2.59$


From the back

$$5/c = 1.93$$

$$(5/3)c/b = 1.93$$

$$(5/3)b/a = 1.93$$

# Our old problem: which one is better?

 

$$LE = 10/3 \quad 1$$

$$\prod LE = 10/3$$

$$P = 8 + 1$$

$$LE = 2 \quad 5/3$$

$$\prod LE = 10/3$$

$$P = 4 + 2$$


$$LE = 4/3 \quad 5/3 \quad 4/3 \quad 1$$

$$\prod LE = 80/27$$

$$P = 2 + 2 + 2 + 1$$



# Adding Branching

 

$$\begin{aligned} LE &= 1 \\ F &= 90/5 = 18 \\ PE &= 18 \text{ (wrong!)} \end{aligned}$$

---

$$\begin{aligned} EF_1 &= (15+15)/5 = 6 \\ EF_2 &= 90/15 = 6 \\ PE &= 36, \text{ not } 18! \end{aligned}$$

Better:  $PE = F \cdot LE \cdot B = 18 \cdot 1 \cdot 2 = 36$

# Example 2 with Branching

Select gate sizes  $y$  and  $z$  to minimize delay from  $A$  to  $B$

Logical Effort:  $LE =$

Electrical Fanout:  $F =$


Branching Effort:  $B =$

Path Effort:  $PE =$

---

Best Effective Fanout:  $EF =$

Delay:  $D =$

 

# Example 2 with Branching


Select gate sizes  $y$  and  $z$  to minimize delay from  $A$  to  $B$

Logical Effort:  $LE = (4/3)^3$

Electrical Fanout:  $F = C_{out}/C_{in} = 9$

Branching Effort:  $B = 2 \cdot 3 = 6$

 Path Effort:  $PE = \prod LE \cdot F \cdot B = 128$



Best Effective Fanout:  $EF = PE^{1/3} \approx 5$

Delay:  $D = 3 \cdot 5 + 3 \cdot 2 = 21$

Work backward for sizes:

$$z = \frac{9C \cdot (4/3)}{5} = 2.4C$$

$$y = \frac{3z \cdot (4/3)}{5} = 1.9C$$