



# **EECS 151/251A**

## **Spring 2018**


### **Digital Design and Integrated Circuits**

Instructors:


Nick Weaver & John Wawrzynek

## **Lecture 12**

# Wire Models

 

All-inclusive model

 


Capacitance-only



**Capacitance**

# Capacitance: The Parallel Plate Model

 

$$C_{int} = \frac{\epsilon_{di}}{t_{di}} WL$$

- Cap scaling (s – process scaling factor)
  - Local wires
    - $W$ ,  $L$ ,  $t_{di}$  all decrease ( $\sim s$ )
    - Cap decreases linearly with feature size ( $\sim s$ )
  - Global wires
    - $W$ ,  $t_{di}$  decrease ( $\sim s$ ),  $L$  constant
    - Cap  $\sim$  constant
- Permittivity is a property of the dielectric:  $\epsilon_{di} = \kappa \epsilon_0$



# Permittivity/Dielectric Constant

Material	$\kappa$ (factor of $\epsilon_0$ )
Free space	1
Aerogels	$\sim 1.5$
Polyimides (organic)	3-4
Silicon dioxide	3.9
Glass-epoxy (PC board)	5
Silicon Nitride ( $\text{Si}_3\text{N}_4$ )	7.5
Alumina (package)	9.5
Silicon	11.7

- Low-k dielectrics used sub-130nm
  - Carbon-doped oxide
  - Fabs also looking at air-gaps

  
# Fringing Capacitance

$$C_{wire} = C_{pp} + C_{fringe} = \frac{w\epsilon_{di}}{t_{di}} + \frac{2\pi\epsilon_{di}}{\log(t_{di}/H)}$$



- Fringe cap per unit length ~const  
(good rule of thumb 0.2fF/um)


# Fringing versus Parallel Plate

 

(from [Bakoglu89])


- ❑ Narrow, tall wires in modern processes
  - Trying to keep resistance from increasing
  - Comes at the expense of fringe cap

# *Interwire Capacitance*

 



# Impact of Interwire Capacitance

 


(from [Bakoglu89])




**Resistance**

# Wire Resistance

 

$$R = \frac{\rho L}{HW}$$


 
Sheet Resistance  $R_o$  Units  $\Omega\text{-m}$




# Interconnect Resistance

Material	$\rho$ ( $\Omega\text{-m}$ )
Silver (Ag)	$1.6 \times 10^{-8}$
Copper (Cu)	$1.7 \times 10^{-8}$
Gold (Au)	$2.2 \times 10^{-8}$
Aluminum (Al)	$2.7 \times 10^{-8}$
Tungsten (W)	$5.5 \times 10^{-8}$

Resistivity ( $\Omega\text{-cm}$ )

  

# Impact on Delay

 


Source: Applied Materials




## Interconnect Modeling



# *The Lumped Model*

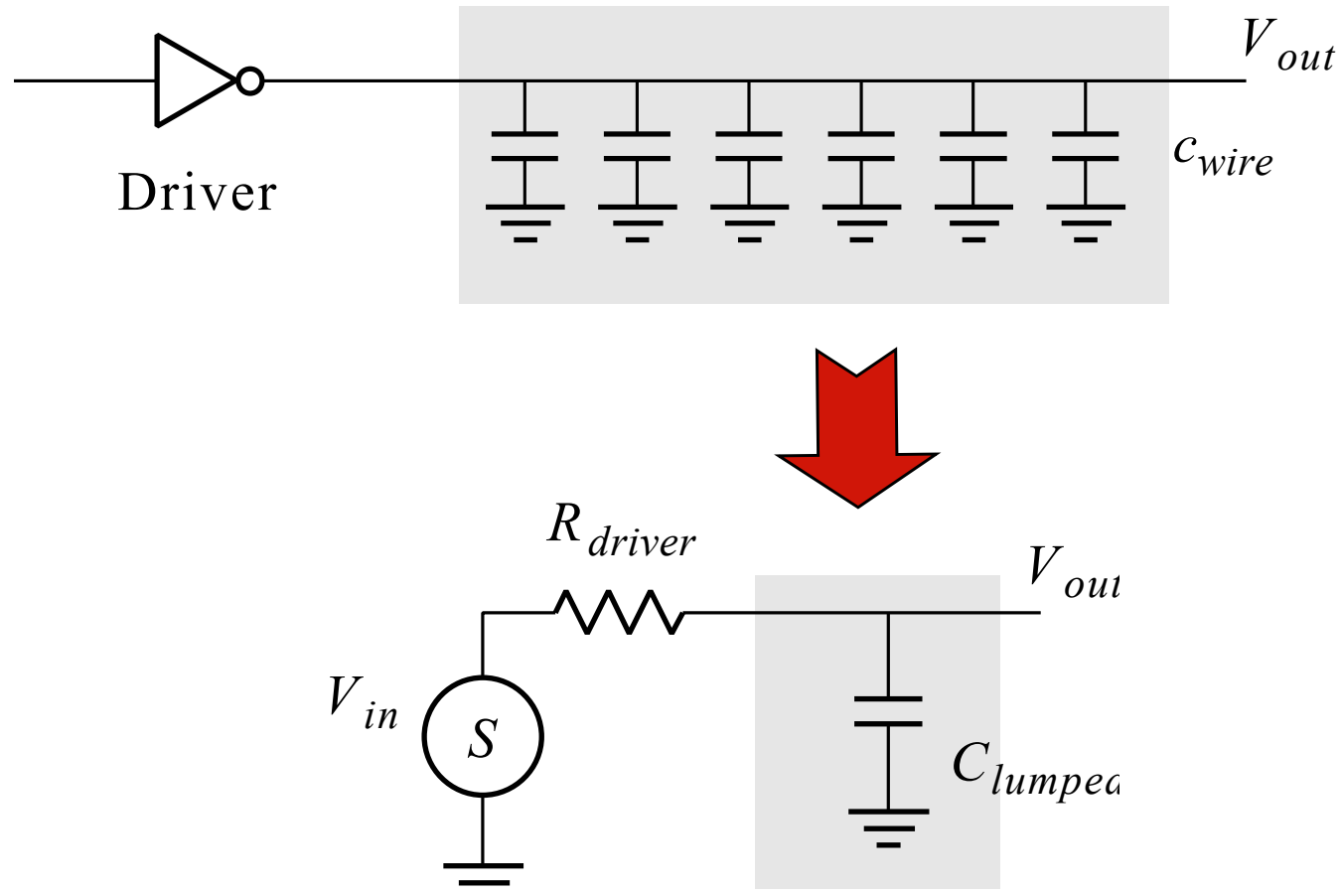

# *The Distributed RC-line*

 


## □ Analysis method:

- Break the wire up into segments of length  $dx$
- Each segment resistance ( $r dx$ )
- Capacitance ( $c dx$ )



# The Distributed RC-line

 


$$I_C = c \Delta L \frac{\partial V}{\partial t} = \frac{(V_{i-1} - V_i) - (V_i - V_{i+1})}{r \Delta L} \longrightarrow \boxed{rc \frac{\partial V}{\partial t} = \frac{\partial^2 V}{\partial x^2}}$$

*The diffusion equation*

## Intermezzo – Delay of RC-networks:

- ❑ Idea: Lets approximate things somewhat...
  - ❑ But its a reasonably good approximation
- ❑ Time delay to fill each capacitor:
  - ❑ Resistance to that capacitor & that capacitor's capacitance
- ❑ Total time: Time to fill all capacitors
- ❑ Its a **conservative** and **easy to calculate** delay estimate
  - ❑ Will overestimate delays


### Delay Model of RC Networks:

 

$$\tau_{Di} = \sum_{k=1}^N C_k R_{ik}$$

$$R_{ik} = \sum R_j \Rightarrow (R_j \in [path(s \rightarrow i) \cap path(s \rightarrow k)])$$

# Elmore Delay Example

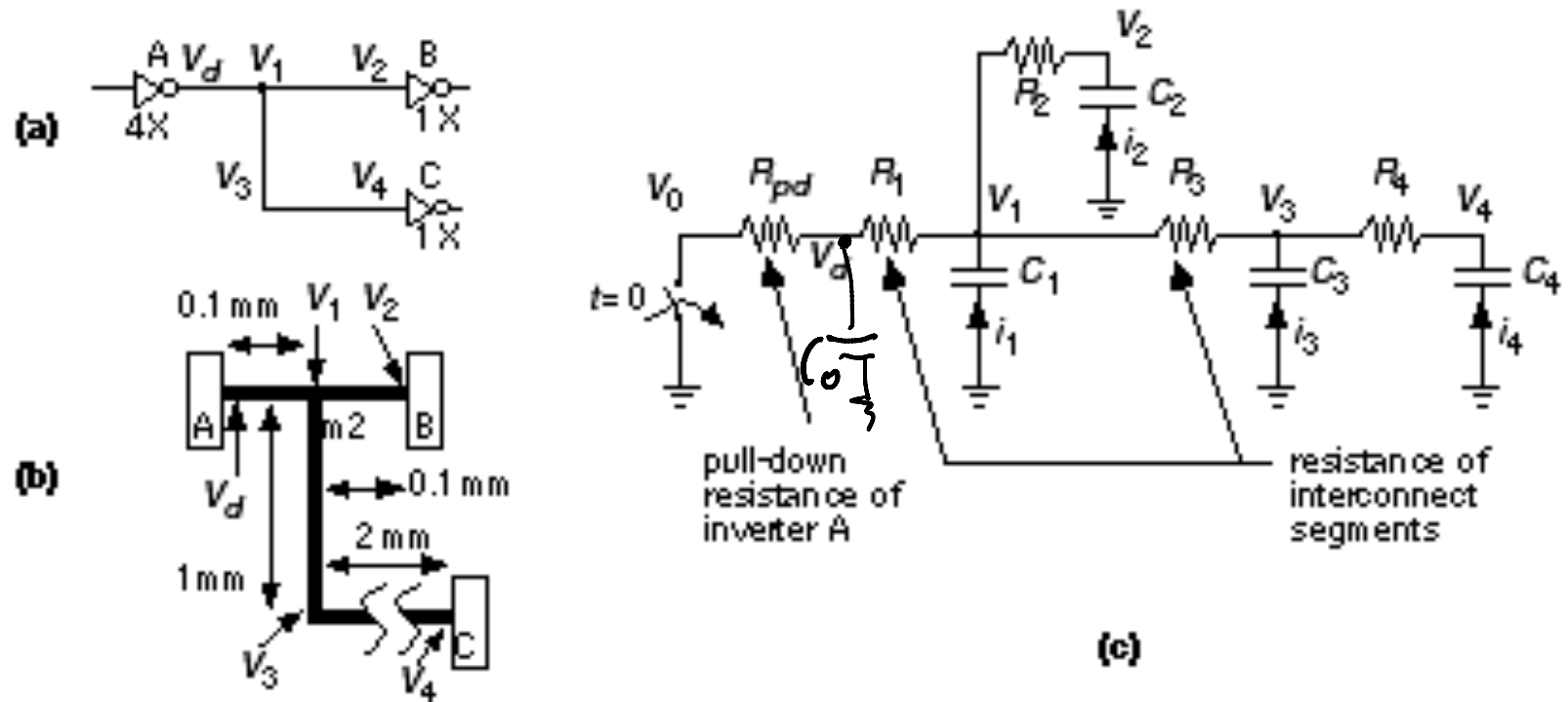


$$\begin{aligned} \tau_{D4} = \sum_{k=0}^4 C_k R_{4k} = & C_0 R_{pd} + \\ & C_1 (R_{pd} + R_1) + \\ & C_2 (R_{pd} + R_1) + \\ & C_3 (R_{pd} + R_1 + R_3) + \\ & C_4 (R_{pd} + R_1 + R_3 + R_4) = \\ & R_{pd} (C_0 + C_1 + C_2 + C_3 + C_4) + \\ & R_1 (C_1 + C_2 + C_3 + C_4) \\ & + R_3 (C_3 + C_4) + R_4 C_4 \end{aligned}$$

# *Elmore Delay Example*

## □ Assume:

- m2  $r$  is  $50 \text{ m}\Omega/\square$
- m2  $c$  (for a minimum-width line) is  $0.2\text{fF}/\mu\text{m}$
- m2 minimum width is  $90\text{nm}$
- 4x inverter  $R_{pd} = 500\Omega$
- 1X inverter input capacitance is  $20\text{fF}$  (a standard load)

# Elmore Delay Example

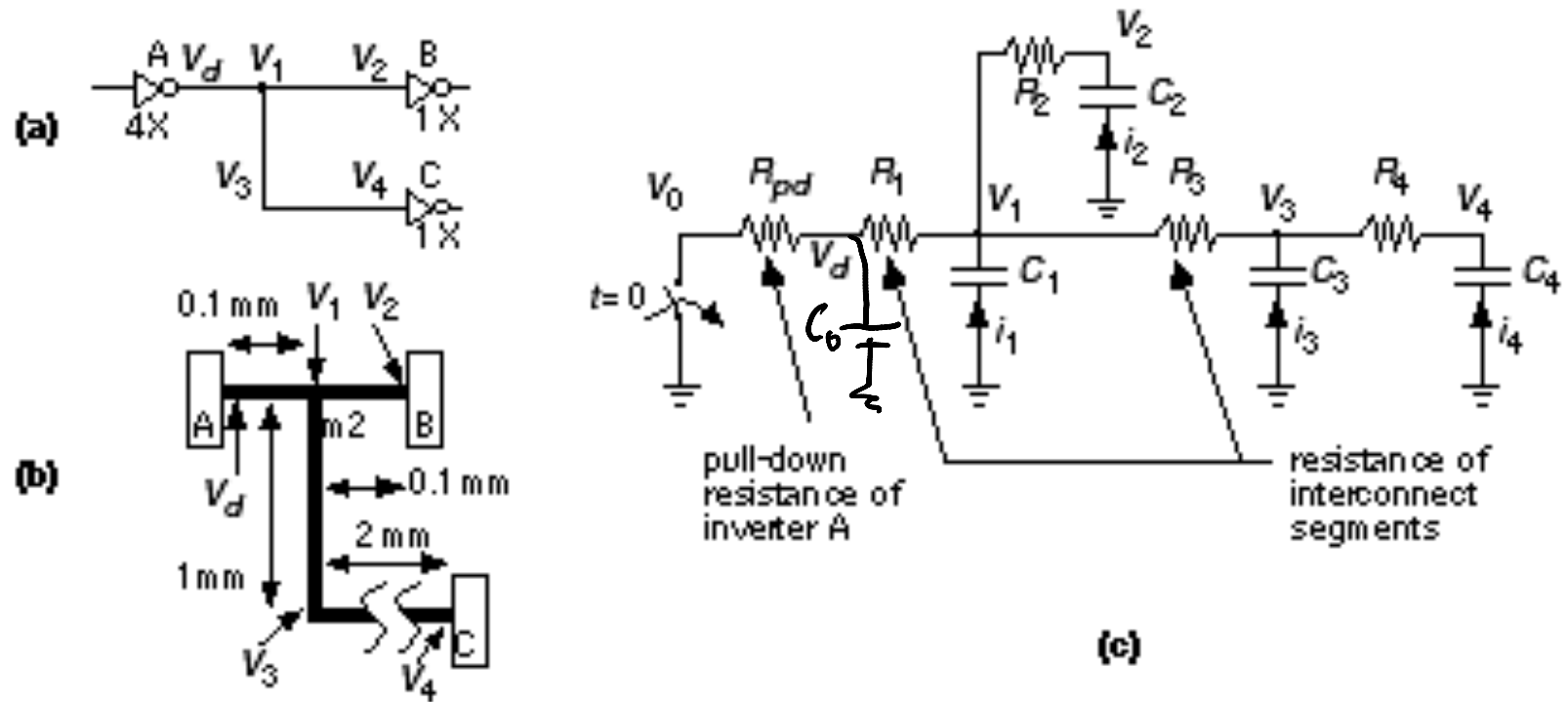


$$R_{pd} = 500\Omega, R_1 = R_2 = \frac{0.1\text{mm}}{90\text{nm}} 50\text{m}\Omega = 6\Omega, R_3 = 56\Omega, R_4 = 112\Omega$$

$$C_0 = 4 * 20\text{fF} = 80\text{fF}, C_1 = \frac{0.1\text{mm} \cdot 0.2\text{fF}}{\text{um}} = 20\text{fF} \cdot$$

$$C_2 = C_1 + 20\text{fF} = 40\text{fF}, C_3 = 200\text{fF}, C_4 = 420\text{fF}$$

$$\tau_{D4} = 380\text{ps}$$

## Back to Wire Delay

 

# Wire Model

Model the wire with N equal-length segments:

$$\tau_{DN} = \left(\frac{L}{N}\right)^2 (rc + 2rc + \dots + Nrc) = (rcL^2) \frac{N(N+1)}{2N^2} = RC \frac{N+1}{2N}$$

For large values of N:


$$\tau_{DN} = \frac{RC}{2} = \frac{rcL^2}{2}$$



# RC-Models

Voltage Range	Lumped RC-network	Distributed RC-network
0→50% ( $t_p$ )	0.69 RC	0.38 RC
0→63% ( $\tau$ )	RC	0.5 RC
10%→90% ( $t_r$ )	2.2 RC	0.9 RC

 Step Response of Lumped and Distributed RC Networks:  
Points of Interest.





**Characteristic  
Impedence**

# *When You Get To A Board...*

- ❑ We have to fully treat the wires as transmission lines
  - ❑ Which means inductance also comes into play
- ❑ Modeled with "Characteristic impedance"
  - ❑ Measured in  $\Omega$ s as well
- ❑ Propagation delay also matters even more
  - ❑ Since we are going longer distances
  - ❑  $\sim 150$  pS/inch
- ❑ But we don't do the math ourselves...

# *Why Impedance Matters...*

- ❑ Low impedance transmits energy better
- ❑ When you have an impedance mismatch...
  - ❑ Energy gets reflected back...
  - ❑ Which means noise & less efficiency
- ❑ Devices will specify the trace impedance needed:
  - ❑ EG, WiFi Antenna trace: 50  $\Omega$
  - ❑ DDR3 DRAM on Zynq:  
40  $\Omega$  single, 80  $\Omega$  differential pair
- ❑ Fatter wires -> lower impedance
- ❑ Thinner boards -> lower impedance
  - ❑ It ups the capacitance but that lowers the impedance because it lowers the inductance/capacitance ratio

# *The Board "Stack-Up"*

- ❑ Boards are produced in layers just like chips
  - ❑ Signal layers with wires
  - ❑ Plane layers with large areas of conductor for power or ground
  - ❑ Vias to connect between them
- ❑ In generating the stack-up can also find the characteristic impedance for traces

# An Example Stack-Up

All MicroVias shown as  are STACKED MICROVIAS

			Finished Copper Weight	Finished Thickness (inches)
	<b>SOLDER MASK</b>			0.0005
L-1	<b>TOP SIGNAL</b>		1 Oz	0.0014
	<b>DIELECTRIC</b>			0.0035
L-2	<b>PLANE</b>		0.5 Oz	0.0007
	<b>DIELECTRIC</b>			0.0035
L-3	<b>SIGNAL</b>		0.5 Oz	0.0007
	<b>DIELECTRIC</b>			0.0035
L-4	<b>SIGNAL</b>		0.5 Oz	0.0007
	<b>DIELECTRIC</b>			0.0035
L-5	<b>PLANE</b>		0.5 Oz	0.0007
	<b>DIELECTRIC</b>			0.0100
L-6	<b>PLANE</b>		0.5 Oz	0.0007
	<b>DIELECTRIC</b>			0.0035
L-7	<b>SIGNAL</b>		0.5 Oz	0.0007
	<b>DIELECTRIC</b>			0.0035
L-8	<b>SIGNAL</b>		0.5 Oz	0.0007
	<b>DIELECTRIC</b>			0.0035
L-9	<b>PLANE</b>		0.5 Oz	0.0007
	<b>DIELECTRIC</b>			0.0035
L-10	<b>BOTTOM SIGNAL</b>		1 Oz	0.0014
	<b>SOLDER MASK</b>			0.0005
<b>Total Thickness</b>			<b>0.0474 (inches)</b>	

## Customer Saved Impedance Results

Layer	Impedance Model	Impedance (ohms)	Trace Width (mils)	Space (mils)
Layer 1	Soldermask Coated Microstrip Single-ended	51.7	5	--
Layer 1	Soldermask Coated Microstrip Differential Pair	97.82	5	10
Layer 3	Stripline Single-ended	39.32	6	--
Layer 3	Stripline Differential Pair	82.67	4	4


# *Board Return Paths...*

- ❑ On a board, it isn't just transmitting a signal...
  - ❑ You also need a return path for the current for the ground plane
- ❑ In general, the return path should follow the trace
  - ❑ So if you have a break in the ground plane, the signal should route around the break too
- ❑ "Bypass capacitors": Read the data sheets
  - ❑ Act as temporary power reservoirs which can support specific frequency responses


 
## *Seeing Some Of This In Action...*


- ❑ Board With Routing...
- ❑ Areas of focus:
  - ❑ DDR: Controlled Impedance & length matching
  - ❑ Power & Ground planes:  
Low impedance,  
Lots of Bypassing





 
# DDR Constraints

- ❑ 40Ω signal, 80Ω differential
- ❑ Obtained from Xilinx datasheet
- ❑ 3 major groups of signals
  - ❑ 2 data banks:  
8 data lines,  
differential data  
strobe
  - ❑ 1 group of control  
& address lines



 
# *This Routing of DDR...*

- ❑ Data-sheet's very low impedance requirement needs fat wires & thin layers
  - ❑ Limits routing to the internal layers:  
Can't "escape" the BGA on the top
- ❑ Length matching a semi-manual process
  - ❑ Target of .025"
  - ❑ Based on micron's data sheet


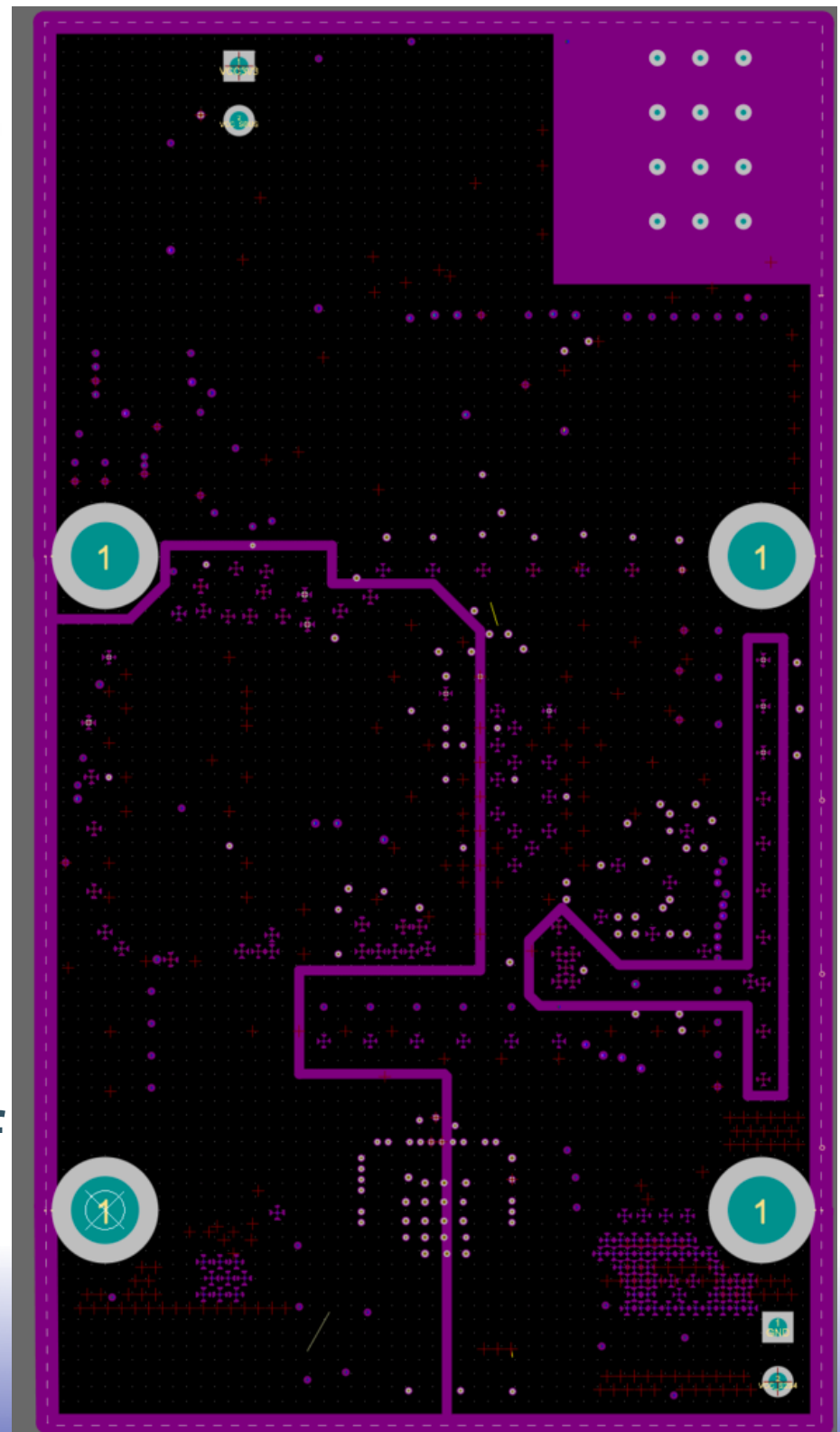
# *Ground and Power*

- ❑ Ground: 2 unified planes
  - ❑ Only exception a bit of isolation for the WiFi chip
- ❑ Power: L1: 1.0/3.3/1.5
- ❑ L2:  
1.5/1.8/3.3
  - ❑ And a crap-ton<sup>®</sup> of bypass capacitors






## Gates and Wires



# Driving an RC-line

 

$$\tau_D = R_s C_w + \frac{R_w C_w}{2} = R_s C_w + 0.5 r_w c_w L^2$$

$$t_p = 0.69(R_s C_w + R_w C_w / 2)$$


# *The Global Wire Problem*

$$Td = 0.69(0.5R_w C_w + R_N C_{in} + R_N C_w + R_w C_{in})$$

## Challenges


- ❑ No further improvements to be expected after the introduction of Copper (superconducting, optical?)
- ❑ Design solutions
  - Use of fat wires
  - Efficient chip floorplanning
  - Insert repeaters

# Reducing RC-delay Using Repeaters

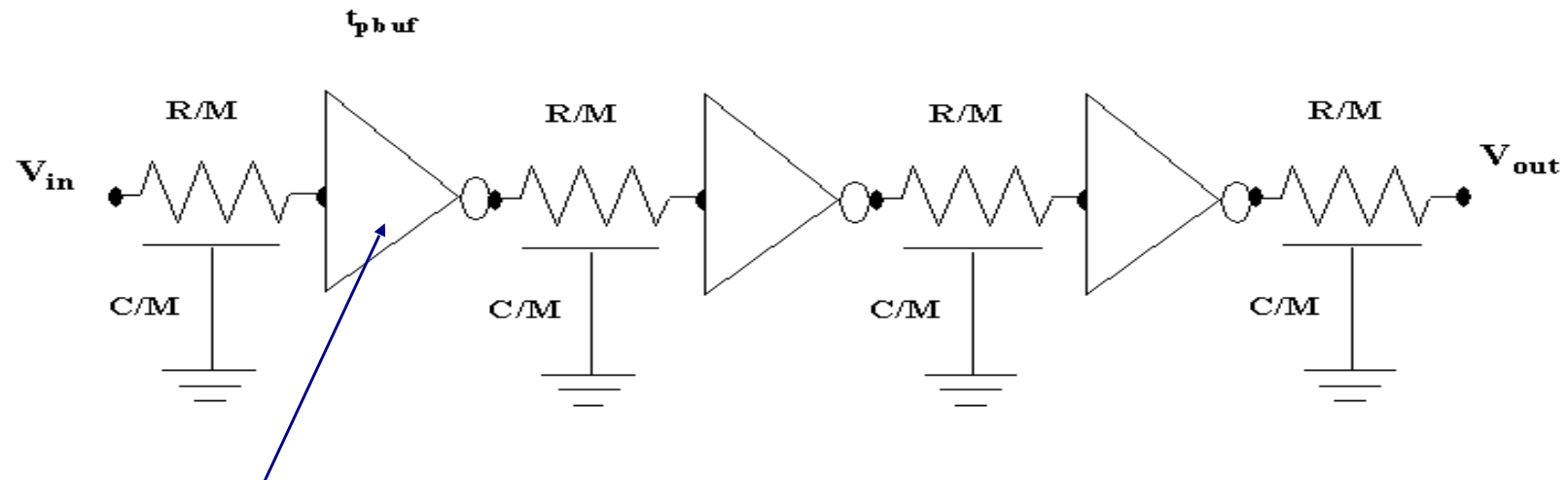

Repeater

# Repeaters

 

$$t_p = 0.69m \left( \frac{R_N}{W} (W\gamma C_{in} + \frac{cL}{m} + WC_{in}) + \frac{rL}{m} (WC_{in} + 0.5 \frac{cL}{m}) \right)$$

$$m_{opt} = L \sqrt{\frac{rc}{2R_N C_{in} (\gamma + 1)}} = \sqrt{\frac{t_{pwire(unbuffered)}}{t_{p1}}}$$

$$W_{opt} = \sqrt{\frac{R_N c}{r C_{in}}}$$



# Repeater Insertion

$$m_{opt} = L \sqrt{\frac{rc}{2R_N C_{in} (\gamma + 1)}} = \sqrt{\frac{t_{pwire(unbuffered)}}{t_{p1}}}$$

$$W_{opt} = \sqrt{\frac{R_N c}{r C_{in}}}$$


For a given technology and a given interconnect layer, there exists an optimal length of the wire segments between repeaters. The delay of these wire segments is **independent of the routing layer!**

$$L_{crit} = \frac{L}{m_{opt}} = \sqrt{\frac{2t_{p1}}{0.69rc}}$$

$$t_{p,crit} = \frac{t_{p,min}}{m_{opt}} = 2 \left( 1 + \sqrt{\frac{2}{(1+\gamma)}} \right) t_{p1}$$

From Elmore example:  $rc = 0.1 \text{fs}/\mu\text{m}^2$ ,  $t_{p1} = 55 \text{ps}$ ,  $L_{crit} = 1262 \mu\text{m}$   
(rule of thumb  $\sim 0.5\text{-}1 \text{mm}$ )


# Importance of Repeaters

 

Source: IBM POWER processors,  
R. Puri et al SRC Interconnect Forum 2006

- ❑ In modern designs the number of repeaters increases dramatically

# Wire and Gate Delay Scaling

 

Delay for Metal 1 and Global Wiring versus Feature Size



□ Gate delay gets better, wire delay gets worse



## Logical Effort

 
 
# Question #1

- How to best combine logic and drive for a big capacitive load?


  
## Question #2

- All of these are “decoders”
  - Which one is “best”?



## *Method to answer both of these questions*


- ❑ Extension of buffer sizing problem
- ❑ Logical effort

# *Complex Gate Sizing*


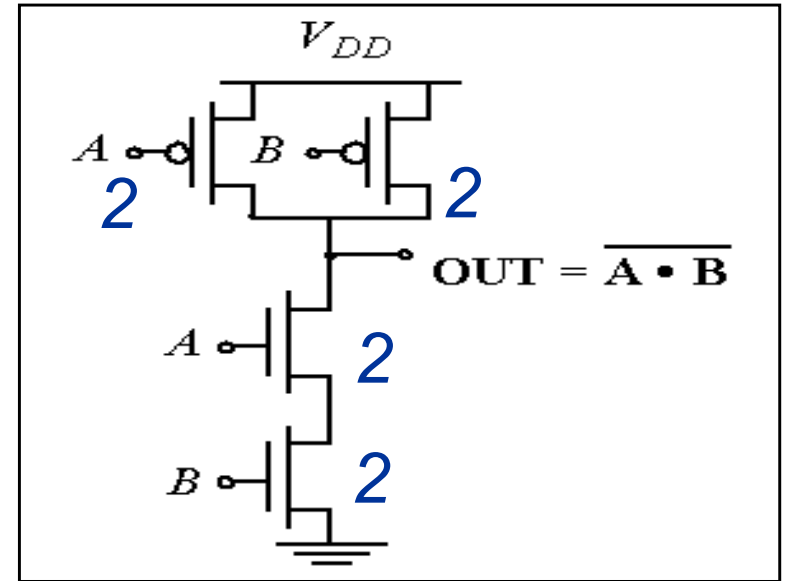
# Complex Gate Sizing: NAND-2 Example

$$\begin{aligned}C_{gnand} &= 4C_G = (4/3) C_{ginv} \\C_{dnand} &= 6C_D = 6\gamma C_G = 2\gamma C_{ginv} \\f &= C_L/C_{gnand} = (3/4) C_L/C_{ginv}\end{aligned}$$



$$\begin{aligned}t_{pNAND} &= kR_N(C_{dnand} + C_L) \\&= kR_N(2\gamma C_{ginv} + C_L) \\&= kR_N C_{ginv} (2\gamma + C_L/C_{ginv}) \\&= t_{inv} (2\gamma + (4/3)f)\end{aligned}$$

# Logical Effort

- ❑ Defines ease of gate to drive external capacitance
- ❑ Inverter has the smallest logical effort and intrinsic delay of all static CMOS gates
- ❑ Logical effort LE is defined as:
  - $(R_{eq,gate} C_{in,gate}) / (R_{eq,inv} C_{in,inv})$
  - Easiest way to calculate (usually):
    - Size gate to **deliver same current** as an inverter, take ratio of **gate input capacitance** to inverter capacitance
- ❑ LE increases with gate complexity

# Logical Effort

$$t_{pgate} = t_{inv} (p + LEf)$$

Measure everything in units of  $t_{inv}$  (divide by  $t_{inv}$ ):

$p$  – intrinsic delay - gate parameter  $\neq f(W)$

$LE$  – logical effort – gate parameter  $\neq f(W)$

$f$  – electrical fanout =  $C_L/C_{in} = f(W)$

Normalize everything to an inverter:

$$LE_{inv} = 1, p_{inv} = \gamma$$

# Delay of a Logic Gate

Gate delay:


$$\text{Delay} = \underset{\text{effective fanout}}{EF} + \underset{\text{intrinsic delay}}{p} \quad (\text{measured in units of } t_{inv})$$

Effective fanout:

$$EF = \underset{\text{logical effort}}{LE} \underset{\text{electrical fanout}}{f} = C_L / C_{in}$$


Logical effort is a function of topology, independent of sizing  
Effective fanout is a function of load/gate size

# Logical Effort of Gates

 

# Delay Of NOR-2 Gate

 1. Size for same resistance as inverter
2. LE = ratio of input cap of gate versus inverter



Intrinsic capacitance ( $C_{dnor}$ ) =


$t_{pint}$  (NOR) =

# Question

Any logic function can be implemented using NOR gates only or NAND gates only!

Which of the two approaches is preferable in CMOS (from a performance perspective)?

# Logical Effort

 

Gate Type	Number of Inputs			
	1	2	3	n
Inverter	1			
NAND		$4/3$	$5/3$	$(n + 2)/3$
NOR		$5/3$	$7/3$	$(2n + 1)/3$
Multiplexer		2	2	2
XOR		4	12	

[From Sutherland, Sproull, Harris]