



EECS151/251A
Spring 2018
Digital Design and Integrated Circuits

Instructors:
John Wawrzynek and Nick Weaver

Lecture 17:
State


State...

- For digital design, we are always building finite state machines
 - Just the state can be damn large when you include external memory
 - So how do we build state?
- 4 basic state elements:
 - Registers
 - Fast, large, little array overhead
 - SRAM
 - Fairly fast, smaller, significant overhead
 - DRAM
 - Fairly slow, very dense, significant overhead
 - FLASH/EEPROM
 - Glacial, very dense, static, significant overhead

State Requires Storage & Access...



- Either as a feedback loop
 - Latches, Registers, SRAM
 - "Static"
- Or as a stored property
 - Electrons on a capacitor for DRAM
 - Electrons injected into a floating gate for FLASH
- Feedback loop...
 - Can just read the output directly (but there are tricks to speed it up)
- Stored property...
 - **Need** measurement circuits

Basic Static Storage Element


 


- If D is high, D_{b} will be driven low
 - Which makes D stay high
- Positive feedback

Positive Feedback: Bi-Stability

  



Meta-Stability

  



Gain should be larger than 1 in the transition region:
For flip-flops we hate metastability...
But for DRAM we love it (as we will see soon)!

Reminder: Latch versus Register (Flip-flop)

  - ◆ **Latch: level-sensitive**
clock is low - hold mode
clock is high - transparent





  - ◆ **Register: edge-triggered**
stores data when
clock rises



Creating a Latch & Flip-Flop...

  - Take our basic static storage element...
 - And make it switchable between storage
- When clock is low, have the feedback loop active
- When lock is high, Q gets D
- Can then chain 2 latches to make a Flip/Flop
 - One negative clocked, one positive




Adding an Enable

- A very common motif
 - `always @posedge clk begin`
 `q := en ? {something} : q`
 - Namely, only update Q if an additional enable signal is high
- Just simply add a higher level feedback loop with a mux.
 - {see board}

Creating a Register File... Reading

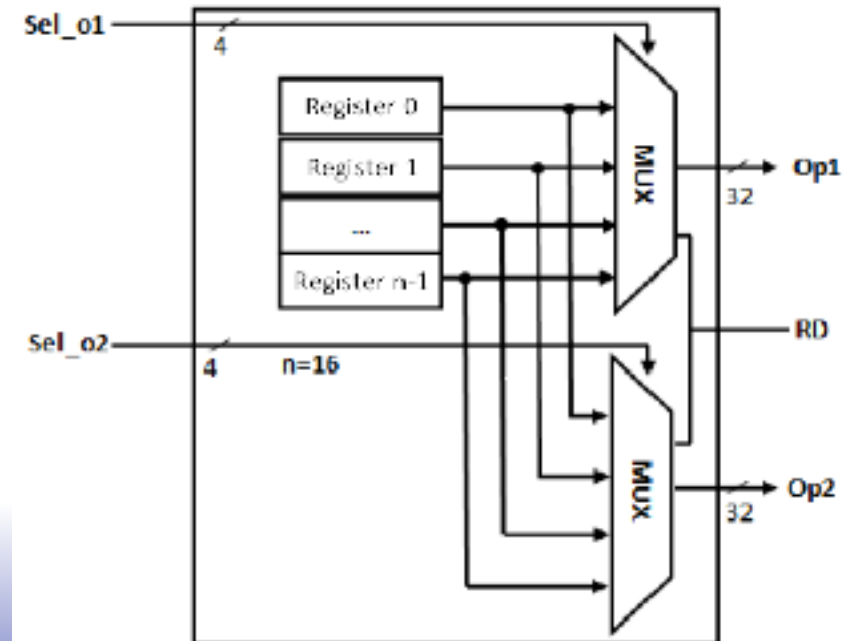
- Easiest thing is to start with a flip-flop...
- For reading, just have a MUX on the output to select the register in question
 - A common motif for all array memories:
If you want the n^{th} column/entry, you need a mux to select which one
- If done as flip/flops, this is simple...



Creating A Regfile... Write Enable

- We need to decode/demux the register address to determine which register to write...
 - Decoder is a very common operation:
 - Take an n bit number and assert a different line for each bit
 - Basically each output is an AND gate
- Commonly done with a "predecoder"
 - Compute $\overline{A_0}\overline{A_1}, \overline{A_0}A_1, A_0\overline{A_1}, A_0A_1$
 - Compute $\overline{A_2}\overline{A_3}, \overline{A_2}A_3, A_2\overline{A_3}, A_2A_3$
 - Then do the AND of the intermediaries


Predecoder and Decoder

 

But Flip-Flops are big...


- 12 transistors for both latches...
 - Plus 2 to create a negated clock (can be shared)
- Plus the multiplexor to add an enable...
 - Since we don't want to always write
- Can we use the basic static element...
 - And make something more compact?
- Yes: SRAM

SRAM Memory Cell

 


Complementary data values are written (read) from two sides

6-Transistor CMOS SRAM Cell

 

6T-SRAM — Layout

 


Compact cell

Bitlines: M2

Wordline: bootstrapped in M3


SRAM Operation - Read

Read

 


- Initially precharge both the bit lines to VDD
- BL gets pulled down if storing a 1, ~BL if its a 0
 - There is a fair amount of capacitance, must not overwhelm the inverter...


CMOS SRAM Analysis (Read)

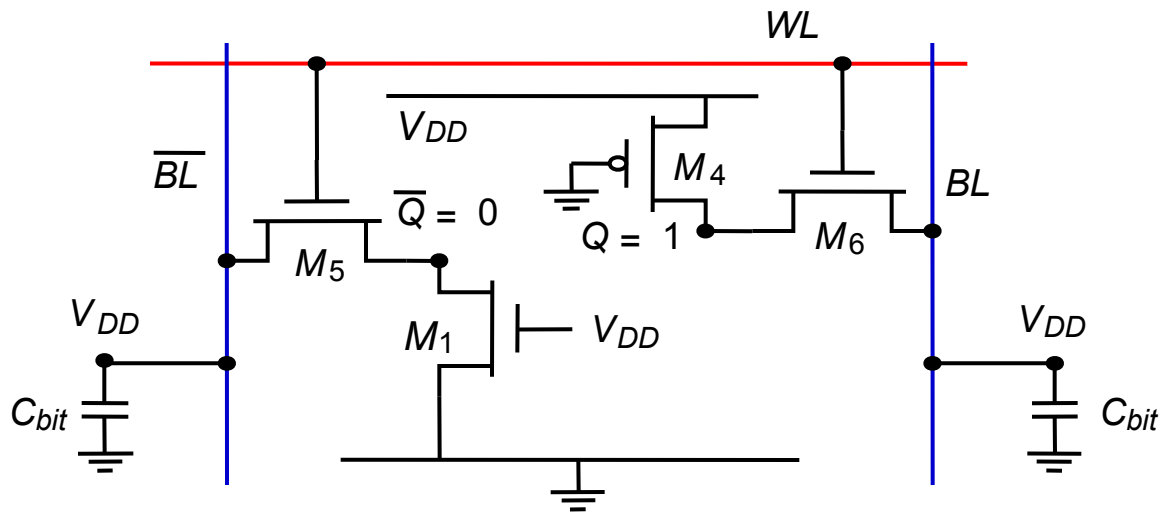

CMOS SRAM Analysis (Write is a fight)

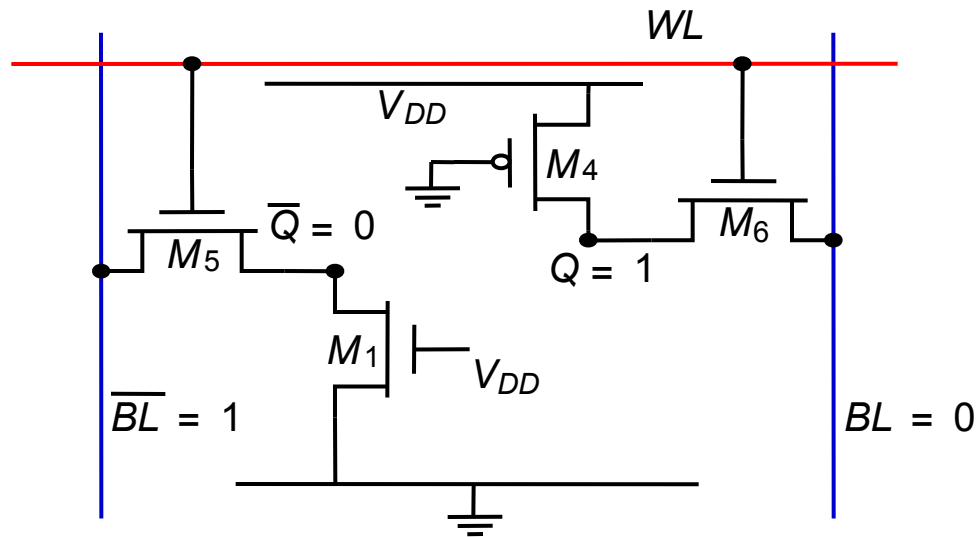


SRAM Column

 

Periphery

- ❑ Decoders
- ❑ Sense Amplifiers
- ❑ Input/Output Buffers
- ❑ Control / Timing Circuitry


Row Decoder

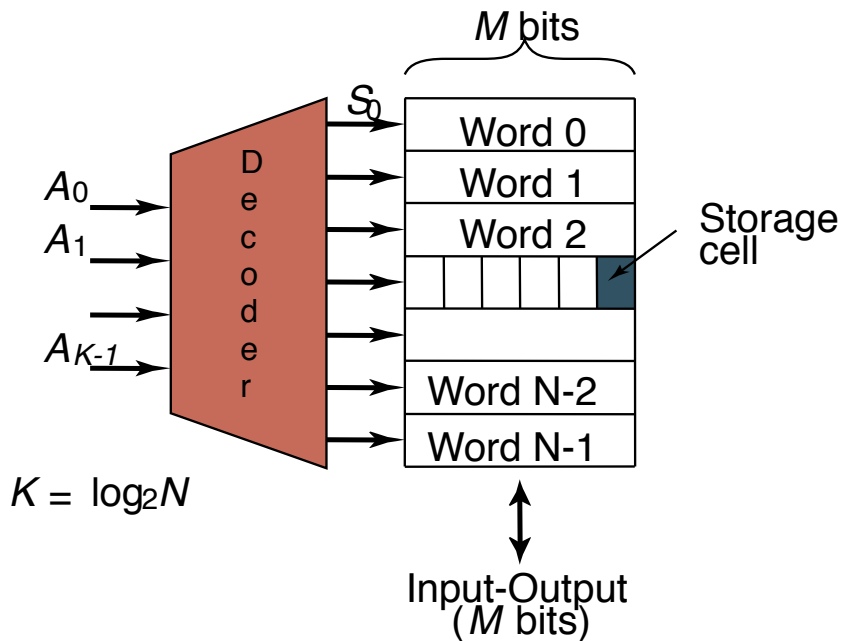


- Expands K address lines into N word lines
- A perfect example of logic/wire optimization
- Typically implemented in hierarchical fashion
- Area/Energy Trade-off

Speeding the Read: Sense-Amp

 - It takes a fair bit of time to pull down the appropriate bitline...
 - But really, why not just detect a difference
- Idea: Precharge a reference and then look for a small change




Differential Sense Amplifier

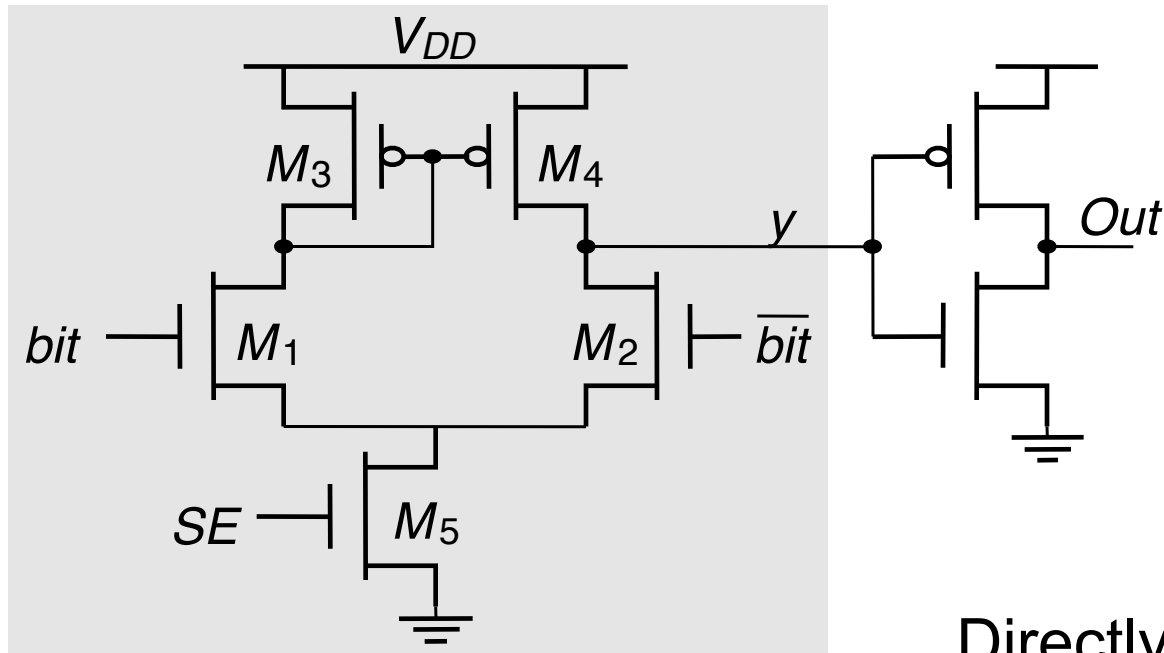


Directly applicable to
SRAMs

Differential Sensing – SRAM

 


(a) SRAM sensing scheme

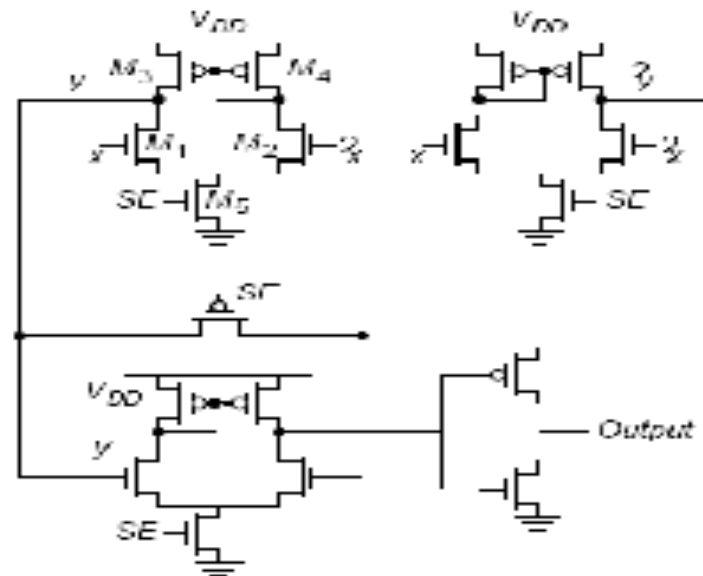

(b) two stage differential amplifier

Column Decoder

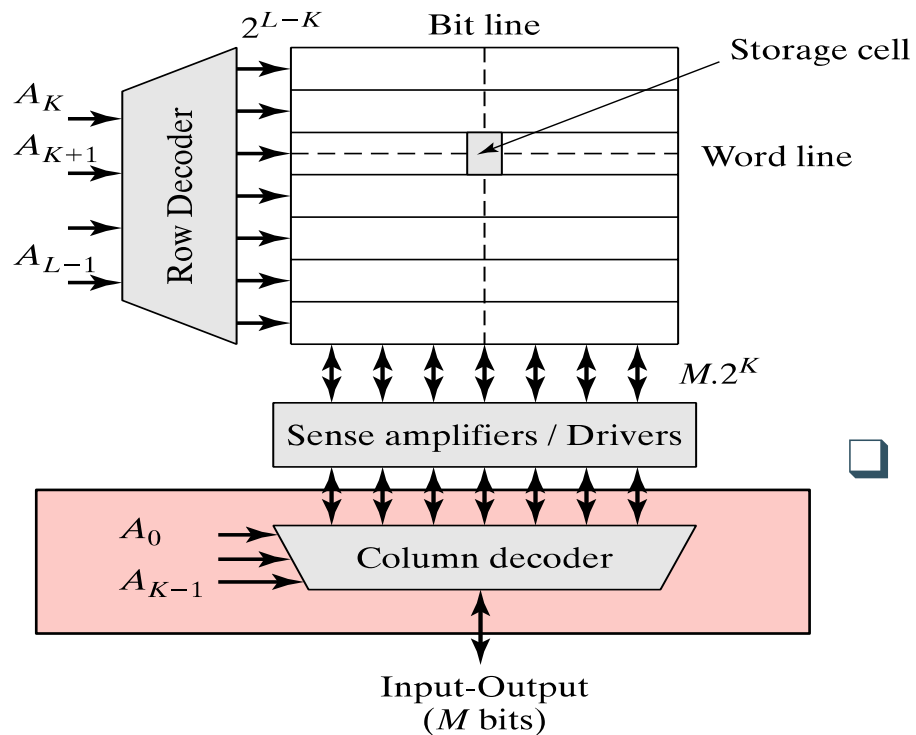

□ Basically a multiplexer


SRAM Read Cycle

- **Precharge** all the bitlines to Vdd...
- Then assert the word line from the decoder
 - One or the other bit lines starts to drop towards ground...
 - Sense-amp uses this to amplify the result quickly

SRAM Write Cycle


- Actively drive the bitlines to the correct value
 - Then assert the correct word line
- Result is that it will flip the data to the correct value

Sample Memory Interface Logic

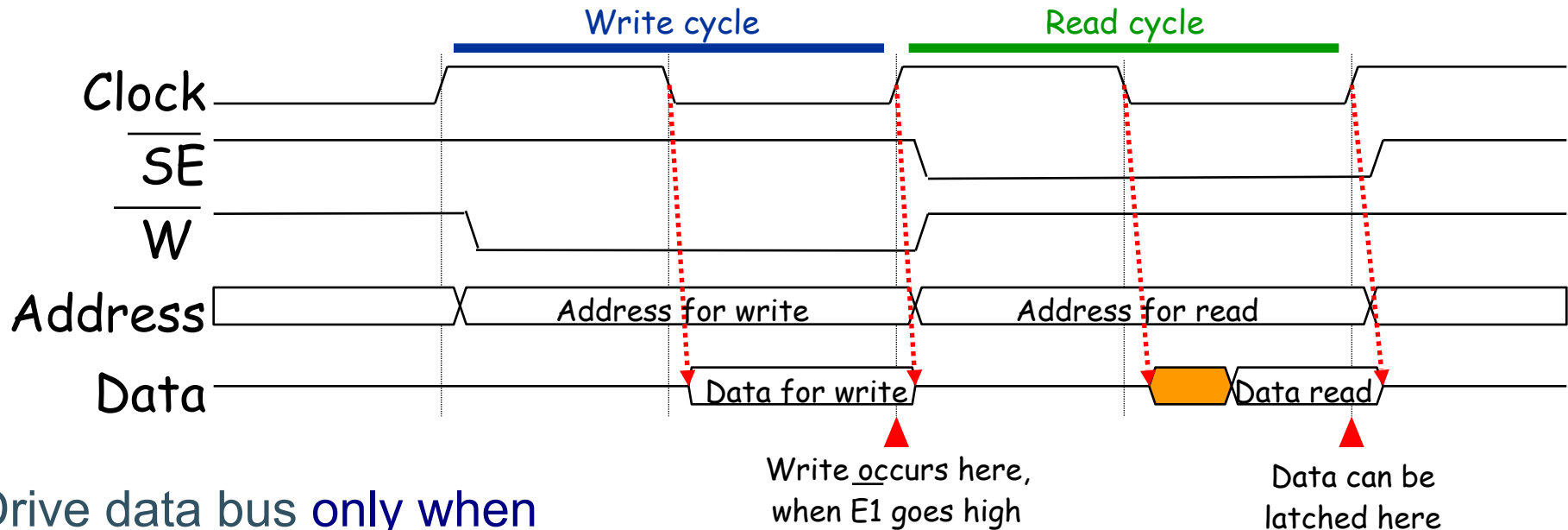


Drive data bus only when clock is low

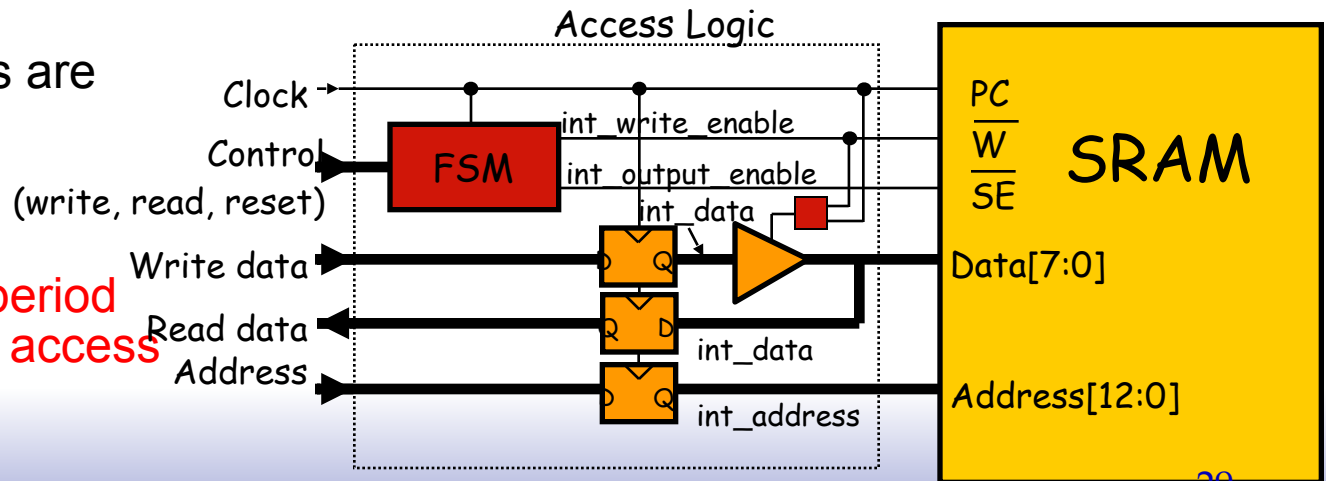- Ensures address are stable for writes
- Prevents bus contention (write, read, reset)
- Minimum clock period is twice memory access time



Adding More Ports

 
- Just add a separate set of row selection decoders, bitlines, wordlines, sense-amps...
 - But keep the common cell



DRAM...

- Damn, that SRAM cell is still big...
 - 6 transistors!!!!
- But we can also build small capacitors...
 - And small capacitors can hold their charge...
- IDEA: Lets store using ***dynamic*** logic...
 - Memory as state of charge on a capacitor
- Sense a very small amount of charge...
 - And when we check it, we can then update it

1-Transistor DRAM Cell

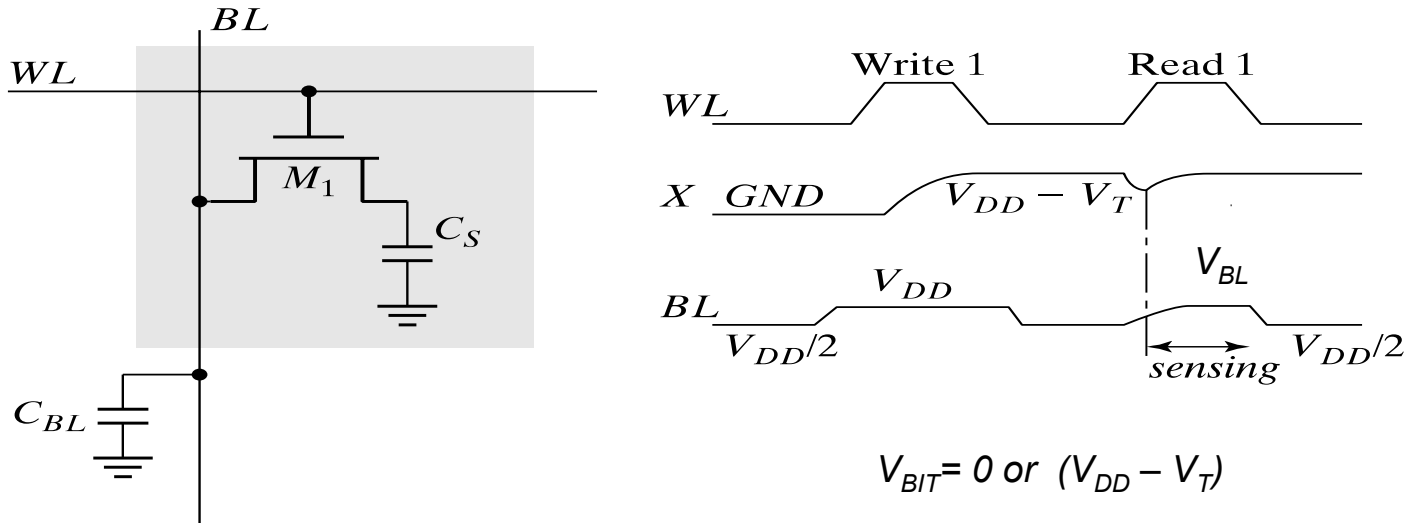


Write: C_S is charged or discharged by asserting WL and BL.
 Read: Charge redistribution takes place between bit line and storage capacitance

Voltage swing is small; typically around 250 mV.

$$\Delta V_1 = (V_{BIT1} - V_{PRE}) \frac{C_S}{C_S + C_{BL}} = \left(\frac{V_{DD}}{2} - V_T \right) \frac{C_S}{C_S + C_{BL}} \quad C_S \ll C_{BL}$$

$$\Delta V_0 = (V_{BIT0} - V_{PRE}) \frac{C_S}{C_S + C_{BL}} = -\frac{V_{DD}}{2} \frac{C_S}{C_S + C_{BL}}$$

Latch-Based Sense Amplifier (DRAM)

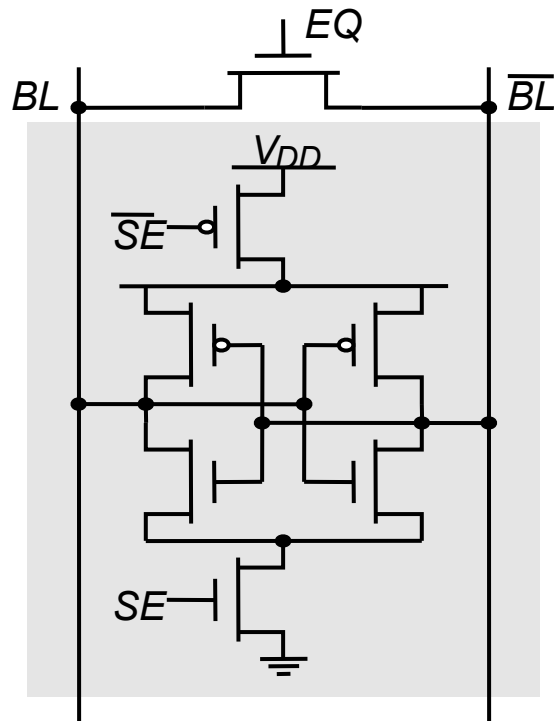

- Initialized in its meta-stable point with EQ
 - We also precharge the bit lines to the metastable point
- Once adequate voltage gap created, sense amp enabled with SE
- Positive feedback quickly forces output to a stable operating point.
 - Also acts to "write back" the value by driving the bit lines apart

What about that other bitline?

- We want something of the same capacitance as the bitline
 - Idea: Hey, we have a reference: The *next* column
- So we only read 1/2 the cells on a row for a given read
 - And use the other set of bit lines for reference


What About "Leakage"

- Those capacitors aren't great...
 - They will slowly lose charge over time...
- Idea: Just read **every cell** at a regular interval
 - This is called DRAM refresh
- Highly temperature dependent:
 - Hot DRAM tends to flip

What About Errors?


- Redundancy & sparing for manufacturing faults...
 - Check all the cells. If any fail in a column, replace that column with a spare column
- ECC memory for transient faults
 - EG, radioactive decay, cosmic ray, etc...
 - Cheap systems don't use ECC, but you ***should***

Advanced 1T DRAM Cells

 

Cell Plate Si
Capacitor Insulator
Storage Node Poly
2nd Field Oxide
Refilling Poly
Si Substrate


Trench Cell

 

Stacked-capacitor Cell

A “bank” of 128 Mb (512Mb chip -> 4 banks)

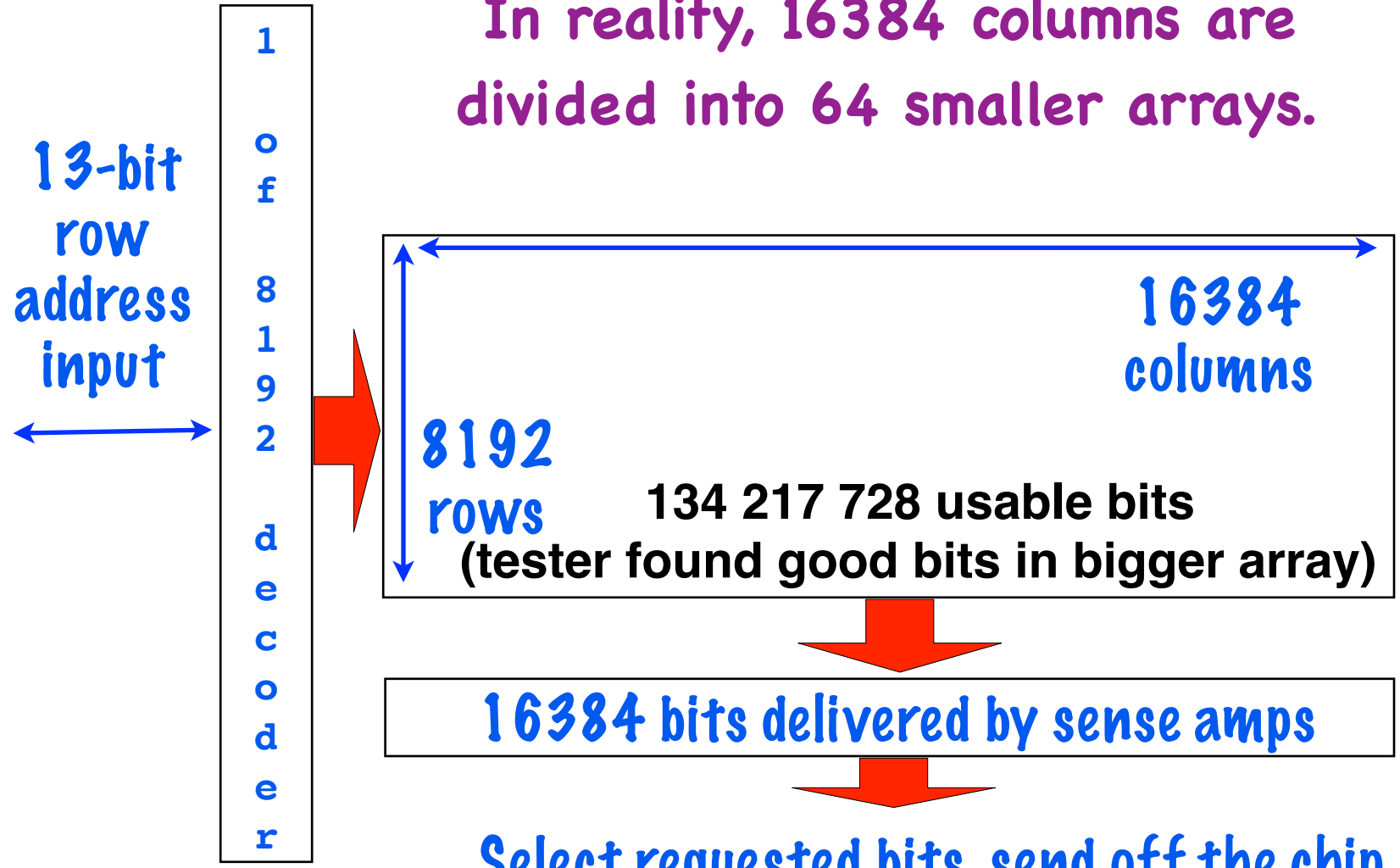In reality, 16384 columns are divided into 64 smaller arrays.




So *basic DRAM read operation...*

- Precharge all the bit lines in a block to $.5V_{dd}$
- Enable the word line for the desired row
 - "Row Access"
- Activate the sense-amps
 - Acts to read the bits *and* restore the bits
- Once the sense-amps have the row
 - Do the column access to get the sub pieces within the row
- A write will start with a read...
 - Then override the bits you want to set

“Sensing” is row read into sense amps

Slow! A **2.5ns** period DRAM (400 MT/s) can do row reads at only **55 ns** (18 MHz).

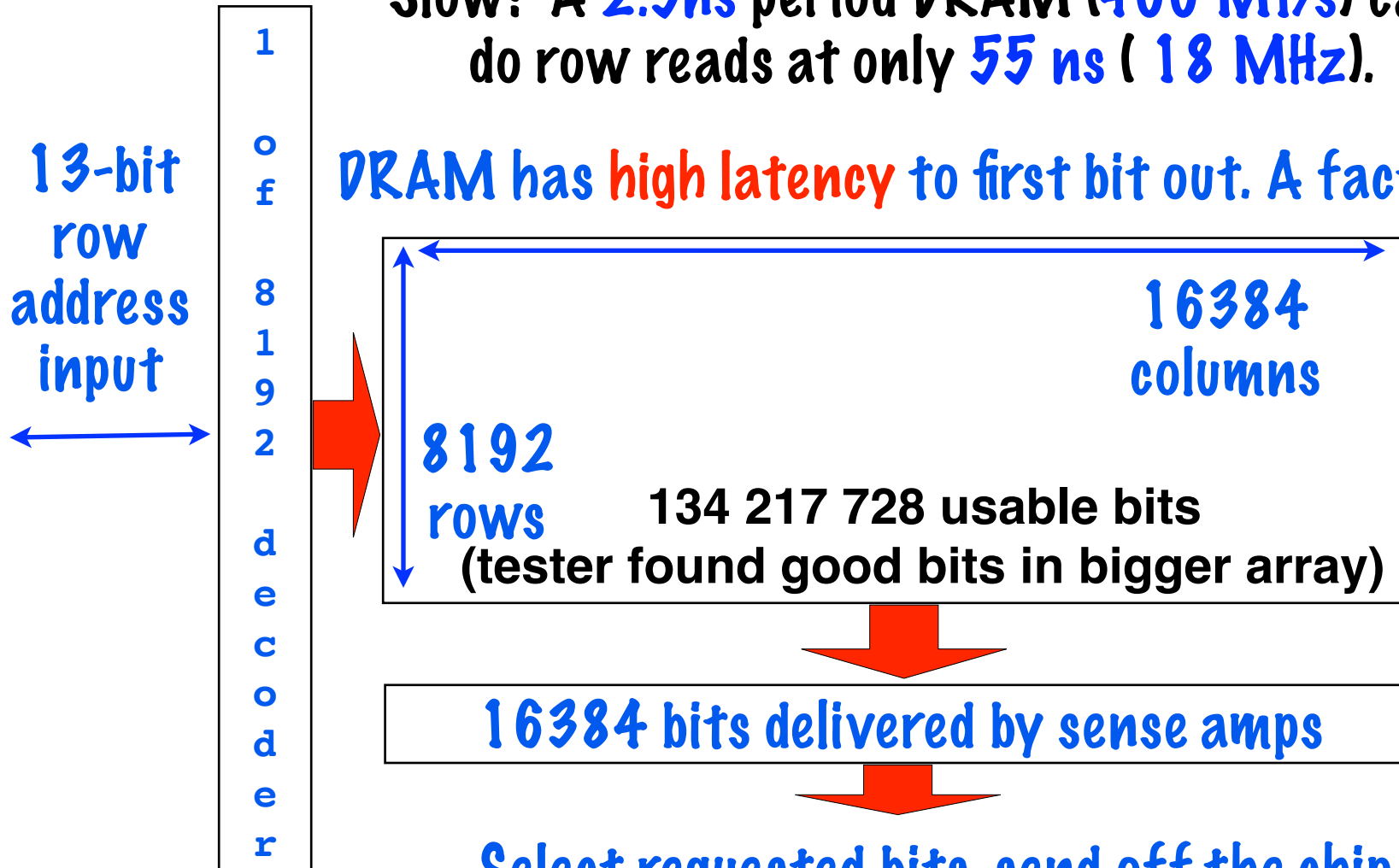DRAM has **high latency** to first bit out. A fact of life.



Select requested bits, send off the chip

Latency is not the same as bandwidth!

Thus, push to faster DRAM interfaces

13-bit row address input




What if we want all of the 16384 bits?

In row access time (55 ns) we can do

22 transfers at 400 MT/s.

16-bit chip bus $\rightarrow 22 \times 16 = 352 \text{ bits} \ll 16384$

Now the row access time looks fast!

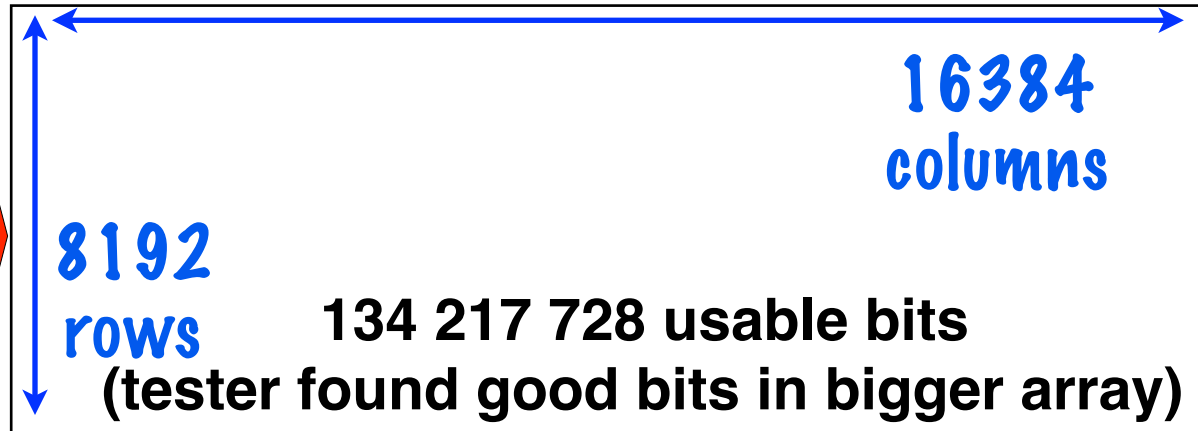

16384 bits delivered by sense amps

Select requested bits, send off the chip




Sadly, it's rarely this good ...

What if we want all of the 16384 bits?

The "we" for a CPU would be the program running on the CPU.

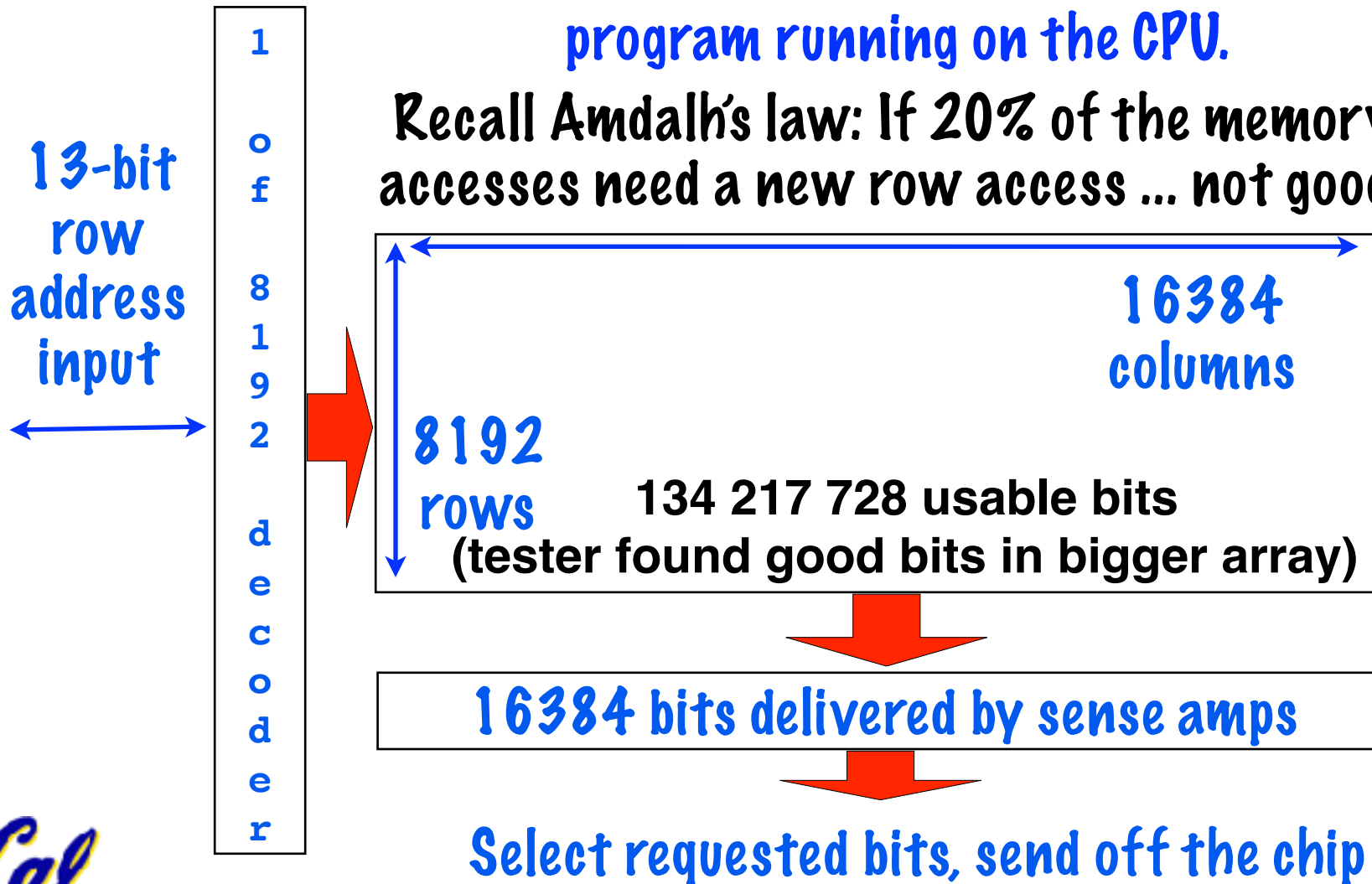Recall Amdahl's law: If 20% of the memory accesses need a new row access ... not good.



DRAM latency/bandwidth chip features



Columns: Design the right interface for CPUs to request the subset of a column of data it wishes:

16384 bits delivered by sense amps



Select requested bits, send off the chip



Interleaving: Design the right interface to the 4 memory banks on the chip, so several row requests run in parallel.

Bank 1

Bank 2


Bank 3

Bank 4

Off-chip interface for a Micron DDR part ...

A clocked bus:
200 MHz clock,
data transfers on
both edges (**DDR**).

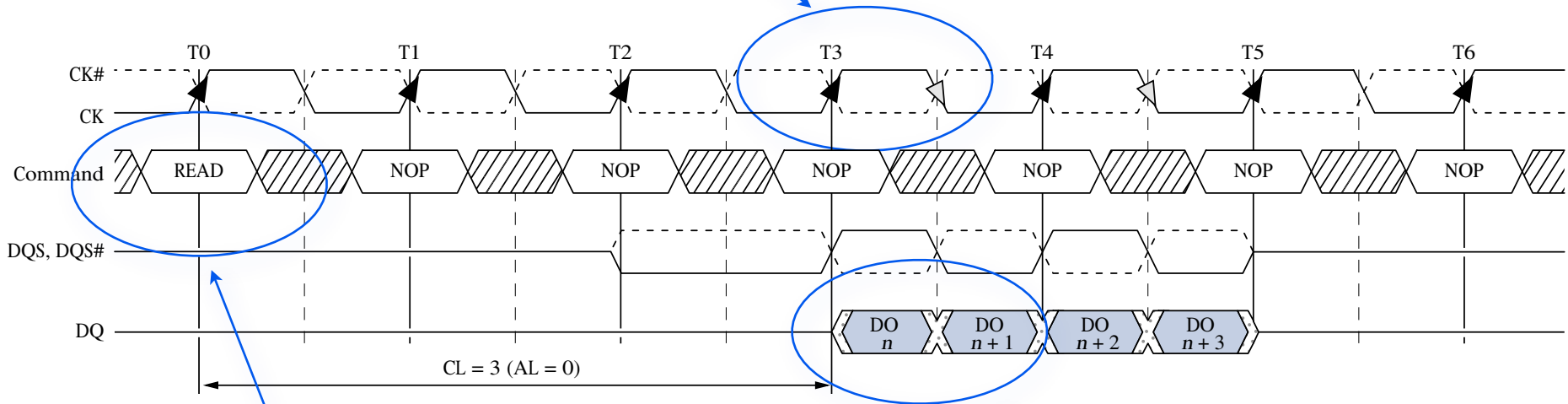Note! This example is **best-case!**
To access a new row, a slow **ACTIVE**
command must run before the **READ**.




DRAM is controlled via
commands
(**READ, WRITE,**
REFRESH, ...)

Synchronous data
output.



Opening a row before reading ...


Auto-Precharge
READ

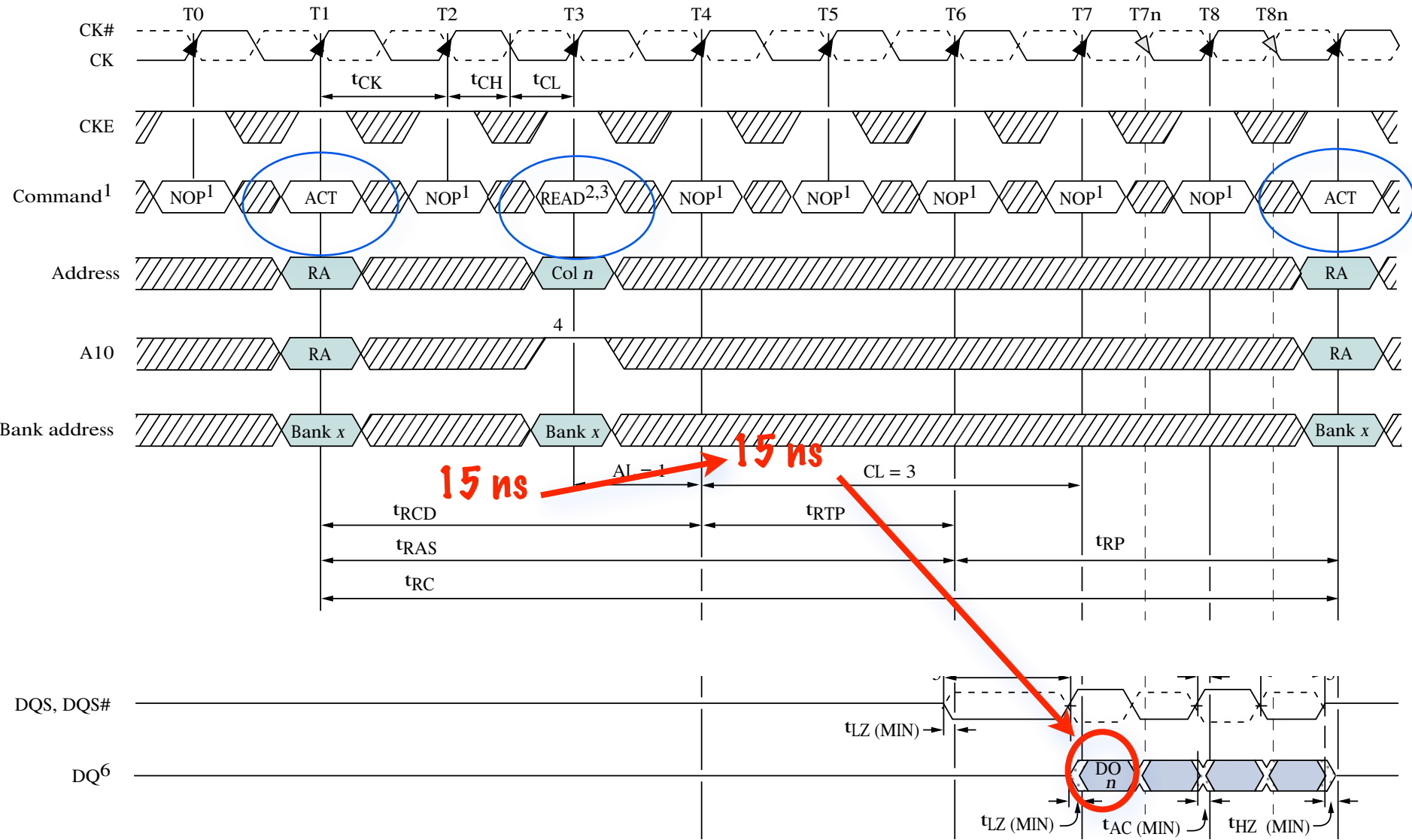

← 55 ns between row opens. →


55 ns between row opens.

However, we can read columns quickly

 


Note: This is a "normal read" (not Auto-Precharge).
Both READs are to the same bank, but different columns.

Why can we read columns quickly?

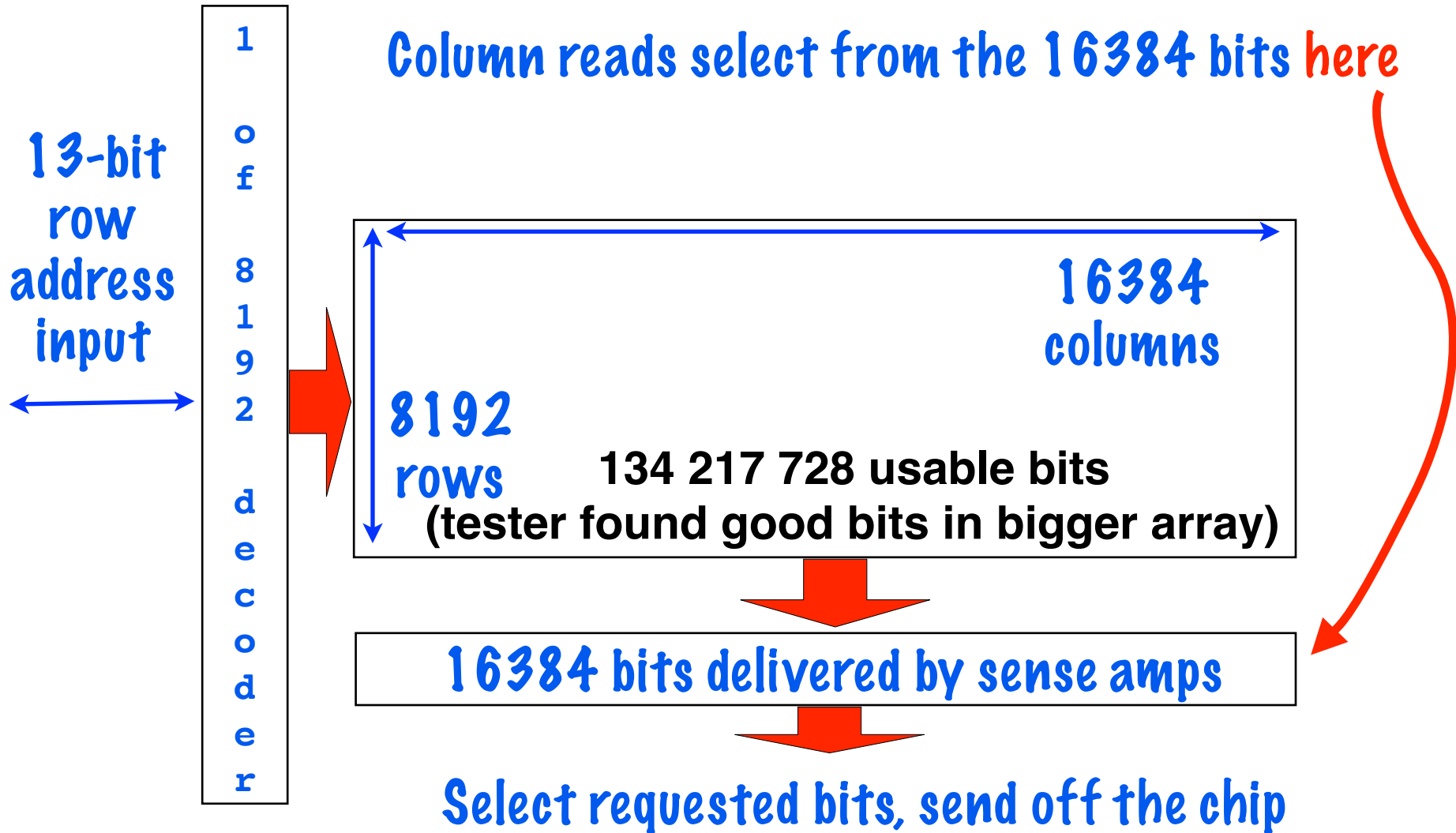

 Interleave: Access all 4 banks in parallel



Interleaving: Design the right interface to the 4 memory banks on the chip, so several row requests run in parallel.

Bank a

Bank b

Bank c


Bank d

Can also do other commands on banks concurrently.



The SDRAM interface evolution

- Initially: 1b transferred per data line per clock cycle
- DDR: Double Data Rate: 2b per clock
 - Rising & falling edge
- DDR2: 4b per clock
- DDR3: 8b per clock
- DDR4: 16b per clock!
- But the latency hasn't really improved much in a decade+!!!
 - So if you are touching DRAM, try to make everything sequential

Only part of a bigger story ...

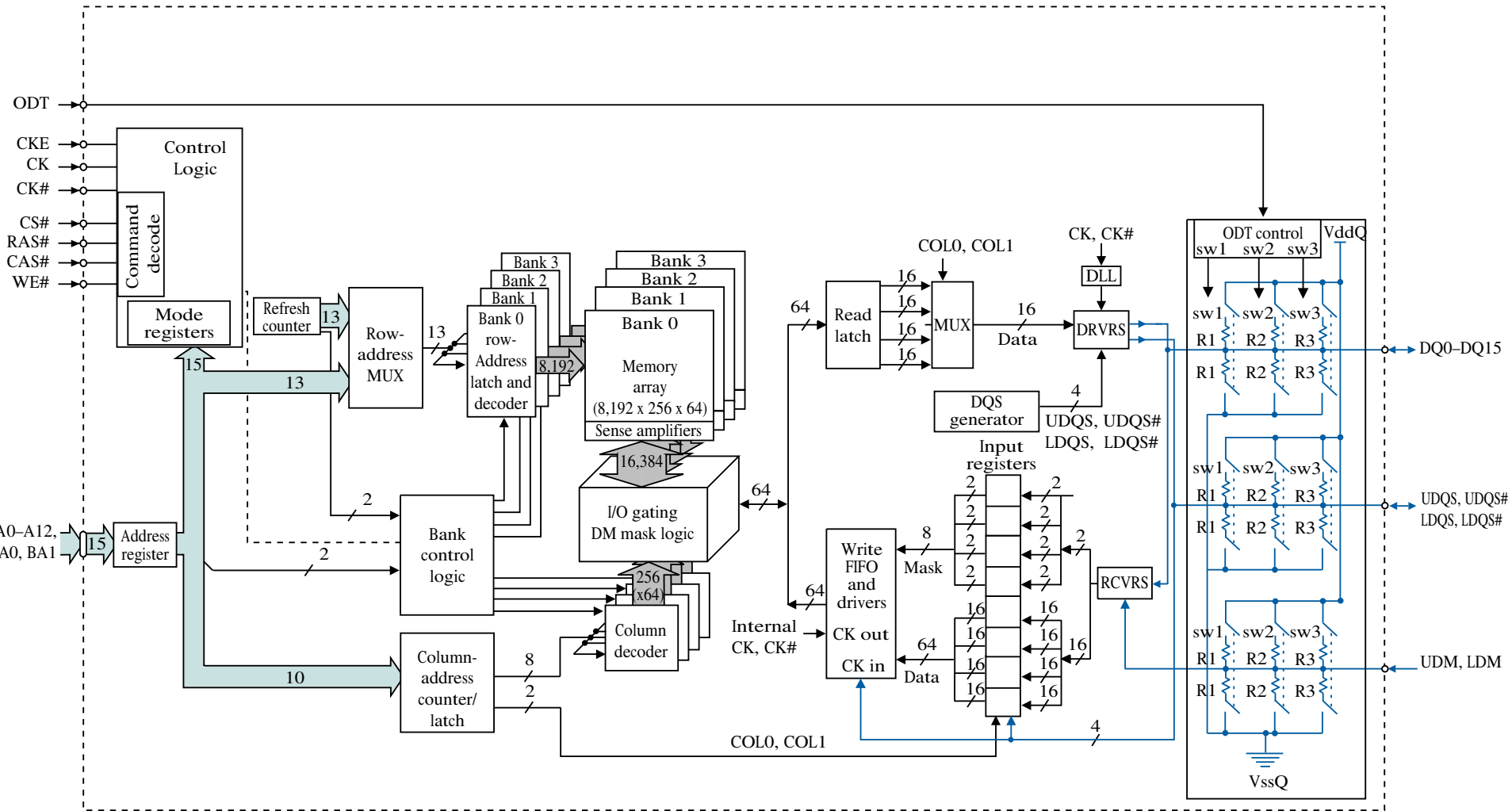


Only part of a bigger story ...

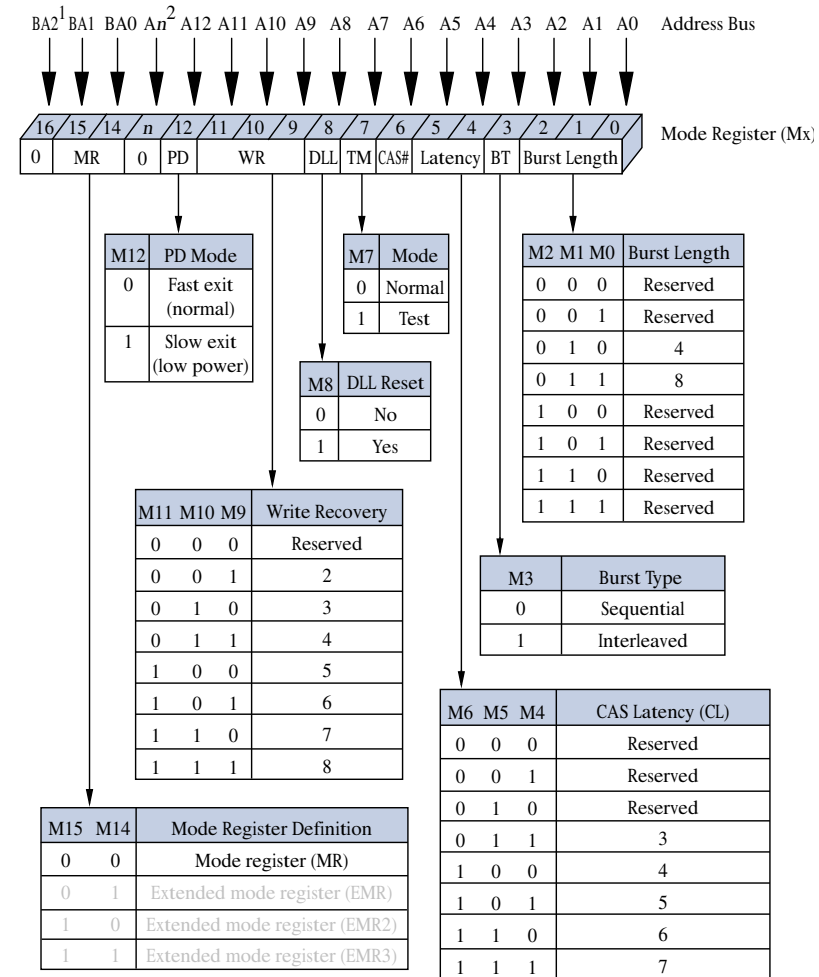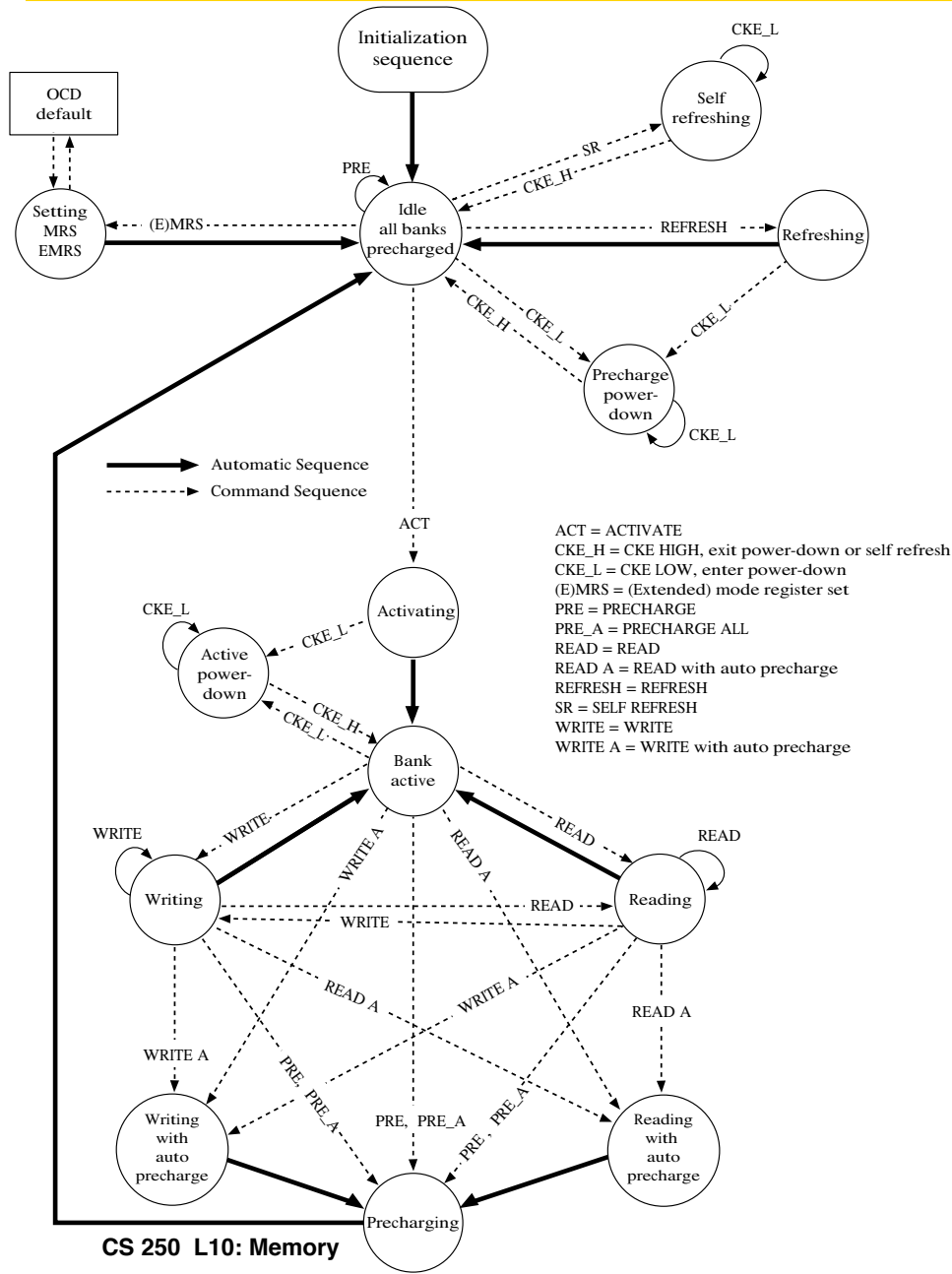


DRAM controllers: reorder requests

 (A) Without access scheduling (56 DRAM Cycles)



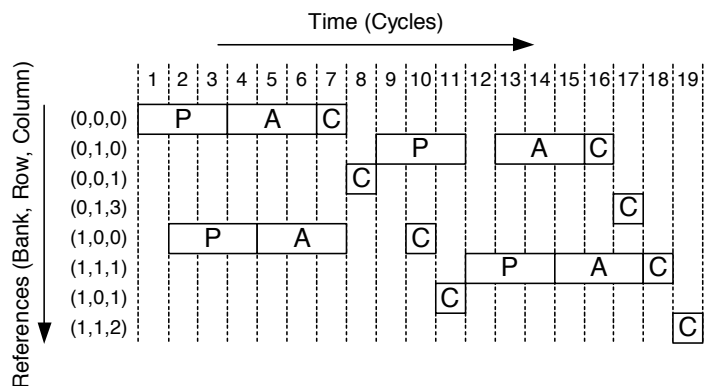(B) With access scheduling (19 DRAM Cycles)



DRAM Operations:

- P:** bank precharge (3 cycle occupancy)
- A:** row activation (3 cycle occupancy)
- C:** column access (1 cycle occupancy)




From: Memory Access Scheduling

And Rowhammer....


- These DRAM cells are not *perfectly* isolated...
 - In reading a row, there is a chance that it could flip a bit in a different row
- Rowhammer is a hardware attack
 - Repeatedly read the same DRAM row to cause bit-flips elsewhere
 - Asking the OS to effectively fill the memory with page tables...
 - And then when a bit flips, it will cause the page table to be mapped into the process address space...
 - And once you do that, you win!

The physics of FLASH memory

 

Two gates. But the middle one is not connected.

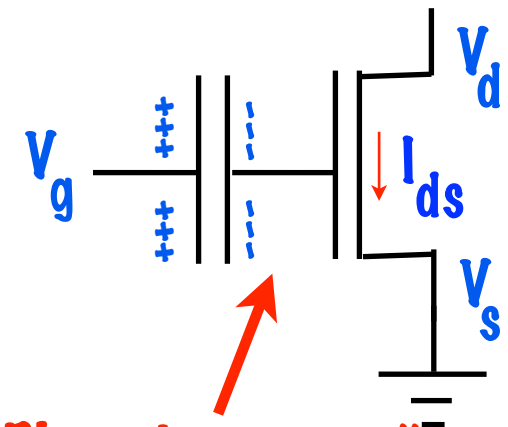1. Electrons “placed” on floating gate stay there for many years (ideally).
2. 10,000 electrons on floating gate shift transistor threshold by 2V.
3. In a memory array, shifted transistors hold “0”, unshifted hold “1”.




“Floating gate.”

Moving electrons on/off floating gate

A high drain voltage injects "hot electrons" onto floating gate.

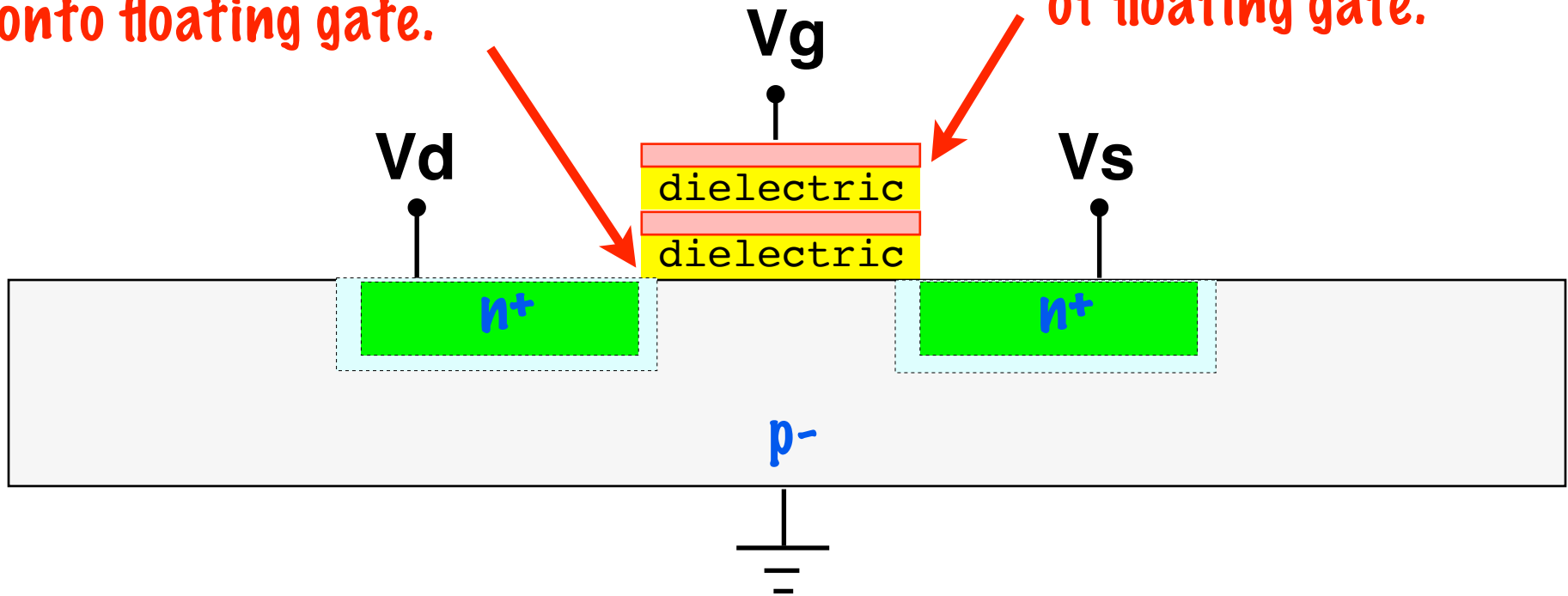A high gate voltage "tunnels" electrons off of floating gate.



1. Hot electron injection and tunneling produce tiny currents, thus writes are slow.

2. High voltages damage the floating gate. Too many writes and a bit goes "bad".

NAND Flash Memory



Flash: Disk Replacement

Chip “remembers”
for 10 years.

Presents memory to the
CPU as a set of **pages**.

Page format:

2048 Bytes

(user data)

+

64 Bytes

(meta data)

1GB Flash: 512K pages

2GB Flash: 1M pages


4GB Flash: 2M pages



Reading a Page ...


33 MB/s Read Bandwidth

Bus Control

 


8-bit data or address
(bi-directional)

Read Operation

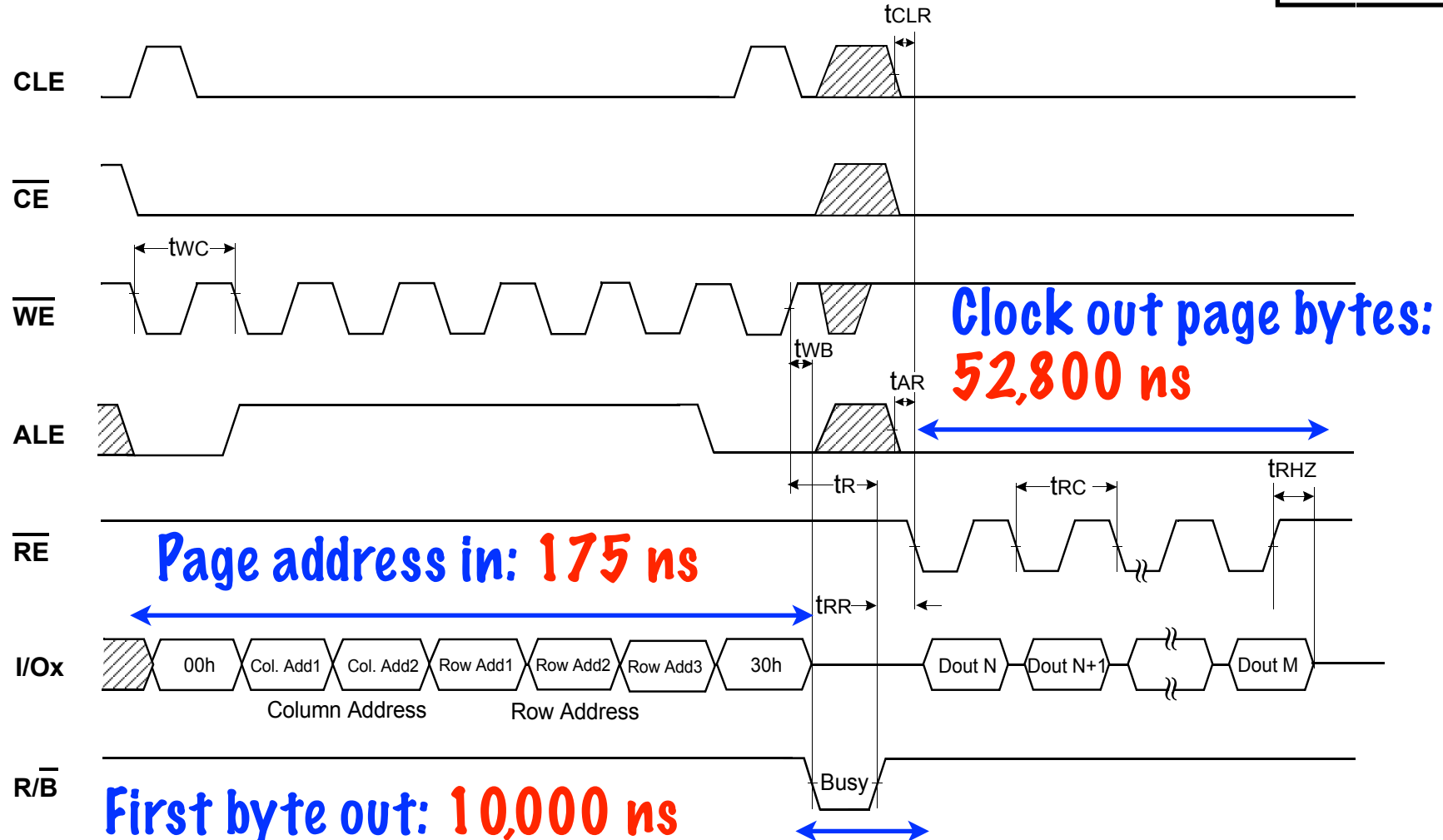

Where Time Goes

Figure 1. K9K8G08U0A Functional Block Diagram

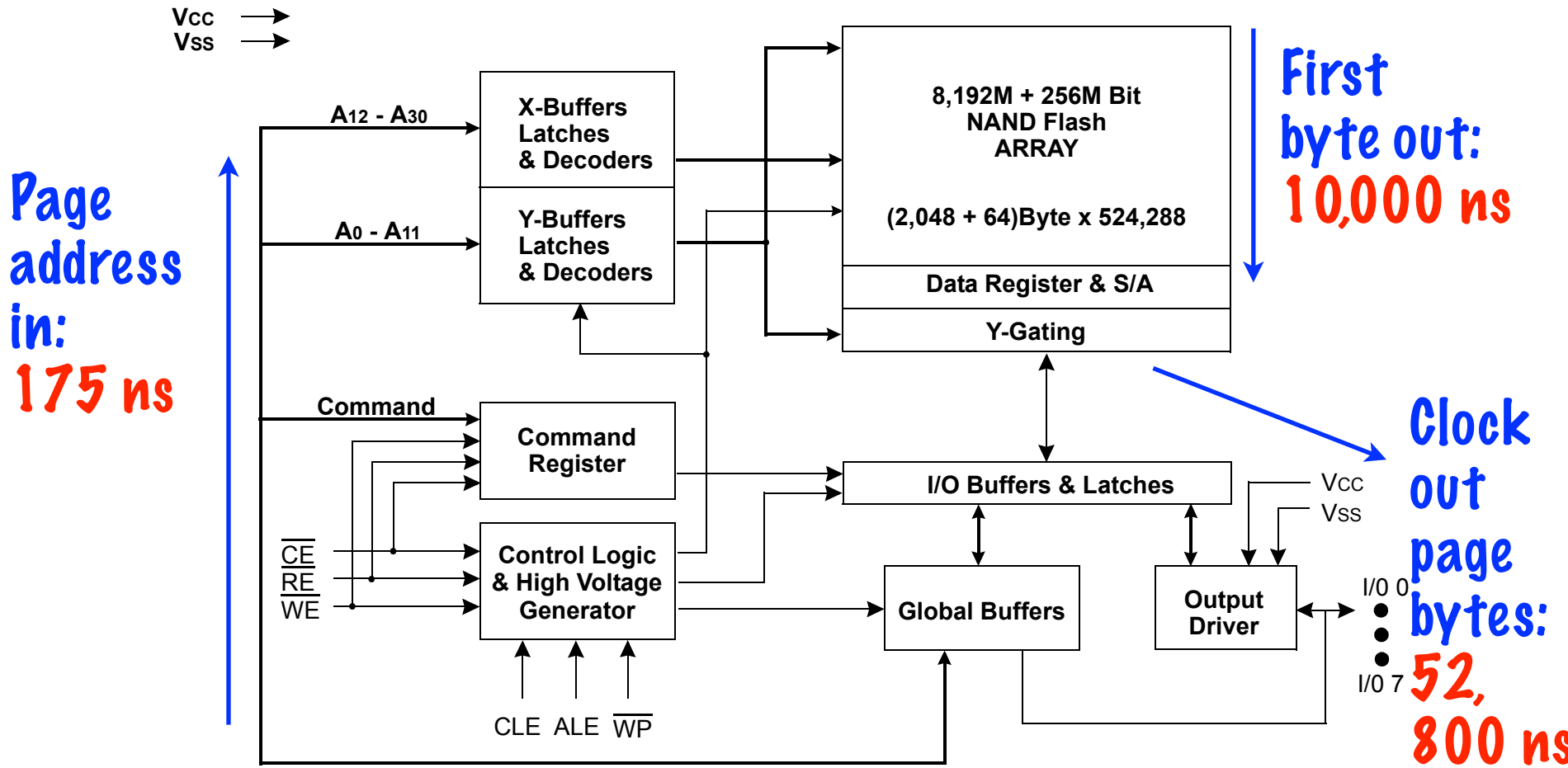


Writing a Page ...

A page lives in a **block** of 64 pages:

1GB Flash: 8K blocks

2GB Flash: 16K blocks

4GB Flash: 32K blocks

 

To write a page:

1. **Erase** all pages in the block
(cannot erase just one page).

Time: 1,500,000 ns

2. May **program** each page
individually, exactly **once**.

Time: 200,000 ns
per page.

Block lifetime: 100,000 erase/program cycles.


Block Failure

Even when new, not all blocks work!

1GB: 8K blocks, **160** may be bad.

2GB: 16K blocks, **220** may be bad.

4GB: 32K blocks, **640** may be bad.

 

During factory testing, Samsung writes **good/bad** info for each block in the **meta data bytes**.




After an erase/program, chip can say **“write failed”**, and **block** is now **“bad”**. OS must recover (migrate bad block data to a new block). **Bits** can also go bad **“silently”** (!!!).

Flash controllers: Chips or Verilog IP ...

Flash memory controller manages write lifetime management, block failures, silent bit errors ...

Denali NAND Flash Controller

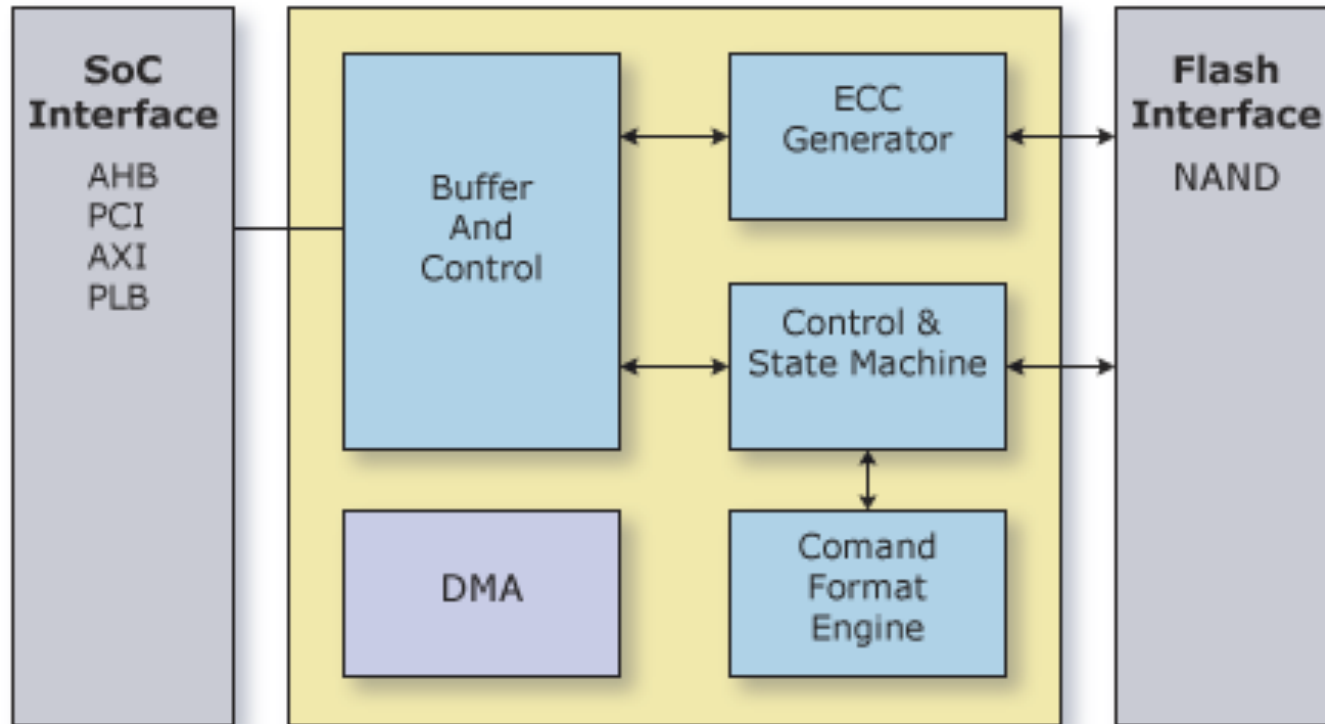

Software sees a **“perfect”** disk-like storage device.

Actually Using Memory

- Two options:
 - Directly instantiate memory blocks:
Can either use IP generators or instantiate primitives directly
 - Write Verilog with something the tools can infer
 - `parameter n = 4;`
`parameter w = 8;`
`reg [w-1:0] reg_array [2**n-1:0];`
`always @ posed clk begin`
`if (we) reg[write_addr] <= din;`
`end`
`always @* begin`
`dout <= reg[read_addr]`
`end`
 - **should** be inferred as a simple dual-port memory:
One synchronous write port, one asynchronous read port

Some Types of Memory...

- Single port:
 - One address port, one data in port, one data out port
 - Can read or write
- Simple dual port:
 - Two address ports, one for reading, one for writing
 - Very good for implementing FIFOs!
- True dual port:
 - Two address ports, both can be used for reading or writing
- Suggestion for Xilinx version of the project:
 - Best way to do the processor reg-file is instantiate simple-dual-port memories