



EECS 151/251A
Spring 2018
Digital Design and
Integrated Circuits

Instructors:
Weaver & Wawrzynek

Lecture 4

Administrativa




Verilog Assignment Types

Verilog – So Far


- Two types of description:
 - Structural: design as a composition of blocks (also called a netlist)
 - Maps directly into hardware
 - Behavioral: design as a set of equations
 - Requires “compiler” (synthesis tool) to generate hardware

Example - Ripple Adder

```
module FullAdder(a, b, ci, r, co);  
  input a, b, ci;  
  output r, co;  
  
  assign r = a ^ b ^ ci;  
  assign co = a&ci | a&b | b&cin;  
  
endmodule
```

 
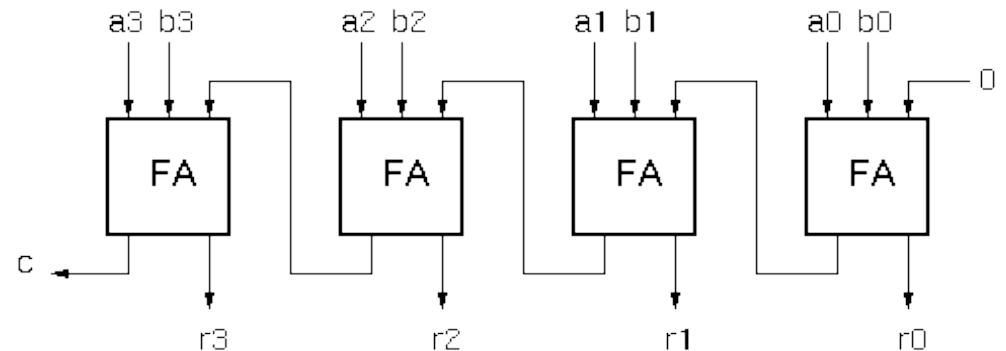
```
module Adder(A, B, R);  
  input [3:0] A;  
  input [3:0] B;  
  output [4:0] R;  
  
  wire c1, c2, c3;  
  FullAdder  
  add0(.a(A[0]), .b(B[0]), .ci(1'b0), .co(c1), .r(R[0]) ),  
  add1(.a(A[1]), .b(B[1]), .ci(c1), .co(c2), .r(R[1]) ),  
  add2(.a(A[2]), .b(B[2]), .ci(c2), .co(c3), .r(R[2]) ),  
  add3(.a(A[3]), .b(B[3]), .ci(c3), .co(R[4]), .r(R[3]) );  
  
endmodule
```



Non-continuous Assignments

A bit strange from a hardware specification point of view.
Shows off Verilog roots as a simulation language.

“always” block example:

```
module and_or_gate (out, in1, in2, in3);
```

```
  input      in1, in2, in3;
```

```
  output    out;
```

```
  reg      out;
```

“reg” type declaration. Not really a register in this case. Just a Verilog idiosyncrasy.

```
  always @(in1 or in2 or in3) begin
```

```
    out = (in1 & in2) | in3;
```

```
  end
```

keyword

“sensitivity” list, triggers the action in the body.

```
endmodule
```

brackets multiple statements (not necessary in this example).

Isn't this just: `assign out = (in1 & in2) | in3;?`

Why bother?

Always Blocks

Always blocks give us some constructs that are impossible or awkward in continuous assignments.

case statement example:

```
module mux4 (in0, in1, in2, in3, select, out);  
  input in0,in1,in2,in3;  
  input [1:0] select;  
  output      out;  
  reg         out;
```

```
  always @ (in0 in1 in2 in3 select)  
    case (select)  
      2'b00: out=in0;  
      2'b01: out=in1;  
      2'b10: out=in2;  
      2'b11: out=in3;  
    endcase  
endmodule // mux4
```

keyword

The statement(s) corresponding to whichever constant matches "select" get applied.

Couldn't we just do this with nested "if"s?

Well yes and no!

Always Blocks


Nested if-else example:

```
module mux4 (in0, in1, in2, in3, select, out);  
    input in0,in1,in2,in3;  
    input [1:0] select;  
    output      out;  
    reg         out;  
  
    always @ (in0 in1 in2 in3 select)  
        if (select == 2'b00) out=in0;  
        else if (select == 2'b01) out=in1;  
            else if (select == 2'b10) out=in2;  
                else out=in3;  
endmodule // mux4
```


Nested if structure leads to “priority logic” structure, with different delays for different inputs (in3 to out delay > than in0 to out delay). Case version treats all inputs the same.

Review - Ripple Adder Example
 
```
module FullAdder(a, b, ci, r, co);  
  input a, b, ci;  
  output r, co;  
  
  assign r = a ^ b ^ ci;  
  assign co = a&ci + a&b + b&cin;  
  
endmodule
```


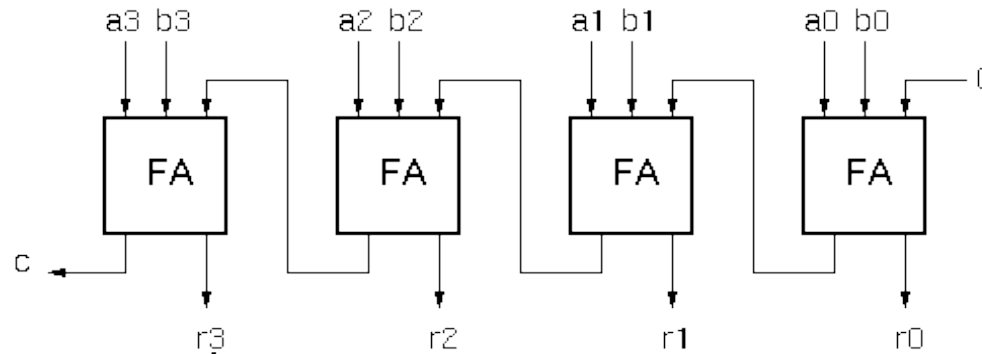
```
module Adder(A, B, R);  
  input [3:0] A;  
  input [3:0] B;  
  output [4:0] R;  
  
  wire c1, c2, c3;  
  FullAdder  
  add0(.a(A[0]), .b(B[0]), .ci(1'b0), .co(c1), .r(R[0]) ),  
  add1(.a(A[1]), .b(B[1]), .ci(c1), .co(c2), .r(R[1]) ),  
  add2(.a(A[2]), .b(B[2]), .ci(c2), .co(c3), .r(R[2]) ),  
  add3(.a(A[3]), .b(B[3]), .ci(c3), .co(R[4]), .r(R[3]) );  
  
endmodule
```



Example - Ripple Adder Generator

Parameters give us a way to generalize our designs. A module becomes a “generator” for different variations. Enables design/module reuse. Can simplify testing.

Declare a parameter with default value.

```
module Adder(A, B, R);  
  parameter N = 4;  
  input [N-1:0] A;  
  input [N-1:0] B;  
  output [N:0] R;  
  wire [N:0] C;
```

Note: this is not a port. Acts like a “synthesis-time” constant.

Replace all occurrences of “4” with “N”.

variable exists only in the specification - not in the final circuit.

Keyword that denotes synthesis-time operations

For-loop creates instances (with unique names)

```
  genvar i;  
  generate  
    for (i=0; i<N; i=i+1) begin:bit  
      FullAdder add(.a(A[i], .b(B[i]), .ci(C[i]), .co(C[i+1]), .r(R[i]));  
    end  
  endgenerate  
  
  assign C[0] = 1'b0;  
  assign R[N] = C[N];  
endmodule
```

```
Adder adder4 ( ... );
```

```
Adder #(.N(64))  
adder64 ( ... );
```

**Overwrite parameter
N at instantiation.**

More on Generate Loop

Permits variable declarations, modules, user defined primitives, gate primitives, continuous assignments, initial blocks and always blocks to be instantiated multiple times using a for-loop.

```
// Gray-code to binary-code converter
module gray2bin1 (bin, gray);
    parameter SIZE = 8;
    output [SIZE-1:0] bin;
    input  [SIZE-1:0] gray;
```

```
genvar i;
```

```
generate for (i=0; i<SIZE; i=i+1) begin:bit
    assign bin[i] = ^gray[SIZE-1:i];
end endgenerate
```

```
endmodule
```

variable exists only in the specification - not in the final circuit.

Keywords that denotes synthesis-time operations

For-loop creates instances of assignments

Loop must have constant bounds


generate if-else-if based on an expression that is deterministic at the time the design is synthesized.

generate case : selecting case expression must be deterministic at the time the design is synthesized.

Defining Processor ALU in 5 mins

- Modularity is essential to the success of large designs
- High-level primitives enable direct synthesis of behavioral descriptions (functions such as additions, subtractions, shifts (<< and >>), etc.

Example: A 32-bit ALU

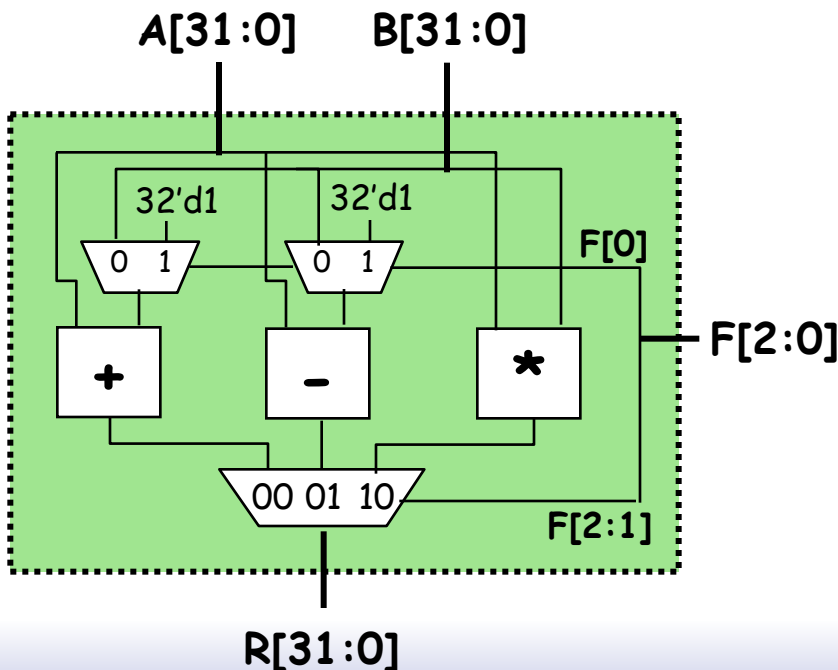

Function Table

F2	F1	F0	Function
0	0	0	A + B
0	0	1	A + 1
0	1	0	A - B
0	1	1	A - 1
1	0	X	A * B

Module Definitions

2-to-1 MUX

```
module mux32two(i0,i1,sel,out);
```

```
input [31:0] i0,i1;
```

```
input sel;
```

```
output [31:0] out;
```

```
assign out = sel ? i1 : i0;
```

```
endmodule
```

32-bit Adder

```
module add32(i0,i1,sum);
```

```
input [31:0] i0,i1;
```

```
output [31:0] sum;
```

```
assign sum = i0 + i1;
```

```
endmodule
```

32-bit Subtractor

```
module sub32(i0,i1,diff);
```

```
input [31:0] i0,i1;
```

```
output [31:0] diff;
```

```
assign diff = i0 - i1;
```

```
endmodule
```

3-to-1 MUX

```
module mux32three(i0,i1,i2,sel,out);
```

```
input [31:0] i0,i1,i2;
```

```
input [1:0] sel;
```

```
output [31:0] out;
```

```
reg [31:0] out;
```

```
always @ (i0 or i1 or i2 or sel)
```

```
begin
```

```
case (sel)
```

```
2'b00: out = i0;
```

```
2'b01: out = i1;
```

```
2'b10: out = i2;
```

```
default: out = 32'bx;
```

```
endcase
```

```
end
```

```
endmodule
```

16-bit Multiplier

```
module mul16(i0,i1,prod);
```

```
input [15:0] i0,i1;
```

```
output [31:0] prod;
```

```
// this is a magnitude multiplier
```

```
// signed arithmetic later
```

```
assign prod = i0 * i1;
```

```
endmodule
```

Top-Level ALU Declaration

Given submodules:

```

module mux32two(i0,i1,sel,out);
module mux32three(i0,i1,i2,sel,out);
module add32(i0,i1,sum);
module sub32(i0,i1,diff);
module mul16(i0,i1,prod);


```

Declaration of the ALU Module:

```

module alu(a, b, f, r);
input [31:0] a, b;
input [2:0] f;
output [31:0] r;
wire [31:0] addmux_out, submux_out;
wire [31:0] add_out, sub_out, mul_out;
mux32two adder_mux(.io(b), .i1(32'd1), .sel(f[0]), .out(addmux_out));
mux32two sub_mux(.io(b), .i1(32'd1), .sel(f[0]), .out(submux_out));
add32 our_adder(.i0(a), .i1(addmux_out), .sum(add_out));
sub32 our_subtractor(.i0(a), .i1(submux_out), .diff(sub_out));
mul16 our_multiplier(.i0(a[15:0]), .i1(b[15:0]), .prod(mul_out));
mux32three_output_mux(.i0(add_out), .i1(sub_out), .i2(mul_out), .sel(f[2:1]), .out(r));
endmodule

```

 

intermediate output nodes ●

module names


(unique) instance names

corresponding wires/regs in module alu

Top-Level ALU Declaration, take 2

- No Hierarchy:
- Declaration of the ALU Module:
 
```
module alu(a, b, f, r);  
  input [31:0] a, b;  
  input [2:0] f;  
  output [31:0] r;  
  always @ (a or b or f)  
  case (f)  
    3'b000: r = a + b;  
    3'b001: r = a + 1'b1;  
    3'b010: r = a - b;  
    3'b011: r = a - 1'b1;  
    3'b100: r = a * b;  
    default: r = 32'bx;  
  endcase  
endmodule
```



Will this synthesize into 2 adders and 2 subtractors or 1 of each?

Verilog in EECS 151/251A – Simple Rules

- ❑ We use behavioral modeling at the bottom of the hierarchy
- ❑ Use instantiation to 1) build hierarchy and, 2) map to FPGA and ASIC resources not supported by synthesis.
- ❑ Favor continuous assign and avoid always blocks unless:
 - no other alternative: ex: state elements, case
 - helps readability and clarity of code: ex: large nested if else
- ❑ Use named ports.
- ❑ Verilog is a big language. This is only an introduction.
 - Harris & Harris book chapter 4 is a good source.
 - ***Be careful of what you read on the web.*** Many bad examples out there.
 - We will be introducing more useful constructs throughout the semester. Stay tuned!

Final thoughts on Verilog Examples

Verilog looks like C, but it describes hardware:

Entirely different semantics: multiple physical elements with parallel activities and temporal relationships.

A large part of digital design is knowing how to write Verilog that gets you the desired circuit. First understand the circuit you want then figure out how to code it in Verilog. If you try to write Verilog without a clear idea of the desired circuit, you will struggle.

As you get more practice, you will know how to best write Verilog for a desired result.


Be suspicious of the synthesis tools! Check the output of the tools to make sure you get what you want.



Sequential Elements

Only Two Types of Circuits Exist

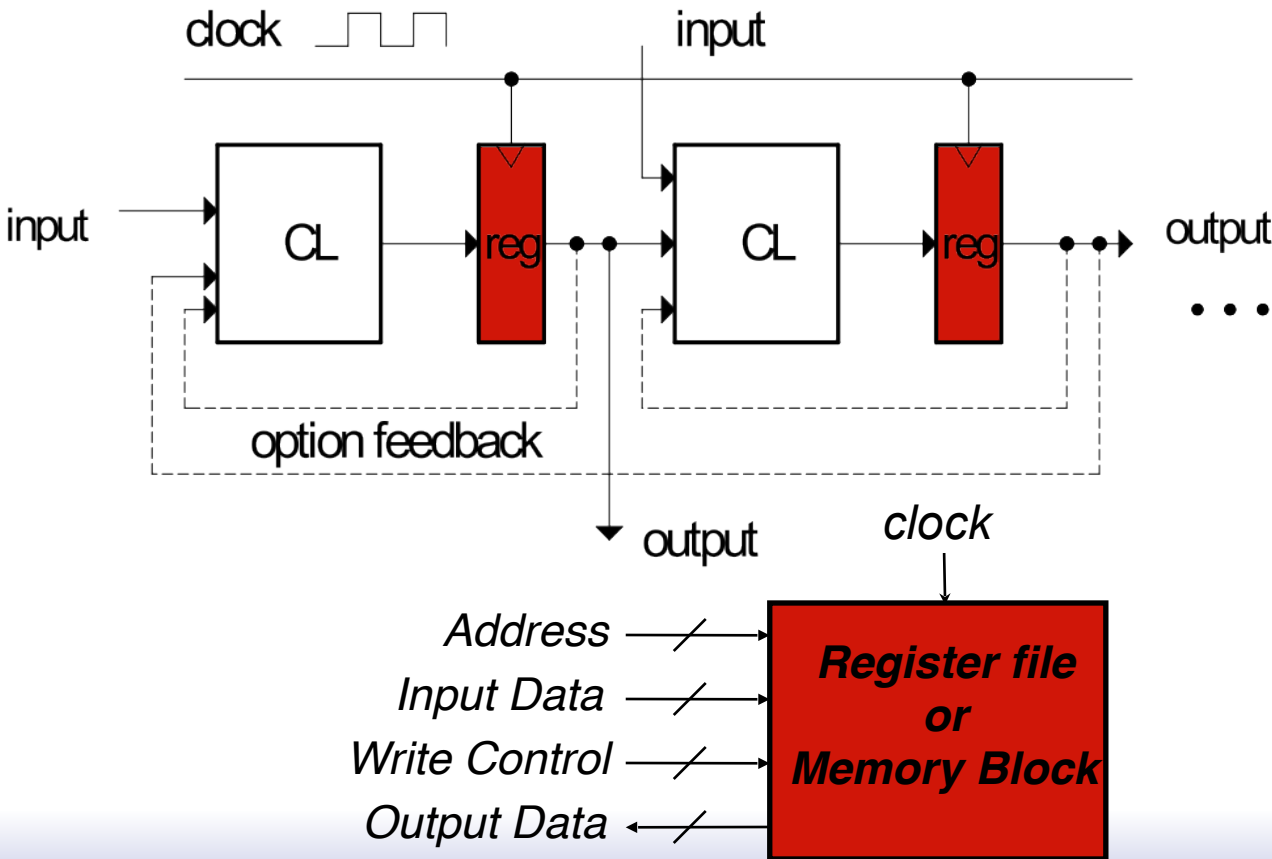
- ❑ Combinational Logic Blocks (CL)
- ❑ State Elements (registers)



- State elements are mixed in with CL blocks to control the flow of data.

- Sometimes used in large groups by themselves for "long-term" data storage.




Register Details...What's inside?

 

- ❑ n instances of a “Flip-Flop”
- ❑ Flip-flop name because the output flips and flops between 0 and 1
- ❑ D is “data”, Q is “output”
- ❑ Also called “d-type Flip-Flop”


Flip-flop Timing Waveforms

   - Edge-triggered d-type flip-flop
 - This one is “positive edge-triggered”
- “On the rising edge of the clock, the input d is sampled and transferred to the output. At all other times, the input d is ignored.”
- Example waveforms:




Accumulator Example

 Assume X is a vector of N integers, presented to the input of our accumulator circuit one at a time (one per clock cycle), so that after N clock cycles, S hold the sum of all N numbers.




$S=0$; Repeat N times
 $S = S + X$;

- We need something like this:

 


- *But not quite.*
- *Need to use the clock signal to hold up the feedback to match up with the input signal.*

Accumulator


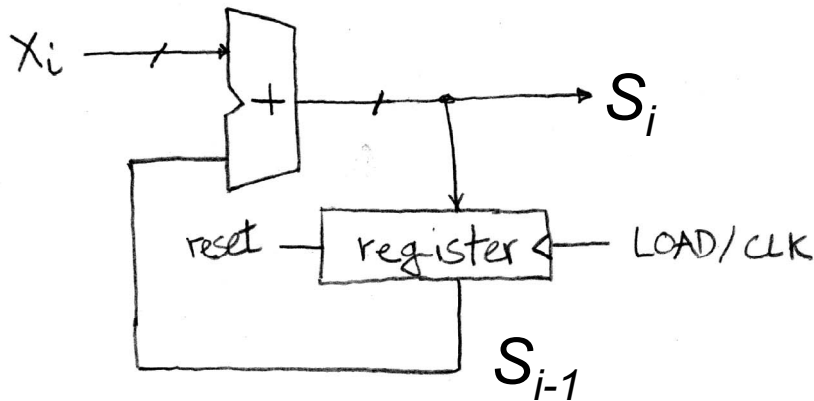


- ❑ Put register in feedback path.
- ❑ On each clock cycle the register prevents the new value from reaching the input to the adder prematurely. (The new value just waits at the input of the register)

Timing:

 


Flip-Flop Timing Details

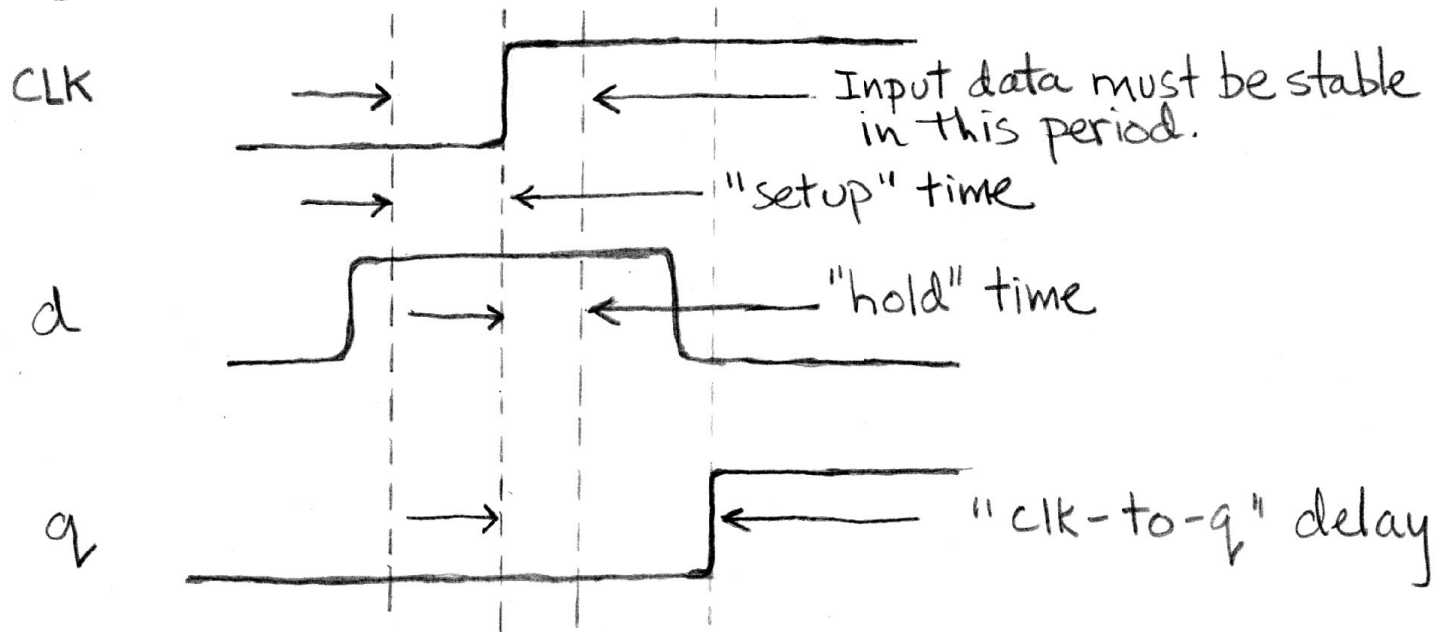 

Three important times associated with flip-flops:

- Setup time - *How long d must be stable before the rising edge of CLK*
- Hold time - *How long D must be stable after the rising edge of CLK*
- Clock-to-q delay – *Propagation delay after rising edge of the CLK*


Accumulator Revisited

 

□ Note:



- Reset signal (synchronous)
- Timing of X signal is not known without investigating the circuit that supplies X. Here we assume it comes just after S_{i-1} .

Observe transient behavior of S_i .

 


Level-sensitive Latch Inside Flip-flop

Positive Level-sensitive latch:

  

When CLK is high, latch is transparent, when clk is low, latch retains previous value.

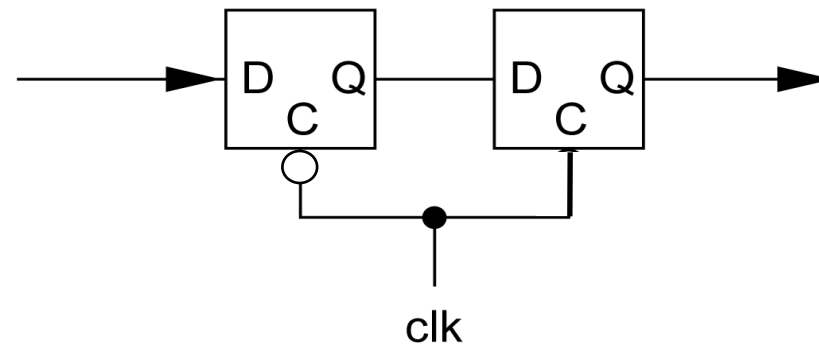Positive Edge-triggered flip-flop built from two level-sensitive latches:





Sequential Elements in Verilog

State Elements in Verilog

Always blocks are the only way to specify the “behavior” of state elements. Synthesis tools will turn state element behaviors into state element instances.

D-flip-flop with synchronous set and reset example:

```
module dff(q, d, clk, set, rst);  
  input d, clk, set, rst;  
  output q;  
  reg q;
```


```
  always @(posedge clk)  
    if (rst)  
      q <= 1'b0;  
    else if (set)  
      q <= 1'b1;  
    else  
      q <= d;  
endmodule
```

keyword

“always @(posedge clk)” is key to flip-flop generation.

This gives priority to reset over set and set over d.


On FPGAs, maps to native flip-flop.

 

The Sequential always Block


Combinational
 
```
module comb(input a, b, sel,  
            output reg out);  
    always @(*) begin  
        if (sel) out = b;  
        else out = a;  
    end  
endmodule
```



Sequential
 
```
module seq(input a, b, sel, clk,  
            output reg out);  
    always @(posedge clk) begin  
        if (sel) out <= b;  
        else out <= a;  
    end  
endmodule
```



Latches vs. Flip-Flops

Flip-Flop

Latch



```
module flipflop  
(  
  input clk,  
  input d,  
  output reg q  
);
```

```
  always @(posedge clk)  
  begin  
    q <= d;  
  end  
endmodule
```



```
module latch  
(  
  input clk,  
  input d,  
  output reg q  
);
```
  
```
  always @(clk or d)  
  begin  
    if ( clk )  
      q <= d;  
  end  
endmodule
```



Importance of the Sensitivity List

- ❑ The use of `posedge` and `negedge` makes an `always` block sequential (edge-triggered)
- ❑ Unlike a combinational `always` block, the sensitivity list **does** determine behavior for synthesis!

D-Register with *synchronous* clear

```
module dff_sync_clear(  
  input d, clearb, clock,  
  output reg q);  
  
  always @(posedge clock)  
  begin  
    if (!clearb) q <= 1'b0;  
    else q <= d;  
  end  
endmodule
```

`always` block entered only at
each positive clock edge

D-Register with *asynchronous* clear

```
module dff_async_clear(  
  input d, clearb, clock,  
  output reg q);  
  
  always @(negedge clearb or posedge clock)  
  begin  
    if (!clearb) q <= 1'b0;  
    else q <= d;  
  end  
endmodule
```

`always` block entered immediately when
(active-low) `clearb` is asserted

Note: The following is incorrect syntax: `always @(clear or negedge clock)`

If one signal in the sensitivity list uses `posedge/negedge`, then all signals must.

- Assign any signal or variable from only one `always` block.
Be wary of race conditions: `always` blocks with same trigger execute concurrently...

Blocking vs. Nonblocking Assignments

- ❑ Verilog supports two types of assignments within **always** blocks, with subtly different behaviors.
- ❑ *Blocking assignment (=)*: evaluation and assignment are immediate

```
always @(*) begin
  x = a | b;    // 1. evaluate alb, assign result to x
  y = a ^ b ^ c; // 2. evaluate a^b^c, assign result to y
  z = b & ~c;   // 3. evaluate b&(~c), assign result to z
end
```


- ❑ *Nonblocking assignment (<=)*: all assignments deferred to end of simulation time step after all right-hand sides have been evaluated (*even those in other active always blocks*)

```
always @(*) begin
  x <= a | b;    // 1. evaluate alb, but defer assignment to x
  y <= a ^ b ^ c; // 2. evaluate a^b^c, but defer assignment to y
  z <= b & ~c;   // 3. evaluate b&(~c), but defer assignment to z
  // 4. end of time step: assign new values to x, y and z
end
```

Sometimes, as above, both produce the same result. **Sometimes, not!**

Assignment Styles for Sequential Logic

 What we want:
Register Based
Digital Delay
Line



Will nonblocking and blocking assignments both produce the desired result?

```
module nonblocking(  
  input in, clk,  
  output reg out  
);  
  reg q1, q2;  
  always @(posedge clk) begin  
    q1 <= in;  
    q2 <= q1;  
    out <= q2;  
  end  
endmodule
```

```
module blocking(  
  input in, clk,  
  output reg out  
);  
  reg q1, q2;  
  always @(posedge clk) begin  
    q1 = in;  
    q2 = q1;  
    out = q2;  
  end  
endmodule
```

Use Nonblocking for Sequential Logic

```
always @(posedge clk) begin
  q1 <= in;
  q2 <= q1; // uses old q1
  out <= q2; // uses old q2
end
```

```
always @(posedge clk) begin
  q1 = in;
  q2 = q1; // uses new q1
  out = q2; // uses new q2
end
```

("old" means value before clock edge, "new" means the value after most recent assignment)



"At each rising clock edge, q1, q2, and out **simultaneously receive the old values** of in, q1, and q2."

"At each rising clock edge, q1 = in.

After that, q2 = q1.


After that, out = q2.

Therefore out = in."

  


- ❑ Blocking assignments **do not** reflect the intrinsic behavior of multi-stage sequential logic
- ❑ Guideline: use **nonblocking** assignments for sequential always blocks

Example: A Simple Counter

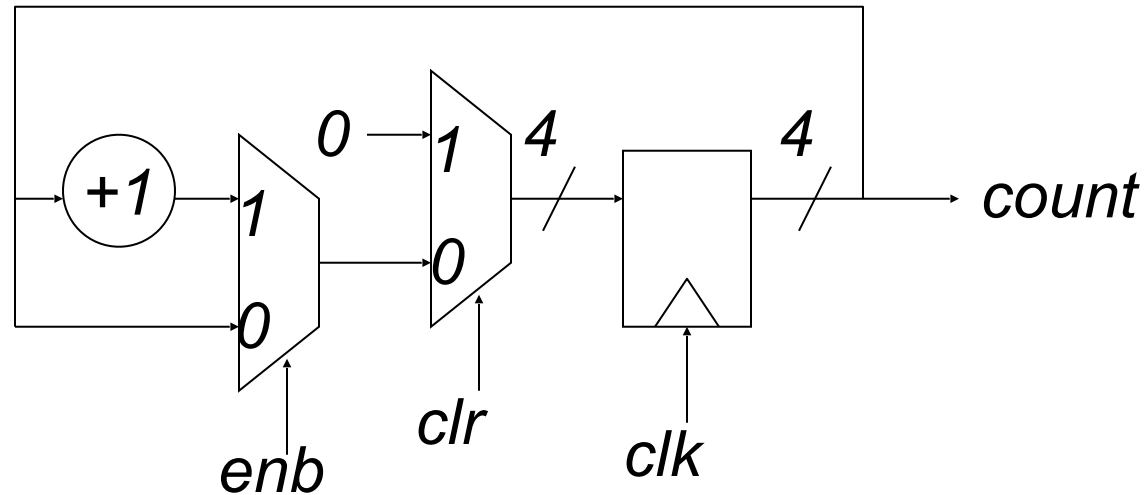

```
// 4-bit counter with enable and synchronous clear  
module counter(input clk,enb,clr,  
               output reg [3:0] count);  
  always @(posedge clk) begin  
    count <= clr ? 4'b0 : (enb ? count+1 : count);  
  end  
endmodule
```

Example - Parallel to Serial Converter

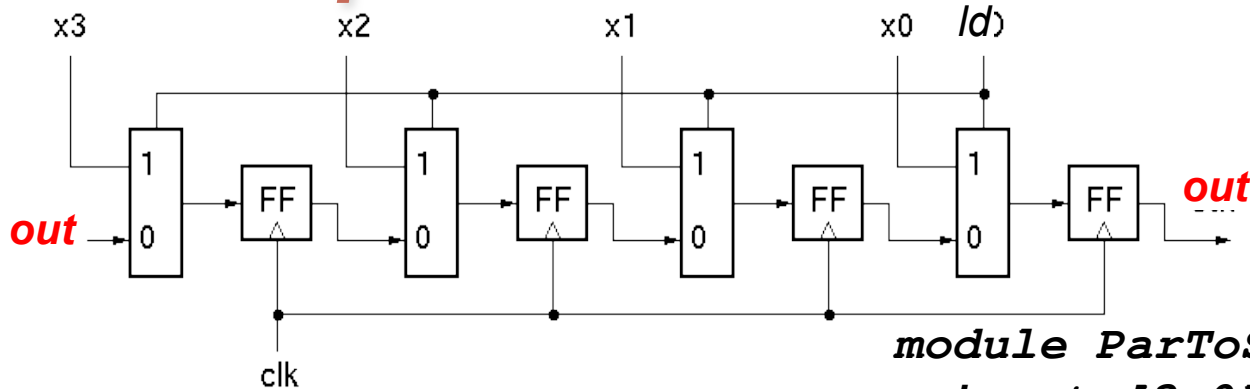

```
module ParToSer(ld, X, out, clk);  
  input [3:0] X;  
  input ld, clk;  
  output out;
```

```
  reg [3:0] Q;  
  wire [3:0] NS;
```

```
  assign NS =  
    (ld) ? X : {Q[0], Q[3:1]};
```

```
  always @ (posedge clk)  
    Q <= NS;
```

```
  assign out = Q[0];  
endmodule
```

Specifies the muxing with "rotation"

forces Q register (flip-flops) to be rewritten every cycle

connect output