



**EECS 151/251A**  
**Spring 2018**  
**Digital Design and**  
**Integrated Circuits**

Instructors:  
Nick Weaver & John Wawrzynek

**Lecture 9**


# Administration

- ❑ First Midterm Thursday
  
- ❑ *Decided on closed book (sorry), but will give you extra time. We will make an exam that is expected to take 90 minutes, but will give you 3 hours.*
  - 5-8PM
  - 405 Soda
  - Material: Everything up to slide 35 of Thursdays lecture (Lecture 8) – that is, CMOS logic is included.



**Previous Lecture**

# Static Complementary CMOS

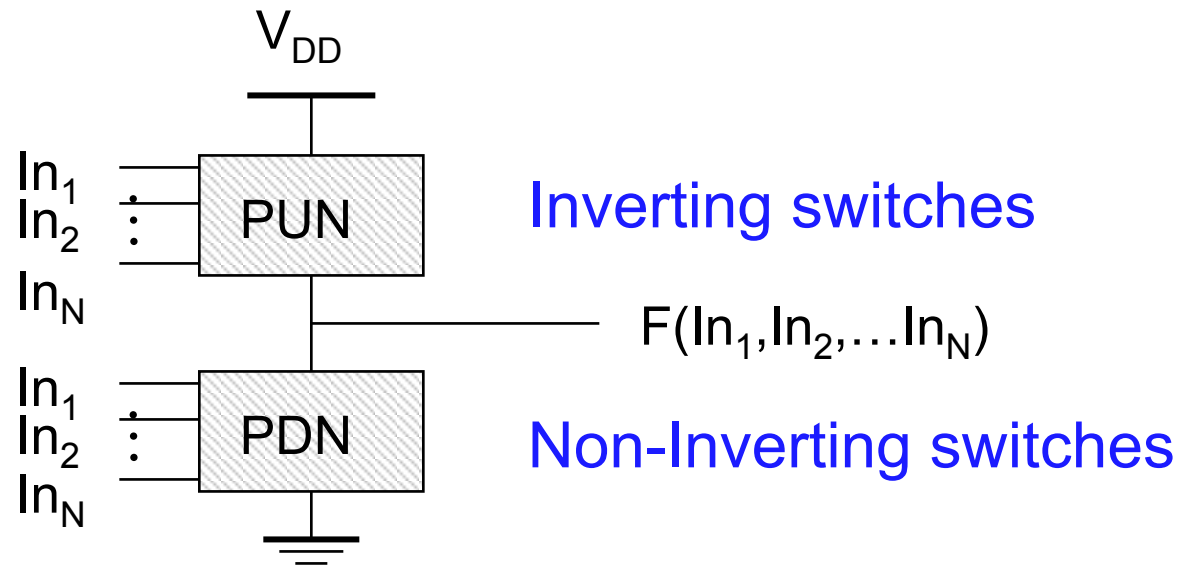


PUN and PDN are **dual** logic networks  
PUN and PDN functions are **complementary**

- ❑ Full rail-to-rail swing
- ❑ Symmetrical VTC
- ❑ No (...) static power dissipation
- ❑ Direct path current during switching
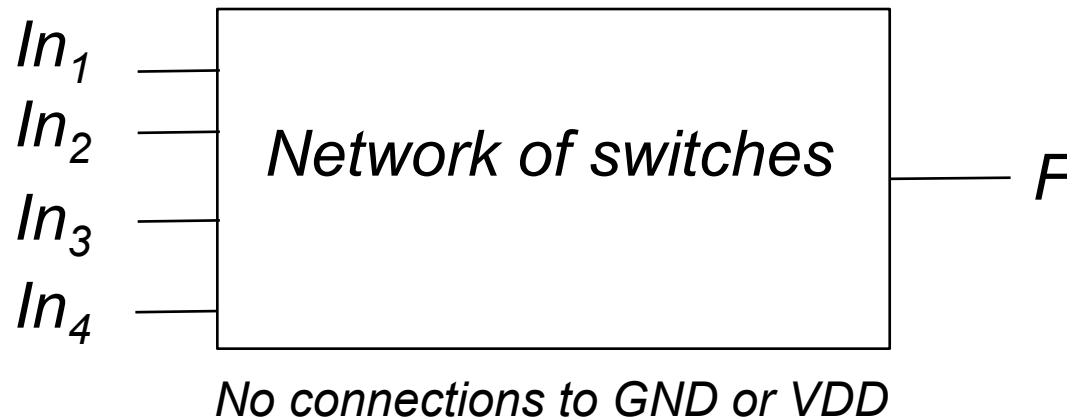
# Switch (Transmission Gate Logic)


Static:

Output always defined by GND or VDD, never both



# Tri-state Buffers


Tri-state Buffer:

 

OE	IN	OUT
0	0	Z
0	1	Z
1	0	0
1	1	1


“high impedance” (output disconnected)

Variations:

 



OE	IN	OUT
0	-	Z
1	0	1
1	1	0

Inverting buffer

 

OE	IN	OUT
0	0	0
0	1	1
1	-	Z


Inverted enable

  


transmission gate useful in implementation
 
# Tri-state Buffers

Tri-state buffers enable "bidirectional" connections.




 Tri-state buffers are used when multiple circuits all connect to a common wire. Only one circuit at a time is allowed to drive the bus. All others "disconnect" their outputs, but can "listen".




# Tri-state Based Multiplexor



Multiplexor

 

 Transistor Circuit for inverting multiplexor:





If  $s=1$  then  $c=a$

  




# Latches and Flip-flops


Positive Level-sensitive *latch*:

  

 Positive Edge-triggered **flip-flop**  
built from two level-sensitive  
latches:



Latch Implementation:

 




**Digital abstraction**

# Noise and Digital Systems

- ❑ Circuit needs to work despite “analog” noise
  - Digital gates can and must reject noise
  - This is actually how digital systems are defined
  
- ❑ Digital system is one where:
  - Discrete values mapped to analog levels and back
  - Elements (gates) can reject noise
    - For “small” amounts of noise, output noise is less than input noise
  - Thus, for sufficiently “small” noise, the system acts as if it was noiseless
  - This is called **regeneration**
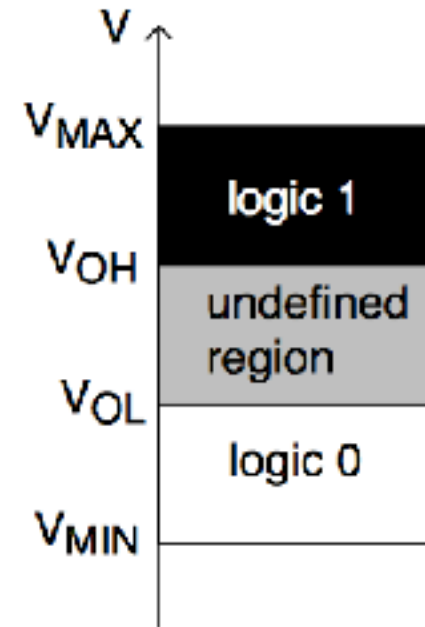
# Bridging the digital and the analog worlds

- How to represent 0's and 1's in a world that is analog?




## The Static Definition

- **Logic 0:**  $V_{MIN} \leq V \leq V_{OL}$
- **Logic 1:**  $V_{OH} \leq V \leq V_{MAX}$
- **Undefined logic value:**  $V_{OL} \leq V \leq V_{OH}$


 
# Ideal Inverter

Circuit representation and ideal transfer function:





Define *switching point* or *logic threshold* :

- $V_M \equiv$  input voltage for which  $V_{OUT} = V_{IN}$ 
  - For  $0 \leq V_{IN} < V_M \Rightarrow V_{OUT} = V^+$
  - For  $V_M < V_{IN} \leq V^+ \Rightarrow V_{OUT} = 0$

Ideal inverter returns well defined logical outputs (0 or  $V^+$ ) even in the presence of considerable noise in  $V_{IN}$  (from voltage spikes, crosstalk, etc.)



$\Rightarrow$  signal is *regenerated*!

# “Real Inverter”

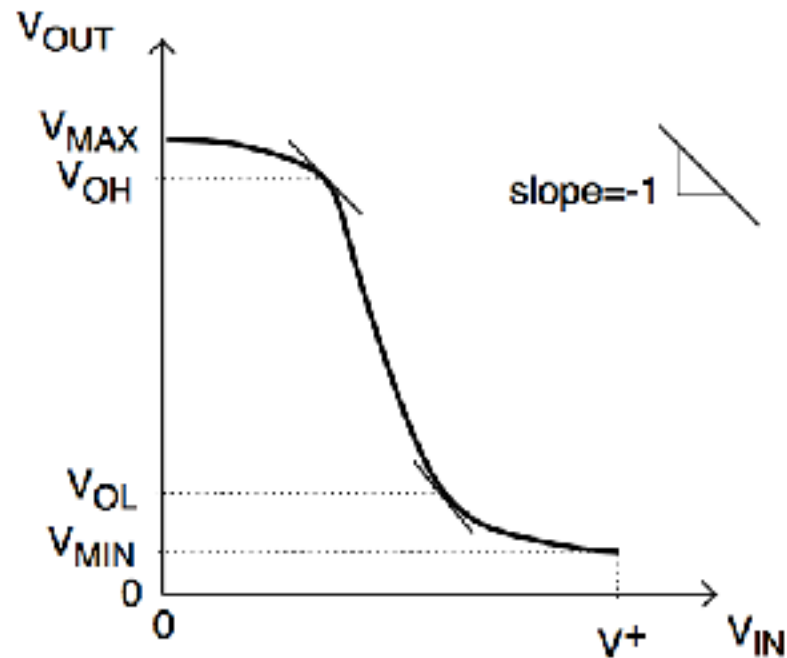 

- Logic 0:
  - $V_{MIN}$   $\equiv$  output voltage for which  $V_{IN} = V^+$
  - $V_{OL}$   $\equiv$  smallest output voltage where slope = -1
- Logic 1:
  - $V_{OH}$   $\equiv$  largest output voltage where slope = -1
  - $V_{MAX}$   $\equiv$  output voltage for which  $V_{IN} = 0$



# Valid Input Ranges

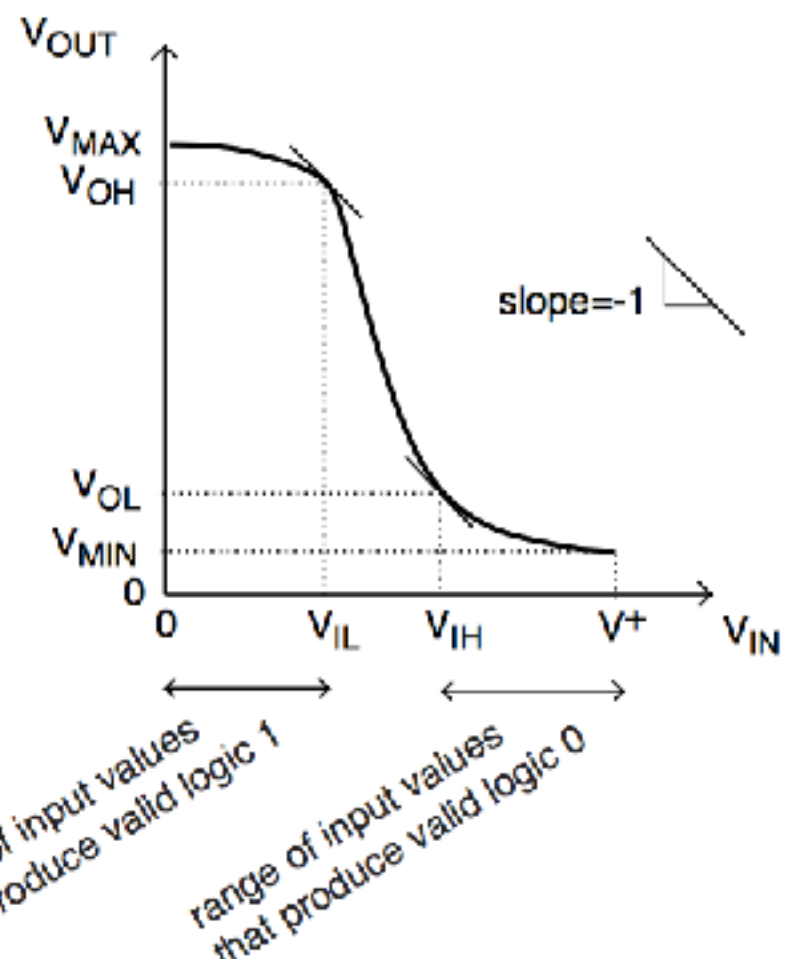 

If range of output values  $V_{OL}$  to  $V_{OH}$  is *wider* than the range of input values  $V_{IL}$  to  $V_{IH}$ , then the inverter exhibits some noise immunity. (Voltage gain  $> 1$ )

Quantify this through *noise margins*.

# Definition of Noise Margins

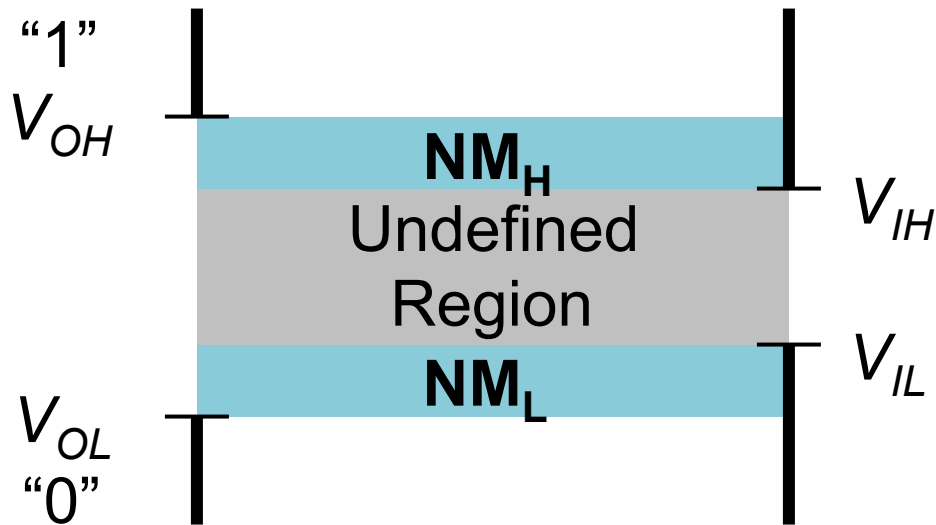 

Noise margin high:  
 $NM_H = V_{OH} - V_{IH}$

Noise margin low:  
 $NM_L = V_{IL} - V_{OL}$


Gate  
Output  
(Stage M)



Gate  
Input  
(Stage M+1)



# Simulated Inverter VTC (Spice)

 

$V_{OH} =$

$V_{OL} =$

$V_{IL} =$

$V_{IH} =$

$N_{MH} =$



$N_{ML} =$

$V_M =$




**Transient properties**

# The Switch – Dynamic Model

  

 
# The Switch – Dynamic Model (Simplified)




# The Switch Inverter: Transient Response

$$V(t) = V_0 e^{-t/RC}$$

$$t_{1/2} = \ln(2) \times RC$$

 

(a) Low-to-high

 


(b) High-to-low

$$t_{pHL} = f(R_{on} C_L) \\ = 0.69 R_n C_L$$

 
# Switch Sizing

What happens if we make a switch  $W$  times larger (wider)




# Switch Parasitic Model

The pull-down switch (NMOS)

 

Minimum-size switch

 

Sizing the transistor (factor  $W$ )

*We assume transistors of minimal length (or at least constant length).  $R$ 's and  $C$ 's in units of per unit width.*

# *PMOS Sizing*


The PMOS challenge:

For the same voltages, it provides less current (approximately 2 times less)




# Switch Parasitic Model


## The pull-up switch (PMOS)

 

Minimum-size switch

 


Sized for symmetry

 

General sizing

# Inverter Parasitic Model

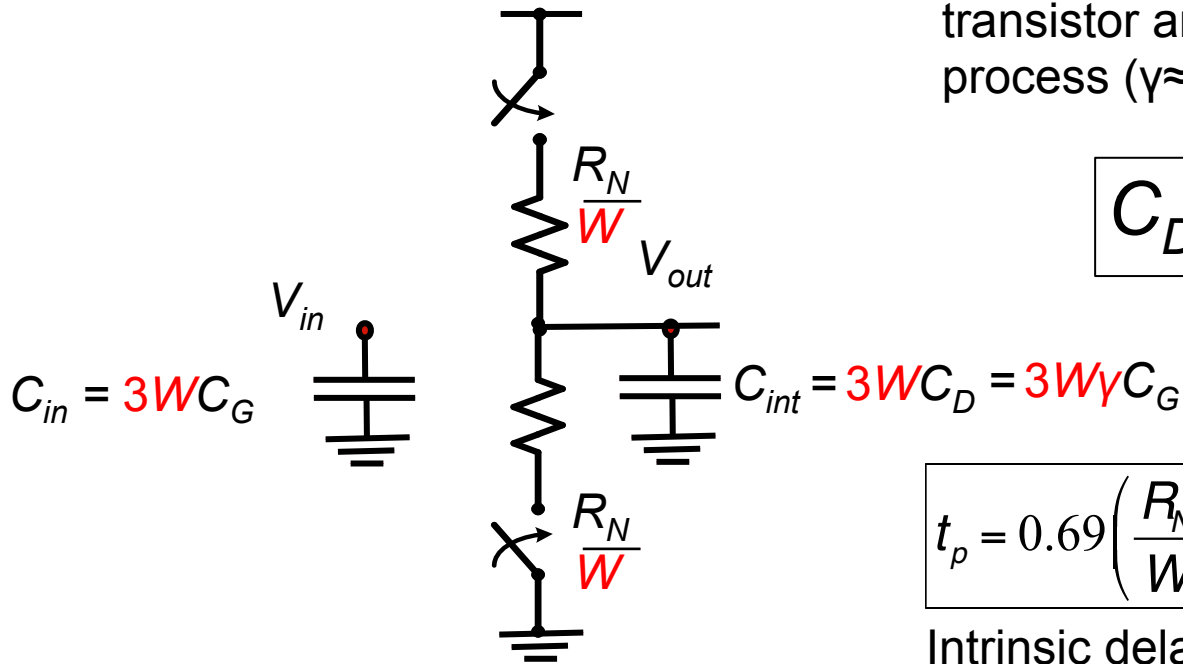


Drain and gate capacitance of transistor are **directly** related by process ( $\gamma \approx 1$ )

$$C_D = \gamma C_G$$

$$t_p = 0.69 \left( \frac{R_N}{W} \right) (3W\gamma C_G) = 0.69(3\gamma) R_N C_G$$

Intrinsic delay of inverter  
**independent of size**

# Inverter with Load Capacitance

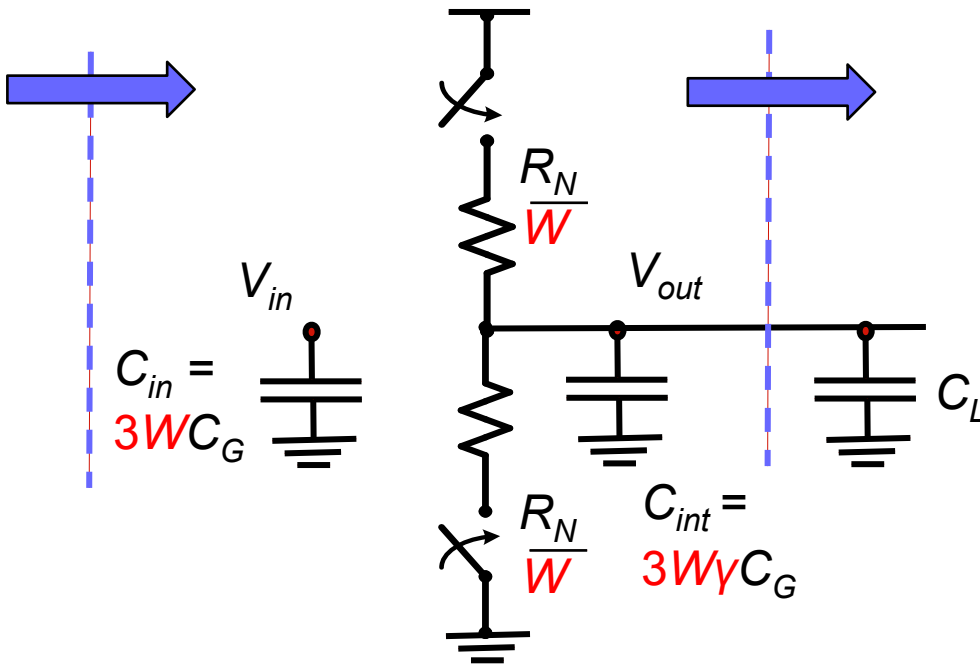

$$\begin{aligned}
 t_p &= 0.69 \left( \frac{R_N}{W} \right) (C_{int} + C_L) \\
 &= 0.69 \left( \frac{R_N}{W} \right) (3W\gamma C_G + C_L) \\
 &= 0.69 (3C_G R_N) \left( \gamma + \frac{C_L}{C_{in}} \right) \\
 &= t_{inv} \left( \gamma + \frac{C_L}{C_{in}} \right) = t_0 (\gamma + f)
 \end{aligned}$$


$f$  = fanout = ratio between load and input capacitance of gate

# Inverter Delay Model

$$t_p = t_{inv}(\gamma + f)$$

$t_{inv}$  technology constant

 - Can be dropped from expression
- Delay unit-less variable (expressed in unit delays)




Question: how does transistor sizing ( $W$ ) impact delay?



## Inverter Delay Optimization


# Inverter Chain

 

- ❑ For some given  $C_L$ :
  - How many stages are needed to minimize delay?
  - How to size the inverters?
- ❑ Anyone want to guess the solution?
 
# Careful about Optimization Problems

- Get fastest delay if build one **very** big inverter
  - So big that delay is set only by self-loading



- Likely not the problem you're interested in
  - Someone has to drive this inverter...

# *Engineering Optimization Problems in General*


- ❑ Need to have a set of constraints
- ❑ Constraints key to:
  - Making the result useful
  - Making the problem have a 'clean' solution
- ❑ For sizing problem:
  - Need to constrain size of first inverter



# *Delay Optimization Problem #1*

- You are given:
  - A fixed number of inverters
  - The size of the first inverter
  - The size of the load that needs to be driven
- Your goal:
  - Minimize the delay of the inverter chain
- Need model for inverter delay vs. size

# Apply to Inverter Chain

 

$$t_p = t_{p1} + t_{p2} + \dots + t_{pN}$$

$$t_{pj} = t_{inv} \left( \gamma + \frac{C_{in,j+1}}{C_{in,j}} \right)$$

$$t_p = \sum_{j=1}^N t_{p,j} = t_{inv} \sum_{i=1}^N \left( \gamma + \frac{C_{in,j+1}}{C_{in,j}} \right), \quad C_{in,N+1} = C_L$$

# Optimal Sizing for Given N

- Delay equation has  $N-1$  unknowns,  $C_{in,2} \dots C_{in,N}$
- **To minimize the delay**, find  $N-1$  partial derivatives:

$$t_p = \dots + t_{inv} \frac{C_{in,j}}{C_{in,j-1}} + t_{inv} \frac{C_{in,j+1}}{C_{in,j}} + \dots$$
$$\frac{dt_p}{dC_{in,j}} = t_{inv} \frac{1}{C_{in,j-1}} - t_{inv} \frac{C_{in,j+1}}{C_{in,j}^2} = 0$$

# Optimal Sizing for Given N (cont'd)

- Result: every stage has equal fanout (f):

$$\frac{C_{in,j}}{C_{in,j-1}} = \frac{C_{in,j+1}}{C_{in,j}}$$

- Size of each stage is geometric mean of two neighbors:

$$C_{in,j} = \sqrt{C_{in,j-1} C_{in,j+1}}$$

- Equal fanout  $\rightarrow$  every stage will have same delay

# Optimum Delay and Number of Stages

- When each stage has same fanout  $f$ :

$$f^N = F = C_L / C_{in,1}$$


- Fanout of each stage:

$$f = \sqrt[N]{F}$$

- Minimum path delay:

$$t_p = Nt_{inv} \left( \gamma + \sqrt[N]{F} \right)$$

# Example

 

$C_L/C_1$  has to be evenly distributed across  $N = 3$  stages:

# Delay Optimization Problem #2

- You are given:
  - The size of the first inverter
  - The size of the load that needs to be driven
- Your goal:
  - Minimize delay by finding optimal number and sizes of gates
- So, need to find  $N$  that minimizes:

$$t_p = Nt_{inv} \left( \gamma + \sqrt[N]{C_L / C_{in}} \right)$$

# Untangling the Optimization Problem

- Rewrite  $N$  in terms of fanout/stage  $f$ :

$$f^N = C_L / C_{in} \rightarrow N = \frac{\ln(C_L / C_{in})}{\ln f}$$

$$t_p = N t_{inv} \left( (C_L / C_{in})^{1/N} + \gamma \right) = t_{inv} \ln(C_L / C_{in}) \left( \frac{f + \gamma}{\ln f} \right)$$

$$\frac{\partial t_p}{\partial f} = t_{inv} \ln(C_L / C_{in}) \cdot \frac{\ln f - 1 - \gamma / f}{\ln^2 f} = 0$$

$$f = \exp(1 + \gamma / f) \quad (\text{no explicit solution})$$


For  $\gamma = 0$ ,  $f = e$ ,  $N = \ln(C_L / C_{in})$




# Optimum Effective Fanout $f$

- Optimum  $f$  for given process defined by  $\gamma$

$$f = \exp(1 + \gamma / f)$$

 

# In Practice: Plot of Total Delay

 

[Hodges, p.281]

- Why the shape?
- Curves very flat for  $f > 2$ 
  - Simplest/most common choice:  $f = 4$

# Normalized Delay As a Function of F


$$t_p = Nt_{inv} \left( \gamma + \sqrt[N]{F} \right), F = C_L / C_{in}$$


<i>F</i>	Unbuffered	Two Stage	Inverter Chain
10	11	8.3	8.3
100	101	22	16.5
1000	1001	65	24.8
10,000	10,001	202	33.1

**( $\gamma = 1$ )**

[Rabaey: page 210]

# Buffer Design


 


 

**Logical Effort**

 
 
# Question #1

- How to best combine logic and drive for a big capacitive load?


  
# Question #2

- All of these are “decoders”
  - Which one is “best”?



## *Method to answer both of these questions*

- ❑ Extension of buffer sizing problem
- ❑ Logical effort




# *Complex Gate Sizing*

# Complex Gate Sizing: NAND-2 Example

$$C_{gnand} = 4C_G = (4/3) C_{ginv}$$

$$C_{dnand} = 6C_D = 6\gamma C_G = 2\gamma C_{ginv}$$
 
$$f = C_L/C_{gnand} = (3/4) C_L/C_{ginv}$$



$$\begin{aligned} t_{pNAND} &= kR_N(C_{dnand} + C_L) \\ &= kR_N(2\gamma C_{ginv} + C_L) \\ &= kR_N C_{ginv} (2\gamma + C_L/C_{ginv}) \\ &= t_{inv} (2\gamma + (4/3)f) \end{aligned}$$

# Logical Effort

- ❑ Defines ease of gate to drive external capacitance
- ❑ Inverter has the smallest logical effort and intrinsic delay of all static CMOS gates
- ❑ Logical effort LE is defined as:
  - $(R_{eq,gate} C_{in,gate}) / (R_{eq,inv} C_{in,inv})$
  - Easiest way to calculate (usually):
    - Size gate to deliver same current as an inverter, take ratio of gate input capacitance to inverter capacitance
- ❑ LE increases with gate complexity

# Logical Effort

$$t_{pgate} = t_{inv} (p + LEf)$$

Measure everything in units of  $t_{inv}$  (divide by  $t_{inv}$ ):

$p$  – intrinsic delay - gate parameter  $\neq f(W)$

$LE$  – logical effort – gate parameter  $\neq f(W)$

$f$  – electrical fanout =  $C_L/C_{in} = f(W)$

Normalize everything to an inverter:

$$LE_{inv} = 1, p_{inv} = \gamma$$

# Delay of a Logic Gate

Gate delay:

$$\text{Delay} = \text{EF} + p \quad (\text{measured in units of } t_{inv})$$

**effective fanout**      **intrinsic delay**


Effective fanout:

$$\text{EF} = \text{LE } f$$

**logical effort**      **electrical fanout** =  $C_L/C_{in}$


Logical effort is a function of topology, independent of sizing  
Effective fanout is a function of load/gate size

# Logical Effort of Gates

 

# Delay Of NOR-2 Gate

 1. Size for same resistance as inverter
2. LE = ratio of input cap of gate versus inverter



Intrinsic capacitance ( $C_{dnor}$ ) =  
 $t_{pint}(\text{NOR}) =$


# Question

Any logic function can be implemented using NOR gates only or NAND gates only!

Which of the two approaches is preferable in CMOS (from a performance perspective)?



# Logical Effort

 

Gate Type	Number of Inputs			
	1	2	3	n
Inverter	1			
NAND		$4/3$	$5/3$	$(n+2)/3$
NOR		$5/3$	$7/3$	$(2n+1)/3$
Multiplexer		2	2	2
XOR		4	12	

[From Sutherland, Sproull, Harris]



## Optimizing Complex Combinational Logic

# Multistage Networks

$$Delay = \sum_{i=1}^N (p_i + LE_i \cdot f_i)$$

Effective fanout:  $EF_i = LE_i f_i$

*Only for tree networks*


Path delay  $D = \sum d_i = \sum p_i + \sum EF_i$

Path electrical fanout:  $F = C_L / C_{in} = \prod f_i$

Path logical effort:  $\prod LE = LE_1 LE_2 \dots LE_N$

Path effort:  $PE = \prod LE F$

# Adding branching

 

Branching effort: 
$$b = \frac{C_{L,on-path} + C_{L,off-path}}{C_{L,on-path}}$$

# Multistage Networks

$$Delay = \sum_{i=1}^N (p_i + LE_i \cdot f_i)$$

Effective fanout:  $EF_i = LE_i f_i$

Path delay  $D = \sum d_i = \sum p_i + \sum EF_i$

Path electrical fanout:  $F = C_L / C_{in}$

Branching effort:  $\Pi B = b_1 b_2 \dots b_N$

$\Pi f_i = \Pi B F$  (assuming all paths in the tree are important)

Path logical effort:  $\Pi LE = LE_1 LE_2 \dots LE_N$

Path effort:  $PE = \Pi LE \Pi B F$

# Optimum Effort per Stage

When each stage bears the same effort (effective fanout):

$$EF^N = PE$$

$$EF = \sqrt[N]{PE}$$

Effective fanouts:  $LE_1f_1 = LE_2f_2 = \dots = LE_Nf_N$

Minimum path delay

$$\hat{D} = \sum_{i=1}^N (LE_i f_i + p_i) = N \cdot PE^{1/N} + \sum_{i=1}^N p_i$$

# Optimal Number of Stages

For a given load,

and given input capacitance of the first gate

Find optimal number of stages and optimal sizing

$$D = N \cdot PE^{1/N} + \sum p_i$$

*Remember: we can always add inverters to the end of the chain*

The 'best effective fanout'  $EF = PE^{1/\hat{N}}$  is still around 4  
(3.6 with  $\gamma=1$ )

# Method of Logical Effort: Summary

- Compute the path effort:  $PE = (\Pi LE)BF$
- Find the best number of stages  $N \sim \log_4 PE$
- Compute the effective fanout/stage  $EF = PE^{1/N}$
- Sketch the path with this number of stages
- Work either from either end, find sizes:  
 $C_{in} = C_{out} * LE/EF$


Reference: Sutherland, Sproull, Harris, "Logical Effort", Morgan-Kaufmann 1999.





## Optimizing Complex Combinational Logic: Examples

# Example 1: No branching

 

Electrical fanout,  $F =$

$\prod LE =$

$PE =$

$EF/\text{stage} =$


$a =$

$b =$

$c =$
 
# Example 1: No branching

*a, b, c are input capacitances normalized to the unit inverter*



Electrical fanout,  $F = 5$

$\Pi LE = 25/9$

$PE = 125/9$

$EF/stage = 1.93$

$a = 1.93$

$b = 2.23$

$c = 2.59$


From the back

$$5/c = 1.93$$

$$(5/3)c/b = 1.93$$

$$(5/3)b/a = 1.93$$

# Our old problem: which one is better?

 

$$LE=10/3 \quad 1$$

$$\prod LE = 10/3$$

$$P = 8 + 1$$

$$LE=2 \quad 5/3$$

$$\prod LE = 10/3$$


$$P = 4 + 2$$

$$LE=4/3 \quad 5/3 \quad 4/3 \quad 1$$

$$\prod LE = 80/27$$

$$P = 2 + 2 + 2 + 1$$

# Adding Branching

 

$$\begin{aligned}LE &= 1 \\F &= 90/5 = 18 \\PE &= 18 \text{ (wrong!)}\end{aligned}$$

---

$$\begin{aligned}EF_1 &= (15+15)/5 = 6 \\EF_2 &= 90/15 = 6 \\PE &= 36, \text{ not } 18!\end{aligned}$$

Better:  $PE = F \cdot LE \cdot B = 18 \cdot 1 \cdot 2 = 36$

# Example 2 with Branching

Select gate sizes  $y$  and  $z$  to minimize delay from  $A$  to  $B$

Logical Effort:  $LE =$

Electrical Fanout:  $F =$


Branching Effort:  $B =$

Path Effort:  $PE =$

---

Best Effective Fanout:  $EF =$

Delay:  $D =$

 

# Example 2 with Branching


Select gate sizes  $y$  and  $z$  to minimize delay from  $A$  to  $B$

Logical Effort:  $LE = (4/3)^3$

Electrical Fanout:  $F = C_{out}/C_{in} = 9$

Branching Effort:  $B = 2 \cdot 3 = 6$

 Path Effort:  $PE = \prod LE \cdot F \cdot B = 128$



Best Effective Fanout:  $EF = PE^{1/3} \approx 5$

Delay:  $D = 3 \cdot 5 + 3 \cdot 2 = 21$

Work backward for sizes:

$$z = \frac{9C \cdot (4/3)}{5} = 2.4C$$

$$y = \frac{3z \cdot (4/3)}{5} = 1.9C$$