

# EECS 151/251A

## Discussion 1

01/26/2018

# Hi

Arya Reais-Parsi  
aryap@berkeley.edu

- 1st year Berkeley PhD student
- From Iran, New Zealand and Australia (so far)
- Received BE in 2010 from Victoria University of Wellington (New Zealand)
- Worked for Google in Sydney for 6 years
- Super fun guy
  
- Questions? Comments? Feedback? Advice? A chat?  
aryap@berkeley.edu



# Happy Australia Day!

- Public holiday
- Actually controversial
- Here's 9 News using the wrong flag →



# Reminder

- Homework 1 due tonight at 11:59 pm
- Homework 2 posted, due next Friday at 11:59 pm
  
- Not too late to get help for homework 1


# Discussions

- Enrich class material
  - Provide some review
  - Cover additional examples
- Will feed off questions on Piazza
- Are here to help
- Will address topics you want to cover

# Agenda


- ASIC vs FPGA
- Verilog

# ASIC vs FPGA

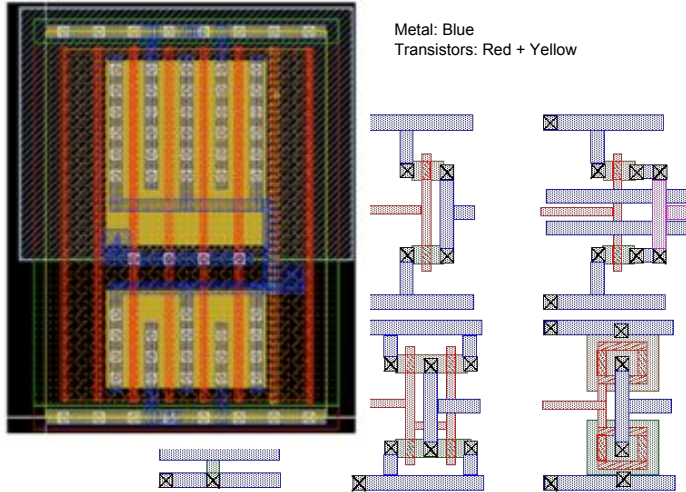

[http://ece-research.unm.edu/jimp/vlsil/labs/layout\\_lecture-1.gif](http://ece-research.unm.edu/jimp/vlsil/labs/layout_lecture-1.gif)

 Use standard cells, SRAM, custom analog circuits



Use LUTs, block RAM, on-die IP cores

# \$\$\$ Blockchain \$\$\$

Bitcoin mining platform progression

1. Software
2. GPU
3. FPGA
4. ASIC

Why?



<https://www.bitcoinmining.com/images/usb-bitcoin-miner-gekko-science.jpg>



# ASIC vs FPGA

Ali Moin

ASIC	FPGA
Use standard cells, SRAM, custom analog	Use LUTs, block RAM, on-die IP cores
Maximum performance ☹️	Lower performance ☹️
High design cost (NRE*) ☹️	Low design cost ☹️
Low per-unit cost ☹️	High per-unit cost ☹️
Year(s) to design and manufacture ☹️	Minutes to reprogram ☹️
Access to custom analog circuits ☹️	Restricted to whatever is on the FPGA ☹️
Jobs at chip companies and big tech players (Google, FB, Apple)	Wide range of jobs both in EE fields and outside

\*NRE: Non-Recurring Engineering cost

# Verilog

- One of several Hardware Design Languages (HDLs)
- Not a traditional programming language
- Have to learn mindset from scratch
  
- Don't think about it like a traditional programming language
- Stop thinking about it like a traditional programming language
- Stop it
- This isn't C/Java/Python/Ruby/JavaScript/...
- You're describing a circuit
  - not a sequence of instructions to execute

# Verilog


Two general ways of description:

1. Structural Verilog
  - Describe the schematic in text format
2. Behavioral Verilog
  - Describe the desired functionality
  - Two assignment types:
    - Continuous assignments (assign ...)
    - Non-continuous assignments (always @(...))

# Sequential Logic

 
## Combinational

```
module comb(input a, b, sel,  
            output reg out);  
    always @(*) begin  
        if (sel) out = b;  
        else out = a;  
    end  
endmodule
```


 
## Sequential

```
module seq(input a, b, sel, clk,  
           output reg out);  
    always @(posedge clk) begin  
        if (sel) out <= b;  
        else out <= a;  
    end  
endmodule
```



*event driven*



# Blocking vs. non-blocking assignment



Blocking (=): evaluation and assignment are immediate; sequence matters. *Value of expressions at that point in the description matters.*

```
always @(*) begin
  x = a | b;    // 1. evaluate a|b, assign result to x
  y = a ^ b ^ c; // 2. evaluate a^b^c, assign result to y
  z = b & ~c;   // 3. evaluate b&(~c), assign result to z
end
```

Non-blocking (<=): all assignments deferred to end of simulation time step after all right-hand expressions have been evaluated.

```
always @(*) begin
  x <= a | b;    // 1. evaluate a|b, but defer assignment to x
  y <= a ^ b ^ c; // 2. evaluate a^b^c, but defer assignment to y
  z <= b & ~c;   // 3. evaluate b&(~c), but defer assignment to z
  // 4. end of time step: assign new values to x, y and z
end
```

# Blocking vs. non-blocking example

  

```
module nonblocking(  
  input in, clk,  
  output reg out  
);  
  reg q1, q2;  
  always @(posedge clk) begin  
    q1 <= in;  
    q2 <= q1;  
    out <= q2;  
  end  
endmodule
```

```
module blocking(  
  input in, clk,  
  output reg out  
);  
  reg q1, q2;  
  always @(posedge clk) begin  
    q1 = in;  
    q2 = q1;  
    out = q2;  
  end  
endmodule
```

**Guideline: use non-blocking assignments for sequential always blocks**

# References

- Ali Moin, EECS 151 Spring 2017 Discussion 1