

# EECS 151/251A

## Discussion 3

02/09/2018

# Agenda

- Announcements
- FSM
- Karnaugh Maps
- CMOS logic

# Announcements

- Midterm next Thursday
  - 3 hour exam (though we don't expect you'll need the entire time)
  - In the lecture slot next Thursday with extra time; 5 pm - 8 pm
  - Closed book, but you are allowed one hand-written two-sided cheat sheet (8.5x11 inch)
  - Location to-be-decided
- I'll be away for two weeks
  - Only an email away. Or an SMS. Or Piazza. Or Skype. It's 2018, c'mon
  - Taehwan will attend Thursday FPGA labs
  - No one will staff Wednesday labs; I can be available in real-time on Slack
  - FPGA labs 3, 4 and 5 will be not need to be checked off until Friday, 2 March
  - Discussions will be moved temporarily so Taehwan can staff 'em
    - This is the last one before your first midterm

# Warmup

1. Use blocking assignments to model combinational logic within an always block ( “=”). Why?
2. Use non-blocking assignments to implement sequential logic (“<=”). Why?
3. Do not mix blocking and non-blocking assignments in the same always block.
4. Do not make assignments to the same variable from more than one always block.

Be rigorous and disciplined to minimise unexpected results!

# Finite State Machines

Moore vs Mealy?

Traffic lights!

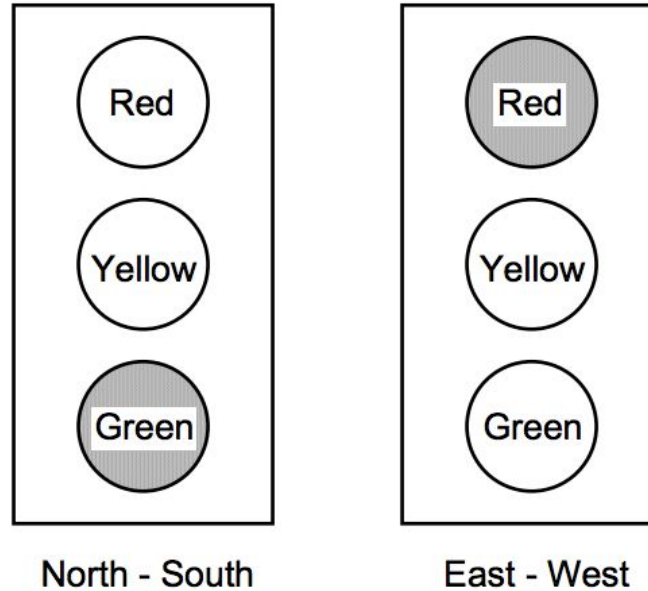


Figure 8.13 Six colored LEDs can represent a set of traffic lights

# Traffic Light FSM

**Table 8.2 Traffic Light States**

State	North - South	East - West	Delay (sec.)
0	Green	Red	5
1	Yellow	Red	1
2	Red	Red	1
3	Red	Green	5
4	Red	Yellow	1
5	Red	Red	1

# Traffic Light FSM

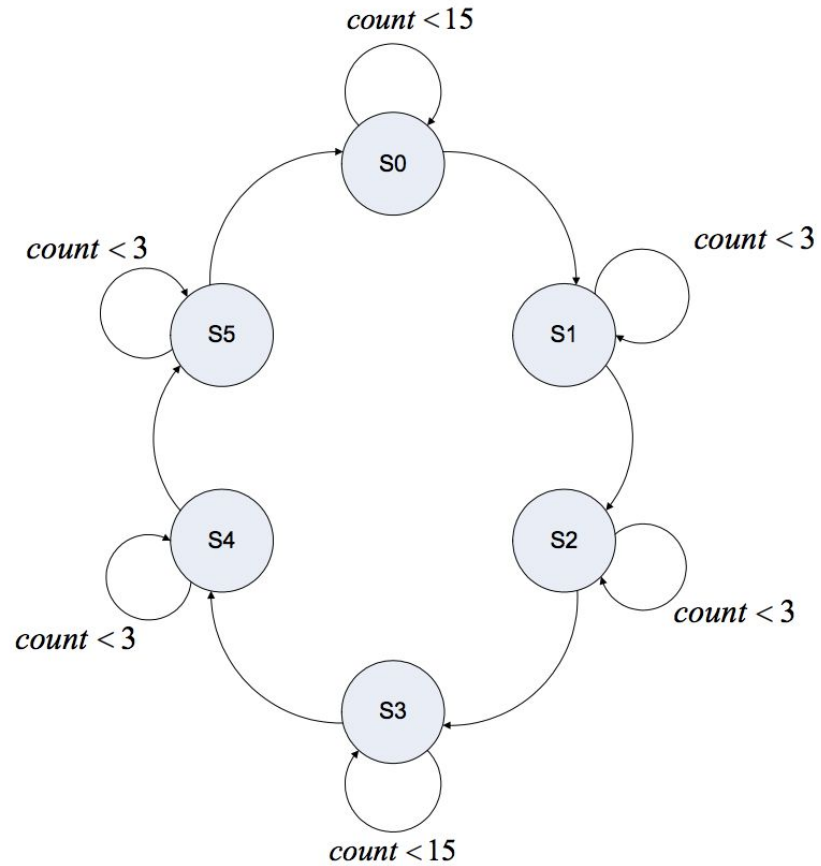


Figure 8.14 State diagram for controlling traffic lights

# FSM design steps

- ~~1. Specify/convince yourself of circuit function (natural language, e.g. English)~~
- ~~2. Draw state transition diagram~~
- ~~3. Write down symbolic state transition table [kind of]~~
4. Assign encodings (bit patterns) to symbolic states
5. Code as Verilog behavioral description.. (Or just skip from 1 to 4+5...)



## Listing 8.6 traffic.v

```
// Example 62a: traffic lights
module traffic (
input wire clk ,
input wire clr ,
output reg [5:0] lights
);
reg[2:0] state;
reg[3:0] count;

parameter S0 = 3'b000, S1 = 3'b001, S2 = 3'b010, // states
           S3 = 3'b011, S4 = 3'b100, S5 = 3'b101;
parameter SEC5 = 4'b1111, SEC1 = 4'b0011;      // delays

always @(posedge clk or posedge clr)
begin
    if (clr == 1)
        begin
            state <= S0;
            count <= 0;
        end
    else
        case (state)
```

```
always @(posedge clk or posedge clr)
```

```
begin
```

```
if (clr == 1)
```

```
begin
```

```
state <= S
```

```
count <= 0
```

```
end
```

```
else
```

```
case (state)
```

```
case (state)
```

```
S0: if (count < SEC5)
```

```
begin
```

```
state <= S0;
```

```
count <= count + 1;
```

```
end
```

```
else
```

```
begin
```

```
state <= S1;
```

```
count <= 0;
```

```
end
```

```
S1: if (count < SEC1)
```

```
begin
```

```
state <= S1;
```

```
count <= count + 1;
```

```
end
```

```
else
```

```
begin
```

```
state <= S2;
```

```
count <= 0;
```

```
end
```

```
S2: if (count < SEC1)
```

```
begin
```

```
state <= S2;
```

```
count <= count + 1;
```

```
end
```

```
else
```

```
begin
```

```
always @(*)  
  begin  
    case (state)  
      S0: lights = 6'b100001;  
      S1: lights = 6'b100010;  
      S2: lights = 6'b100100;  
      S3: lights = 6'b001100;  
      S4: lights = 6'b010100;  
      S5: lights = 6'b100100;  
      default lights = 6'b100001;  
    endcase  
  end  
endmodule
```

# Waiting for a green at night on empty streets

What about a sensor for cars waiting in each direction?

# Karnaugh Maps

Copyright 2007 © Elsevier

<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	<i>Y</i>
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

<i>Y</i>	<i>CD</i> \ <i>AB</i>	00	01	11	10
00					
01					
11					
10					

# Karnaugh Maps

Copyright 2007 © Elsevier

<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	<i>Y</i>
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

<i>Y</i>	<i>AB</i>	00	01	11	10
<i>CD</i>	00	1	0	0	1
01	0	1	0	1	
11	1	1	0	0	
10	1	1	0	1	

# Karnaugh Maps

Copyright 2007 © Elsevier

<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	<i>Y</i>
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

<i>Y</i>	<i>CD</i> \ <i>AB</i>	00	01	11	10
00	00	1	0	0	1
01	01	0	1	0	1
11	11	1	1	0	0
10	10	1	1	0	1

# Karnaugh Maps

Copyright 2007 © Elsevier

A	B	C	D	Y
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

Y CD \ AB		AB			
		00	01	11	10
00	1	0	0	1	
01	0	1	0	1	
11	1	1	0	0	
10	1	1	0	1	

Sum of products?



# More Karnaugh Maps

<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	<i>Y</i>
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	X
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	X
1	0	1	1	X
1	1	0	0	X
1	1	0	1	X
1	1	1	0	X
1	1	1	1	X

<i>Y</i> <i>CD</i> \ <i>AB</i>	00	01	11	10
00				
01				
11				
10				

<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	<i>Y</i>
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	X
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	X
1	0	1	1	X
1	1	0	0	X
1	1	0	1	X
1	1	1	0	X
1	1	1	1	X

		<i>Y</i>			
		<i>CD</i> \ <i>AB</i>			
		00	01	11	10
<i>CD</i>	00	1	0	X	1
	01	0	X	X	1
<i>CD</i>	11	1	1	X	X
	10	1	1	X	X

<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	<i>Y</i>
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	X
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	X
1	0	1	1	X
1	1	0	0	X
1	1	0	1	X
1	1	1	0	X
1	1	1	1	X


<i>Y</i>		<i>AB</i>			
		00	01	11	10
<i>CD</i>	00	1	0	X	1
	01	0	X	X	1
11	1	1	X	X	
10	1	1	X	X	

$$Y = A + \bar{B}\bar{D} + C$$

# CMOS logic
 
## nMOS + pMOS


- Several conceptual inversions happening
  - n-type vs p-type channels
  - gate-to-source voltage vs threshold
  - a few different symbols
- For the same +ve source voltage,  $V_{DD}$ ,
  - nMOS: logic 1 (near  $V_{DD}$ ), the transistor is ON
  - pMOS: logic 0 (near  $V_{SS}$ ), the transistor is ON
- Drawn to show logic inversion
  - Note the bubble
  - Abstracts physical operation




# How do you build a three-input NOR gate?

A	B	Out
0	0	1
0	1	0
1	0	0
1	1	0


Truth Table of a 2 input NOR gate

 

How do you build a three-input NOR gate?

 

# Transmission gates

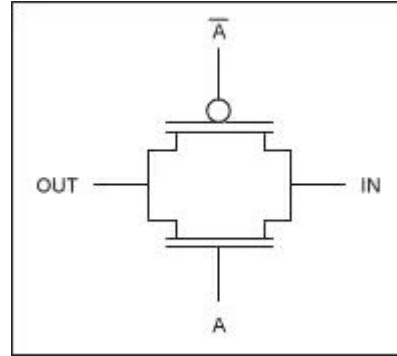

Logic gates:


nMOS passes 1s poorly; pMOS passes 0s poorly

Transmission gates:

In general, nMOS (bottom): pass zeros

pMOS (top): pass ones

 Bi-directional, useful for simplifying circuits



Qu'est-ce que c'est?

# References

- [http://www.lbebooks.com/downloads/exportal/verilog\\_basys\\_example62-trafficlights.pdf](http://www.lbebooks.com/downloads/exportal/verilog_basys_example62-trafficlights.pdf)
- Digital Design and Computer Architecture, David M. Harris & Sarah L. Harris
- Maxim Integrated,  
<https://www.maximintegrated.com/en/app-notes/index.mvp/id/4243>
- Wikipedia