

# Discussion 5


Taehwan Kim

031318


# Logical effort

- Property of the gate type (topology)
  - NAND2, NAND3, NOR2, NOR3, XOR, ...
  - The way the transistors geometrically connected decides logical effort
- Easiest way to calculate LE
  - Match the resistance of the pull-up & pull-down to unit inverter
  - Calculate  $C_{in\_gate}/C_{in\_inv}$
- Same for intrinsic delay

# Example

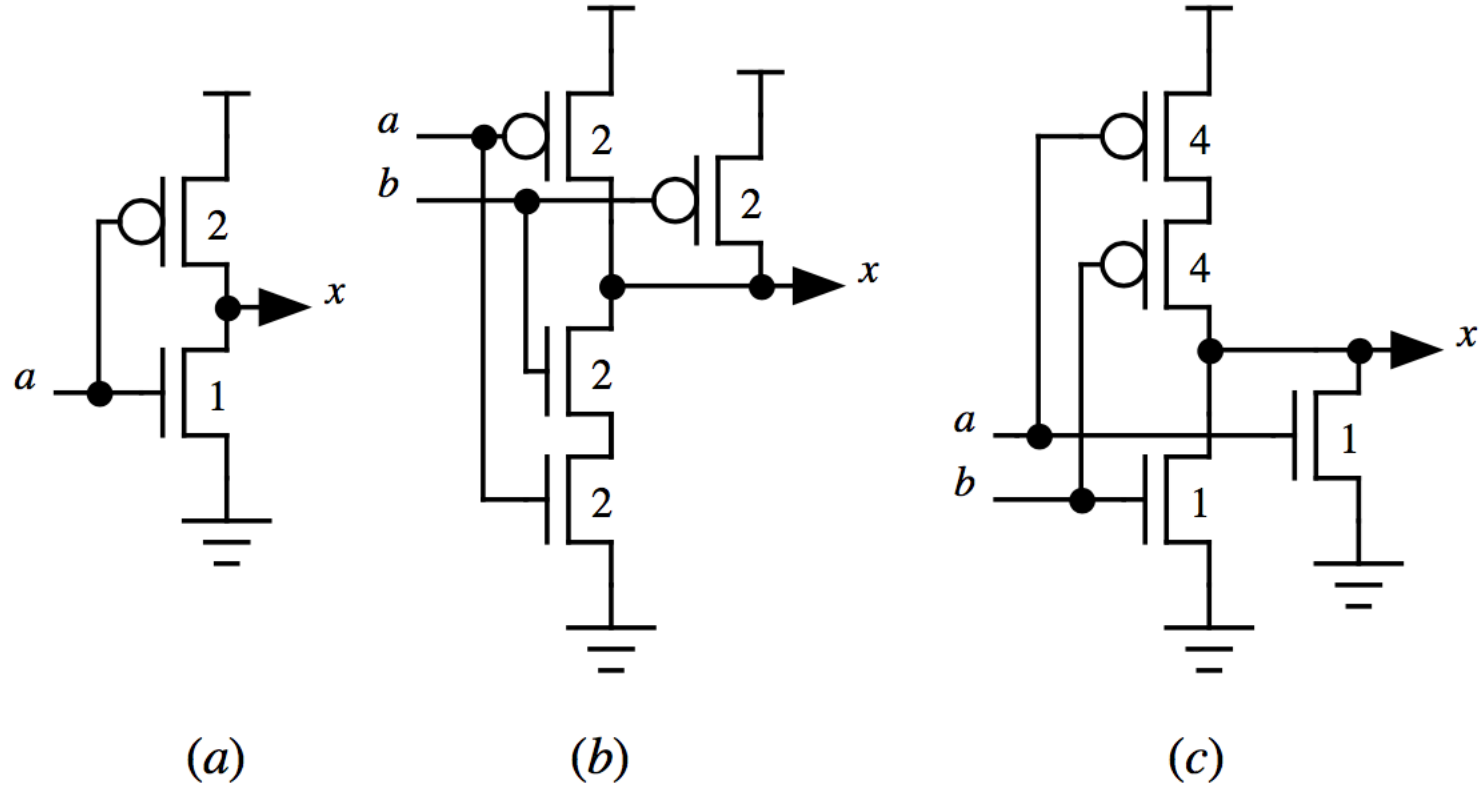

 
# Advanced example – CMOS transmission gate




- Used in tri-state buffer, multiplexers, etc.
- PMOS & NMOS are generally equally sized
- We can model the two transistors in parallel as an ideal switch with resistance equal to that of an NMOS transistor for both rising and falling transitions.
- How to calculate the logical effort of a transmission gate?

# Advanced example – transmission gate

 


(a)

 


(b)

- There should always be pull-up & pull-down path from VDD/GND to define logical effort!!
- LE can be defined with a driver circuit for the transmission gate
- With an inverter,
  - LE for d: 2
  - LE for s:  $4/3$  (should always drive s & s')

# Advanced example – transmission gate

 


(a)

 

(b)
 
# Applying LE for path delay calculation


- Any gate can now be treated as simple inverter, you just need to use LE as a weight factor for the fanout of that gate ( $F \cdot LE = EF$ )



What do value a, b, c mean??  
→ Absolute input capacitance, in the unit of reference inverter input capacitance

Electrical fanout,  $F =$   
 $\Pi LE =$   
 $PE =$   
 $EF/stage =$   
 $a =$   
 $b =$   
 $c =$

# Applying LE for path delay calculation

 

**Electrical fanout,  $F = 5$**

**$\Pi LE = 25/9$**

**$PE = 125/9$**

**$EF/\text{stage} = 1.93$**

**$a = 1.93$**

**$b = 2.23$**

**$c = 2.59$**

From the back


$$5/c = 1.93$$

$$(5/3)c/b = 1.93$$

$$(5/3)b/a = 1.93$$




# Easy way to think of power dissipation

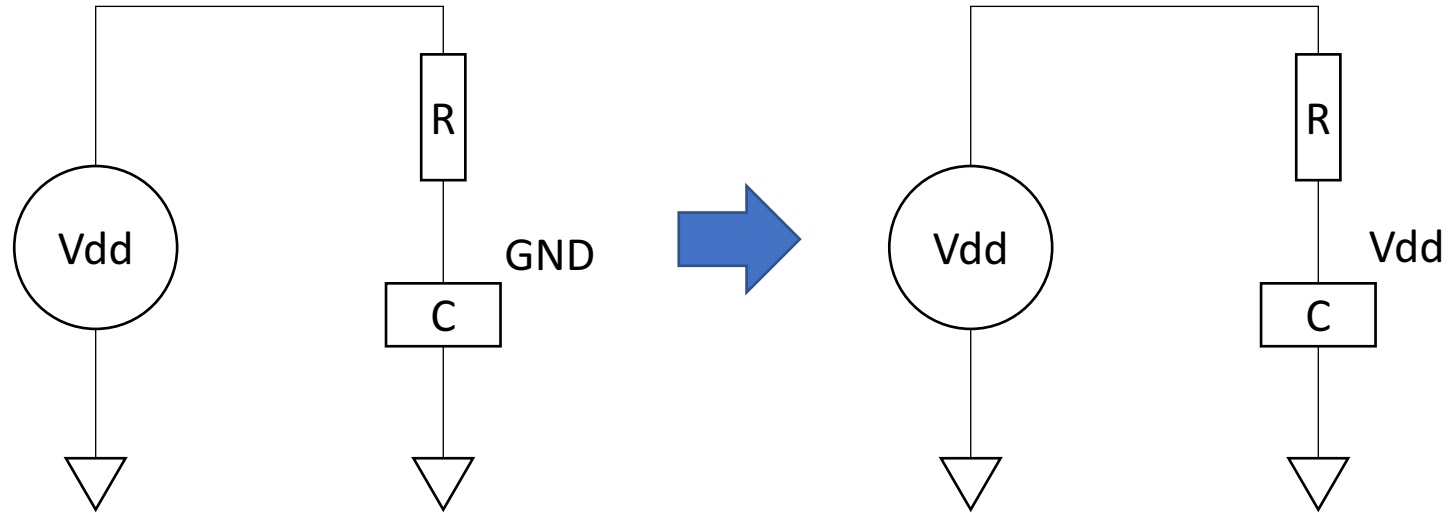

- You burn power only at pull-up transition
- Cap charge:  $0 \rightarrow CV_{dd}$  (C)

# Easy way to think of power dissipation

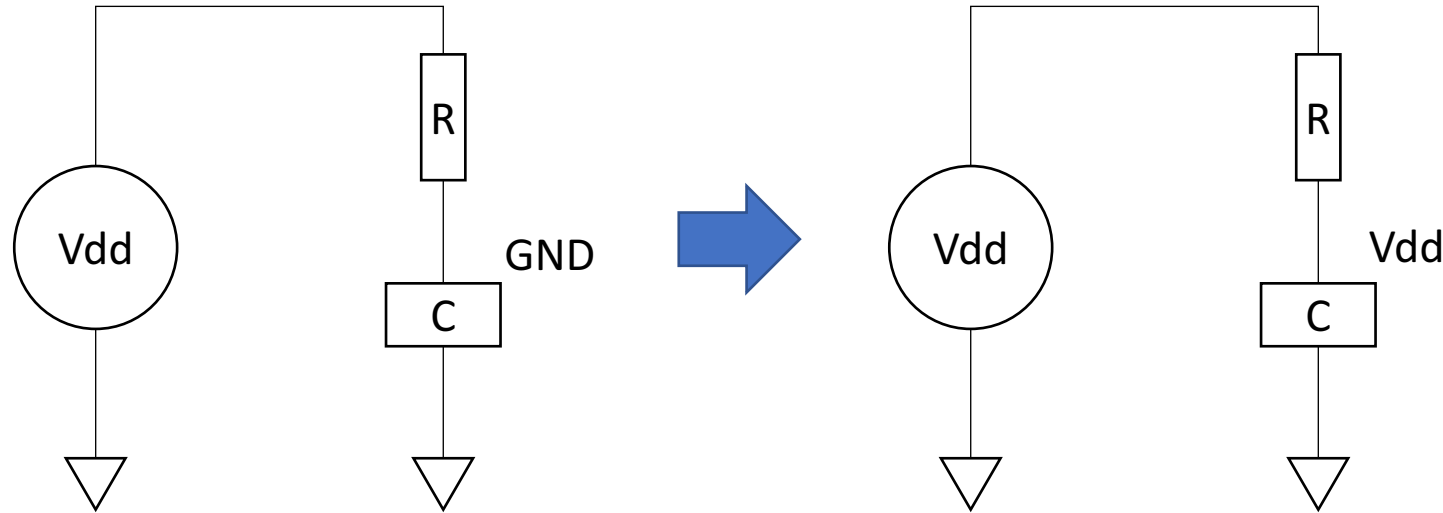

- Electrical work:  $W = Q \int_a^b \mathbf{E} \cdot d\mathbf{r}$
- From power source (Vdd) perspective:  $\int \mathbf{E} \cdot d\mathbf{r} = V_{dd}$  (constant)
- Therefore,  $W = QV_{dd} = CV_{dd}^2$

# Reviewing the basics

- Resistors in parallel:  $R = (R1 * R2) / (R1 + R2)$
- Resistors in series:  $R = R1 + R2$
- Capacitors in parallel:  $C = C1 + C2$
- Capacitors in series:  $C = (C1 * C2) / (C1 + C2)$
- $Q = CV$
- $i = Cdv/dt$  (from  $i = dq/dt$ , take  $d/dt$  of  $Q = CV$ )
- Stored energy is work required to charge it.  $v = q/C$ ,  $dw = v dq = q dq/C$ , integrate to find  $E = Q^2 / (2C)$
- Or  $E_{\text{stored}} = 1/2 Cv^2 = 1/2 QV$  (from  $E = \int P dt$ , plug in  $P = IV$  and  $I = Cdv/dt$ )
- Transistor  $C = C * W, R = R/W$ ... Doubling width of transistor halves the resistance and doubles the capacitance

# Reviewing the basics

- $P=IV$  (power is product of voltage and current) ...Watts
- $E=PT$  (energy is power integrated over interval  $T$ ) =  $\int vi dt$  ...Joules = Watt\*seconds.  
1 Watt\*hour = 3600 Watt\*seconds
- $V=IR$  (ohms law)
- $P=i^2R=v^2/R$

# Things you need to know

- Draw a VTC for a given gate
- Describe the interesting points in a VTC. How is  $V_{IH}$  and  $V_{IL}$  defined? What is the noise margin and why does it matter?
- Switch model for an NMOS and PMOS. When is it on? Off?
- Implement arbitrary CMOS logic gates (PUN, PDN)
- Draw CMOS implementations of NAND/NOR/INV/
- How can transmission gates be used?
- What are tri-state buffers?
- Draw a switch model of a gate
- Size a gate to balance rise/fall times
- Draw the capacitances associated with a CMOS gate
- Translate RC network to delay

# Things you need to know

- How do you optimize a variable?
- Redo the inverter chain optimal delay proof
- What is the optimal effective fanout? Why?
- Is it better for the fanout to be too high or too low?
- Trade-off between fanout and number of stages
- Logical effort of common gates
- Derive the logical effort for an arbitrary gate
- Translate logical effort to delay
- Solve for delay of network with different gates, fanout, branching. Optimize this delay

# Things you need to know

- Where does the capacitance come from
- How does capacitive coupling work?
- **Calculate resistance from sheet resistance**
- RC models for interconnect
- **Calculate Elmore delay of a network**
- Derive tau for a wire
- Delay for lumped vs. distributed RC
- **Derivation of delay from step on an RC circuit (where 0.69 comes from)**
- **How many repeaters do you need?**

# Things you need to know

- Instantaneous vs. peak vs. average power
- Derivation of energy drawn from the supply vs. stored on a capacitor
- Use switch model/results of derivation to calculate how much energy is drawn/stored on a capacitor
- **What is short circuit current. More common on big load or small load?**
- Find power based on capacitance, frequency and activity
- Convert between power and energy
- What is glitching?
- Describe a simple current model for a transistor (beyond the switch model)
- How does parallelism and pipe-lining help power?