

EECS 151/251A Homework 6

Due Monday, March 12th, 2018

Problem 1: RC Delay and Logical Effort Basics

Take a CMOS inverter in a process where $\gamma = \frac{C_d}{C_g}$, and the PMOS effective on-resistance is equal to K times that of the NMOS (i.e. $R_p = K \cdot R_n$) for minimally sized transistors.


- Draw the inverter at the transistor-level and size each FET for equal pull-up and pull-down strength. Assume the NMOS is of size '1', normalized to the minimum width of the process.
- Write down the delay of this unloaded inverter using RC time constants in terms of γ , R_n , and C_g . Call this delay t_p . Assume input step transitions.
- Now let the inverter have a load of C_L attached to its output. Call the quantity $f = C_L/C_{in}$. Write the delay of the inverter in terms of γ , t_p , and f .
- Recall that the gate delay for any CMOS gate can be expressed as:

$$t_{p,gate} = t_{inv}(p + f \cdot LE)$$

where t_{inv} is a process constant, p is the intrinsic delay of the gate, and LE is the logical effort of the gate.

What are these values for an inverter?

 
- Take the following sizing of a NAND2 gate. What is W_p for inverter equivalent delay? Prove that $W_{n,a} = W_{n,b} = 2$ so the gate has equivalent self-loaded delay to an inverter and consumes minimal area.



- (f) Find the logical effort of this NAND2 gate for both inputs. What happens to the LE as K increases, and why does it make intuitive sense?
- (g) What is the intrinsic delay of a NAND2 gate (i.e. find p_{NAND2})? Make the assumption that $K = 2$.

Problem 2: Gate Delay Optimization and Branching

Size the gates in the chain below for minimum delay. As usual, all gates are sized so that the pull-up and pull-down resistance match that of the reference inverter.

 

Problem 3: Voltage Scaling

To gain intuition about voltage scaling, it is important to estimate delay and energy as a function of voltage. The Alpha Power Law model of a transistor's current can estimate delay over a wide voltage range. According to that model:

$$I_{ON} \propto (V_{DD} - V_{TH})^\alpha$$

$$I_{OFF} \propto e^{\frac{-V_{TH}}{kT/q}}$$


Use this model with $\alpha = 1.3$, $V_{TH} = 0.3V$ and $V_{DD,nom} = 1V$ to answer the following questions about voltage scaling. Assume that at nominal supply voltage a given design runs at $1GHz$ and that the total capacitance is $C_{TOT} = 1nF$.

- a) For $0.35V < V_{DD} < 1V$, considering dynamic energy only and an activity factor of 0.1, generate the power vs. delay (t_d) plot.
- b) Now consider power as a combination of dynamic energy and leakage power. Using $I_{OFF} = 100mA$ for your given design, plot V_{DD} vs. the energy per cycle for activity factors $a = 0.1, 0.2, 0.3$. Is voltage scaling more or less effective for higher activity factors? Explain why.

 Problem 4: Elmore Delay

For the following problem, $C_G = C_D = 2fF/um$, the minimum sized (labeled as 1x in the picture) inverter has $L = 0.1um$, $W_p = 2um$, $W_n = 1um$ and for this technology $R_{n,on} = 10k\Omega/sq.$ (i.e. the resistance of an NMOS with width W and length L is equal to $10k\Omega \frac{L}{W}$) and $R_{p,on} = 20k\Omega/sq.$ (i.e. the resistance of a PMOS with width W and length L is equal to $20k\Omega \frac{L}{W}$). Note that a 6x inverter has 6 times the width of a 1x inverter

For the wire, $R_{wire} = 0.1\Omega/sq.$, the parallel plate capacitance is $C_{pp} = 20aF/um^2$ and the fringing capacitance per each side of wire is $C_{fr} = 14aF/um$. The wire widths and lengths are shown in the picture.




- a) Using the π wire model, draw the equivalent RC switch model. What is the propagation delay from a step at V_{in} to V_a and V_b ?
- b) What is the skew (difference in arrival time between V_a and V_b)?

Problem 5: Energy

Given the circuit below, answer the following questions. Assume that the capacitances associated with the FETs are negligible.

$$C_1 = C_2 = 90fF$$

$$V_{th,n} = |V_{th,p}| = 0.4V$$

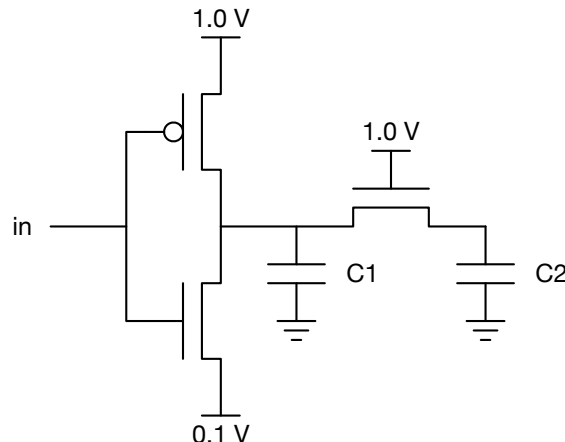

Part a

How much energy is stored in each capacitor after a 1V to 0V transition on in? Please show your work.

Part b

How much energy was drawn by the supply in part a? Is this what you expected? Please show your work.

Part c

How much total energy is dissipated when the input goes from 1V to 0V and then back to 1V? Please show your work.

Problem 6: Processor Datapath

You are to add a *store with postincrement* instruction to a single-stage MIPS processor. The instruction **swinc** updates the index register to point to the next memory word after completing the store. **swinc \$rt, imm(\$rs)** is equivalent to the following two instructions:

```
sw      $rt, imm($rs)
addi   $rs, $rs, 4
```

(Reminder: The first line syntax means store the word from register **\$rt** to address **imm + contents of register \$rs**.)

How would you modify the following datapath to accommodate this instruction? Try to add as little hardware as possible.

