


University of California at Berkeley
College of Engineering
Department of Electrical Engineering and Computer Science

EECS 150
Fall 2005

R. H. Katz

Problem Set #2: Programmable Logic
Assigned 7 September 2005, Due 16 September at 2 PM

 1. Consider the following multilevel schematic constructed from AND-OR gates.



- a. What is the Boolean algebra equation derived from this schematic?
 - b. What is the minimized AND-OR schematic that is equivalent to this schematic? Show your work using a K-map.
 - c. Suppose that the schematic is restricted to only using NAND, NOR, and NOT gates. Convert the original schematic to a similar one making use of these gates only.
 - d. Suppose that the schematic is restricted to only using NAND gates. Convert the original schematic to a similar one using only NAND gates. NOTE: You may have to add some gates to make the mapping work!
 - e. Suppose that the schematic is restricted to only using NOR gates. Convert the original schematic to a similar one using only NOR gates. NOTE: You may have to add some gates to make the mapping work!
2. Consider the following four functions to be implemented in Programmable Logic Arrays:
- $$F(A,B,C,D) = \Sigma m(1,4,5,7,9,12,13,15)$$
- $$G(A,B,C,D) = \Sigma m(1,3,5,6,7,13,14,15)$$
- $$H(A,B,C,D) = \Sigma m(4,6,12,13,14,15)$$
- $$I(A,B,C,D) = \Sigma m(1,3,13,15)$$
- a. Use K-maps to minimize in sum of products form each of the four functions independently. Write down the Boolean expressions that result.
 - b. How many unique product terms span the four functions?
 - c. Now minimize the four functions, seeking to find the minimum number of product terms across all four functions simultaneously.

- d. How many unique terms does your solution require? Is it a savings compared with your answer to part b?
 - e. Show how you would program the AND-OR array to implement the four functions using your solution to part c.
3. Programmable logic arrays as presented in class are based on AND-OR two-level logic. It is also possible to implement logic arrays in OR-AND logic. Repeat parts (a) through (d) except where the target is product of sums expressions for the functions F, G, H, I described above.
 - e. Which solution is better and why, 2(d) versus 3(d)?
 4. Given the function $F(A,B,C) = \Sigma m(1,3,4,6,7)$:
 - a. Show how to implement F with an 8:1 multiplexer.
 - b. Show how to implement F with a 4:1 multiplexer (HINT: put A and B on the selection inputs).
 5. Given the function $G(A,B,C,D) = \Pi M(0,1,3,4,5,10,11)$:
 - a. Show how to implement G with a 16:1 multiplexer.
 - b. Show how to implement G with an 8:1 multiplexer (HINT: put A, B, and C on the selection inputs).
 6. Given the function $H(A,B,C,D) = \Sigma m(1,3,5,7,12,13,14,15)$, show how to implement H with a single 4:1 multiplexer and no other logic.
 7. Given the same function from problem 6:
 - a. Implement H using a 4:16 decoder as a function generator along with a single large fan-in OR gate.
 - b. Implement H using a 3:8 decoder as a function generator along with a single 4-input OR gate.
 8. Given the functions F, G, H, I of Problem 2:
 - a. How many Xilinx CLBs would it take to implement your answer to Problem 2(a) for all four functions together?
 - b. How many Xilinx CLBs would it take to implement your answer to Problem 2(c) for all four functions together?
 - c. Considering just the truth tables for the four functions, how many Xilinx CLBs would it take to implement them together?