

# Structural Verilog

UCB EECS150 Spring 2010


Lab Lecture #2

# Agenda

- CAD Flow Extension
- Verilog
- Structural Verilog
- Administrative Info
- Lab #2: A Structural Accumulator
  - Circuit
  - Testing
  - Analysis of resource usage and timing
  - PreLab
- Questions?

# CAD Flow Extension


(1)

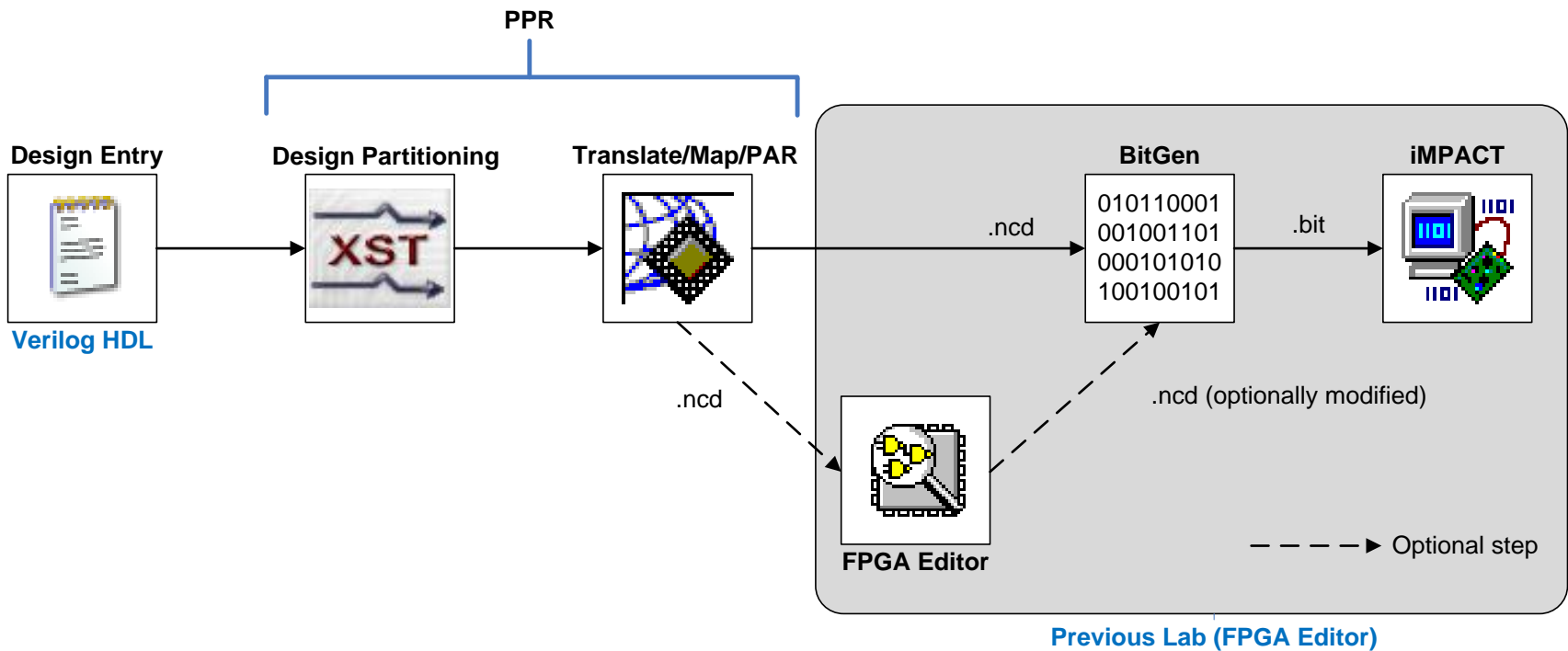

# CAD Flow Extension

(2)

- The Big Picture

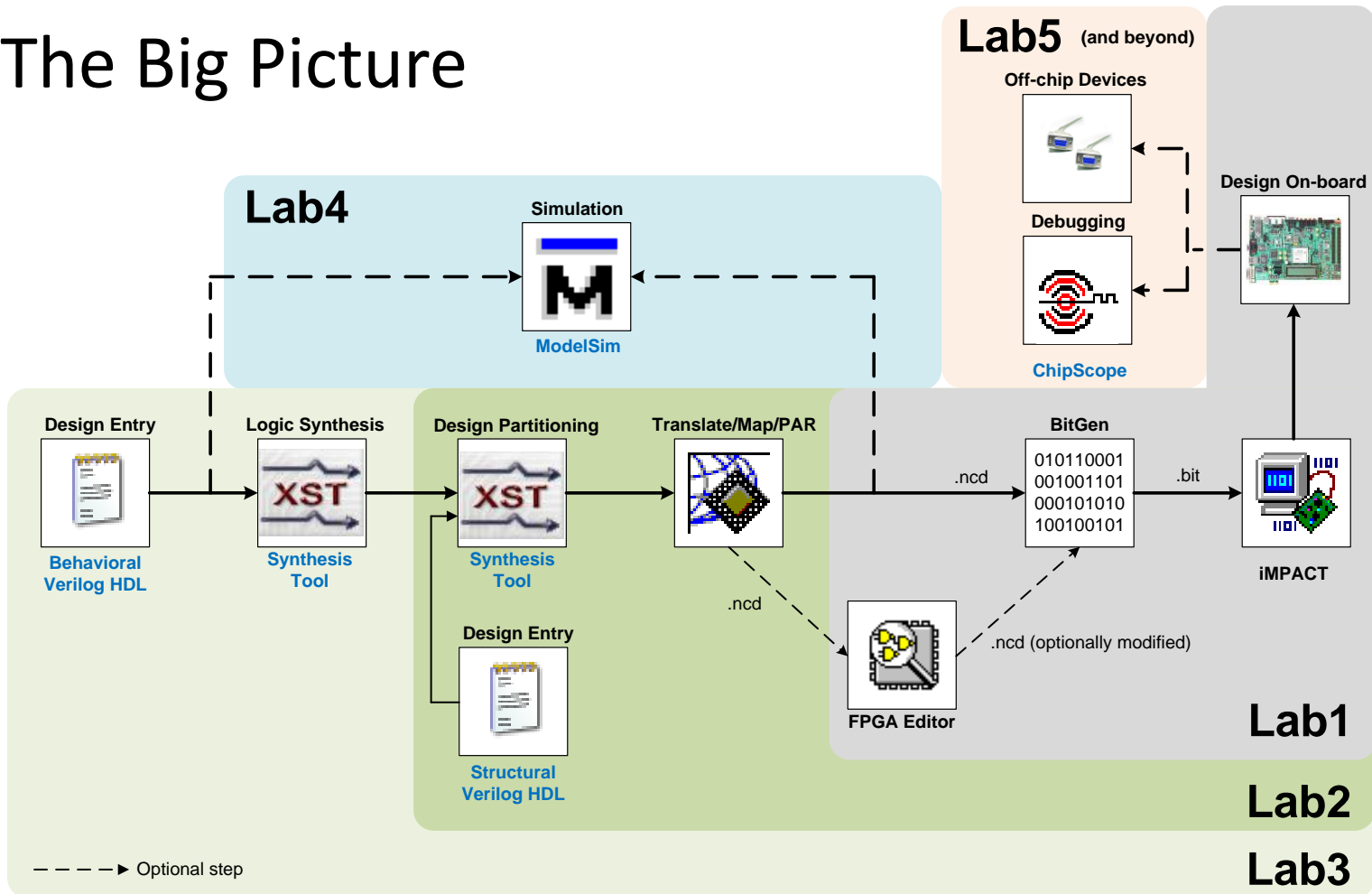



# Verilog

(1)


- What's an HDL?
  - Textual Description of a Circuit
  - Human and Machine Readable
  - Hierarchical
  - Meaningful Naming
- NOT A PROGRAM
  - Describe what the circuit IS
  - Not what it DOES

# Verilog + CAD

design on napkin

 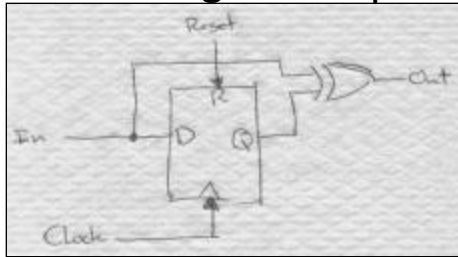


notepad

 

CAD Tools


```
assign Out = Q ^ In;  
always @ (posedge Clock) begin  
    if (Reset) Q <= 1'b0;  
    else Q <= In;  
end
```

textual hardware description

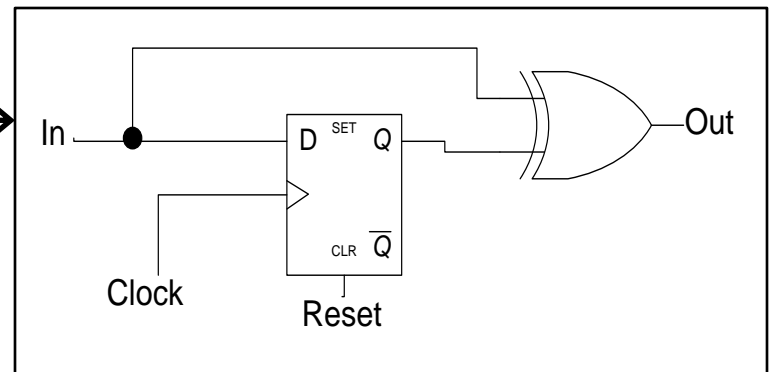





placed & routed design
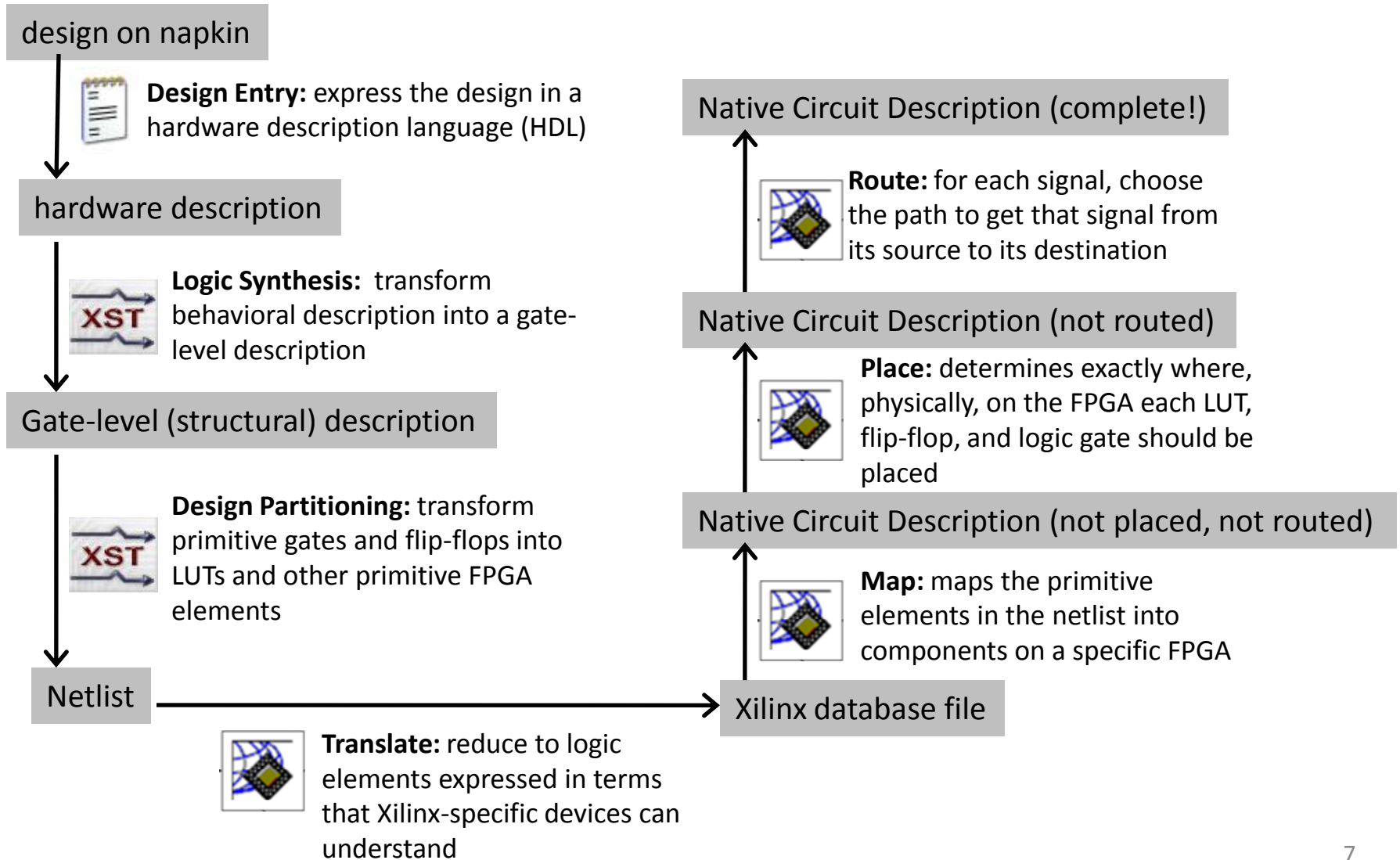
# Verilog + CAD



# Digital Design Productivity, Gates/Week

Source: DataQuest

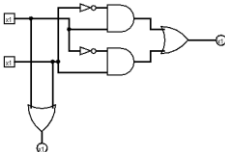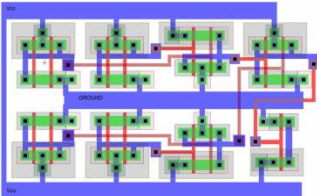- Behavioral HDL  2K-10K
- RTL HDL  1K-2K
- Gates  100-200
- Transistors  10-20



# Structural Verilog

(1)

- Verilog Subsets
  - Structural: primitive gates + modules
    - Gate level design
    - **You will ONLY use Structural Verilog in this lab**
  - Dataflow: compact boolean expressions
    - More compact expression of structural Verilog
  - Behavioral: abstract syntax
    - Timing nuances
    - You will see this starting next lab

# Structural Verilog

(2)

- Structural 2:1 Mux example

```
module Mux21(A, B, S, Out);  
  input wire A, B, S;  
  output wire Out;  
  
  wire notS, ATemp, BTemp;  
  
  not invertS(notS, S);  
  and and(ATemp, A, notS),  
    andB(BTemp, B, S);  
  or result(Out, ATemp, BTemp);  
endmodule
```


Key

Module wrapper

Input/Output wire declarations

Wire declarations

Gates

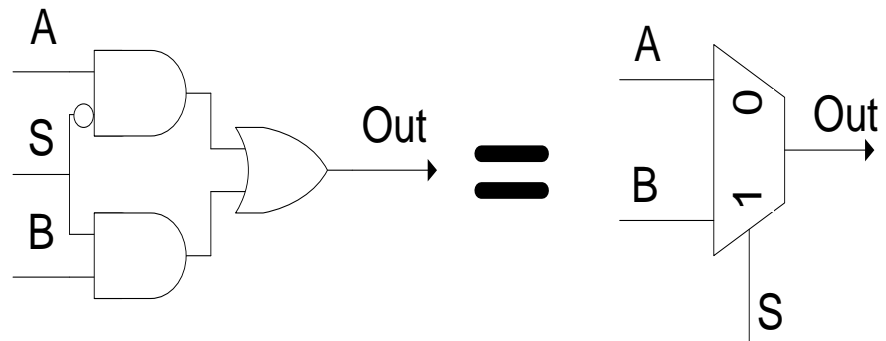

# Administrative Info

(1)

- Homework submission
- Lab lecture conflicts
- Card key access
- Check-off procedure
- Questions?

# Lab #2


(1)

- Build a structural Accumulator
  - Work with a real design
  - Write parameterized Verilog
- Debugging
  - Synplicity RTL/Technology schematic
- Analysis
  - Resource consumption
  - Timing

# Lab #2

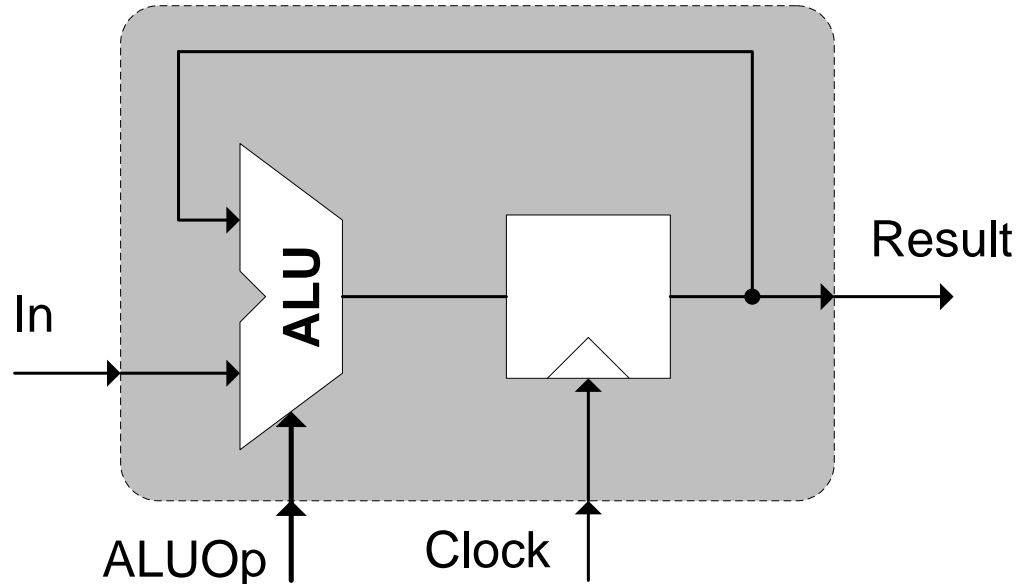(2)


- Structural Accumulator
  - ALU
  - 'FDRSE' Xilinx primitive flip-flop



# Lab #2

(3)


- ALU
  - We provide the Verilog for N-bit version
  - You must implement the 1-bit ALU model
  - **Must support our ALUOp**
  - Supports: +, -, &, |, ~, pass-through (7 operations)

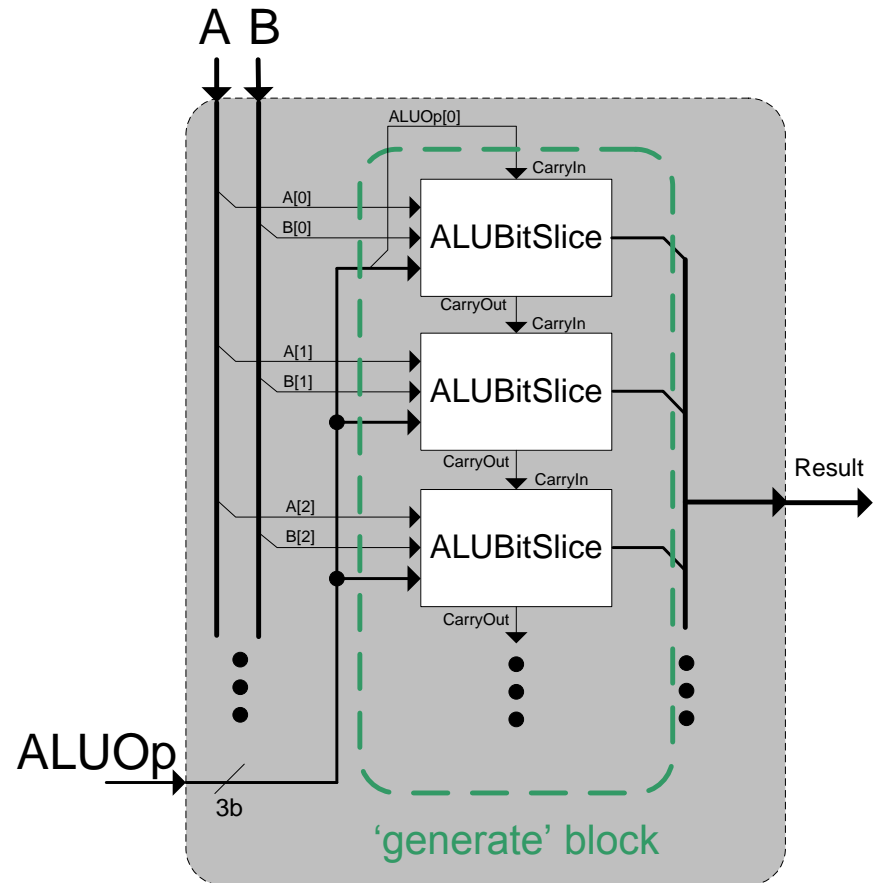

# Lab #2

 (4)

- FDRSE
  - Xilinx primitive
  - D-type flip-flop
    - Instantiated like a simple module
    - Specific Set/Reset characteristics
  - “Read all about it!” → [virtex5\\_hdl.pdf](#)
    - It’s part of the PreLab!



# Lab #2

(5)


- Accumulator
  - We give you port specification
  - You will implement the rest of the circuit
- Use code examples
  - Mux21: Structural Verilog (gates, wires)
  - ALU: generate statements
- Abide by our interfaces!



# Lab #2

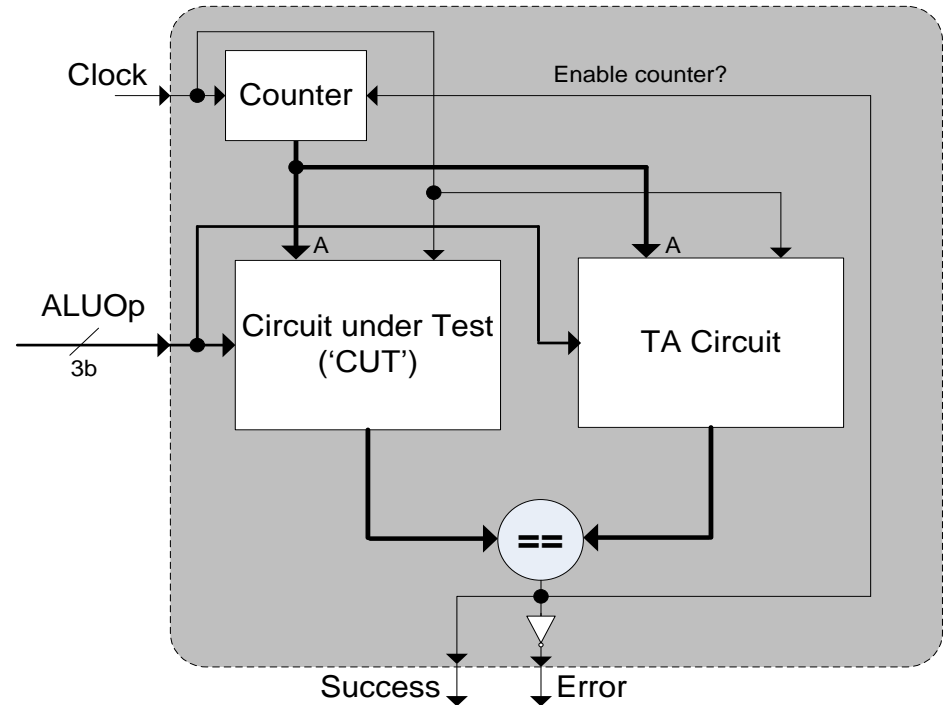(6)

- HW test harness
  - TA Accumulator vs. your Accumulator
  - Check all input combinations
  - Signal error



# Lab #2

(7)

- Circuit Analysis
  - Resource Usage
    - Accumulator(width) = how many LUTs / SLICES?
    - generate allows you to experiment
  - Timing
    - Locate nets → **“Technology Schematic”**
    - Calculate delay on the nets → **FPGA Editor**

# Lab #2

(8)

- PreLab
  - Read specified material
    - [Virtex-5 Libraries Guide for HDL Designs](#) (FDRSE section)
  - Design your ALUBitSlice and Accumulator
  - Write all of your Verilog
- Lab starts at debugging phase
  - Assumption:  
**you have written all of your Verilog ahead of time**

# Acknowledgements & Contributors

Slides developed by Brandon Myers & John Wawrzynek (1/2010).

This work is based closely on slides by:

Chris Fletcher (2008-2009)

Greg Gibeling (2003-2005)

This work has been used by the following courses:

- UC Berkeley CS150 (Spring 2010): Components and Design Techniques for Digital Systems