

EECS150 - Digital Design


Lecture 9- CMOS (part 2)

Feb 16, 2010
John Wawrzynek

CMOS Devices

Review: Transistor switch-level models

 The gate acts like a capacitor. A high voltage on the gate attracts charge into the channel. If a voltage exists between the source and drain a current will flow. In its simplest approximation, the device acts like a switch.




Transistor-level Logic Circuits

Simple rule for wiring up MOSFETs:

nFET is used only to pass logic zero.
pFET is used only to pass logic one.



For example, consider the NAND gate:

 

Note: This rule is sometimes violated by expert designers under special conditions.

Transistor-level Logic Circuits

NOR gate:

  


Note:

- $\text{out} = 0$ iff $a \text{ OR } b = 1$ therefore $\text{out} = (a+b)'$
- Again pFET network and nFET networks are **duals** of one another.


Other more complex functions are possible. Ex: $\text{out} = (a+bc)'$

CMOS Logic Gates in General

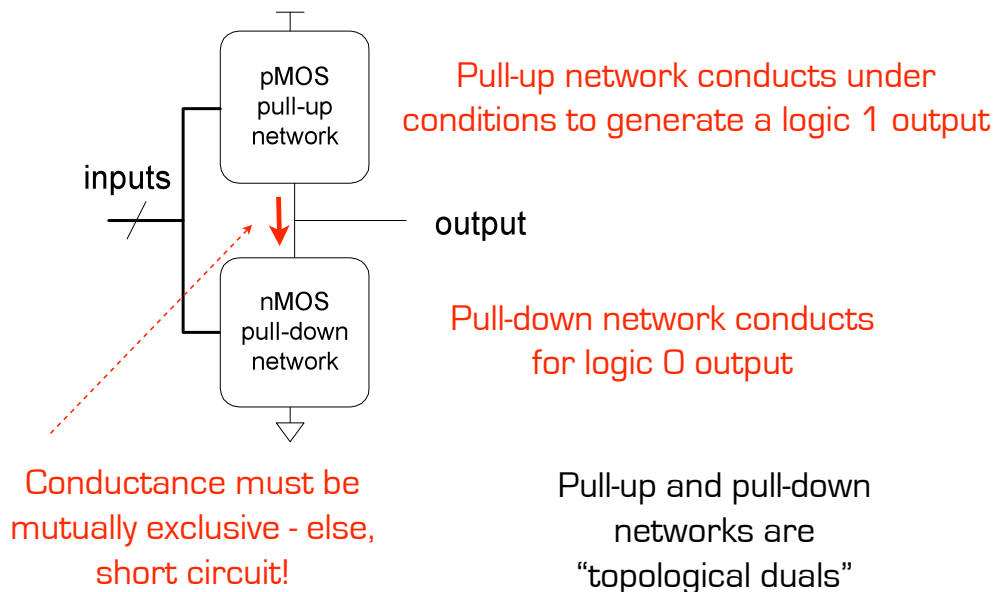

Transmission Gate

 
- Transmission gates are the way to build "switches" in CMOS.
- In general, both transistor types are needed:
 - nFET to pass zeros.
 - pFET to pass ones.
- The transmission gate is bi-directional (unlike logic gates).





- Does not directly connect to Vdd and GND, but can be combined with logic gates or buffers to simplify many logic structures.

Transmission-gate Multiplexor

2-to-multiplexor:
 $C = sa + s'b$

 

Switches simplify the implementation:

  

Compare the cost to logic gate implementation.

Tri-state Buffers

Tri-state Buffer:

OE	IN	OUT
0	0	Z
0	1	Z
1	0	0
1	1	1

"high impedance" (output disconnected)


Variations:

OE	IN	OUT
0	-	Z
1	0	1
1	1	0

Inverting buffer

OE	IN	OUT
0	0	0
0	1	1
1	-	Z


Inverted enable

 


transmission gate useful in implementation

Tri-state Buffers

 Tri-state buffers enable "bidirectional" connections.




 Tri-state buffers are used when multiple circuits all connect to a common wire. Only one circuit at a time is allowed to drive the bus. All others "disconnect" their outputs, but can "listen".





Tri-state Based Multiplexor


Multiplexor

 

If $s=1$ then $c=a$ else

 
 


 Transistor Circuit for inverting multiplexor:




Latches and Flip-flops

Positive level-sensitive latch:

  

 Positive Edge-triggered flip-flop built from two level-sensitive latches:



Latch Implementation:

