

EECS150 - Digital Design

Lecture 10- CPU Microarchitecture

Feb 18, 2010
John Wawrzynek

Processor Microarchitecture Introduction

Microarchitecture: how to implement an architecture in hardware

Good examples of how to put principles of digital design to practice.

Introduction to final project.


Application Software	programs
Operating Systems	device drivers
Architecture	instructions registers
Micro-architecture	datapaths controllers
Logic	adders memories
Digital Circuits	AND gates NOT gates
Analog Circuits	amplifiers filters
Devices	transistors diodes
Physics	electrons

MIPS Processor Architecture

- For now we consider a subset of MIPS instructions:
 - R-type instructions: **and**, **or**, **add**, **sub**, **slt**
 - Memory instructions: **lw**, **sw**
 - Branch instructions: **beq**
- Later we'll add **addi** and **j**

MIPS Microarchitecture Organization


Datapath + Controller + External Memory

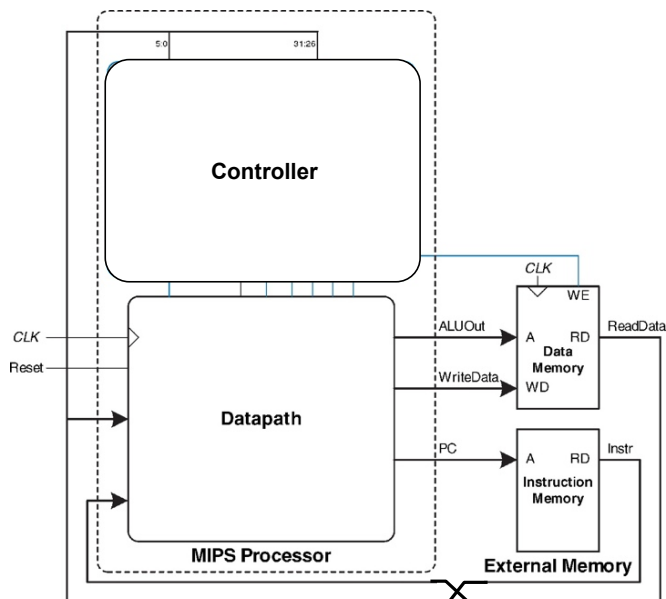

How to Design a Processor: step-by-step

1. Analyze instruction set architecture (ISA) \Rightarrow datapath requirements
 - meaning of each instruction is given by the *data transfers (register transfers)*
 - datapath must include storage element for ISA registers
 - datapath must support each data transfer
2. Select set of datapath components and establish clocking methodology
3. Assemble datapath meeting requirements
4. Analyze implementation of each instruction to determine setting of control points that effects the data transfer.
5. Assemble the control logic.

Review: The MIPS Instruction

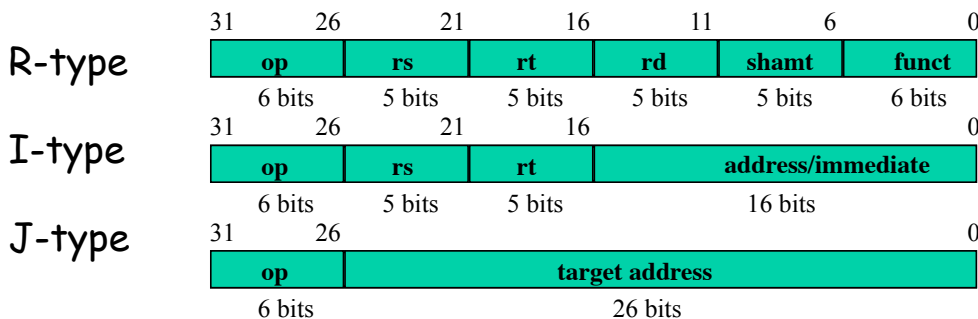

The different fields are:

op: operation ("opcode") of the instruction

rs, rt, rd: the source and destination register specifiers

shamt: shift amount


funct: selects the variant of the operation in the "op" field

address / immediate: address offset or immediate value


target address: target address of jump instruction

Subset for Lecture


`add, sub, or, slt`

 

`lw, sw`

 

`beq`

 

Register Transfer Descriptions

All start with instruction fetch:

$\{op, rs, rt, rd, shamt, funct\} \leftarrow IMEM[PC]$ OR
 $\{op, rs, rt, Imm16\} \leftarrow IMEM[PC]$ THEN

inst Register Transfers

- | | | |
|------------|---|------------------------|
| add | $R[rd] \leftarrow R[rs] + R[rt];$ | $PC \leftarrow PC + 4$ |
| sub | $R[rd] \leftarrow R[rs] - R[rt];$ | $PC \leftarrow PC + 4$ |
| or | $R[rd] \leftarrow R[rs] R[rt];$ | $PC \leftarrow PC + 4$ |
| slt | $R[rd] \leftarrow (R[rs] < R[rt]) ? 1 : 0;$ | $PC \leftarrow PC + 4$ |
| lw | $R[rt] \leftarrow DMEM[R[rs] + sign_ext(Imm16)];$ | $PC \leftarrow PC + 4$ |
| sw | $DMEM[R[rs] + sign_ext(Imm16)] \leftarrow R[rt];$ | $PC \leftarrow PC + 4$ |
| beq | $if (R[rs] == R[rt]) then PC \leftarrow PC + 4 + \{sign_ext(Imm16), 00\}$
else $PC \leftarrow PC + 4$ | |


Microarchitecture

Multiple implementations for a single architecture:

- **Single-cycle**
 - Each instruction executes in a single clock cycle.
- **Multicycle**
 - Each instruction is broken up into a series of shorter steps with one step per clock cycle.
- **Pipelined**
 - Each instruction is broken up into a series of steps with one step per clock cycle
 - Multiple instructions execute at once.


CPU clocking (1/2)

 - Single Cycle CPU: All stages of an instruction are completed within one **long** clock cycle.
 - The clock cycle is made sufficient long to allow each instruction to complete all stages without interruption and within one cycle.



CPU clocking (2/2)

 
- Multiple-cycle CPU: Only one stage of instruction per clock cycle.
 - The clock is made as long as the slowest stage.



Several significant advantages over single cycle execution: Unused stages in a particular instruction can be skipped OR instructions can be pipelined (overlapped).

MIPS State Elements

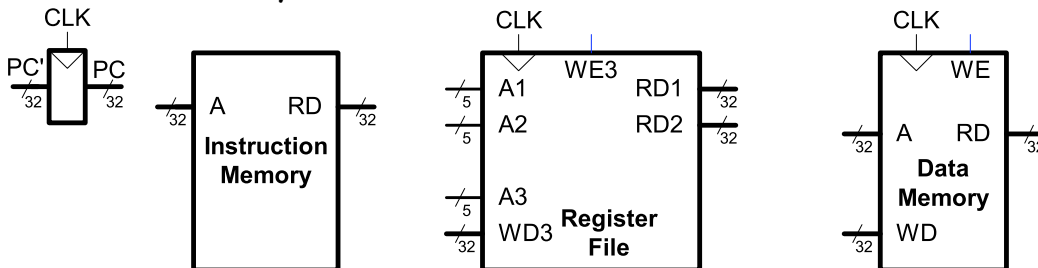- Determines everything about the execution status of a processor:
 - PC register
 - 32 registers
 - Memory




Note: for these state elements, clock is used for write but not for read (asynchronous read, synchronous write).

Single-Cycle Datapath: 1w fetch

- First consider executing 1w

$$R[rt] \leftarrow DMEM[R[rs] + \text{sign_ext}(Imm16)]$$


- **STEP 1: Fetch instruction**

 

Single-Cycle Datapath: 1w register read

$$R[rt] \leftarrow DMEM[R[rs] + \text{sign_ext}(Imm16)]$$

 
- **STEP 2: Read source operands from register file**



Single-Cycle Datapath: lw immediate

$$R[rt] \leftarrow DMEM[R[rs] + \text{sign_ext}(Imm16)]$$


- **STEP 3: Sign-extend the immediate**

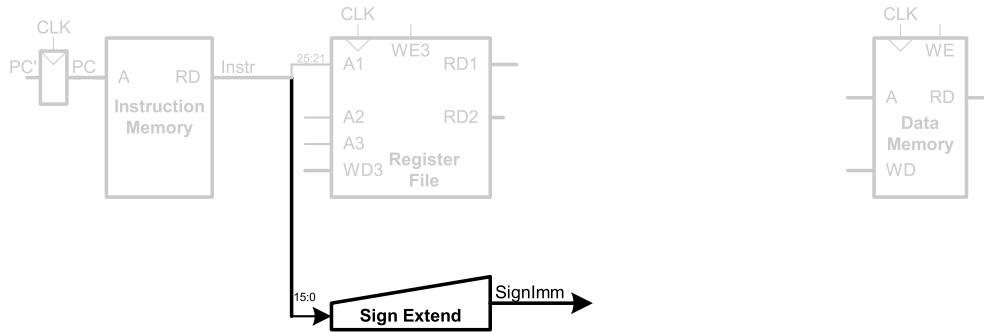

Single-Cycle Datapath: lw address

$$R[rt] \leftarrow DMEM[R[rs] + \text{sign_ext}(Imm16)]$$


- **STEP 4: Compute the memory address**

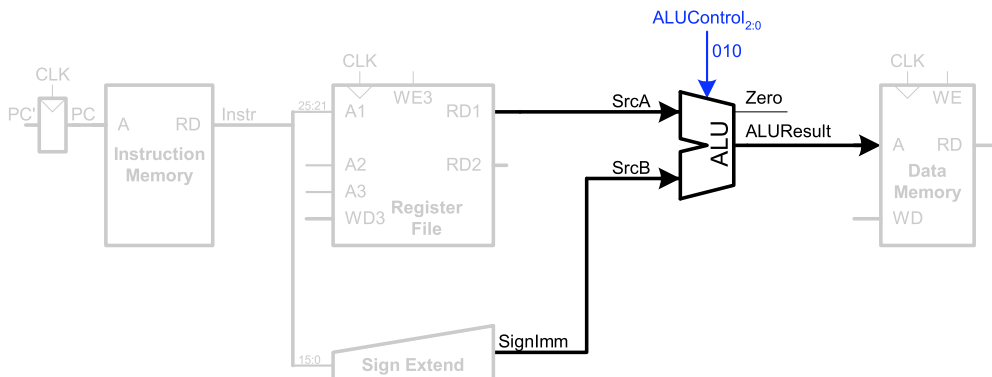

Single-Cycle Datapath: 1w memory read

$$R[rt] \leftarrow \text{DMEM}[R[rs] + \text{sign_ext}(\text{Imm16})]$$

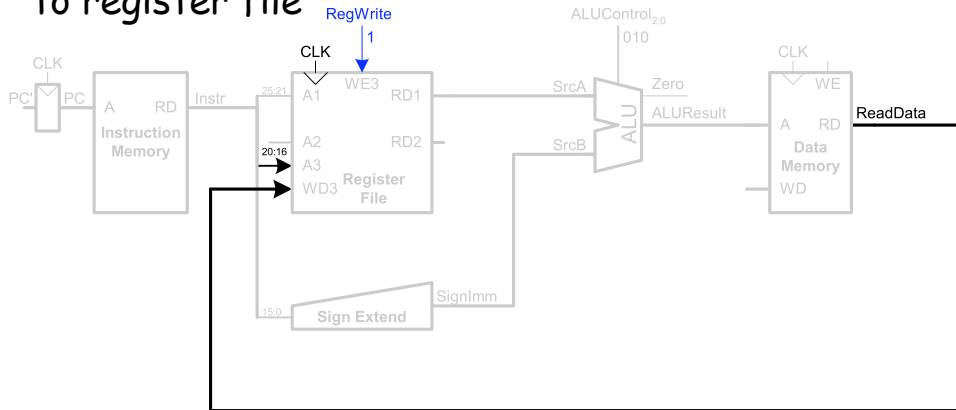
- STEP 5: Read data from memory and write it back to register file



Single-Cycle Datapath: 1w PC increment

- STEP 6: Determine the address of the next instruction


$$PC \leftarrow PC + 4$$

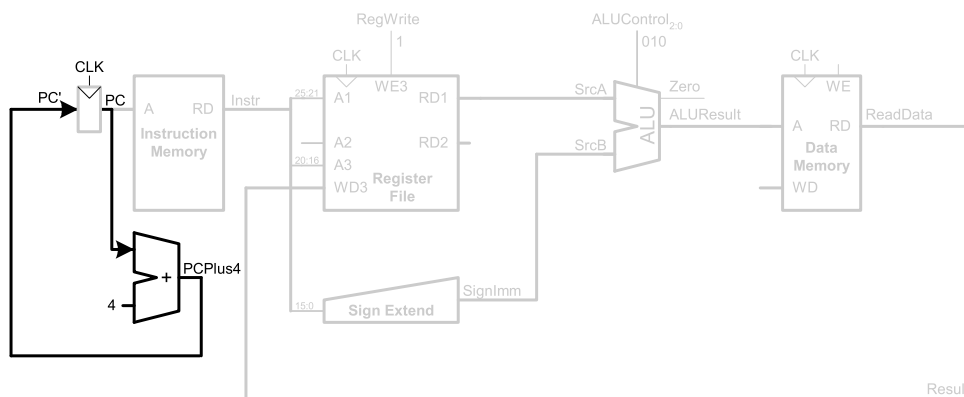

Single-Cycle Datapath: sw


$$DMEM[R[rs] + \text{sign_ext}(Imm16)] \leftarrow R[rt]$$

- Write data in rt to memory

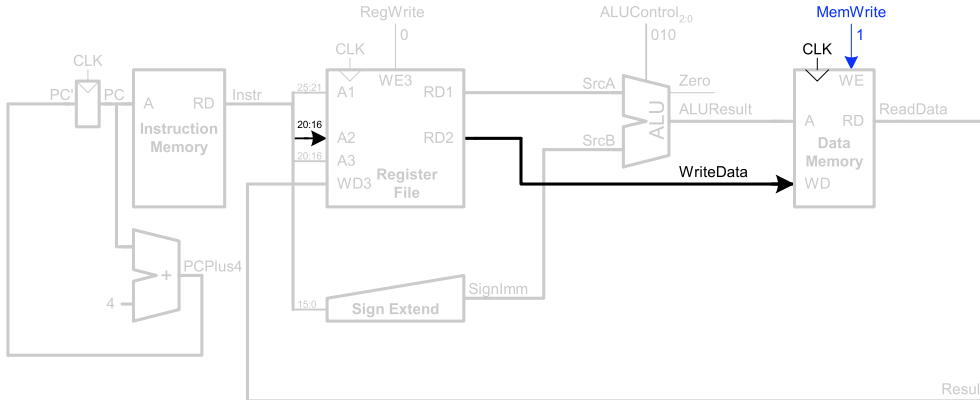

Single-Cycle Datapath: R-type instructions

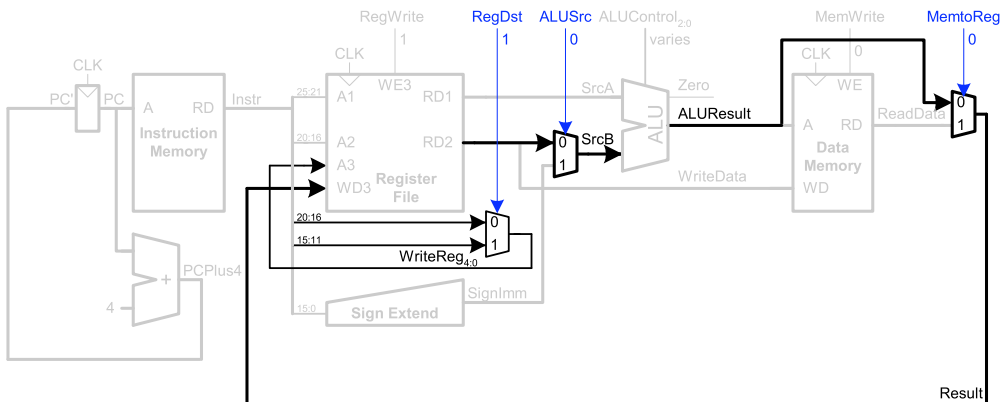- Read from rs and rt $R[rd] \leftarrow R[rs] \text{ op } R[rt]$
- Write $ALUResult$ to register file
- Write to rd (instead of rt)




Single-Cycle Datapath: beq


if ($R[rs] == R[rt]$) then $PC \leftarrow PC + 4 + \{sign_ext(Imm16), 00\}$

- Determine whether values in rs and rt are equal
- Calculate branch target address:

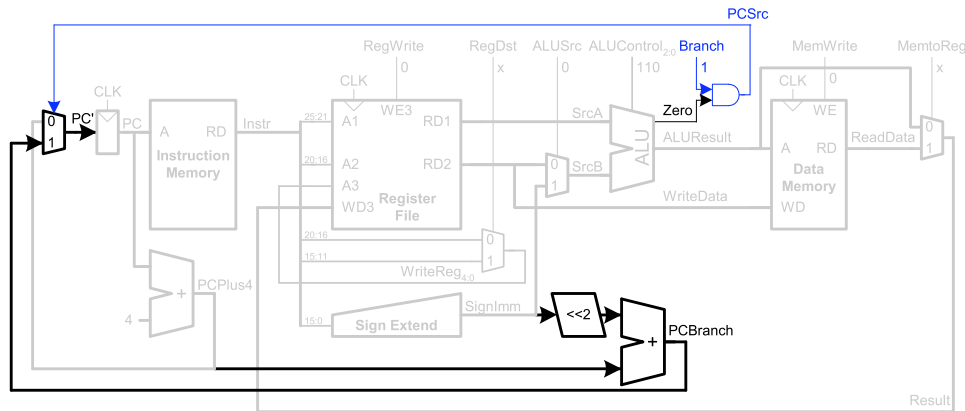
$$BTA = (\text{sign-extended immediate} \ll 2) + (PC+4)$$




Complete Single-Cycle Processor

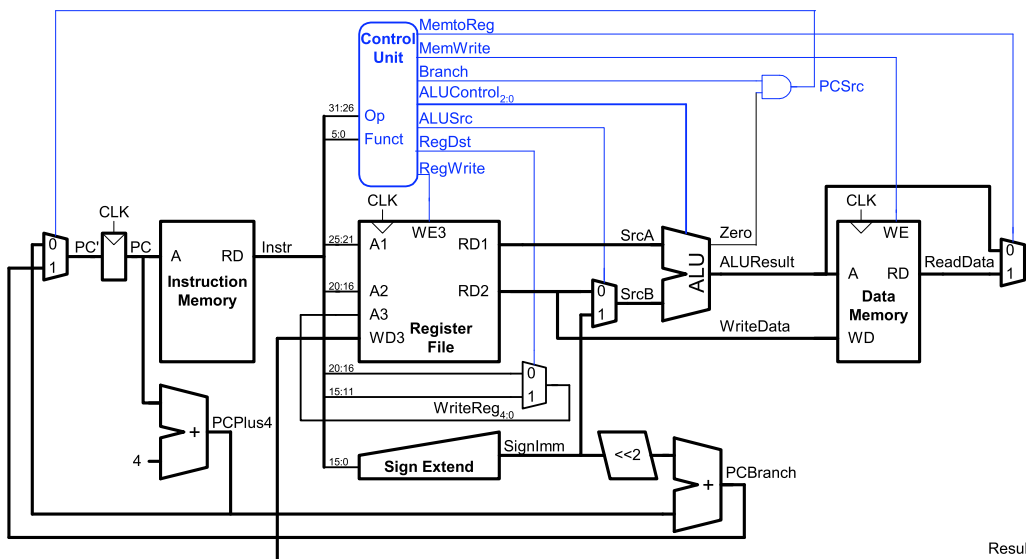

Control Unit

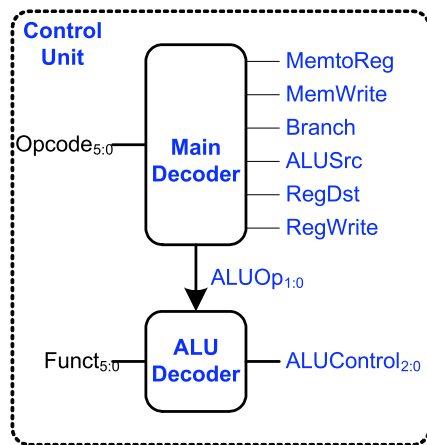

Review: ALU

 

$F_{2:0}$	Function
0	$A \& B$
1	$A B$
10	$A + B$
11	not used
100	$A \& \sim B$
101	$A \sim B$
110	$A - B$
111	SLT

Control Unit: ALU Decoder

ALUOp _{1:0}	Meaning
0	Add
1	Subtract
10	Look at Funct
11	Not Used


ALUOp _{1:0}	Funct	ALUControl _{2:0}
0	X	010 (Add)
X1	X	110 (Subtract)
1X	100000 (add)	010 (Add)
1X	100010 (sub)	110 (Subtract)
1X	100100 (and)	000 (And)
1X	100101 (or)	001 (Or)
1X	101010 (slt)	111 (SLT)

Spring 2010

Page 25

Control Unit: Main Decoder

Instruction	Op _{5:0}	RegWrite	RegDst	AluSrc	Branch	MemWrite	MemtoReg	ALUOp _{1:0}
R-type	0							
lw	1E+05							
sw	1E+05							
beq	100							

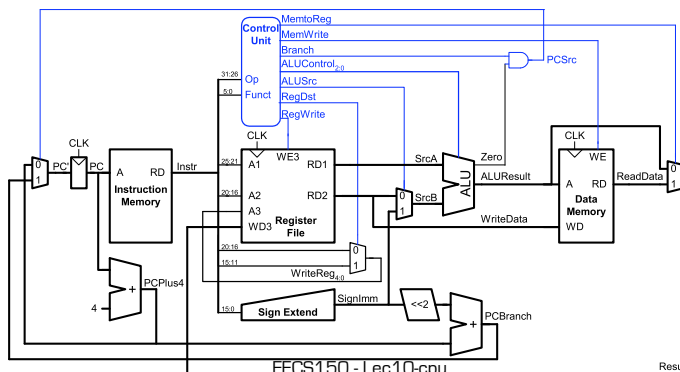


Spring 2010

Page 26


Control Unit: Main Decoder

Instruction	Op _{5:0}	RegWrite	RegDst	AluSrc	Branch	MemWrite	MemtoReg	ALUOp _{1:0}
R-type	0	1	1	0	0	0	0	10
lw	1E+05	1	0	1	0	0	0	0
sw	1E+05	0	X	1	0	1	X	0
beq	100	0	X	0	1	0	X	1

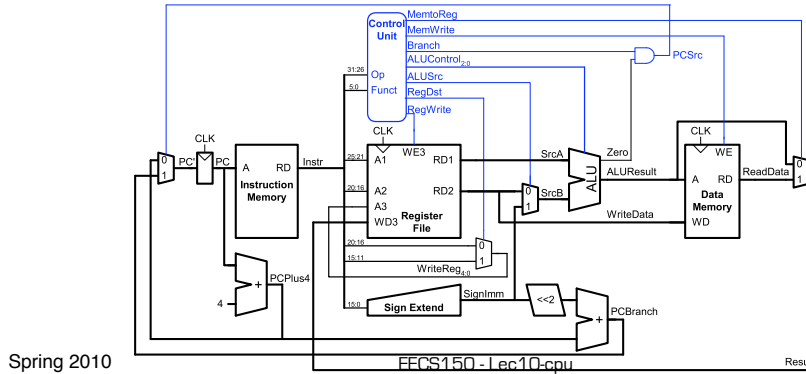

Page 27

Single-Cycle Datapath Example: or

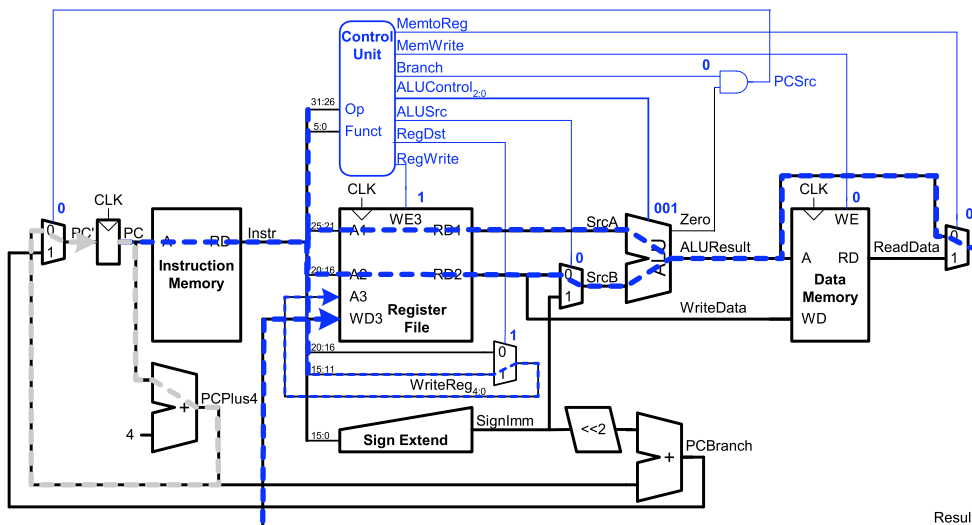


Spring 2010

EECS150 - Lec10-cpu

Page 28

Extended Functionality: addi

- No change to datapath

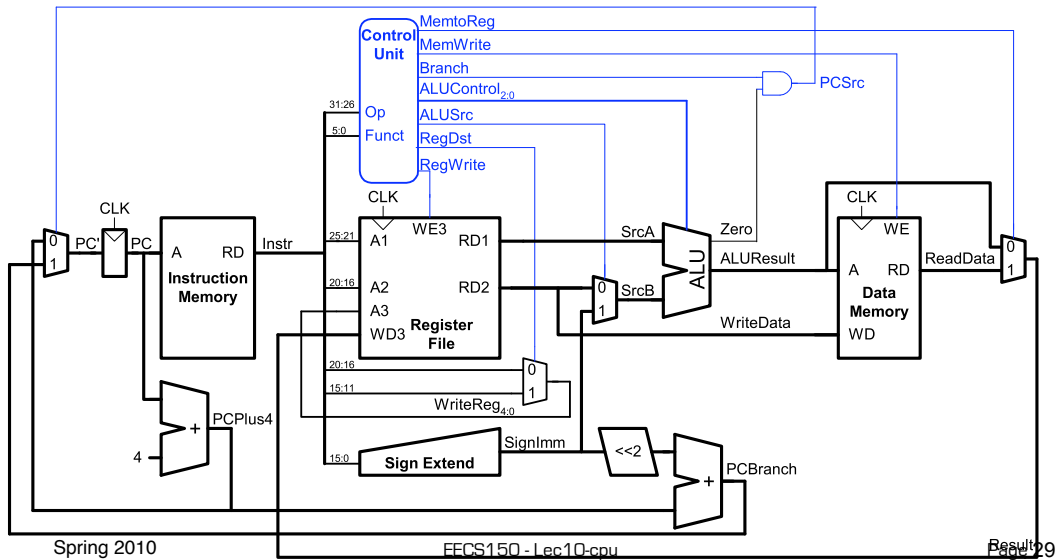

Spring 2010

EECS150 - Lec10-cpu

Page 29


Control Unit: addi

Instruction	Op _{5:0}	RegWrite	RegDst	AluSrc	Branch	MemWrite	MemtoReg	ALUOp _{1:0}
R-type	0	1	1	0	0	0	0	10
lw	1E+05	1	0	1	0	0	1	0
sw	1E+05	0	X	1	0	1	X	0
beq	100	0	X	0	1	0	X	1
addi	1000							

Control Unit: addi

Instruction	Op _{5:0}	RegWrite	RegDst	AluSrc	Branch	MemWrite	MemtoReg	ALUOp _{1:0}
R-type	0	1	1	0	0	0	0	10
lw	1E+05	1	0	1	0	0	1	0
sw	1E+05	0	X	1	0	1	X	0
beq	100	0	X	0	1	0	X	1
addi	1000	1	0	1	0	0	0	0

Extended Functionality: j

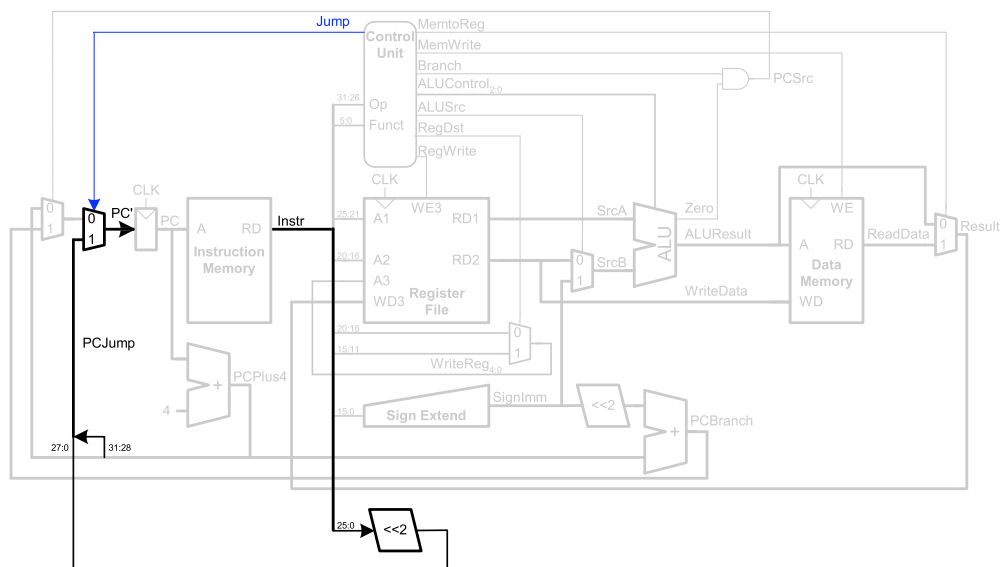

Control Unit: Main Decoder

Instruction	Op _{5:0}	RegWrite	RegDst	AluSrc	Branch	MemWrite	MemtoReg	ALUOp _{1:0}	Jump
R-type	0	1	1	0	0	0	0	10	0
lw	1E+05	1	0	1	0	0	1	0	0
sw	1E+05	0	X	1	0	1	X	0	0
beq	100	0	X	0	1	0	X	1	0
j	100								

Control Unit: Main Decoder

Instruction	Op _{5:0}	RegWrite	RegDst	AluSrc	Branch	MemWrite	MemtoReg	ALUOp _{1:0}	Jump
R-type	0	1	1	0	0	0	0	10	0
lw	1E+05	1	0	1	0	0	1	0	0
sw	1E+05	0	X	1	0	1	X	0	0
beq	100	0	X	0	1	0	X	1	0
j	100	0	X	X	X	0	X	XX	1

Review: Processor Performance


Program Execution Time

$$= (\# \text{ instructions})(\text{cycles/instruction})(\text{seconds/cycle})$$

$$= \# \text{ instructions} \times \text{CPI} \times T_C$$

Single-Cycle Performance

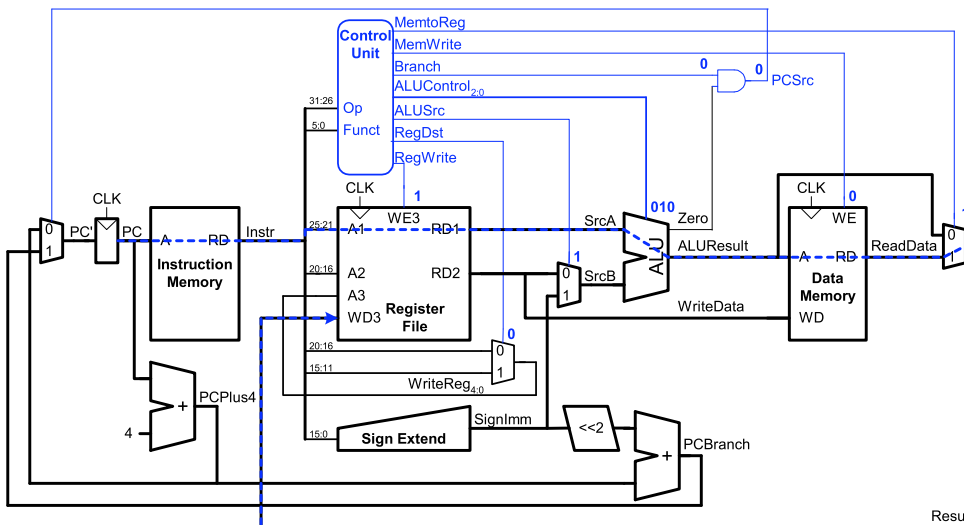- T_C is limited by the critical path (**1w**)



Single-Cycle Performance

- Single-cycle critical path:

$$T_c = t_{pcq_PC} + t_{mem} + \max(t_{RFread}, t_{sext} + t_{mux}) + t_{ALU} + t_{mem} + t_{mux} + t_{RFsetup}$$

- In most implementations, limiting paths are:

- memory, ALU, register file.

- $T_c = t_{pcq_PC} + 2t_{mem} + t_{RFread} + t_{mux} + t_{ALU} + t_{RFsetup}$

Single-Cycle Performance Example

Element	Parameter	Delay (ps)
Register clock-to-Q	t_{pcq_PC}	30
Register setup	t_{setup}	20
Multiplexer	t_{mux}	25
ALU	t_{ALU}	200
Memory read	t_{mem}	250
Register file read	t_{RFread}	150
Register file setup	$t_{RFsetup}$	20

$$T_c =$$

Single-Cycle Performance Example

Element	Parameter	Delay (ps)
Register clock-to-Q	t_{pcq_PC}	30
Register setup	t_{setup}	20
Multiplexer	t_{mux}	25
ALU	t_{ALU}	200
Memory read	t_{mem}	250
Register file read	t_{RFread}	150
Register file setup	$t_{RFsetup}$	20

$$\begin{aligned}T_c &= t_{pcq_PC} + 2t_{mem} + t_{RFread} + t_{mux} + t_{ALU} + t_{RFsetup} \\ &= [30 + 2(250) + 150 + 25 + 200 + 20] \text{ ps} \\ &= 925 \text{ ps}\end{aligned}$$

Single-Cycle Performance Example

- For a program with 100 billion instructions executing on a single-cycle MIPS processor,

Execution Time =

Single-Cycle Performance Example

- For a program with 100 billion instructions executing on a single-cycle MIPS processor,


$$\begin{aligned}\text{Execution Time} &= \# \text{ instructions} \times \text{CPI} \times T_C \\ &= (100 \times 10^9)(1)(925 \times 10^{-12} \text{ s}) \\ &= 92.5 \text{ seconds}\end{aligned}$$

Pipelined MIPS Processor


- Temporal parallelism
- Divide single-cycle processor into 5 stages:
 - Fetch
 - Decode
 - Execute
 - Memory
 - Writeback
- Add pipeline registers between stages

Single-Cycle vs. Pipelined Performance


Single-Cycle

 



Pipelined

 

Pipelining Abstraction

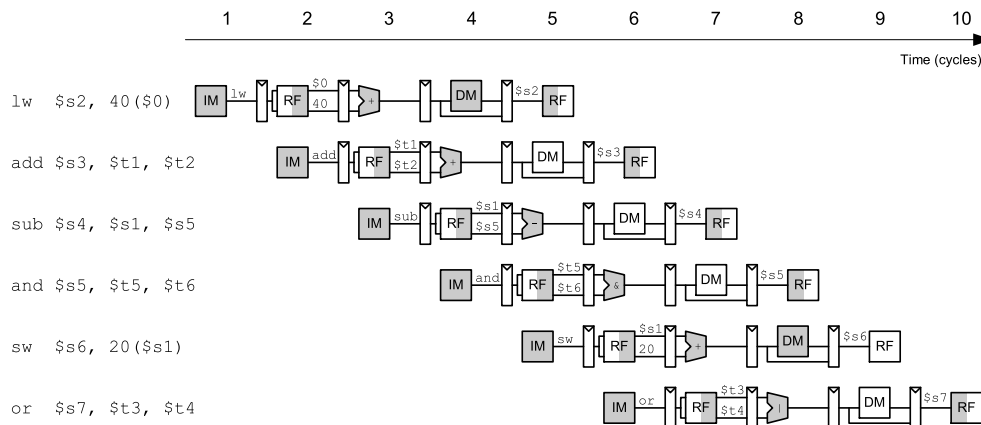

Single-Cycle and Pipelined Datapath

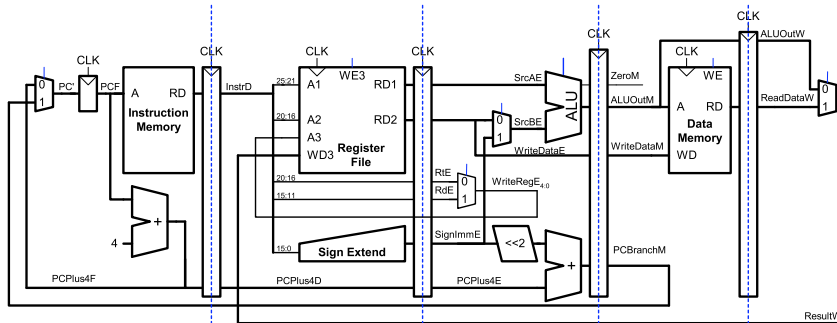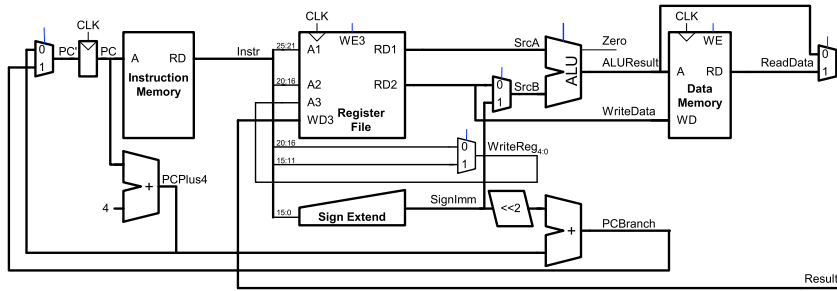


Spring 2010

EECS150 - Lec10-cpu

Page 45

Corrected Pipelined Datapath

- WriteReg must arrive at the same time as Result

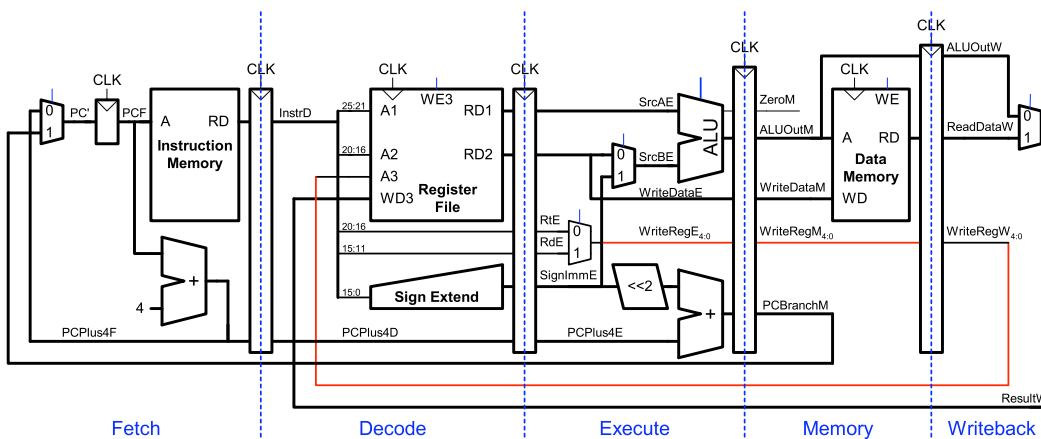


Spring 2010

EECS150 - Lec10-cpu

Page 46

Pipelined Control

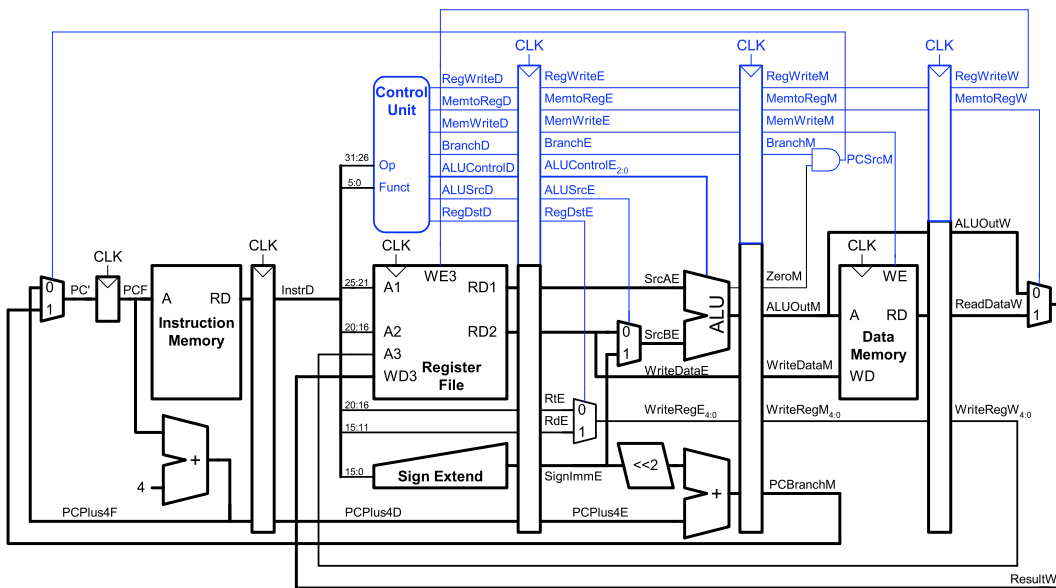

Same control unit as single-cycle processor

Control delayed to proper pipeline stage

Pipeline Hazards

- Occurs when an instruction depends on results from previous instruction that hasn't completed.
- Types of hazards:
 - **Data hazard:** register value not written back to register file yet
 - **Control hazard:** next instruction not decided yet (caused by branches)