 


EECS150 - Digital Design

Lecture 17 - Circuit Timing

March 15, 2010
John Wawrzynek

Performance, Cost, Power





- How do we measure performance?
operations/sec? cycles/sec?
- Performance is directly proportional to clock frequency.
Although it may not be the entire story:

Ex: CPU performance

$$= \# \text{ instructions} \times \text{CPI} \times \text{clock period}$$

Timing Analysis

ARM processor Microarch

 
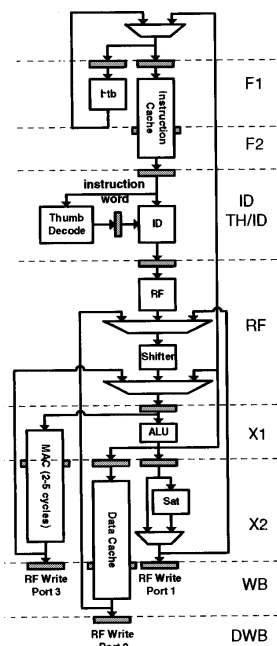


Timing Analysis

What is the smallest T that produces correct operation?

f	T
1 MHz	1 μ s
10 MHz	100 ns
100 MHz	10 ns
1 GHz	1 ns


Timing Analysis and Logic Delay

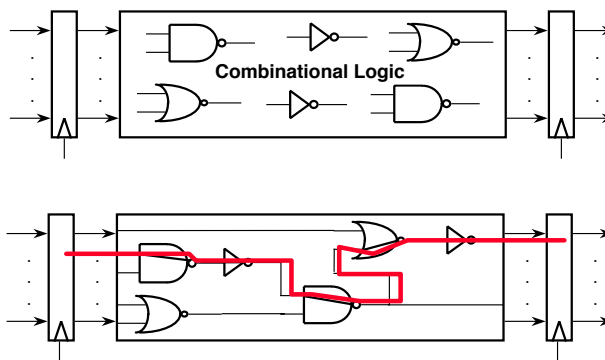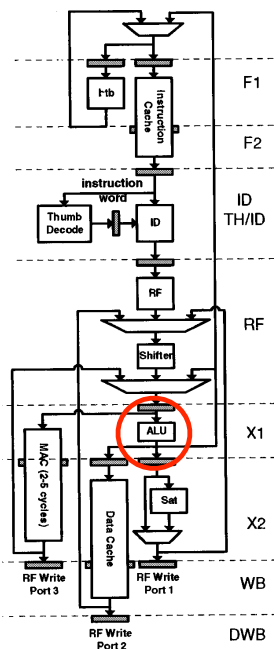

If $T >$ worst-case delay through CL, does this ensure correct operation?


Limitations on Clock Rate

1 Logic Gate Delay

 

What are typical delay values?

2 Delays in flip-flops


 


Both times contribute to limiting the clock period.


- What must happen in one clock cycle for correct operation?
 - All signals connected to FF (or memory) inputs must be ready and "setup" before rising edge of clock.
 - For now we assume perfect clock distribution (all flip-flops see the clock at the same time).

Example

Parallel to serial converter circuit

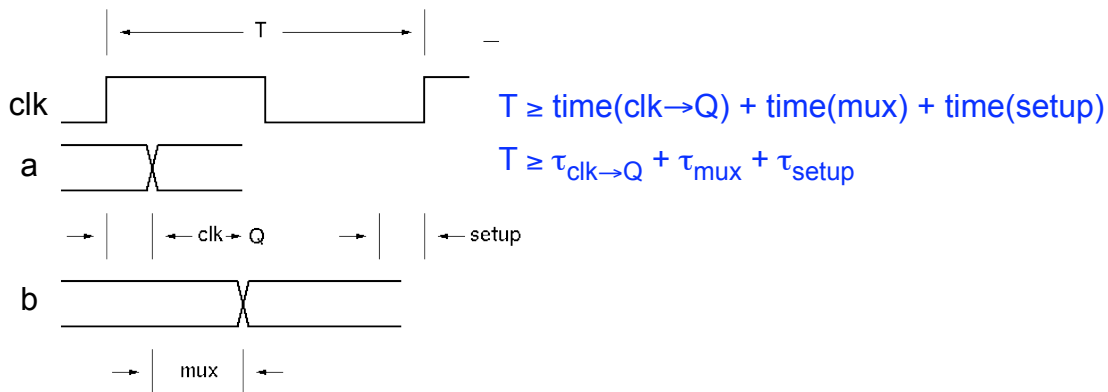 

In General ...

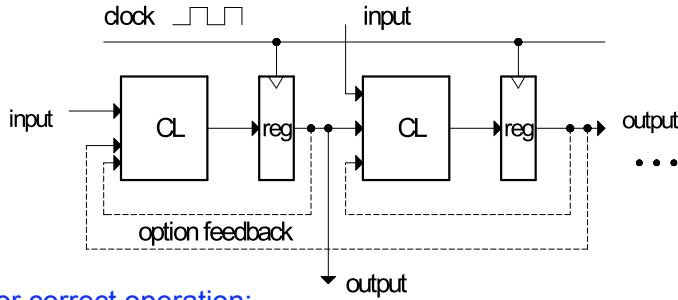

For correct operation:



$$T \geq \tau_{\text{clk} \rightarrow \text{Q}} + \tau_{\text{CL}} + \tau_{\text{setup}} \quad \text{for all paths.}$$

- How do we enumerate **all** paths?
 - Any circuit input or register output to any register input or circuit output?
- Note:
 - "setup time" for outputs is a function of what it connects to.
 - "clk-to-q" for circuit inputs depends on where it comes from.



CL Delay: Transistors as water valves

If electrons are water molecules,
and a capacitor a bucket ...

  A "on" p-FET fills
up the capacitor
with charge.




A "on" n-FET
empties the bucket.

  




Transistors as Conductors

- Improved Transistor Model: nFET

 


- We refer to transistor "strength" as the amount of current that flows for a given V_{ds} and V_{gs} .
- The strength is linearly proportional to the ratio of W/L .

pFET

   


Gate Delay is the Result of Cascading

- Cascaded gates:

 


"transfer curve" for inverter.

 


In general:
prop. delay = sum of individual prop. delays of gates in series.



Delay in Flip-flops

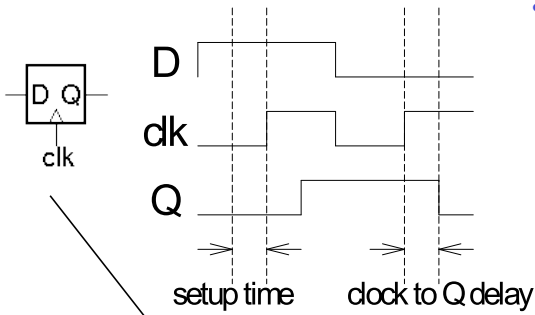

 
- Setup time results from delay through *first* latch.



  - Clock to Q delay results from delay through *second* latch.



Wire Delay

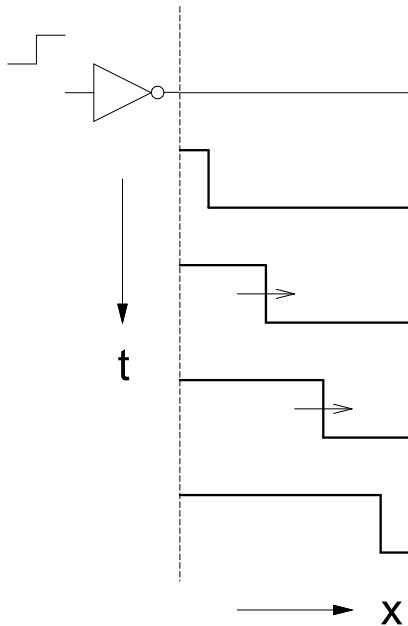


- In general, wires behave as "transmission lines":
 - signal wave-front moves close to the speed of light
 - $\sim 1\text{ft/ns}$
 - Time from source to destination is called the "transit time".
 - In ICs most wires are short, and the transit times are relatively short compared to the clock period and can be ignored.
 - Not so on PC boards.


Wire Delay

- Even in those cases where the transmission line effect is negligible:

 - Wires possess distributed resistance and capacitance



 - Time constant associated with distributed RC is proportional to the square of the length




- For **short wires** on ICs, resistance is insignificant (relative to effective R of transistors), but C is important.


- Typically around half of C of gate load is in the wires.

- For **long wires** on ICs:

 - busses, clock lines, global control signal, etc.
- Resistance is significant, therefore distributed RC effect dominates.
- signals are typically “rebuffered” to reduce delay:




Delay and “Fan-out”

 

- The delay of a gate is proportional to its output capacitance. Connecting the output of gate one increases its output capacitance. Therefore, it takes increasingly longer for the output of a gate to reach the switching threshold of the gates it drives as we add more output connections.
- Driving wires also contributes to fan-out delay.
- What can be done to remedy this problem in large fan-out situations?


“Critical” Path

 - *Critical Path*: the path in the entire design with the maximum delay.
 - This could be from state element to state element, or from input to state element, or state element to output, or from input to output (unregistered paths).
- For example, what is the critical path in this circuit?



- Why do we care about the *critical path*?

Searching for processor critical path

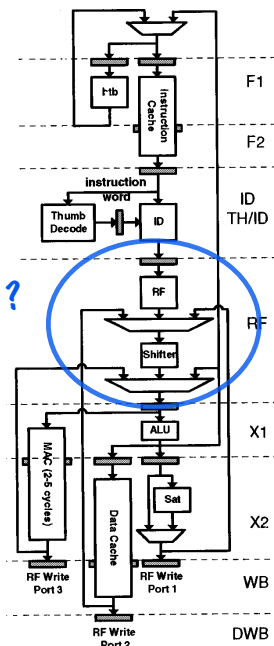

Must consider all connected register pairs, paths from input to register, register to output. Don't forget the controller.


- Design tools help in the search.
 - **Synthesis tools** report delays on paths,
 - Special **static timing analyzers** accept a design netlist and report path delays,
 - and, of course, **simulators** can be used to determine timing performance.

Tools that are expected to **do something** about the timing behavior (such as synthesizers), also include provisions for specifying input arrival times (relative to the clock), and output requirements (set-up times of next stage).

Real Stuff: Timing Analysis

The critical path

 Most paths have hundreds of picoseconds to spare.




From "The circuit and physical design of the POWER4 microprocessor", IBM J Res and Dev, 46:1, Jan 2002, J.D. Warnock et al.

Spring 2010

EECS150 - Lec17-timing

Page 17

Clock Skew

 



- Unequal delay in distribution of the clock signal to various parts of a circuit:
 - if not accounted for, can lead to erroneous behavior.
 - Comes about because:
 - clock wires have delay,
 - circuit is designed with a different number of clock buffers from the clock source to the various clock loads, or
 - buffers have unequal delay.
 - All synchronous circuits experience some clock skew:
 - more of an issue for high-performance designs operating with very little extra time per clock cycle.

Spring 2010

EECS150 - Lec17-timing



Page 18

Clock Skew (cont.)

  


- If clock period $T = T_{CL} + T_{setup} + T_{clk \rightarrow Q}$, circuit will fail.
- Therefore:
 1. Control clock skew
 - a) Careful clock distribution. Equalize path delay from clock source to all clock loads by controlling wires delay and buffer delay.
 - b) don't "gate" clocks in a non-uniform way.
 2. $T \geq T_{CL} + T_{setup} + T_{clk \rightarrow Q} + \text{worst case skew}$.
- Most modern large high-performance chips (microprocessors) control end to end clock skew to a small fraction of the clock period.

Clock Skew (cont.)

  

- **Note reversed buffer.**
- In this case, clock skew actually provides *extra time* (adds to the effective clock period).
- This effect has been used to help run circuits as higher clock rates. Risky business!

Real Stuff: Floorplanning Intel XScale 80200

 

Spring 2010

